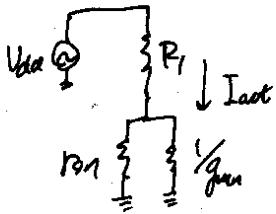


$K_n' = 200 \mu A/V^2$
 $K_p' = 190 \mu A/V^2$ $I_{out} = 1 \mu A$ $(V_{ed} = |V_{ep}| = 0.3 V)$
 $R_i = \frac{1.2 - 0.3 - \sqrt{\frac{2 \cdot I_{out}}{K_n' \cdot Y_1}}}{1 \mu A} = 0.8 M\Omega$




Power Supply Sensitivity.

$$\frac{V_{dd}}{R_i + (r_{on} \parallel \frac{1}{g_m})} \cdot \frac{1}{1} = I_{out}$$

$$r_{on} = \frac{1}{\lambda I_d} = 20 M\Omega$$

$$g_m = \sqrt{2 \cdot K_n' \cdot \frac{W}{L} \cdot I_d} = 2 \times 10^{-5} \quad \frac{1}{g_m} = 50 K$$
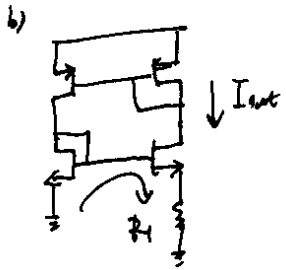
$$\therefore \frac{I_{out}}{V_{dd}} \approx \frac{1}{R_i + \frac{1}{g_m}} = \frac{1}{850 K}$$




Solve KVL loop, assume $V = 0$, no body effect

$$I_{out} \cdot R_i + V_{tn} + \sqrt{\frac{2 \cdot I_{out}}{K_n' \cdot Y_1}} = V_{tn} + \sqrt{\frac{2 \cdot I_{out}}{K_n' \cdot Y_1}}$$

$$\therefore R_i = 50 K\Omega$$

Power Supply Sensitivity.

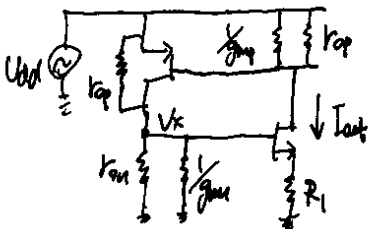

$$\frac{V_{dd} - V_x}{r_{op}} + I_{out} \cdot (r_{op} \parallel \frac{1}{g_m}) \cdot g_m = \frac{V_x}{r_{on} \parallel \frac{1}{g_m}} \quad (*)$$

$$I_{out} \sim \frac{g_m}{(+g_m R_i)} \cdot V_x \quad (\text{CS with } R_i \text{ degeneration})$$

$$r_{op} = \frac{1}{\lambda \cdot I_D} = 40 \text{ M}\Omega, \quad g_{mp} = 1.414 \times 10^{-5}, \quad \frac{1}{g_{mp}} = 70.7 \text{ K} \quad (2)$$

$$r_{on} = 20 \text{ M}\Omega$$


$$g_{mn} = 2 \times 10^{-5}$$

$$I_{out} \approx \frac{2 \cdot 10^{-5}}{1 + 2 \cdot 10^{-5} \cdot 50 \text{K}} \cdot V_x = 10^{-5} \cdot V_x$$

$$\therefore (*) \rightarrow \frac{V_{dd} - (g^s I_{out})}{40 \text{M}} + I_{out} = \frac{V_x}{g_{mn}} = 2 \cdot I_{out}$$

$$\frac{V_{dd}}{40 \text{M}} \sim I_{out}, \quad \therefore \frac{I_{out}}{V_{dd}} = \frac{1}{40 \text{M}} *$$

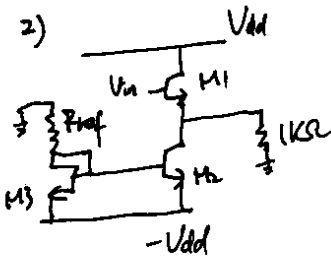Conclusion: 2nd topology has much better power supply
insensitivity than 1st topology!



a) $V_{dd} = 1.2 \text{V}, \quad L = 0.13 \mu\text{m}$

$V_{out} \text{ swing } -0.8 \text{V} \sim 0.8 \text{V}$

for highest efficiency:

$$V_{out, \text{max}} = -I_Q \cdot R_b \Rightarrow -0.8 = -I_Q \cdot 1 \text{K}$$

$$I_Q = 0.8 \text{mA}$$

Also, $V_{out, \text{min}} = -V_{dd} + V_{dsat2} = -0.8$

$$\therefore 0.4 = \sqrt{\frac{2 \cdot I_Q}{K_n' \left(\frac{W}{L}\right)_2}} \Rightarrow \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = 100 *$$

$$P_{ref} = \frac{1.2 - 0.3 - 0.4}{0.8 \text{mA}} = 625 (\Omega) *$$

3

$$V_{out,max} = V_{dd} - V_t - V_{dsat1}$$

$$\therefore V_{dsat1} = 1.2 - 0.3 - 0.8 = 0.1 = \sqrt{\frac{2 \cdot (2 I_D)}{K' (\frac{W}{L})_1}}$$

$$(\frac{W}{L})_1 = 3200 *$$

b) Output Swing: $-0.8 \sim 0.8V$

Input Swing: $(-0.8+0.3) \sim 1.2V$

∴ Input sine wave 

$$P_{L,ave} = \frac{1}{2} \frac{V_o^2}{R_L} = \frac{0.64}{2 \cdot 1K} = 0.32 \text{ mW} \quad \# \quad \begin{matrix} \text{SPICE:} \\ \underline{\underline{0.325 \text{ mW}}} \end{matrix}$$

$$P_{supply} = 3 \cdot I_D \cdot V_{dd} = 2.88 \text{ mW} \quad \# \quad \begin{matrix} \text{SPICE:} \\ \underline{\underline{2.865 \text{ mW}}} \end{matrix}$$

$$\eta = \frac{P_{L,ave}}{P_{supply}} = 11.11 \% \quad \#$$


$$\underline{\underline{\text{SPICE: } 11.36 \%}}$$

b)

④

Wave	Symbol
D0:A0:v(vo)	○—

ee140 hw5 spring 2004 for 2nd problem

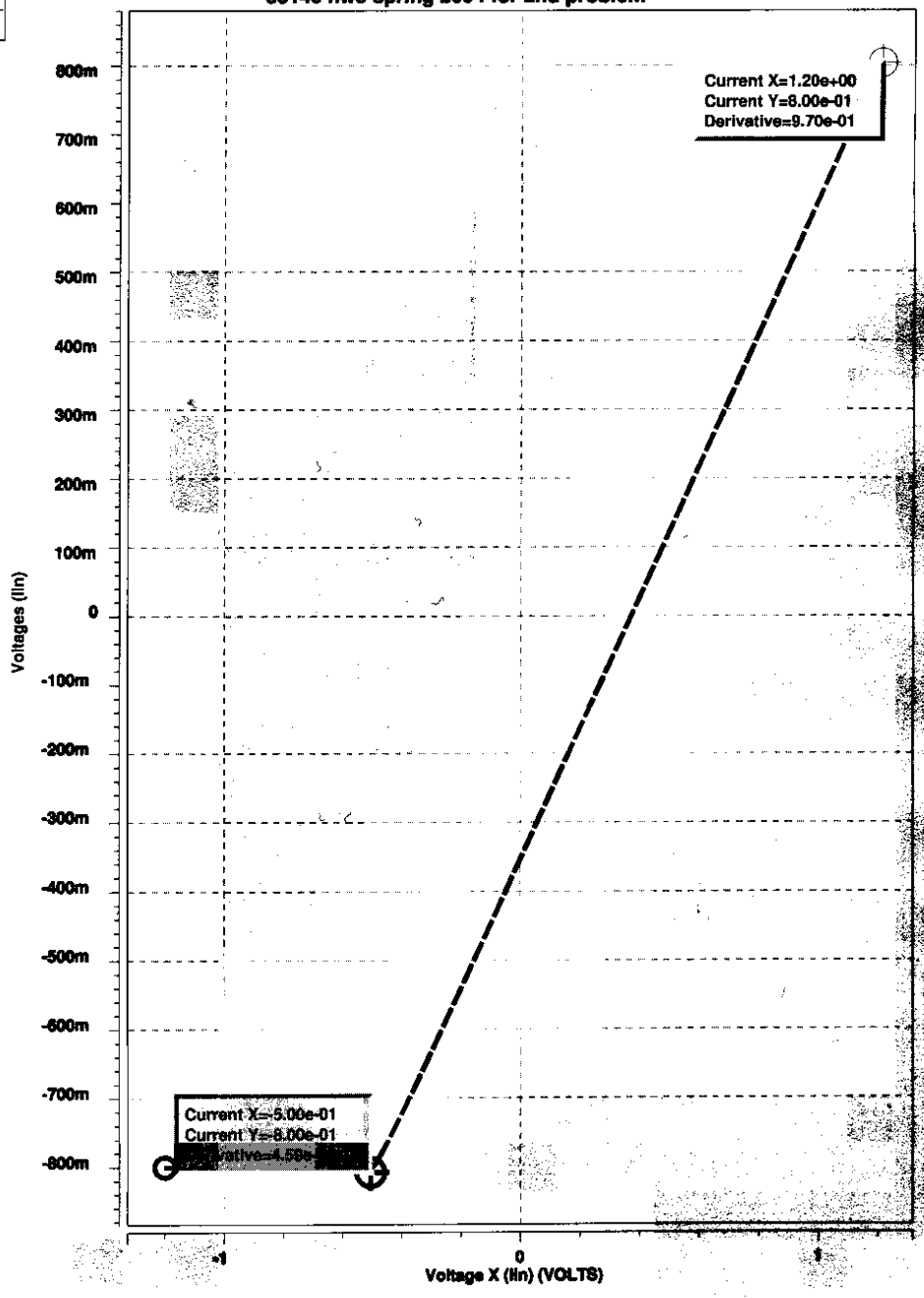

c)

5

EE140 HW5 Spring 2004 for 2nd problem

```
.model nch nmos LEVEL=1 TOX=25 VTO=0.3 KP=100.0e-6 LAMBDA=0
+GAMMA=0.01 PHI=0.6
```

```
*-----
vdd vdd 0 1.2
vss vss 0 -1.2
vin vin 0 sin(0.35 0.85 1)
```

```
Rref 0 vb 625
R1 0 vo 1k
```

```
M1 vdd vin vo vo nch L=0.13u W=416u
M2 vo vb vss vss nch L=0.13u W=13u
M3 vb vb vss vss nch L=0.13u W=13u
```

```
*-----
.dc vin -1.2 1.2 0.01
.tran 1m 1
```

```
.meas tran p_load avg p(R1) *power to the load
.meas tran p_sup avg power *power dissipated in supply
.meas tran eff param='100*p_load/p_sup' *calculate efficiency
```

```
.option nomod post
.op
.end
```

```
***** transient analysis      tnom= 25.000 temp= 25.000
*****
p_load= 3.2539E-04 from= 0.0000E+00 to= 1.0000E+00
p_sup= 2.8648E-03 from= 0.0000E+00 to= 1.0000E+00
eff= 1.1358E+01
```