

**UNIVERSITY OF CALIFORNIA AT BERKELEY**  
**College of Engineering**  
**Department of Electrical Engineering and Computer Science**

**R.W. Brodersen**  
**Jianhui Zhang**

**Homework #6**  
**Due 10/08/03**

**EECS 140**  
**Fall 2003**

**.model nmos**

+ **nmos level=1 tox=2.6n vt0=0.3 gamma=0.2 phi=0.6 u0=250 ld=0.025u**  
+ **capop=0 acm=3 ldif=0 hdif=0.2u cj=8e-4 cjsw=8e-12 cjgate=8e-11**  
+ **lambda=0.2**

**.model pmos**

+ **pmos level=1 tox=2.6n vt0=-0.3 gamma=0.2 phi=0.6 u0=100 ld=0.025u**  
+ **capop=0 acm=3 ldif=0 hdif=0.2u cj=8e-4 cjsw=8e-12 cjgate=8e-11**  
+ **lambda=0.15**

**When using the above models, remember to use  $W/L_{eff}$  in your calculations, where  $L_{eff}=L-2*L_d$  and  $L_d=0.025\mu m$ . You can calculate  $k'$  directly from the SPICE model parameters  $u_0$  and  $tox$ .**

1. A circuit as shown in Fig.1 has  $V_{CC}=15V$ ,  $R = 5K\Omega$ ,  $V_{CE(sat)} = 0.2V$ , and  $V_{BE}=0.7V$ .
  - (a) Sketch load lines in the  $I_{c1}$ -  $V_{CE1}$  plane for  $R_L = 2K\Omega$  and  $R_L = 10K\Omega$ .
  - (b) Calculate the maximum average sinusoidal output power that can be delivered to  $R_L$  ( both values ) before clipping occurs in (a) above. Sketch corresponding waveforms for  $I_{c1}$ ,  $V_{ce1}$ , and  $P_{cl}$ .
  - (c) Calculate the circuit efficiency for each value of  $R_L$  in (b). (Neglect power dissipated in  $Q_3$  and  $R$ )
  - (d) Select  $R_L$  for maximum efficiency in this circuit and calculate the corresponding average output power with sinusoidal signals.

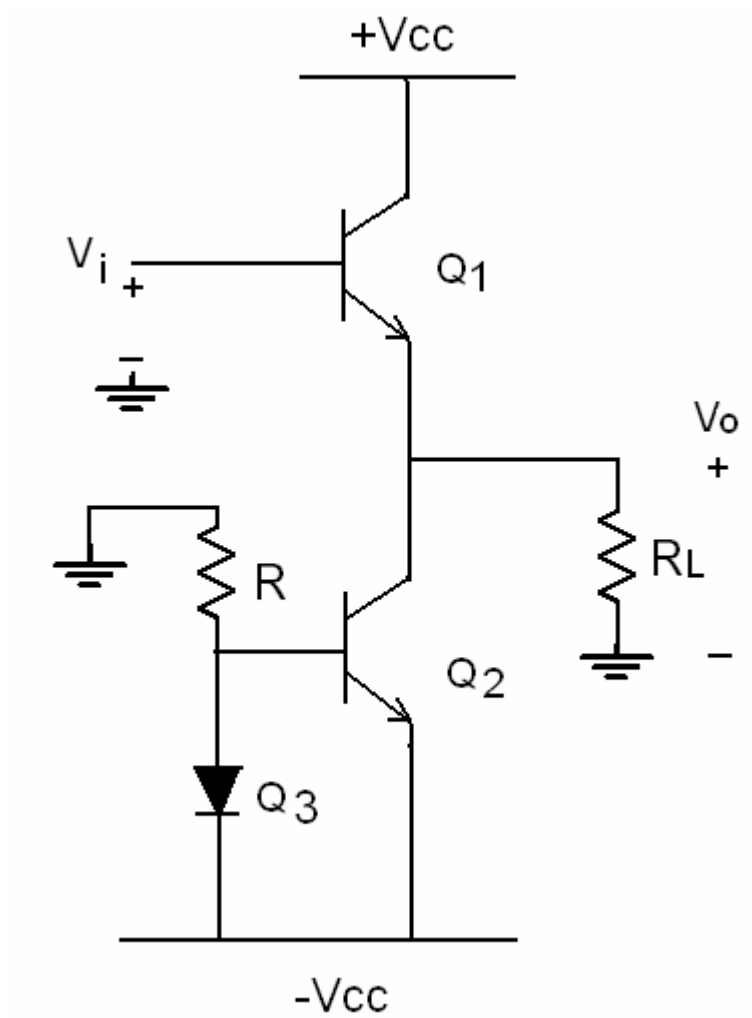


Fig. 1

- Design a CMOS output stage based on the circuit of Fig.2 to deliver  $\pm 0.6V$  before clipping at  $V_o$  with  $R_L = 1K\Omega$  and  $V_{DD} = 1.2V$ . Use  $I_B = 10\mu A$  and  $100\mu A$  idling current in  $M_{1a}$  and  $M_{1b}$ . Set  $(W/L)_{4a} = (W/L)_{4b} = 0.5\mu/0.13\mu$ ,  $(W/L)_3 = 0.2\mu/0.13\mu$ . Total chip area is to be minimized. Specify  $W/L$  for  $M_{1a}$ ,  $M_{1b}$ ,  $M_{2a}$ ,  $M_{2b}$ . Use SPICE to verify your design by plotting the  $V_o$  vs  $V_i$  characteristic. Minimum  $L$  is  $0.13\mu$ .

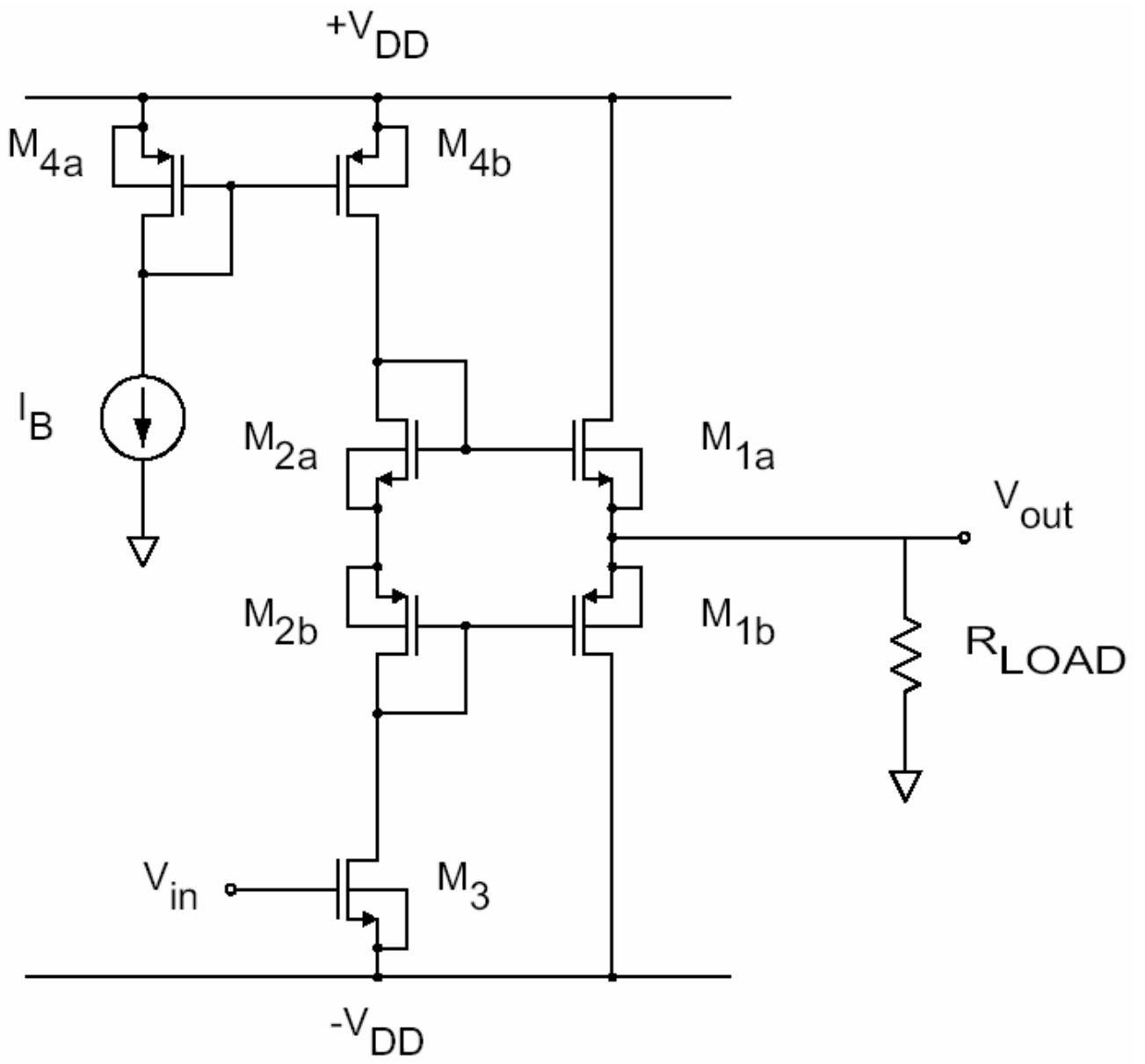


Fig. 2