

HW7 solution

Mike Chen

1.

$$k_n' = \mu_n C_{ox} = \frac{q}{2.6n} \cdot 250' = 332 \mu A/V^2 \quad \lambda_n = 0.2$$

$$\lambda_p = 0.15$$

$$k_p' = \mu_p C_{ox} = 132.8 \mu A/V^2$$

$$g_{m2} \cong \sqrt{2 \cdot \left( \frac{19}{0.13-2.6} \right) \cdot 132.8 \mu \cdot 19 \mu} = 576 \mu S$$

$$g_{m6} = \sqrt{2 \cdot \left( \frac{19}{0.13-2.6} \right) \cdot 332 \mu \cdot 29 \mu} = 1.29 \text{ mS}$$

$$r_{o1,2} = \frac{1}{0.15 \cdot 19 \mu} = 666.7 \text{ k}\Omega$$

$$r_{o3,4} = \frac{1}{0.2 \cdot 10 \mu} = 500 \text{ k}\Omega$$

$$r_{o6} = \frac{1}{0.2 \cdot 29 \mu} = 250 \text{ k}\Omega$$

$$r_{o7} = \frac{1}{0.15 \cdot 29 \mu} = 333.3 \text{ k}\Omega$$

$$\therefore A_{vo} = -g_{m2} \cdot (r_{o2} || r_{o4}) \cdot g_{m6} \cdot (r_{o6} || r_{o7}) \cong -30k$$

Spice  $\rightarrow 9k$

$\therefore$  current flow MI. Hz,  
not exactly  $10 \mu A$ .

Unity Gain BW:

$$v_o = v_i \cdot g_{m2} \cdot \frac{1}{sC_o}$$


$$\therefore \frac{v_o}{v_i} = 1 \Rightarrow \omega_u = \frac{g_{m2}}{C_o}$$

$$f_u = 18.33 \text{ MHz}$$

Spice: 18.9 MHz

slew rate:
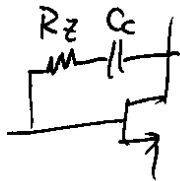
$$\frac{dV_o}{dt} = \frac{I_{ss}}{C_c} = \frac{20 \mu A}{5 pF} = 4 \frac{V}{\mu s}$$



$$z = \frac{-1}{C_c \left( R_z - \frac{1}{g_{m6}} \right)}$$

$\therefore$  should make  $R_z = \frac{1}{g_{m6}} = 775 \Omega$ .

$$\frac{1}{R_z} = \frac{\partial I_D}{\partial V_{GS}} = K_n' \frac{W}{L} (V_{GS} - V_t - V_{DS}) = \frac{1}{775 \Omega}$$

$$\left( \frac{W}{L} \right)_{eff} = 6.8$$

$$\text{Spice } \frac{W}{L}_{eff} = 7.37$$

zero will be cancel, (push to  $\infty$ )

From Spice zero  $44 \text{ MHz} \rightarrow 1.47 \text{ GHz}$ .

EE140 HW7 Spring 2004 for 1st problem

```
.model nch nmos LEVEL=1 tox=2.6n vt0=0.3 gamma=0.2 phi=0.6 u0=250 ld=0.025u  
+ capop=0 acm=3 ldif=0 hdif=0.2u cj=8e-4 cjsw=8e-12 cjgate=8e-11  
+ lambda=0.2
```

```
.model pch pmos LEVEL=1 tox=2.6n vt0=-0.3 gamma=0.2 phi=0.6 u0=100 ld=0.025u  
+ capop=0 acm=3 ldif=0 hdif=0.2u cj=8e-4 cjsw=8e-12 cjgate=8e-11  
+ lambda=0.15
```

```
*-----  
vdd vdd 0 1.2
```

```
vic vic 0 dc=0.6  
vid vid 0 dc=0 ac=1  
e1 vi1 vic vid 0 0.5  
e2 vi2 vic vid 0 -0.5
```

```
m1 g3 vi1 s1 vdd pch w=10u l=0.13u  
m2 g6 vi2 s1 vdd pch w=10u l=0.13u  
m3 g3 g3 0 0 nch w=5u l=0.13u  
m4 g6 g3 0 0 nch w=5u l=0.13u  
m5 s1 g5 vdd vdd pch w=10u l=0.13u  
m6 vout g6 0 0 nch w=10u l=0.13u  
m7 vout g5 vdd vdd pch w=10u l=0.13u  
m8 g5 g5 vdd vdd pch w=10u l=0.13u
```

```
m9 d9 vdd g6 g6 nch w=0.59u l=0.13u  
c1 d9 vout 5p
```

```
iss g5 0 20u
```

```
*-----
```

```
.ac dec 100 1 1T  
.pz v(vout) vid
```

```
.option nomod post
```

```
.op
```

```
.probe ac vout1=vdb(vout) vp1=vp(vout)  
.tf v(vout) vid
```

```
.end
```

=====Without M9 compensation=====


```
poles (rad/sec)      poles ( hertz)
*****
real      imag      real      imag
-2.9881k  0.      -475.5753  0.
-19.0211g 0.      -3.0273g  0.
-22.9217g 0.      -3.6481g  0.
-52.0193g 10.5942g -8.2791g  1.6861g
-52.0193g -10.5942g -8.2791g -1.6861g
node=e2  real= 8.0962E-17 imaginary= 0.
**warning** underflow 1 time(s) in pole/zero analysis
zeros (rad/sec)     zeros ( hertz)
*****
real      imag      real      imag
277.4201x 0.      44.1528x 0.
-18.3979g 0.      -2.9281g  0.
-42.2575g 0.      -6.7255g  0.
-72.0742g 0.      -11.4710g 0.
180.1588g 0.      28.6732g  0.
```

=====With M9 compensation=====



```
poles (rad/sec)     poles ( hertz)
*****
real      imag      real      imag
-2.9881k  0.      -475.5699  0.
-17.4903g 0.      -2.7837g  0.
-31.8379g 0.      -5.0672g  0.
-39.5285g 0.      -6.2912g  0.
-84.5776g 19.4522g -13.4609g  3.0959g
-84.5776g -19.4522g -13.4609g -3.0959g
zeros (rad/sec)     zeros ( hertz)
*****
real      imag      real      imag
9.2409g   0.      1.4707g 0.
-11.7546g 0.      -1.8708g  0.
-18.4015g 0.      -2.9287g  0.
-42.2543g 0.      -6.7250g  0.
-72.0751g 0.      -11.4711g 0.
180.1588g 0.      28.6732g  0.
```

Wave	Symbol
D0:A0:vdb(vout1)	X

ee140 hw7 spring 2004 for 1st problem

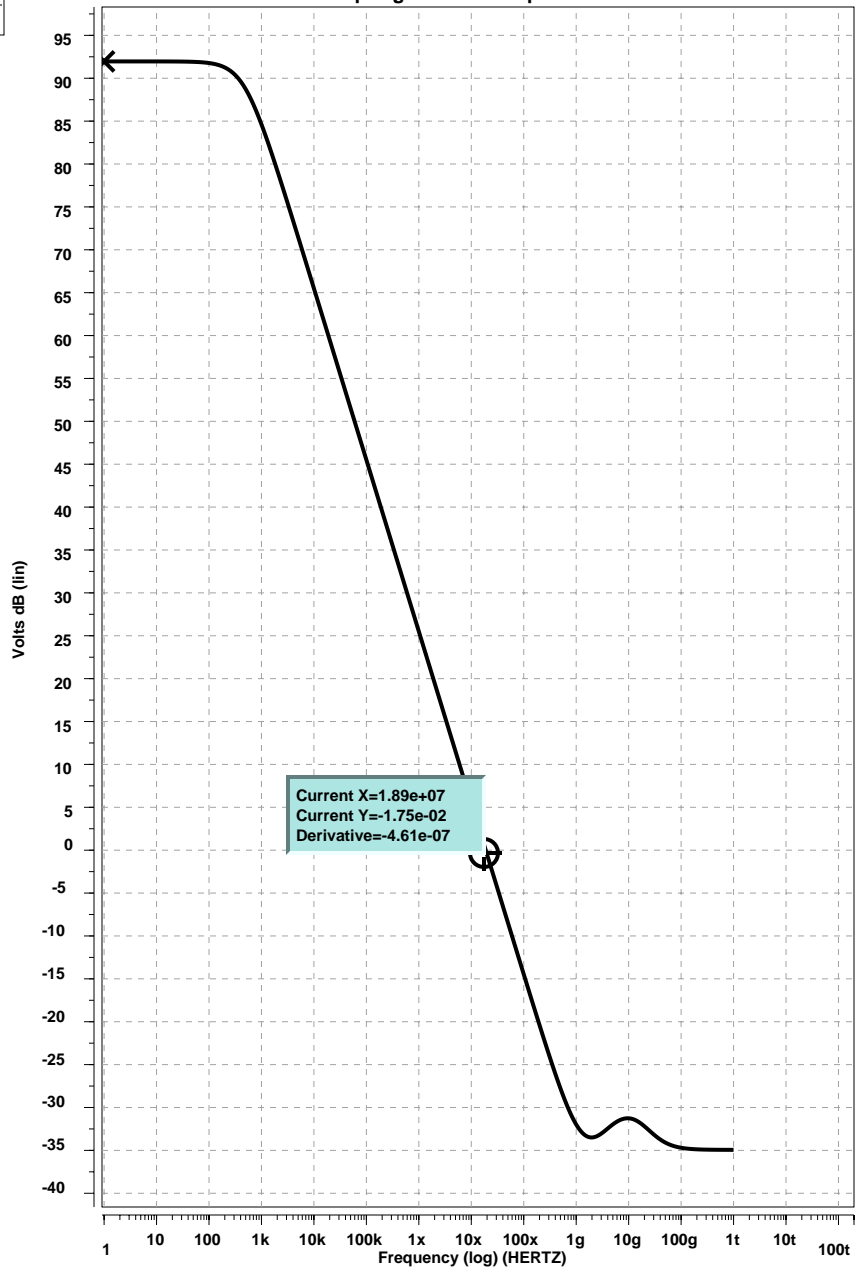

2. a)

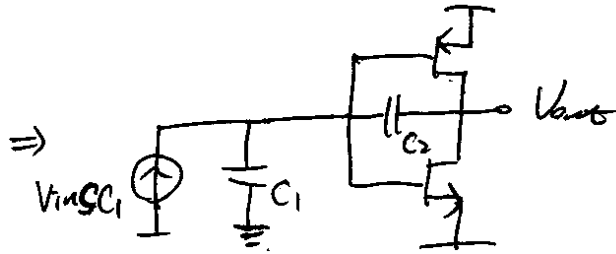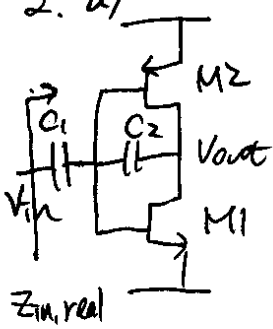


sense voltage, feedback current.

⇒ Shunt-Shunt FB.

(Ignoring feedforward thru  $C_2$ .)
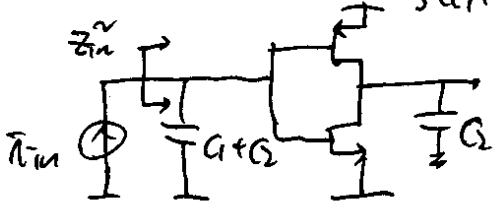
$$\therefore A_R(s) = \frac{1}{s(C_1 + C_2)} \cdot (g_{m1} + g_{m2}) \cdot (r_{o1} \parallel r_{o2} \parallel \frac{1}{sC_2})$$



$$f = sC_2$$

$$T(s) = A_R(s) \cdot f = \frac{C_2}{C_1 + C_2} (g_{m1} + g_{m2}) \cdot (r_{o1} \parallel r_{o2} \parallel \frac{1}{sC_2})$$


$$A = \frac{A_R}{1 + fA_R} \approx \frac{1}{sC_2} = \frac{V_{out}}{\tilde{i}_{in}} \Rightarrow \frac{V_{out}}{V_{in}} = \frac{C_1}{C_2}$$

$$\tilde{z}_{in} = \frac{1}{s(C_1 + C_2)} \cdot \frac{1}{1 + T}$$

$$z_{in,real} = \frac{1}{sC_1} + (\tilde{z}_{in}^{-1} - sC_1)^{-1}$$

$$z_{out} = (r_{o1} \parallel r_{o2} \parallel \frac{1}{sC_2}) \cdot \frac{1}{1 + T} \approx \frac{C_1 + C_2}{C_2} \cdot \frac{1}{g_{m1} + g_{m2}}$$

b)

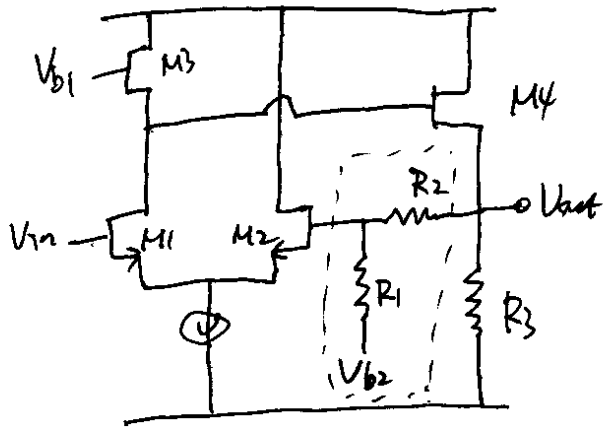


sense voltage. fB voltage  
 → series - shunt.

$$a = \frac{g_{m1}}{1 + g_{m1} \frac{1}{g_{m2}}} \cdot (r_{o3} \parallel r_{o1} (1 + \frac{g_{m1}}{g_{m2}})) \cdot g_{m4} \cdot (R_3 \parallel (R_1 + R_2))$$

1st stage

2nd stage

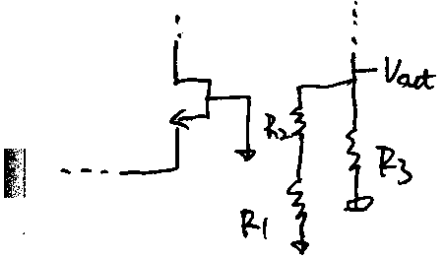

$$f = \frac{R_1}{R_1 + R_2}$$


$$T = a \cdot f$$

$$Z_{in} = \infty$$

$$Z_{out} = \frac{r_{o4} \parallel R_3 \parallel (R_1 + R_2)}{1 + T}$$

$$A = \frac{a}{1 + af} \sim \frac{1}{f} = \frac{R_1 + R_2}{R_1}$$

3.

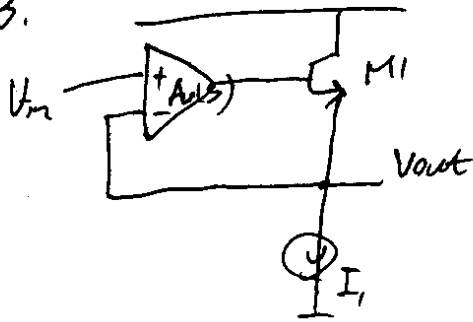


sense voltage, FB. voltage

⇒ series-shunt.

$$A_v(s) = \frac{K}{1 + \frac{s}{\omega_p}}$$

Open loop.

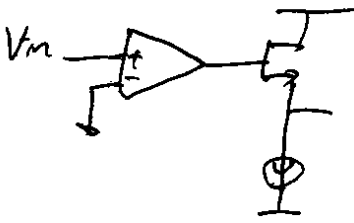

$$Q(s) = A_v(s) \cdot \frac{g_m}{g_m + g_{ob}}$$

$$f = 1.$$

$$T(s) = \frac{K}{1 + \frac{s}{\omega_p}} \cdot \frac{g_m}{g_m + g_{ob}} \approx \frac{K}{1 + \frac{s}{\omega_p}}$$

for  $g_{ob} \ll g_m$ .

$$Z_{in} = \infty.$$

$$Z_{out} = \frac{1}{g_m + g_{ob}} \cdot \frac{1}{1 + T} \approx \frac{1}{g_m + g_{ob}} \cdot \frac{1}{1 + \frac{K}{1 + \frac{s}{\omega_p}}}$$

original O.D. output impedance.

reduction due to feedback.

Lost the reduction of impedance when.

$$\frac{K}{1 + \frac{s}{\omega_p}} \ll 1.$$

dominate

$$\frac{s}{\omega_p} \gg 1.$$

$$\frac{K}{s\omega_p} \ll 1. \Rightarrow \omega \gg K \cdot \omega_p = \text{Gain BW product of } A_v(s)$$

∴ Once freq. goes beyond GBW of  $A_v(s)$ , output impedance goes back to  $\frac{1}{g_m + g_{ob}}$ .