

- From inspection of the circuit :

$$\overline{I_{DS1}} = \overline{I_{DS2}} = \overline{I_{DS}} \quad (1)$$

$$V_{DS} = V_{DS1} + V_{DS2} \quad (2)$$

$$V_{GS} = V_{GS1} \quad (3)$$

$$= V_{GS2} + V_{DS2} \quad (4)$$

- For $V_{GS} < V_T$: $\overline{I_{DS1}} = 0 \Rightarrow \overline{I_{DS}} = 0$

Assume now that $V_{GS} > V_T \Rightarrow \overline{I_{DS1}} = \overline{I_{DS2}} = \overline{I_{DS}} > 0$

From (3) and (4) : $V_{GS2} - V_T = V_{GS1} - V_T - V_{DS1}$
 $= V_{DSat1} - V_{DS1}$

Since $\overline{I_{DS2}} > 0$: $V_{GS2} - V_T > 0$

$$\Rightarrow V_{DS1} < V_{DSat1}$$

M₁ is in the linear region

Assume M_2 is in the linear region also:

$$\begin{aligned}\bar{I}_{DS_1} &= k' \frac{W}{L} \left((V_{GS} - V_T) V_{DS_1} - \frac{V_{DS_1}^2}{2} \right) \\ &= k' \frac{W}{L} \left((V_{GS} - V_T) V_{DS_1} - \frac{V_{DS_1}^2}{2} \right)\end{aligned}$$

$$\begin{aligned}\bar{I}_{DS_2} &= k' \frac{W}{L} \left((V_{GS_2} - V_T) V_{DS_2} - \frac{V_{DS_2}^2}{2} \right) \\ &= k' \frac{W}{L} \left((V_{GS} - V_T) V_{DS_2} - \sqrt{V_{DS_1}} V_{DS_2} - \frac{V_{DS_2}^2}{2} \right) \\ &\quad \text{(using (4))}\end{aligned}$$

$$\begin{aligned}\bar{I}_{DS} &= \frac{\bar{I}_{DS_1} + \bar{I}_{DS_2}}{2} = \frac{\bar{I}_{DS_1} + \bar{I}_{DS_2}}{2} \\ &= k' \frac{W}{2L} \left((V_{GS} - V_T) (V_{DS_1} + V_{DS_2}) - \frac{V_{DS_1}^2 + 2V_{DS_1} V_{DS_2} + V_{DS_2}^2}{2} \right)\end{aligned}$$

$$\bar{I}_{DS} = \frac{k'}{2L} \frac{W}{L} \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

The structure is equivalent
to a single transistor
with ratio $w/2L$

• Assume M_2 is in the saturation region:

$$\text{From (2) and (4): } V_{GS_2} - V_{DS_2} = V_{GS} - V_{DS}$$

$$\Leftrightarrow V_{DSat_2} - V_{DS_2} = V_{DSat} - V_{DS}$$

$$\text{where } V_{DSat} = V_{GS} - V_T$$

$$\rightarrow V_{DS_2} > V_{DSat_2} \Leftrightarrow V_{DS} > V_{DSat}$$

$$\overline{I_{DS_1}} = k' \frac{W}{L} \left((V_{GS} - V_T) V_{DS_1} - \frac{V_{DS_1}^2}{2} \right)$$

$$\overline{I_{DS_2}} = \frac{k'}{2} \frac{W}{L} (V_{GS_2} - V_T)^2$$


$$= k' \frac{W}{L} \frac{(V_{GS} - V_T - V_{DS_1})^2}{2}$$

$$= k' \frac{W}{L} \left[(V_{GS} - V_T) \frac{(V_{GS} - V_T - V_{DS_1})}{2} + \frac{V_{DS_1}^2}{2} \right]$$

$$\overline{I_{DS}} = \frac{\overline{I_{DS}} + \overline{I_{DS}}}{2} = \frac{\overline{I_{DS_1}} + \overline{I_{DS_2}}}{2}$$

$$\boxed{\overline{I_{DS}} = \frac{k'}{2} \frac{W}{2L} (V_{GS} - V_T)^2}$$

2)

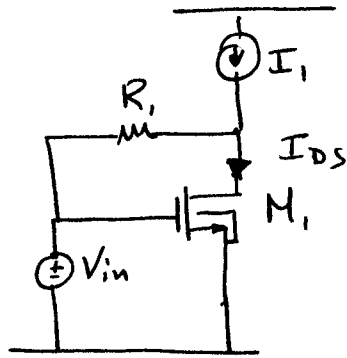

For $V_{in} \leq V_{T0} = 0.5V$,
 M_1 is in cut-off
 and $I_{D_s} = 0$

$$V_D = V_G + R_1 (I_1 - I_{D_s})$$

$$V_{D_s} = V_{D_{sat}} + V_T + R_1 (I_1 - I_{D_s})$$

$\Rightarrow M_1$ is in saturation

$$\text{when } V_T + R_1 (I_1 - I_{D_s}) \geq 0$$

$$\Leftrightarrow V_{G_s} - V_T \leq \sqrt{\frac{R_1 I_1 + V_T}{R_1 \frac{\mu'}{2} \frac{W}{L}}} = 1.06V$$

For $0.5V \leq V_{in} \leq 1.56V$,
 M_1 is in saturation

$$I_{D_s} = \frac{4\mu A}{V^2} (V_{G_s} - V_T)^2$$

$$I_{D_s} \Big|_{V_{G_s} = 1.56V} = 4.5\mu A \quad \left(= \frac{R_1 I_1 + V_T}{R_1} \right)$$


For $V_{in} \geq 1.56V$, M_1 is in the linear region

The exact behavior of $I_{DS}(V_{in})$ in the linear region is hard to calculate, but we can easily calculate the asymptote for $V_{in} \gg 1.56V$

For $V_{in} \gg 1.56V$, $V_{DS} \ll V_{in}$

$$\Rightarrow I_{DS} \approx I_1 + \frac{V_{in}}{R_1}$$

Sketch of $I_{DS}(V_{in})$

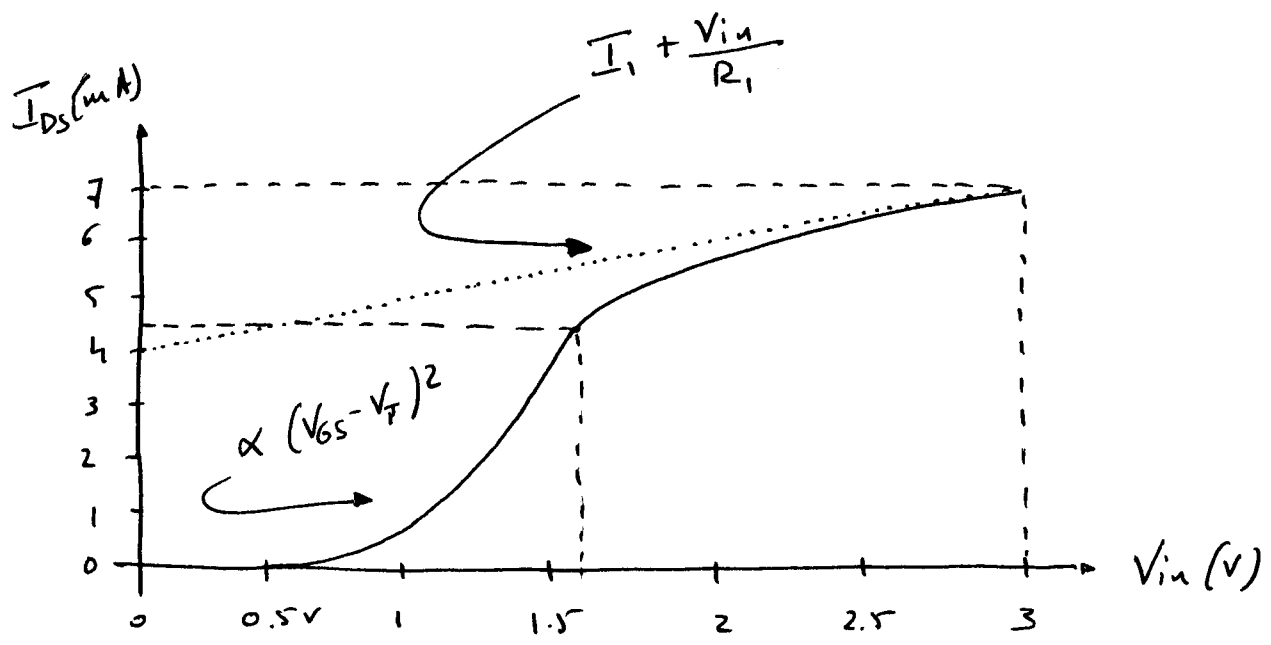

3) α

$$V_{OUT} = 1.5V \Rightarrow V_{R_1} = 1.5V$$

$$\Rightarrow \bar{I}_{R_1} = V_{R_1}/R_1 = 1.5mA$$

$$= \bar{I}_{DS1} = \frac{k'}{2} \frac{W}{L} (V_{GS1} - V_T)^2 (1 + \lambda V_{DS1})$$

(Assuming M_1 is in saturation)

$$\Rightarrow V_{GS1} - V_T = \sqrt{\frac{\bar{I}_{DS1}}{\frac{k'}{2} \frac{W}{L} (1 + \lambda V_{DS1})}}$$

$$= \sqrt{\frac{1.5mA}{\frac{2mA}{V^2} (1 + 0.375)}}$$

$$= 0.74V$$

$$V_{IN} = V_{GS} + V_T$$

$$V_{IN} = 1.24V$$

$$\bar{I}_{DS} = 1.5mA$$

$$V_T = 0.5V$$

$$V_{DSsat} = 0.74V$$

$$g_m = 4.06mS$$

$$g_{mb} = 1.3mS$$

$$r_o \approx 2.7k\Omega$$

$$= 2\bar{I}_{DS}/V_{GS} - V_T$$

$$= \alpha g_m \quad \alpha = \sqrt{1/2V_{GS} - V_T} = 0.32$$

$$r_o \approx 1/\lambda \bar{I}_{DS}$$

b

$$V_{out} = 1.5V \rightarrow V_{R_1} = 1.5V$$

$$\Rightarrow \bar{I}_{R_1} = 1.5 \mu A$$

$$= \bar{I}_{D_{S_1}} = \frac{\mu'}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

First, we need to calculate V_{SB} :

$$V_{SB} = R_2 \bar{I}_{D_{S_1}} = 0.45V$$

$$\Rightarrow V_T = V_{T0} + \gamma \left(\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right) \\ = 0.625V$$

$$V_{DS} = V_{out} - V_{SB} = 1.05V$$

$$\rightarrow V_{GS} - V_T = \sqrt{\frac{\bar{I}_{D_{S_1}}}{\frac{\mu'}{2} \frac{W}{L} (1 + \lambda V_{DS})}} = 0.77V$$

$$V_{in} = (V_{GS} - V_T) + V_T + V_{SB}$$

$$V_{in} = 1.85V$$

$$\bar{I}_{D_{S_1}} = 1.5 \mu A \\ V_T = 0.625V \\ V_{DSat} = 0.77V$$

$$g_m = 3.89 \text{ mS} \\ g_{mb} = 0.95 \text{ mS} \\ r_o \approx 2.7 \text{ k}\Omega$$

$$= 2 \bar{I}_{D_{S_1}} / (V_{GS} - V_T) \\ = x g_m \quad x = \sqrt{2\phi_f} \\ r_o \approx 1/\lambda \bar{I}_{D_{S_1}}$$