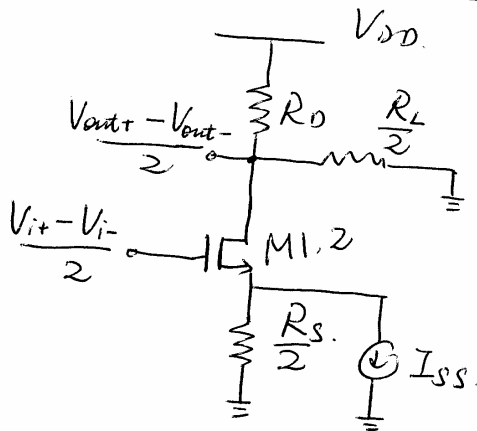


EE140 HW#3 Solution

①

1. Differential half circuit:



It is a common source amplifier with source degeneration $R = \frac{R_S}{2}$.

$$\therefore A_{V-diff} = \frac{V_{out+} - V_{out-}}{V_{i+} - V_{i-}}$$


$$g_{m1} = g_{m2} = g_{m1,2}$$

$$\cong \frac{R_D \parallel \frac{R_L}{2}}{\frac{1}{g_{m1,2}} + \frac{R_S}{2}}$$

$$\left[\text{Assume } \left(R_D \parallel \frac{R_L}{2} \right) \ll \frac{1}{2} g_m R_S r_o \right]$$

$$= \frac{g_{m1,2} \cdot \left(R_D \parallel \frac{R_L}{2} \right)}{1 + g_{m1,2} \cdot \frac{R_S}{2}}$$

Common mode half circuit:

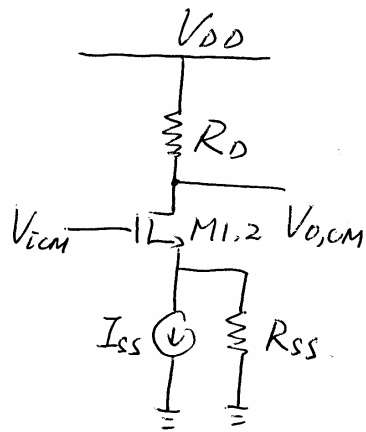

$$\therefore A_{v-cm} = \frac{V_{o,cm}}{V_{i,cm}} \quad (2)$$

$$\approx \frac{R_D}{\frac{1}{g_{m1,2}} + R_{SS}}$$

[Assume $R_D \ll g_m R_{SS} \cdot r_o$ and R_{SS} is the output resistance of the current source]

$$= \frac{g_{m1,2} R_D}{1 + g_{m1,2} \cdot R_{SS}}$$

Since in this problem, we assume the current source is ideal $R_{SS} \rightarrow \infty$. $\therefore A_{v-cm} = 0$.

$$\boxed{CMRR = \frac{A_{v-diff}}{A_{v-cm}} = \infty}$$


* If the current source is not ideal,

$$CMRR = \frac{A_{v-diff}}{A_{v-cm}} = \frac{R_D \parallel \frac{R_L}{2}}{R_D} \cdot \frac{1 + g_{m1,2} \cdot R_{SS}}{1 + g_{m1,2} \cdot \frac{R_S}{2}}$$

2.

(3)

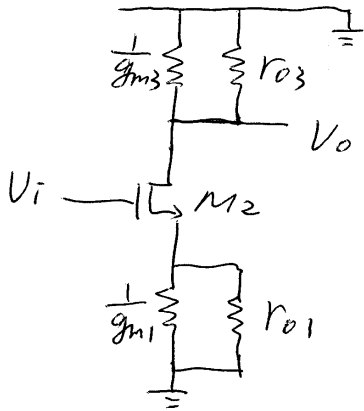(a) The small-signal circuit is shown below: M2 is CS w/ degeneration:




Assume $\frac{1}{g_m} \ll r_o$, then

$$\frac{1}{g_m} \parallel r_o \cong \frac{1}{g_m}$$

$$A_v \cong \frac{-\frac{1}{g_{m3}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$= \boxed{\frac{-g_{m1} \parallel g_{m2}}{g_{m3}}}$$

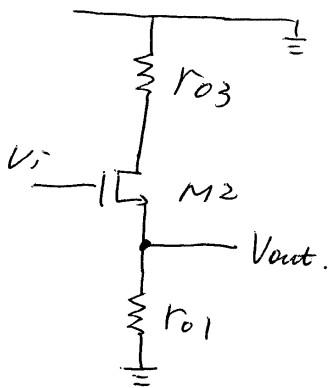(b) The small-signal circuit is shown below: M2 is source follower (CD) connection:



$$A_v = -G_m \cdot R_{out}$$


$$= \boxed{1/2 g_{m2} \cdot \underbrace{(r_{o1} \parallel \dots)}_{\text{resistor looking down}} \cdot \underbrace{\frac{r_{o3} + r_{o2}}{1 + g_{m2} r_{o2}}}_{\text{resistor looking up}}}$$

* Notes: If we assume $g_{m2} r_{o2} \gg 1$, and $r_{o3} = r_{o2}$ (M_2 & M_3 have the same channel length,

$$\text{the } A_v \cong 1/2 g_{m2} \cdot (r_{o1} \parallel \frac{2}{g_{m2}}) \\ \cong 1/2 g_{m2} \cdot \frac{2}{g_{m2}} = 1$$

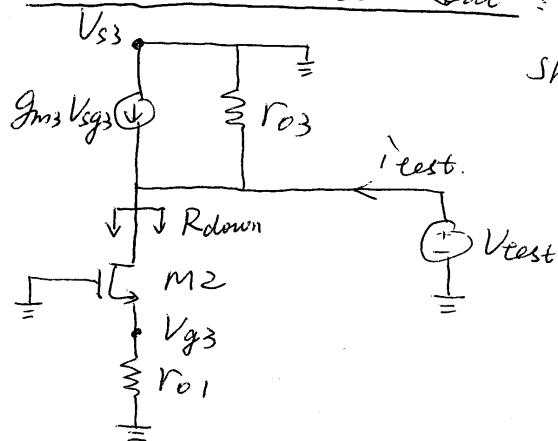(c) $A_v = -G_m \cdot R_{out}$.

First calculate R_{out} : Apply V_{test} at output



short input node to ground.

$$R_{out} = \frac{V_{test}}{i_{test}}$$


$$i_{test} = \frac{V_{test}}{r_{o3}} - g_{m3} \cdot V_{sg3} + \frac{V_{test}}{R_{down}} \quad (1)$$

R_{down} is the ~~output~~ output resistance of a common source stage (M_2) with degeneration resistor = r_{o1}

$$\therefore R_{down} = r_{o1} + (1 + g_{m2} \cdot r_{o1}) \cdot r_{o2} \quad (2)$$

$$V_{sg3} = V_{s3} - V_{g3} = 0 - V_{g3} = -V_{g3} \quad (5)$$

To calculate V_{g3} :

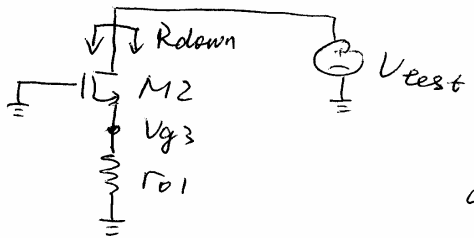

In order to calculate V_{g3} , we can use the concept of voltage divider :

$$V_{g3} = V_{test} \cdot \frac{r_{o1}}{R_{down}} \quad (5)$$

Substitute (3), (4) into (1)

$$i_{test} = \frac{V_{test}}{r_{o3}} + g_{m3} \cdot V_{test} \cdot \frac{r_{o1}}{R_{down}} + \frac{V_{test}}{R_{down}}$$

$$\therefore R_{out} = \frac{V_{test}}{i_{test}} = r_{o3} \parallel R_{down} \parallel \frac{R_{down}}{g_{m3} \cdot r_{o1}} \quad (5)$$

Substitute (2) into (5) and assume $g_m \cdot r_o \gg 1$.

$$R_{out} \cong r_{o3} \parallel \frac{g_{m2} \cdot r_{o1} \cdot r_{o2}}{g_{m3} \cdot r_{o1}}$$


$$= \boxed{r_{o3} \parallel \frac{g_{m2} \cdot r_{o2}}{g_{m3}}}$$

Calculation of G_m :

6

In order to calculate G_m , we need to short output to ground, apply V_{in} , then
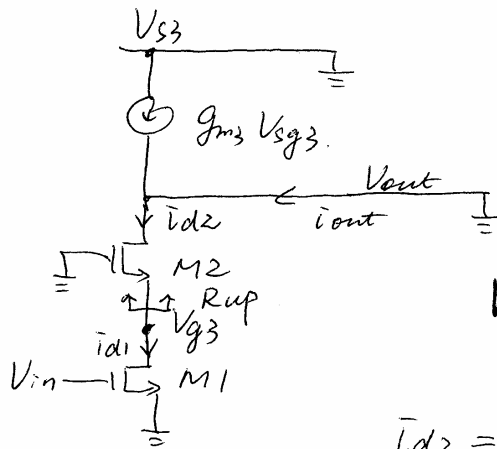
$$G_m = \frac{\bar{i}_{out}}{V_{in}} \quad \text{the equivalent ckt is:}$$



KCL @ output :

$$\bar{i}_{out} = -g_{m3} \cdot V_{sg3} + \bar{i}_{d1} \quad (1)$$

$$V_{sg3} = V_{s3} - V_{g3}$$

$$= 0 - V_{g3} = -V_{g3} \quad (2)$$

$$\bar{i}_{d2} = \bar{i}_{d1} = g_{m1} \cdot V_{in} \quad (3)$$

If we define $A_{v1} = \frac{V_{g3}}{V_{in}}$, the A_{v1} is the vol. gain of a common source (M_1) amplifier.

$$A_{v1} = -g_{m1} \cdot (R_{up} || r_{o1}) - g_{m1} \cdot \left(\frac{1}{g_{m2}} || r_{o1} \right) \approx -g_{m1} / g_{m2}$$

$$\therefore V_{g3} = V_{in} \cdot A_{v1} = -V_{in} \cdot \frac{g_{m1}}{g_{m2}} \quad (4)$$

Substitute (2), (3), (4) in (1)

$$\begin{aligned} \bar{i}_{out} &= g_{m3} \cdot V_{g3} + g_{m1} \cdot V_{in} \\ &= \left(g_{m1} - g_{m3} \cdot \frac{g_{m1}}{g_{m2}} \right) V_{in} \end{aligned}$$

$$G_m = \frac{i_{out}}{V_{in}} = \boxed{g_{m1} - g_{m3} \cdot \frac{g_{m1}}{g_{m2}}} \quad (5)$$


$$\therefore A_v = -G_m \cdot R_{out}$$

$$= \left[- \left(g_{m1} - g_{m3} \cdot \frac{g_{m1}}{g_{m2}} \right) \cdot \left(r_{o3} \parallel \frac{g_{m2} \cdot r_{o2}}{g_{m3}} \right) \right]$$

(d) $A_v = -G_m \cdot R_{out}$.

$$\boxed{G_m = g_{m1}}$$

Calculation of R_{out}

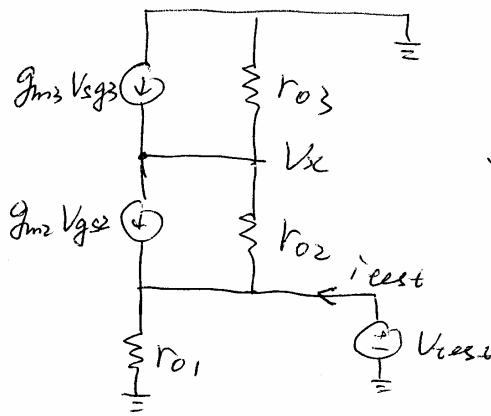

i_{test} has two parts,
one is flowing down
through r_{o1} ;

another part flows up
we define it as i_{up}

According to the KCL

@ output & node V_x .

$$\bar{i}_{up} = \frac{V_{test} - V_x}{r_{o2}} - g_{m2} \cdot V_{gs2} = \frac{V_x}{r_{o3}} - g_{m3} \cdot V_{gs3}$$

⑧

$$V_{gs2} = V_{g2} - V_{s2} = 0 - V_{test} = -V_{test}$$

$$V_{gs3} = V_{s3} - V_{g3} = 0 - V_{test} = -V_{test}$$

substitute in ①, solve for V_x :

$$V_x = V_{test} \left[(r_{o2} \parallel r_{o3}) \left(\frac{1}{r_{o2}} + g_{m2} - g_{m3} \right) \right] \quad \text{②}$$

substitute in ①, solve for i_{up} :

$$i_{up} = \frac{V_x}{r_{o3}} + g_{m3} \cdot V_{test}$$

$$= \left[\frac{r_{o2} \parallel r_{o3}}{r_{o3}} \left(\frac{1}{r_{o2}} + g_{m2} - g_{m3} \right) + g_{m3} \right] \cdot V_{test}$$

$$\therefore R_{up} = \frac{V_{test}}{i_{up}} = \frac{1}{\frac{r_{o2} \parallel r_{o3}}{r_{o3}} \left(\frac{1}{r_{o2}} + g_{m2} - g_{m3} \right) + g_{m3}}$$

if g_{m2} is close to g_{m3} , $g_m \cdot r_o \gg 1$

then $R_{up} \approx \frac{1}{g_{m3}}$

$$\text{Total } R_{out} = R_{up} \parallel r_{o1} \approx \frac{1}{g_{m3}} \parallel r_{o1} \approx \frac{1}{g_{m3}}$$

$$\therefore A_v = -G_m \cdot R_{out}$$

$$\approx -\frac{g_{m1}}{g_{m3}}$$