

EE140 HW#4 Solution


Ⓟ

1.


a)

Gain calculation.

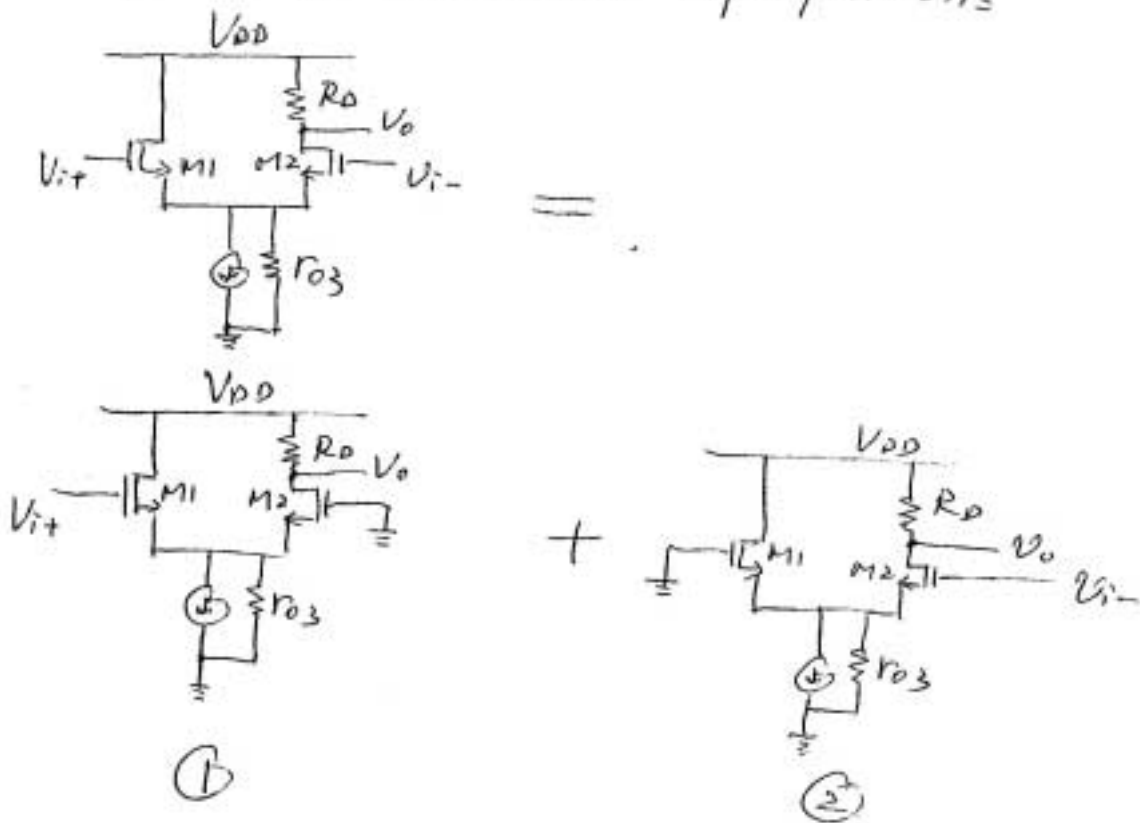
Since the circuit is asymmetric, we can not use the half circuit method. Instead of that, we can use linear superposition =



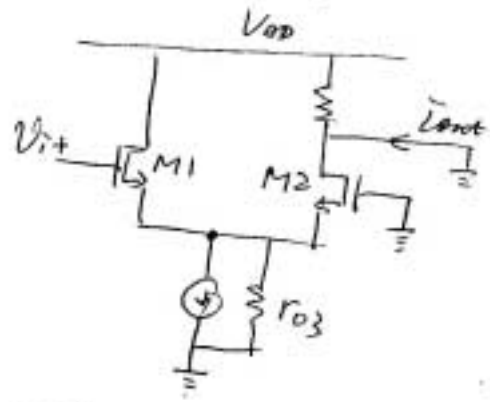In circuit (1), to calculate G_m , short output node to ground:




The eqv. small-signal model circuit:

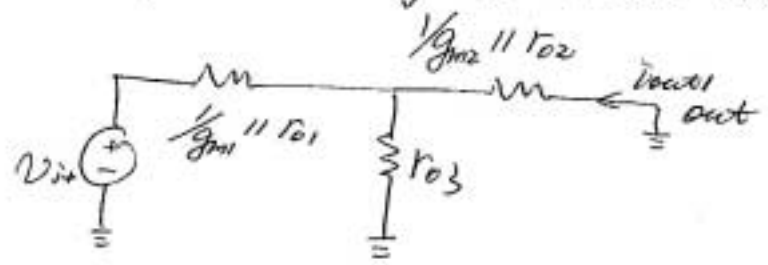


$$\therefore \frac{I_{out1}}{V_{i+}} = \frac{-1}{\frac{1}{g_{m1}} \parallel r_{o1} + r_{o3} \parallel r_{o2} \parallel \frac{1}{g_{m2}}} \times \frac{r_{o3}}{r_{o3} + \frac{1}{g_{m2}} \parallel r_{o2}}$$

In circuit (2), to calculate G_m , short output node to ground:

(3)

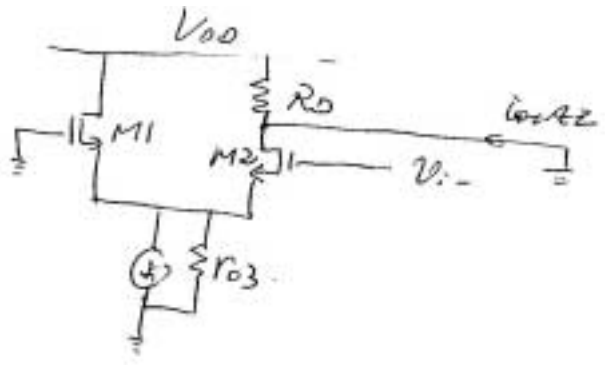

The eqv. small-signal model circuit:

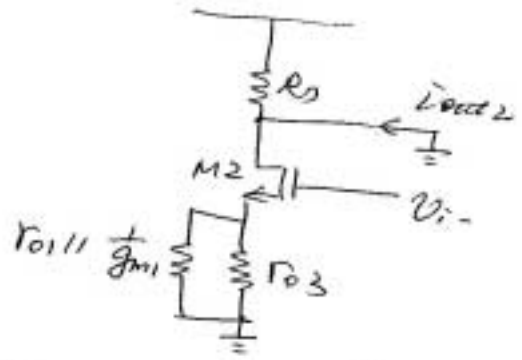

$$\therefore \frac{i_{out2}}{V_{i-}} = \frac{g_{m2}}{1 + g_{m2} \cdot (r_{03} \parallel r_{01} \parallel \frac{1}{g_{m1}})}$$

Since $\bar{v}_{out} = \bar{v}_{out1} + \bar{v}_{out2}$

$$V_{i+} = \frac{V_{id}}{2} \quad \text{and} \quad V_{i-} = -\frac{V_{id}}{2}$$

$$\therefore \bar{v}_{out} = -\frac{V_{id}}{2} \left[\frac{r_{03}}{\frac{1}{g_{m1}} \parallel r_{01} + r_{03} \parallel r_{02} \parallel \frac{1}{g_{m2}}} \cdot \frac{1}{r_{03} + \frac{1}{g_{m2}} \parallel r_{02}} + \frac{g_{m2}}{1 + g_{m2} \cdot (r_{03} \parallel r_{01} \parallel \frac{1}{g_{m1}})} \right]$$

④

$$i.e. G_m = \frac{i_{out}}{V_{in}} = -\frac{1}{2} \left[\frac{r_{o3}}{\left(\frac{1}{g_{m1}} \parallel r_{o1} + r_{o3} \parallel r_{o2} \parallel \frac{1}{g_{m2}}\right) \left(r_{o3} + \frac{1}{g_{m2}} \parallel r_{o2}\right)} + \frac{g_{m2}}{1 + g_{m2} \cdot \left(r_{o3} \parallel r_{o1} \parallel \frac{1}{g_{m1}}\right)} \right]$$


Assume $\frac{1}{g_m} \ll r_o$ and $g_{m1} = g_{m2} = g_{m1,2}$ (since V_{os} is small, we can ignore the channel length modulation in hand calculation and assume $i_{d1} = i_{d2}$)

$$i.e. G_{m, \text{sim}} \approx -\frac{1}{2} g_{m1,2} = -\frac{1}{2} \sqrt{2 I_{D1,2} \cdot k' \cdot \frac{w}{L_{eff}}}$$


$$k' \cdot \frac{w}{L_{eff}} = 16.6 \text{ mA/V}^2 \quad I_{D1,2} = \frac{1}{2} I_B = 300 \mu\text{A}$$

$$i.e. G_{m, \text{sim}} \approx -1.58 \text{ mA/V} \quad \left[-1.65 \text{ ms from simulation} \right]$$

Root calculation :-

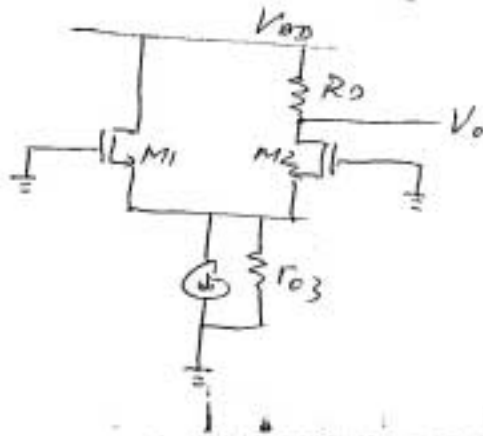

The eqv. small signal model circuit is:

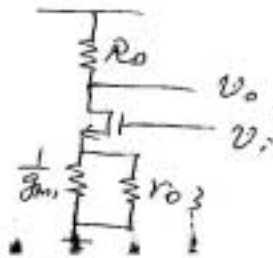

$$\therefore R_{out} = R_o \parallel \left[\frac{1}{g_{m1}} \parallel r_{o3} + (1 + g_{m2} (r_{o3} \parallel \frac{1}{g_{m1}})) r_{o2} \right] \quad \textcircled{5}$$

$$r_{o3} = \frac{1}{\lambda I_{o3}} = \frac{1}{0.2 \times 600 \mu A} \approx 8.33 \text{ k}\Omega$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda I_{o1,2}} = \frac{1}{0.2 \times 300 \mu A} \approx 16.67 \text{ k}\Omega$$

$$g_{m1,2} = 3.16 \text{ mS} \quad R_o = 1 \text{ k}\Omega$$

$$\therefore \boxed{R_{out} = 970.6 \Omega} \quad (974.6 \Omega \text{ from spice simulation})$$

$$A_{v-dm} = -G_{m,dm} \cdot R_{out}$$

$$= 1.58 \text{ mA/V} \times 970.6 \Omega$$

$$= \boxed{1.53} \quad (1.61 \text{ from spice simulation})$$

$G_{m,cm}$ calculation

the common mode circuit is a common-source w/ degeneration circuit

$$\therefore G_{m,cm} = \frac{g_{m1,2}}{1 + g_{m1,2} \cdot 2 \cdot r_{o3}} = \frac{3.16 \text{ mS}}{1 + 3.16 \text{ mS} \times 2 \times 8.33 \text{ k}\Omega}$$

$$= \boxed{0.059 \text{ mS}} \quad (0.050 \text{ mS from simulation})$$

⑥

$$\therefore A_{v-cm} = -G_{m,cm} \cdot R_{out}$$

$$= -0.059 \text{ ms} \cdot 970.6 \Omega$$

$$= \boxed{-57.17 \text{ m}} \quad (-48.62 \text{ m from simulation}).$$

⑦

2.

a) $V_{GDS} = V_{GSb} = V_{t0} + V_{dsatb} > V_{t0}$ of NMOS

\therefore There must exist channel around drain region of NMOS \Rightarrow M5 in linear region

b) Since $V_{G2} = V_{GSb} + V_{DS1}$ (ignore body effect)
 $= V_{t0} + V_{dsatb} + V_{DS1}$

Since M1 \rightarrow M4 have the same size

$\therefore I_{out} = I_{ref} \Rightarrow I_{Dsb} = I_{Dsa2} = I_{Dsa1} = I_{ref}$

$\therefore V_{dsatb} = V_{dsat1}$

$\therefore V_{G2} = V_{t0} + 2V_{dsat1}$

In order to make M2 in the saturation region

$V_{sat(min)} = V_{G2} - V_{t0} = 2V_{dsat1}$

c). Since M5 in linear region:

$$I_{D5} = K' m_5 \cdot \frac{W}{L} (V_{GS5} - V_{th5} - \frac{V_{DS5}}{2}) V_{DS5} \quad (1)$$

$$\text{define } m_5 = \frac{(\frac{W}{L})_5}{(\frac{W}{L})_6} ; (\frac{W}{L})_6 = \frac{W}{L}$$

$$I_{D6} = \frac{1}{2} K' \frac{W}{L} (V_{GS6} - V_{th6})^2 \quad (2)$$

$$I_{D5} = I_{D6} \quad (3)$$

$$V_{GS5} = V_{GS6} + V_{DS5} = V_{GS6} + V_{DS6} \quad (4)$$

$$V_{GS6} = V_{th6} + V_{DS6} = V_{th6} + V_{DS6} \quad (5)$$

$$\text{Solve for } m_5 = \frac{1}{3}$$

$$\therefore (\frac{W}{L})_5 = \frac{1}{3} \frac{W}{L}$$

(9)

3. In order to make a PMOS transistor in saturation region, It must satisfy:

$$V_{DS} \leq |V_{tp}|$$

For M1:

$$\begin{aligned} V_{DS1} &= V_{D1} - V_{S1} \\ &= V_{S2} - I_{ref} \cdot R \quad (\text{From KVL}) \\ &= |V_{tp}| + V_{DS2} - I_{ref} \cdot R \end{aligned}$$

Since $V_{DS1} \leq |V_{tp}|$

$$\therefore |V_{tp}| + V_{DS2} - I_{ref} \cdot R \leq |V_{tp}|$$

Solve for I_{ref} :

$$I_{ref} \geq \frac{V_{DS2}}{R} = \frac{\sqrt{\frac{2I_{ref}}{\mu_p C_{ox} \cdot \frac{W}{L}}}}{R}$$

$$\Rightarrow \boxed{I_{ref} \geq \frac{2}{\mu_p C_{ox} \cdot \left(\frac{W}{L}\right) \cdot R^2}}$$

For M2:

⑩

$$V_{out2} = I_{ref} \cdot R \leq |V_{op1}|$$

$$\therefore \boxed{I_{ref} \leq \frac{|V_{op1}|}{R}}$$

SPICE deck for Prob.1

HW#4 Problem 1

```
.include 'model.m'
```

```
VDD vdd 0 dc 1.2v
RD vdd vo 1k
IB vdd g4 dc 600u
Vid vid 0 dc
Vic vin 0 dc 0.8
Evi+ vi+ vin vid 0 0.5
Evi- vi- vin vid 0 -0.5
```

```
M1 vdd vi+ d3 d3 NMOS W=4u L=0.13u
```

```
M2 vo vi- d3 d3 NMOS W=4u L=0.13u
```

```
M3 d3 g4 0 0 NMOS W=4u L=0.13u
```

```
M4 g4 g4 0 0 NMOS W=4u L=0.13u
```

```
.tf V(vo) vid
```

```
*.tf V(vo) vic
```

```
.op
```

```
.end
```

Output Result:

**** small-signal transfer characteristics (**Differential mode operation**)

```
v(vo)/vid = 1.6111
input resistance at vid = 1.000e+20
output resistance at v(vo) = 974.5869
```

**** small-signal transfer characteristics (**Common mode operation**)

```
v(vo)/vic = -48.6176m
input resistance at vic = 1.000e+20
output resistance at v(vo) = 974.5869
```

Notes: Gm can be got from -Av/Rout.