

EECS 140 FALL 2002

RW BRODERSEN

NAME SOLUTIONS

SHOW YOUR WORK

COPY YOUR ANSWERS TO THIS PAGE

⑤ D .8 V

④ 6a 400

⑤ Z 600 μ A

④ b -1.45 V.

④ 3a 15 $k\Omega$

④ 7 $\frac{w}{L_1} = 204$

④ b -1 Volts

② $\frac{w}{L_2} = 816$

⑤ 4 a LINEAR

b ~~$\frac{w}{L} =$~~


TOTAL (45)

⑤ 5 a 100 Ω

⑤ b .005 Ω

⑤ c 50 Ω

⑤ d .01 Ω

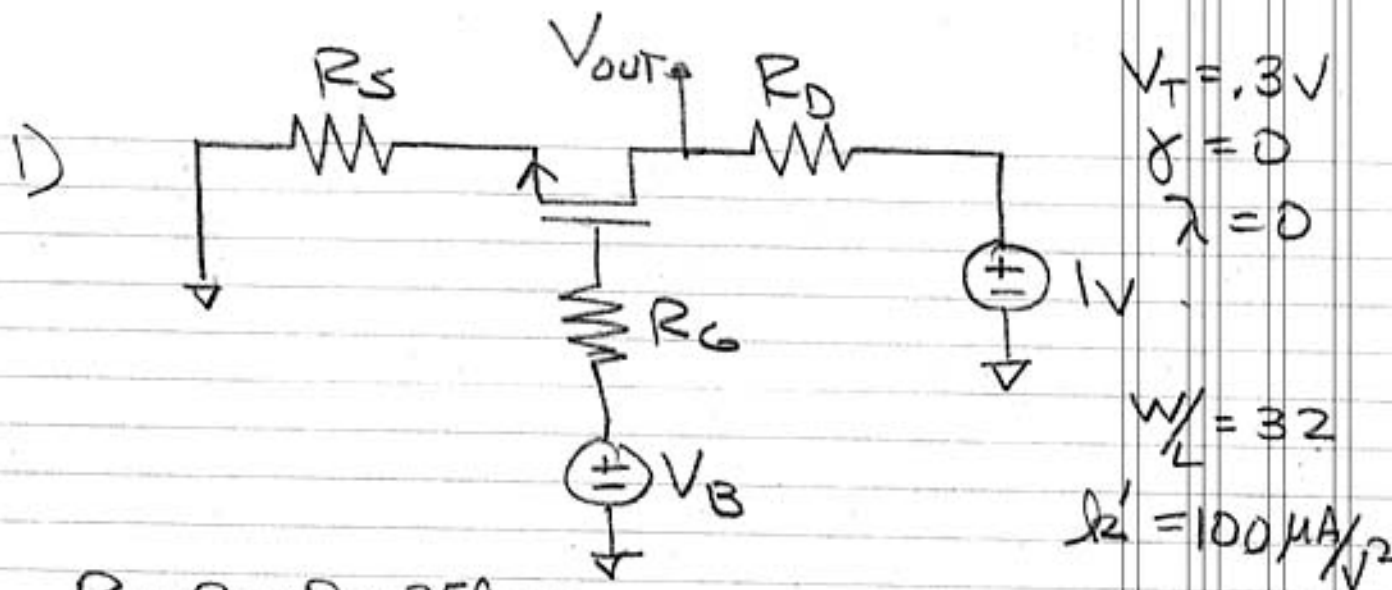

$$R_S = R_D = R_G = 2.5k\Omega$$

WHAT IS V_B SO THAT $V_{OUT} = 0.75V$?


$$V_B = 0.8V$$

$$I_{DS} = \frac{1 - 0.75}{2.5k} = 100\mu A$$

$$-V_B + V_{GS} + I_{DS}R_S = 0$$

$$V_{GS} = V_T + \left(\frac{2I_{DS}}{k'W/L} \right)^{1/2} = 0.3 + 0.25V$$

$$V_B = 0.3 + 0.25 + 0.25 = 0.8V$$

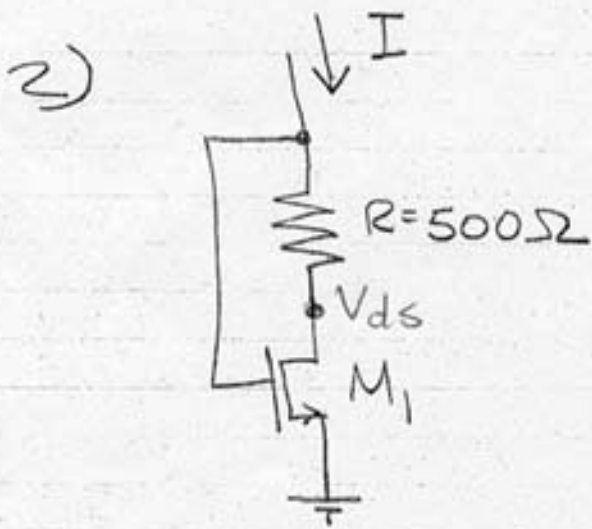

$$V_T = 0.3V$$

$$\gamma = 0$$

$$\lambda = 0$$

$$W/L = 1$$

$$\mu_n' = 100 \mu A/V^2$$


AT WHAT CURRENT DOES M_1
GO FROM SATURATION TO LINEAR?

$$V_{gs} - I(500) = V_{dsat}$$

$$V_T + V_{dsat} - I(500) = V_{dsat}$$

$$I = \frac{V_T}{500} = \frac{0.3}{500} = 0.6 \mu A$$

3)

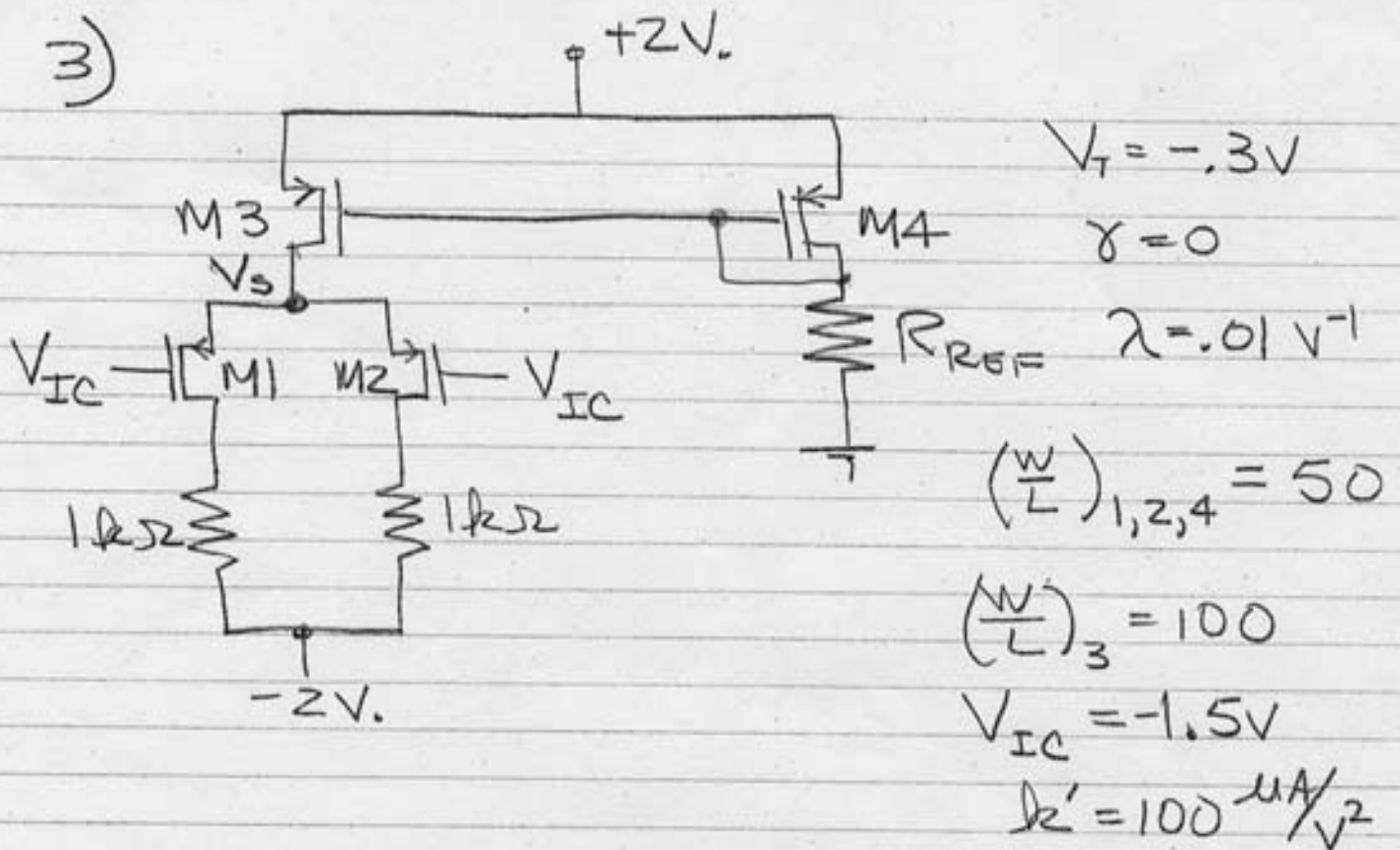

a) CALCULATE R_{REF} SO THAT $I_{DS4} = 100 \mu A$

$R_{REF} = 15 k\Omega$

$$2 - (100 \mu A) R_{REF} = V_{SG4} = V_T + \left(\frac{2 (100 \mu A)}{100 \mu A / V^2 \cdot 50} \right)^{1/2}$$

$$2 - 100 \mu A (R_{REF}) = 0.3 + 2$$

$$R_{REF} = \frac{1.5}{10^{-4}} = 15 k\Omega$$


b) WHAT IS THE VOLTAGE AT THE

SOURCE OF M_1 & M_2 ? $V_S = -1V$

$$V_S = V_{IC} + V_{GS} = -1.5 + 0.2 + 0.3$$

$$= -1V$$

4)

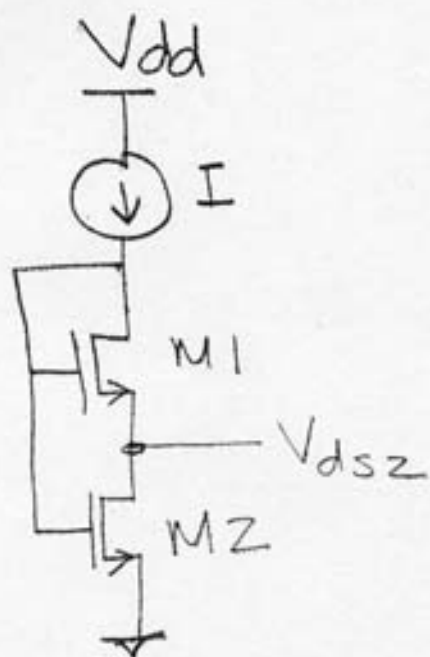

YOU DON'T
NEED TO KNOW
THE VALUE OF I

$$\gamma \neq 0$$

$$(W/L)_1 \neq (W/L)_2$$

a) WHAT IS THE REGION OF OPERATION OF M2 AND WHY?

Is $V_{GS2} - V_{T2} > V_{DS2}$, IF SO THEN M2 IS IN LINEAR.

FROM CIRCUIT $V_{DS2} = V_{GS2} - V_{GS1}$

SUBSTITUTING $V_{GS2} - V_{T2} > V_{GS2} - V_{GS1}$

OR $V_{GS1} > V_{T2}$


SINCE $V_{GS1} = V_{DSAT1} + V_{T0} + \gamma (V_{DS2})^{1/2}$

$V_{T2} = V_{T0}$

WE HAVE $V_{DSAT1} + \gamma (V_{DS2})^{1/2} > 0$

YES IT IS - SO M2 IS
IN LINEAR.

5)

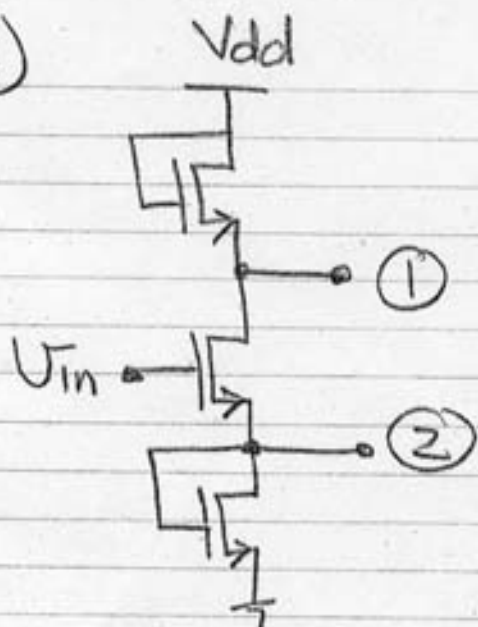

ASSUME THE FOLLOWING
VALUES FOR ALL THE
TRANSISTORS

$$r_o = 1\text{M}\Omega, g_m = 0.0125$$

$$g_{mb} = 0$$

a) WHAT IS R_{out} AT ①? 100 Ω

$$g_m \parallel r_o (1 + g_m \frac{1}{g_m}) \approx g_m$$

b) WHAT IS G_m AT ①? .005 Ω


$$G_m = \frac{g_m}{1 + g_m (\frac{1}{g_m})} = \frac{g_m}{2}$$

c) WHAT IS R_{out} AT ②? 50 Ω

$$\frac{1}{g_m} \parallel \frac{1}{g_m}$$

d) WHAT IS G_m AT ②? .01 Ω

G_m OF SOURCE FOLLOWER IS g_m

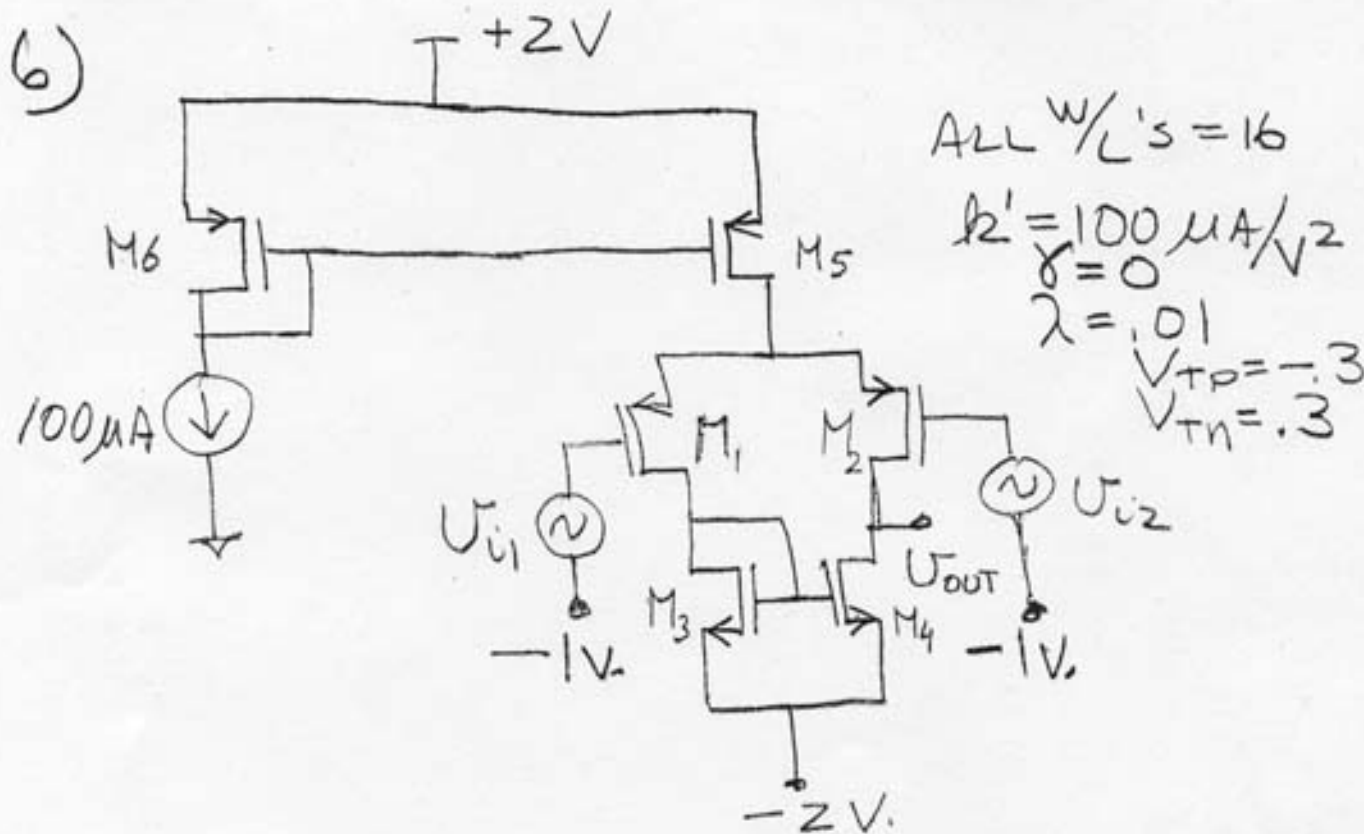

a) WHAT IS THE GAIN $\frac{U_{OUT}}{U_{i1} - U_{i2}}$? $g_m R_{OUT} = 400$

$I_{DS} = 50 \mu A$

$$V_{DSAT,1} = \left(\frac{2 \cdot 50 \mu A}{10^{-4} \times 16} \right)^{1/2} (U_{i1} - U_{i2})$$

$$= .25 V$$


$$g_m = \frac{2 I_{DS}}{V_{DSAT}} = .4 \times 10^{-3} S$$

$$r_{OUT} = (r_{o4} \parallel r_{o2}) = \frac{1}{2 \times 50 \times 10^{-6} \times .01} = 10^6$$

b) WHAT IS THE DC VOLTAGE AT U_{OUT} ?
-1.45 V.

$$-2 + V_T + V_{dsat} = -2 + .3 + .25 = -1.45 V$$

7)

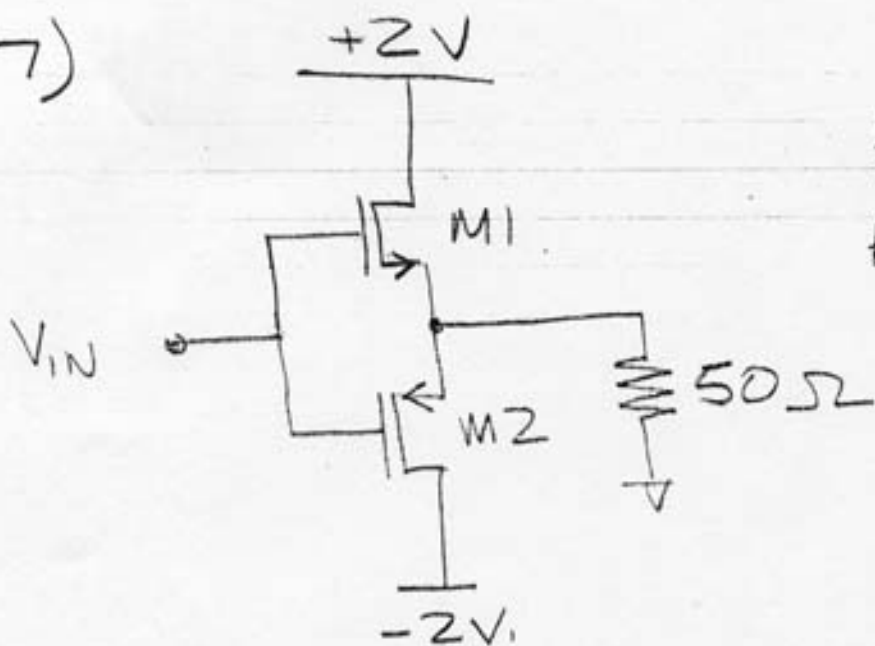

$$k'_n = 400 \mu\text{A}/\text{V}^2$$

$$k'_p = 100 \mu\text{A}/\text{V}^2$$

$$\gamma = \lambda = 0$$

$$V_{Tn} = 0.3 \text{ V}$$

$$V_{Tp} = -0.3 \text{ V}$$

WHAT ARE THE W/L 'S OF $M1$ & $M2$ SO THAT THE OUTPUT CAN SWING $\pm 1 \text{ V}$.

IF THE INPUT CAN GO TO THE

SUPPLIES ($\pm 2 \text{ V}$)? $(W/L)_1$ 204

$$I_{Ds} = \frac{1 \text{ V}}{50 \Omega} = 20 \text{ mA}$$

$$(W/L)_2$$
 816

$$\text{For } M1: 20 \times 10^{-3} = \frac{k'_n}{2} \frac{W}{L} (2 - 1 - 0.3)^2$$

$$\left(\frac{W}{L}\right)_1 = \frac{20 \times 10^{-3} \times 2}{400 \times 10^{-6} (0.7)^2} = 204$$

THE k' OF $M2$ IS $1/4$ THAT OF $M1$

$$\text{SO } \left(\frac{W}{L}\right)_2 = 4 \left(\frac{W}{L}\right)_1$$