

P24.1.

Solution: Large signal


$$\textcircled{1} \quad i_{D1} + i_{D2} = I_{SS}$$

$$\textcircled{2} \quad V_{GS1} = V_{THN} + \sqrt{\frac{2i_{D1}}{\beta_1}}$$

$$V_{GS2} = V_{THN} + \sqrt{\frac{2i_{D2}}{\beta_2}}$$

if, same size $\Rightarrow \beta_1 = \beta_2 = \beta$
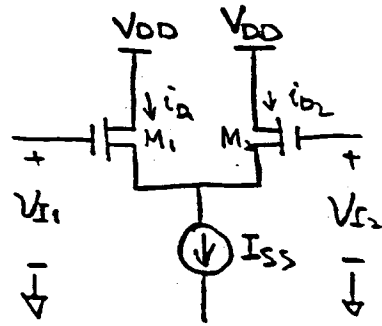
$$\text{then } V_{I1} - V_{I2} = V_{GS1} - V_{GS2} = \sqrt{\frac{2i_{D1}}{\beta}} - \sqrt{\frac{2i_{D2}}{\beta}} = \sqrt{\frac{2}{\beta}} (\sqrt{i_{D1}} - \sqrt{i_{D2}})$$



$$\textcircled{3} \text{ Solving: } \begin{cases} i_{D1} + i_{D2} = I_{SS} & \textcircled{a} \\ \sqrt{i_{D1}} - \sqrt{i_{D2}} = \sqrt{\frac{\beta}{2}} (V_{I1} - V_{I2}) & \textcircled{b} \end{cases}$$

From \textcircled{b} , square both side

$$i_{D1} - 2\sqrt{i_{D1}i_{D2}} + i_{D2} = \frac{\beta}{2} (V_{I1} - V_{I2})^2$$

Note: $i_{D1} + i_{D2} = I_{SS}$

$$\Rightarrow 2\sqrt{i_{D1}i_{D2}} = I_{SS} - \frac{\beta}{2} (V_{I1} - V_{I2})^2 \quad \textcircled{c}$$

 $\textcircled{a} + \textcircled{c}$:

$$\Rightarrow (\sqrt{i_{D1}} + \sqrt{i_{D2}})^2 = 2I_{SS} - \frac{\beta}{2} (V_{I1} - V_{I2})^2$$

$$\text{or } \sqrt{i_{D1}} + \sqrt{i_{D2}} = \sqrt{2I_{SS} - \frac{\beta}{2} (V_{I1} - V_{I2})^2} \quad \textcircled{d}$$

 $\textcircled{b} + \textcircled{d}$

$$\Rightarrow 2\sqrt{i_{D1}} = \sqrt{\frac{\beta}{2} (V_{I1} - V_{I2})^2} + \sqrt{2I_{SS} - \frac{\beta}{2} (V_{I1} - V_{I2})^2}$$

$$\text{or } 4i_{D1} = \frac{\beta}{2} (V_{I1} - V_{I2})^2 + 2\sqrt{\frac{\beta}{2} (V_{I1} - V_{I2})^2} \sqrt{2I_{SS} - \frac{\beta}{2} (V_{I1} - V_{I2})^2} + 2I_{SS} - \frac{\beta}{2} (V_{I1} - V_{I2})^2$$

$$\Rightarrow 4i_{D1} = 2I_{SS} + 2\sqrt{I_{SS}\beta(V_{I1} - V_{I2})^2 - \frac{\beta^2}{4}(V_{I1} - V_{I2})^4}$$


24.2

Repeat Ex. 24.1 if the widths of M1 + M2 are increased to 100 μm . Determine the transconductance of the diff-amp. Write i_{dz} as a product of $g_m (= g_{m1} = g_{m2})$ and V_{I1} (with $V_{I2} = \text{AC ground}$), V_{I2} (with $V_{I1} = \text{AC ground}$), and $V_{I1} - V_{I2}$.

$$V_{O1\text{MAX}} = \sqrt{\frac{2 I_{SS}}{\beta}} = \sqrt{\frac{2 \cdot 10 \mu}{50 \mu \cdot \frac{100}{5}}} = 14 \text{ mV}$$

$$G_m = \frac{\sqrt{2 \beta I_{SS}}}{4} = \frac{\sqrt{2 \cdot 50 \mu \left(\frac{100}{5}\right) (10 \mu)}}{4} = 35.3 \mu\text{A/V}$$

$$g_m = 4 G_m = 141.4 \mu\text{A/V}$$

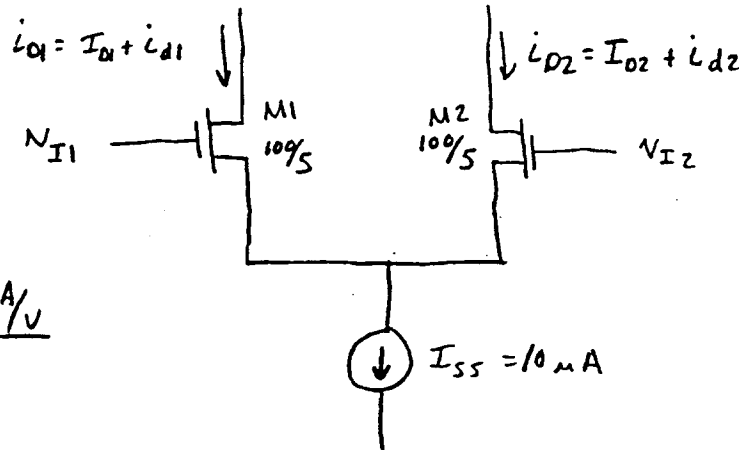

- When $V_{I2} = 0$

$$i_{dz} = g_{m2} v_{gs2} = g_m \left(\frac{-V_{O1}}{2} \right) = \underline{\underline{-g_m \frac{V_{I1}}{2}}}$$


- When $V_{I1} = 0$

$$i_{dz} = g_{m2} v_{gs2} = g_m \left(\frac{V_{O1}}{2} \right) = \underline{\underline{g_m \frac{V_{I2}}{2}}}$$

- In terms of $V_{I1} - V_{I2}$

$$i_{dz} = g_{m2} v_{gs2} = g_m \frac{-V_{O1}}{2} = \underline{\underline{-g_m \frac{V_{I1} - V_{I2}}{2}}}$$

Problem 24.3 and 24.4

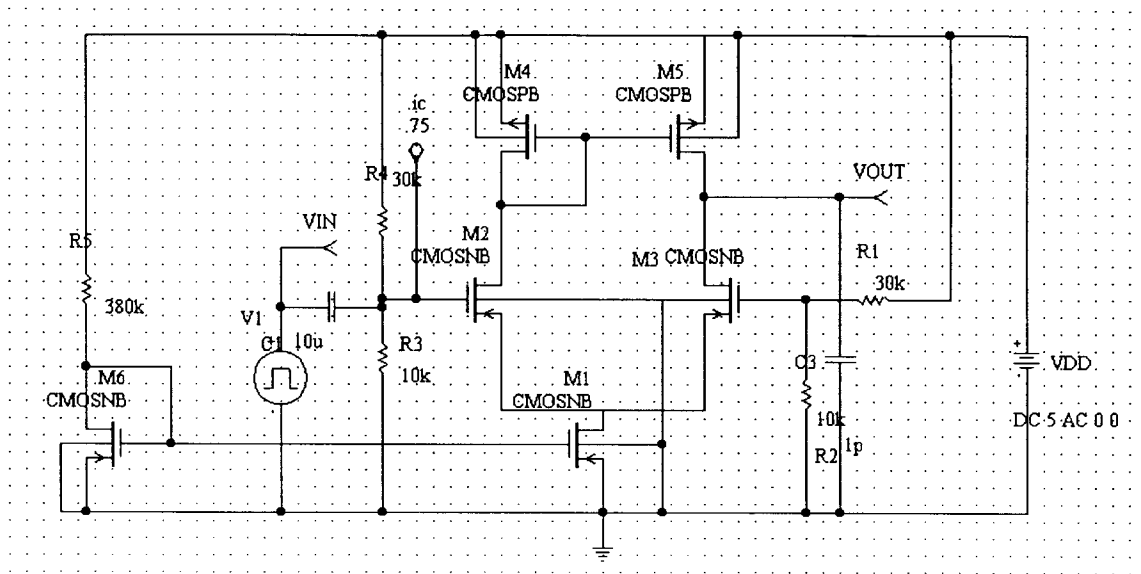

*** Top Level Netlist ***

```
.ic      V(5)=.75
C1      VIN 5 10u
C3      0 VOUT 1p IC=0
M1      1 2 0 0 CMOSNB L=5u W=30u
M2      4 5 1 0 CMOSNB L=5u W=15u
M3      VOUT 6 1 0 CMOSNB L=5u W=15u
M4      4 4 7 7 CMOSPFB L=5u W=70u
M5      VOUT 4 7 7 CMOSPFB L=5u W=70u
M6      2 2 0 0 CMOSNB L=5u W=15u
R1      6 7 30k
R2      0 6 10k
R3      5 0 10k
R4      7 5 30k
R5      7 2 380k
V1      VIN 0 DC 0 AC 0 0 PULSE(0 1 0 100n 100n 500u 1m)
VDD     7 0 DC 5 AC 0 0
```

***** Spice models and macro models *****


```
.MODEL CMOSNB NMOS LEVEL=4
```

```
.MODEL CMOSPFB PMOS LEVEL=4
```

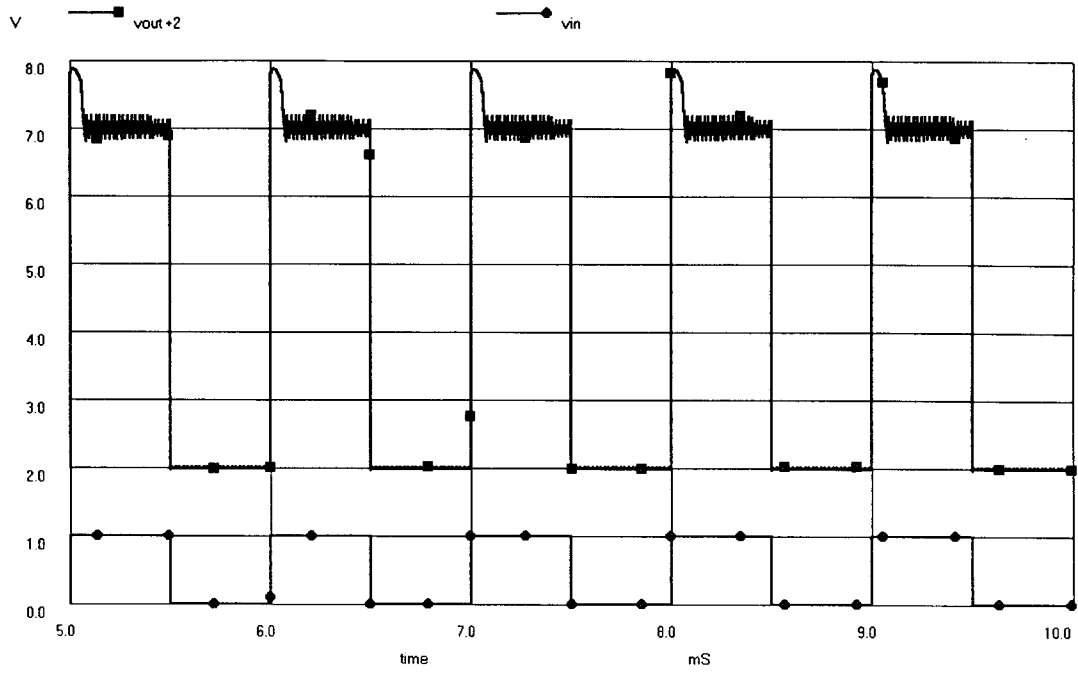***** End of spice models and macro models *****

```
.OPTION ABSTOL=10u RELTOL=0.01 VNTOL=10mv
.tran 10u 10m 5m 10u uic
.end
```


The SPICE simulation result is shown below:



24.5

Determine the small signal gain and the input common-mode range (CMR) for the diff-amps shown in Fig. P24.5. All n-channels are $15/5$, all p-channels are $70/5$, and the resistors are 3.8 MEG.

(a) First Circuit

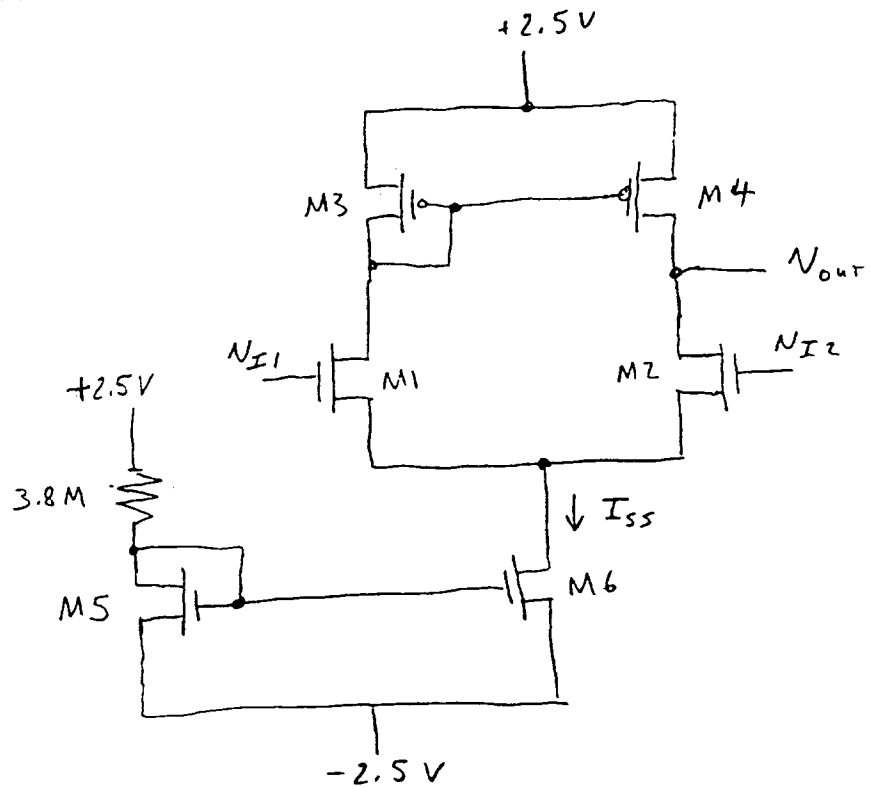

- Find DC current I_{SS}

$$\frac{5.0 - V_{GSS}}{3.8 \times 10^6} = \frac{50\mu}{2} \left(\frac{15}{5}\right) (V_{GSS} - .83)^2$$

$$0 = V_{GSS}^2 - 1.6635 V_{GSS} + .67136$$

$$V_{GSS} = .97478 \text{ V}$$

$$\therefore I_{SS} = \underline{1.06 \mu\text{A}}$$

- Determine the small signal gain

$$V_{out} = 2i_{d1}(r_{o2} || r_{o4})$$

$$\begin{aligned} V_{in} &= V_{gs1} - V_{gs2} \\ &= i_{d1} \frac{1}{g_{m1}} - i_{d2} \frac{1}{g_{m2}} \\ &= 2i_{d1} \frac{1}{g_{mn}} \end{aligned}$$


$$A_v = \frac{V_{out}}{V_{in}} = \frac{2i_{d1}(r_{o2} || r_{o4})}{2i_{d1} \frac{1}{g_{mn}}}$$

$$A_v = g_{mn}(r_{o2} || r_{o4})$$

$$g_{mn} = \sqrt{2(50\mu)(3) \frac{1.06\mu}{2}} = 12.61 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \frac{1}{.06 \left(\frac{1.06\mu}{2} \right)} = 31.45 \text{ M}\Omega$$

$$A_v = \underline{198 \text{ V/V}}$$

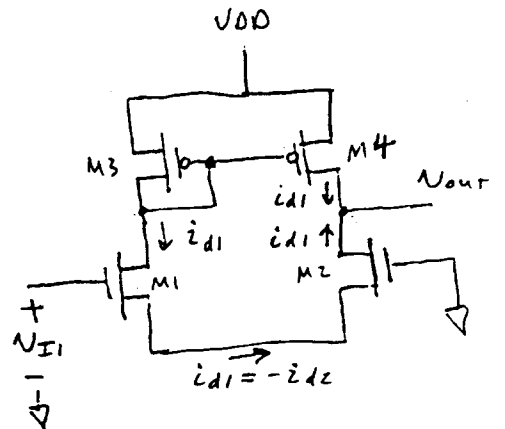

AC currents

- Determine the CMR

The maximum V_I is limited by M1 + M2 going into the triode region of operation.

$$V_{I\text{MAX}} = V_{DD} - \left[\sqrt{\frac{I_{SS}}{B_3}} + V_{THP} \right] + V_{THN}$$

$$= 2.5 - \left[\sqrt{\frac{1.06\mu}{17\mu \left(\frac{70}{5} \right)}} + .91 \right] + .83$$

$$= \underline{2.35 \text{ V}}$$

The minimum V_I is limited by M6 entering the triode region of operation

$$V_{I\text{MIN}} = V_{GS1} + V_{DS6} + V_{SS}$$

$$= \sqrt{\frac{I_{SS}}{B_1}} + V_{THN} + \sqrt{\frac{2I_{SS}}{B_6}} + V_{SS}$$

$$= \sqrt{\frac{1.06\mu}{50\mu(3)}} + .83 + \sqrt{\frac{2(1.06\mu)}{50\mu(3)}} - 2.5$$

$$= -1.47 \text{ V}$$

(b) Second Circuit


- Determine the DC currents

$$\frac{5 - V_{SG3}}{3.8(10^6)} = \frac{1721}{2} \left(\frac{20}{5}\right) (V_{SG3} - .91)^2$$

$$0 = V_{SG3}^3 - 1.818 V_{SG3} + 1.81704$$

$$V_{SG3} = 1.004 \text{ V}$$
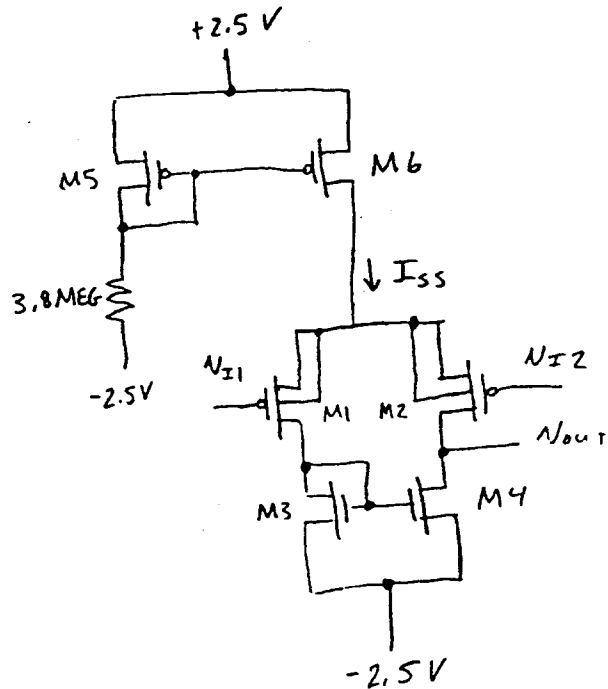
$$I_{SS} = \underline{1.05 \mu\text{A}}$$



- Determine the small signal gain

$$V_{out} = -2 i_{d1} (r_{o2} \parallel r_{o4})$$

$$V_{iN} = -i_{d1} \cdot \frac{1}{g_{m1}} - i_{d2} \cdot \frac{1}{g_{m2}}$$

$$V_{iN} = -2 i_{d1} \cdot \frac{1}{g_{mp}}$$


$$A_v = \frac{V_{out}}{V_{iN}} = \frac{-2 i_{d1} (r_{o2} \parallel r_{o4})}{-2 i_{d1} \cdot \frac{1}{g_{mp}}}$$

$$A_v = g_{mp} (r_{o2} \parallel r_{o4})$$

$$g_{mp} = \sqrt{2(17\mu)(14)\left(\frac{1.05\mu}{2}\right)} = 15.81 \mu\text{A/V}$$

$$r_{o2} = r_{o4} = \frac{1}{(0.06)\left(\frac{1.05\mu}{2}\right)} = 31.25 \text{ MEG}$$

$$A_v = \underline{251 \text{ V/V}}$$

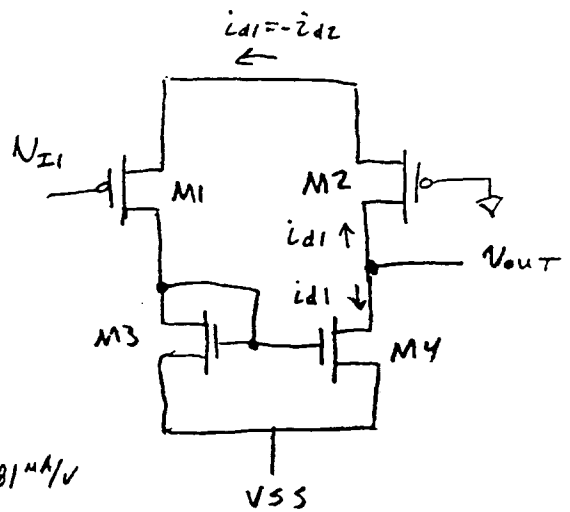

AC currents

- Determine the CMR

The maximum V_I is limited by M_6 entering the triode region.

$$\begin{aligned}V_{I\text{MAX}} &= -V_{SG1} - V_{S06} + V_{DD} \\&= -\left(\sqrt{\frac{I_{SS}}{B_1}} + V_{THP}\right) - \sqrt{\frac{2I_{SS}}{B_6}} + V_{DD} \\&= -\left(\sqrt{\frac{1.05\mu}{17\mu(14)}} + .91\right) - \sqrt{\frac{2(1.05\mu)}{17\mu(14)}} + 2.5 \\&= \underline{1.43\text{ V}}\end{aligned}$$

The minimum V_I is limited by M_1 & M_2 entering the triode region

$$\begin{aligned}V_{I\text{MIN}} &= V_{D1} - V_{THP} \\&= \left[\sqrt{\frac{I_{SS}}{B_3}} + V_{THN}\right] + V_{SS} - V_{THP} \\&= \left[\sqrt{\frac{1.05\mu}{50\mu(3)}} + .83\right] - 2.5 - .91 \\&= \underline{-2.50\text{ V}}\end{aligned}$$

Problem 24.6

* Prob ~~24~~.6 (Gain simulation for circuit b)

```
R1 2 3 3.8E6
M1 6 5 4 4 CMOSPB L=5U W=70U
M2 8 0 4 4 CMOSPB L=5U W=70U
M3 6 6 3 3 CMOSNB L=5U W=15U
M4 8 6 3 3 CMOSNB L=5U W=15U
M5 2 2 1 1 CMOSPB L=5U W=70U
M6 4 2 1 1 CMOSPB L=5U W=70U
VDD 1 0 DC 2.5
VSS 3 0 DC -2.5
Vin 5 0 DC 0
```

```
* BSIM model for n-channel CN20
.MODEL CMOSNB NMOS LEVEL=4
```

```
* BSIM model for p-channel CN20
.MODEL CMOSPB PMOS LEVEL=4
```

```
.probe
.DC Vin -.2 .2 .001
.end
```

* Prob ~~24~~.6 (CMR simulation for circuit b)

```
R1 2 3 3.8E6
M1 6 5 4 4 CMOSPB L=5U W=70U
M2 8 5 4 4 CMOSPB L=5U W=70U
M3 6 6 3 3 CMOSNB L=5U W=15U
M4 8 6 3 3 CMOSNB L=5U W=15U
M5 2 2 1 1 CMOSPB L=5U W=70U
M6 4 2 1 1 CMOSPB L=5U W=70U
VDD 1 0 DC 2.5
VSS 3 0 DC -2.5
Vin 5 0 DC 0
```

```
* BSIM model for n-channel CN20
.MODEL CMOSNB NMOS LEVEL=4
```


```
* BSIM model for p-channel CN20
.MODEL CMOSPB PMOS LEVEL=4
```

```
.probe
.DC Vin -3 3 .01
.end
```

Date/Time run: 03/03/98 17:25:28 * Problem 24.6 (Simulation for CMR of circuit a)

Temperature: 27.0

(D) A:\246CMRA.DAT

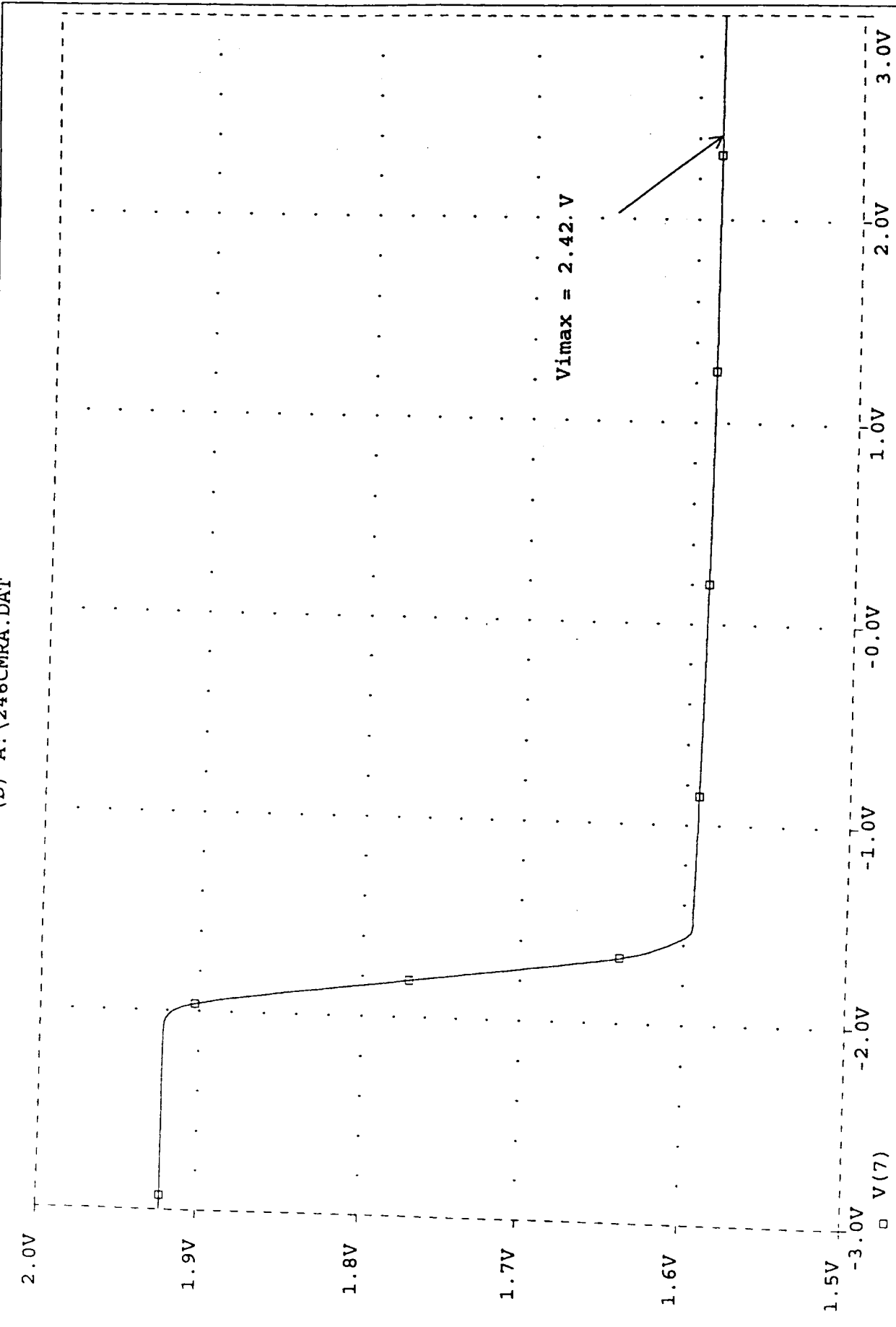


* Problem 24.6 (Simulation for CMR of circuit a)

Temperature: 27.0

Date/Time run: 03/03/98 17:25:28

(D) A:\246CMRA.DAT

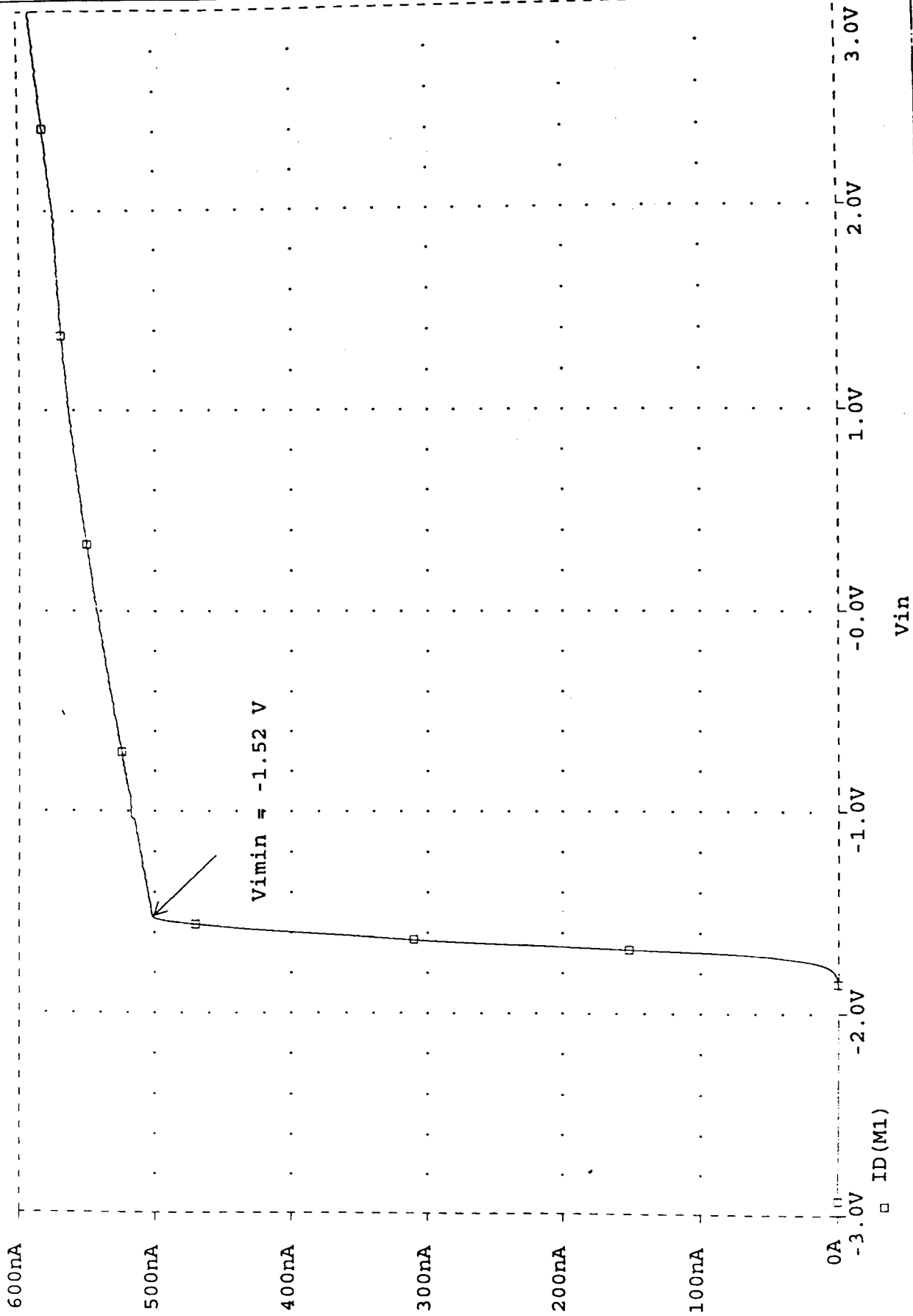


* Problem 24.6 (Gain simulation for circuit a)

Temperature: 27.0

Date/Time run: 03/05/98 10:00:24

(A) 246gaina.dat

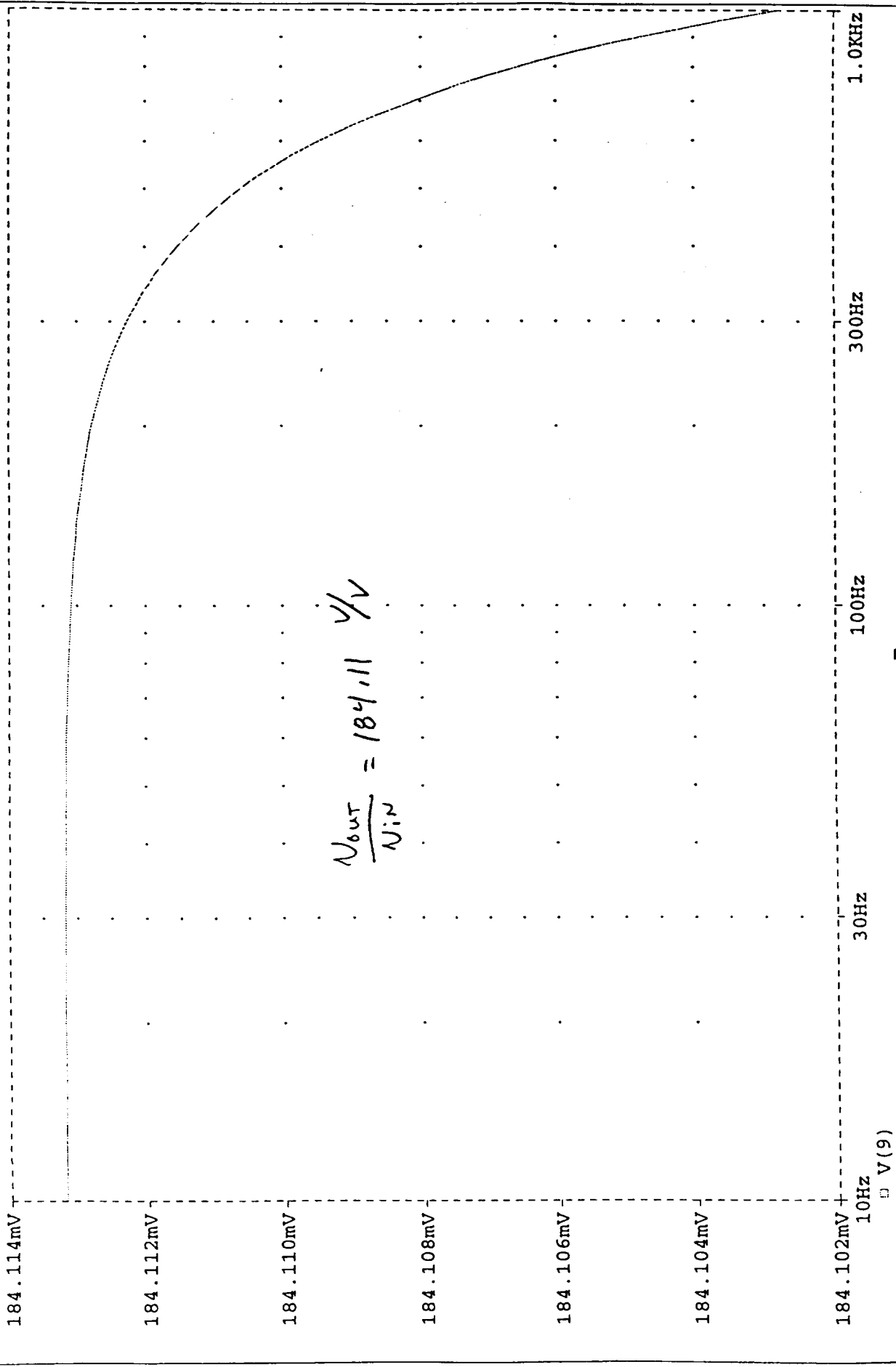

Time: 10:05:14

* Problem 24.6 (Gain simulation for circuit a)

```
R1 10 3 3.8E6
M5 3 3 4 4 CMOSNB L=5U W=15U
M6 5 3 4 4 CMOSNB L=5U W=15U
M1 7 6 5 4 CMOSNB L=5U W=15U
M2 9 0 5 4 CMOSNB L=5U W=15U
M3 7 7 10 10 CMOSPB L=5U W=70U
M4 9 7 10 10 CMOSPB L=5U W=70U
VDD 10 0 DC 2.5
VSS 4 0 DC -2.5
Vin 6 0 DC 0
```

```
* BSIM model for n-channel CN20
.MODEL CMOSNB NMOS LEVEL=4
```

```
* BSIM model for p-channel CN20
.MODEL CMOSPB PMOS LEVEL=4
.probe
.DC Vin -.2 .2 .001
.end
```

* Problem 24.6 (Simulation for CMR of circuit a)

```
R1 10 3 3.8E6
M5 3 3 4 4 CMOSNB L=5U W=15U
M6 5 3 4 4 CMOSNB L=5U W=15U
M1 7 6 5 4 CMOSNB L=5U W=15U
M2 9 6 5 4 CMOSNB L=5U W=15U
M3 7 7 10 10 CMOSPB L=5U W=70U
M4 9 7 10 10 CMOSPB L=5U W=70U
VDD 10 0 DC 2.5
VSS 4 0 DC -2.5
Vin 6 0 DC 0
```


```
* BSIM model for n-channel CN20
.MODEL CMOSNB NMOS LEVEL=4
```

```
* BSIM model for p-channel CN20
.MODEL CMOSPB PMOS LEVEL=4
.probe
.DC Vin -3 3 .01
.end
```

Date/Time run: 03/03/98 16:58:54 * Prob 24.6 (CMR simulation for circuit b)

Temperature: 27.0


(B) A:\246CMRB.DAT

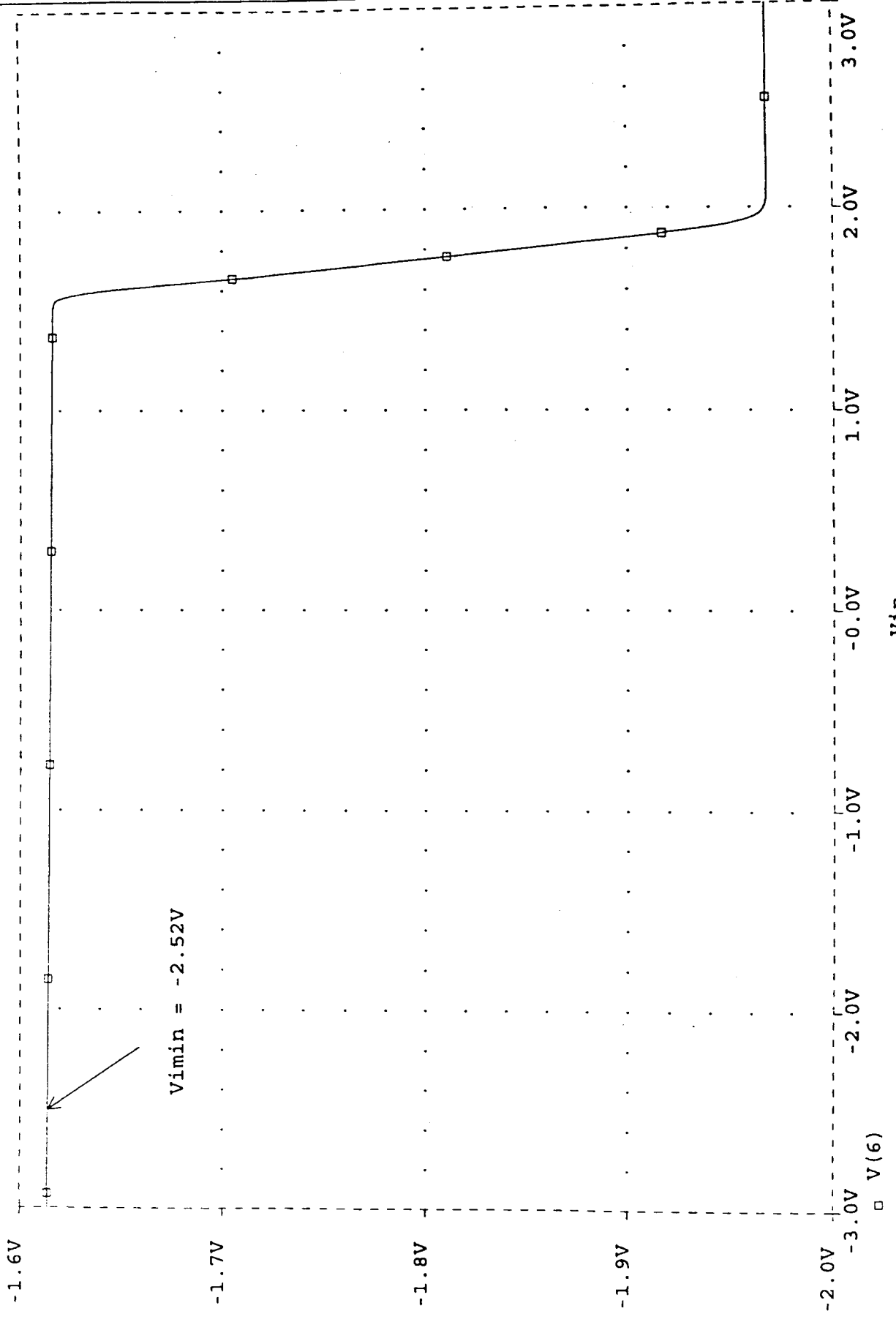

Date/Time run: 03/03/98 16:58:54 * Prob 24.6 (CMR simulation for circuit b)

Temperature: 27.0

(B) A:\246CMRB.DAT

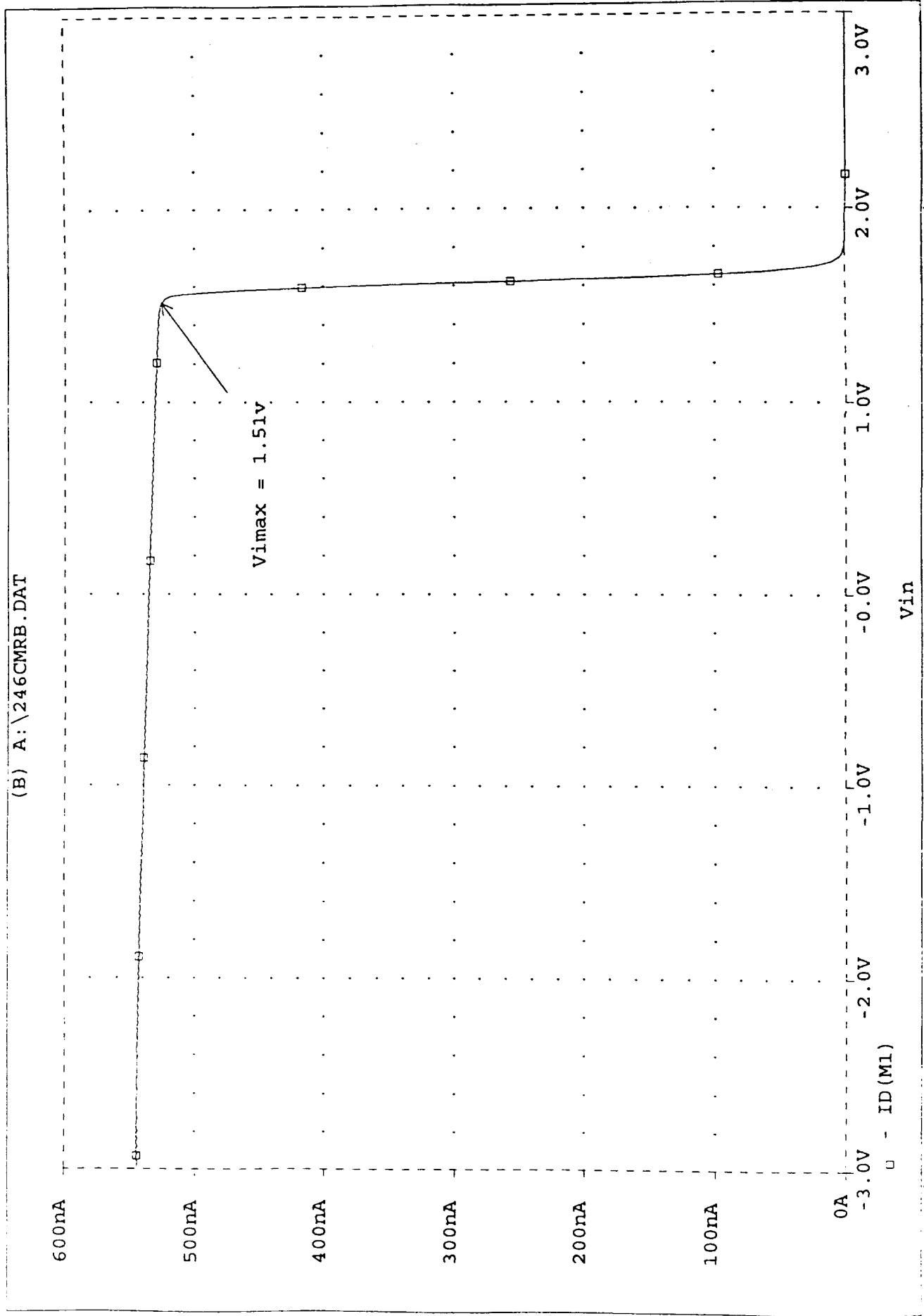


* Prob 24.6 (Gain simulation for circuit b)

Date/Time run: 03/05/98 10:07:15


Temperature: 27.0

(B) 246gainb.dat

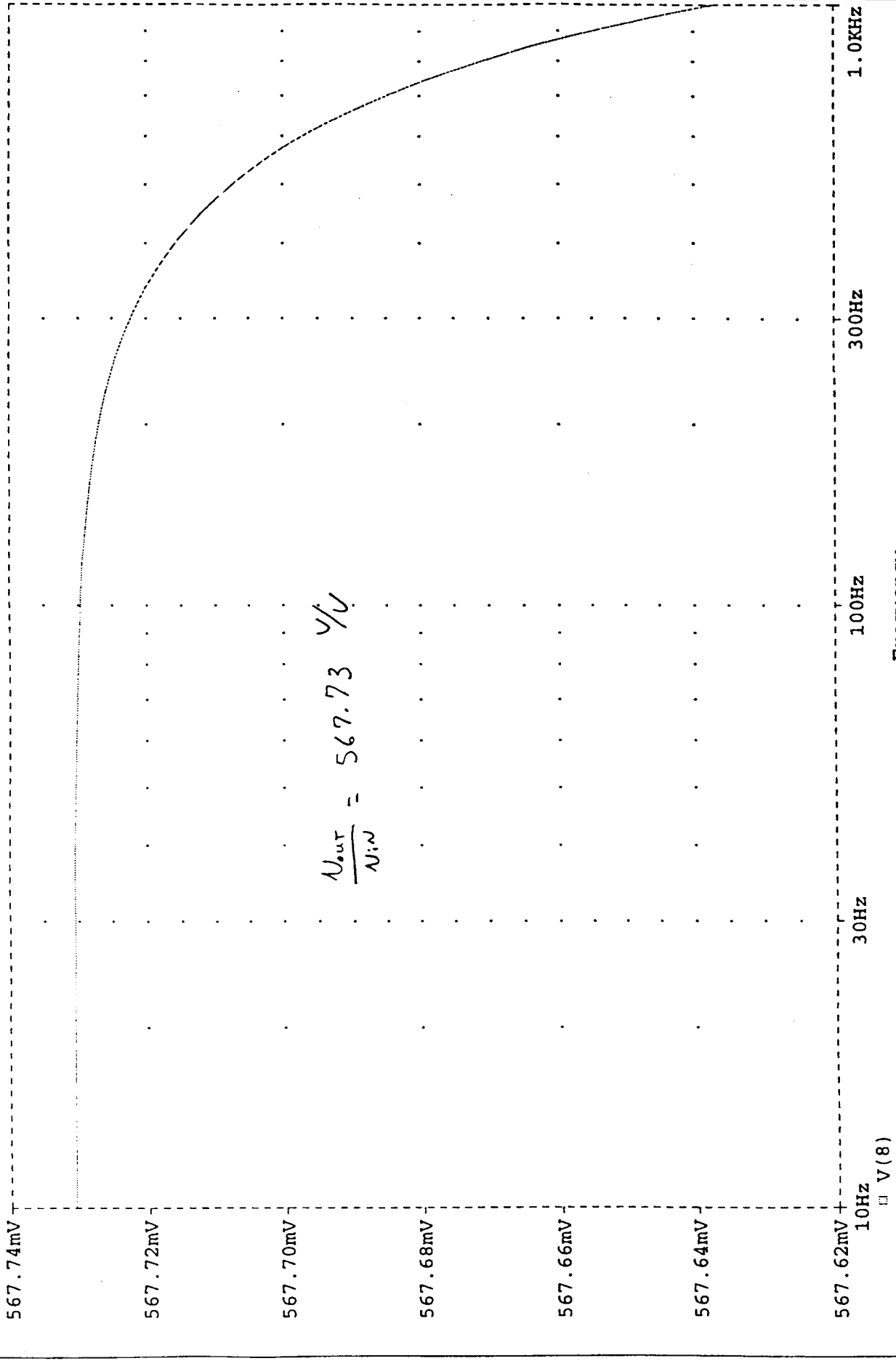

247

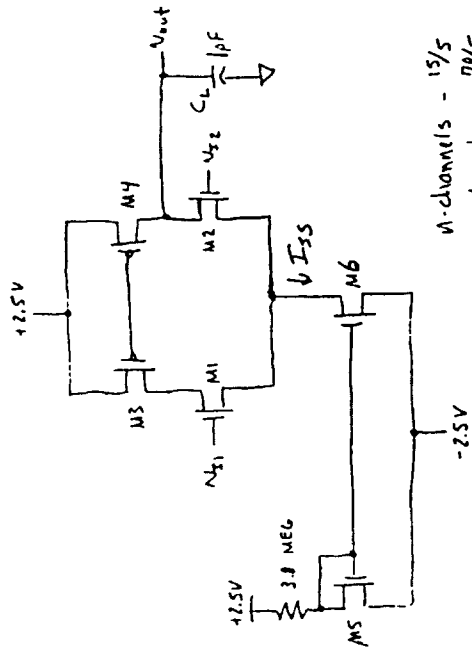Estimate the slew-rate limitations in charging and discharging a 1pF capacitor tied to the outputs of the diffamps shown in Fig. P24.5.



n-channels - 15/5
p-channels - 70/5

$$SR_{MAX} = \frac{dV}{dt} = \frac{I_{SS}}{C_L}$$

$$I_{SS} = \frac{5 - V_{GS5}}{3.8 (10)^6} = \frac{50 \mu A}{2} \frac{15}{5} (V_{GS5} - 0.3)^2$$


$$\frac{5 - V_{GS5}}{285} = V_{GS5}^2 - 1.66 V_{GS5} + 0.6889$$

$$0 = V_{GS5}^2 - 1.6565 V_{GS5} + 0.67136$$

$$V_{GS5} = 0.949 \text{ V}$$

$$I_{SS} = \frac{5 - 0.949}{3.8 (10)^6} = 1.066 \mu A$$
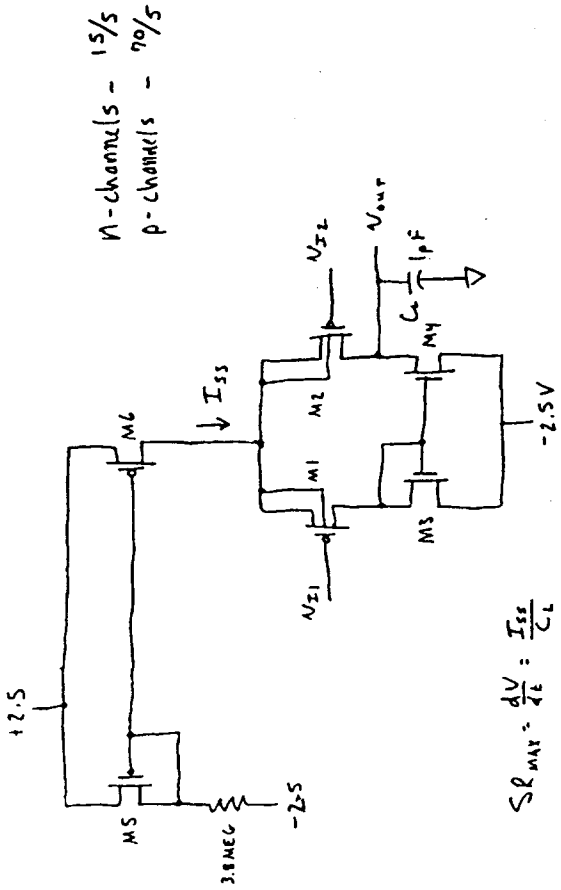
$$SR_{MAX} = \frac{1.066 \mu A}{1 p} = 1.066 \text{ V}/\mu S$$



n-channels - 15/5
p-channels - 70/5

$$SR_{MAX} = \frac{dV}{dt} = \frac{I_{SS}}{C_L}$$

$$I_{SS} = \frac{5 - V_{GS5}}{3.8 (10)^6} = \frac{170 \mu A}{2} \frac{20}{5} (V_{GS5} - 0.91)^2$$

$$\frac{5 - V_{GS5}}{4157.2} = V_{GS5}^2 - 1.82 V_{GS5} + 0.281$$


$$0 = V_{GS5}^2 - 1.8179 V_{GS5} + 0.81704$$

$$V_{GS5} = 1.0046 \text{ V}$$


$$I_{SS} = \frac{5 - 1.0046}{3.8 (10)^6} = 1.051 \mu A$$

$$SR_{MAX} = \frac{1.051 \mu A}{1 p} = 1.051 \text{ V}/\mu S$$

PA.8 ANS:

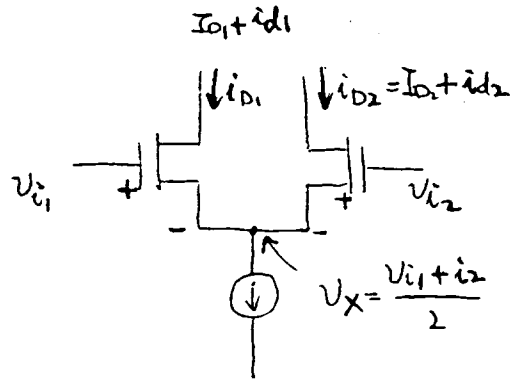

Small signal model:

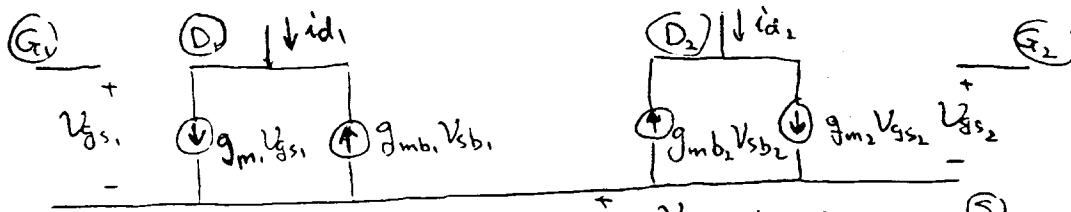

$$v_{gs1} = v_{i1} - v_x = v_{i1} - \frac{v_{i1} + v_{i2}}{2}; \quad v_{gs2} = v_{i2} - v_x = v_{i2} - \frac{v_{i1} + v_{i2}}{2}$$

$$= \frac{v_{i1} - v_{i2}}{2}; \quad = -\frac{v_{i1} - v_{i2}}{2};$$

$$v_{sb1} = v_{sb2} = v_x = \frac{v_{i1} + v_{i2}}{2}$$


$$g_{m1} = g_{m2} = g_m, \quad g_{mb1} = g_{mb2} = g_{mb}$$

$$i_{d1} = g_{m1} v_{gs1} - g_{mb1} v_{sb1} = g_m \frac{v_{i1} - v_{i2}}{2} - g_{mb} \frac{v_{i1} + v_{i2}}{2} = \frac{g_m}{2} (v_{i1} - v_{i2}) - \frac{g_{mb}}{2} (v_{i1} + v_{i2})$$

$$i_{d2} = g_{m2} v_{gs2} - g_{mb2} v_{sb2} = g_m \left(-\frac{v_{i1} - v_{i2}}{2} \right) - g_{mb} \frac{v_{i1} + v_{i2}}{2} = -\frac{g_m}{2} (v_{i1} - v_{i2}) - \frac{g_{mb}}{2} (v_{i1} + v_{i2})$$

249

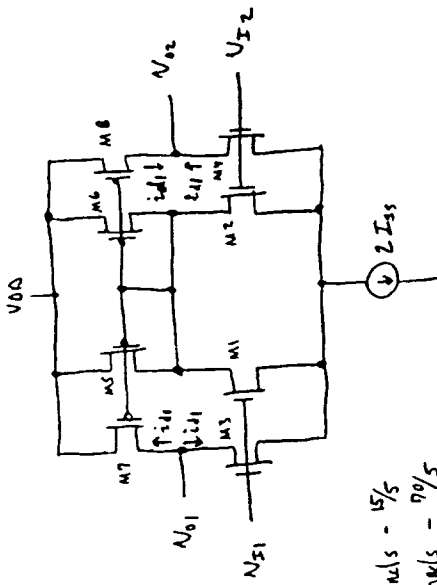The diff-amp configuration shown in Fig. P24.9 is wanted in situations where a truly differential output is needed. Determine the following:



all n-channels - $\frac{1}{5}$
all p-channels - $\frac{2}{5}$

(a) The transconductance of the diff-amp.

$$G_m = \frac{g_{mn}}{4}$$

(b) The drain currents of all MOSFETs in terms of the input voltages and g_{mn} .

$$I_{D1} = g_{mn} V_{GS1} = g_{mn} \frac{V_{I1} - V_{I2}}{2}$$

$$I_{D2} = g_{mn} V_{GS2} = g_{mn} \frac{V_{I2} - V_{I1}}{2}$$

$$I_{D3} = g_{mp} V_{GS3} = g_{mp} \frac{V_{I1} - V_{I2}}{2}$$

$$I_{D4} = g_{mp} V_{GS4} = g_{mp} \frac{V_{I2} - V_{I1}}{2}$$

(c) The small-signal voltage gain, $(V_{O1} - V_{O2}) / (V_{I1} - V_{I2})$

$$V_{O2} = (i_{D1} + i_{D1})(r_{on1} || r_{op})$$

$$V_{O1} = -(i_{D1} + i_{D1})(r_{on1} || r_{op})$$

$$I_{D1} = g_{mn} V_{GS1} = g_{mn} \frac{V_{I1} - V_{I2}}{2}$$

$$V_{O2} = g_{mn} (V_{I1} - V_{I2}) (r_{on1} || r_{op})$$

$$V_{O1} = -g_{mn} (V_{I1} - V_{I2}) (r_{on1} || r_{op})$$


$$\frac{V_{O1} - V_{O2}}{V_{I1} - V_{I2}} = -2 \frac{g_{mn} (r_{on1} || r_{op})}{1}$$

P24.10

Now. $R_{out} = r_{o5} (1 + g_{m5} r_{o6})$

replace r_{o6} by R_{out} in equ. (24.36)

$$CMRR \approx 20 \log \left| \frac{2g_{m1}g_{m4} (r_{o2} \parallel r_{o4})}{r_{o5} (1 + g_{m5} r_{o6})} \right|$$

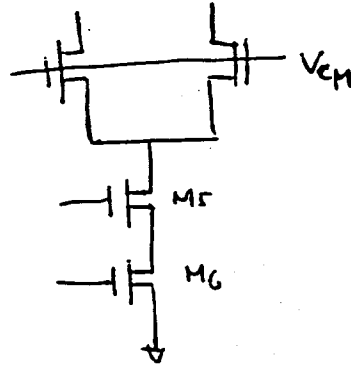

Problem 24.11

\therefore Current source output impedance can be modeled by a simple capacitor,

Assume $R_{out} = \frac{1}{C_{out} \cdot s}$, where R_{out} is the output impedance of the current source.


$$A_v = g_{m1} (r_{o2} \parallel r_{o4}), \quad A_c = - \frac{1}{2g_{m4} \frac{1}{C_{out} \cdot s}} = - \frac{C_{out} \cdot s}{2g_{m4}}$$

$$\Rightarrow CMRR = 20 \log \left| \frac{A_v}{A_c} \right| = 20 \log \left| \frac{2g_{m1}g_{m4} (r_{o2} \parallel r_{o4})}{C_{out} \cdot s} \right|$$

$$\Rightarrow CMRR(j\omega) = 20 \log \left| \frac{2g_{m1}g_{m4} (r_{o2} \parallel r_{o4})}{C_{out} \cdot j\omega} \right|$$

24/2

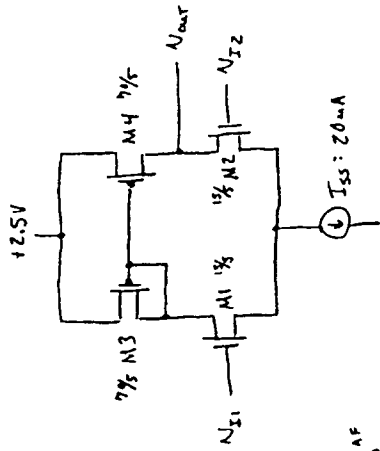Determine the RMS input noise voltage for the diff-amp of Ex. 24.2 over a bandwidth of 1 to 1 MHz. Assume $KF = 10^{-25} V^2/F$ and $AF = 1.3$.



$$\overline{V_{in}^2} = \overline{V_{Therm}^2} + \overline{V_c^2}$$

$$= 6kT \sqrt{2\beta I_0} + \frac{KF \cdot I_0^{AF}}{f \cdot C_m \cdot L^2}$$

$$K = 1.38 \cdot 10^{-23}$$

$$T = 300 \text{ °K}$$

$$= 6(1.38 \cdot 10^{-23})(300) \sqrt{2(50 \cdot 10^{-18})(10 \mu)} + \frac{(10^{-25})(10 \mu)^{1.3}}{f \cdot 800(10^{-18}) \cdot (5)^2}$$

$$= 1.3605 \cdot (10)^{-24} + \frac{1.5811(10)^{-18}}{f}$$

$$\overline{V_{NE}^2} = \overline{V_{n1}^2} = 1.3605(10)^{-24} + \frac{1.5811(10)^{-18}}{f}$$

$$\overline{V_{n3}^2} = \overline{V_{Therm}^2} + \overline{V_c^2}$$

$$= 6(1.38 \cdot 10^{-23})(300) \sqrt{2(50 \mu)(\frac{20}{3})(10 \mu)} + \frac{(10^{-25})(10 \mu)^{1.3}}{f \cdot 800(10^{-18}) \cdot (5)^2}$$

$$= 2.939 \cdot (10)^{-24} + \frac{1.5811(10)^{-18}}{f}$$

$$\overline{V_{n7}^2} = \overline{V_{n3}^2} = 2.939(10)^{-24} + \frac{1.5811(10)^{-18}}{f}$$

$$\overline{V_{out}^2} = \int_{f_c}^{f_H} \frac{1}{f} (\overline{V_{n1}^2} + \overline{V_{n2}^2} + \overline{V_{n3}^2} + \overline{V_{n4}^2}) df$$

$$g_{mi}^2 = 2\beta I_0 = 2(50 \mu)(\frac{5}{3})(10 \mu) = 3 \cdot (10)^{-9} \frac{A^2}{V^2}$$

$$\overline{V_{out}^2} = \int_{f_c}^{f_H} \frac{1}{3 \cdot 10^{-9}} \left(8.69 \cdot (10)^{-24} + \frac{6.324 \cdot (10)^{-18}}{f} \right) df$$

$$= 2.90 \cdot (10)^{-15} (1000 - 1) + 2.108(10)^{-11} [\ln(1000) - \ln(1)] V^2$$

$$= 14.57 \text{ nV}^2$$

$$\sqrt{\overline{V_{out}^2}} = 0.121 \text{ mV}$$

24.13

Verify the calculated noise voltage determined in Problem 24.12 with SPICE simulation results.

$$20\mu A = \frac{50}{2} \frac{15}{3} (V_{GS} - 0.3)^2$$


$$0.2667 = V_{GS}^2 - 1.66 V_{GS} + 0.689$$

$$0 = V_{GS}^2 - 1.66 V_{GS} + 0.4222$$

$$V_{GS} = 1.35 V$$

$$20\mu A = \frac{5 - 1.35 V}{R}$$

$$R = 182.5 \text{ k}\Omega$$

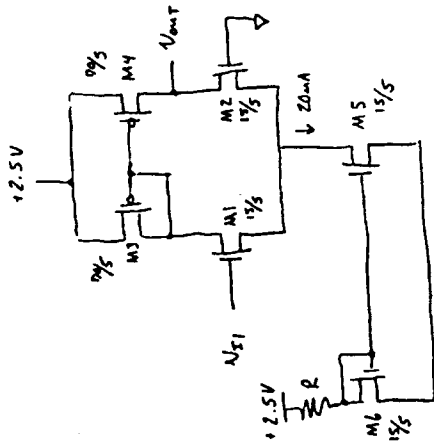

• Problem 24.13 - Noise verification of Problem 24.12

```

.noise v(3,0) vin
.ac dec 100 1 1k
M1 2 4 5 7 CHOSNB L=5u W=15u
M2 3 0 5 7 CHOSNB L=5u W=15u
M3 2 2 1 1 CHOSPB L=5u W=70u
M4 3 2 1 1 CHOSPB L=5u W=70u
M5 5 6 7 7 CHOSNB L=5u W=15u
M6 6 6 7 7 CHOSNB L=5u W=15u
R1 1 6 182.5k
VDD 1 0 dc 2.5v
VSS 7 0 dc -2.5v
vin 4 0 ac 1v

* BSIM model for n-channel CN20
.MODEL CHOSNB NMOS LEVEL=4
AF=1.3 KP=1E-25

* BSIM model for p-channel CN20
.MODEL CHOSPB PMOS LEVEL=4
AF=1.3, KP=1E-25

.probe
.end

```

Problem 24.14

For both n and p channels are of size of $100\mu/5\mu$, we have

$$I_{SS} = 10\mu A = \frac{50\mu A/V^2 \times 100}{2 \times 5} (V_{GSN} - 0.83)^2$$

$$\Rightarrow V_{GSN} = 0.97 V$$


$$I_{SS} = 10\mu A = \frac{17\mu A/V^2 \times 100}{2 \times 5} (V_{SGP} - 0.91)^2$$

$$\Rightarrow V_{SGP} = 1.15 V$$

$$\therefore |V_{DMIN}| = -0.97 V - 1.15 V + 0.91 V + 0.83 V = \underline{\underline{-380 mV}}$$

See next page for SPICE simulation.

Problem 24.14 (Simulation)

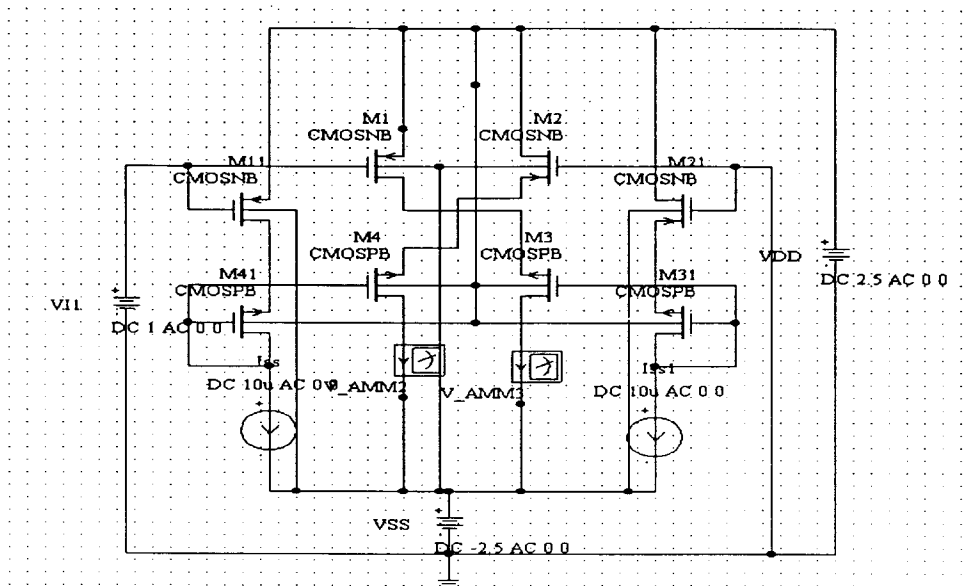

*** Top Level Netlist ***

```

Iss      7 3    DC 10u AC 0 0
Iss1     6 3    DC 10u AC 0 0
M1       1 2 12 3 CMOSNB L=5u W=100u
M11      8 2 12 3 CMOSNB L=5u W=100u
M2       12 0 5 3 CMOSNB L=5u W=100u
M21      12 0 9 3 CMOSNB L=5u W=100u
M3       11 6 1 12 CMOSPFB L=5u W=100u
M31      6 6 9 12 CMOSPFB L=5u W=100u
M4       10 7 5 12 CMOSPFB L=5u W=100u
M41      7 7 8 12 CMOSPFB L=5u W=100u
V_AMM2   10 3 0V
V_AMM3   11 3 0V
VDD      12 0   DC 2.5 AC 0 0
VI1      2 0    DC 1 AC 0 0
VSS      3 0    DC -2.5 AC 0 0

```

***** Spice models and macro models *****


```
.MODEL CMOSNB NMOS LEVEL=4
```


```
.MODEL CMOSPFB PMOS LEVEL=4
```

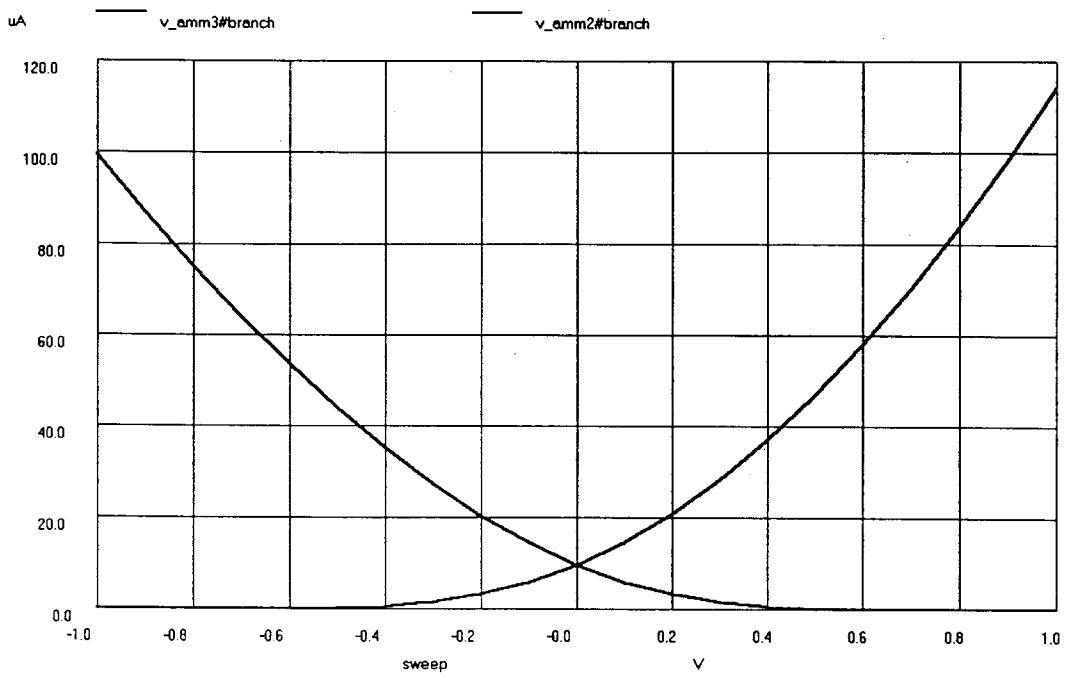***** End of spice models and macro models *****

```
.DC VI1 -1 1 .1
.end
```


The SPICE simulation result is shown below:



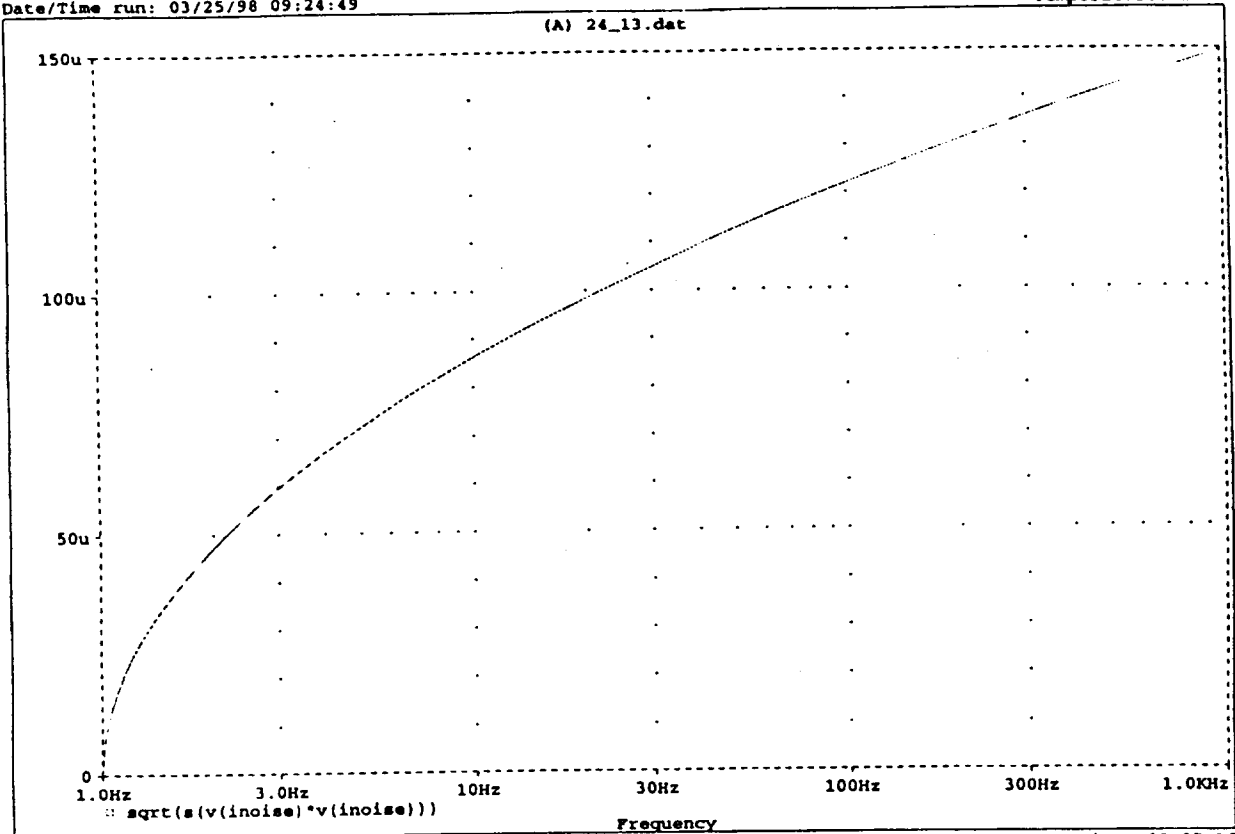

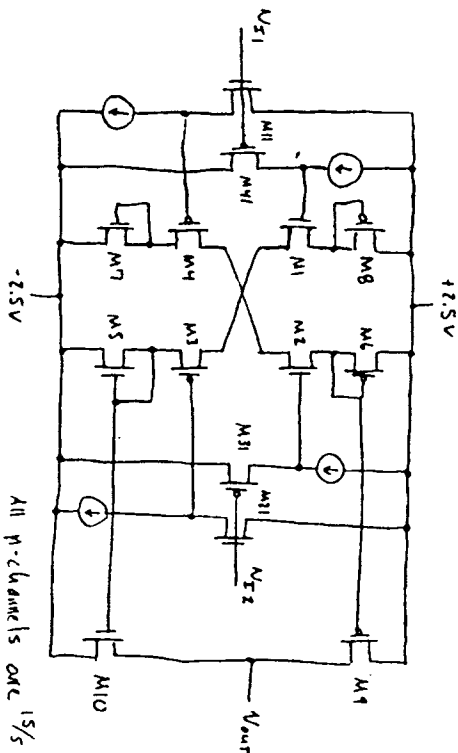24.15


Determine the small signal gain of the amplifier shown in Fig. P24.15. Also determine the input CMR of the amplifier if the minimum voltage across a current source/sink is 0.3V.



Use superposition to find the gain
 If $V_{S2} = 0$, $\frac{V_{out}}{V_{S1}}$ for the 1st path is:
 All n-channels are $15/5$
 All p-channels are $7/5$
 The current sources/sinks are 10 μ A.

$$\frac{V_{O1}}{V_{I1}} \approx 1$$
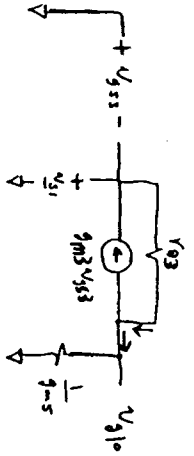
$$\frac{V_{S1}}{V_{O1}} = \frac{g_{m1} \frac{1}{g_{m1}}}{1 + g_{m1} \frac{1}{g_{m1}}}$$



$$V_{S1} = (V_{S10} g_{m3} + g_{m3} V_{S10}) r_{o3} + V_{S10}$$

$$V_{S1} \approx -V_{S3}$$

$$V_{S1} = V_{S10} (1 + g_{m3} r_{o3}) - g_{m3} r_{o3} V_{S1}$$

$$\frac{V_{S10}}{V_{S1}} = \frac{1 + g_{m3} r_{o3}}{1 + g_{m3} r_{o3}} \approx \frac{g_{m3}}{g_{m3}}$$

$$\frac{V_{out}}{V_{S10}} = -g_{m3} (r_{o3} \parallel r_{in})$$

∴ When $V_{S2} = 0$, $\frac{V_{out}}{V_{S1}}$ for the 1st path is

$$\left(\frac{V_{out}}{V_{S1}} \right)_1 = \frac{V_{S1}}{V_{S1}} \cdot \frac{V_{S1}}{V_{S1}} \cdot \frac{V_{S10}}{V_{S1}} \cdot \frac{V_{out}}{V_{S10}}$$

$$= \left[\frac{g_{m1} g_{m3}}{1 + g_{m1} \frac{r_{o1}}{g_{m1}}} \right] \cdot \left[\frac{g_{m3}}{g_{m3}} \right] \cdot \left[-g_{m3} (r_{o3} \parallel r_{in}) \right]$$

Find $\frac{V_{out}}{V_{S1}}$ when $V_{S2} = 0$ for the 2nd path:

$$\frac{V_{S1}}{V_{S1}} \approx 1$$

$$\frac{V_{S1}}{V_{S1}} = \frac{g_{m1} \frac{r_{o1}}{g_{m1}}}{1 + g_{m1} \frac{r_{o1}}{g_{m1}}}$$

$$\frac{V_{S1}}{V_{S1}} \approx \frac{g_{m1}}{g_{m2}}$$

$$\frac{V_{out}}{V_{S1}} = -g_{m1} (r_{o1} \parallel r_{in})$$

∴ When $V_{S2} = 0$, $\frac{V_{out}}{V_{S1}}$ for the 2nd path is

$$\left(\frac{V_{out}}{V_{S1}} \right)_2 = \frac{V_{S1}}{V_{S1}} \cdot \frac{V_{S1}}{V_{S1}} \cdot \frac{V_{S1}}{V_{S1}} \cdot \frac{V_{out}}{V_{S1}}$$

$$= \left[\frac{g_{m1} g_{m2}}{1 + g_{m1} \frac{r_{o1}}{g_{m1}}} \right] \cdot \left[\frac{g_{m2}}{g_{m2}} \right] \cdot \left[-g_{m1} (r_{o1} \parallel r_{in}) \right]$$

Since $g_{m1} \approx g_{m2}$

$$\frac{V_{out}}{V_{S1}} = \left(\frac{V_{out}}{V_{S1}} \right)_1 + \left(\frac{V_{out}}{V_{S1}} \right)_2 = -g_{m1} (r_{o1} \parallel r_{in})$$

First Find $\frac{V_{out}}{V_{S2}}$ when $V_{S1} = 0$ for the 1st path

$$\frac{V_{S1}}{V_{S2}} = \frac{g_{m1} r_{o1}}{1 + g_{m1} r_{o1}} \approx 1$$

$$\frac{V_{S10}}{V_{S2}} = \frac{-g_{m3} \frac{r_{o3}}{g_{m3}}}{1 + g_{m3} \frac{r_{o3}}{g_{m3}}}$$

$$\frac{V_{out}}{V_{S10}} = -g_{m3} (r_{o3} \parallel r_{in})$$

∴ When $V_{S1} = 0$, $\frac{V_{out}}{V_{S2}}$ for the 1st path is

$$\left(\frac{V_{out}}{V_{S2}} \right)_1 = \frac{V_{S1}}{V_{S2}} \cdot \frac{V_{S10}}{V_{S2}} \cdot \frac{V_{out}}{V_{S10}}$$

$$\begin{pmatrix} V_{out} \\ V_{z2,1} \end{pmatrix} = \begin{bmatrix} -g_{m3} \left(\frac{1}{g_{m5}} \right) \\ 1 + g_{m3} \frac{1}{g_{m1}} \end{bmatrix} \begin{bmatrix} -g_{m2} (r_{o11} || r_{o10}) \end{bmatrix}$$

Find $\frac{V_{out}}{V_{z2}}$ when $V_{z1} = 0$ for the 2nd path

$$\frac{V_{z1}}{V_{z2}} \approx 1$$

$$\frac{V_{z1}}{V_{z2}} = \frac{-g_{m2} \frac{1}{g_{m5}}}{1 + g_{m3} \frac{1}{g_{m1}}}$$

$$\frac{V_{out}}{V_{z1}} \approx -g_{m2} (r_{o11} || r_{o10})$$

∴ When $V_{z1} = 0$, $\frac{V_{out}}{V_{z2}}$ for the 2nd path is

$$\left(\frac{V_{out}}{V_{z2}} \right)_2 = \frac{V_{z1}}{V_{z2}} \cdot \frac{V_{z1}}{V_{z2}} \cdot \frac{V_{out}}{V_{z1}}$$

$$= \left[\frac{-g_{m2} \frac{1}{g_{m5}}}{1 + g_{m3} \frac{1}{g_{m1}}} \right] \left[-g_{m2} (r_{o11} || r_{o10}) \right]$$

So if $g_{m3} \approx g_{m1}$

$$\frac{V_{out}}{V_{z2}} \approx \left(\frac{V_{z1}}{V_{z2}} \right)_1 + \left(\frac{V_{out}}{V_{z2}} \right)_2 = \frac{g_{m2} (r_{o11} || r_{o10})}{2}$$

$$\frac{V_{out}}{V_{z1} - V_{z2}} \approx -\frac{g_{m2} (r_{o11} || r_{o10})}{2} \quad g_{m2} = \sqrt{2(50\mu A)(\frac{15}{2})} (10\mu A) = 57.8 \mu A/V$$

$$\approx -46.5 \mu V$$

Determine the CMR

For M11 + M41:

$$V_{in,CM} = V_{GS11} + .3 + V_{SS}$$

$$= \sqrt{\frac{2I_D}{\beta_1}} + V_{TH11} + .3 + V_{SS}$$

$$= \sqrt{\frac{2(10\mu A)}{50\mu A(\frac{1}{2})}} + .83 + .3 - 2.5$$

$$= -1.0 V$$

$$V_{I,CM,AV} = -V_{GS411} - .3 + V_{DD}$$

$$= -\sqrt{\frac{2I_D}{\beta_4}} - V_{TH41} - .3 + V_{DD}$$

$$= -\sqrt{\frac{2(10\mu A)}{10\mu A(\frac{1}{2})}} - .91 - .3 + 2.5$$

$$= 1.0 V$$

P24.16. 1) DC Biasing same as in P24.15

$I_{SS} = 10 \mu A$ through all MOSFETs.

2) AC gain expression are same

$$\frac{V_{out}}{V_{i1} - V_{i2}} = - \frac{2(R_{oq} \parallel R_{o10})}{\frac{1}{g_{m1}} + \frac{1}{g_{m3}}}$$


but $R_{oq} = r_{op} (1 + g_{mp} r_{op}) \approx g_{mp} r_{op}^2 = 68.99 \times 1.67^2 = 192.4 \mu\Omega$

$R_{o10} = r_{on} (1 + g_{mn} r_{on}) \approx g_{mn} r_{on}^2 = 54.77 \times 1.67^2 = 152.8 \mu\Omega$

$$\frac{V_{out}}{V_{i1} - V_{i2}} = - \frac{2(152.8 \parallel 192.4)}{\frac{1}{54.77} + \frac{1}{68.99}} \approx \boxed{-5200 \text{ V/V}}$$


($r_{on} = r_{op} = \frac{1}{0.06 \times 10^{-4}} = 1.67 \mu$)

3)

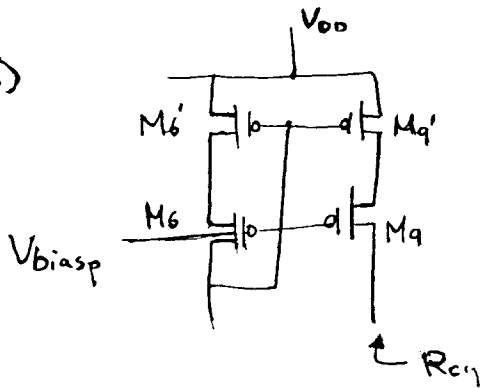

$$V_{bias,p} = V_{DD} - V_{DSq'_{sat}} - V_{SSq} = 2.5 - (1.2 - 0.916) - 1.2 \approx 1V$$
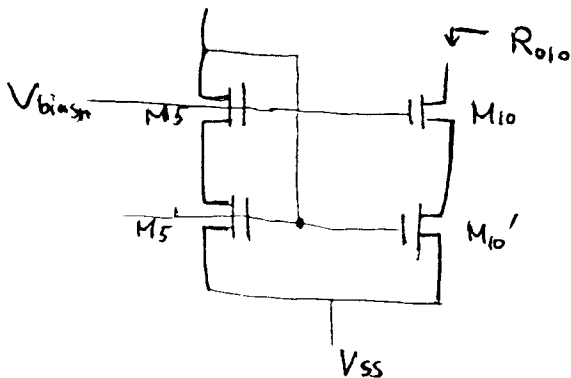
$$V_{bias,n} = V_{GS10} + V_{DS10'_{sat}} + V_{SS} = 1.2 + (1.2 - 0.83) - 2 = -0.93V$$



CMR same as $(-1V \sim 1V)$

Problem 24.17

$$\frac{I_{SS}}{2} = 1\mu A = \frac{\beta_{C1}}{2} (V_{GS1(c1)} - V_{THW})^2 = \frac{50\mu A/V^2 \times \frac{15}{5}}{2} \times (V_{GS1(c1)} - 0.83)^2$$

$$\Rightarrow V_{GS1} = V_{GS2} \approx 0.95 \text{ (V)}$$

\therefore The minimum voltage of V_{GSC6} is $V_{GS1} + V_{DS,sat} \approx 0.95V + 0.12V = 1.07V$

Design $I_{BIAS} = 1\mu A$, for M_{C6} , we have

$$1\mu A = \frac{50\mu A/V^2 \times W_{C6}}{2 \times L_{C6}} \times (1.07 - 0.83)^2 \Rightarrow \frac{W_{C6}}{L_{C6}} \approx 0.694$$

$$\text{Set } \underline{L_{C6} = 10\mu m}, \underline{W_{C6} = 7\mu m}$$

Assume $1\mu A$ current flowing through $M5$ ($15/5$) ($R = 9.05M$)

We can set $M_{B3} = M_{B1}$ ($15/5$) and $M_6 = 3M_{B1}$ ($45/5$)

All the remaining MOSFETs still use the size of Fig 24.25.


$$A_v = g_{m1} (g_{m2} r_{o2}^2 \parallel g_{m4} r_{o4}^2) = 17.32\mu A/V \times (17.32\mu A/V \times (16.6M)^2 \parallel 21.82\mu A/V \times (16.6M)^2)$$

$$\approx \underline{\underline{46473 \text{ (V/V)}}}$$

$$V_{INMIN} = 0.115V + 0.115V + 0.83V - 5V = \underline{\underline{-3.94(V)}}$$

$$V_{INMAX} = 5V - 0.115V - 0.092V - 0.092V + 0.4V - 2 \times 0.91V + 0.83V = \underline{\underline{4.11(V)}}$$

Problem 24.19

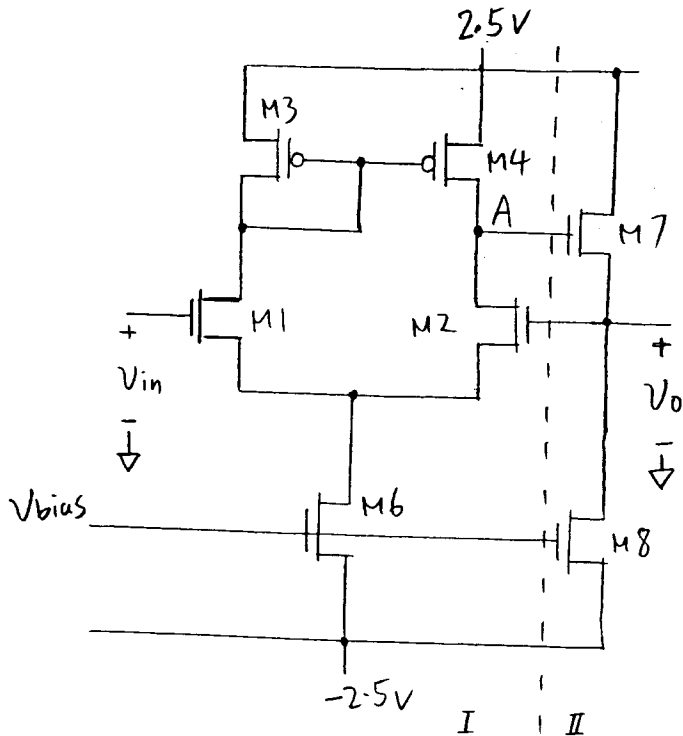

For the dif-amp stage,

$$V_{out} = V_A = g_{m1,2} (r_{o2} \parallel r_{o4}) (V_{in} - V_A)$$

For the second stage, which is a voltage follower,

$$V_o \approx V_A.$$


$$\therefore V_o = V_A = g_{m1,2} (r_{o2} \parallel r_{o4}) (V_{in} - V_o)$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{g_{m1,2} (r_{o2} \parallel r_{o4})}{1 + g_{m1,2} (r_{o2} \parallel r_{o4})} \approx 1.$$

Problem 24.20

If the common mode input voltage becomes large enough to shut the P-channel diff-pair off, the MOSFETs M3 and M4 are also off, causing the current in M5 to become I_o and current in M6 become $3I_o$. The circuit thus remains a constant g_m . Similarly, when n-channel diff-pair off, M3 and M4 are off, causing $3I_o$ flowing through M7 and keeping the transconductance a constant.

Problem 24.21

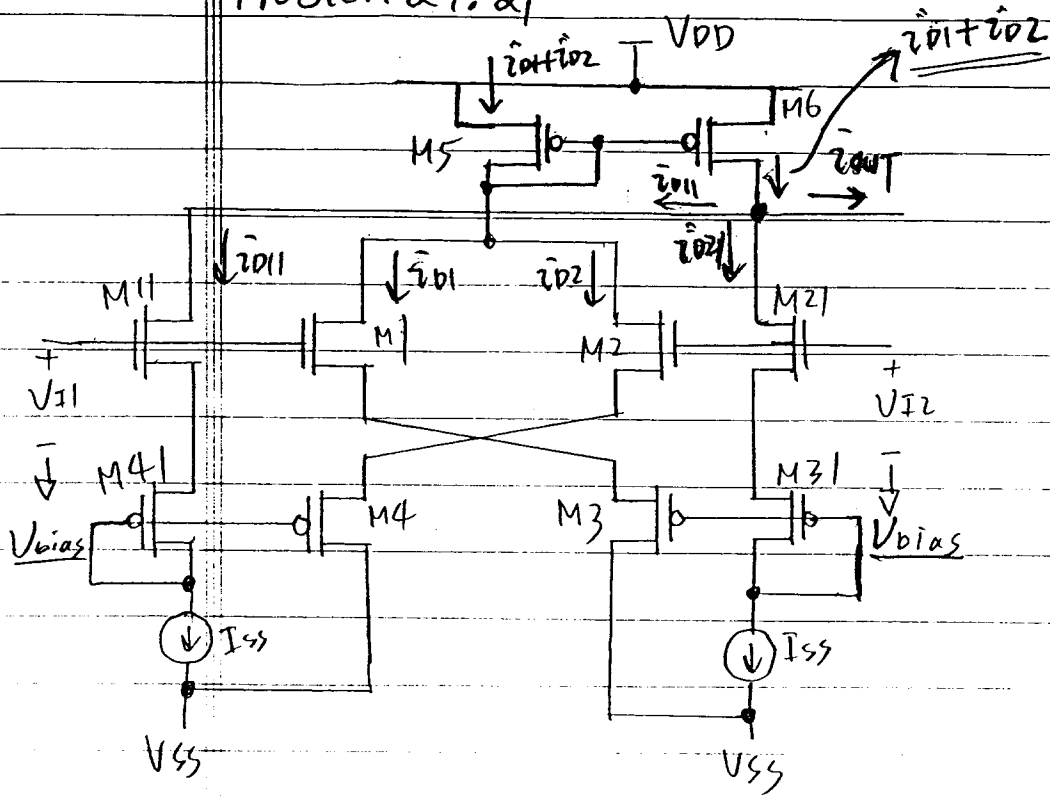

For the output node, using KCL, we have

$$\underline{i_{OUT} = (i_{D1} + i_{D2}) - (i_{D11} + i_{D21})} \quad (I_{D5} = I_{D6} = i_{D1} + i_{D2})$$

$$\begin{cases} i_{D1} = \frac{1}{2} (V_{DI} - V_{bias} - V_{THP} - V_{THN})^2 \cdot \frac{\beta_1 \beta_3}{(\sqrt{\beta_1} + \sqrt{\beta_3})^2} \\ i_{D2} = \frac{1}{2} (-V_{DI} - V_{bias} - V_{THP} - V_{THN})^2 \cdot \frac{\beta_2 \beta_4}{(\sqrt{\beta_2} + \sqrt{\beta_4})^2} \end{cases}$$

$V_{DI} = V_{I1} - V_{I2}$

Assume $\beta_1 = \beta_2, \beta_3 = \beta_4$, (1) + (2) \Rightarrow

$$\underline{i_{D1} + i_{D2} = \frac{\beta_1 \beta_3}{(\sqrt{\beta_1} + \sqrt{\beta_3})^2} \left[V_{DI}^2 + (V_{bias} + V_{THP} + V_{THN})^2 \right]}$$

$$i_{D11} + i_{D21} = I_{SS} + I_{SS} = 2 I_{SS}$$

Now determine the I_{SS} :

Problem 24.21 (cont.)

determine I_{SS} :

When V_{I2} grounded ($V_{I2} = 0$), we have

$$V_{I2} = 0 = V_{GS21} + V_{SG31} + V_{bias}$$

$$= \sqrt{\frac{2I_{SS}}{\beta_{21}}} + V_{THN} + \sqrt{\frac{2I_{SS}}{\beta_{31}}} + V_{THP} + V_{bias} \dots$$

$$(4) \Rightarrow I_{SS} = \frac{(V_{THN} + V_{THP} + V_{bias})^2}{2 \left(\frac{1}{\sqrt{\beta_{21}}} + \frac{1}{\sqrt{\beta_{31}}} \right)^2} = \frac{(V_{THN} + V_{THP} + V_{bias})^2 \beta_{21} \beta_{31}}{2 (\sqrt{\beta_{21}} + \sqrt{\beta_{31}})^2}$$

$$\therefore i_{OUT} = (i_{O1} + i_{O2}) - (i_{O11} + i_{O21}) = (i_{O1} + i_{O2}) - 2I_{SS}$$

$$= \frac{\beta_1 \beta_3}{(\sqrt{\beta_1} + \sqrt{\beta_3})^2} \left[V_{DI}^2 + (V_{bias} + V_{THP} + V_{THN})^2 \right] - \frac{\beta_{21} \beta_{31}}{(\sqrt{\beta_{21}} + \sqrt{\beta_{31}})^2} (V_{THN} + V_{THP} + V_{bias})^2$$

If $\beta_{21} = \beta_2 = \beta_1$; and $\beta_{31} = \beta_3 = \beta_4$ (all matched)

Then we have

$$i_{OUT} = \frac{\beta_1 \beta_3}{(\sqrt{\beta_1} + \sqrt{\beta_3})^2} V_{DI}^2 = \frac{\beta_1 \beta_3}{(\sqrt{\beta_1} + \sqrt{\beta_3})^2} (V_{I1} - V_{I2})^2$$