




CHAPTER 7

Differential and Multistage Amplifiers

Outline


- The MOS Differential Pair
- Small-Signal Operation of the MOS Differential Pair
- The BJT Differential Pair
- Other Nonideal Characteristics of the Differential Amplifier
- The Differential Amplifier with Active Load
- **Frequency Response of the Differential Amplifier**
- Multistage Amplifiers

High CMRR at Higher Frequencies

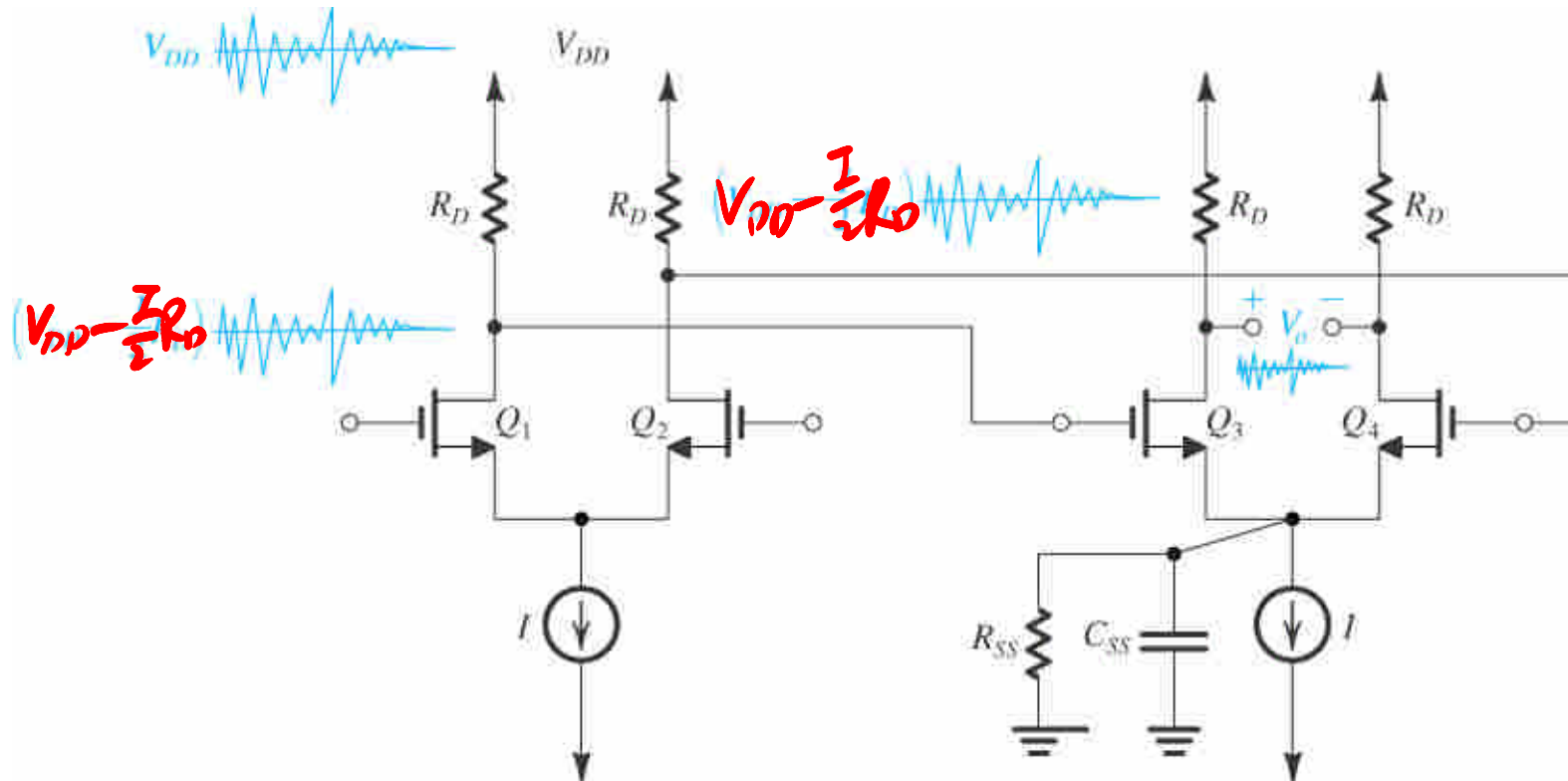

Active-Loaded MOS Amplifier
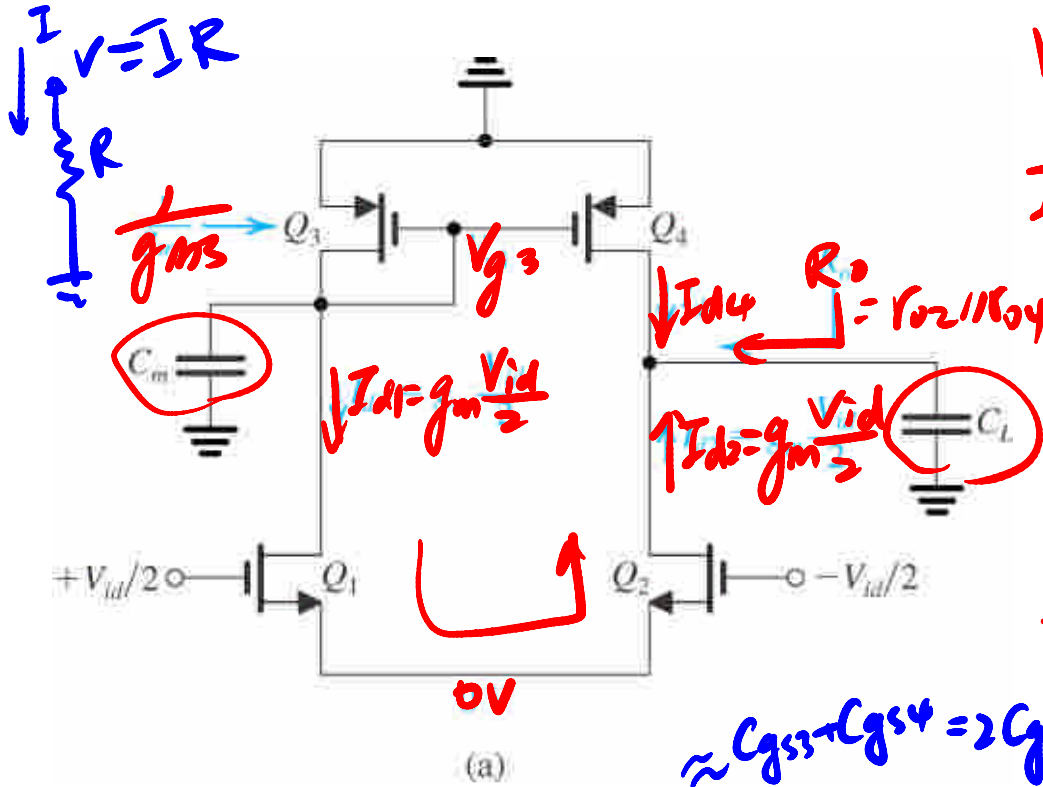
$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gs'})} \approx \frac{g_m}{2\pi C_{gs}}$$



$$V_{g3} = -g_{m3} \frac{V_{id}}{2} \cdot \frac{1}{g_{m3} + sC_m}$$

$$I_{d4} = -g_{m4} V_{g3} = \frac{g_{m3} \frac{V_{id}}{2}}{1 + s \frac{C_m}{g_{m3}}}$$

$$f_{p2} = \frac{g_{m3}}{2\pi \cdot (2C_{gs})} = \frac{f_T}{2}$$

$$I_o = I_{d2} + I_{d4} = g_{m3} \frac{V_{id}}{2} + \frac{g_{m3} \frac{V_{id}}{2}}{1 + s \frac{C_m}{g_{m3}}}$$

$$C_m = C_{gd1} + C_{db1} + C_{db3} + C_{gs3} + C_{gs4}$$

$$C_L = C_{gd2} + C_{db2} + C_{gd4} + C_{db4} + C_x$$



$$f_{p1} = \frac{1}{2\pi C_L R_o}, \quad f_{p2} = \frac{g_{m3}}{2\pi C_m}$$

$$V_o = I_o \cdot \frac{1}{\frac{1}{R_o} + sC_L}$$

$$A_{d1} = \frac{V_o}{V_{id}} = (g_{m3} R_o) \left(\frac{1}{1 + sC_L R_o} \right) \left(\frac{1 + s \frac{C_m}{2g_{m3}}}{1 + s \frac{C_m}{g_{m3}}} \right)$$


$$f_{z1} = \frac{2g_{m3}}{2\pi C_m}, \quad f_{z2} = \frac{1}{2\pi C_m} \cdot \frac{1}{f_{p1}} \cdot \frac{1}{f_{p2}}$$

C_m on Transconductance G_m

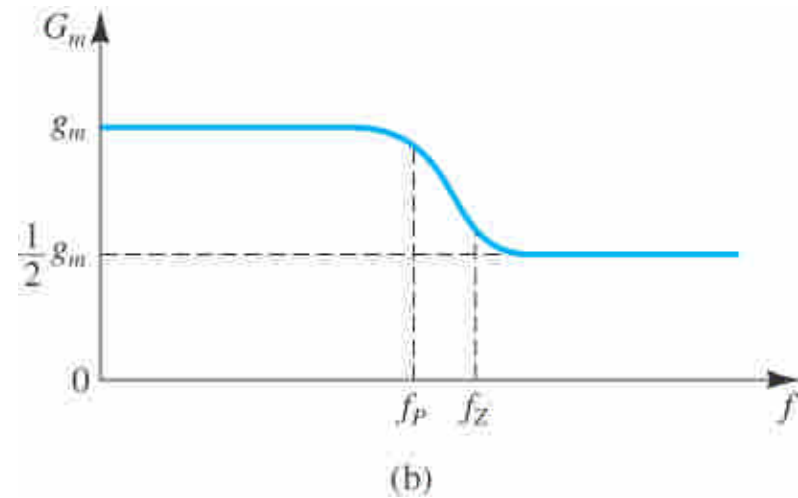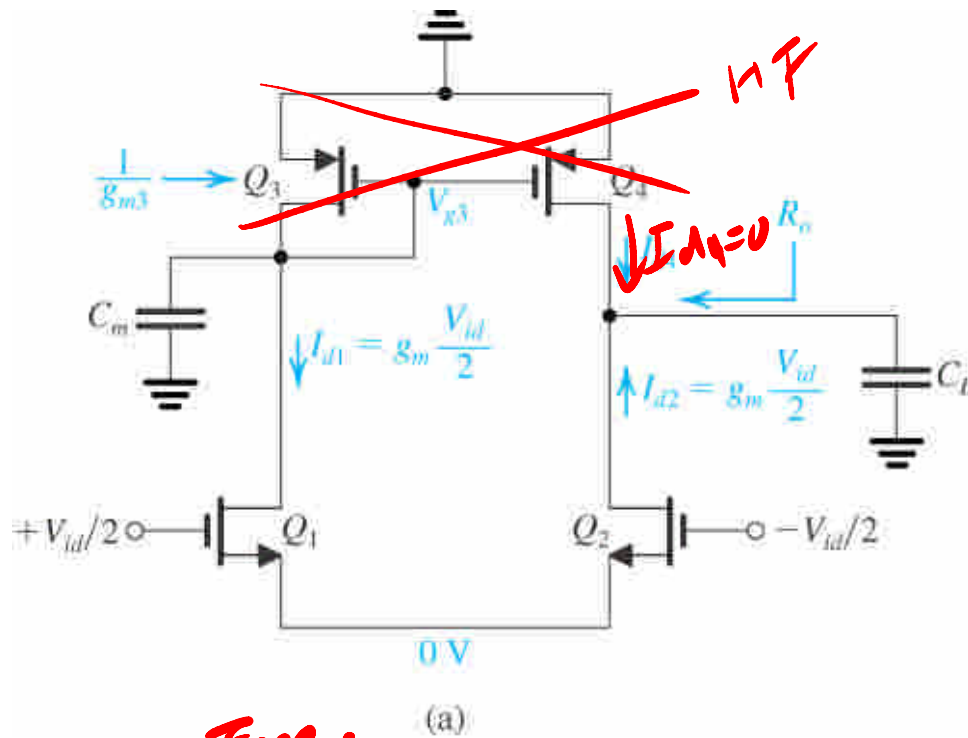

Low Freq: $G_m = g_m$
 High Freq: $G_m = \frac{1}{2} g_m$

Example 7.2

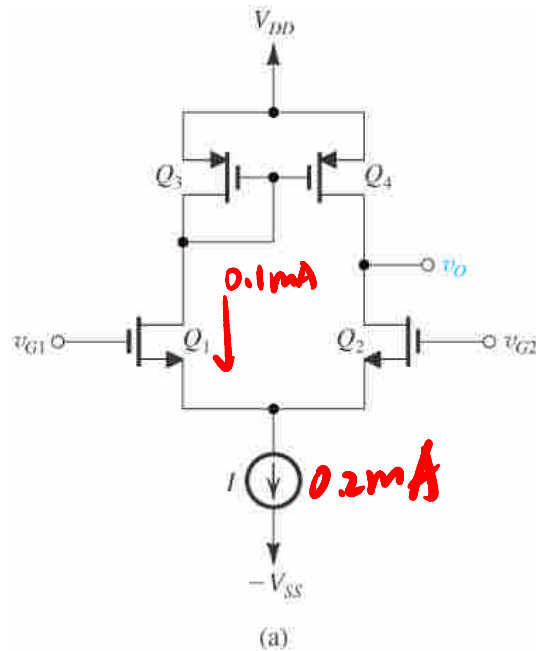

To find:

A_d , A_{cm} , CMRR

Poles and zeros of A_d

Dominant pole of CMRR

Q_1, Q_2
 $100 = \frac{1}{2} \cdot 387 \cdot \frac{7.2}{0.36} \times V_{ov}^2$
 $\Rightarrow V_{ov} = 0.16 \text{ V}$

$g_{m1} = g_{m2} = \frac{2 \times 0.1}{0.16} = 1.25 \left(\frac{\text{mA}}{\text{V}} \right)$

$r_{o1} = r_{o2} = \frac{5 \times 0.36}{0.1} = 18 \text{ k}\Omega$

Q_3, Q_4
 $V_{ov} = 0.34 \text{ V}$
 $g_m = 0.6 \text{ mA/V}$
 $r_o = 21.6 \text{ k}\Omega$

Low Freq.

$A_d = g_m (r_{o2} // r_{o4})$
 $= 12.3 \left(\frac{\text{V}}{\text{V}} \right)$

$A_{cm} = -\frac{1}{2g_m r_{SS}} = -0.033$

CMRR = 369 = 51.3 dB

$W/L = 7.2 \mu\text{m} / 0.36 \mu\text{m}$, $C_{gs} = 20 \text{ fF}$

$C_{gd} = 5 \text{ fF}$, $C_{db} = 5 \text{ fF}$, $\mu_n C_{ox} = 387 \mu\text{A/V}^2$

$\mu_p C_{ox} = 86 \mu\text{A/V}^2$, $V_{An}' = 5 \text{ V}/\mu\text{m}$, $|V_{Ap}'| = 6 \text{ V}/\mu\text{m}$

$I = 0.2 \text{ mA}$, $R_{SS} = 25 \text{ k}\Omega$, $C_{SS} = 0.2 \text{ pF}$

Another output capacitance $C_x = 25 \text{ fF}$

$C_m = 55 \text{ fF}$
 $C_L = 45 \text{ fF}$

$f_{p1} = 360 \text{ MHz}$


$f_{p2} = 1.746 \text{ MHz}$
 $f_z = 3.56 \text{ MHz}$

$f_z = \frac{1}{2\pi C_{SS} R_{SS}} = 31.8 \text{ MHz}$

Outline

- The MOS Differential Pair
- Small-Signal Operation of the MOS Differential Pair
- The BJT Differential Pair
- Other Nonideal Characteristics of the Differential Amplifier
- The Differential Amplifier with Active Load
- Frequency Response of the Differential Amplifier
- **Multistage Amplifiers**

Multistage Amplifiers

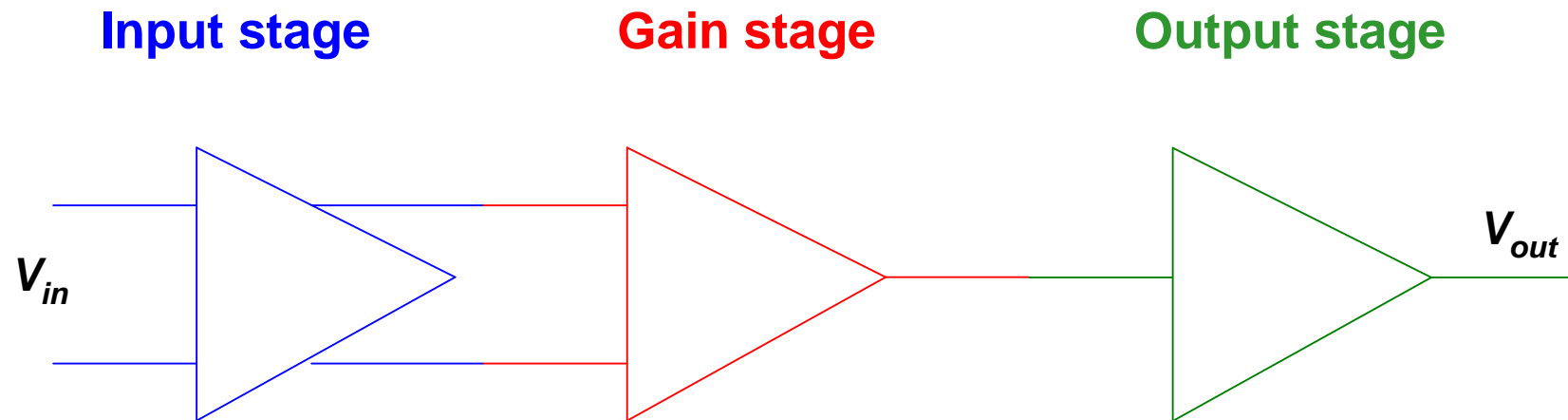

First stage:

- High input resistance
- Large CMRR
- Voltage gain

Middle stages:

- Voltage gain
- Differential to Single-ended
- DC-level shifting

Last stage:

- Low output resistance
- Supply current efficiently




A Two-Stage CMOS Op Amp

Switch-cap ckt

Current mirror

$$R_{out} = r_{o6} || r_{o7}$$

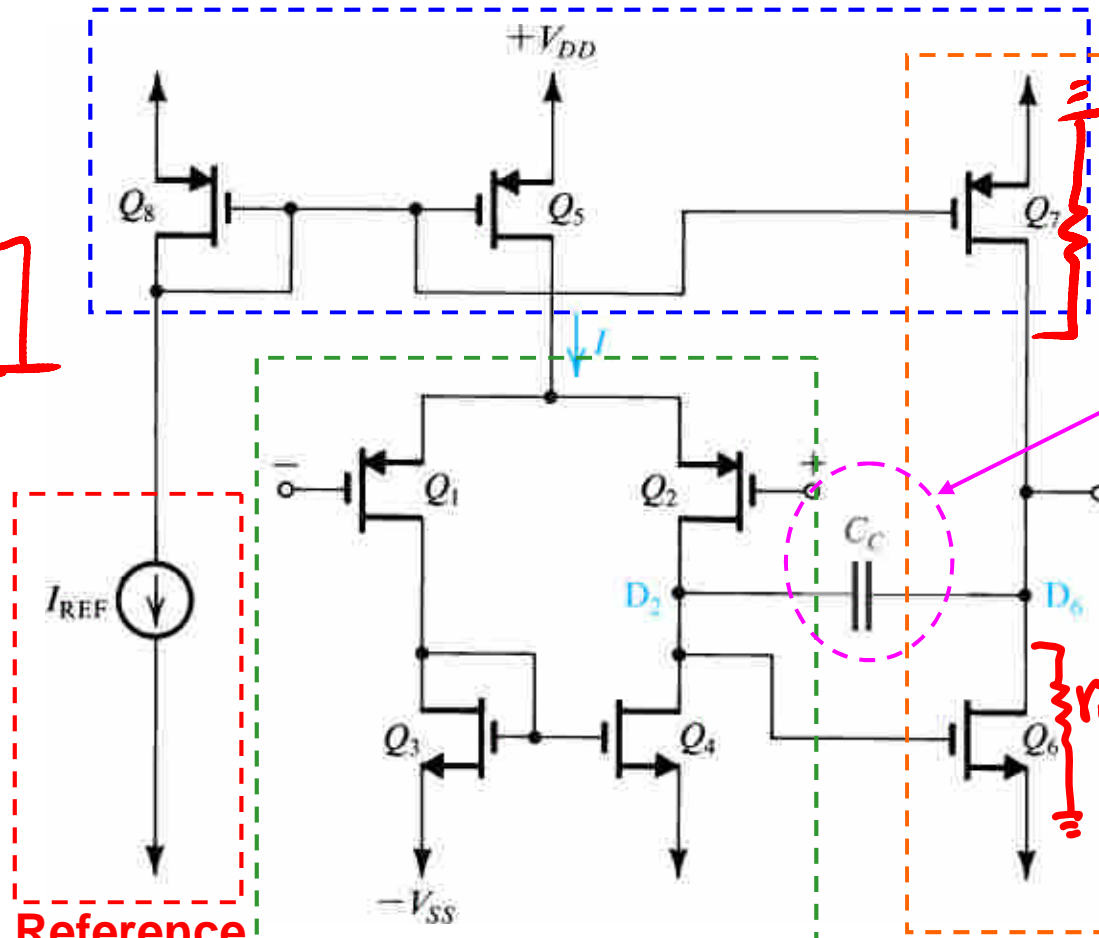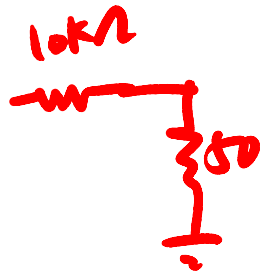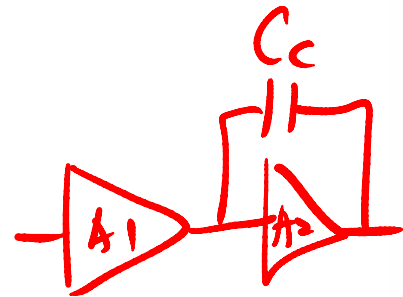
Enhance the Miller effect (Frequency Compensated)



Reference bias current


Differential Amplifier

CS Amp

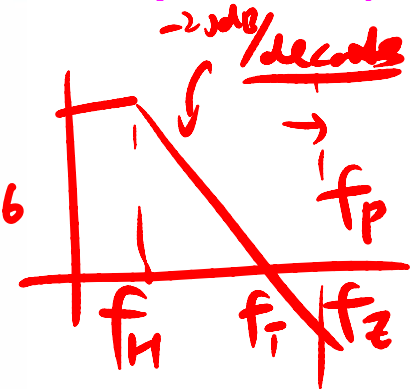

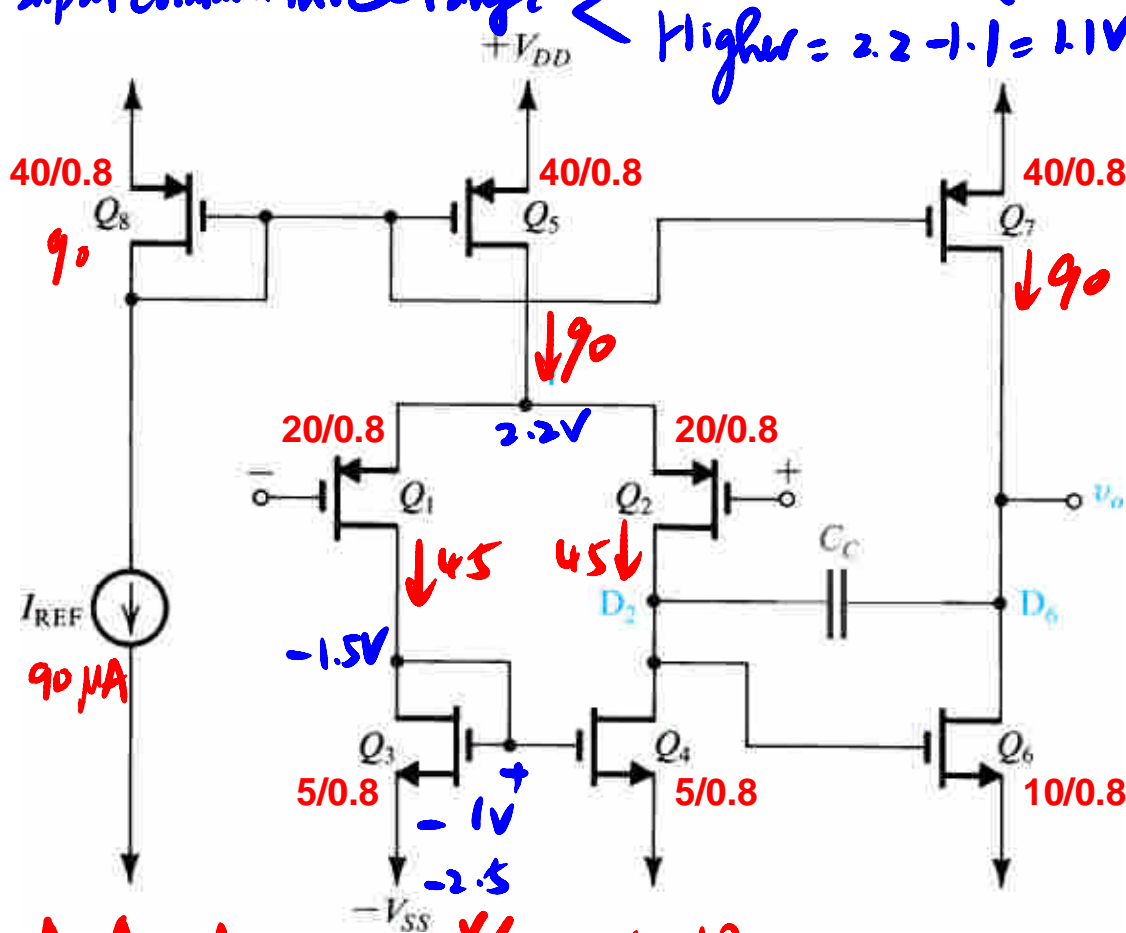Example 7.3

Input common mode range $\left\{ \begin{array}{l} \text{Lower} = -1.5 - 0.8 = -2.3\text{V} \\ \text{Higher} = 2.2 - 1.1 = 1.1\text{V} \end{array} \right.$



$I_{REF} = 90\mu\text{A}$, $V_{tn} = 0.7\text{V}$,
 $V_{tp} = -0.8\text{V}$, $\mu_n C_{ox} = 160\mu\text{A/V}^2$
 $\mu_p C_{ox} = 40\mu\text{A/V}^2$, $|V_A| = 10\text{V}$,
 $V_{DD} = V_{SS} = 2.5\text{V}$

$V_{GS} = 1.1\text{V}$ for $Q_{1,2,5,7,8}$
 1V for $Q_{3,4,6}$

- (a) I_D (0.3V)
- (b) $|V_{ov}|$ $I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} V_{ov}^2$
- (c) $|V_{GS}|$ $|V_{GS} - |V_{E}| = |V_{ov}|$
- (d) g_m $2I_D / |V_{ov}|$ 0.3mA/V Q_{1-4}
- (e) r_o $|V_A| / I_D$ 0.6 Q_{5-8}
- (f) A_1 -33.3(%) 222k Ω Q_{1-4}
- (g) A_2 111k Ω Q_{5-8}
- (h) Input common-mode range
- (i) Output voltage range


$$A = A_1 \times A_2 = 1109 (\text{V/V}) = 61\text{dB}$$

$-2.2\text{V} - 2.2\text{V}$

Frequency Response

$$G_{m1} = g_{m1} = g_{m2}$$

$$R_1 = r_{o2} // r_{o4}$$

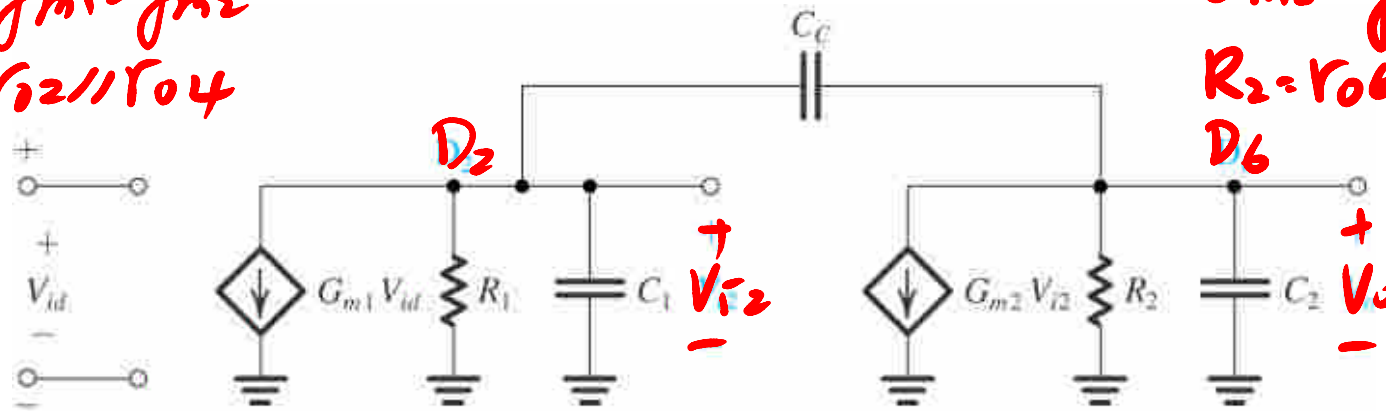

$$G_{m2} = g_{m6}$$

$$R_2 = r_{o6} // r_{o7}$$

$$C_1 = C_{gd4} + C_{db4} + C_{gd2} + C_{db2} + C_{gs6}$$

$$C_2 = C_{db6} + C_{db7} + C_{gd7} + C_L$$

$$\text{Node } D_2 \quad G_{m1} V_{id} + \frac{V_{i2}}{R_1} + s C_1 V_{i2} + s C_c (V_{i2} - V_o) = 0$$

$$\text{Node } D_6 \quad G_{m2} V_{i2} + \frac{V_o}{R_2} + s C_2 V_o + s C_c (V_o - V_{i2}) = 0$$

$$\frac{V_o}{V_{id}} = \frac{G_{m1} (G_{m2} - s C_c) R_1 R_2}{1 + s [C_1 R_1 + C_2 R_2 + C_c (G_{m2} R_1 R_2 + R_1 + R_2)] + s^2 [C_1 C_2 + C_c (C_1 + C_2)] R_1 R_2}$$

Frequency Response (con't)


$$\frac{V_o}{V_{id}} = \frac{G_{m1}(G_{m2} - sC_c)R_1R_2}{1 + s[C_1R_1 + C_2R_2 + C_c(G_{m2}R_1R_2 + R_1 + R_2)] + s^2[C_1C_2 + C_c(C_1 + C_2)]R_1R_2}$$

1) For $s=0$ $V_o/V_{id} = (G_{m1} \cdot R_1) \cdot (G_{m2} \cdot R_2)$

2) ω_z . $G_{m2} - s_z C_c = 0 \Rightarrow s_z = G_{m2}/C_c$

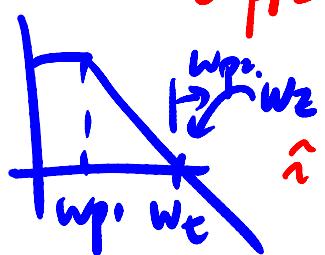3) $D(s) = (1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}}) = 1 + s(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}) + \frac{s^2}{\omega_{p1}\omega_{p2}} \approx 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1}\omega_{p2}}$

$\Rightarrow \omega_{p1} = \frac{1}{C_1R_1 + C_2R_2 + C_c(G_{m2}R_1R_2 + R_1 + R_2)} = \frac{1}{R_1 \left[\underbrace{C_1 + C_c(1 + G_{m2}R_2)}_{\text{Miller}} + R_2 \underbrace{(C_2 + C_c)}_M \right]}$



$\Rightarrow \omega_{p2} = \frac{G_{m2}C_c}{C_1C_2 + C_c(C_1 + C_2)} \approx \frac{G_{m2}}{C_2}$ (under assumptions $C_1 \ll C_2$ and $C_1 \ll C_c$)


$\omega_z = \omega_{p1} \cdot (G_{m1}R_1 G_{m2}R_2) = \frac{G_{m1}}{C_c}$

$\omega_z = \frac{G_{m1}}{C_c}$

$\omega_{p1} = \frac{1}{R_1 C_c G_{m2} R_2}$

$\omega_{p2} = \frac{G_{m2}}{C_c}$

A Bias Circuit

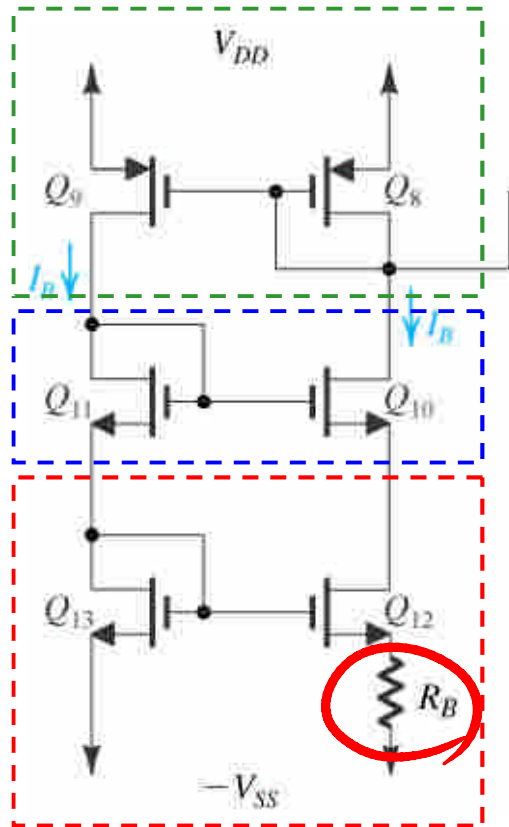

$$\begin{cases} I_B = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_8 (V_{GS12} - V_t)^2 \\ = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_{13} (V_{GS13} - V_t)^2 \\ V_{GS13} = V_{GS12} + I_B R_B \end{cases}$$

$$\Rightarrow I_B = \frac{2}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{12} R_B^2} \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)^2$$

$$\Rightarrow R_B = \frac{2}{\sqrt{\mu_n C_{ox} \left(\frac{W}{L}\right)_{12} I_B}} \cdot \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)$$

$$\Rightarrow g_{m12} = \frac{2}{R_B} \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)$$

$$g_m \propto \sqrt{I_D \left(\frac{W}{L}\right)}$$

$$g_{m_i} = g_{m12} \sqrt{\frac{I_{D_i} (W/L)_i}{I_B (W/L)_{12}}} \quad \text{NFET}$$

Announcements

- 下星期五(5/11)補課: 8AM

- HW #2

- Due date 5/22/07

- Late policy: Turn in class: 100%, before 12PM: 90%,
5/22 after 12AM: 80%, 5/23: 60%, 5/24: 40%, 5/25:
20%, after 5/26: 0%

Exercise

*7.2, 7.14, 7.17, 7.39, 7.40
7.50, 7.63, 7.71, 7.80, 7.90*

- Midterm #2

- Test date 5/15/07 ~~18:00-20:00~~ *19:00 - 21:00*

- Coverage: Ch6, Ch7, and a part of Ch8 (8.1-8.4)