

UNIVERSITY OF CALIFORNIA AT BERKELEY  
College of Engineering  
Department of Electrical Engineering and Computer Science

R. W. Brodersen,

Homework #2

EECS140  
Fall 2004

1. Consider the structure shown in Figure 1. This two-transistor structure can be considered a new type of single device (the "Cal-sistor") with the drain, source, and gate nodes as given. For this problem, assume that  $\lambda=\gamma=0$ .


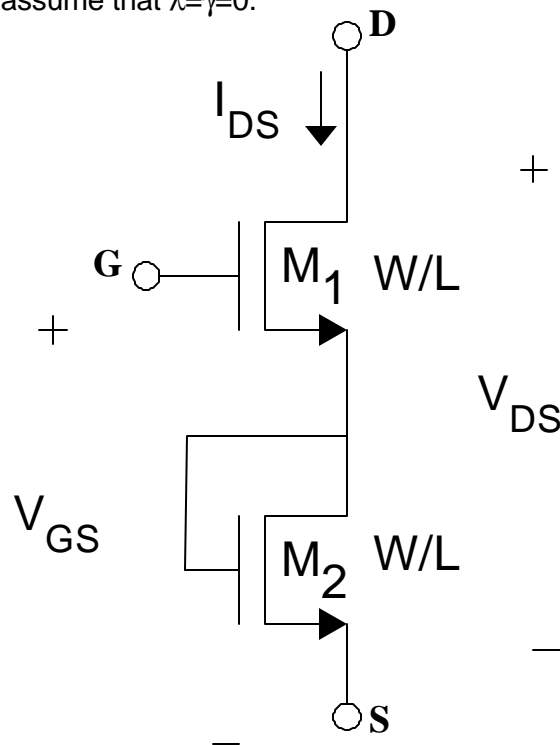


Figure 1

- a) Determine the  $V_{DS}$  and  $V_{GS}$  conditions for each of the 3 operating modes (cutoff, saturation, and linear) for the Cal-sistor.
- b) Determine  $I_{DS}$  as a function of  $V_{GS}$  and  $V_{DS}$  for each of these 3 modes.

2. For each of the two circuits in figure 2, perform the calculations for (a) and (b) by hand. Assume  $V_{T0}=0.5V$ ,  $k'W/L = 8mA/V^2$ ,  $\lambda=0.1V^{-1}$ ,  $\gamma=0.2V^{1/2}$ ,  $R_1=10k\Omega$ ,  $R_2=2k\Omega$ ,  $R_3=10k\Omega$ ,  $R_4=10k\Omega$ ,  $V_{DD}=3V$ .

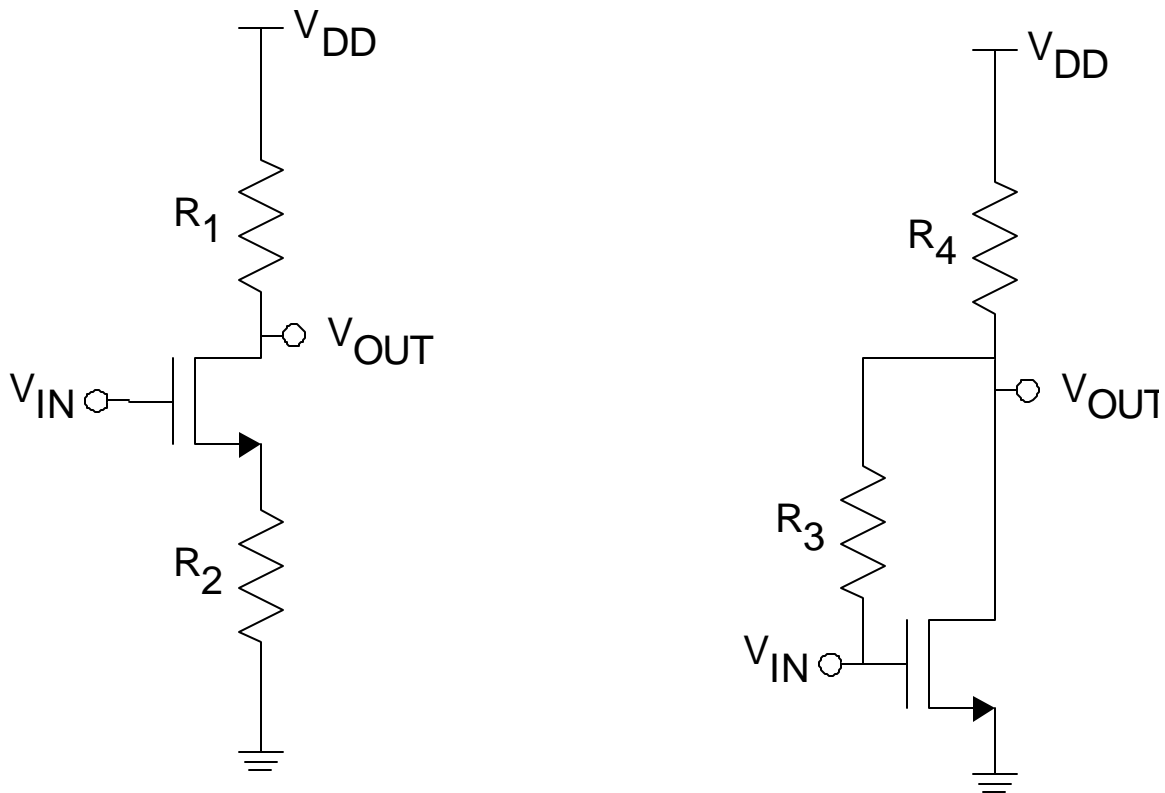

**Figure 2**

- a) Determine the dc voltage  $V_{IN}$  so that  $V_{OUT}$  is at 1.5V. Assume that  $V_{IN}$  is between 0 and  $V_{DD}$ .
  - b) Calculate the operating point parameters  $I_{DS}$ ,  $V_T$  and  $V_{DSAT}$ , and the small signal-parameters  $g_m$ ,  $g_{mbs}$ , and  $r_o$ .
3. Razavi, problem 2.5, parts a-d. Some notes on the problems are below
- a. Table 2-1 w/ the required device parameters is on p. 37
  - b. Be sure to numerically label the voltages breakpoints at which the transistor changes modes (i.e. from linear to saturation and so forth).
  - c. Remember that the notation for a drain vs. source node is only notation! For an NMOS device, the drain is determined by which of these two nodes has a higher voltage. Therefore, as voltages are swept, the drain and source nodes can become interchanged!