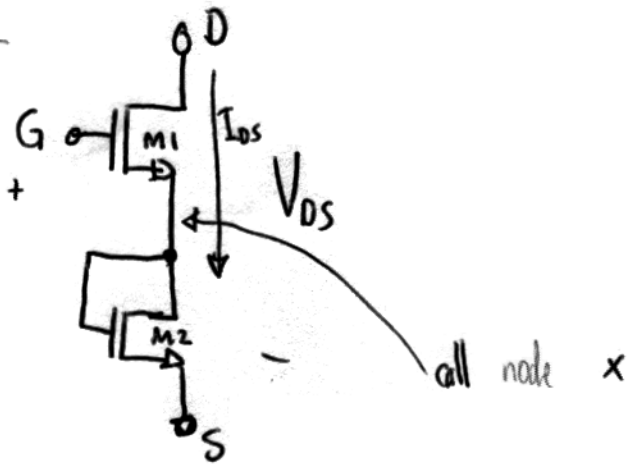


Problem 1Cutoff mode

To be in cutoff either  $V_{GS1} < V_T$  or  $V_{GS2} < V_T$  (or bot).

$V_{GS} = V_{GS1} + V_{GS2} \Rightarrow V_{GS} < 2 \cdot V_T$  ~~causes~~ causes cutoff

Also, we know that  $V_x < V_D \Rightarrow$  if  $V_D < V_T$ ,  $M_2$  cutoff

$\Rightarrow$

Cutoff happens when  $V_{GS} < 2V_T$   
 or  $V_D < V_T$ .  
 $I_{CUTOFF} = \emptyset$

Saturation mode

For the "calculator" to be in saturation, BOTH  $M_1$  &  $M_2$  must  
 in saturation  $\Rightarrow V_{GS1} > V_T$  and  $V_{GS2} > V_T$  and  $V_{DS1} > V_{GS1}$

$\Rightarrow$  conditions for saturation are:

$$V_{GS} > 2V_T \text{ and}$$

$$V_{DS} > V_{GS} - V_T$$

continued on  
next page

Problem 1, cont'd

saturation mode current:

Note that  $I_{DS1} = I_{DS2} = I_{DS} \Rightarrow V_{DSAT1} = V_{DSAT2}$ . Therefore

$$V_{GS1} = V_T + V_{DSAT1} \quad \text{equals} \quad V_{GS2} = V_T + V_{DSAT2}$$

$$\left. \begin{aligned} I_{DS2} &= \frac{1}{2} k \frac{W}{L} (V_X - V_S - V_T)^2 \\ I_{DS1} &= \frac{1}{2} k \frac{W}{L} (V_G - V_X - V_T)^2 \end{aligned} \right\} \rightarrow I_{DS1} = I_{DS2} \Rightarrow (V_X - V_S - V_T) = (V_G - V_X - V_T)$$

~~Handwritten scribbles and crossed-out text below the equations.~~

~~Handwritten scribbles and crossed-out text.~~

~~Handwritten scribbles and crossed-out text.~~

$$\text{So } V_X - V_S - V_T = V_G - V_X - V_T \Rightarrow V_X = \frac{V_G + V_S}{2}$$

$$I_{DS} = I_{DS2} = \frac{1}{2} k \frac{W}{L} \left( \frac{V_G + V_S}{2} - V_S - V_T \right)^2 = \frac{1}{2} k \frac{W}{L} \left( \frac{V_G - V_S}{2} - V_T \right)^2$$

$$I_{DS, \text{SATURATION}} = \frac{1}{2} k \frac{W}{L} \left( \frac{V_{GS}}{2} - V_T \right)^2$$

continued on  
next page

Linear mode: By process of elimination, linear mode occurs

When

$$\begin{aligned} V_{GS} &> 2V_T \\ V_T < V_{DS} &< V_{GS} - V_T \end{aligned}$$

In this mode: M1 is in linear and M2 is in saturation

(NOTE: M2 can NEVER be in linear mode as  $V_{GS} = V_{DS}$ .)

$$I_2 = \frac{k}{2} \frac{W}{L} (V_X - V_S - V_T)^2 \quad (\text{eq 1})$$

$$I_1 = k \frac{W}{L} \left( V_G - V_X - V_T - \frac{V_D - V_X}{2} \right) (V_D - V_X) \quad (\text{eq 2})$$

$$I_1 = I_2 \quad (\text{eq 3})$$

Plugging eq 1 & eq 2 into eq 3, we get

$$\frac{1}{2} (V_X - V_S - V_T)^2 = \left( V_G - V_T - \frac{V_D}{2} - \frac{V_X}{2} \right) (V_D - V_X)$$

without loss of generality, assume  $V_S = 0$  and expand: (eq 4)

$$\frac{1}{2} V_X^2 - V_X V_T + \frac{V_T^2}{2} = \left( V_G - V_T - \frac{V_D}{2} \right) V_D - \left( V_G - V_T - \frac{V_D}{2} \right) V_X - \frac{V_X V_D}{2} + \frac{V_X^2}{2}$$

Regrouping terms to solve for  $V_X$ :

$$\frac{V_T^2}{2} - \left( V_G - V_T - \frac{V_D}{2} \right) V_D = V_X \left( V_T - V_G + V_D + \frac{V_D}{2} - \frac{V_D}{2} \right) \quad (\text{eq 5})$$

$$\text{or } \frac{V_T^2}{2} - \left( V_G - V_T - \frac{V_D}{2} \right) V_D = -V_X (V_G - 2V_T) \quad (\text{eq 6})$$

Rearranging (eq 6):

$$V_x = \frac{(V_G - V_T - \frac{V_D}{2})V_D - \frac{V_T^2}{2}}{V_G - 2V_T} \quad (\text{eq -7})$$

And, we know

$$I_{DS} \Big|_{V_S=0} = I_{DS1} \Big|_{V_S=0} = \frac{k}{2} \frac{W}{L} (V_x - V_T)^2 \quad (\text{eq 8})$$

From (eq-7):  $V_x - V_T = \frac{-\frac{V_D^2}{2} + V_D V_G - V_D V_T - V_G V_T + \frac{3}{2} V_T^2}{V_G - V_T}$  (eq 9)

Plugging (9) into (8) we get:


$$I_{DS, \text{Linear}} = \frac{k}{2} \frac{W}{L} \left( \frac{-\frac{V_D^2}{2} + V_D V_G - V_D V_T - V_G V_T + \frac{3}{2} V_T^2}{V_G - V_T} \right)^2 \quad \text{if } V_S = 0$$

or more generally:

$$I_{DS, \text{Linear}} = \frac{k}{2} \frac{W}{L} \left( \frac{-\frac{V_{DS}^2}{2} + V_{DS} V_{GS} - V_{DS} V_T - V_{GS} V_T + \frac{3}{2} V_T^2}{V_{GS} - V_T} \right)^2$$

P-2

1st circuit:

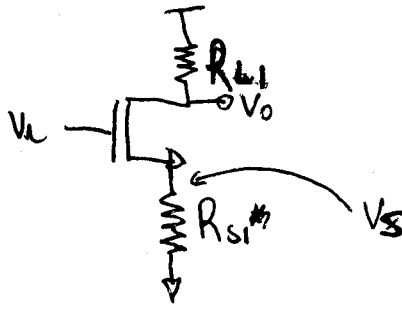

page 5

$$(a) V_O = 1.5V \Rightarrow I_{D_S} = \frac{V_{DD} - V_O}{R_{L1}} = \frac{3V - 1.5V}{10k\Omega} = 150\mu A$$

$$V_{S_B} = I_{D_S} \cdot R_{S1} = 150\mu A \cdot 2k\Omega = 300mV \Rightarrow V_{S_B} = 300mV$$

$$V_T(V_{S_B}) = V_{T0} + \gamma \left( \sqrt{2\phi_F + V_{S_B}} - \sqrt{2\phi_F} \right)$$

$$= 0.5V + 0.2 \left( \sqrt{0.900V} - \sqrt{0.6V} \right) = 0.535V$$

Now find required  $V_{GS}$ :

$$\frac{1}{2} k \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{D_S}) = I_{D_S} \quad (\text{assume saturation mode})$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{I_{D_S}}{1 + \lambda V_{D_S}} \cdot \frac{2}{k \cdot \frac{W}{L}}$$

$$\Rightarrow V_{GS} = V_T + \sqrt{\frac{2I_{D_S}}{(1 + \lambda V_{D_S}) \cdot k \frac{W}{L}}} = 0.535 + \sqrt{\frac{2 \cdot 150e-6}{[1 + 0.1 \cdot (1.5 - 0.3)] \cdot 8e-3}}$$

$$V_{GS} = 0.718V$$

$$V_{IN} = V_{GS} + V_S = 0.718V + 0.3V = \boxed{1.018V = V_{IN}}$$

Check for validity of saturation mode:

$$V_{GS} = 0.718V$$

$$V_{D_S} = 1.2V$$

Is  $V_{GS} > V_T$ ? Yes!Is  $V_{D_S} > V_{GS} - V_T$ ? Yes!

~~1st~~ 1st circuit, part b

$$I_{DS} = 150 \mu A \quad (\text{calculated in part a})$$

$$V_T = 0.535 V \quad (\text{calculated in part a})$$


$$V_{DSAT} = V_{GS} - V_T = 0.718 V - 0.535 V = 0.183 V = V_{DSAT}$$

$$g_m \approx k \frac{W}{L} V_{DSAT} = 8e-3 A/V^2 \cdot 0.183 V = 1.46e-3 A/V = g_m$$

$$g_{mbs} = g_m \cdot \frac{K}{2\sqrt{2\phi_f + V_{SB}}} = 1.46e-3 \cdot \frac{0.2}{2\sqrt{0.6+0.3}} = 1.539e-4 A/V = g_{mb}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{10 V}{150 \mu A} = 6.66e+4 \frac{V}{A} = 66.66 k\Omega = r_o$$

Circuit 2

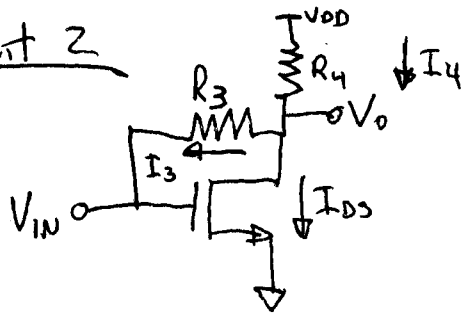

page 7

$$(a) V_0 = 1.5 \Rightarrow I_4 = \frac{V_{DD} - V_0}{R_4} = \frac{1.5V}{10k\Omega} = 150\mu A$$

$$I_{DS} = \frac{1}{2} k \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) = 4 \frac{mA}{V} \cdot (V_{IN} - 0.5)^2 \cdot (1 + 0.1 \cdot 1.5)$$

$$= 4.6 \frac{mA}{V} \cdot (V_{IN} - 0.5)^2$$

$$I_3 = \frac{V_0 - V_{IN}}{R_3} = \frac{1.5V - V_{IN}}{10k}$$

By KCL:  $I_3 + I_{DS} = I_4$

$$\Rightarrow \left( \frac{1.5V - V_{IN}}{10k} \right) + 4.6e-3 \cdot (V_{IN} - 0.5)^2 = 150e-6$$

Solving for  $V_{IN} \Rightarrow V_{IN} = 0.6156V$  or  $0.406V$  less than  $V_T$ , hence invalid solution

Checking assumptions:

$$I_{DS} = \frac{1}{2} k \frac{W}{L} (0.1156)^2 (1.15) = 61.5\mu A = I_{DS}$$

$$I_3 = \frac{1.5 - 0.615V}{10k\Omega} = 88.5\mu A = I_3$$

$$I_3 + I_{DS} = 61.5\mu A + 88.5\mu A = 150\mu A \checkmark = I_4$$

Saturation?  $V_{GS} > V_T$ ? Yes

$V_{DS} > V_{GS} - V_T$ ? Yes

$$I_{D_S} = \frac{1}{2} k' \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) = 4 \text{ mA/V}^2 \cdot (0.1156 \text{ V})^2 (1 + 0.1 \cdot 1.5 \text{ V})$$

$$I_{D_S} = 61.5 \mu\text{A}$$

$$V_T = 0.5 \text{ V}$$

$$V_{DSAT} = V_{GS} - V_T = 0.1156 \text{ V} = V_{DSAT}$$


~~$$g_m = \frac{2I_D}{V_{DSAT}} = \frac{123 \text{ mA}}{0.1156 \text{ V}} = 1.064 \frac{\text{mA}}{\text{V}} = g_m$$~~

$$g_m = \frac{2I_D}{V_{DSAT}} = \frac{123 \text{ mA}}{0.1156 \text{ V}} = 1.064 \frac{\text{mA}}{\text{V}} = g_m$$

$$g_{mbs} = g_m \cdot \frac{\gamma}{2\sqrt{2}\phi_f} = 1.064 \frac{\text{mA}}{\text{V}} \cdot \frac{0.2 \sqrt{V}}{2\sqrt{0.6 \text{ V}}} = 0.1374 \frac{\text{mA}}{\text{V}} = g_{mbs}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{10 \text{ V}}{61.5 \mu\text{A}} = 162 \text{ k}\Omega = r_o$$

2.5) a)

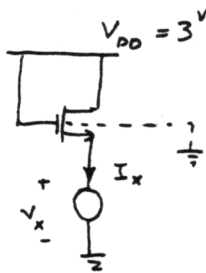

$$\lambda = 0.1, \quad \gamma = 0.45, \quad 2\phi_F = 0.9, \quad V_{TH0} = 0.7$$

$$V_{GS} = 3 - V_x, \quad V_{DS} = 3 - V_x, \quad V_{SB} = V_x$$

$$V_{TH} = V_{TH0} + \gamma (\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F})$$


$$\text{So, } I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (3 - V_x - 0.7 - 0.45(\sqrt{0.9 + V_x} - \sqrt{0.9}))^2 (1 + \lambda(3 - V_x))$$

The above equation is valid for


$$3 - V_x - 0.7 - 0.45(\sqrt{0.9 + V_x} - \sqrt{0.9}) > 0, \quad \text{i.e. } V_x < 1.97 \text{ V}$$

$$\text{So, } I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (2.727 - V_x - 0.45\sqrt{0.9 + V_x})^2 (1.3 - 0.1V_x)$$

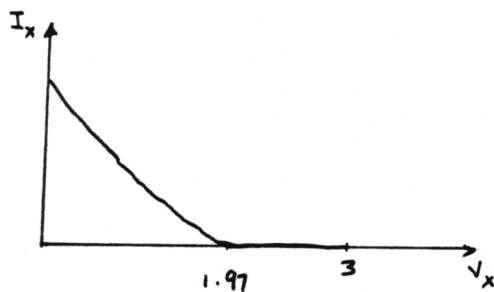
$$\text{and } I_x = 0 \text{ for } 1.97 < V_x$$


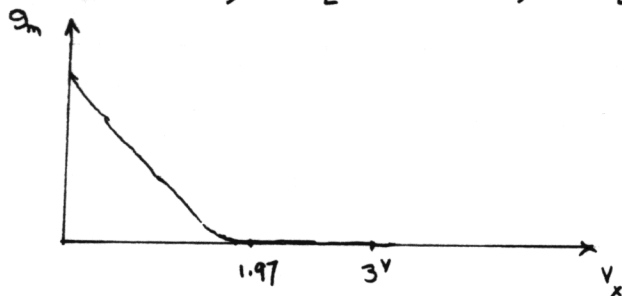
$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_x}$$



2.5) b,

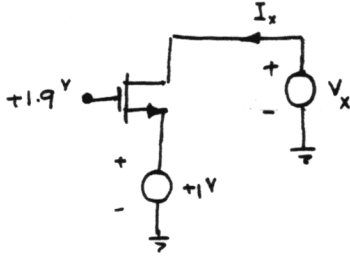

$$\lambda = \gamma = 0 \quad V_{TH} = 0.7$$

for  $0 < V_x < 1$ , S and D exchange their roles.

$$V_{GS} = 1.9 - V_x \quad V_{DS} = 1 - V_x, \quad V_{DD} = 1.2 - V_x$$

$$I_x = -\frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[ (1.2 - V_x) \times 2 \times (1 - V_x) - (1 - V_x)^2 \right]$$

$$I_x = -\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (1 - V_x) (1.4 - V_x)$$

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{DS} = \mu_n C_{ox} \frac{W}{L} (1 - V_x) \text{ (absolute value)}$$

The above equations are valid for  $V_x < 1$

Then the direction of current is reversed.

$$V_{GS} = 1.9 - 1 = 0.9 \quad V_{DS} = V_x - 1, \quad V_{DD} = 0.9 - 0.7 = 0.2$$

for  $V_x < 1.2$ , device operates in the triode region.

$$I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[ 2 \times 0.2 \times (V_x - 1) - (V_x - 1)^2 \right]$$



$$g_m = \mu_n C_{ox} \frac{W}{L} (V_x - 1)$$

for  $V_x > 1.2$ , Device goes into saturation region


2.5) b Cont

$$\text{So, } I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.2)^2 ,$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (0.2)$$

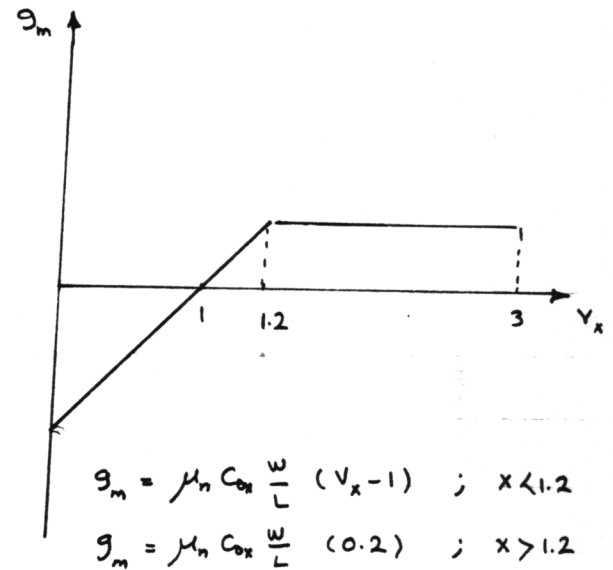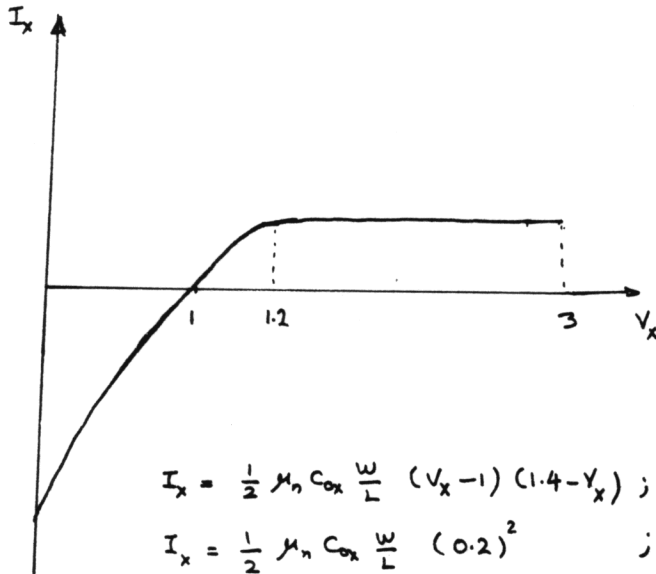

2.5) c

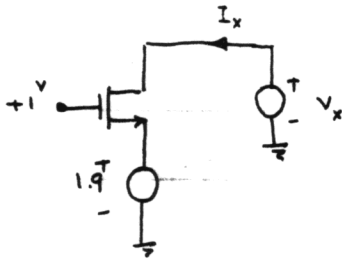

$$\lambda = \gamma = 0$$

$$V_{TH} = 0.7$$

S and D exchange their roles.

$$V_{GS} = 1 - V_x \quad V_{DS} = 1.9 - V_x \quad V_{GD} = V_{GS} - V_{TH} = 0.3 - V_x$$

Device is in saturation region, so,  $I_x = -\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.3 - V_x)^2$



Device turns off when  $V_x = 0.3$  and never turns on again.

$$\text{So, } I_x = -\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.3 - V_x)^2 \quad ; x < 0.3$$


$$I_x = 0 \quad ; \text{otherwise}$$

$$\text{Then } g_m = -\mu_n C_{ox} \frac{W}{L} (0.3 - V_x) \quad ; x < 0.3$$

$$g_m = 0 \quad ; \text{otherwise}$$

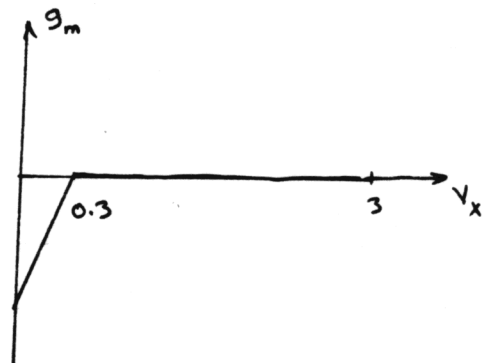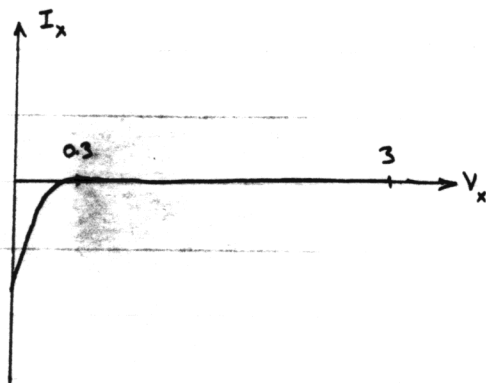

2.5) d)

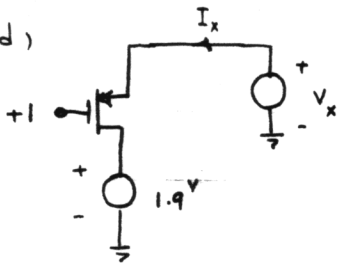

$$V_{TH} = -0.8 \quad \gamma = 0$$

D and S exchanging their roles.

$$V_{GS} = -0.9 \quad V_{DS} = V_x - 1.9$$

for  $V_x < 1.8$  :

$$I_x = -\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (0.1)^2$$

$$g_m = -\mu_p C_{ox} \frac{W}{L} (0.1)$$

Device remains in the saturation region until

$$V_x = 1.9 - 0.1 = 1.8, \text{ then device goes into the triode}$$

region.

for  $1.8 < V_x < 1.9$  :

$$I_x = -\mu_p C_{ox} \frac{W}{L} \left[ (-0.1)(V_x - 1.9) - \frac{1}{2} (V_x - 1.9)^2 \right]$$

$$g_m = +\mu_p C_{ox} \frac{W}{L} (V_x - 1.9)$$

for  $V_x > 1.9$  :

S and D exchange their roles again, when  $V_x = 1.9$

for  $V_x > 1.9$ , Device operates in the triode region.

$$V_{GS} = 1 - V_x, \quad V_{DS} = 1.9 - V_x$$

$$I_x = +\mu_p C_{ox} \frac{W}{L} \left[ (1.8 - V_x)(1.9 - V_x) - \frac{1}{2} (1.9 - V_x)^2 \right]$$

$$g_m = -\mu_p C_{ox} \frac{W}{L} (1.9 - V_x)$$

$$2.5)d \quad 50; \quad 0 < V_x < 1.8$$

$$I_x = -\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (0.1)^2$$

$$g_m = -\mu_p C_{ox} \frac{W}{L} (0.1)$$

$$1.8 < V_x < 3$$

$$I_x = +\mu_p C_{ox} \frac{W}{L} \times \frac{1}{2} (V_x - 1.9)(V_x - 1.7)$$

$$g_m = \mu_p C_{ox} \frac{W}{L} (V_x - 1.9)$$

