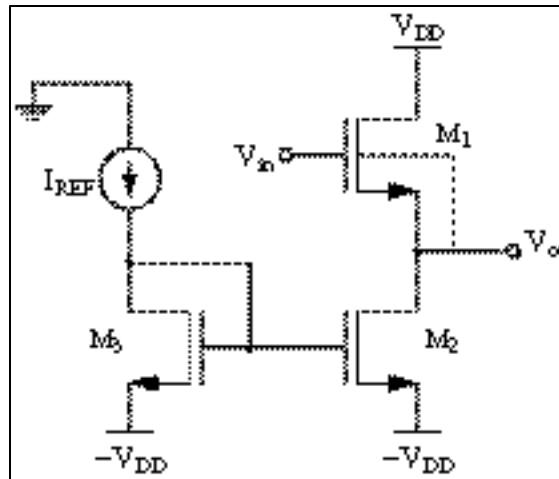


**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering**  
**and Computer Sciences**

R. W. Brodersen

**EECS 140**  
**Fall 2004**

**PROBLEM SET #6**




1) For the circuit above, assume all wells are tied to their respective sources.  $V_{DD}=1.8$  V. All  $W/L=6/0.18$ .  $I_{REF}=100$   $\mu$ A.  $V_{IN}$  is set so that the output is biased at 0 V. Use the following device model:

```
.model nch nmos LEVEL=1 TOX=25 VTO=0.5 KP=140.0e-6 LAMBDA=0.1  
+GAMMA=0.5 PHI=0.6
```

In this problem, use the feedback circuit techniques developed in class to analyze the above source follower.

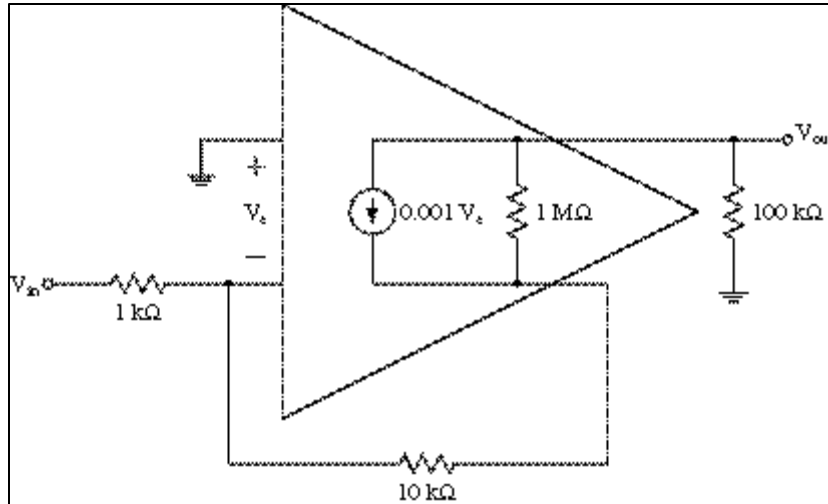- a) What kind of feedback is it?
- b) Find an expression for the feedback factor,  $f$ .
- c) Give an expression for the loop gain,  $T$ , with loading, and calculate the value.
- d) Give expressions and calculate  $v_{out}/v_{in}$  and  $R_{out}$  using the feedback formulas and compare to the exact expressions.



2) For the circuit above, determine the following:

a) What kind of feedback is it?

b) Find the feedback factor,  $f$ .

c) Find  $R_{out}$ .

d) Find  $v_{out}/v_{in}$ .

e) Use SPICE to check your answers for parts (c) and (d). Macromodel the opamp using `.subckt`.