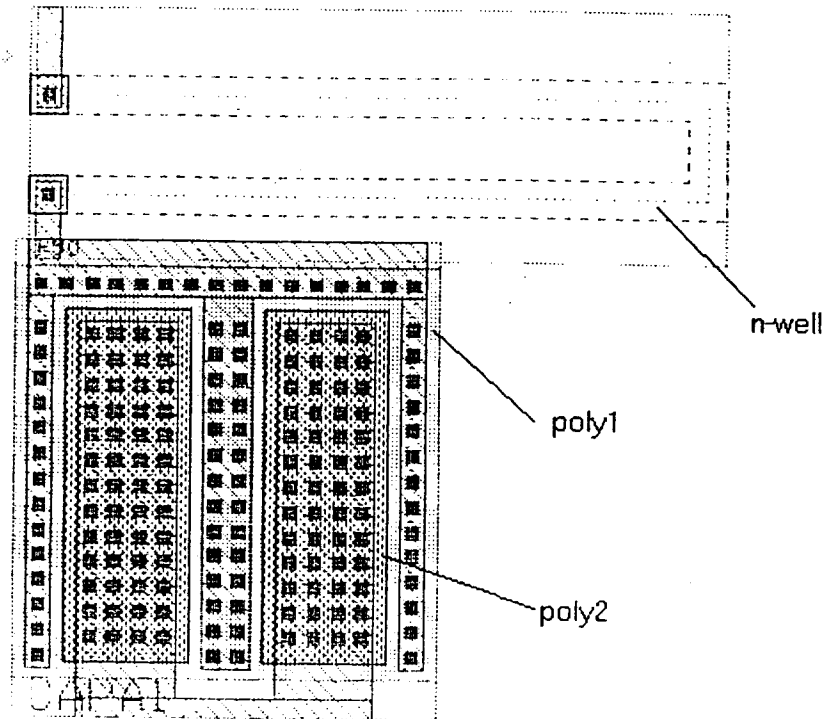


Chapter 7

Problem 7.1:

The layout of the RC circuit is shown in the following Fig.



The capacitor is composed of poly2 and poly1, and the capacitance $C \cong 1.10432 \text{ pF}$ (which measured by "Cap" command of the LASI, $C'_{\text{nom}} = 493 \text{ aF}/\mu\text{m}^2$ in CN20 process).

The resistor is composed of n-well, and the resistance $R \cong 90250 \Omega$ (which measured by "Res" command of the LASI, $R_{\text{sheet}(\text{nom})} = 2500 \Omega$ in CN20 process).

$$\therefore \tau = RC \cong 100 \text{ ns.}$$



Because C' can vary from 443 to 557 $\text{aF}/\mu\text{m}^2$, and R_{sheet} can vary from 2000 to 3000 per square,


$$\therefore \text{The minimum time constant } \tau_{\text{min}} = 100 \times (2000/2500) \times (443/493) \cong 71.9 \text{ ns.}$$

$$\text{The maximum time constant } \tau_{\text{max}} = 100 \times (3000/2500) \times (557/493) \cong 135.6 \text{ ns.}$$

Problem 7.2:


$R(T) = R_{T_0} \cdot (1 + \text{TCR} \cdot (T - T_0)) = 20000 \cdot (1 + 0.0002(T - 27))$, and T vary from -50 to 100°C. The result is shown below:

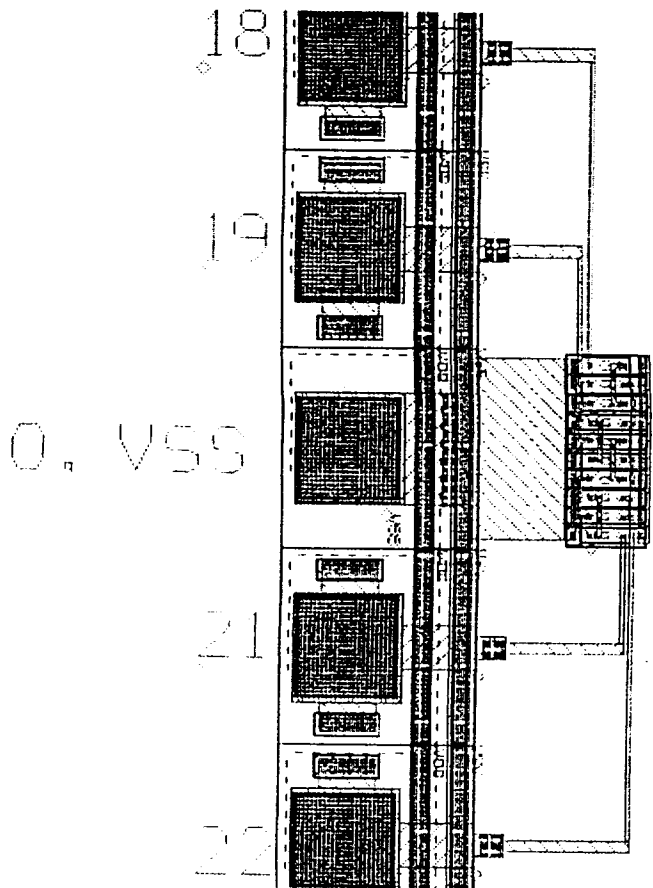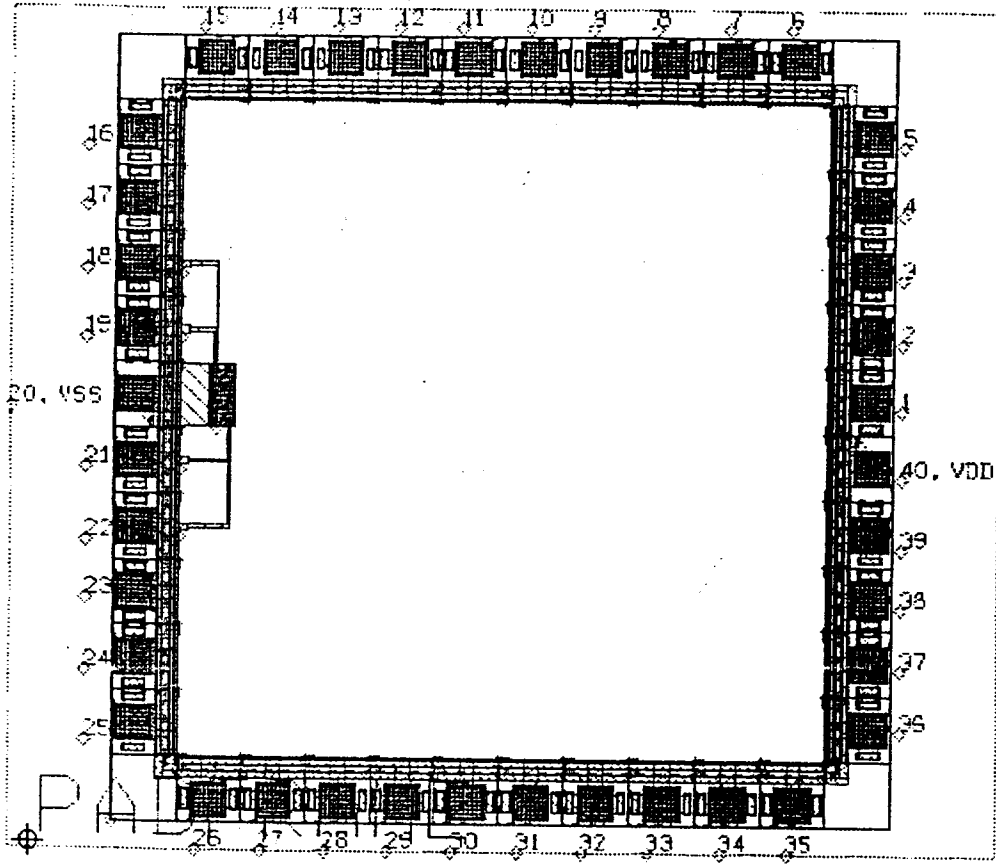

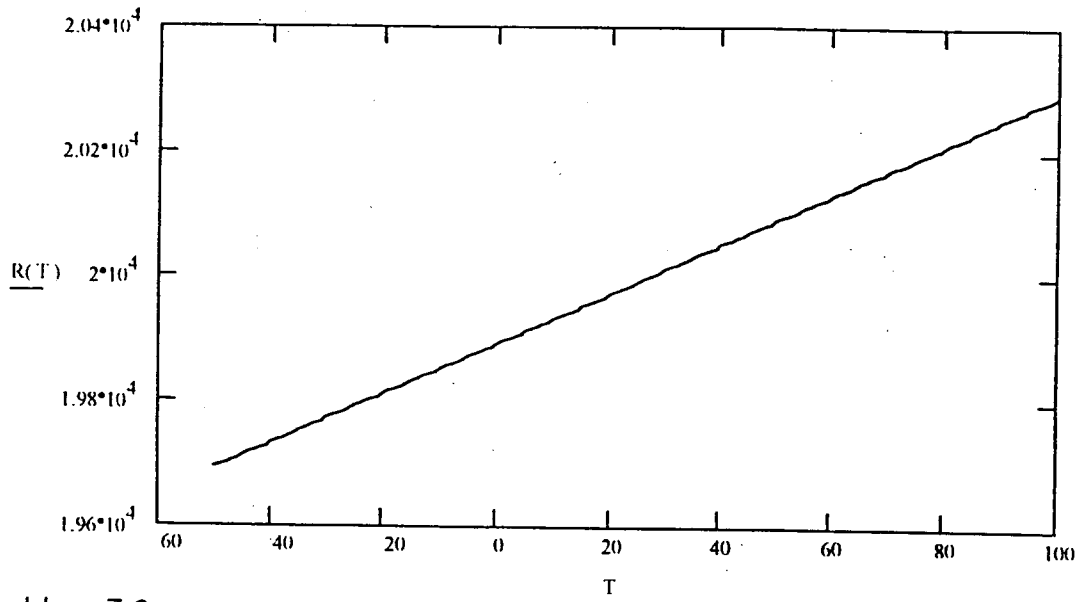


Problem 7.3:

$C(T) = C_{T_0} \cdot (1 + TCC \cdot (T - T_0)) = 1 \cdot (1 + 0.0001(T - 27))$ (pF), and T vary from -40 to 100°C .
The result is shown below:

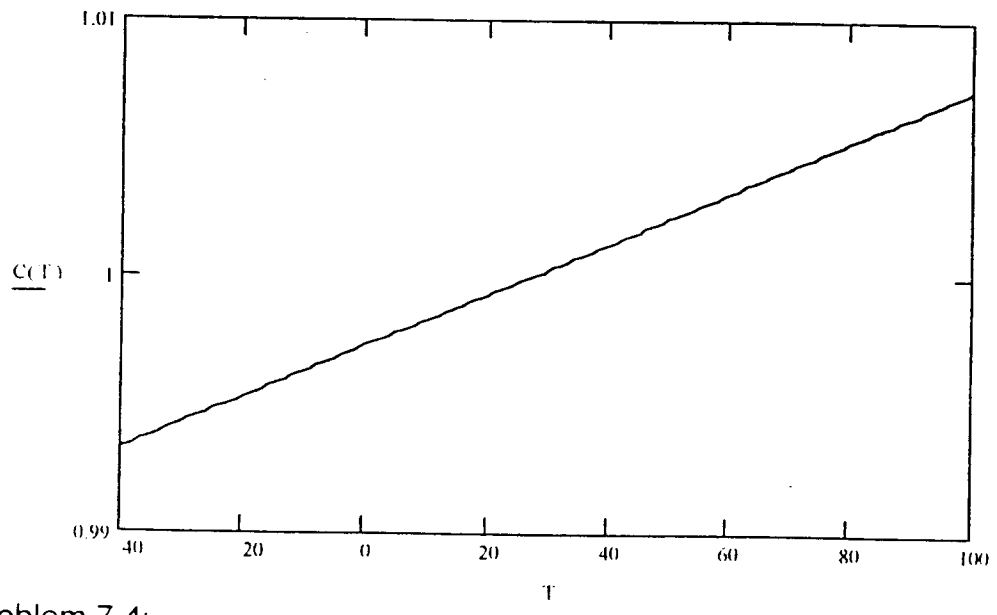

Problem 7.4:

The layout is shown below:

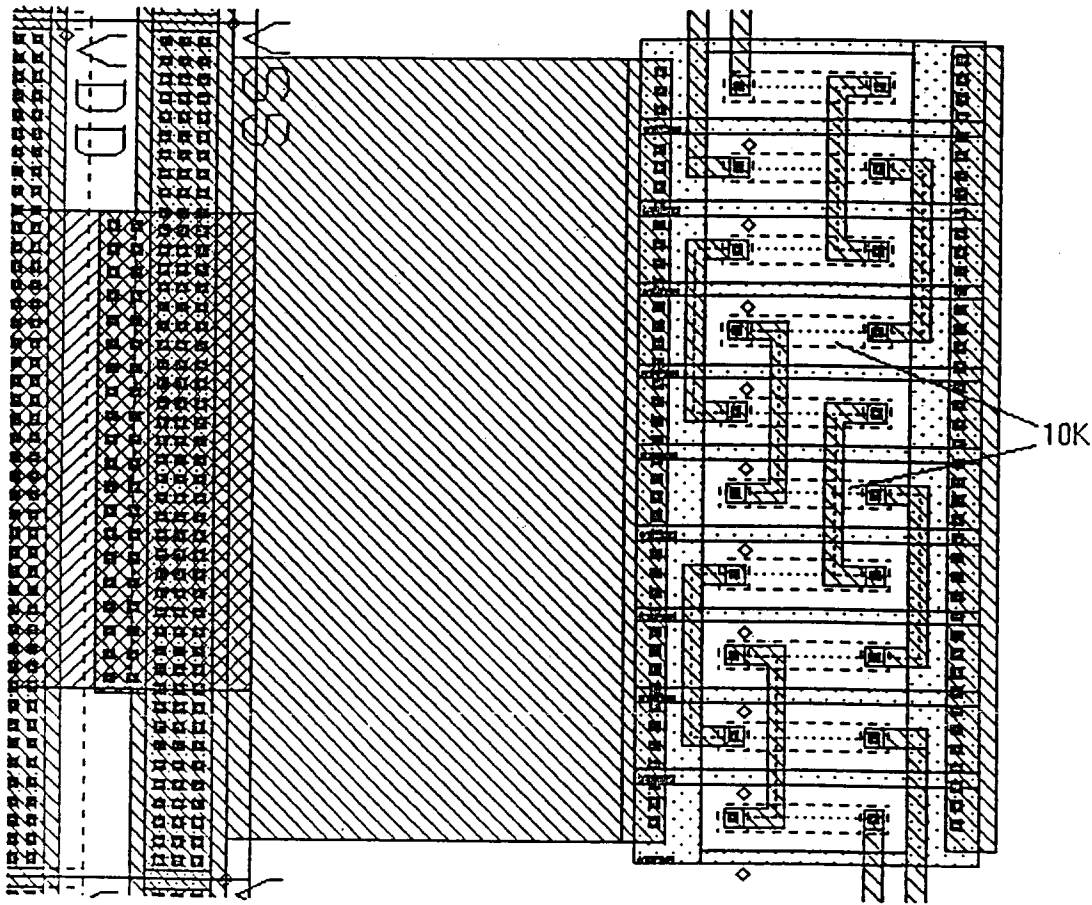

Problem 7.5:

The RMS noise current of each resistor:

$$\sqrt{i_n^2} = \sqrt{\frac{4kT}{R}} = \sqrt{\frac{4 \times 1.38 \times 10^{-23} \times 300}{20000}} = 9.1 \times 10^{-13} \left(\frac{\text{A}}{\sqrt{\text{Hz}}} \right)$$

The RMS noise voltage of each resistor:

$$\sqrt{v_n^2} = \sqrt{4kTR} = \sqrt{i_n^2 \cdot R} = 9.1 \times 10^{-13} \times \frac{20 \times 20}{20 + 20} = 9.1 \left(\frac{\text{nV}}{\sqrt{\text{Hz}}} \right)$$

$$\overline{(v_{\text{out}})^2} = \int_{f_L}^{f_H} \overline{(v_T)^2} df = \int_0^{100\text{kHz}} 9.1^2 + 9.1^2 df = 165.6 \times 10^{13} \text{V}^2$$

$$\overline{(v_{\text{out}})^2} = \int_{f_L}^{f_H} \overline{(v_T)^2} df = \int_0^{100\text{kHz}} 9.1^2 + 9.1^2 df = 165.6 \times 10^{13} \text{V}^2$$

$$\sqrt{\overline{(v_{\text{out}})^2}} = 4.07 \mu\text{V}$$

$$\sqrt{\overline{(v_{\text{in}})^2}} = 4.07 \times \frac{20 + 20}{20} = 8.14 \mu\text{V}$$

Problem 7.6:

The RMS noise current of the resistor:

$$\sqrt{i^2} = \sqrt{\frac{4kT}{R}} = \sqrt{\frac{4 \times 1.38 \times 10^{-23} \times 300}{20000}} = 9.1 \times 10^{-13} \left(\frac{\text{A}}{\sqrt{\text{Hz}}} \right)$$


$$\overline{(v_{\text{out}})^2} = \frac{(i_{20k})^2 \cdot R^2}{2\sqrt{pRC}} \left[\tan(2\sqrt{pRC} f_H)^{(-1)} - \tan(2\sqrt{pRC} f_L)^{(-1)} \right] = 0.412 \text{ nV}^2$$

$$\therefore \sqrt{(v_{\text{out}})^2} = 2.03 \mu\text{V}$$

Because
$$\frac{v_{\text{out}}}{v_{\text{in}}} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$

$$\overline{(v_{\text{in}})^2} = \int_{f_L}^{f_H} \frac{i^2}{(2\pi C f)^2} df = \frac{\sqrt{i^2}}{2\pi C} \left(-\frac{1}{100\text{MHz}} + \frac{1}{0} \right) = \infty$$

2) for pmos,

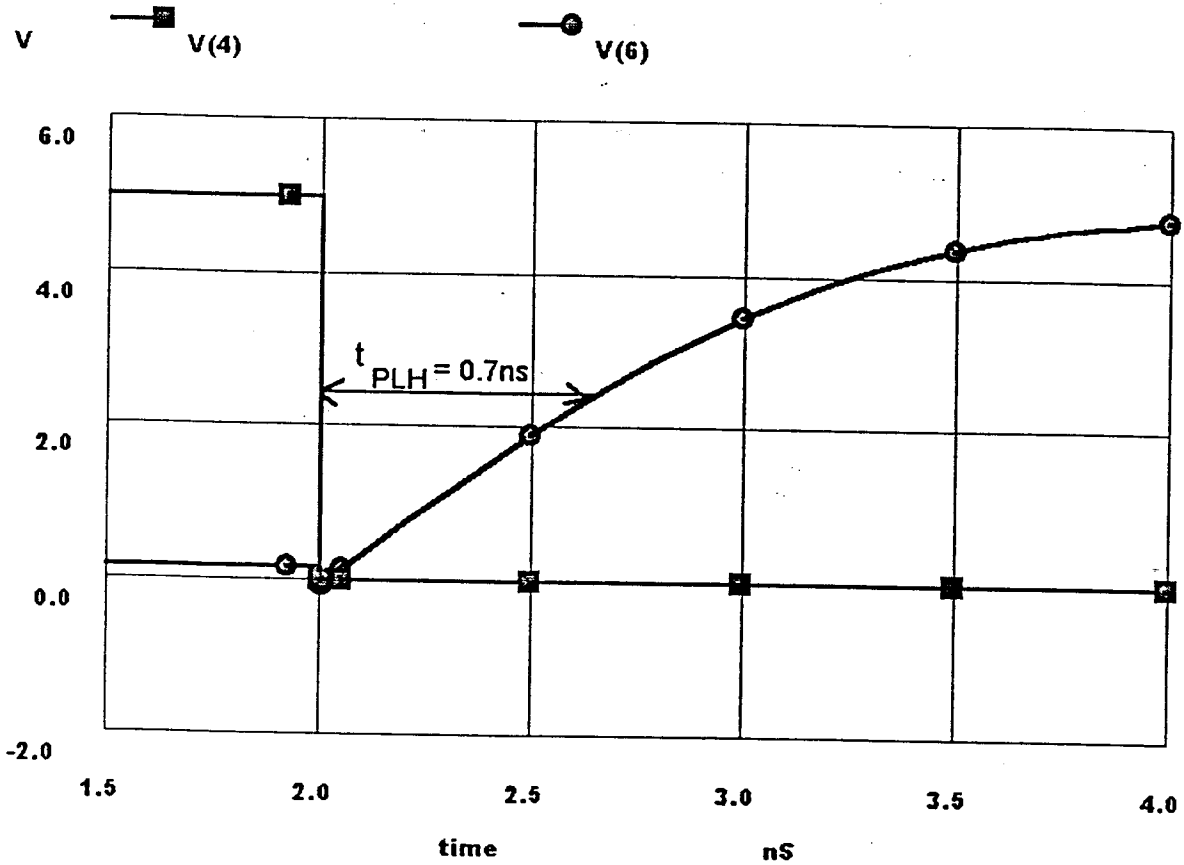

3) netlist

```

C1 3 0 150f IC=5 C2 6 0 50f IC=0
M1 0 2 3 0 CMOSNB L=2u W=10u
M2 5 4 6 5 CMOSP B L=2u W=10u
V1 2 0 DC 0 AC 5 0 PULSE(0 5 2n 1p 0 5n 10n)
V2 4 0 DC 0 AC 0 0 PULSE(5 0 2n 1p 0 5n 10n)
V3 5 0 DC 5 AC 0 0
.MODEL CMOSNB NMOS LEVEL=4 ...appendix A
.MODEL CMOSP B PMOS LEVEL=4 ...appendix A
***** End of spice models and macro models *****
.OPTION ABSTOL=1u ITL4=100 RELTOL=0.01 VNTOL=0.1mv
.tran 1n 5n 0 0.01n uic
.end

```