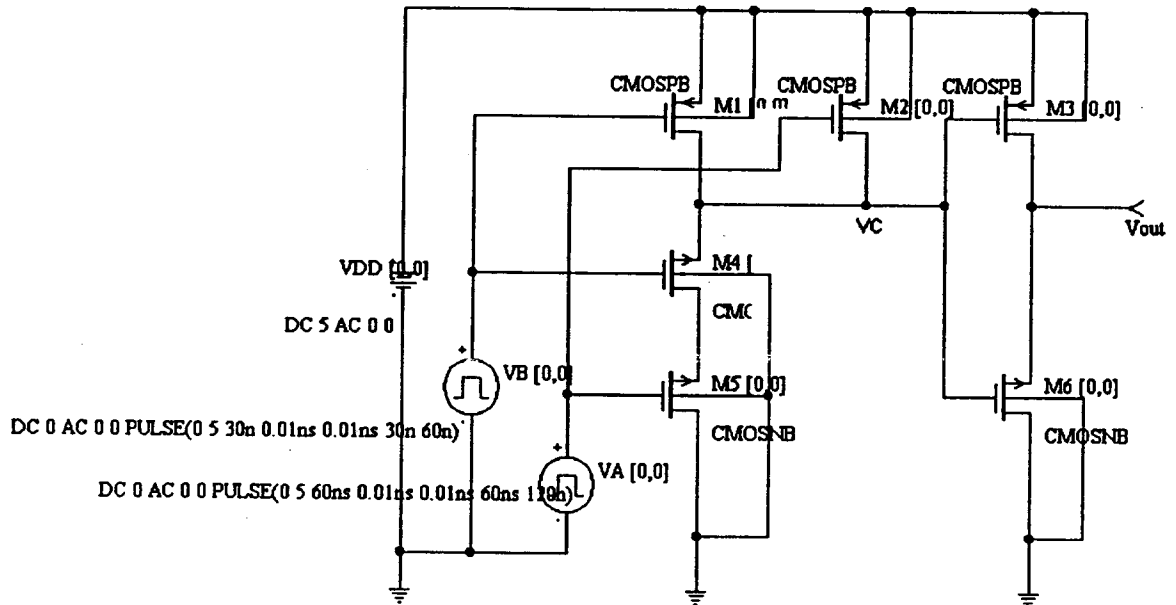


Problem 12.1

Solution: a) Design and hand-cal: The 2-input CMOS AND gate circuit diagram is shown below which consists of two parts NAND and INVERTOR cascaded:



To find V_{sp} , tie input A and B together as V_{in} . From NAND gate part, ignoring the body effect, we have

$$V_c = V_{in} = V_{sp} = \frac{\sqrt{\frac{\beta_n}{4\beta_p}} V_{thn} + (V_{dd} - V_{thp})}{1 + \sqrt{\frac{\beta_n}{4\beta_p}}} \quad (12.1a)$$

$$V_{out} = V_c = V_{sp} = \frac{\sqrt{\frac{\beta_n}{\beta_p}} V_{thn} + (V_{dd} - V_{thp})}{1 + \sqrt{\frac{\beta_n}{\beta_p}}} \quad (12.1b)$$

$V_{thn}=0.83V$, $V_{thp}=0.91V$, choosing all the length of CMOS $L=2\mu$, all $W_p=3\mu$ for p-channel. Let both V_{sp} expression equals to $1.5V$, $\implies W_4=W_5=60\mu$, $W_6=15\mu$.

b) Spice simulation: The following netlist was simulated on TurboSim:

Problem 12.1 (cont.)

*** (TurboSim V 1.1) Netlist for C:\TSE504\PI201DC.CKT

*** Top Level Netlist ***

```
M1 1 6 2 2 CMOSPB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M2 1 6 2 2 CMOSPB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M3 Vout 1 2 2 CMOSPB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M4 4 6 1 0 CMOSNB L=2u W=60u AD=3600p AS=360p PD=132u PS=132u
M5 0 6 4 0 CMOSNB L=2u W=60u AD=360p AS=360p PD=132u PS=132u
M6 0 1 Vout 0 CMOSNB L=2u W=15u AD=90p AS=90p PD=42u PS=42u
VDD 2 0 DC 5 AC 0 0
Vin 6 0 DC 1 AC 0 0
```

***** Spice models and macro models *****


```
.MODEL CMOSPB PMOS LEVEL=4
** PMOS BSIM parameters **
```

```
.Model CMOSNB NMOS LEVEL=4
** NMOS BSIM parameters **
```


***** End of spice models and macro models *****

```
.OPTION ABSTOL=1m CHGTOL=1n ITL1=1000 ITL2=1000 ITL4=10 RELTOL=0.1
+ VNTOL=10mv
.DC Vin 0 5 0.1
.end
```

which produce the following plot. It gives V_{sp} 1.5V exact same as the hand calculation.

 


Problem 12.1 (cont.)

 

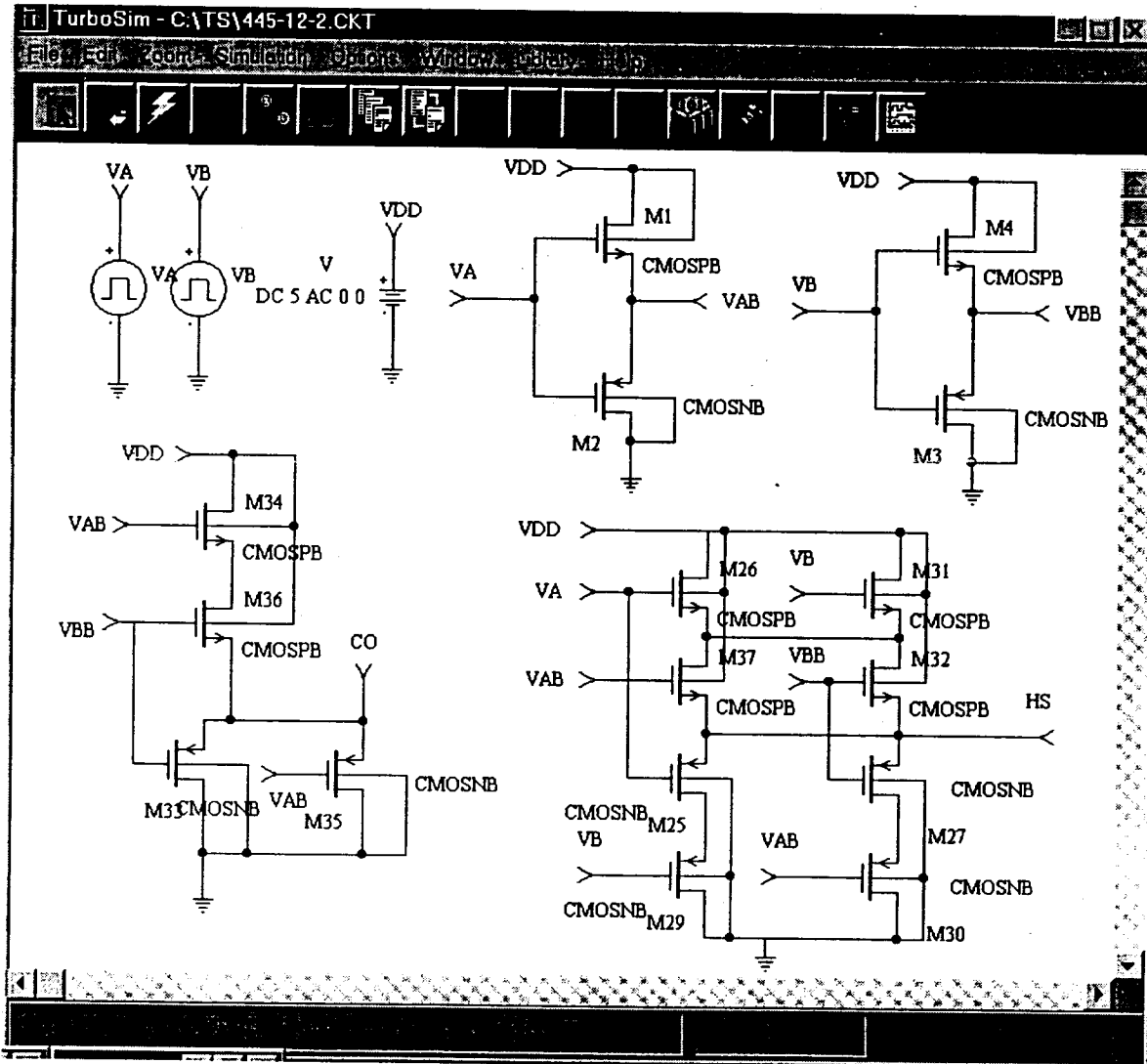Problem 12.2

Solution: The following schematic using AOI to build a half adder is simulated on TurboSim:



*** (TurboSim V 1.87) Netlist for C:\TS\445-12-2.CKT

*** Top Level Netlist ***

```

M1      VDD VA VAB VDD CMOSPB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M2      0 VA VAB 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M25     8 VA HS 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M26     VDD VA 7 VDD CMOSPB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M27     6 VBB HS 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M29     0 VB 8 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M3      0 VB VBB 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M30     0 VAB 6 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M31     VDD VB 7 VDD CMOSPB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M32     7 VBB HS VDD CMOSPB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
    
```

```

M33 0 VBB CO 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M34 VDD VAB 10 VDD CMOSP B L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M35 0 VAB CO 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M36 10 VBB CO VDD CMOSP B L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M37 7 VAB HS VDD CMOSP B L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M4   VDD VB VBB VDD CMOSP B L=2u W=3u AD=36p AS=36p PD=24u PS=24u
V    VDD 0 DC 5 AC 0 0
VA   VA 0 DC 0 AC 0 0 PULSE(0 5 1u 5ns 5ns 2u 4u)
VB   VB 0 DC 0 AC 0 0 PULSE(0 5 4u 5ns 5ns 2u 4u)

```

***** Spice models and macro models *****

```

.MODEL CMOSNB NMOS LEVEL=4
.MODEL CMOSP B PMOS LEVEL=4


```

***** End of spice models and macro models *****

```

.OPTION ABSTOL=1u CHGTOL=1p ITL2=500 ITL4=400 RELTOL=0.01 VNTOL=5m
.tran 5ns 6u 0 5n
.end

```

 

Problem 12.3

Solution: For N-input NOR gate, we have:

$$t_{PLH} = NRp(Coutp / N + NCoutn + Cload) + 0.35RpCinp(N - 1)^2 \quad (12.3a)$$

$$t_{PHL} = (Rn / N)(NCoutn + Coutp / N + Cload) \quad (12.3b)$$

With minimum size MOSFET, $Rn=8k\Omega$, $Rp=24k\Omega$, $Coutn=Coutp=4.8fF$, $Cinp=7.2fF$. and 3input.

a) With $Cload=0$:

$$t_{PLH} = 3 \times 24k(4.8f / 3 + 3 \times 4.8f + 0) + 0.35 \times 24k \times 7.2f(3 - 1)^2 = 1.394ns$$

$$t_{PHL} = (8k / 3)(3 \times 4.8f + 4.8f / 3 + 0) = 42.67ps$$

b) With $Cload=100fF$:

$$t_{PLH} = 3 \times 24k(4.8f / 3 + 3 \times 4.8f + 100) + 0.35 \times 24k \times 7.2f(3 - 1)^2 = 8.594ns$$

$$t_{PHL} = (8k / 3)(3 \times 4.8f + 4.8f / 3 + 100) = 309ps$$

It can be seen that for 3-input NOR gate, the $t_{PLH} > t_{PHL}$, while for 3-input NAND gate, the $t_{PLH} < t_{PHL}$, also that the maximum delay time of NOR is bigger than the maximum delay time of NAND. Plus we already know that NAND gate has better V_{sp} and better noise margins. That is why in CMOS digital design, the NAND gate is used most often.

c) SPICE simulation is shown in the next page.

Problem 12.4

Solution: For N-input NOR gate, a more useful, but not as precise, equations to estimate the delay are:

$$t_{PLH} = NRpCload \quad (12.4a)$$

$$t_{PHL} = RnCload \quad (12.4b)$$

With minimum size MOSFET, $Rn=8k\Omega$, $Rp=24k\Omega$, $Cload=100fF$. and 3input.

$$t_{PLH} = 3 \times 24k \times 100 = 7.2ns$$

$$t_{PHL} = 8k \times 100 = 800ps$$

Problem 12.3 SPICE simulation:


Netlist:

```
*** (TurboSim V 1.1) Netlist for C:\TSVE504\H5\P1203.CKT

*** Top Level Netlist ***
C1      Vout 0 100f
M1      0 2 Vout 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M2      0 2 Vout 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M3      0 2 Vout 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M4      Vout 2 4 5 CMOSP B L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M5      4 2 6 5 CMOSP B L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M6      6 2 5 5 CMOSP B L=2u W=3u AD=36p AS=36p PD=24u PS=24u
V2      2 0      DC 0 AC 0 0 PULSE(5 0 0 5ps 5ps 30ns 60ns)
VDD     5 0      DC 5 AC 0 0


***** Spice models and macro models *****
.MODEL CMOSNB NMOS LEVEL=4
...BSIM Parameters of Appendix A...
.MODEL CMOSP B PMOS LEVEL=4
...BSIM Parameters of Appendix A...
***** End of spice models and macro models *****
.OPTION ABSTOL=1u CHGTOL=1n ITL1=500 ITL2=500 ITL4=500 RELTOL=0.1
+ VNTOL=10mv
.tran 0.1n 60n 0 0.1n
.end
```

Plot is as below, simulation gives t_{PLH} about 5ns, t_{PHL} about 300ps (when zoom in):

 

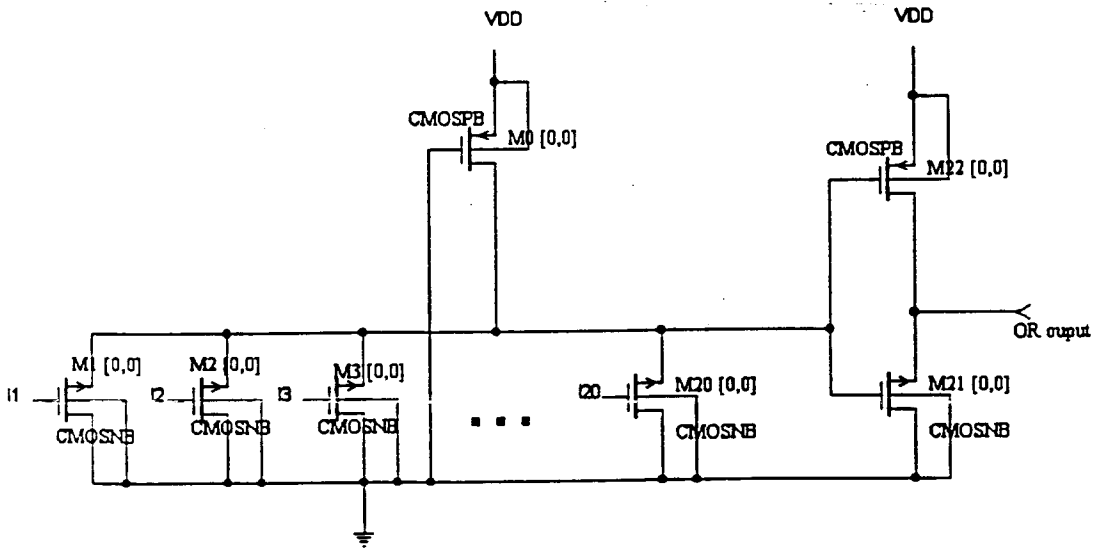Problem 12.5


Solution: The 20-input OR gate is consist of an 20-input NOR and an INVERTOR. For 20 input, the scheme of NOR shown in figure 12.4 is not practical because of the long delay time associated with the 20 p-channel MOSFET in series and requiring total 40 MOSFETs. So, the scheme of NOR shown in figure 12.11 is needed. The schematic of an OR gate with 20 inputs is shown below which uses 23 MOSFETs:



For all the n-channel MOSFET, chose $W_n=3\mu$, $L_n=2\mu$, for p-channel, chose $W_{22p}=3\mu$, $L_{22p}=2\mu$. By using equation (12.21), set V_{OL} about 500mv, get $W_{0p}=L_{0n}=3\mu$. When the ouput is low, the static power dissipation of the OR gate is about zero, but static power is dissipated when the output is high due to both n- and p-channel of NOR part conducting.

 Problem 12.6

$$Z = (A + B \cdot \bar{C}) \cdot D, \quad \bar{Z} = \bar{A}(\bar{B} + C) + \bar{D} \Rightarrow Z = \overline{\bar{A}(\bar{B} + C) + \bar{D}}$$



Chosing minimum size ($3\mu/2\mu$) for all MOSFETs.


$$R_n = 8k\Omega, \quad R_p = 24k\Omega, \quad C_{outn} = C_{outp} = C = 4.8fF.$$

Worst-case delay: \bar{B}, C, \bar{D} ON, for t_{pLH}

$$\begin{aligned} t_{pLH} &= 3R_p \cdot C_{load} + 3R_p \left[C_{outn}(\bar{D}) + \frac{C_{outn}(\bar{A}) \times 2C}{C_{outn}(\bar{A}) + 2C} + \frac{C_{outp}(\bar{D}) \times \frac{3}{2}C}{C_{outp}(\bar{D}) + \frac{3}{2}C} \right] \\ &= 3R_p \left[C_{load} + C + \frac{2}{3}C + \frac{3}{5}C \right] \\ &= 3 \times 24k\Omega \times \left(50 + \frac{34}{15} \times 4.8 \right) fF \approx \underline{\underline{4.4ns}} \end{aligned}$$

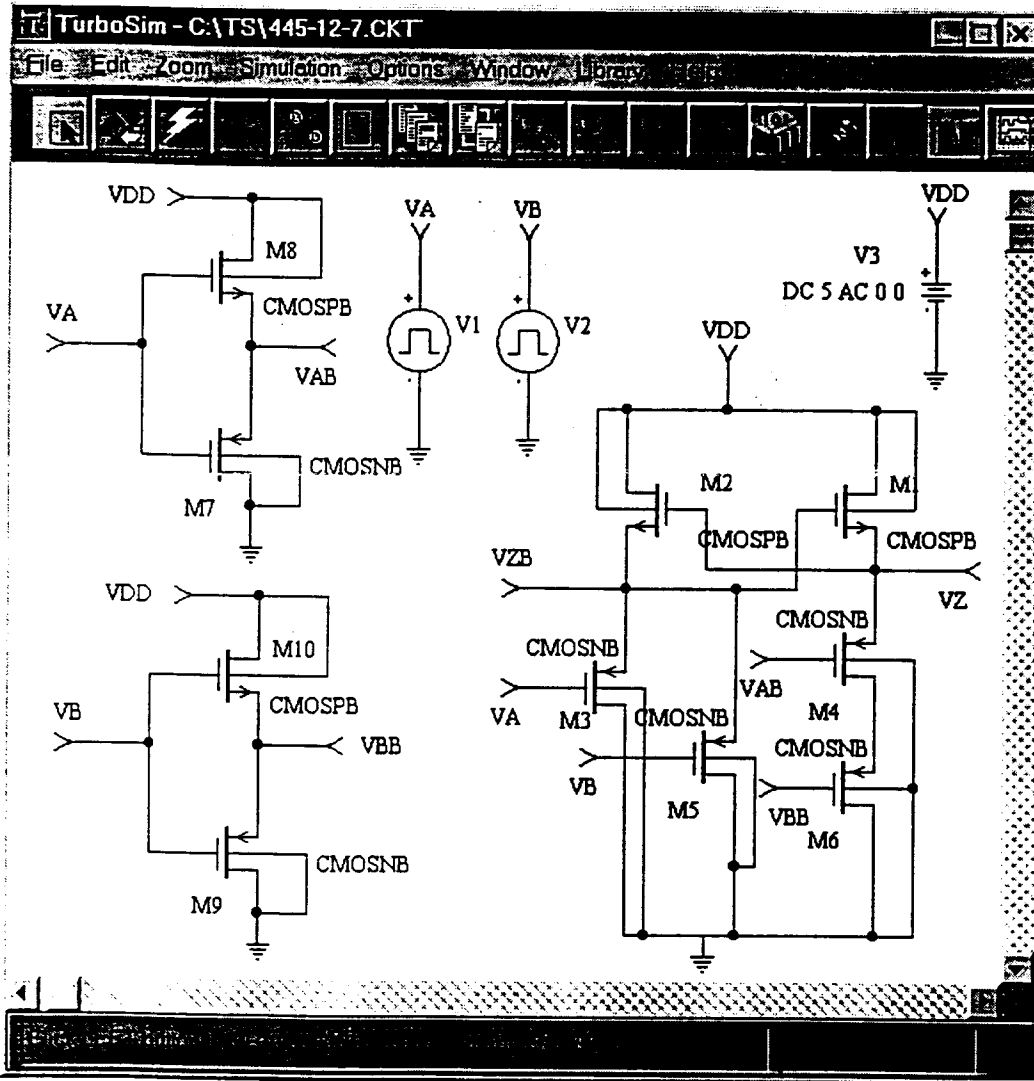Problem 12.7

The following schematic using CSVL to build a OR gate with minimum-size devices.



*** Top Level Netlist ***

```

M1    VDD VZB VZ VDD CMOSPB L=2u W=3u
M10   VDD VB VBB VDD CMOSPB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M2    VDD VZ VZB VDD CMOSPB L=2u W=3u
M3    0 VA VZB 0 CMOSNB L=2u W=3u
M4    6 VAB VZ 0 CMOSNB L=2u W=3u
M5    0 VB VZB 0 CMOSNB L=2u W=3u
M6    0 VBB 6 0 CMOSNB L=2u W=3u
M7    0 VA VAB 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M8    VDD VA VAB VDD CMOSPB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M9    0 VB VBB 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
V1    VA 0 DC 0 AC 0 0 PULSE(0 5 1u 5ns 5ns 2u 4u)
V2    VB 0 DC 0 AC 0 0 PULSE(0 5 4u 5ns 5ns 2u 4u)
V3    VDD 0 DC 5 AC 0 0
    
```


***** Spice models and macro models *****

```
.MODEL CMOSPB PMOS LEVEL=4  
.MODEL CMOSNB NMOS LEVEL=4
```

***** End of spice models and macro models *****


```
.OPTION ABSTOL=1u ITL4=100 RELTOL=.1 VNTOL=5mv  
.tran 5n 6u 0 5n  
.end
```

The simulation produced the following plot with labels.

 

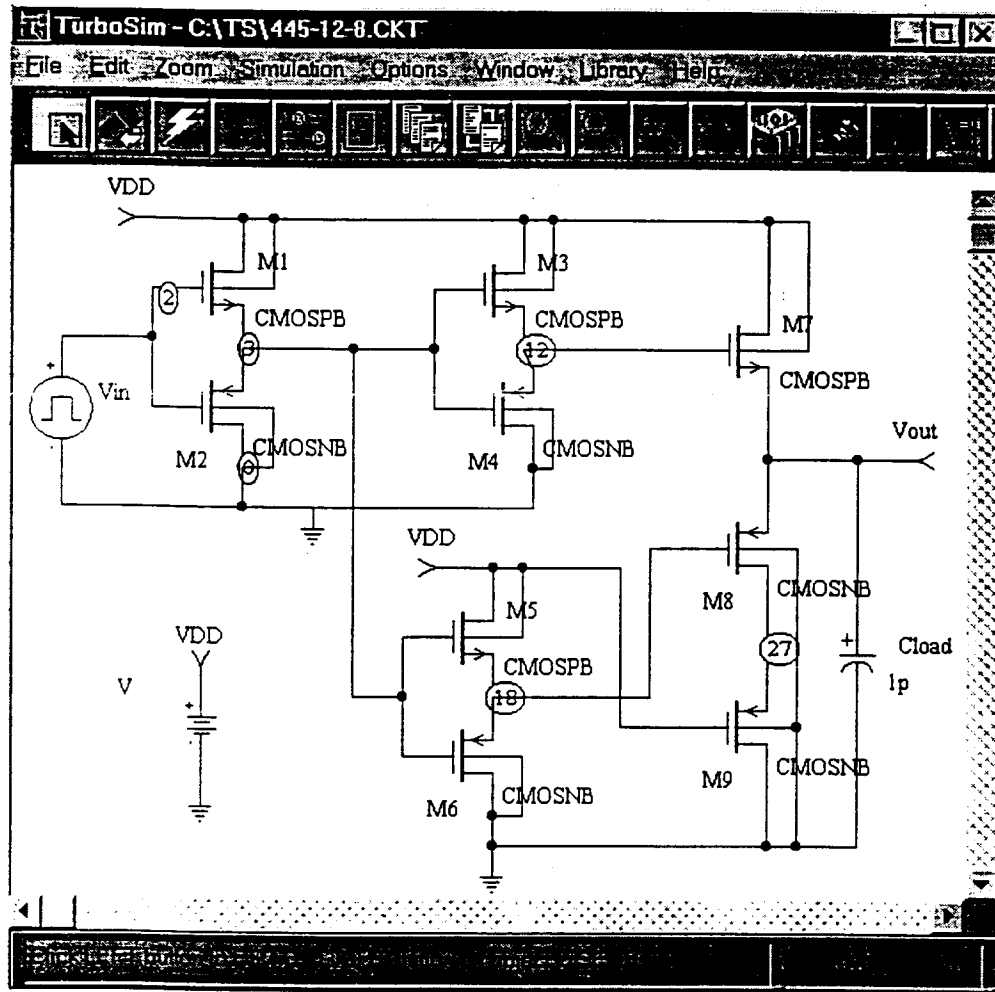Problem 2.8

Using tri-state inverting buffer (Fig 12.24), assume Enable at logic high. Design the circuit as following. The input capacitance is 48fF and the propagation delay is under 10ns.



*** Top Level Netlist ***

```


Cload  Vout 0 1p
M1     VDD 2 3 VDD CMOSPB L=2u W=10u
M2     0 2 3 0 CMOSNB L=2u W=10u
M3     VDD 3 12 VDD CMOSPB L=2u W=20u
M4     0 3 12 0 CMOSNB L=2u W=20u
M5     VDD 3 18 VDD CMOSPB L=2u W=20u
M6     0 3 18 0 CMOSNB L=2u W=20u
M7     VDD 12 Vout VDD CMOSPB L=2u W=40u
M8     27 18 Vout 0 CMOSNB L=4u W=40u
M9     0 VDD 27 0 CMOSNB L=4u W=40u
V      VDD 0 DC 5 AC 0 0
Vin    2 0    DC 0 AC 0 0 PULSE(0 5 0 1p 1p 20n 40n)
    
```

***** Spice models and macro models *****

```
.MODEL CMOSPB PMOS LEVEL=4 ...  
.MODEL CMOSNB NMOS LEVEL=4 ...
```

***** End of spice models and macro models *****

```
.OPTION ABSTOL=1u ITL4=100 RELTOL=.1 VNTOL=8m  
.tran .1 40n 0 .1n  
.end
```

 


Problem 12.9


$$z = A \oplus B \oplus C = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$\bar{z} = AB\bar{C} + A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}\bar{C}$$
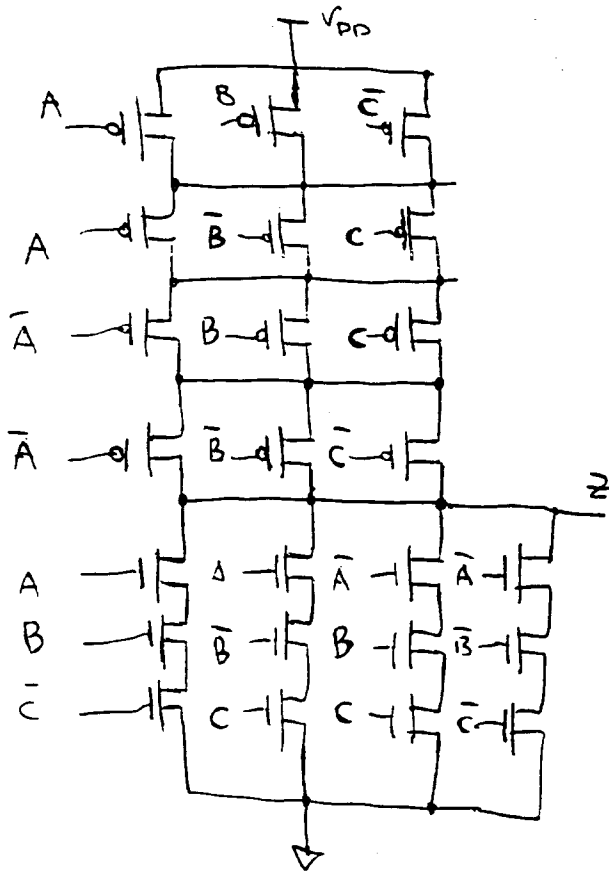
$$z = \overline{AB\bar{C} + A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}\bar{C}}$$



another implementation.

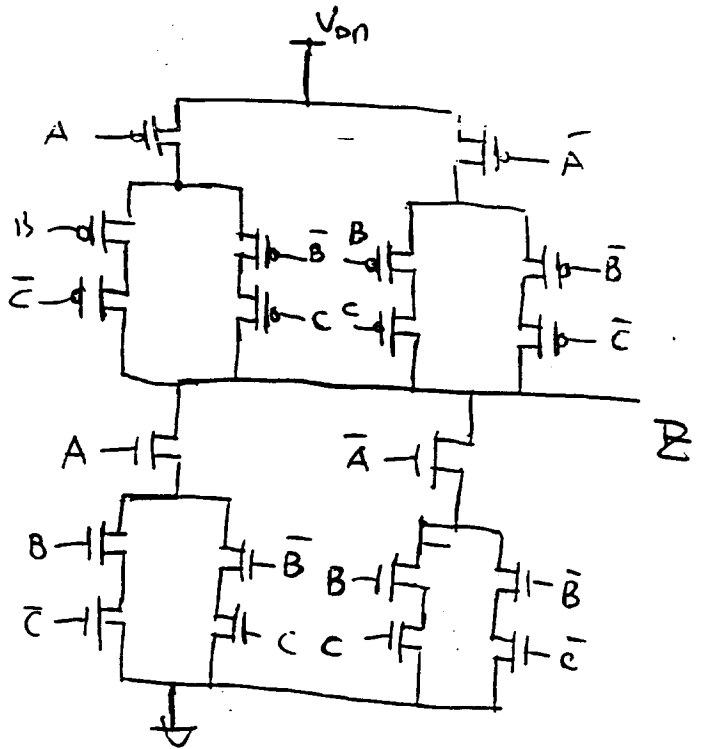

Problem 12.10:

$$Z = A(BD + CE)$$

Problem 12.11:

This is a NOR gate, and the logic function is: $OUT = \overline{A + B}$.

If we tie A and B together, it becomes an inverter. When $V_{SP} = V_{in} = V_{out}$, all of these n-MOSFETs are operated in saturation region. If we named them as M1(3/10), M2(3/2) and M3(3/2), we have (neglecting body effect):

$$\frac{\beta_1}{2} \cdot (V_{DD} - V_{SP} - V_{THN})^2 = \frac{\beta_2 + \beta_3}{2} \cdot (V_{SP} - V_{THN})^2$$
$$\therefore V_{SP} = \frac{\left(\sqrt{\frac{\beta_2 + \beta_3}{\beta_1}} - 1 \right) \cdot V_{THN} + V_{DD}}{1 + \sqrt{\frac{\beta_2 + \beta_3}{\beta_1}}}$$

Because $\beta = KP_n \cdot \frac{W}{L}$, $\frac{\beta_2 + \beta_3}{\beta_1} = 1$. Using $V_{DD} = 5V$, $V_{THN} = 0.83V$,

$$V_{SP} \approx 1.632V.$$

Problem 12.12:

$$V_{out(MAX)} = V_{DD} - V_{THN} \approx 3.5V \text{ (Body-effect).}$$

For minimum output voltage, the $V_{out(MIN)} \approx 0$. If using current equations, the output voltage is slightly higher than 0.


Problem 12.13:

If we use 4 basic CMOS inverters (assume each MOSFET has same size) to form the delay buffer, the delay time of this buffer,

$$t_d = 2(t_{PHL} + t_{PLH}) = 2(R_n + R_p)C_{tot} = 2(12k + 36k) \times (L/W) \times 5 \times C'_{ox} \times W \times L$$

$$t_d = 0.384 \times L^2 \text{ (ns).}$$

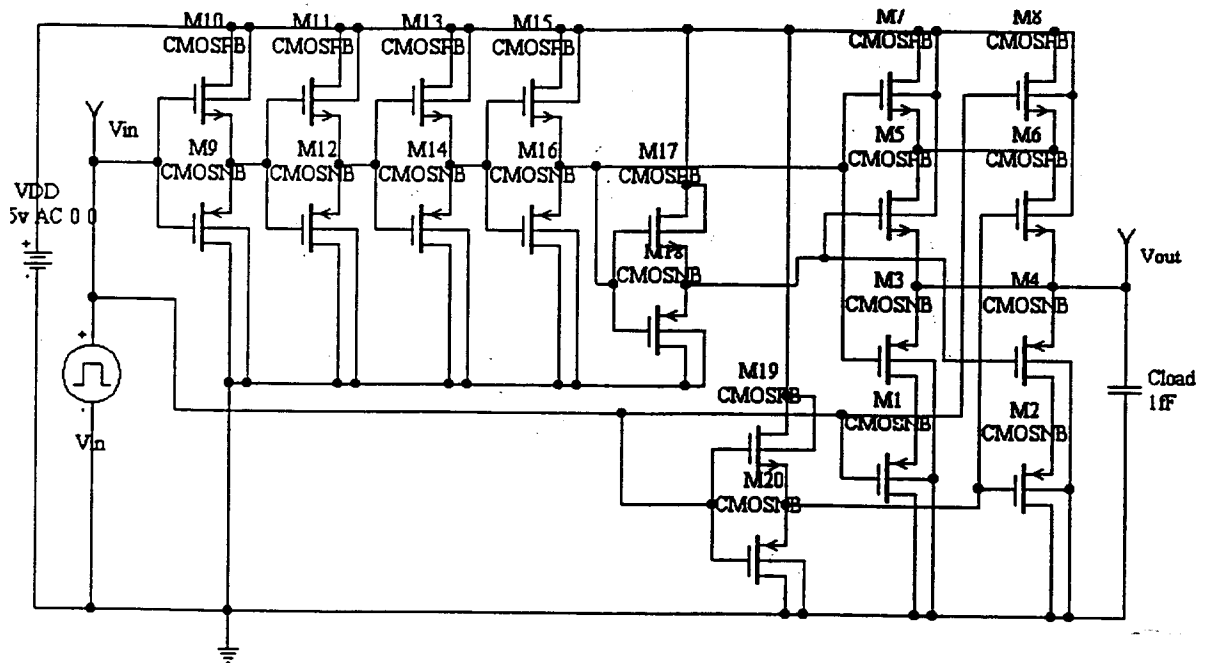If $t_d = 10ns$, we can get $L \approx 5.1\mu m$. If we use $L = 6\mu m$, $W = 3\mu m$ for the delay buffer, we use minimum size (3/2) in other MOSFET, the BISM simulating circuit is shown below:



*** Top Level Netlist ***

```

Cload  Vout 0 1fF
M1     0 Vin 1 0 CMOSNB L=2u W=3u
M10    5 Vin 6 5 CMOSP B L=6u W=3u
M11    5 6 7 5 CMOSP B L=6u W=3u
M12    0 6 7 0 CMOSNB L=6u W=3u
M13    5 7 8 5 CMOSP B L=6u W=3u
M14    0 7 8 0 CMOSNB L=6u W=3u
M15    5 8 9 5 CMOSP B L=6u W=3u
M16    0 8 9 0 CMOSNB L=6u W=3u
M17    5 9 10 5 CMOSP B L=2u W=3u
M18    0 9 10 0 CMOSNB L=2u W=3u
M19    5 Vin 3 5 CMOSP B L=2u W=3u
M2     0 3 2 0 CMOSNB L=2u W=3u
M20    0 Vin 3 0 CMOSNB L=2u W=3u
M3     1 9 Vout 0 CMOSNB L=2u W=3u
M4     2 10 Vout 0 CMOSNB L=2u W=3u
M5     4 10 Vout 5 CMOSP B L=2u W=3u
M6     4 3 Vout 5 CMOSP B L=2u W=3u
M7     5 9 4 5 CMOSP B L=2u W=3u
M8     5 Vin 4 5 CMOSP B L=2u W=3u
M9     0 Vin 6 0 CMOSNB L=6u W=3u
VDD    5 0 DC 5v AC 0 0
Vin    Vin 0 DC 0 AC 0 0 PULSE(0 5v 2n .1n .1n 30n 60n)

```

***** Spice models and macro models *****

```

.MODEL CMOSNB NMOS LEVEL=4 ...
.MODEL CMOSP B PMOS LEVEL=4 ...


```

***** End of spice models and macro models *****

```

.OPTION ABSTOL=1u ITL4=1000 RELTOL=0.1 VNTOL=8mv
.tran .1ns 100ns 0 .1ns uic
.end

```

 

If the width of the input pulse is less than 10ns, the output cannot trigger the rise and fall edges of input pulse exactly. The result is shown below with input pulse width = 5ns.

