

Chapter 13

Problem 13.1

*** Top Level Netlist ***

```
C2      0 VOUT2 100f IC=0
C3      VOUT1 0 100f IC=5v
M2      2 VG VOUT2 0 CMOSNB L=2u W=3u OFF
M3      VOUT1 VG 0 0 CMOSNB L=2u W=3u
VDD     2 0    DC 5 AC 0 0
VG      VG 0   DC 0 AC 0 0 PULSE(0 5 5n 1p 1p 20n 40n)
```


***** Spice models and macro models *****

```
.MODEL CMOSNB NMOS LEVEL=4
+VFB=-9.73820E-01, LVFB=3.67458E-01, WVFB=-4.72340E-02
... ..
+pbsw=0.8  mj=0.66036  mjsw=0.178543  wdf=0  dell=0
```

 ***** End of spice models and macro models *****

```
.OPTION ABSTOL=1m RELTOL=0.1 VNTOL=10mv
.tran 0.1n 20n 0 0.1n uic
.end
```


The SPICE simulation result is shown below:



SPICE simulation showed T_{plh} is about 0.58nS and T_{phl} is about 0.6nS. If we increase the width of the MOSFETs, since the load capacitance is relatively larger than the parasitic capacitance of MOSFET, although parasitic capacitance increases along with resistance of MOSFET decreasing, the total delay time will decrease. However, the internal logic driving this circuit will see an increase of its load capacitance.

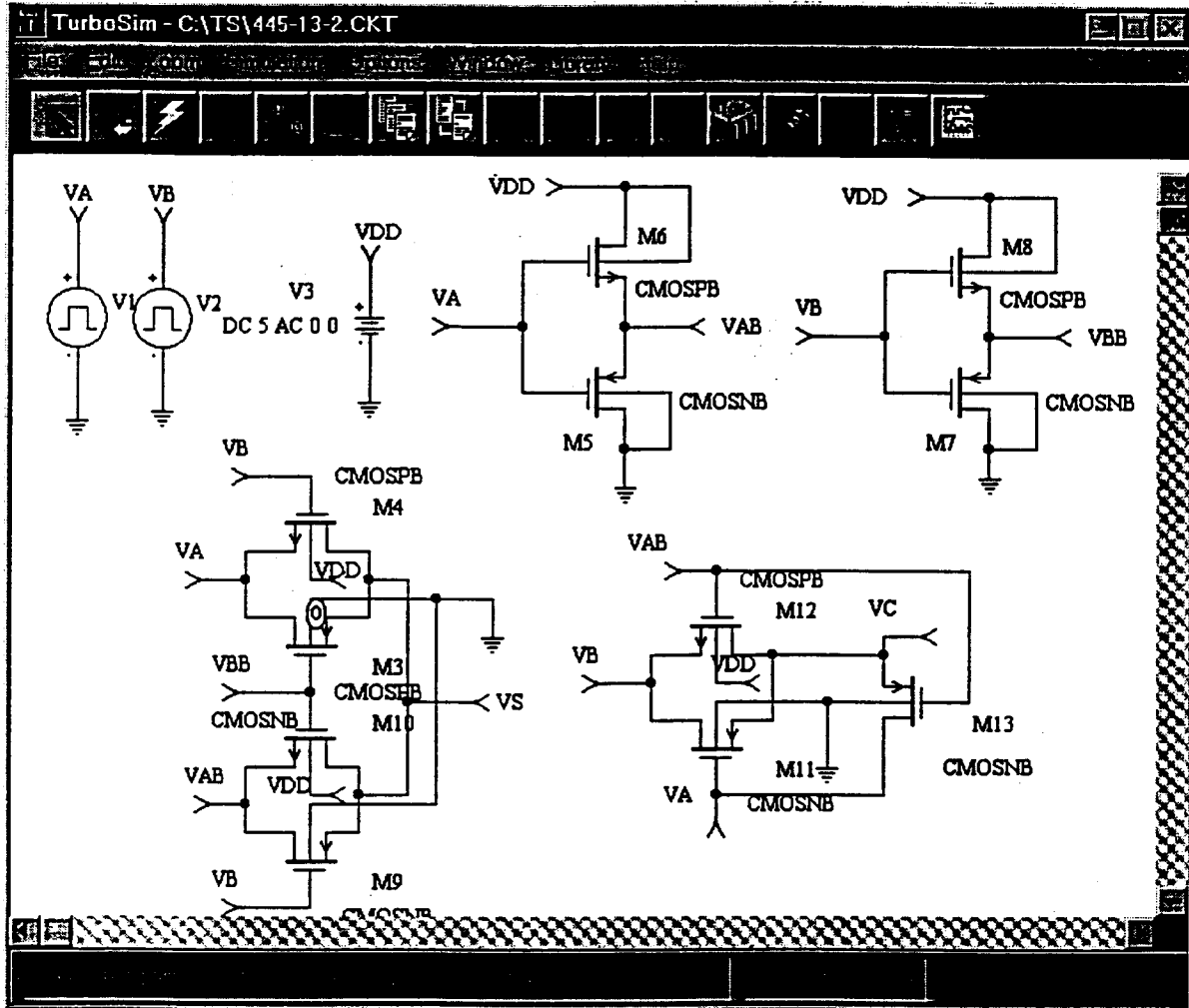Problem 13.2

Design and simulate the operation of a half adder circuit using Tgs.



*** Top Level Netlist ***

```

M10  VS VBB VAB VDD CMOSPB L=2u W=3u
M11  VB VA VC 0 CMOSNB L=2u W=3u
M12  VC VAB VB VDD CMOSPB L=2u W=3u
M13  VA VAB VC 0 CMOSNB
M3   VA VBB VS 0 CMOSNB L=2u W=3u
M4   VS VB VA VDD CMOSPB L=2u W=3u
M5   0 VA VAB 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M6   VDD VA VAB VDD CMOSPB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M7   0 VB VBB 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M8   VDD VB VBB VDD CMOSPB L=2u W=3u AD=36p AS=36p PD=24u PS=24u
M9   VAB VB VS 0 CMOSNB L=2u W=3u
V1   VA 0 DC 0 AC 0 0 PULSE(0 5 1u 5ns 5ns 2u 4u)
V2   VB 0 DC 0 AC 0 0 PULSE(0 5 4u 5ns 5ns 2u 4u)
V3   VDD 0 DC 5 AC 0 0

```


***** Spice models and macro models *****

```
.MODEL CMOSNB NMOS LEVEL=4 ...
.MODEL CMOSPB PMOS LEVEL=4 ...
```

***** End of spice models and macro models *****

```
.OPTION ABSTOL=1u ITL4=100 RELTOL=.1 VNTOL=2mv
.tran 10n 10u 0
.end
```

Simulation results:

 


Problem 13.3

Series connection of 10 TGs, the delay to drive a 100fF load capacitance can be estimated: (using minimum size MOSFETs)

$$t_{PHL} = t_{PLH} = 10 \times (8k\Omega || 24k\Omega) \times 100fF + .35 \times (8k\Omega || 24k\Omega) \times (4.8fF + 4.8fF) \times 1.5 \times 100 \approx 9 \text{ ns}$$

SPICE simulation results:

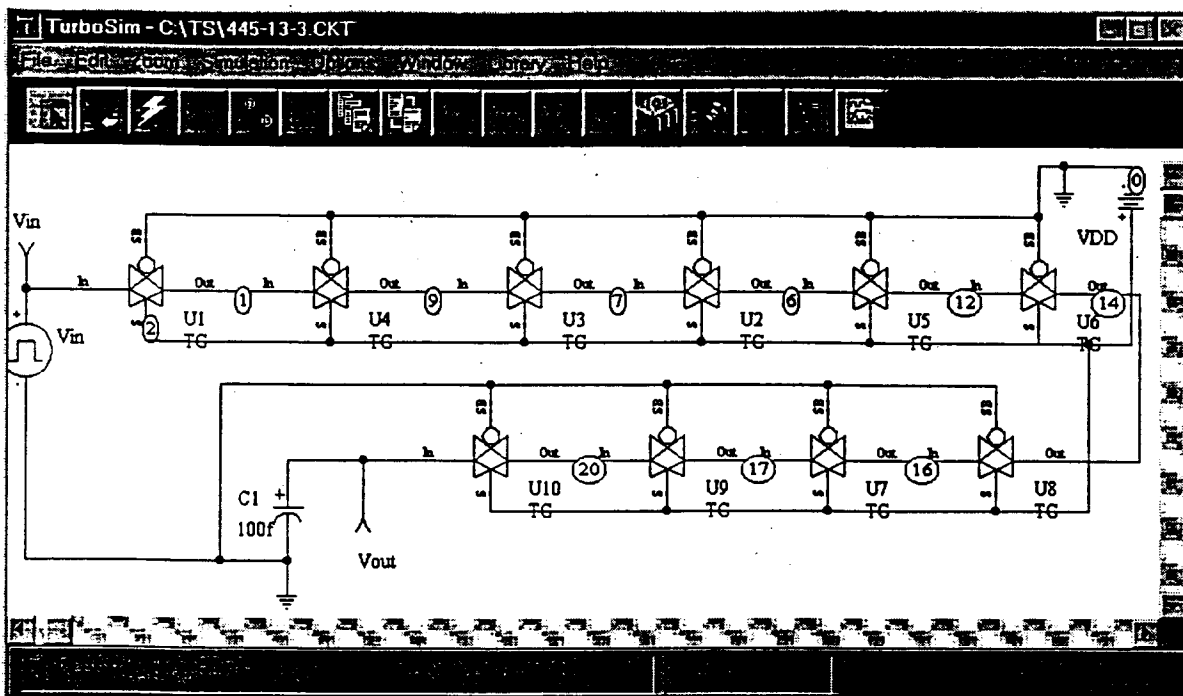

```

.subckt tg.sub 3 2 6 1
M1      1 2 3 0 CMOSNB L=2u W=3u
M2      3 6 1 8 CMOSP B L=2u W=3u
VDD     8 0    DC 5 AC 0 0
.ends tg.sub

*** Top Level Netlist ***
C1      Vout 0 100f
XU1     1 2 0 Vin      tg.sub
XU10    20 2 0 Vout    tg.sub
XU2     6 2 0 7 tg.sub
XU3     7 2 0 9 tg.sub
XU4     9 2 0 1 tg.sub
XU5     12 2 0 6tg.sub
XU6     14 2 0 12      tg.sub
XU7     16 2 0 17      tg.sub
XU8     14 2 0 16      tg.sub
XU9     17 2 0 20      tg.sub
VDD     2 0    DC 5 AC 0 0
Vin     Vin 0  DC 0 AC 0 0 PULSE(0 5 5n .1n .1n 80n 160n)

***** Spice models and macro models *****

.MODEL CMOSNB NMOS LEVEL=4 ...
.MODEL CMOSP B PMOS LEVEL=4 ...


***** End of spice models and macro models *****


.OPTION ABSTOL=1u ITL4=100 RELTOL=.1 VNTOL=8mv
.tran .1n 150n 0
.end

```

see next page for SPICE simulation results of problem 13.3

Problem 13.4

 


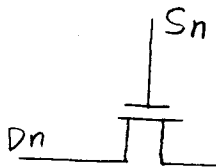where X =  Z_{OUT} or Source (Drain) of next passing transistor.

If $C_{load} = 50 \text{ fF}$, the total delay is (assuming minimum size)

$$\begin{aligned}
 t_d &= 0.35 \times 2.5 C_{ox} \times R_n \times N^2 + N \times R_n \times C_{load} \\
 &= 0.35 \times 2.5 \times 800 \text{ aF}/\mu\text{m}^2 \times 6 \mu\text{m}^2 \times 8 \text{ k} \times 9 + 3 \times 8 \text{ k} \times 50 \text{ fF} \\
 &\approx 1.5 \text{ nS}.
 \end{aligned}$$

Simulation result of Problem 13-3

 

From SPICE simulation, the delay is about 10ns.

Problem 13.5

SPICE simulation for XORgate used Tgs.

*** (TurboSim V 1.87) Netlist for C:\TSS\445-13-4.CKT

* _

.subckt tg.sub 3 2 6 1

M1 1 2 3 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u NRD=1 NRS=1

M2 3 6 1 8 CMOSP B L=2u W=3u AD=36p AS=36p PD=24u PS=24u NRD=1 NRS=1

VDD 8 0 DC 5 AC 0 0

.ends tg.sub

*** Top Level Netlist ***

M5 0 VA VAB 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u

M6 VDD VA VAB VDD CMOSP B L=2u W=3u AD=36p AS=36p PD=24u PS=24u

M7 0 VB VBB 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u

M8 VDD VB VBB VDD CMOSP B L=2u W=3u AD=36p AS=36p PD=24u PS=24u

XU1 OUT VBB VB VA tg.sub

XU2 OUT VB VBB VAB tg.sub

V1 VA 0 DC 0 AC 0 0 PULSE(0 5 1u 5ns 5ns 2u 4u)

V2 VB 0 DC 0 AC 0 0 PULSE(0 5 4u 5ns 5ns 2u 4u)


V3 VDD 0 DC 5 AC 0 0

***** Spice models and macro models *****

```
.MODEL CMOSNB NMOS LEVEL=4 ...
.MODEL CMOSPB PMOS LEVEL=4 ...
```

```
***** End of spice models and macro models *****
```

```
.OPTION ABSTOL=50u RELTOL=.1 VNTOL=5m
.tran 10n 10u 100n 50n
.end
```

 

Problem 13.6

Using minimum-size MOSFETs NAND gates to realize the SR FF. the netlist and simulation results are followed.

```
*** (TurboSim V 1.87) Netlist for C:\TS\445-13-6.CKT
```

```
* --
```

```
.subckt NAND.sub 6 4 5
```

```
M10 2 6 5 2 CMOSPB L=2u W=3u
```

```
M11 2 4 5 2 CMOSPB L=2u W=3u
```

```
M7 1 6 5 0 CMOSNB L=2u W=3u
```

```
M8 0 4 1 0 CMOSNB L=2u W=3u
```

```
V1 2 0 DC 5 AC 0 0
```

```
.ends NAND.sub
```

```
*** Top Level Netlist ***
```

```

XU1  S VQ VQB  NAND.sub
XU2  R VQB VQ  NAND.sub
VR   R 0      DC 0 AC 0 0 PULSE(0 5 5u 5ns 5ns 3u 6u)
VS   S 0      DC 0 AC 0 0 PULSE(0 5 1u 5ns 5ns 2u 5u)

```

***** Spice models and macro models *****

```

.MODEL CMOSNB NMOS LEVEL=4 ...
.MODEL CMOSPB PMOS LEVEL=4 ...


```

***** End of spice models and macro models *****


```

.OPTION ABSTOL=50u RELTOL=.1 VNTOL=5m
.tran 10n 10u 100n 50n
.end

```

 

Problem 13.7

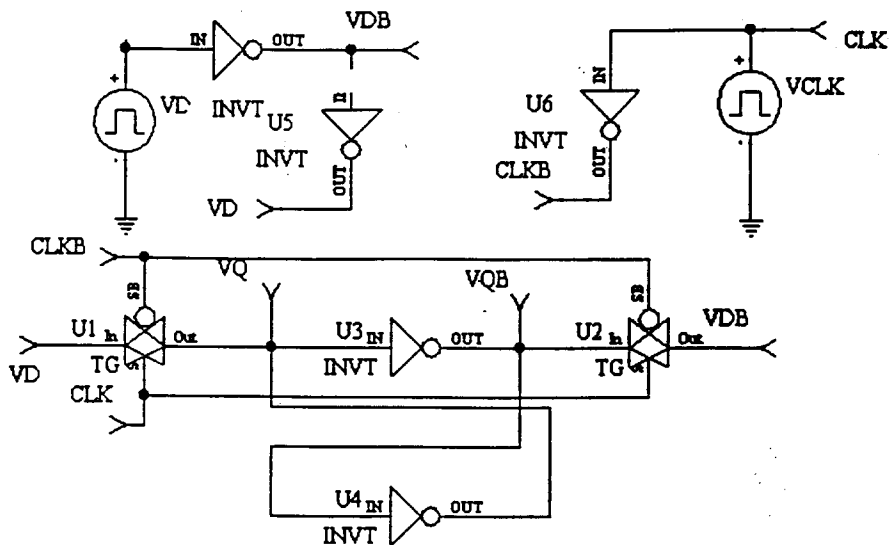

*** (TurboSim V 1.87) Netlist for C:\TS\CIRCUITS\445-13-7.CKT

```
* _
.subckt tg.sub 3 2 6 1
M1 1 2 3 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u NRD=1 NRS=1
M2 3 6 1 8 CMOSPFB L=2u W=3u AD=36p AS=36p PD=24u PS=24u NRD=1 NRS=1
VDD 8 0 DC 5 AC 0 0
.ends tg.sub
```

```
* _
.subckt inverter.sub 2 3
M1 0 2 3 0 CMOSNB L=2u W=3u AD=36p AS=36p PD=24u PS=24u NRD=1 NRS=1
M2 4 2 3 4 CMOSPFB L=2u W=3u AD=36p AS=36p PD=24u PS=24u NRD=1 NRS=1
VDD 4 0 DC 5 AC 0 0
.ends inverter.sub
```


```
*** Top Level Netlist ***
XU1 VQ CLK CLKB VD tg.sub
XU17 13 VDB inverter.sub
XU2 VDB CLK CLKB VQB tg.sub
XU3 VQ VQB inverter.sub
XU4 VQB VQ inverter.sub
XU5 VDB VD inverter.sub
XU6 CLK CLKB inverter.sub
VCLK CLK 0 DC 0 AC 0 0 PULSE(0 5 10n 5ns 5ns 20n 50n)
VD 13 0 DC 0 AC 0 0 PULSE(0 5 5n 5ns 5ns 15n 60n)
```

***** Spice models and macro models *****

```
.MODEL CMOSNB NMOS LEVEL=4
.MODEL CMOSPFB PMOS LEVEL=4
```

***** End of spice models and macro models *****


```
.OPTION ABSTOL=10u RELTOL=.01 VNTOL=5m  
.tran 1n 150n 0 1n  
.end
```

 

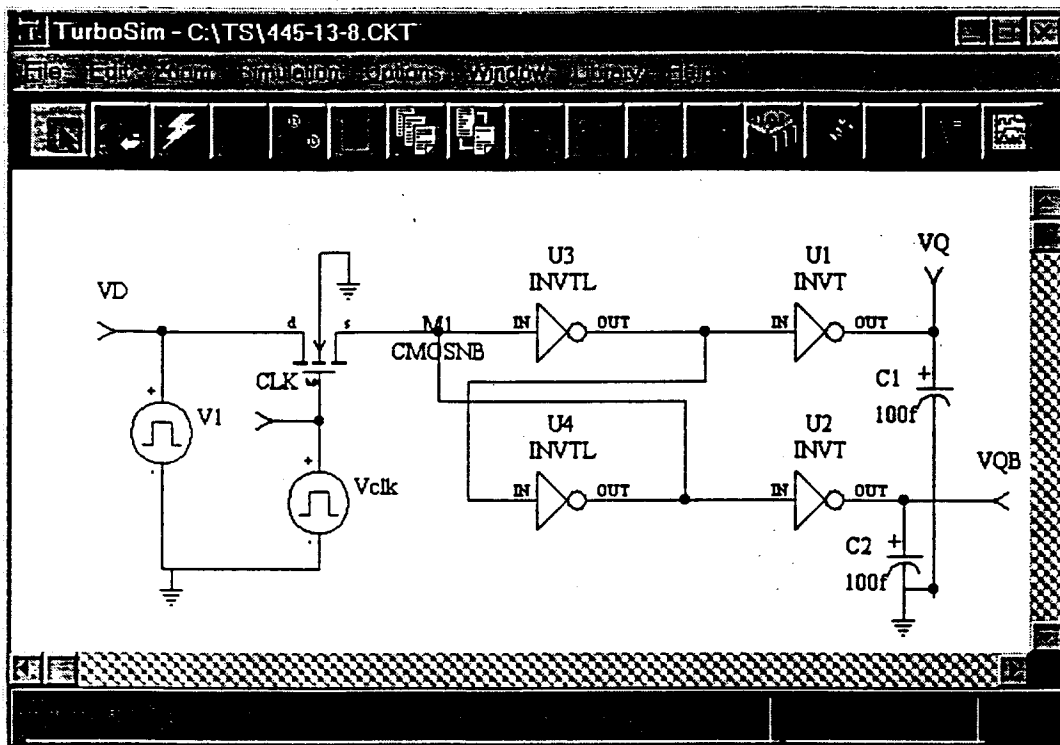Problem 13.8

In order to change the voltage at outputs of U4, the effective digital resistances of this inverters is made large and sinks small current which is provided by the input driver and pass transistor, in another words, make U4 the long L inverter.

The circuit for SPICE simulation is shown below



The netlist of this design is shown below.

*** (TurboSim V 1.87) Netlist for C:\TS\445-13-8.CKT

* --

.subckt invtl.sub 2 3

M1 0 2 3 0 CMOSNB L=15u W=3u

M2 4 2 3 4 CMOSPFB L=15u W=3u

VDD 4 0 DC 5 AC 0 0

.ends invtl.sub

* --

.subckt inverter.sub 2 3

M1 0 2 3 0 CMOSNB L=2u W=3u

M2 4 2 3 4 CMOSPFB L=2u W=3u

VDD 4 0 DC 5 AC 0 0

.ends inverter.sub

*** Top Level Netlist ***

C1 VQ 0 100f

C2 VQB 0 100f

M1 VD CLK 13 0 CMOSNB L=6u W=9u

XU1 10 VQ inverter.sub

XU2 13 VQB inverter.sub

XU3 13 10 invtl.sub

XU4 10 13 invtl.sub

V1 VD 0 DC 0 AC 0 0 PULSE(0 5 10n .1n .1n .5u 1u)

Vclk CLK 0 DC 0 AC 0 0 PULSE(0 5 50n .1n .1n 200n 400n)


***** Spice models and macro models *****

```
.MODEL CMOSNB NMOS LEVEL=4 ...  
.MODEL CMOSPB PMOS LEVEL=4 ...
```


```
***** End of spice models and macro models *****
```

```
.OPTION ABSTOL=1u ITL4=100 RELTOL=.1 VNTOL=5mv  
.tran In 4u 0 10n  
.end
```

The simulation result is shown below.

 

Problem 13.9

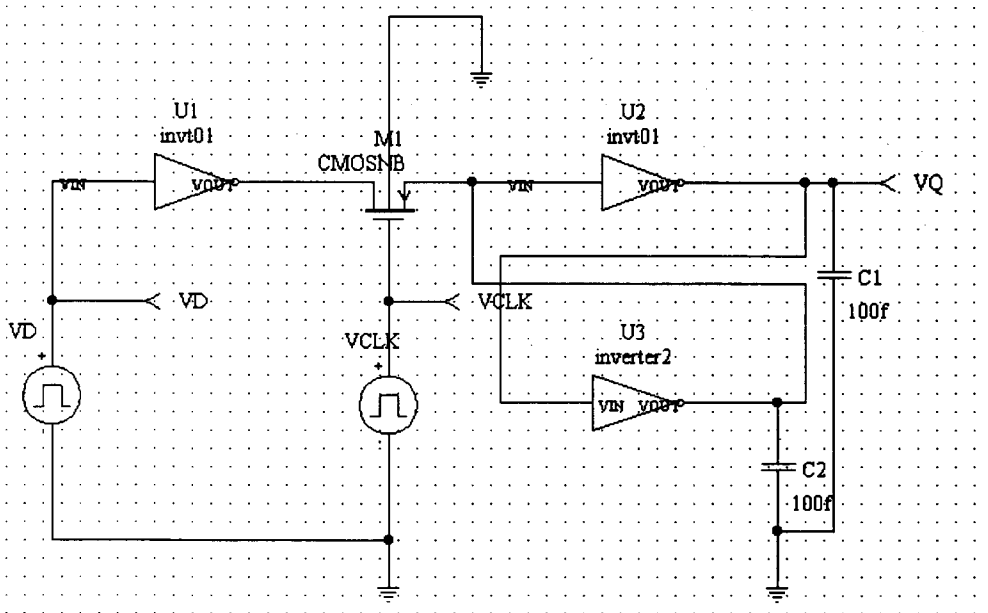

```
.subckt invt01.sub 4 1
```

```
M1 1 4 0 0 CMOSNB L=2u W=3u
```

```
M2 1 4 3 3 CMOSP B L=2u W=3u
```

```
VDD 3 0 DC 5 AC 0 0
```

```
.ends invt01.sub
```

```
.subckt invt02.sub 4 1
```

```
M1 1 4 0 0 CMOSNB L=15u W=3u
```

```
M2 1 4 3 3 CMOSP B L=15u W=3u
```

```
VDD 3 0 DC 5 AC 0 0
```

```
.ends invt02.sub
```

```
*** Top Level Netlist ***
```

```
C1 0 VQ 100f
```

```
C2 0 5 100f
```

```
M1 2 VCLK 5 0 CMOSNB L=2u W=3u
```

```
XU1 VD 2 invt01.sub
```

```
XU2 5 VQ invt01.sub
```

```
XU3 VQ 5 invt02.sub
```

```
VCLK VCLK 0 DC 0 AC 0 0 PULSE(0 5 50n 0.1n 0.1n 200n 400n)
```

```
VD VD 0 DC 0 AC 0 0 PULSE(0 5 10n 0.1n 0.1n 0.5u 1u)
```

```
***** Spice models and macro models *****
```


```
.MODEL CMOSNB NMOS LEVEL=4
```

```
.MODEL CMOSP B PMOS LEVEL=4
```

```
***** End of spice models and macro models *****
```

```
.OPTION ABSTOL=1m RELTOL=0.1 VNTOL=50mv
.tran 10n 4u 0 10n uic
.end
```

The SPICE simulation is shown below:

 

Problem 13.10

For minimum-size (0.9/0.6) MOSFETs using CMOS14TB process,

$$R_n = \frac{9\text{K}\Omega \cdot \mu\text{m}}{0.9\mu\text{m}} = 10\text{K}\Omega$$

$$t_{pHL} = t_{pLH} \approx R_n C_{\text{load}} = 10\text{K}\Omega \times 100\text{fF} = \underline{\underline{1\text{nS}}}$$

*** Top Level Netlist ***

```
C2      0 VOUT2 100f IC=0
C3      VOUT1 0 100f IC=5v
M2      2 VG VOUT2 0 CMOSNB5 L=0.6u W=0.9u OFF
M3      VOUT1 VG 0 0 CMOSNB5 L=0.6u W=0.9u
VDD     2 0    DC 5 AC 0 0
VG      VG 0   DC 0 AC 0 0 PULSE(0 5 5n 1p 1p 20n 40n)
```


***** Spice models and macro models *****

```
.MODEL CMOSNB5 NMOS LEVEL=4
+ vfb=-9.65360E-01    lvfb= 4.11254E-02    wvfb=-1.21737E-01
... ..
+ pbsw=0.99  mj=0.805  mjsw=0.761  wdf=0  dell=0
```

***** End of spice models and macro models *****

```
.OPTION ABSTOL=1m RELTOL=0.1 VNTOL=10mv
.tran 0.1n 20n 0 0.1n uic
.end
```

The SPICE simulation is shown below:

 

Problem 13.11

ANS: The netlist is shown as below:

*** (TurboSim V 1.87) Netlist for CATSE504P1311.CKT

*** Top Level Netlist ***

```
.ic      V(Vout)=0
C1      0 Vout 150f
M1      0 Vout 2 3 0 CMOSNB5 L=0.6u W=0.9u AD=3.24p AS=3.24p PD=7.2u PS=7.2u NRD=1 NRS=1
M2      3 0 Vout 2 CMOSPB5 L=0.6u W=0.9u AD=3.24p AS=3.24p PD=7.2u PS=7.2u NRD=1 NRS=1
VDD     2 0      DC 3.3 AC 0 0
Vin     3 0      DC 0 AC 0 0 PULSE(0 3.3 5ns 0.05ns 0.05ns 30ns 60ns)
```

$$R_n = \frac{9 \text{ k}\Omega \cdot \mu\text{m}}{0.9 \mu\text{m}} = 10 \text{ k}\Omega$$

$$R_p = \frac{18 \text{ k}\Omega \cdot \mu\text{m}}{0.9 \mu\text{m}} = 20 \text{ k}\Omega$$

$$t_{PLH} = t_{PHL} = (R_n + R_p) (150 \text{ fF})$$

$$= 1 \text{ ns}$$

***** Spice models and macro models *****

MODEL CMOSNB5 NMOS LEVEL=4

```
+vfb=-9.65360E-01  ivfb= 4.11254E-02  wvfb=-1.21737E-01
+phi= 9.02436E-01  lphi= 0.00000E+00  wphi= 0.00000E+00
+k1= 9.33678E-01  lk1=-8.15875E-02  wk1= 2.03526E-01
+k2= 7.39228E-02  lk2= 1.48295E-02  wk2= 5.89097E-02
+eta=-2.77969E-03  leta= 1.12296E-02  weta= 1.25263E-03
+muz= 4.71133E+02  dl= 1.57937E-001  dw= 4.09563E-001
+u0= 1.98427E-01  lu0= 1.54850E-01  wu0=-1.05429E-01
+u1= 3.39403E-02  lu1= 3.59469E-02  wu1=-5.00497E-03
+x2mz=-1.25728E+01  lx2mz=-1.24115E+01  wx2mz=-1.77657E+01
+x2c=-9.95217E-05  lx2c=-5.16949E-03  wx2c=-2.83253E-03
+x3c=-4.27269E-04  lx3c=-1.62632E-03  wx3c=-1.60797E-03
+x2u0=-9.02747E-04  lx2u0=-1.66946E-02  wx2u0=2.48458E-02
+x2u1=-7.29822E-04  lx2u1=-2.38803E-03  wx2u1=-9.76918E-04
+mus=-5.36631E+02  lmus=-2.18647E+01  wmus=-4.43373E+00
+x2ms=5.97403E+00  lx2ms=-7.67105E+00  wx2ms=-2.19614E+01
+x3ms=7.60054E+00  lx3ms=4.73779E+00  wx3ms=-2.59952E+00
+x3u1=1.75532E-02  lx3u1=-1.21628E-03  wx3u1=-5.95548E-04
+tox=9.60000E-003  temp=2.70000E+01  vdd=3.30000E+00
+cgdo=4.26077E-010  cgso=-4.26077E-010  cgbo=4.01709E-010
+xpert=1.00000E+000
+n0=1.00000E+000  ln0=0.00000E+000  wn0=0.00000E+000
+nb=0.00000E+000  lnb=0.00000E+000  wnb=0.00000E+000
+nd=0.00000E+000  lnd=0.00000E+000  wnd=0.00000E+000
+rsh=2  cj=6.02e-04  cjsw=2.0e-11  js=1e-08  pb=0.99
+pbsw=0.99  mj=0.805  mjsw=0.761  wdf=0  dell=0
```

MODEL CMOSPB5 PMOS LEVEL=4

```
+vfb=-2.80568E-01  ivfb=5.70163E-02  wvfb=-6.17493E-02
+phi=8.14689E-01  lphi=0.00000E+00  wphi=0.00000E+00
+k1=4.52973E-01  lk1=-9.19899E-02  wk1=1.20834E-01
+k2=-9.42157E-03  lk2=-2.25562E-03  wk2=3.13315E-02
+eta=-7.03956E-03  leta=1.92833E-02  weta=5.45445E-05
+muz=1.36047E+02  dl=1.85988E-001  dw=4.32366E-001
+u0=1.93813E-01  lu0=6.02231E-02  wu0=-4.90734E-02
+u1=8.52399E-03  lu1=-2.60545E-02  wu1=-6.34371E-03
+x2mz=-7.96258E+00  lx2mz=-2.15761E+00  wx2mz=-2.30663E+00
+x2c=-4.37912E-04  lx2c=-1.60046E-03  wx2c=-3.86750E-04
+x3c=-3.52725E-04  lx3c=-4.09096E-04  wx3c=-2.53471E-03
+x2u0=1.18873E-02  lx2u0=-4.81760E-03  wx2u0=8.80040E-03
+x2u1=2.26591E-03  lx2u1=7.96828E-04  wx2u1=-4.70527E-04
+mus=1.44421E+02  lmus=1.63665E+01  wmus=-7.31189E-01
+x2ms=8.18970E+00  lx2ms=-1.25158E+00  wx2ms=-3.62233E+00
+x3ms=7.29640E-01  lx3ms=1.15206E+00  wx3ms=-1.02833E+00
+x3u1=-3.51521E-03  lx3u1=-3.12374E-03  wx3u1=3.48134E-03
+tox=9.60000E-003  temp=2.70000E+01  vdd=3.30000E+00
+cgdo=5.01753E-010  cgso=-5.01753E-010  cgbo=4.14187E-010
+xpert=1.00000E+000
+n0=1.00000E+000  ln0=0.00000E+000  wn0=0.00000E+000
+nb=0.00000E+000  lnb=0.00000E+000  wnb=0.00000E+000
+nd=0.00000E+000  lnd=0.00000E+000  wnd=0.00000E+000
+rsh=2.1  cj=9.34e-04  cjsw=2.41e-10  js=1e-08  pb=0.90
+pbsw=0.90  mj=0.491  mjsw=0.222  wdf=0  dell=0
```


***** End of spice models and macro models *****

.OPTION ABSTOL=10u VNTOL=1mv

.tran 0.05ns 50ns 0 0.05ns uic


.end

The plot indicates that the t_{PLH} is about 1ns and the t_{PHL} is about 0.8ns.

 

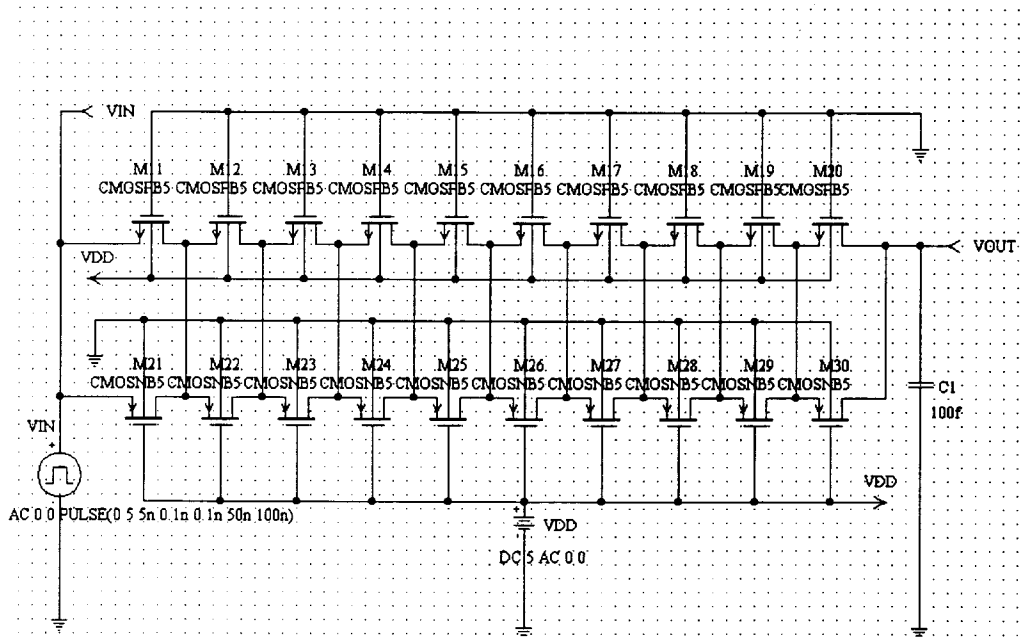Problem 13.12

$$\begin{aligned}
 t_{pHL} = t_{pLH} &= N \times (R_n // R_p) \times (C_{load}) + 0.35 (R_n // R_p) (C_{inn} + C_{inp}) N^2 \\
 &= 10 \times (10k // 20k) \times 100 \text{ fF} + 0.35 \times (10k // 20k) \times \frac{3}{2} \times 3.7 \frac{\text{fF}}{\mu\text{m}^2} \times (0.6 \times 0.9) \times 2 \mu\text{m}^2 \times 10^2 \\
 &\approx \underline{\underline{8.07 \text{ nS}}}
 \end{aligned}$$



*** Top Level Netlist ***

```

C1      0 VOUT 100f IC=0
M11    1 0 VIN VDD CMOSPB5 L=0.6u W=0.9u
M12    4 0 1 VDD CMOSPB5 L=0.6u W=0.9u
M13    5 0 4 VDD CMOSPB5 L=0.6u W=0.9u
M14    6 0 5 VDD CMOSPB5 L=0.6u W=0.9u
M15    7 0 6 VDD CMOSPB5 L=0.6u W=0.9u
M16    8 0 7 VDD CMOSPB5 L=0.6u W=0.9u
M17    9 0 8 VDD CMOSPB5 L=0.6u W=0.9u
M18    10 0 9 VDD CMOSPB5 L=0.6u W=0.9u
M19    11 0 10 VDD CMOSPB5 L=0.6u W=0.9u
M20    VOUT 0 11 VDD CMOSPB5 L=0.6u W=0.9u
M21    1 VDD VIN 0 CMOSNB5 L=0.6u W=0.9u
M22    4 VDD 1 0 CMOSNB5 L=0.6u W=0.9u
    
```

```

M23 5 VDD 4 0 CMOSNB5 L=0.6u W=0.9u
M24 6 VDD 5 0 CMOSNB5 L=0.6u W=0.9u
M25 7 VDD 6 0 CMOSNB5 L=0.6u W=0.9u
M26 8 VDD 7 0 CMOSNB5 L=0.6u W=0.9u
M27 9 VDD 8 0 CMOSNB5 L=0.6u W=0.9u
M28 10 VDD 9 0 CMOSNB5 L=0.6u W=0.9u
M29 11 VDD 10 0 CMOSNB5 L=0.6u W=0.9u
M30 VOUT VDD 11 0 CMOSNB5 L=0.6u W=0.9u
VDD VDD 0 DC 5 AC 0 0
VIN VIN 0 DC 0 AC 0 0 PULSE(0 5 5n 0.1n 0.1n 50n 100n)

```

***** Spice models and macro models *****

.MODEL CMOSPB5 PMOS LEVEL=4

.MODEL CMOSNB5 NMOS LEVEL=4


***** End of spice models and macro models *****

```

.OPTION ABSTOL=1m RELTOL=0.1 VNTOL=50mv
.tran 1n 100n 0 1n uic
.end

```


The SPICE simulation is shown below:

 


Simulation results
 $t_{PLH} \approx 5.2 \text{ nS}$
 $t_{PHL} \approx 4.0 \text{ nS}$

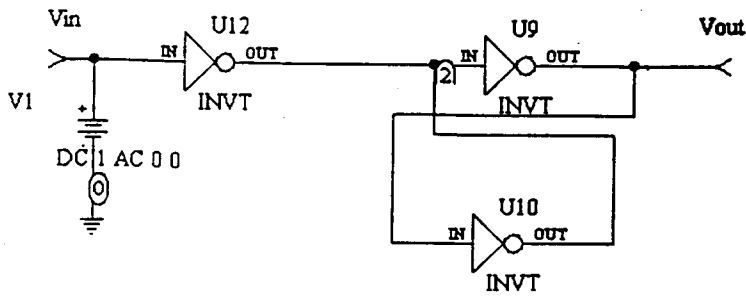Problem 13.13.

Since voltage source used in SPICE can provide infinite current, we use an inverter to simulate the more practical condition. ■



1) Vin from 0 to 5v

 

The switching point is moved to about 3.2v and has bad noise performance.

2) Vin from 5 to 0

In this case, for all minimum size inverters, this circuit doesn't work. The reason is the inverter U10 will sink a lot of current (through the nmos transistor) and pull down the node 2 before inverter U9 far below the switching point of U9, and U9 can never change state. From the simulation results, the output stays in 5V (High) and node voltage V2 is just around threshold voltage. Use long L device of U10 will make this circuit work.

