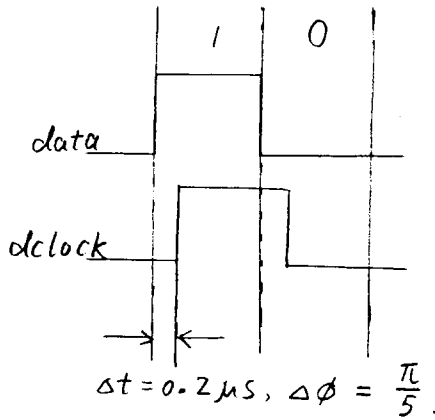


# Chapter 19


## Problem 19.1



$$\Delta \phi = \frac{0.2 \mu s}{1 \mu s} \times \pi = \frac{1}{5} \pi$$

$$V_{P\text{Dout}} = V_{DD} \times \frac{\Delta \phi}{\pi} = \frac{V_{DD}}{5} = 1V.$$

## Problem 19.2

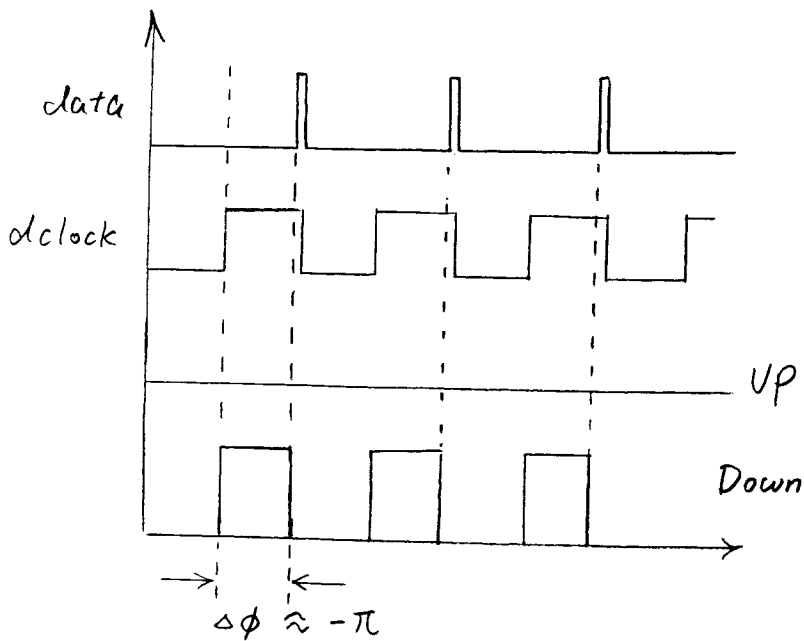

## Problem 19.3

Using 5 stages. Assuming the MOSFETs of inverters, M2 & M3, are sized for equal drive;  $L_n = L_p = 2 \mu m$ ,  $W_n = 3 \mu m$ ,  $W_p = 9 \mu m$ , we get:


$$C_{TOT} = 48 fF$$

$$f_{osc} = \frac{I_D}{N \cdot C_{TOT} \cdot V_{DD}} \Rightarrow I_D = f_{osc} \cdot N \cdot C_{TOT} \cdot V_{DD} = 10 \text{ MHz} \cdot 5 \cdot 48 fF \cdot 5V$$

$$= 12 \mu A$$

$$I_D = \frac{\beta_5}{2} (V_{GS} - V_{THN})^2 \Rightarrow \left(\frac{W}{L}\right)_5 = 0.172. \text{ Choose } \underline{\underline{\frac{W_5}{L_5} = \frac{3 \mu m}{18 \mu m}}}$$

Problem 19.3 (cont.)

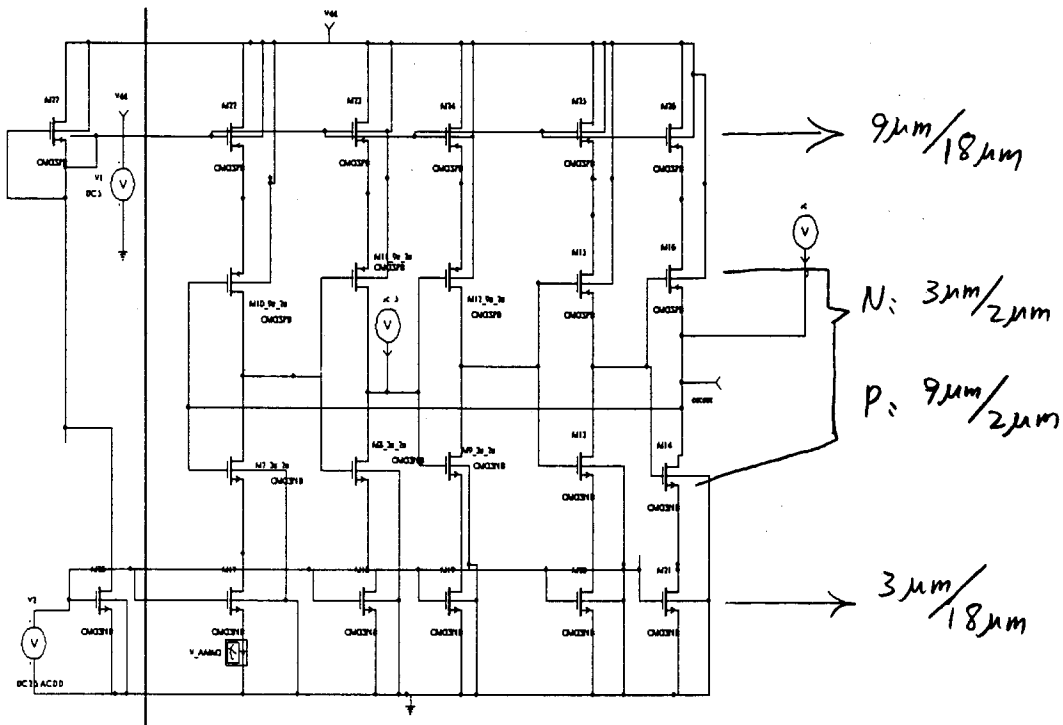

\*\*\* Top Level Netlist \*\*\*

```
.ic      V(2)=5
.ic      V(oscout)=0
M10_9u_2u      1 oscout 6 Vdd CMOSPB L=2u W=9u
M11_9u_2u      2 1 9 Vdd CMOSPB L=2u W=9u
M12_9u_2u      5 2 10 Vdd CMOSPB L=2u W=9u
M13      4 5 17 0 CMOSNB L=2u W=3u
M14      oscout 4 12 0 CMOSNB L=2u W=3u
M15      11 5 4 Vdd CMOSPB L=2u W=9u
M16      8 4 oscout Vdd CMOSPB L=2u W=9u
M17      14 20 19 0 CMOSNB L=18u W=3u
M18      13 20 0 0 CMOSNB L=18u W=3u
M19      16 20 0 0 CMOSNB L=18u W=3u
M20      17 20 0 0 CMOSNB L=18u W=3u
M21      12 20 0 0 CMOSNB L=18u W=3u
M22      Vdd 15 6 Vdd CMOSPB L=18u W=9u
M23      Vdd 15 9 Vdd CMOSPB L=18u W=9u
M24      Vdd 15 10 Vdd CMOSPB L=18u W=9u
M25      Vdd 15 11 Vdd CMOSPB L=18u W=9u
M26      Vdd 15 8 Vdd CMOSPB L=18u W=9u
M27      Vdd 15 15 Vdd CMOSPB L=18u W=9u
M28      15 20 0 0 CMOSNB L=18u W=3u
M7_3u_2u      1 oscout 14 0 CMOSNB L=2u W=3u
M8_3u_2u      2 1 13 0 CMOSNB L=2u W=3u
M9_3u_2u      5 2 16 0 CMOSNB L=2u W=3u
V_AMM3      19 0 0V
V1          Vdd 0 DC 5
V2          20 0 DC 2.5 AC 0 0
```

\*\*\*\*\* Spice models and macro models \*\*\*\*\*

.MODEL CMOSNB NMOS LEVEL=4

.MODEL CMOSPB PMOS LEVEL=4

\*\*\*\*\* End of spice models and macro models \*\*\*\*\*

.OPTION ABSTOL=10u ITL4=1000 RELTOL=0.1 VNTOL=10mv

.probe


.tran 1n 1000n 0n 1n uic

.plot tran all


.print tran all

.end

The SPICE simulation is shown below:

 

### Problem 19.4

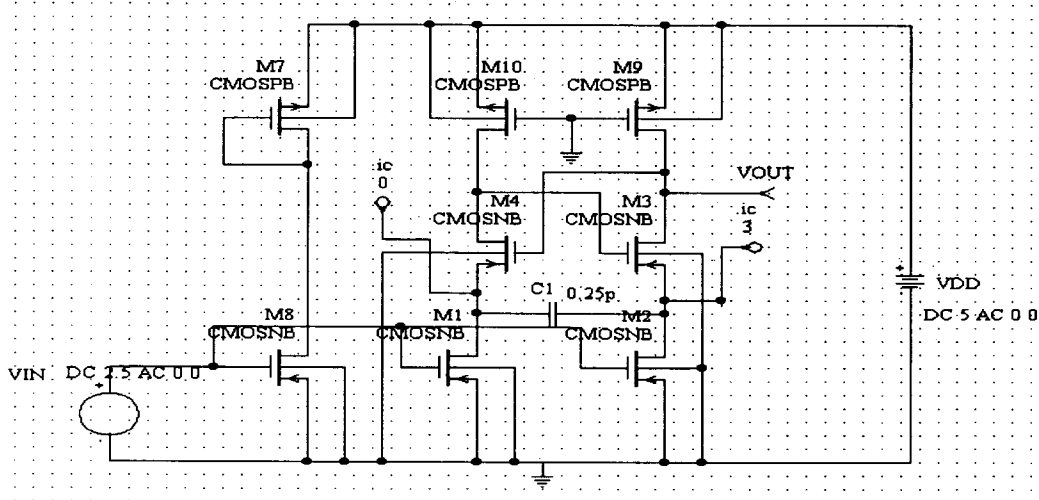

\*\*\* Top Level Netlist \*\*\*


```
.ic      V(3)=3
.ic      V(1)=0
C1       1 3 0.25p
M1       1 8 0 0 CMOSNB L=21u W=3u
M10      6 0 7 7 CMOSP B L=10u W=3u
M2       3 8 0 0 CMOSNB L=21u W=3u
M3       VOUT 6 3 0 CMOSNB L=2u W=30u OFF
M4       6 VOUT 1 0 CMOSNB L=2u W=30u
M7       5 5 7 7 CMOSP B L=21u W=9u
M8       5 8 0 0 CMOSNB L=21u W=3u
M9       VOUT 0 7 7 CMOSP B L=10u W=3u
VDD      7 0      DC 5 AC 0 0
VIN      8 0      DC 2.5 AC 0 0
```

\*\*\*\*\* Spice models and macro models \*\*\*\*\*


```
.MODEL CMOSNB NMOS LEVEL=4
.MODEL CMOSP B PMOS LEVEL=4
```

\*\*\*\*\* End of spice models and macro models \*\*\*\*\*
 
```
.OPTION ABSTOL=1u RELTOL=0.01 VNTOL=5mv
.tran 1n 1000n 0 1n uic
.end
```



### Problem 19.5

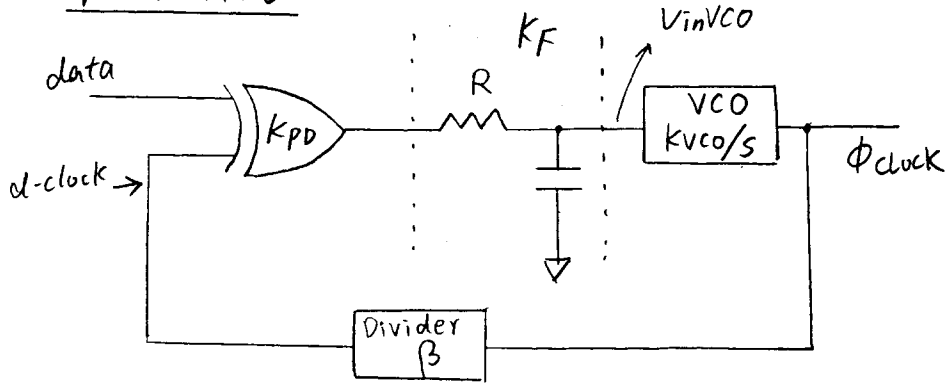


$$H(s) = \frac{A(s)}{1 + A(s)F(s)}$$

$$A(s) = K_{pd} \times K_F \times K_{vco}/s, \quad F(s) = \beta$$

$$\therefore H(s) = \frac{K_{pd} \times K_F \times K_{vco}/s}{1 + K_{pd} \times K_F \times K_{vco} \times \beta/s} = \frac{K_{pd} K_F K_{vco}}{s + \beta K_{pd} K_F K_{vco}}$$
 
### Problem 19.6


One of the implementation of divide by 2 is shown below :




(positive edge-triggered D FF)

### Problem 19.7

When input data rate is 9.04 Mbits/s, the clock is aligned slightly off center of the data, and  $\Delta\phi = 0.62\pi$ .

 


Problem 19.8

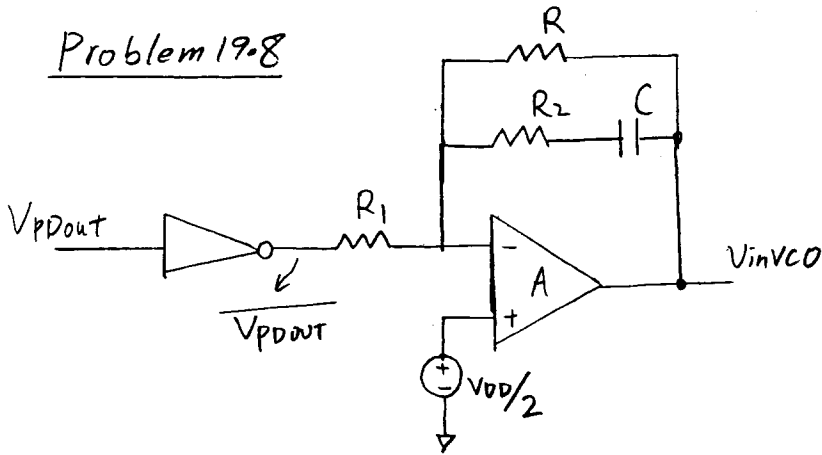

Assume  $R \gg R_1$  &  $R_2$ , and ideal op-amp A is used,

$$K_F = \frac{V_{inVCO}}{V_{pDOUT}} = \frac{-V_{inVCO}}{V_{pDOUT}} = \frac{R_2 + \frac{1}{sC}}{R_1} = \frac{1 + sR_2C}{sR_1C}$$

Problem 19.9

 

Assume VCO oscillates from 6KHz to DC for input voltages ( $V_{inVCO}$ ) from 0 to 5V.

$$K_{VCO} = 2\pi \times \frac{6000 - 0 \text{ (Hz)}}{5 \text{ V}} = 7536 \text{ rad/V}\cdot\text{s}$$


The lock range,  $\Delta f_L$ , is set to 200Hz (800 ~ 1200 Hz).

$$\text{Assume } \xi = 0.7, \quad \omega_n = \frac{2\pi \times 200}{4\pi \times 0.7} = 143 \text{ rad/s}$$

$$\left\{ \begin{array}{l} \omega_n = \sqrt{\frac{K_{pDPLL} K_{VCO}}{N(R_1 + R_2)C}} \\ \xi = \frac{\omega_n R_2 C}{2} \end{array} \right.$$

Insert the data, we get  $R_2 C \approx 9.7 \text{ mS}$ ,  $R_1 C \approx 39.2 \text{ mS}$

### Problem 19.10

 

For unity feedback op-amps  $A_1$  and  $A_2$ , we have


$$V_A = V_{+peak}, \quad V_B = V_{-peak}$$

Since  $I_1 = I_2 = I$ , we have

$$\frac{V_A - V_X}{R} = \frac{V_X - V_B}{R} \quad \Rightarrow \quad V_X = \frac{V_A + V_B}{2} = \frac{V_{+peak} + V_{-peak}}{2}$$

 
### Problem 19.11

Mono-stable (one-shot) circuit can be used for implementing return to zero data format, as shown below:




The pulse width of the mono-stable circuit is adjusted to be half of the data width.

### Problem 19.12

 

 The key point in the design of edge detector is designing of the delay element. Assume we use inverter chain for delay element and we use the equal-drive size, that is,  $3\mu\text{m}/2\mu\text{m}$  for N-channel, and  $9\mu\text{m}/2\mu\text{m}$  for p-channel.



The total propagation delay  $t_{TOT} = N \times [R_n (C_{out} + C_{IN})]$


$$t_{TOT} = N \times \left[ 8k \times \frac{5}{2} \times C_{ox}' \times (3 \times 2\mu\text{m}^2 + 9 \times 2\mu\text{m}^2) \right] = 5 \text{ ns}$$

$$\Rightarrow N \approx 13.02$$


In order to keep the non-inverting function of the delay element, we choose  $N = 12$ . The resulting output width is approximately 4.6 ns.

### Problem 19.13


The optimum delay for using in an edge detector should be close to one-half of the bit-interval time.

 


Problem 19.14

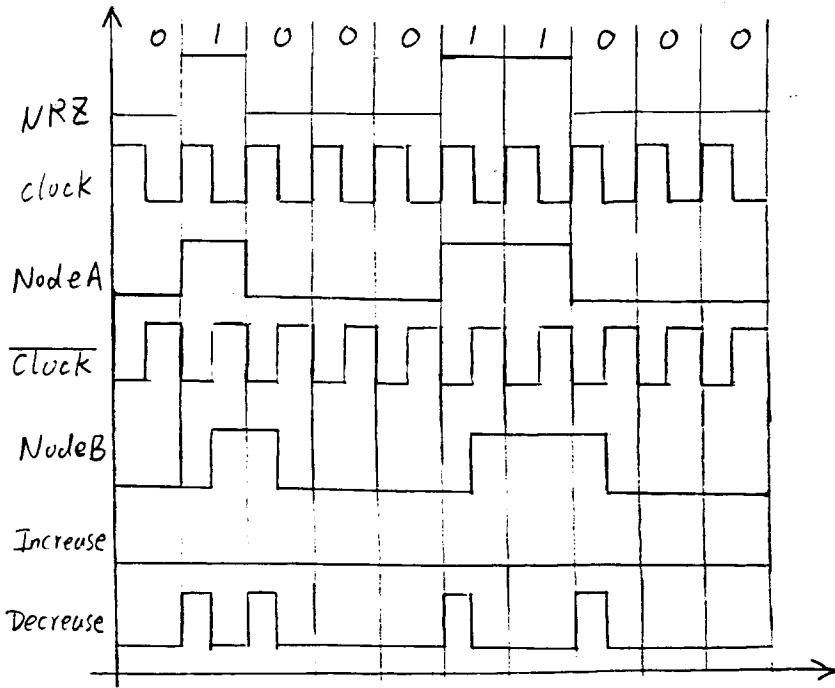

Problem 19.15

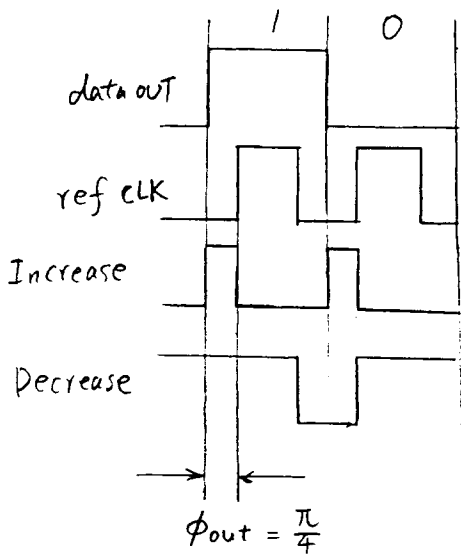

**Problem 19.16**

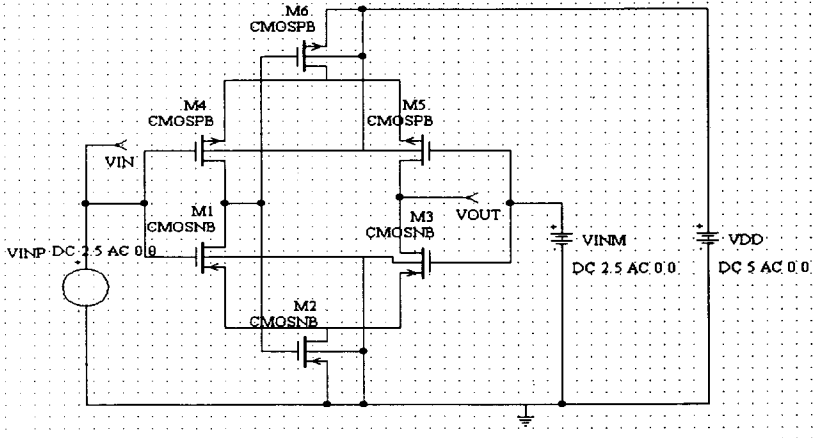

\*\*\* Top Level Netlist \*\*\*

```

M1 1 VIN 3 0 CMOSNB L=2u W=10u
M2 3 1 0 0 CMOSNB L=2u W=10u
M3 VOUT 10 3 0 CMOSNB L=2u W=10u
M4 1 VIN 15 16 CMOSP B L=2u W=30u
M5 VOUT 10 15 16 CMOSP B L=2u W=30u
M6 15 1 16 16 CMOSP B L=2u W=30u
VDD 16 0 DC 5 AC 0 0
VINM 10 0 DC 2.5 AC 0 0
VINP VIN 0 DC 2.5 AC 0 0
    
```

\*\*\*\*\* Spice models and macro models \*\*\*\*\*

```

.MODEL CMOSNB NMOS LEVEL=4
.MODEL CMOSP B PMOS LEVEL=4
    
```

\*\*\*\*\* End of spice models and macro models \*\*\*\*\*

```

.OPTION ABSTOL=1u RELTOL=0.01 VNTOL=5mv
.DC VINP 0 5 0.1
.end
    
```

