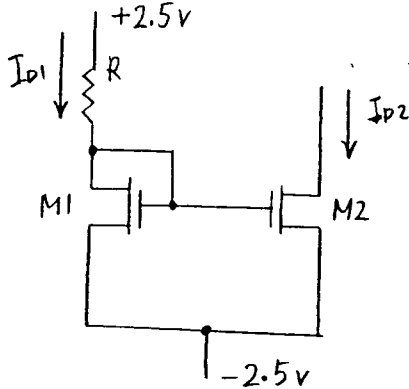


Chapter 20

Problem 20.1




$$R = \frac{2.5 - V_{GS} - (-2.5)}{I_{D1}} = \frac{2.5 - 1 - (-2.5)}{1 \mu A} = 4 \text{ M}\Omega$$

$$I_{D1} = I_{D2} = \frac{k_p}{2} \frac{W}{L} (V_{GS} - V_{THN})^2$$

$$\Rightarrow 1 \mu A = \frac{50 \mu A/V^2}{2} \times \frac{W}{L} \times (1V - 0.83V)^2$$

$$\Rightarrow \frac{W}{L} \approx 1.38 \Rightarrow W_1 = W_2 = 7 \mu m, L_1 = L_2 = 5 \mu m$$

Problem 20.2

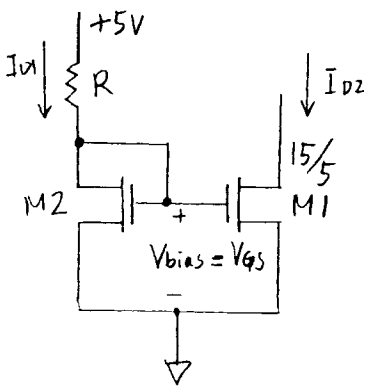

$$I_{D2} = 5 \mu A = \frac{50 \mu A/V^2}{2} \times \frac{15}{5} \times (V_{GS2} - V_{THN})^2$$

$$\Rightarrow V_{GS2} = V_{GS1} = V_{bias} \approx 1.09 \text{ (V)}$$

We choose the size of M2 to be the same of that of M1,
 $W_2 = 15 \mu m, L_2 = 5 \mu m$

$$I_{D1} = I_{D2} = 5 \mu A = \frac{5 - 1.09}{R} \Rightarrow R = \underline{\underline{782 \text{ K}}}$$

Problem 20.3

ANS: Let the drain current through M1 is I_{D1} , obviously,

$$V_{SG1} + I_{D1} \cdot 380k = 5V$$

and $I_{D1} = (K_{pp}/2) \cdot (W/L) \cdot (V_{SG1} - V_{thp})^2$ where $V_{thp} = 0.916V$

Solving the two equations, $\Rightarrow V_{SG1} = 1.516V, I_{D1} = 9.169\mu A$

Since $V_{SG3} = V_{DD} - I_{D2} \cdot 380k = V_{DD} - I_{D1} \cdot 380 = V_{SG1}, \Rightarrow I_{D3} = 3 \cdot I_{D1} = 27.507\mu A$

Problem 20.4

If the size of M2 increased to 30/5, $I_{D2} = I_{D3} = 20\mu A$.

V_{GS2} does not change, but V_{GS3} changes to about 1.32V.

Problem 20.5

ANS: The small signal output resistor of the right NMOS in figure P20.5 r_o is:

$$r_o = 1/(\lambda I_D) = 1/(0.06 \cdot 5\mu A) = 10/3 \text{ megohms}$$

$$it = v_t/r_o = 0.3 v_t (\mu A) \text{ for } v_t \text{'s unit is volt}$$

Problem 20.6

ANS: The schematic is shown below,

$$V_{GS1,3} = V_{thn} + \text{SQRT}(2 \cdot I_D / \beta_n) = 0.83 + \text{SQRT}[2 \cdot 1\mu A / (50 \cdot 15/5)] = 0.95 V$$

Ignoring the body effect of M2 and M4, we have

$$V_{GS2,4} = 0.95 V$$


$$\Rightarrow R = (V_{DD} - V_{GS4} - V_{GS3}) / I_D = (5 - 0.95 - 0.95) / 1\mu = 3.1 \text{ megohms}$$

The small-signal resistance of M1 is $r_o = 1/(\lambda I_D) = 1/(0.06 \cdot 1\mu A) = 16.67 \text{ meg}$

The small-signal resistance of M2 is about $= g_{m1} \cdot r_o^2 = \text{SQRT}(2 \cdot \beta_1 \cdot I_{D1}) \cdot r_o^2 = 17.32\mu A/V \cdot (16.67)^2 = 4.81 \text{ Gohms}$.


$$\Delta V = V_{GS} - V_{thn} = 0.95 - 0.83 = 0.12V$$

The minimum voltage across M1 and M2 $= 2\Delta V + V_{thn} = 2 \cdot 0.12 + 0.83 = 1.07 V$.

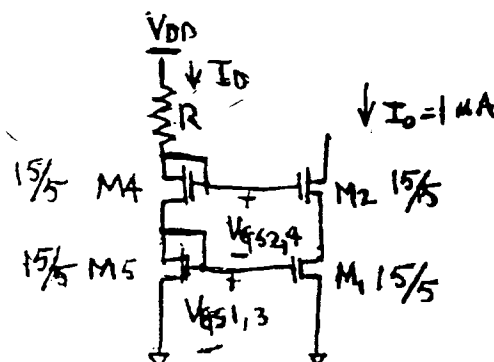


Problem 20.7

ANS. (a) add Test voltage V_t

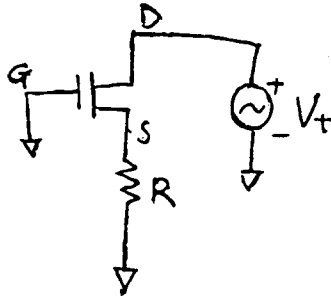

Small signal Model \Rightarrow

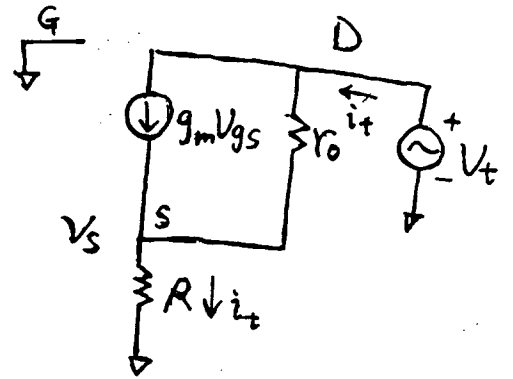

$$(b) \quad i_t = g_m v_{gs} + \frac{V_t - V_s}{r_o} \quad (1)$$

$$v_{gs} = 0 - V_s = -V_s = -(i_t R) = -i_t R \quad (2)$$

Plugging $v_{gs} = -i_t R$ and $V_s = i_t R$ into (1)

$$\Rightarrow i_t = g_m (-i_t R) + \frac{V_t - i_t R}{r_o}$$

$$\Rightarrow i_t r_o + i_t R + i_t g_m R r_o = V_t$$

$$\text{and } R_o = \frac{V_t}{i_t} = \frac{i_t (r_o + R + g_m R r_o)}{i_t} = r_o + g_m R r_o + R$$


$$\Rightarrow R_o = r_o (1 + g_m R) + R$$

Problem 20.9

$$\text{ANS: } S_{V_{SS}}^{I_o} = \frac{V_{SS}}{I_o} \frac{\partial I_o}{\partial V_{SS}} = \frac{V_{SS}}{I_o} \left(-\frac{1}{R}\right) = \frac{-2.5V}{10\mu A} \left(-\frac{1}{380k}\right) = 0.658$$

$$\frac{\Delta I_o}{I_o} = S_{V_{SS}}^{I_o} \frac{-\Delta V_{SS}}{V_{SS}} = 0.658 \frac{-2.6 - (-2.4)}{-2.5} = 5.3\%$$

20.8.

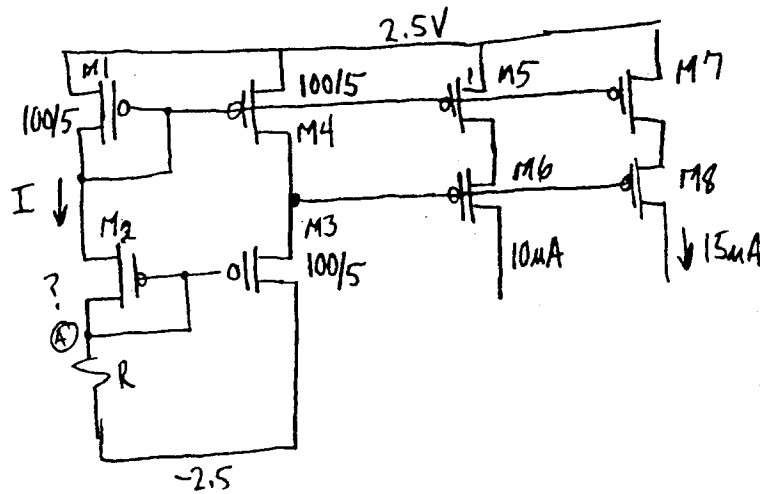

Design this circuit.

This is the PMOS version of Figure 20.6.

In this case, $V_{SG} = \Delta V + |V_{THP1}| \Rightarrow \Delta V = 1.2 - 0.91 = 0.29$

\therefore The voltage at (A) is,

$$V_{\text{A}} = 2.5 - (3\Delta V + 2|V_{THP1}|) \quad \text{The size of } M_3 = \frac{1}{4} M_1$$

$$= 2.5 - (0.87 + 1.8) = \underline{\underline{-0.17 \text{ V.}}}$$

$$I = \frac{17 \mu\text{A}/\text{V}^2}{2} \left(\frac{100}{5}\right) (1.2 - 0.91)^2 = \underline{\underline{14.3 \mu\text{A}}}$$

$$\therefore R = \frac{-0.17 + 2.5}{14.3 \mu\text{A}} = \underline{\underline{163 \text{ k}\Omega}}$$

$$M_3 = \frac{1}{4} M_1 = \frac{25}{5}$$

$$M_5: \quad \frac{100/5}{(W/L)_5} = \frac{14.3 \mu\text{A}}{10 \mu\text{A}} \Rightarrow W_5 = \underline{\underline{70 \mu\text{m}}} = W_6$$

$$M_7: \quad \frac{100/5}{(W/L)_7} = \frac{14.3 \mu\text{A}}{15 \mu\text{A}} \Rightarrow W_7 = \underline{\underline{105 \mu\text{m}}} = W_8$$

Estimate minimum voltages:

$$V_{W6} = 2.5 - (2\Delta V + |V_{THP1}|) = 1.01 \text{ V} \quad \therefore V_{D6(\text{max})} = 1.01 + 0.91 = 1.92 \text{ V}$$

$$\therefore \text{Minimum voltage across both sources is } 2.5 - 1.92 = \underline{\underline{0.58 \text{ V.}}}$$

20.8 (cont)

$$R_{out6} = g_{m6} r_o^2 = \sqrt{2(17\mu A/V^2)(70/5)(10\mu A)(1.67M)^2} = 192.4 M\Omega$$

$$R_{out8} \approx g_{m8} r_o^2 = \sqrt{2(17\mu A/V^2)(105/5)(15\mu A)(1.1M)^2} = 125 M\Omega$$

SPICE Analysis: see plots following.

$$R_{out6}(HSPICE) = 770 M\Omega \quad R_{out8}(HSPICE) = 502 M\Omega$$

*problem 20.8 NOTE: Bulk effects are ignored!

```
m1 g1 g1 vdd vdd cmospb w=100u l=5u
m2 g2 g2 g1 g1 cmospb w=25u l=5u
m3 vss g2 g6 g6 cmospb w=100u l=5u
m4 g6 g1 vdd vdd cmospb w=100u l=5u
m5 d5 g1 vdd vdd cmospb w=70u l=5u
m6 out1 g6 d5 d5 cmospb w=70u l=5u
m7 d7 g1 vdd vdd cmospb w=105u l=5u
m8 out2 g6 d7 d7 cmospb w=105u l=5u
```

```
r1 g2 vss 163k
```

```
vdd vdd 0 dc 2.5
vss vss 0 dc -2.5
vout1 out1 0 dc 0
vout2 out2 0 dc 0
```

```
.lib ../spice.models cmosnb
.lib ../spice.models cmospb
```

```
.op
.end
```

***** operating point information tnom= 25.000 temp= 25.000


node	=voltage	node	=voltage	node	=voltage
+0:d5	= 2.1756	0:d7	= 2.1755	0:g1	= 1.3037
+0:g2	=-201.3197m	0:g6	= 987.8969m	0:out1	= 0.
+0:out2	= 0.	0:vdd	= 2.5000	0:vss	= -2.5000

**** mosfets

```
subckt
element 0:m1 0:m2 0:m3 0:m4 0:m5 0:m6
model 0:cmospb 0:cmospb 0:cmospb 0:cmospb 0:cmospb 0:cmospb
id -14.1023u -14.1023u -14.2386u -14.2386u -9.5349u -9.5349u
vgs -1.1963 -1.5051 -1.1892 -1.1963 -1.1963 -1.1877
vds -1.1963 -1.5051 -3.4879 -1.5121 -324.4447m -2.1756
```

```
subckt
element 0:m7 0:m8
model 0:cmospb 0:cmospb
id -14.3796u -14.3796u
vgs -1.1963 -1.1876
vds -324.5369m -2.1755
```

P20-8 Minimum Voltage Across Sources

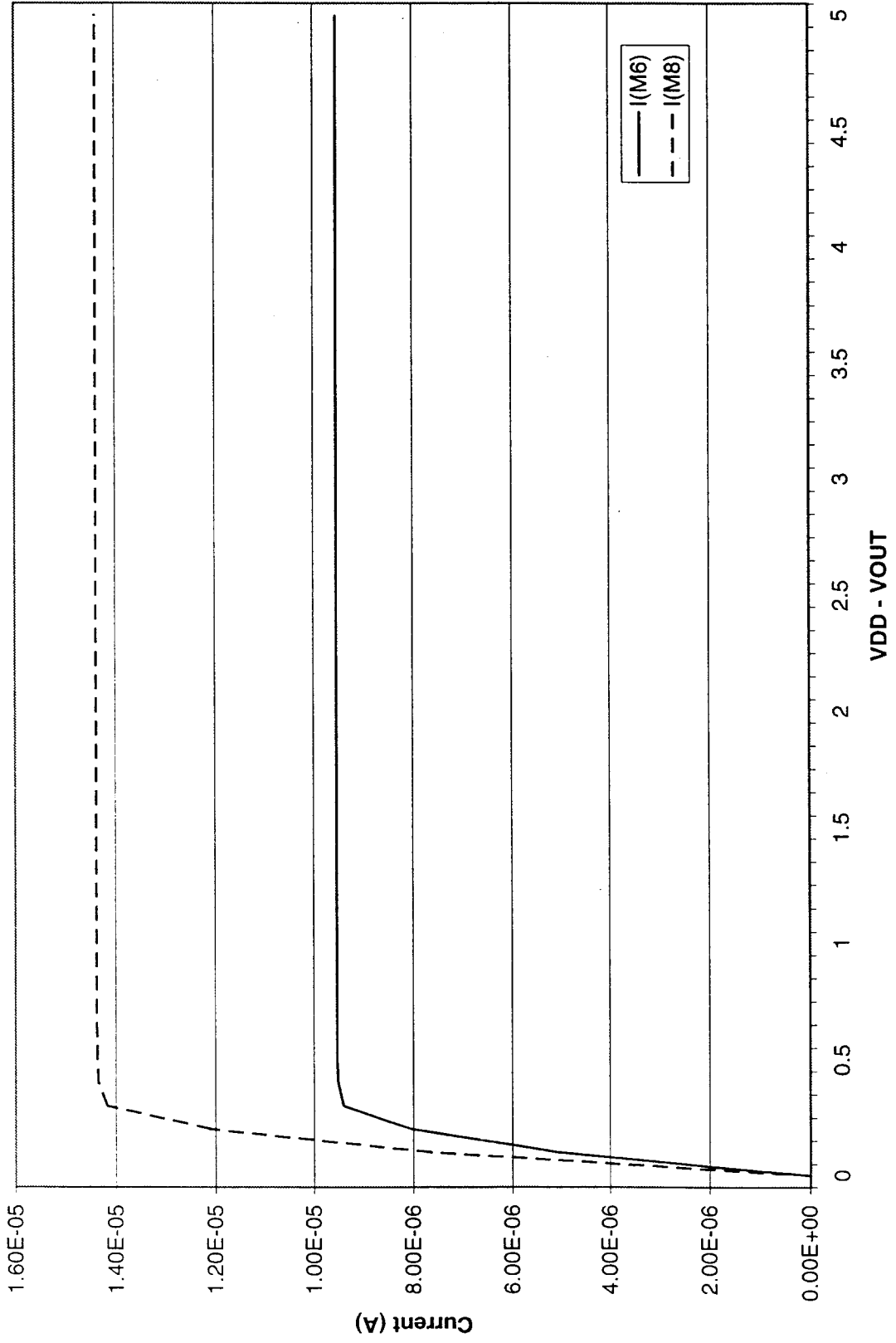

Problem 20.9 (Simulation)

The PSICE netlist is shown below

```
*** Top Level Netlist ***
M1      1 1 2 2 CMOSNB L=5u W=15u
M2      3 1 2 2 CMOSNB L=5u W=15u
R       1 6 380K TC1=0.002
V_AMM1  4 6 0V
VDD     4 0      DC 2.5 AC 0 0
VOUT    3 0 DC -1.3 AC 0 0
VSS     2 0      DC -2.5V AC 0 0

***** Spice models and macro models *****

.MODEL CMOSNB NMOS LEVEL=4
**BSIM MODEL PARAMETERS **

***** End of spice models and macro models *****

.DC VSS -2.4V -2.6V -0.01V
.SENS I(VOUT)
.PROBE
.end
```

The output sensitivity results are

DC SENSITIVITIES OF OUTPUT I(VOUT)

ELEMENT NAME	ELEMENT VALUE	ELEMENT SENSITIVITY (AMPS/UNIT)	NORMALIZED SENSITIVITY (AMPS/PERCENT)
R	3.800E+05	2.420E-11	9.197E-08
V_AMM1	0.000E+00	2.443E-06	0.000E+00
VDD	2.500E+00	-2.443E-06	-6.108E-08
VOUT	-1.300E+00	-8.494E-07	1.104E-08
VSS	-2.500E+00	3.293E-06	-8.231E-08

Problem 20.10

$$TC(I_0) = \frac{1}{I_0} \cdot \frac{\partial I_0}{\partial T} \quad (1)$$

$$I_0 = \frac{W_2 L_1}{W_1 L_2} \cdot \frac{V_{DD} - V_{GS} - V_{SS}}{R} \quad (2)$$

Plugging (2) to (1), we get

$$\begin{aligned} TC(I_0) &= \frac{1}{I_0} \times \frac{W_2 L_1}{W_1 L_2} \times \frac{-\frac{\partial V_{GS}}{\partial T} \cdot R - (V_{DD} - V_{GS} - V_{SS}) \frac{\partial R}{\partial T}}{R^2} \\ &= -\frac{1}{I_0} \left[\frac{W_2 L_1}{W_1 L_2} \times \frac{1}{R} \cdot \frac{\partial V_{GS}}{\partial T} + \frac{I_0}{R} \frac{\partial R}{\partial T} \right] \end{aligned}$$

Problem 20.11


The temperature dependence of the transconductance parameter $KP(T)$ was expressed as below from Chp.9.

$$KP(T) = KP(T_0) \cdot (T/T_0)^{-1.5}$$

$$\frac{\partial KP(T)}{\partial T} = KP(T_0) \cdot (-1.5) \cdot \left(\frac{T}{T_0}\right)^{-2.5} \cdot \frac{1}{T_0}$$

$$\frac{1}{KP(T)} \frac{\partial KP(T)}{\partial T} = \frac{1}{KP(T_0) \cdot (T/T_0)^{-1.5}} \cdot KP(T_0) \cdot (-1.5) \cdot \left(\frac{T}{T_0}\right)^{-2.5} \cdot \frac{1}{T_0} = \frac{-1.5}{T}$$

Problem 20.12

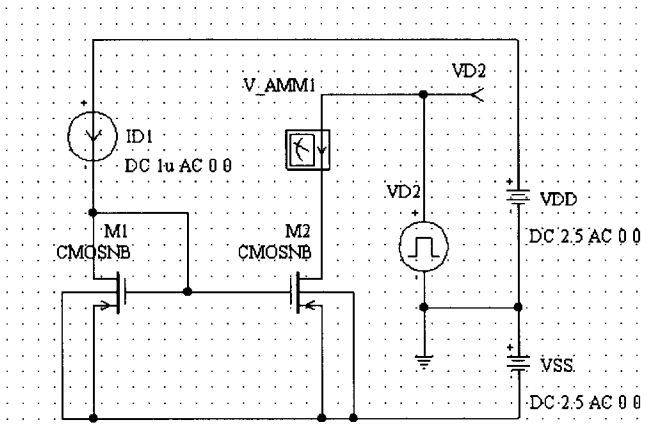

*** Top Level Netlist ***

```

ID1  5 1  DC 1u AC 0 0
M1   1 1 2 2 CMOSNB L=5u W=5u
M2   3 1 2 2 CMOSNB L=5u W=100u
V_AMM1  VD2 3 0V
VD2  VD2 0 DC 0 AC 0 0 PULSE(0 1 5n 0.1n 0.1n 20n 40n)
VDD  5 0  DC 2.5 AC 0 0
VSS  0 2  DC 2.5 AC 0 0
    
```

***** Spice models and macro models *****


.MODEL CMOSNB NMOS LEVEL=4

***** End of spice models and macro models *****


```

.OPTION ABSTOL=1u RELTOL=0.01 VNTOL=5mv
.tran 0.1n 50n 0 0.1n
.end
    
```

The SPICE simulation is shown below:

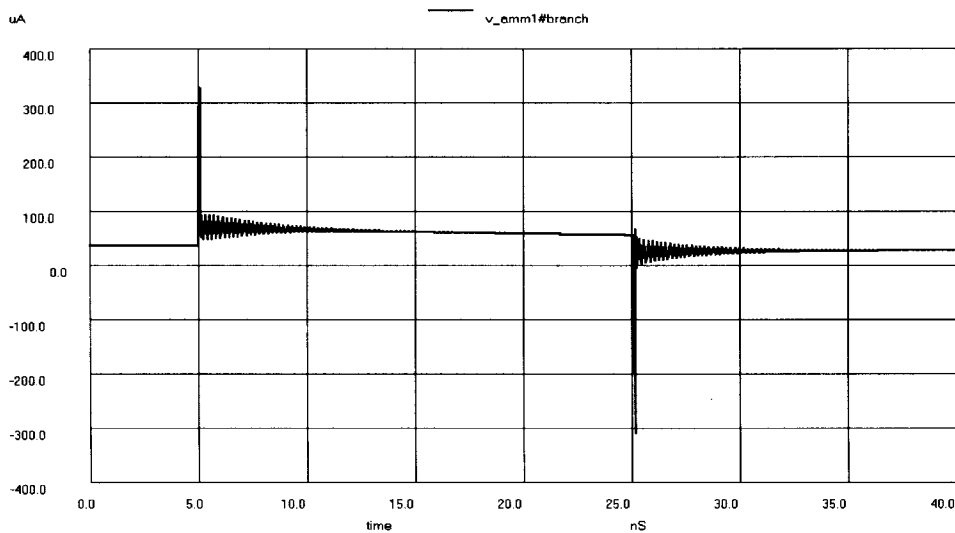

Prb 20.13

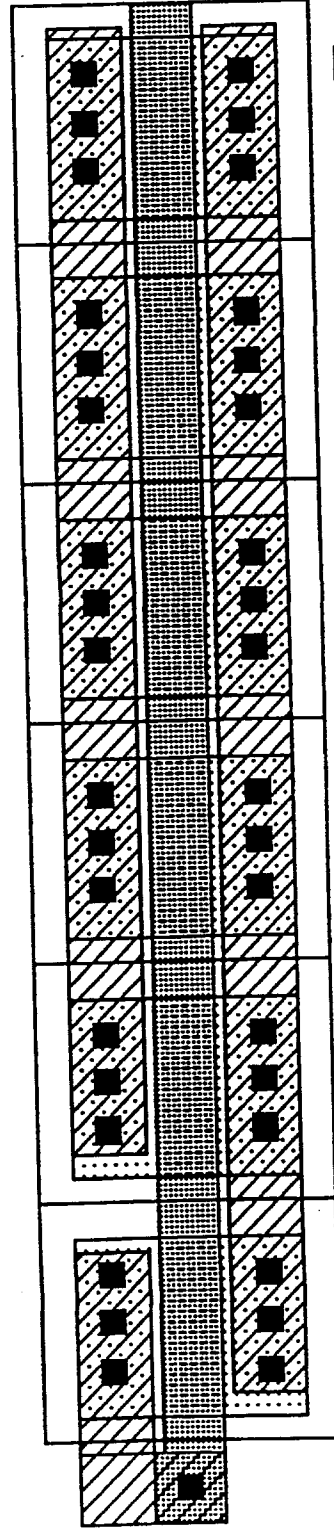

M2 75/5

M1 15/5

P20.13

ANS: See the Hardcopy of the Layout.


P20.14

ANS: a) $I_0/I_{D1} = 1 - 2\Delta V_{thn}/(V_{GS}-V_{thn})^2$. The difference $2\Delta V_{thn}/(V_{GS}-V_{thn})^2$ will decrease as V_{GS} increases.

b) Therefore, the matching would be better with large V_{GS} .

c) The minimum voltage across the current mirror will increase if V_{GS} is increased.

20.15

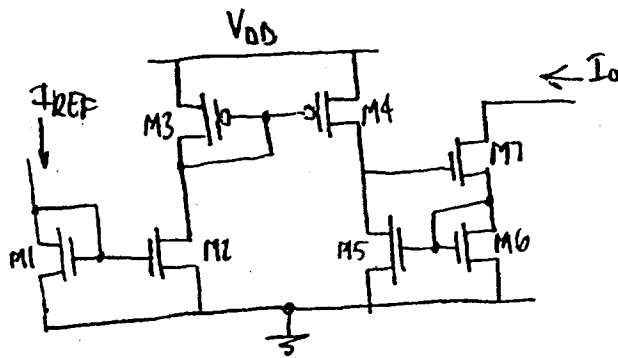

Design so that $I_O = 150\mu A$, $I_{REF} = 50\mu A$, $V_{DD} = 5V$, $V_{SS} = 0$

Philosophy: To minimize area, make $(W/L)_1 = (W/L)_2 = (W/L)_5$.
 Make $(W/L)_3 = (W/L)_4$ + $(W/L)_6 = (W/L)_7 = 3(W/L)_5$.

Iteration 1: Assume $V_{GS} = V_{SG} = 1.2$ + $L = 5$

$$\therefore M1, M2 + M5 \Rightarrow 50\mu A = \frac{50\mu A/U^2}{2} (W/L) (1.2 - 0.83)^2$$

$$(W/L) = 14.6 \Rightarrow W_{1,2,5} = 73\mu m$$

$$M3, M4 \Rightarrow 50\mu A = \frac{17\mu A/U^2}{2} (W/L) (1.2 - 0.91)^2$$

$$(W/L) = 70 \Rightarrow W_{3,4} = 350\mu m$$

Since there is no restriction on $V_{O(min)}$ we can shrink the design by sacrificing the $V_{GS} = V_{SG} = 1.2$ assumption.

Iteration 2: Increase $V_{GS} \approx V_{SG} = 1.5V$. Same analysis as before:

$$(W/L)_{1,2,5} = 4.5 \Rightarrow W_{1,2,5} = 22 \Rightarrow \text{Let's make it } 20\mu m$$

$$\therefore W_{3,4} = 80\mu m \quad ; \quad W_{6,7} = 3(20) = 60\mu m$$

See ASPICE info. following.

The second design will increase $V_{O(min)}$ by $\sim 0.25V$ over the 1st design, but at a greatly reduced area.

*problem 20.15 iteration 2

*

```
m1 g1 g1 vss vss cmosnb w=20u l=5u
m2 g3 g1 vss vss cmosnb w=20u l=5u
m3 g3 g3 vdd vdd cmospb w=80u l=5u
m4 g7 g3 vdd vdd cmospb w=80u l=5u
m5 g7 g6 vss vss cmosnb w=20u l=5u
m6 g6 g6 vss vss cmosnb w=60u l=5u
m7 out g7 g6 vss cmosnb w=60u l=5u
```

```
iref 0 g1 50u
```

```
vdd vdd 0 dc 5
vss vss 0 dc 0
vout out 0 dc 5
```

```
.lib ../spice.models cmosnb
.lib ../spice.models cmospb
.op
.dc vout 0 5 0.25
.print i(m7)
```

```
.end
```

**** mosfets

subckt

element	0:m1	0:m2	0:m3	0:m4	0:m5	0:m6
model	0:cmosnb	0:cmosnb	0:cmospb	0:cmospb	0:cmosnb	0:cmosnb
id	50.0000u	55.7671u	-55.7671u	-55.5374u	55.5374u	153.7303u
vgs	1.6097	1.6097	-1.5673	-1.5673	1.6059	1.6059
vds	1.6097	3.4327	-1.5673	-1.4399	3.5601	1.6059

subckt

element	0:m7
model	0:cmosnb
id	153.7303u
vgs	1.9542
vds	3.3941

20.16 see figure from problem 20.15
 $V_{DD} = 5$, $V_{SS} = 0$, $I_{REF} = 10 \mu A$ all w/L 's = 10/10

a.) Calculate R_{out} , $r_o = \frac{1}{\lambda I_o} \approx \frac{1}{(0.06)(10 \mu A)} = 1.67 M\Omega$

$$R_{out} \approx 2r_o + g_m \frac{r_o^2}{2} \text{ (from eq. 20.47)}$$

$$g_{m2} = \sqrt{(50 \mu A/V^2)(\frac{10}{10} \times 2 \times 10 \mu A)} = 3.16 \times 10^{-5} A/V$$

$$\therefore R_{out} \approx 2(1.67 M\Omega) + (3.16 \times 10^{-5}) \left(\frac{(1.67 M\Omega)^2}{2} \right) = \underline{\underline{47.4 M\Omega}}$$

b.) Verify w/SPICE. See input/output file that follows

$$R_{out} = \frac{v_{oc}}{i_{oc}} = \frac{10 mV}{53 pA} = 188.7 M\Omega! \text{ (HSPICE)}$$

Hand analysis is off by a factor of 4.

c.) $V_{O(min)} = 2 \sqrt{\frac{2I_o L}{kP W}} + V_{THN} = 2.095 V$

d.) See Plot that follows

e.) see Plot that follows - I_o won't go above $\sim 20 \mu A$
 since my w/L 's are so small! Eq. 20.47 doesn't take this into account.

f.) see layout that follows

*problem 20.16

```
m1 g1 g1 vss vss cmosnb w=10u l=10u
m2 g3 g1 vss vss cmosnb w=10u l=10u
m3 g3 g3 vdd vdd cmospb w=10u l=10u
m4 g7 g3 vdd vdd cmospb w=10u l=10u
m5 g7 g6 vss vss cmosnb w=10u l=10u
m6 g6 g6 vss vss cmosnb w=10u l=10u
m7 out g7 g6 vss cmosnb w=10u l=10u
```

```
iref 0 g1 10u
```

```
vdd vdd 0 dc 5
```

```
vss vss 0 dc 0
```

```
vout out 0 ac 10m dc 5 ← 10mV AC signal
```

* Insert models here

*operating point info to check DC values

```
.op
```

*AC analysis for checking Rout

```
.ac lin 10 100 10000
```

* Nested DC sweep for part (e)

```
.dc vout 0 5 0.25 iref 5u 50u 5u
```

```
.print dc i(m7)
```

```
.print ac i(vout)
```

```
.options ingold=2
```

```
.end
```

*problem 20.16

```
***** ac analysis tnom= 25.000 temp= 25.000
```


```
freq current (vout)
```

```
1.0000e+02 5.304e-11
1.2000e+03 5.305e-11
2.3000e+03 5.305e-11
3.4000e+03 5.307e-11
4.5000e+03 5.309e-11
5.6000e+03 5.311e-11
6.7000e+03 5.314e-11
7.8000e+03 5.318e-11
8.9000e+03 5.322e-11
9.9999e+03 5.327e-11
```


← AC current through Vout

$$R_{out} = \frac{10mV}{53pA} = \underline{188.7 M\Omega}$$

Prob. 20-16d

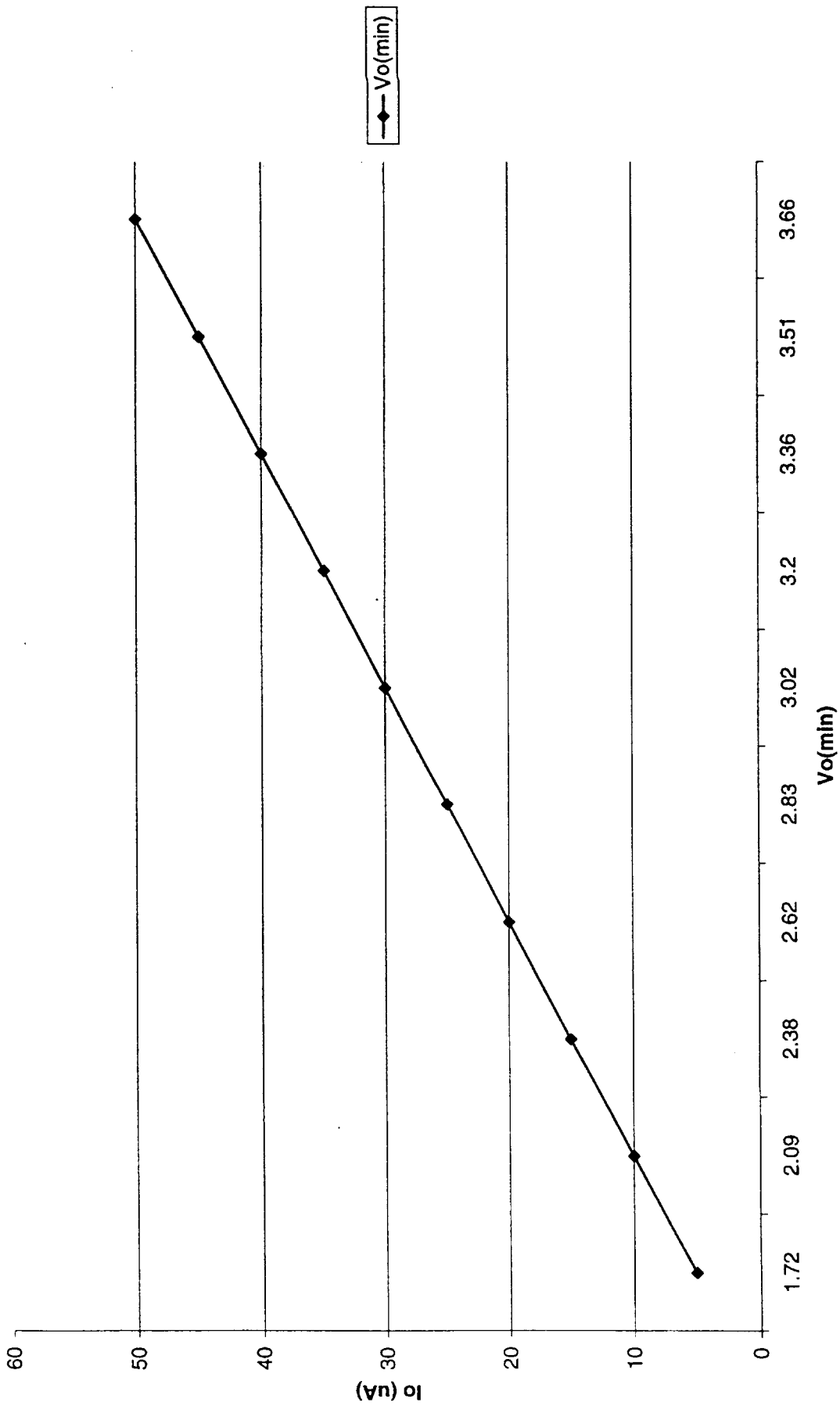


Prob. 20-16e

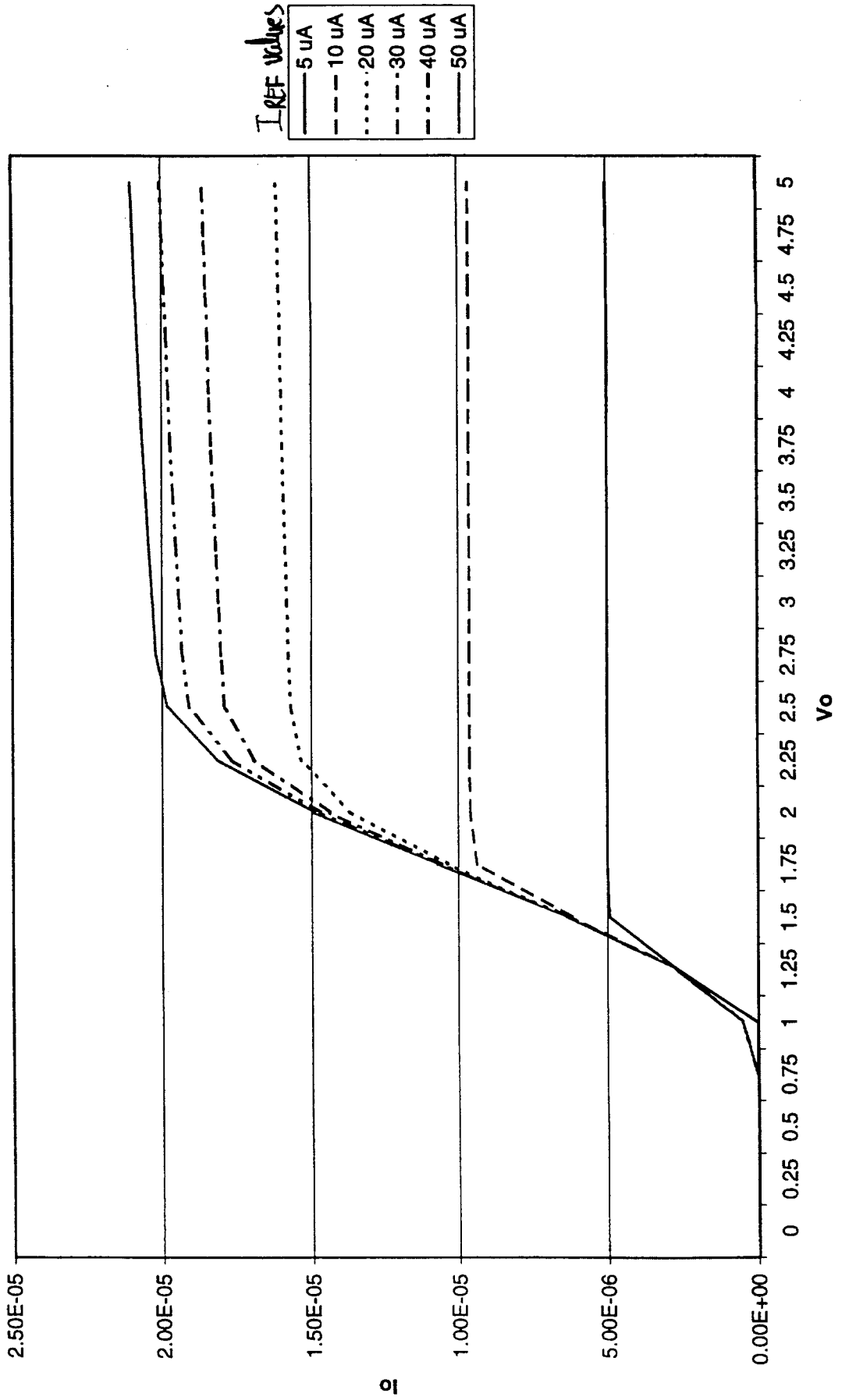


by Kevin McCall

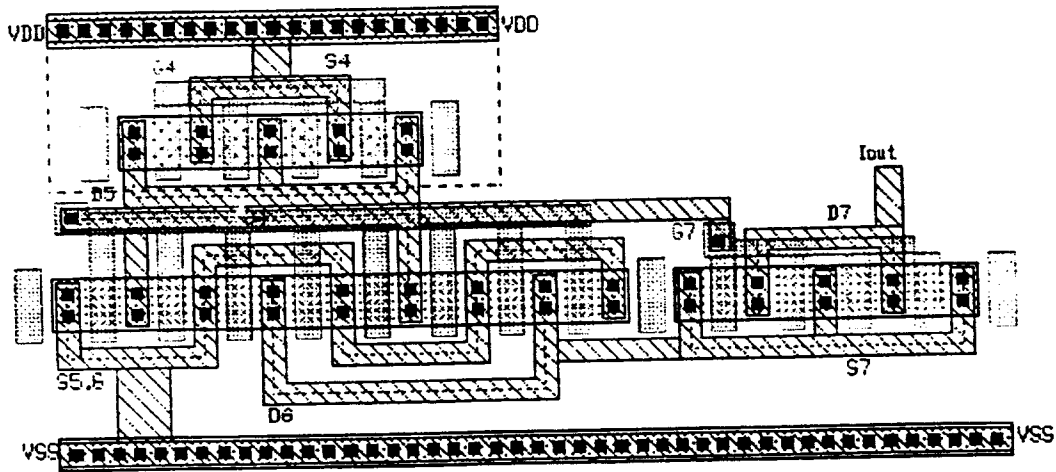Problem 20.16 f) Layout of devices M4 through M7, assuming that each device is 40/5 using an interdigitated layout technique to match devices M5 and M6, using parallel devices for M4 and M7.



20.17

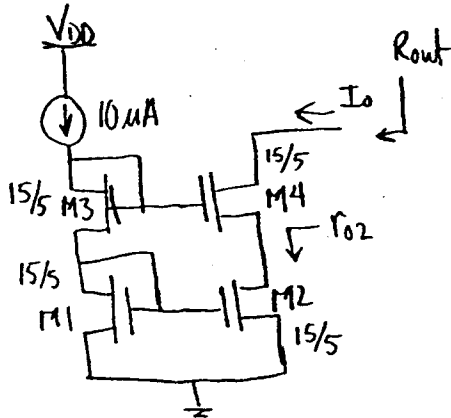a.) Find R_{out}

$$R_{out} = r_{o2} + (1 + g_{m4} r_{o2}) r_{o4}$$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_D} = \frac{1}{(0.06)(10 \mu A)} = 1.67 \text{ M}\Omega$$

$$g_m = \sqrt{2(50 \mu A/V^2)(15/5)(10 \mu A)} = 5.48 \times 10^{-5} \text{ A/V}$$

$$R_{out} = 1.67 \text{ M} + (1 + (5.48 \times 10^{-5})(1.67 \text{ M}))(1.67 \text{ M}) = \underline{\underline{156 \text{ M}\Omega}}$$

b.) Verify w/ SPICE: (see page following)

c.) Calculate $V_{o(\min)}$

$$V_{o(\min)} = 2(\Delta V + V_{THN}) - V_{THN}$$

$$V_{o(\min)} = \sqrt{\frac{2(5)(10 \mu A)}{50 \mu A/V^2(15)}} + 0.83 \approx 1.2 \text{ V}$$

$$\therefore V_{o(\min)} = 2(0.37) + 0.83 = \underline{\underline{1.57 \text{ V}}}$$

d.) Construct plot of I_o vs $V_{o(\min)}$: see page followinge.) Generate I_o vs V_o curves w/ SPICE: see page following

```

*problem 20.17 cascode current mirror
m1 g1 g1 vss vss cmosnb w=15u l=5u
m2 d2 g1 vss vss cmosnb w=15u l=5u
m3 g3 g3 g1 vss cmosnb w=15u l=5u
m4 out g3 d2 vss cmosnb w=15u l=5u

```

```
iref 0 g3 10u
```

```
vss vss 0 dc 0
vout out 0 ac 10m dc 5
```

```
.lib ../spice.models cmosnb
.lib ../spice.models cmospb
```

```
.op
.dc vout 0 5 0.25 iref 5u 50u 5u
.ac lin 10 10 100
.print dc i(m4)
.print ac i(vout)
.options ingold=2
```


```
.end
**** mosfets
```

```
subckt
element 0:m1      0:m2      0:m3      0:m4
model    0:cmosnb 0:cmosnb 0:cmosnb 0:cmosnb
id       1.000e-05 1.002e-05 1.000e-05 1.002e-05
vgs      1.235e+00 1.235e+00 1.608e+00 1.579e+00
vds      1.235e+00 1.263e+00 1.608e+00 3.736e+00
```

```
*problem 20.17 cascode current mirror
```

freq	current vout
1.0000e+01	8.153e-11
2.0000e+01	8.153e-11
3.0000e+01	8.153e-11
4.0000e+01	8.153e-11
5.0000e+01	8.153e-11
6.0000e+01	8.153e-11
7.0000e+01	8.153e-11
8.0000e+01	8.153e-11
9.0000e+01	8.153e-11
1.0000e+02	8.153e-11


p20-17d

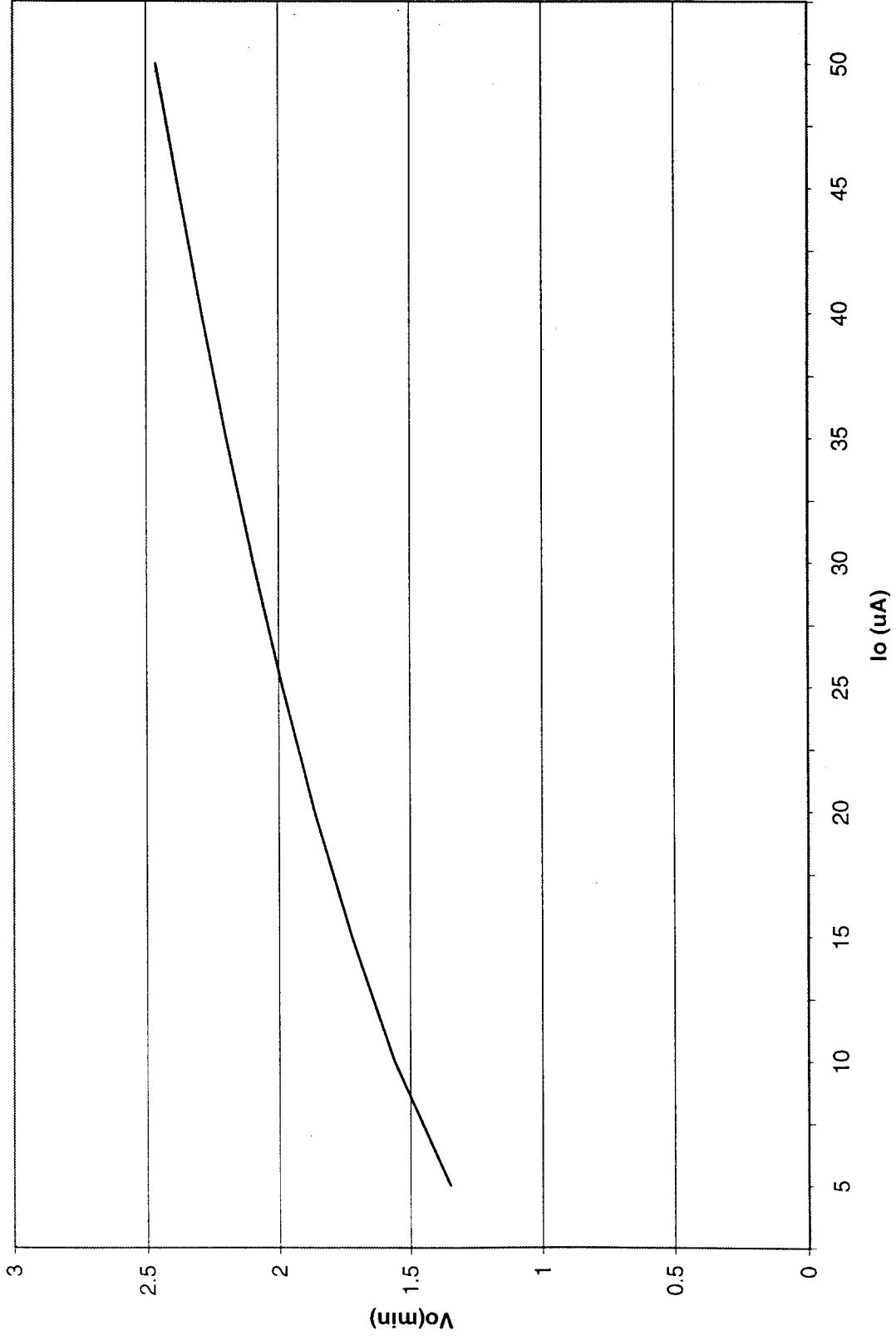

p20-17e



20.18

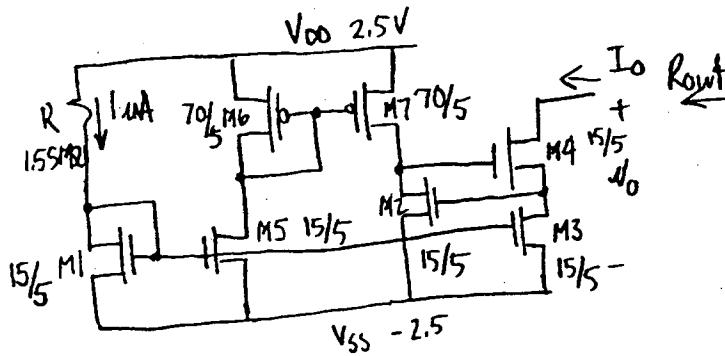

Design the regulated current mirror to sink 1uA.

Since no requirement is specified for $V_{o(min)}$, the design in EX. 20.8 will work fine with difference being the value of R and the fact that V_{GS} for the NMOS devices will be $\approx 0.95V$ & V_{SG} for all the PMOS dev's will be $\approx 1V$. See schematic above.

$$R = \frac{5 - 0.95}{1\mu A} = 4.05 \text{ MEG}$$

$$R_{out} \approx \frac{g_m^2 r_o^3}{2} \Rightarrow g_m = \sqrt{2(50 \times 10^{-6} \text{ A/V}^2)(15/5)(1\mu A)} = 1.732 \times 10^{-5}$$

$$r_o \approx \frac{1}{(0.06)(1\mu A)} = 16.67 \text{ M}\Omega$$

$$\underline{\underline{R_{out} = 6.94 \times 10^{11} \Omega}} \Rightarrow \underline{\underline{R_{out} (HSPICE) = 1.44 \times 10^{12} \Omega}}$$

see SPICE Plot on following page.

*problem 20.18 regulated cascode current mirror

```
m1 g1 g1 vss vss cmosnb w=15u l=5u
m2 g4 g2 vss vss cmosnb w=15u l=5u
m3 g2 g1 vss vss cmosnb w=15u l=5u
m4 out g4 g2 vss cmosnb w=15u l=5u
m5 g6 g1 vss vss cmosnb w=15u l=5u
m6 g6 g6 vdd vdd cmospb w=70u l=5u
m7 g4 g6 vdd vdd cmospb w=70u l=5u
```

```
r1 vdd g1 4.05meg
```

```
vdd vdd 0 dc 2.5
vss vss 0 dc -2.5
```

```
vout out 0 ac 10m dc 2.5
```


```
.lib ../spice.models cmosnb
.lib ../spice.models cmospb
```

```
.op
.ac lin 10 10 100
.print ac i(vout)
.options ingold=2
.end
```

**** mosfets


```
subckt
element 0:m1      0:m2      0:m3      0:m4      0:m5      0:m6
model    0:cmosnb 0:cmosnb 0:cmosnb 0:cmosnb 0:cmosnb 0:cmospb
  id      1.004e-06 1.126e-06 1.004e-06 1.004e-06 1.108e-06 -1.108e-06
  vgs     9.351e-01 9.401e-01 9.351e-01 1.243e+00 9.351e-01 -9.746e-01
  vds     9.351e-01 2.183e+00 9.401e-01 4.059e+00 4.025e+00 -9.746e-01
```
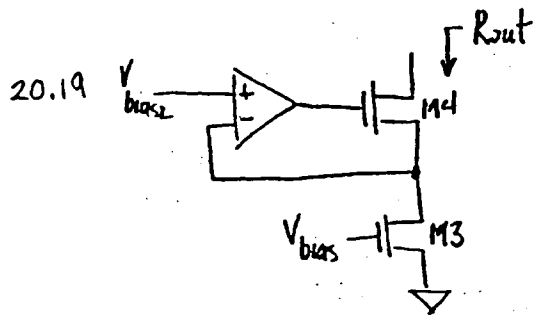
```
subckt
element 0:m7
model    0:cmospb
  id      -1.126e-06
  vgs     -9.746e-01
  vds     -2.816e+00
```



Find R_{out} .
 Show that if the gain of A is $g_m(r_o/2)$, that R_{out} reduces to eq. 20.51.

ignoring bulk effects

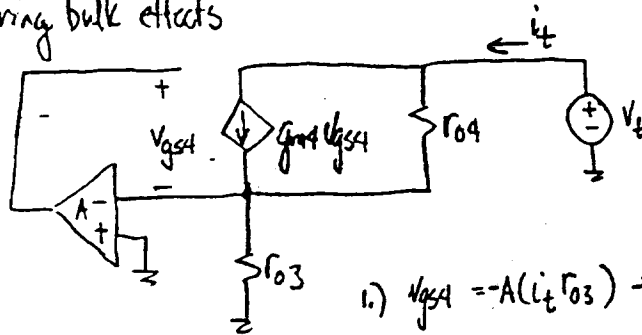

$$1.) v_{gs4} = -A(i_t r_{o3}) = -i_t r_{o3} = -i_t r_{o3} (1+A)$$

$$2.) i_t r_{o3} + (i_t - g_m v_{gs4}) r_{o4} = v_t$$

1.) \rightarrow 2.)

$$i_t r_{o3} + (i_t + g_m i_t r_{o3} (1+A)) r_{o4} = v_t$$

$$\therefore \frac{v_t}{i_t} = \underline{\underline{r_{o3} + (1 + g_m r_{o3} (1+A)) r_{o4} = R_{out}}}$$

If $A = g_m r_o/2$, (and $r_{o3} = r_{o4} = r_o$), then

$$R_{out} = r_o + (1 + g_m r_o (1 + g_m r_o/2)) r_o$$

$$\approx \underline{\underline{\frac{g_m^2 r_o^3}{2}}} \Rightarrow \text{same as eq. 20.51.}$$

P20.20

ANS: a) $V_{G5} = 2\Delta V + V_{thn}$. Plug it into $I_{ref} = (1/2) K_{pn} (W/4L) (V_{G5} - V_{thn})^2 \Rightarrow I_{ref} = (1/2) K_{pn} (W/4L) (2\Delta V - V_{thn} - V_{thn})^2 = I_{ref} = (1/2) K_{pn} (W/4L) (2\Delta V)^2 \Rightarrow$

$$I_{ref} = (1/2) K_{pn} (W/L) (\Delta V)^2 \quad (1)$$


b) Same current goes through M3 and M4,

$$I_{ref} = (1/2) K_{pn} (W/L) (V_{GS3,4} - V_{thn})^2 \quad (2)$$


Comparing equation (1) and (2) $\Rightarrow V_{GS3,4} - V_{thn} = \Delta V$ or $V_{GS3,4} = \Delta V + V_{thn}$.

c) $V_{D1,2} = V_{S3,4} = V_{G3,4} - V_{GS3,4} = V_{G5} - V_{GS3,4} = (2\Delta V + V_{thn}) - (\Delta V + V_{thn}) = \Delta V$

20.21

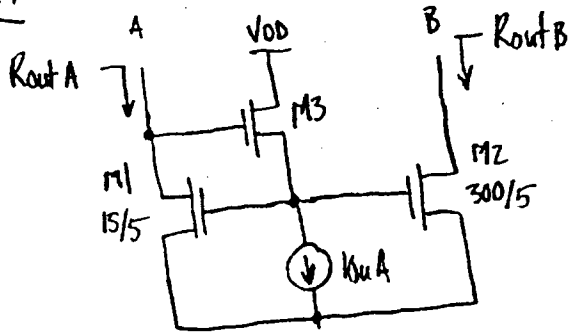

$R_{outB} = r_{o2}$

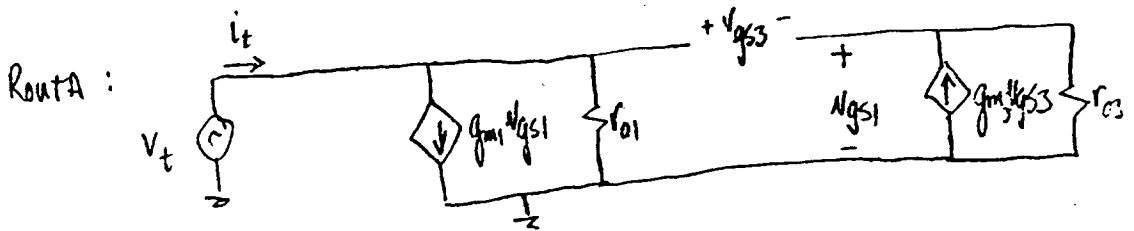

1.) $v_{gs1} = g_{m3} v_{gs3} r_{o3}$

2.) $v_{gs3} = V_t - g_{m1} v_{gs1} r_{o1} \Rightarrow v_{gs3} (1 + g_{m1} r_{o1}) = V_t$

3.) $V_t = (i_t - g_{m1} v_{gs1}) r_{o1}$

$\therefore 1), 2) \rightarrow 3)$

$$V_t = \left(i_t - g_{m1} g_{m3} r_{o3} \frac{V_t}{1 + g_{m3} r_{o3}} \right) r_{o1}$$

$$V_t \left(1 + g_{m1} g_{m3} r_{o3}^2 \left(\frac{1}{1 + g_{m3} r_{o3}} \right) \right) = i_t r_{o1}$$

$$\frac{V_t}{i_t} = \frac{r_{o1}}{\left(1 + g_{m1} g_{m3} r_{o3}^2 \left(\frac{1}{1 + g_{m3} r_{o3}} \right) \right)}$$

$$\approx \frac{r_{o1}}{1 + g_{m1} r_{o3}} = \frac{r_{o1}}{r_{o3}} \frac{1}{\frac{1}{r_{o3}} + g_{m1}} \approx \underline{\underline{\frac{1}{g_{m1}}}} \quad (\text{if } r_{o1} \approx r_{o3})$$

20.21 (cont)

If a resistor connects A to V_{DD} find an equation relating the resistor to both drain currents.

$$V_{GS1} = \sqrt{\frac{2I_{D1}}{\beta_1}} + V_{THN1} = \sqrt{\frac{2I_{D2}}{\beta_2}} + V_{THN2}$$

If $V_{THN1} = V_{THN2}$, then,

$$\frac{I_{D1}}{I_{D2}} = \frac{\beta_1}{\beta_2}$$

$$\frac{V_{DD} - (V_{GS1} + V_{GS3} + V_{SS})}{R} = I_{D1}$$

$$R = \frac{V_{DD} - V_{SS} - \left(\sqrt{\frac{2I_{D1}}{\beta_1}} + V_{THN1} + \sqrt{\frac{2(10\mu A)}{\beta_3}} + V_{THN3} \right)}{I_{D2} \beta_1 / \beta_2}$$