


Problem 21.1

ANS: The schematic is shown in the following figure. To achieve $V_{ref} = 2V$.

$\Rightarrow R = (V_{DD} - V_{ref}) / I_D = (5 - 2)V / 10\mu A = 300\text{ k}\Omega$.

and for $10\mu A$ through the transistor with $V_{GS} = 2V$. $I_D = (K_{Pn}/2) (W/L) (V_{GS} - V_{thn})^2$. Plugging $I_D = 10\mu A$, $K_{Pn} = 50\mu A/V^2$, $V_{GS} = 2V$, and $V_{thn} = 0.83V$. $\Rightarrow W/L = 0.29221$. Choosing $L = 10\mu m$, $\Rightarrow W = 3\mu m$.

 In Summation, $R = 300\text{ k}\Omega$, $W = 3\mu m$, $L = 10\mu m$.




SPICE gives $V_{ref} = 2.2V$ and $I_D = 9.2\mu A$, for details see the following simulation results.

Operating point information:

Node	Voltage
vref	2.244527e+000
V(3)	5.000000e+000
V(4)	5.000000e+000
m1#drain	2.244271e+000
m1#source	2.562588e-004

Source	Current
vdd#branch	-9.18491e-006
v_amm1#branch	9.184909e-006

Problem 21.2

 

$$\frac{5 - V_{ref}}{400k} = \frac{50 \mu A / \sqrt{2}}{2} \times \frac{20}{5} \times (V_{ref} - V_{THN})^2$$

$$\Rightarrow V_{ref} \approx \underline{\underline{1.14 V}}$$

$$TC(V_{ref}) = \frac{1}{V_{ref}} \times \left[V_{THN} \cdot TC V_{TH} - \frac{1}{2} \sqrt{\frac{2L}{W_1} \times \frac{V_{DD}}{R \cdot KP(T)}} \cdot \left[\frac{1}{R} \frac{\partial R}{\partial T} - \frac{1.5}{T} \right] \right]$$

$$TC V_{TH} \approx -3,000 \text{ ppm}/^\circ\text{C} \quad \text{and} \quad TCR = \frac{1}{R} \frac{\partial R}{\partial T} \approx 10,000 \text{ ppm}/^\circ\text{C}$$

$$\Rightarrow TC(V_{ref}) \approx \underline{\underline{-3740 \text{ ppm}/^\circ\text{C}}}$$

SPICE simulation result is shown on next page.

Problem 21.2 (Simulation)

*** (TurboSim V 1.87) Netlist for C:\TS\SOLUTION\21_2.CKT

*** Top Level Netlist ***

```
M1 Vref Vref 0 0 CMOSNB L=5u W=20u
R1 Vref 3 400k TC1=0.01
VDD 3 0 DC 5 AC 0 0
```


***** Spice models and macro models *****

```
.MODEL CMOSNB NMOS LEVEL=4
```

***** End of spice models and macro models *****

```
.DC temp -50 150 1
.probe
.end
```

The SPICE simulation is shown below:

 


```
Exit Add_trace Remove_trace X_axis Y_axis Plot_control Display_control
File Macros Hard_copy Cursor Zoom Label config_colors
```

 Problem 21.3

ANS: Same as problem 21.1, for M1, it will come out the design results $W1 = 3\mu\text{m}$ and $L1 = 10\mu\text{m}$. For M2, solving the equation $10\ \mu\text{A} = (17\ \mu\text{A}/\text{V}^2/2) \cdot (W2/L2) \cdot (3 - 0.916)^2$, $\implies W2/L2 = 0.27$. Choosing $W2 = 3\mu\text{m}$, $\implies L2 = 11\mu\text{m}$.

For the sizes, SPICE simulation gives $V_{\text{ref}} = 2.05\ \text{V}$ but the $I_D = 6.67\ \mu\text{A}$. There is some deviation between hand calculation and SPICE simulation. Remember the two MOSFETs behave like two resistors. If we want to keep V_{ref} as about $2\ \text{V}$ and increase I_D to about $10\ \mu\text{A}$, we need to decrease the two resistors in same ratio. The MOSFET resistor is proportional to L/W , so either increasing W or decreasing L will achieve the goal. The trial and error yields that $I_D = 9.68\ \mu\text{A}$ and $V_{\text{ref}} = 2.04\ \text{V}$ by keeping $W1 = W2 = 3\ \mu\text{m}$ but reducing $L1$ to $7\ \mu\text{m}$ and $L2$ to $8\ \mu\text{m}$. See the following data list for the detail.




Operating point information:

Node	Voltage
vref	2.036651e+000
V(4)	5.000000e+000
V(3)	5.000000e+000
m2#drain	2.037180e+000
m2#source	4.999470e+000
m1#drain	2.036381e+000
m1#source	2.700999e-004

Source	Current
vdd#branch	-9.68101e-006
v_amm1#branch	9.681000e-006

Problem 21.4 and 21.5

 

$$V_{ref} = \frac{V_{DD} - V_{THP} + \sqrt{\frac{\beta_1}{\beta_2}} (V_{SS} + V_{THN})}{\sqrt{\frac{\beta_1}{\beta_2}} + 1}$$

$$= \frac{5 - 0.91 + \sqrt{\frac{50}{17}} (0 + 0.83)}{\sqrt{\frac{50}{17}} + 1}$$

$$\approx 2.03 \text{ V}$$

$$TC(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{1}{\sqrt{\frac{\beta_1}{\beta_2}} + 1} \left[\frac{\partial(-V_{THP})}{\partial T} + \sqrt{\frac{\beta_1}{\beta_2}} \frac{\partial V_{THN}}{\partial T} \right]$$

$$= \frac{1}{2.03} \cdot \frac{1}{\sqrt{\frac{50}{17}} + 1} \left[2.7 \cdot 10^{-3} \text{ V}/^\circ\text{C} + \sqrt{\frac{50}{17}} \cdot (-2.4 \cdot 10^{-3}) \text{ V}/^\circ\text{C} \right]$$

$$\approx \underline{\underline{-256.9 \text{ ppm}/^\circ\text{C}}}$$

$$S_{V_{DD}}^{V_{ref}} = \frac{V_{DD}}{V_{DD} - V_{THP} + \sqrt{\frac{\beta_1}{\beta_2}} (V_{SS} + V_{THN})}$$

$$= \frac{5}{5 - 0.91 + \sqrt{\frac{50}{17}} (0 + 0.83)} \approx \underline{\underline{0.907}}$$

Problem 21.4 (simulation)

*** Top Level Netlist ***

```
M1 Vref Vref 0 0 CMOSNB L=20u W=20u
M2 Vref Vref 3 3 CMOSPFB L=20u W=20u
VDD 3 0 DC 5 AC 0 0
```

***** Spice models and macro models *****

```
.MODEL CMOSNB NMOS LEVEL=4
```

```
.MODEL CMOSPFB PMOS LEVEL=4
```


***** End of spice models and macro models *****

```
.DC temp -50 150 1
```

```
.probe
```

```
.end
```

The SPICE simulation is shown below:

 


Problem 21.7

ANS: The figure is shown in Figure P21.7 @page 462. For M1:
 $ID1 = (KPn/2) * (W1/L1) * (VGS1 - V_{thn})^2$. Notice $VGS1 = ID2 * 830K = ID1 * 830k$ i.e.
 $ID1 = (50\mu A/V^2/2) * (100\mu/2\mu) * (ID1 * 830k - 0.83)^2$, solving the equation $\implies ID1 \approx 1\mu A$. Therefore,
 $\implies I = 2 * ID1 = 2\mu A$.

Problem 21.9


Layout of the PNP

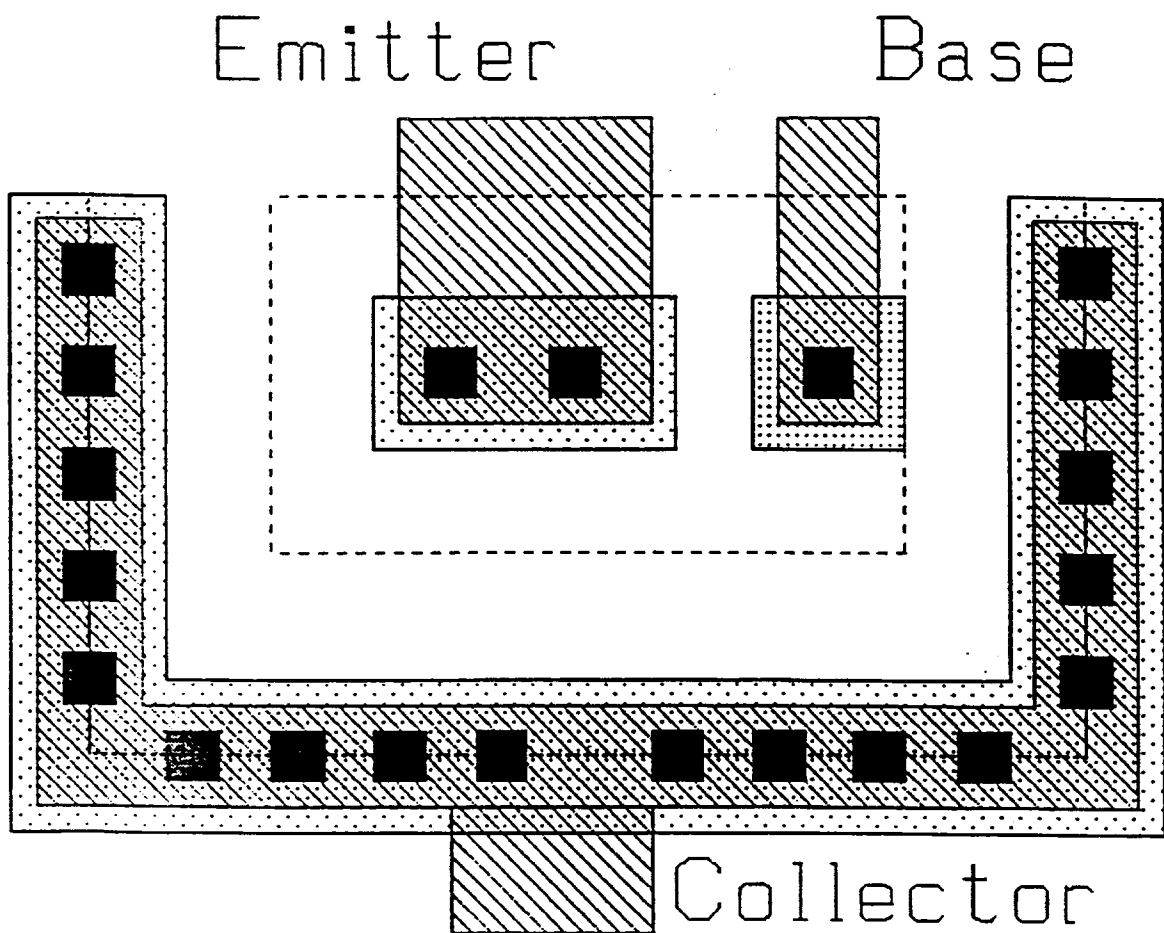

The more realistic value for the scale current of the diode model is 10^{-15} A if the area specified for the diode is 1.

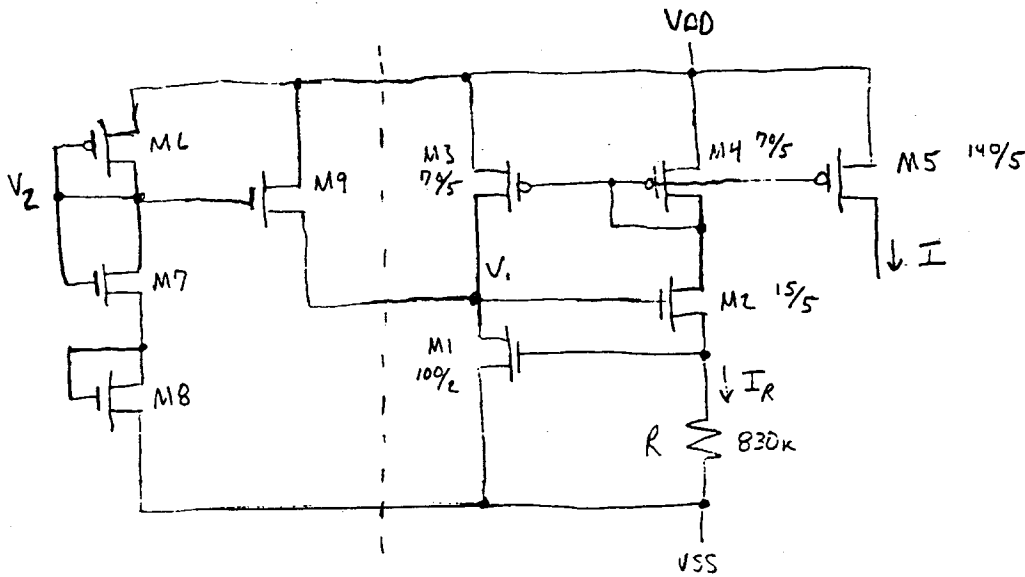21.8

Sketch a startup circuit for the threshold-voltage referenced current source of Fig. P21.7. Assume the maximum current in the startup circuit is 1 μ A.



$$I_R \approx \frac{.83}{830k} \approx 1 \mu A$$

Find V_1 when the devices in the current source are saturated.

$$1 \mu A = \frac{50 \mu A/V^2}{2} \frac{15}{5} (V_{GS2} - .83)^2$$

$$V_{GS2}^2 - 1.66 V_{GS2} + .6756$$

$$V_{GS2} = 0.9455 V$$

$$\therefore V_1 = .83 + .9455 = 1.78 V$$

To design the startup circuit, make V_{GS} of M9 less than V_{THN} when M1, M2, M3, + M4 are saturated.

$$\text{Choose } V_2 = 2.0V \text{ so } V_{GS9} = 2 - 1.78 = .22V$$

$$\text{Make } V_{GS7} = V_{GS8} = 1.0V$$

$$1 \mu A = \frac{50 \mu A/V^2}{2} \frac{W}{L} (1 - .83)^2$$

$$\frac{W}{L} = 1.384$$

$$L = 5 \mu m \quad \text{for } M7 + M8$$

$$W = 7 \mu m$$

Now size M6

21.8 can't

$$V_{SG6} = 5 - 2 = 3V$$

$$I_{uA} = \frac{17 \mu A / \sqrt{2}}{2} \frac{W}{L} (3 - 0.91)^2$$

$$\frac{W}{L} = .02693$$

$$L = 150 \mu m$$

$$W = 4 \mu m$$

Now size M9

The size of M9 is not critical for the operation of the startup circuit since it only operates for a short period of time then turns off. We want M9 to be able to source current until V_i is high enough to shut M9 off, and thus the current source will be operating at the correct point.

To minimize layout area, make M9 minimum size.

$$W = 3 \mu m$$

$$L = 2 \mu m$$

21.10

Design a 5 μ A current source using the diode referenced self-biasing circuit of Fig. 21.11. Verify the operation of your design using SPICE.

For the current source:

$$R = \frac{n \cdot V_T}{I} \ln \frac{I}{I_S}$$

$$= \frac{26 \text{ mV}}{5 \mu} \ln \frac{5 \mu}{10^{-15}}$$

$$= 116.1 \Omega$$

Make V_{GS} the same for all n-channel devices.

$$V_{GS} = 1.2 \text{ V}$$

$$5 \mu\text{A} = \frac{50 \mu\text{A}/\sqrt{2}}{2} \frac{W}{L} (1.2 - 0.83)^2$$

$$\frac{W}{L} = 1.46$$

$$W_1 = W_2 = W_3 = W_4 = 7 \mu\text{m}$$

$$L_1 = L_2 = L_3 = L_4 = 5 \mu\text{m}$$

For all p-channel devices

Make $V_{SG} = 1.2 \text{ V}$

$$5 \mu\text{A} = \frac{17 \mu\text{A}/\sqrt{2}}{2} \frac{W}{L} (1.2 - 0.91)^2$$

$$\frac{W}{L} = 7$$

$$W_5 = W_6 = W_7 = W_8 = W_9 = W_{10} = 35 \mu\text{m}$$



$$L_5 = L_6 = L_7 = L_8 = L_9 = L_{10} = 5 \mu\text{m}$$

For the start up circuit:

$$V_x = 5 \mu(116.1 \text{ k}) + 2.4 = 2.98 \text{ V}$$

Make $V_{G15} < V_x$ $V_{G15} = 2.5 \text{ V}$

and choose $I_S = 0.5 \mu\text{A}$

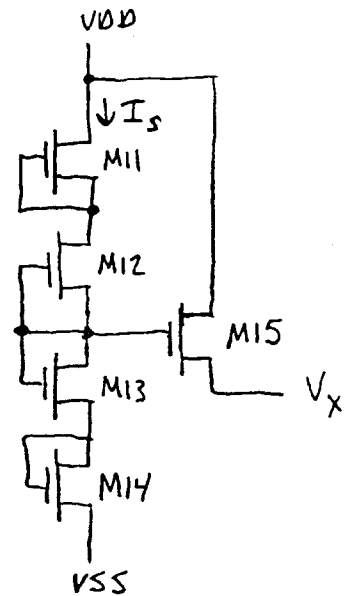 

start up circuit

Make $V_{SG} = V_{GS} = 1.25 \text{ V}$

For M13 + M14

$$0.5 \mu\text{A} = \frac{50 \mu\text{A}/\text{V}^2}{2} \frac{W}{L} (1.25 - 0.83)^2$$

$$\frac{W}{L} = .1134$$

$$W = 5 \mu\text{m}$$

$$L = 45 \mu\text{m}$$

For M11 + M12

$$0.5 \mu\text{A} = \frac{17 \mu\text{A}/\text{V}^2}{2} \frac{W}{L} (1.25 - 0.91)^2$$

$$\frac{W}{L} = .5089$$

$$W = 5 \mu\text{m}$$

$$L = 10 \mu\text{m}$$

Design M6 to be minimum size

$$W = 3 \mu\text{m}$$

$$L = 2 \mu\text{m}$$

**** 02/22/98 19:36:27 ***** Win95 PSpice 6.3a (June 1996) **** ID# 90771 ****

* Problem 21.10

**** CIRCUIT DESCRIPTION

R1 3 0 116.1k
D1 1 0 PNPDIOD
M1 2 2 1 0 CMOSNB L=5u W=7u
M2 4 2 3 0 CMOSNB L=5u W=7u
M3 5 5 2 0 CMOSNB L=5u W=7u
M4 6 5 4 0 CMOSNB L=5u W=7u
M5 5 6 7 9 CMOSPB L=5u W=35u
M6 6 6 8 9 CMOSPB L=5u W=35u
M7 7 8 9 9 CMOSPB L=5u W=35u
M8 8 8 9 9 CMOSPB L=5u W=35u
M9 10 8 9 9 CMOSPB L=5u W=35u
M10 11 6 10 9 CMOSPB L=5u W=35u
M11 13 13 9 9 CMOSPB L=10u W=5u
M12 12 12 13 9 CMOSPB L=10u W=5u
M13 12 12 14 0 CMOSNB L=45u W=5u
M14 14 14 0 0 CMOSNB L=45u W=5u
M15 9 12 5 0 CMOSNB L=2u W=3u
VOUT 11 0 DC 2.2V
VDD 9 0 DC 5.0V
.OP
.MODEL PNPDIOD D(is=1E-15 n=1)

* BSIM model for n-channel CN20
* BSIM model for p-channel CN20

**** MOSFETS

NAME	M1	M2	M3	M4	M5
MODEL	CMOSNB	CMOSNB	CMOSNB	CMOSNB	CMOSPB
ID	4.93E-06	4.96E-06	4.93E-06	4.96E-06	-4.93E-06
VGS	1.51E+00	1.51E+00	1.82E+00	1.86E+00	-1.66E+00
VDS	1.51E+00	1.47E+00	1.82E+00	2.86E-01	-8.28E-02

NAME	M6	M7	M8	M9	M10
MODEL	CMOSPB	CMOSPB	CMOSPB	CMOSPB	CMOSPB
ID	-4.96E-06	-4.93E-06	-4.96E-06	-4.96E-06	-4.96E-06
VGS	-1.49E+00	-1.18E+00	-1.18E+00	-1.18E+00	-1.49E+00
VDS	-1.49E+00	-1.02E+00	-1.18E+00	-1.18E+00	-1.62E+00

NAME	M11	M12	M13	M14	M15
MODEL	CMOSPB	CMOSPB	CMOSNB	CMOSNB	CMOSNB
ID	-9.56E-08	-9.56E-08	9.56E-08	9.56E-08	5.01E-12
VGS	-1.05E+00	-1.32E+00	1.53E+00	1.09E+00	-1.27E+00
VDS	-1.05E+00	-1.32E+00	1.53E+00	1.09E+00	1.10E+00

Problem 21.11

For Fig 21.12, if we require the current is $5\mu\text{A}$, and the gate-source voltages are 1.2V , we get,

For n-channel devices:

$$5\mu\text{A} = \frac{50\mu\text{A}/\text{V}^2 \times W}{2 \times L} (1.2\text{V} - 0.83\text{V})^2 \Rightarrow \left(\frac{W}{L}\right)_n = 1.46$$

Set $L_n = \underline{5\mu\text{m}}$, $W_n = \underline{7\mu\text{m}}$.

For p-channel devices:

$$5\mu\text{A} = \frac{17\mu\text{A}/\text{V}^2 \times W}{2 \times L} (1.2 - 0.91)^2 \Rightarrow \left(\frac{W}{L}\right)_p \approx 7$$

Set $L_p = \underline{5\mu\text{m}}$, $W_p = \underline{35\mu\text{m}}$.

Also, set $k = 8$, ($n = 1$)

$$R = \frac{nV_T \times \ln k}{I} = \frac{1 \times 26\text{mV} \times \ln 8}{5\mu\text{A}} \approx \underline{\underline{10.8\text{k}\Omega}}$$

See next page for SPICE simulations.

Problem 21.11 (*simulation*)

*** Top Level Netlist ***

```
D1 7 3 pnpdioid
D2 8 3 pnpdioid 8
M1 4 4 7 3 CMOSNB L=5u W=7u
M2 2 4 11 3 CMOSNB L=5u W=7u
M3 1 1 4 3 CMOSNB L=5u W=7u
M4 9 1 2 3 CMOSNB L=5u W=7u
M5 1 9 12 6 CMOSP B L=5u W=35u
M6 9 9 10 6 CMOSP B L=5u W=35u
M7 12 10 6 6 CMOSP B L=5u W=35u
M8 10 10 6 6 CMOSP B L=5u W=35u
M9 13 10 6 6 CMOSP B L=5u W=35u
M10 14 9 13 6 CMOSP B L=5u W=35u
R1 8 11 10.8k TC1=0.002
VDD 6 0 DC 2.5v AC 0 0
Vout 14 0 DC 0 AC 0 0
VSS 3 0 DC -2.5v AC 0 0
.NODESET V(8)=0 V(2)=0 V(12)=0
```

***** Spice models and macro models *****

```
.MODEL PNPDIOD D
+IS=1E-15 n=1
.MODEL CMOSNB NMOS LEVEL=4
```

```
.MODEL CMOSP B PMOS LEVEL=4
```

***** End of spice models and macro models *****

```
*.OPTION post=3 acct opts VZERO=2 $probe=1
```

```
.OPTION ABSTOL=1n RELTOL=0.01 VNTOL=1mv ITL1=100 ITL2=100
```

```
.probe
```


```
.DC Vout -1 1 .01 temp -25 75 25
```

```
*.print DC all
```

```
.end
```

The SPICE simulation is shown on next page:

Problem 21.11 (simulation, cont.)

 

Problem 21.12

ANS: The figure is shown in figure 21.14 @Page454.

$$V_{d1} = IR + V_{d2} \quad (1)$$

$$\text{From } I_{d1} = I_s \cdot \exp(V_{d1}/nV_t) \implies V_{d1} = nV_t \cdot \ln(I/I_s) \quad (2)$$

$$I_{d2} = K \cdot I_s \cdot \exp(V_{d2}/nV_t) \implies V_{d2} = nV_t \cdot \ln[I/(K \cdot I_s)] \quad (3)$$

$$IR = V_{d1} - V_{d2} = nV_t \cdot [\ln(I/I_s) - \ln[I/(K \cdot I_s)]] = nV_t \cdot \ln K \quad (4)$$

$$\implies I = nV_t \cdot \ln K / R \quad (5)$$

$$\text{Since } V_{ref} = I \cdot R + L + V_{d3} \quad (6)$$

$$\text{From } I_{d3} = K \cdot I_s \cdot \exp(V_{d3}/nV_t) \implies V_{d3} = nV_t \cdot \ln[I/(K \cdot I_s)] \quad (7)$$

Plugging (5) and (7) into (6)

$$V_{ref} = L + nV_t \cdot \ln K + nV_t \cdot \ln[I/(K \cdot I_s)] \quad (8)$$

Plugging $n=1$, $K=8$, $T=300K$, $I=10\mu A$ and $I_s=10^{-15} A$ into equation (8) \implies

$$\text{@ } L=11.3 \quad V_{ref} = 1.15V$$

$$\text{@ } L=12 \quad V_{ref} = 1.20V$$

So, the reference voltage increases with L increasing.

Problem 21.13

ANS: The figure is shown in figure P21.13. Assuming the current through D1 is $ID1$ and through D2 is $ID2$. Since the voltage at '+' and '-' terminals of the Op-amp with infinite open loop gain is equal, i.e.

$$V_{ref} - ID1 \cdot LR = V_{ref} - ID2 \cdot LR \quad \Rightarrow \quad ID1 = ID2 = I \quad (1)$$

Also

$$I \cdot R + V_{d1} = V_{d2} \quad (2)$$

As shown in problem 21.12, $V_{d1} = nV_t \cdot \ln[I/(K \cdot I_s)]$ and $V_{d2} = nV_t \cdot \ln(I/I_s)$ (3)

Plugging (3) into (2), \Rightarrow

$$I = (nV_t \cdot \ln K) / R \quad (4)$$

$$V_{ref} = I \cdot R \cdot L + V_{d2} = (L \cdot n \cdot \ln K) V_t + nV_t \cdot \ln(I/I_s) \quad (5)$$

By definition of TC from ch.7, $TC_{V_{ref}} = (1/V_{ref}) \cdot dV_{ref}/dT = *1/V_{ref}) \cdot [L \cdot n \cdot \ln K \cdot (dV_t/dT) + dV_{d2}/dT]$
Let $TC_{V_{ref}} = 0$, and plugging $dV_t/dT = 0.085 \text{ mV/C}$, $dV_{d2}/dT = -2 \text{ mV/C}$, \Rightarrow

$$L \cdot n \cdot \ln K = 2/0.085 = 23.5$$

Problem 21.15

Solution: Select M4 $5\mu/5\mu$, M3 and M5 $15\mu/5\mu$, Select $K=4$, \Rightarrow M6 $20\mu/5\mu$. Same start-up circuit as figure 21.17 of Textbook, and the rest PMOS with size $70\mu/5\mu$. Plugging the values into equation (21.46) and @ $T=300 \text{ K}$, It comes out the TC expression of V_{ref} which was chosen as V_{GS4} is:

$$\begin{aligned} dV_{ref}/dT &= -2400 + 3000/(R\beta_4) \\ &= -2400 + 6 \times 10^7 / R \end{aligned} \quad (1)$$

Note: β_1 in the equation becomes β_4 , see the schematic below.

By definition of TC in Ch.7,

$$TC_{V_{ref}} = (1/V_{ref}) \cdot dV_{ref}/dT \quad (2)$$

Notice: $V_{ref} = V_{GS4} = V_{thn} + \text{SQRT}(2 \cdot ID/\beta_4)$ (3)


ID is the current through MOSFETs M3, M4, M5, M6, and M9 ~ M12. By neglecting the body effect of M6, \Rightarrow (see equation (21.39) to (21.41)

$$ID = [2/(R^2 \cdot \beta_4)] \cdot [1 - \text{SQRT}(1/K)]^2 = 1000/R^2 \quad (4)$$

Plugging equation (4) into (3), $\Rightarrow V_{ref} = V_{thn} + 20000/R$ (5)

Plugging equation (1), (5) into (2), Let $TC_{V_{ref}}$ equals to $1000 \text{ ppm/}^\circ\text{C}$, get $R = 8 \times 10^7 / 3230 = 24.77 \text{ k}\Omega$.
The circuit design is shown below which was simulated in Turbosim. $V_{SS} = -2.55 \text{ V}$, $V_{DD} = 2.5 \text{ V}$.

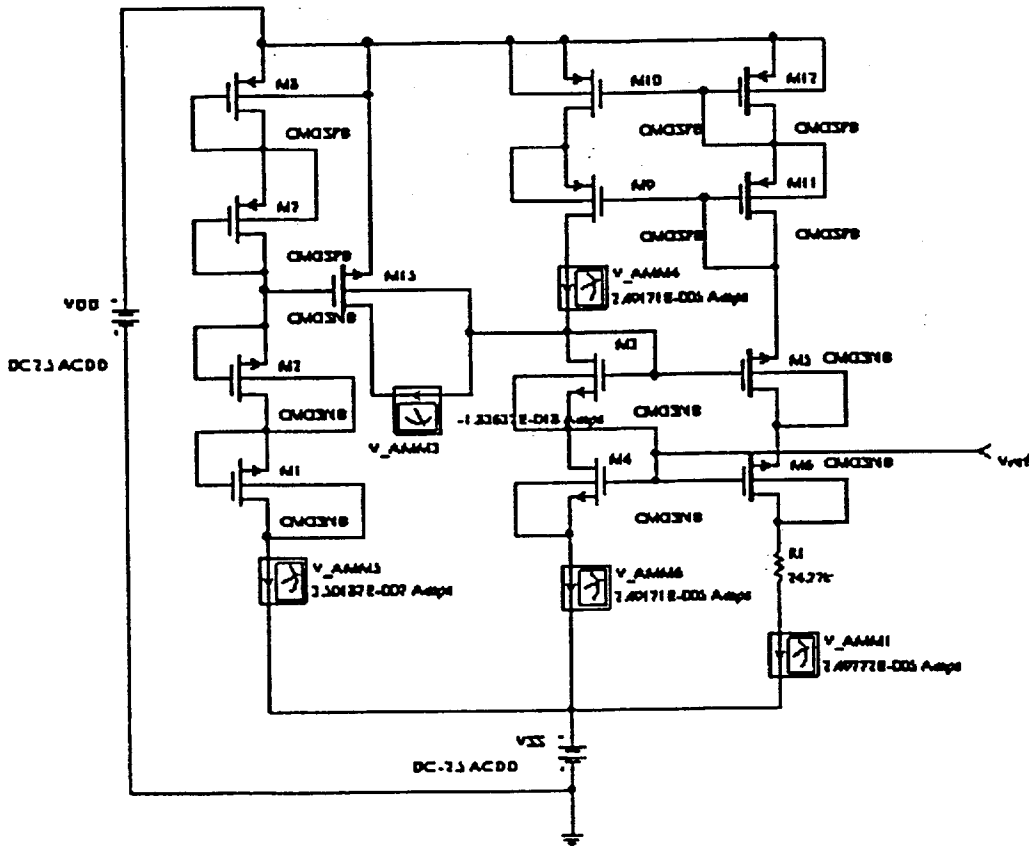Notice equation (3) gives hand calculation of V_{ref} is about 1.63 V . But TurboSim gives about $-0.5 - (-2.5) = 2 \text{ V}$. The error mainly due to the body effect of M6.



The following netlist was generated:
 *** (TurboSim V 1.1) Netlist for C:\TSP2115V4.CKT

```

*** Top Level Netlist ***
M1      1 2 2 1 CMOSNB L=5u W=15u
M10     13 14 18 18 CMOSPBL=5u W=70u
M11     9 9 14 14 CMOSPBL=5u W=70u
M12     14 14 18 18 CMOSPBL=5u W=70u
M15     15 3 18 4 CMOSNB L=2u W=3u
M2      2 3 3 2 CMOSNB L=5u W=15u
M3      4 4 Vref Vref CMOSNB L=5u W=15u
M4      Vref Vref 7 7 CMOSNB L=5u W=5u
M5      8 4 9 8 CMOSNB L=5u W=15u
M6      10 Vref 8 10 CMOSNB L=5u W=20u
M7      3 3 11 11 CMOSPBL=50u W=5u
M8      11 11 18 18 CMOSPBL=50u W=5u
M9      12 9 13 13 CMOSPBL=5u W=70u
R1      10 17 24.77k
V_AMM1  17 6 0V
V_AMM3  4 15 0V
V_AMM4  12 4 0V
V_AMM5  1 6 0V
V_AMM6  7 6 0V
VDD     180      DC 2.5 AC 0 0
VSS     60      DC -2.5 AC 0 0
***** Spice models and macro models *****
.MODEL CMOSNB NMOS LEVEL=4
*BSIM model*
.MODEL CMOSPBL PMOS LEVEL=4
*BSIM model*
***** End of spice models and macro models *****
.OPTION ABSTOL=1u CHGTOL=1p RELTOL=0.01 VNTOL=1mv
.op
.end
  
```

Operating Point Analysis gives the following results:


Operating point information:

Node	Voltage
V(1)	-2.50000e+000
V(2)	-1.64389e+000
V(13)	1.213438e+000
V(14)	1.138767e+000
V(18)	2.500000e+000
V(9)	-2.22467e-001
V(15)	9.795691e-001
V(3)	-7.87785e-001
V(4)	9.795691e-001
vref	-4.96132e-001
V(7)	-2.50000e+000
V(8)	-5.62917e-001
V(10)	-1.88132e+000
V(11)	8.561073e-001
V(12)	9.795691e-001
V(17)	-2.50000e+000
V(6)	-2.50000e+000
m9#drain	9.809321e-001
m9#source	1.212075e+000
m8#drain	8.561265e-001
m8#source	2.499981e+000
m7#drain	-7.87766e-001
m7#source	8.560881e-001
m12#drain	1.140133e+000
m12#source	2.498634e+000
m11#drain	-2.21101e-001
m11#source	1.137400e+000
m10#drain	1.214801e+000
m10#source	2.498637e+000
m6#drain	-1.88062e+000
m6#source	-5.63614e-001
m5#drain	-5.62220e-001
m5#source	-2.23164e-001
m4#drain	-4.96827e-001
m4#source	-2.49930e+000
m3#drain	9.788739e-001
m3#source	-4.95437e-001
m2#drain	-1.64388e+000
m2#source	-7.87795e-001
m15#drain	9.795691e-001
m15#source	2.500000e+000
m1#drain	-2.49999e+000
m1#source	-1.64390e+000

Source Current

Source	Current
vss#branch	5.024445e-005
vdd#branch	-5.024445e-005
v_amm6#branch	2.491711e-005
v_amm5#branch	3.501874e-007
v_amm4#branch	2.491711e-005
v_amm3#branch	-1.83637e-018
v_amm1#branch	2.497715e-005

Problem 21.14

 

The power dissipation of the startup circuit is

$$P_{ST} = I_{ST} \cdot (2.5V - (-2.5V)) = I_{ST} \cdot 5(V)$$

We first calculate V_{GSN} and V_{SGP} ,

$$\begin{cases} 2(V_{GSN} + V_{SGP}) = 5 \\ \frac{50\mu A/V^2 \times 15}{2 \times 5} (V_{GSN} - 0.83)^2 = \frac{17\mu A/V^2 \times 5}{2 \times 50} (V_{SGP} - 0.91)^2 \end{cases}$$

$$\Rightarrow V_{GSN} \approx 0.9V \text{ and } V_{SGP} \approx 1.6V.$$


$$I_{ST} = \frac{17\mu A/V^2 \times 5}{2 \times 50} \cdot (1.6 - 0.91)^2 \approx \underline{\underline{0.4\mu A}}$$

$$\therefore P_{ST} = I_{ST} \cdot (V_{DD} - V_{SS}) = 5V \times 0.4\mu A = \underline{\underline{2\mu W}}$$

 21.16

The β multiplier reference is an example of a circuit that uses positive feedback. Discuss methods of ensuring a stable operating point for the circuit.

Since the gain from V_1 to V_2 is negative and the gain from V_2 to V_1 is negative, the loop has positive feedback. For a stable circuit the feedback, the feedback gain must be less than 1.



$$\text{Gain} = \frac{V_2}{V_1} \cdot \frac{V_1}{V_2} = \left(\frac{-\frac{1}{g_{m4}}}{\frac{1}{g_{m4}} + R} \right) \left(-\frac{g_{m3}}{g_{m1}} \right)$$

$$\text{since } g_{m3} = g_{m4}$$

$$\text{Gain} = \frac{1}{\frac{g_{m1}}{g_{m2}} + g_{m1} R}$$

$$\text{also } g_{m2} = \sqrt{K} g_{m1}$$

$$\text{Gain} = \frac{1}{\frac{1}{\sqrt{K}} + g_{m1} R}$$

$$g_{m1} = \sqrt{2\beta_1 I_0}$$

$$I_0 = \frac{2}{R^2 \beta_1} \cdot \left(1 - \sqrt{\frac{1}{K}} \right)^2$$

Substituting I_0 into the equation for g_{m1} yields

$$g_{m1} = \frac{2}{R} \left(1 - \sqrt{\frac{1}{K}} \right)$$

$$\therefore \text{Gain} = \frac{1}{2 - \sqrt{\frac{1}{K}}}$$


For the Gain < 1 , $K > 1$!

21.17


An important consideration in the design of a voltage or current reference is the design of the startup circuit. Consider the portion of the bandgap reference of Fig. P21.13 shown in Fig. 21.17a. Using SPICE, plot V_{REF} against V_{plus} and V_{minus} . The result should look similar to Fig. P21.17b. Design a start up circuit for the bandgap of Fig. 21.13

For the simulation use the values calculated for a TC=0 on p. 479.

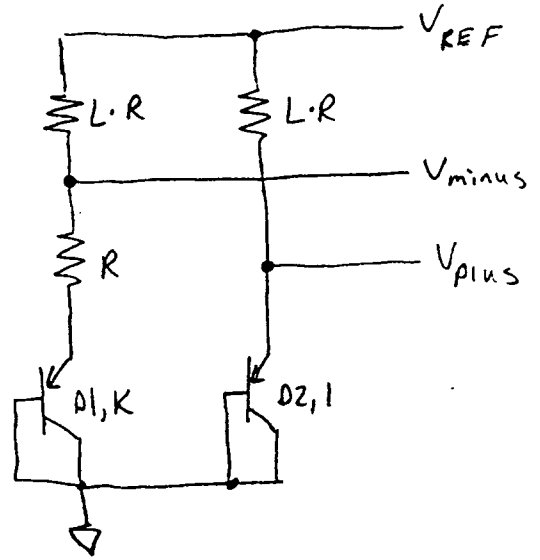- $K = 8$
- $L = 12$
- $R = 65 \text{ k}\Omega$



 The startup circuit should look similar to the following:



To design the start up circuit want to make V_{minus} large than V_{plus} . From the simulation results we can see that when V_{minus} is larger than $0.55V$ it will be larger than V_{plus} . V_{REF} must be larger than $1.2V$.

For designing the start up circuit, ideally we would like to make V_1 less than V_{minus} once the circuit is stable, but in this case $V_{\text{minus}} > .55V$ so it's impossible to make $V_1 < .55V$. For this case make $V_{G51} < V_{\text{THN}}$. Design M4 so $V_1 = 1.2V$.

$$1\mu A = \frac{50\mu A/V^2}{2} \frac{W_4}{L_4} (1.2 - .83)^2$$

$$\frac{W_4}{L_4} = .292$$

$$W_4 = 6\mu m$$

$$L_4 = 20\mu m$$

$$\text{Make } V_{S62} = V_{S63} = \frac{5 - 1.2}{2} = 1.9V$$

$$1\mu A = \frac{17\mu A/V^2}{2} \frac{W}{L} (1.9 - .91)^2$$

$$\frac{W}{L} = .12$$

$$W_2 = W_3 = 6\mu m$$


$$L_2 = L_3 = 50\mu m$$

Make M1 minimum size

$$W_1 = 3\mu m$$


$$L_2 = 2\mu m$$

```
* Problem 21.17
D1 1 0 PNPDIOD 8
D2 VPLUS 0 PNPDIOD
R1 VMINUS 1 65k
R2 2 VMINUS 780K
R3 2 VPLUS 780K
VREF 2 0 DC 0V
.DC VREF 0 2V 0.1V
.MODEL PNPDIOD D(is=1E-15 n=1)
.PROBE
.END
```

 

Problem 2.17 (Simulation)

Problem 21.18

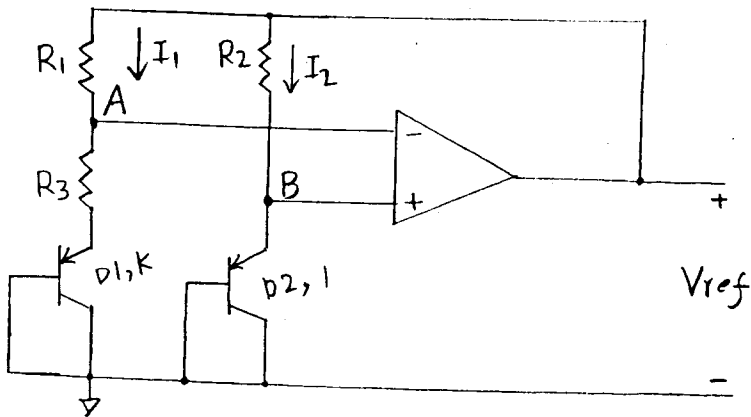

$$V_{ref} = I_2 R_2 + V_{d2} \quad (1)$$

$$\therefore V_A = V_B$$

$$\therefore I_1 R_1 = I_2 R_2 \implies \frac{I_1}{I_2} = \frac{R_2}{R_1} \quad (2)$$

$$\text{Also, } I_1 R_3 + V_{d1} = V_{d2}$$

$$\implies I_1 R_3 + nV_T \ln \frac{I_1}{I_S} = nV_T \ln \frac{I_2}{I_S}$$

$$\implies I_1 = \frac{1}{R_3} nV_T \ln \frac{I_2}{I_1} = \frac{1}{R_3} nV_T \ln \frac{R_1}{R_2} \quad (\text{inserting (2)}) \quad (3)$$

Plugging (3) into (1), we get

$$V_{ref} = I_2 R_2 + V_{d2} = I_1 R_1 + V_{d2} = \underline{\underline{\frac{R_1}{R_3} nV_T \ln \frac{R_1}{R_2} + V_{d2}}}$$

Problem 21.19

$$R = \frac{nV_T}{I_D} \ln k, \text{ where } k=8, n=1, V_T = 26\text{mV} @ 300\text{K}$$

$$\Rightarrow R = \frac{1 \times 26 \times 10^{-3} \text{ V}}{0.1 \text{ mA}} \ln 8 = 540\text{k}.$$

SPICE simulation is shown below:

*** Top Level Netlist ***

```
M1 3 3 0 0 CMOSNB L=5u W=5u
M10 12 5 9 4 cmospb L=5u W=70u
M2 2 3 7 0 CMOSNB L=5u W=40u
M3 1 1 3 0 CMOSNB L=5u W=15u
M4 5 1 2 0 CMOSNB L=5u W=15u
M5 1 5 8 4 cmospb L=5u W=70u
M6 5 5 6 4 cmospb L=5u W=70u
M7 8 6 4 4 cmospb L=5u W=70u
M8 6 6 4 4 cmospb L=5u W=70u
M9 9 6 4 4 cmospb L=5u W=70u
R1 0 7 540k
V_Iout 12 10 0V
VDD 4 0 DC 5 AC 0 0
Vout 10 0 DC 0 AC 0 0
```

***** Spice models and macro models *****

```
.MODEL CMOSNB NMOS LEVEL=4
```

```
.MODEL CMOSPb PMOS LEVEL=4
```

***** End of spice models and macro models *****

```
.probe
.DC Vout 0 5 .01
*.plot dc all
*.print dc all
.end
```

The SPICE simulation result is shown below:

