


23.1

$A_{ol} = 150k \pm 10\% \text{ v/v}$        $\beta = .1$

$$A_{cl} = \frac{A_{ol}}{1 + A_{ol}\beta} \Rightarrow \frac{dA_{cl}}{dA_{ol}} = \frac{-1}{(1 + A_{ol}\beta)^2} \Rightarrow \frac{dA_{cl}}{A_{cl}} = \frac{-dA_{ol}}{(1 + A_{ol}\beta)^2} \cdot \frac{(1 + A_{ol}\beta)}{A_{ol}}$$

$$\frac{dA_{cl}}{A_{cl}} = \frac{-dA_{ol}}{A_{ol}} \cdot \frac{1}{1 + A_{ol}\beta} \Rightarrow \% \text{ tolerance } A_{cl} = (-) \% \text{ tolerance } A_{ol} \left( \frac{1}{1 + A_{ol}\beta} \right)$$
$$= + (.1) \left( \frac{1}{1 + (.1)(150k)} \right)$$
$$= + .00067\%$$


23.2 non-inverting op-amp:

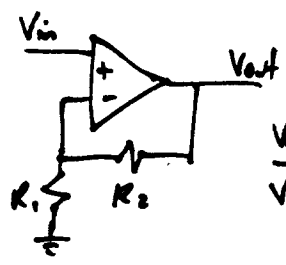

$$\frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_1} = \frac{1}{\beta} \left\{ \text{ideal op-amp} \Rightarrow A_{ol} = \infty \right\}$$

$\Rightarrow \beta = \frac{R_1}{R_1 + R_2} \Rightarrow \text{max is } 1 \text{ if } R_2 = \text{very small (zero)}$   
and  $R_1 = \text{very large (open)}$

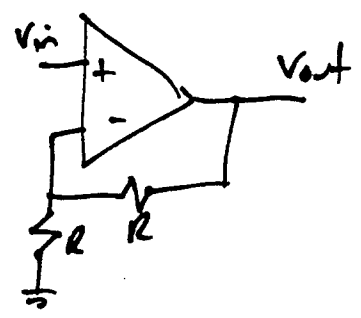for  $\beta = \frac{1}{2} = \frac{R_1}{R_1 + R_2} \Rightarrow R_1 = R_2 = R$



23.3 a)  $v_o = v_i A_1 A_2 + v_n A_2$  ①

$$v_i = v_s - v_f$$
 ②

$$v_f = \beta v_o$$
 ③

③ into ②:  $v_i = v_s - \beta v_o$  ④

④ into ①:  $v_o = A_1 A_2 (v_s - \beta v_o) + A_2 v_n$

$$v_o = A_1 A_2 v_s - A_1 A_2 \beta v_o + A_2 v_n$$


$$\Rightarrow v_o = \frac{A_1 A_2 v_s + A_2 v_n}{1 + A_1 A_2 \beta} = \boxed{\frac{A_1 A_2 v_s}{1 + A_1 A_2 \beta} + \frac{A_2 v_n}{1 + A_1 A_2 \beta}}$$

b) if  $\beta = 0 \Rightarrow \underline{v_o = A_1 A_2 v_s + A_2 v_n}$

c) if  $A_1 = A_2 = 200$ , what  $\beta$  value is required to reduce  $v_n$  by  $1/2$  as compared to  $\beta = 0$ ?

$$\frac{A_2 v_n}{1 + A_1 A_2 \beta} = \frac{A_2 v_n}{2} \Rightarrow 1 + (200)^2 \beta = 2 \Rightarrow \beta = \frac{2-1}{(200)^2} = \underline{\underline{25 \times 10^{-6}}}$$

23.4

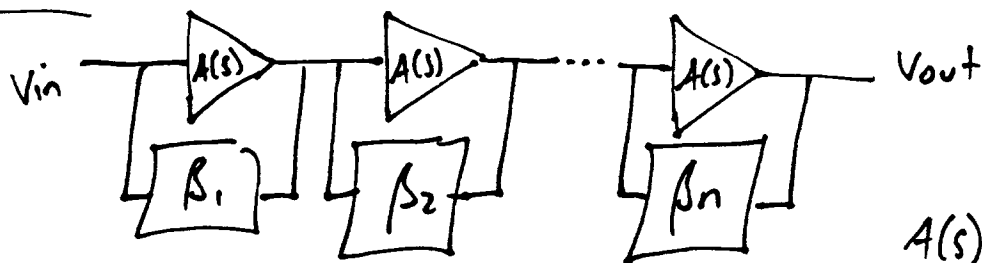

$$A(s) = \frac{1 \text{ MEG}}{s + 100}$$

1<sup>st</sup> stage provides desired pole and want  $\frac{V_{out}}{V_{in}} = \frac{1000}{\left(\frac{s}{100,000} + 1\right)\left(\frac{s}{400,000} + 1\right)^{n-1}}$

$$1^{\text{st}} \text{ stage: } \frac{1 \text{ MEG}}{s + 100 + \underbrace{1 \text{ MEG} \cdot \beta_1}_{100,000}} = \frac{A(s)}{1 + A(s)\beta_1} = \frac{10}{\left(\frac{s}{100,000} + 1\right)}$$

$\Rightarrow$  other stages have identical  $\beta$ 's, giving pole  $\bullet \omega = 400,000 \text{ rad/s}$

$$\Rightarrow \frac{1 \text{ MEG}}{s + 100 + 1 \text{ MEG} \cdot \beta} = \frac{1 \text{ MEG}}{400,000} \cdot \frac{1}{\frac{s}{400,000} + 1} = \frac{2.5}{\left(\frac{s}{400 \text{ K}} + 1\right)}$$

$$\Rightarrow \frac{1000}{\left(\frac{s}{100,000} + 1\right)\left(\frac{s}{400,000} + 1\right)^{n-1}} = \frac{10 \cdot 2.5^n}{\left(\frac{s}{100,000} + 1\right)\left(\frac{s}{400,000} + 1\right)^{n-1}}$$

$$\Rightarrow 2.5^{n-1} = \frac{1000}{10} \Rightarrow n-1 = \frac{\log(100)}{\log(2.5)} \approx 5$$

$$\Rightarrow \underline{\underline{n = 6}}$$

23.5

$$A_{OLL}(s) = 1,000 \frac{s}{s+100} \text{ v/v}$$

$$A_{CLL}(s) = \frac{A_{OLL}(s)}{1 + A_{OLL}(s)\beta} = \frac{1,000 \frac{s}{s+100}}{1 + 1,000 \frac{s}{s+100} \beta} = \frac{1,000 s}{s+100 + 1,000s\beta}$$

$$= \frac{1,000 s}{s(1+1,000\beta) + 100} = \left( \frac{1,000}{1+1,000\beta} \right) \left( \frac{s}{s + \frac{100}{1+1,000\beta}} \right)$$

and want in form:  $A_{CLL}(\text{midband}) \left( \frac{s}{s + \omega_{LCL}} \right) = A_{CLL}(\text{mid}) \left( \frac{s}{s + 50} \right)$

$$\Rightarrow \frac{100}{1+1,000\beta} = 50 \Rightarrow 1,000\beta + 1 = 2 \Rightarrow \underline{\underline{\beta = .001}}$$


and  $A_{CLL}(\text{mid}) = \frac{1,000}{1+(1,000)(.001)} = 500 \text{ v/v}$

23.6

fb topology	i/p var	o/p var	AOL units	$\beta$ units	$R_{fi}$ method	$R_{fo}$ method	$A_{CL}$	$R_{if}$	$R_{of}$
Series-Shunt	Volts	Volts	v/v	v/v	Short o/p to gnd $R_{fi}$ = input into $\beta$ network	"out-of-socket" input device	$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta}$	$R_{if} = R_i (1 + A_{OL}\beta)$	$R_{of} = \frac{R_o}{1 + A_{OL}\beta}$
Series-Series	Volts	Amps	A/v	v/A	"out-of-socket" v/v device	"out-of-socket" i/p device	$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta}$	$R_{if} = R_i (1 + A_{OL}\beta)$	<del><math>R_{of} = \frac{R_o}{1 + A_{OL}\beta}</math></del> $R_{of} = R_o (1 + A_{OL}\beta)$
Shunt-Shunt	Amps	Volts	v/A	A/v	Short o/p to gnd	Short i/p to gnd	$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta}$	$R_{if} = \frac{R_i}{1 + A_{OL}\beta}$	$R_{of} = \frac{R_o}{1 + A_{OL}\beta}$
Shunt-Series	Amps	Amps	A/A	A/A	"out-of-socket" v/p device	Short i/p to gnd	$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta}$	$R_{if} = \frac{R_i}{1 + A_{OL}\beta}$	$R_{of} = R_o (1 + A_{OL}\beta)$

23.7

a) Series-Shunt

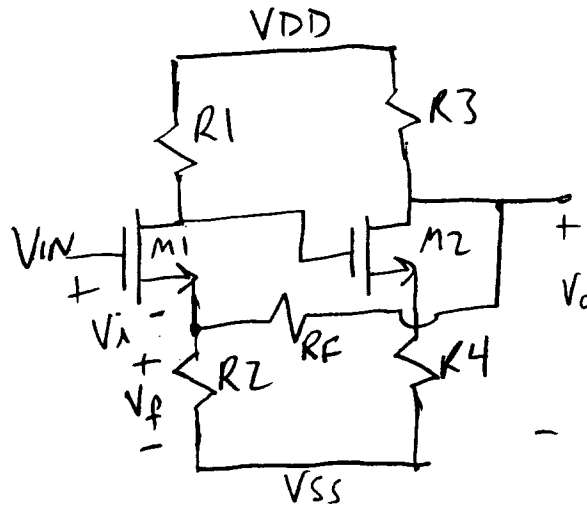


Fwd Path  $M1 \text{ gate} \rightarrow M1 \text{ drain} / M2 \text{ gate} \rightarrow M2 \text{ drain}$

Fb Path  $M2 \text{ drain} \rightarrow M1 \text{ source via } R_F$

$\Rightarrow$  2 inversions for (-) fb w/ Series mixing

b) Series-Series

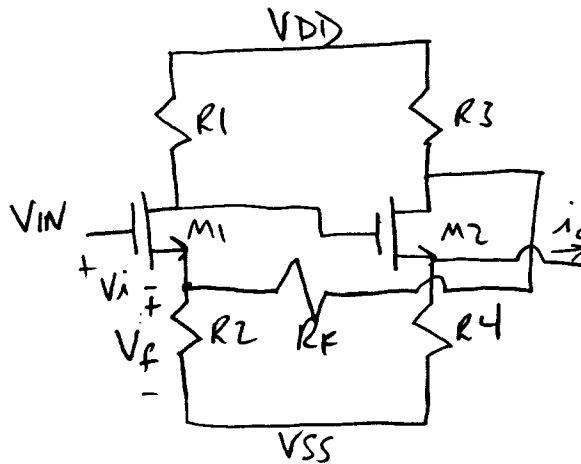


Fwd Path  $M1 \text{ gate} \rightarrow M1 \text{ drain} / M2 \text{ gate} \rightarrow M2 \text{ source}$

Fb Path  $M2 \text{ drain} \rightarrow M1 \text{ source via } R_F$

$\Rightarrow$  2 inversions for (-) fb w/ Series mixing

23.7

c) Shunt-shunt

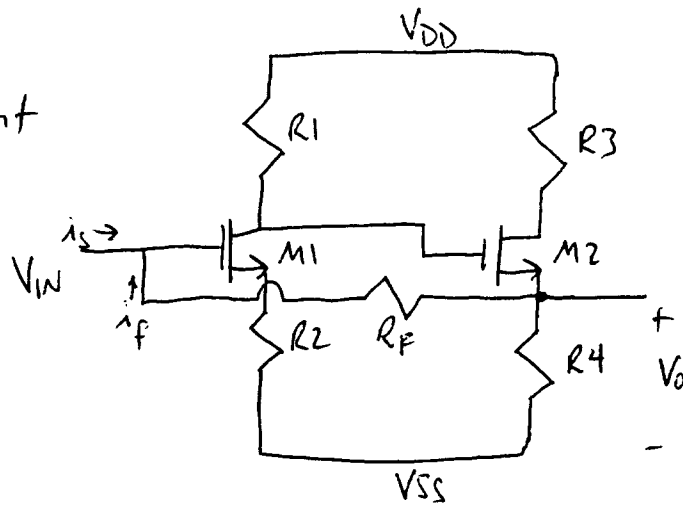


Fwd Path M1 gate  $\rightarrow$  M1 drain / M2 gate  $\rightarrow$  M2 source

Fb Path M2 source  $\rightarrow$  M1 gate via  $R_f$

$\Rightarrow$  1 inversion for (-)  $f_b$  w/ shunt mixing

23.7 d) Shunt-series

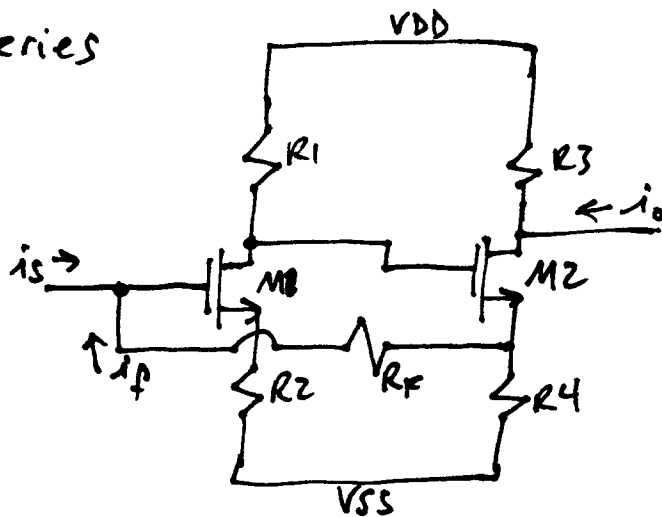


Fwd Path M1 gate  $\rightarrow$  drain  
M2 gate  $\rightarrow$  drain

Fb Path M2 source  $\rightarrow$  M1 gate via  $R_f$

$\Rightarrow$  1 inversion for (-)  $f_b$  w/ shunt mixing

23.8

a) Series-Shunt

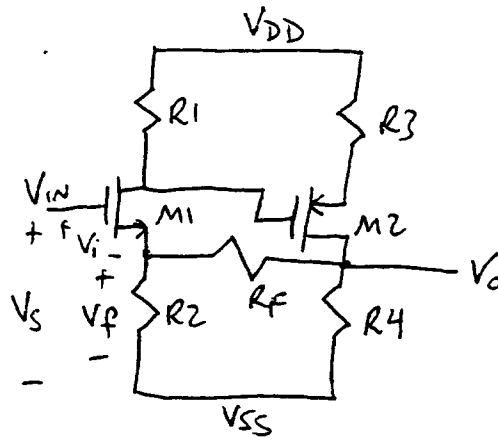


Fwd Path  $M1 \text{ gate} \rightarrow M1 \text{ drain} / M2 \text{ gate} \rightarrow M2 \text{ drain}$

Fb Path  $M2 \text{ drain} \rightarrow M1 \text{ source via } R_f$

$\Rightarrow$  2 inversions for (-) fb w/ series mixing

23.8

b) Series - Series

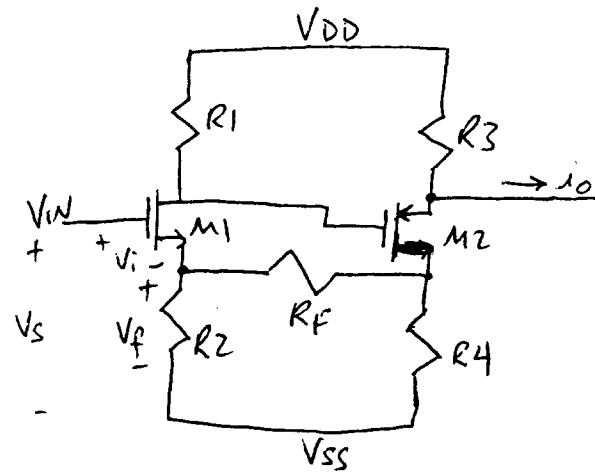


Fwd Path M1 gate  $\rightarrow$  M1 drain / M2 gate  $\rightarrow$  M2 drain

Fb Path M2 drain  $\rightarrow$  M1 source via RF

$\Rightarrow$  2 inversions for (-) fb w/ series mixing

c) Shunt - Shunt

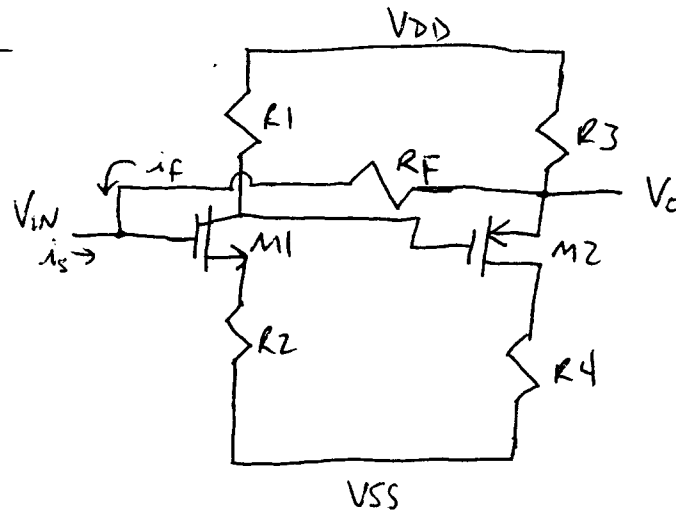


Fwd Path M1 gate  $\rightarrow$  M1 drain  $\rightarrow$  M2 source

Fb Path M2 source  $\rightarrow$  M1 gate via RF

$\Rightarrow$  1 inversion for (-) fb w/ shunt mixing

23.8 d) Shunt-Series

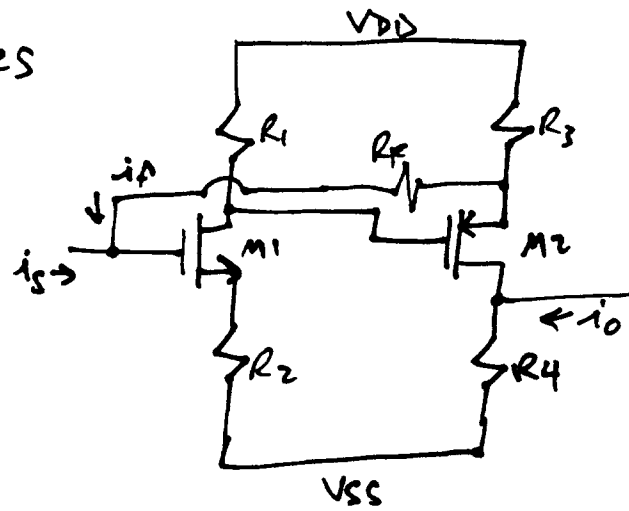


Fwd Path M1 gate  $\rightarrow$  drain, M2 gate  $\rightarrow$  drain

Fb Path M2 source  $\rightarrow$  M1 gate via  $R_f$

1 inversion for (-) fb w/ shunt mixing

23.9

a) Series - Shunt

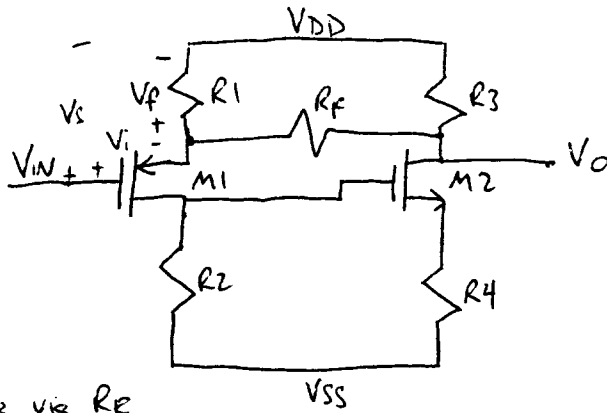


FWD Path M1 gate  $\rightarrow$  M1 drain  $\rightarrow$  M2 drain

Fb Path M2 drain  $\rightarrow$  M1 source via  $R_f$

$\Rightarrow$  2 inversions for (-) fb w/ Series mixing

b) Series - Series

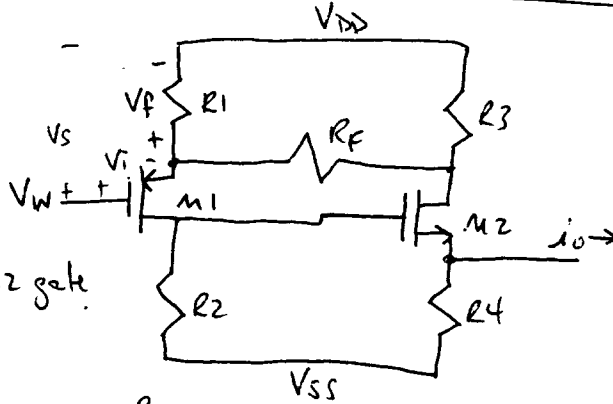


FWD Path M1 gate  $\rightarrow$  M1 drain/M2 gate  $\rightarrow$  M2 source

Fb Path M2 drain  $\rightarrow$  M1 source via  $R_f$

$\Rightarrow$  2 inversions for (-) fb w/ series mixing

c) Shunt - Shunt

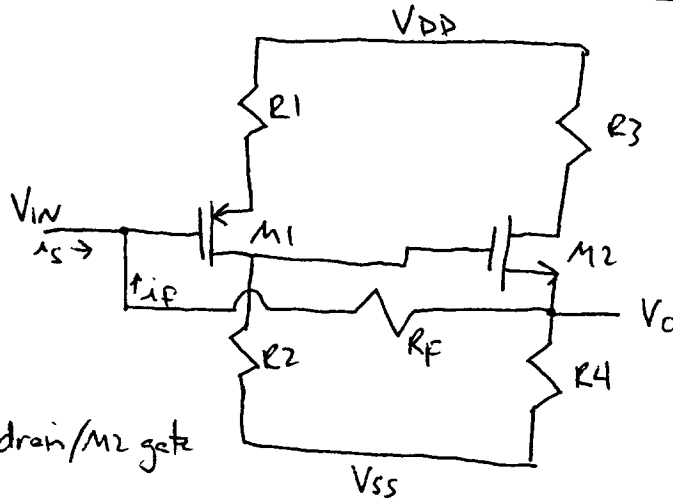


FWD Path M1 gate  $\rightarrow$  M1 drain/M2 gate  $\rightarrow$  M2 source

Fb Path M2 source  $\rightarrow$  M1 gate via  $R_f$

$\Rightarrow$  1 inversion for (-) fb w/ shunt mixing

23.9 d) Shunt-Series

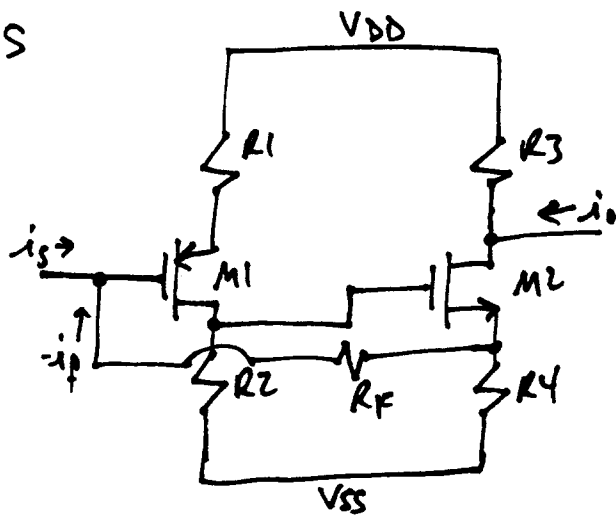

Fwd Path

M1 gate - drain  
M2 gate - drain


Fb Path

M2 source  $\rightarrow$  M1 gate via  $R_f$

1 inversion for (-)  $A_b$  w/ shunt mixing

23.10

a) Series-~~Series~~<sup>Shunt</sup>

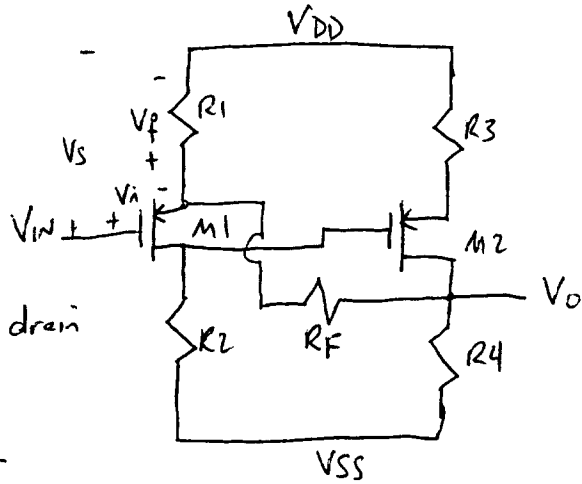

Fwd Path


M1 gate  $\rightarrow$  M1 drain / M2 gate  $\rightarrow$  M2 drain

Fb Path

M2 drain  $\rightarrow$  M1 source via  $R_F$

$\Rightarrow$  2 inversions for (-) fb w/ series mixing

b) Series-series

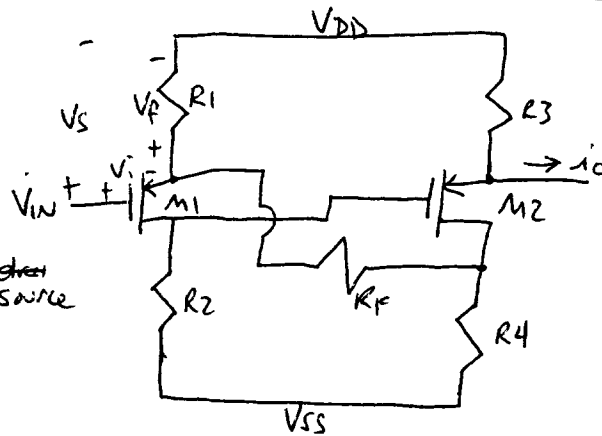

Fwd Path


M1 gate  $\rightarrow$  M1 drain / M2 gate  $\rightarrow$  M2 ~~drain~~ source

Fb Path

M2 drain  $\rightarrow$  M1 source via  $R_F$

$\Rightarrow$  2 inversions for (-) fb w/ series mixing

c) Shunt-shunt

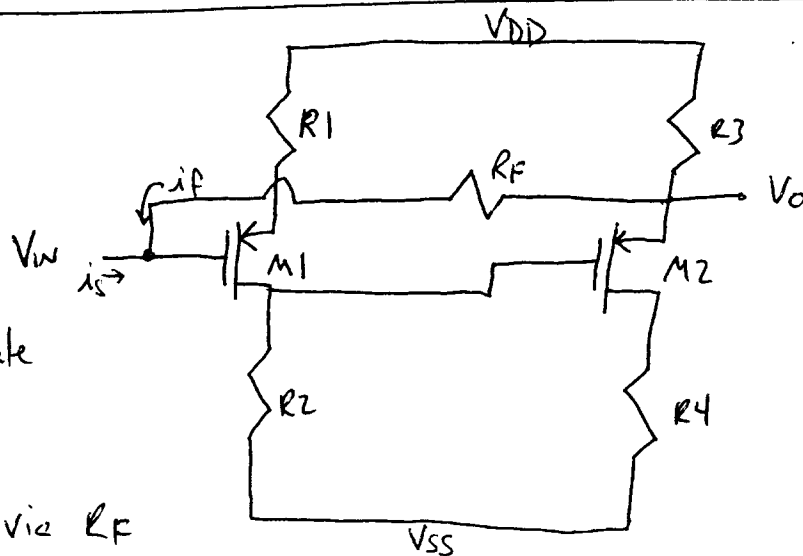

Fwd Path


M1 gate  $\rightarrow$  M1 drain / M2 gate  $\rightarrow$  M2 source

Fb Path

M2 source  $\rightarrow$  M1 drain via  $R_F$

$\Rightarrow$  1 inversion for (-) fb w/ shunt mixing

23.10 d) Shunt-series

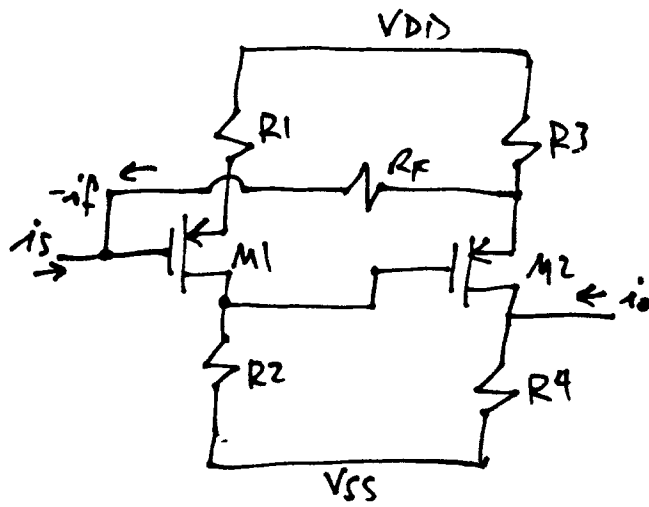

Fwd Path


M1 gate-drain  
M2 gate-drain

Fb Path

M2 source  $\rightarrow$  M1 gate via  $R_f$

1 inversion for  $(-)$   $A_3$  w/ shunt mixing

23.11

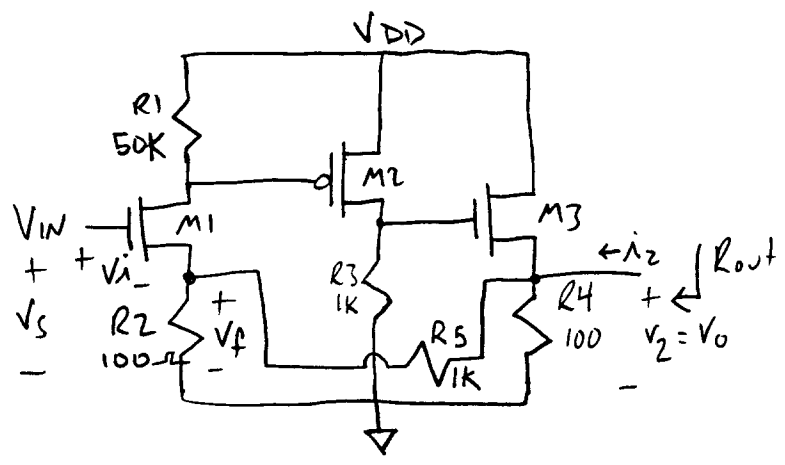


a) Series-Shunt since both input variables ( $V_i, V_f$ ) and output variable ( $V_o$ ) are voltages.

b) negative feedback since 2 inversions and series mixing

M1 gate  $\rightarrow$  M1 drain = inv. #1  
 M2 gate  $\rightarrow$  M2 drain = inv. #2  
 M3 gate  $\rightarrow$  M3 source = no inversion

c) closed-loop small signal model:

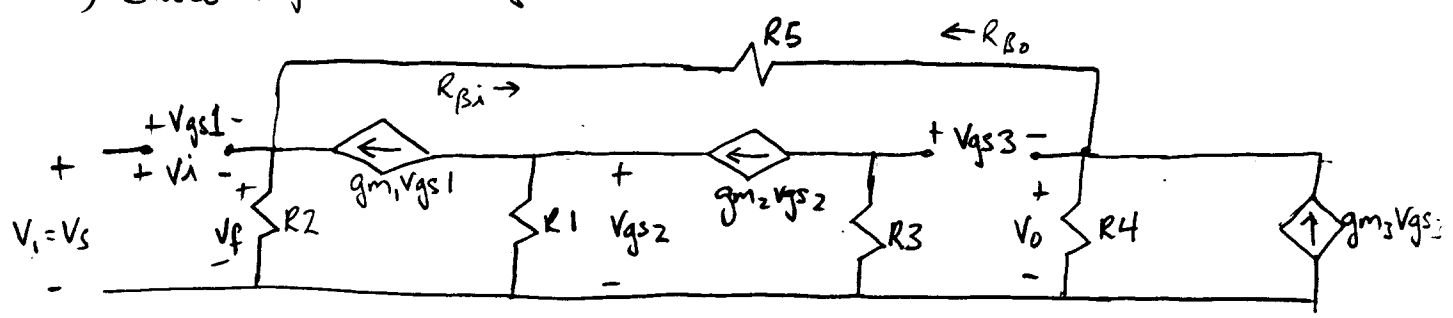


d)  $R_{Bi} = R_5$

$R_{Bo} = R_5 + R_2$

23.12

a) Small signal open loop model:

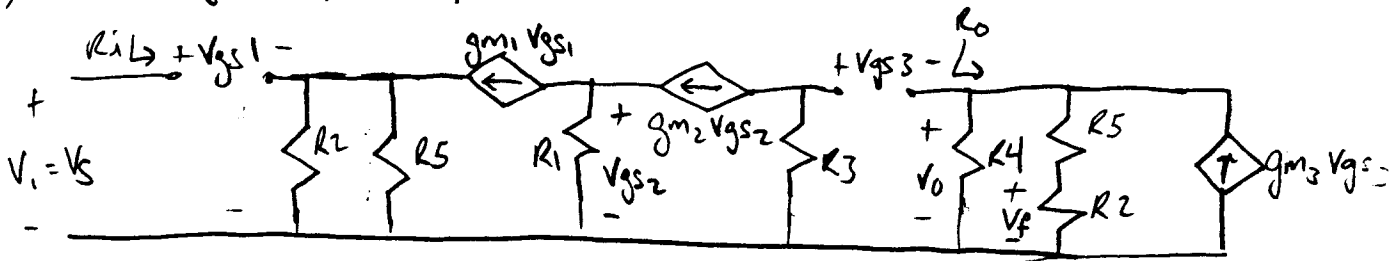

$$b) A_{OL} = \frac{V_o}{V_s} = \left( \frac{g_{m1} R_1}{g_{m1} (R_2 \parallel R_5)} \right) \left( g_{m2} R_3 \right) \left( \frac{g_{m3} R_4 \parallel (R_2 + R_5)}{g_{m3} R_4 \parallel (R_2 + R_5) + 1} \right)$$

$$\beta = \frac{V_f}{V_o} = \frac{R_2}{R_2 + R_5}$$


$$R_i = \infty$$

$$R_o = R_4 \parallel (R_5 + R_2)$$


$$c) A_{CL} = \frac{A_{OL}}{1 + A_{OL} \beta}$$

$$R_{out} = \frac{R_o}{1 + A_{OL} \beta}$$

23.13 a)

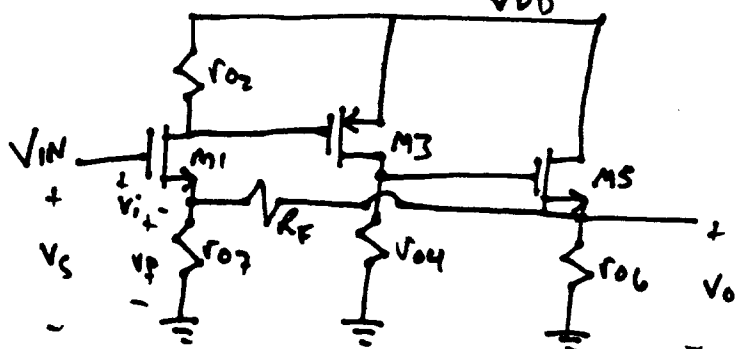


2 Inversions  $\Rightarrow (-)fb !!$

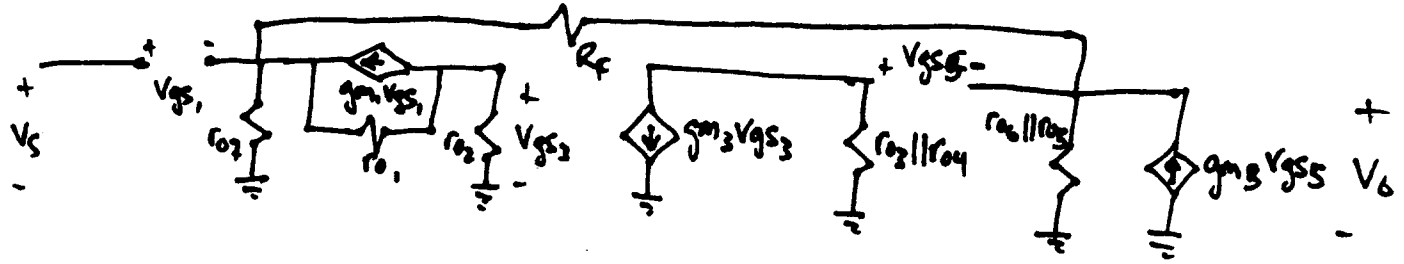

b)  $R_{\beta i} = R_F = 10k\Omega$   
 $R_{\beta o} = R_F + r_{07} = 80k\Omega$

23.14

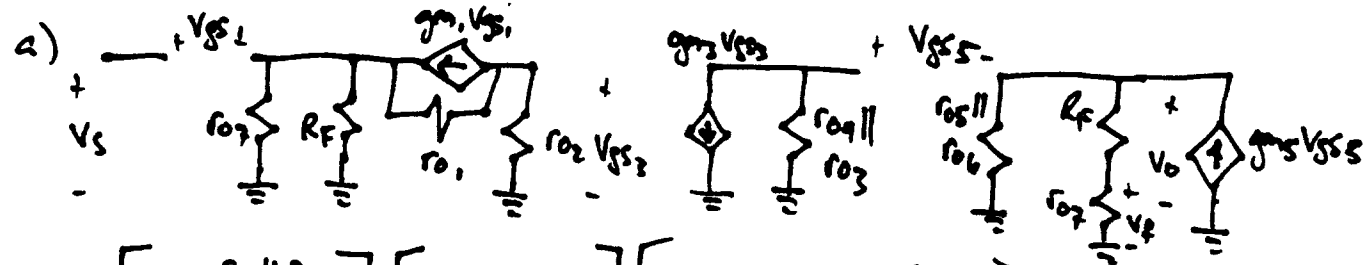

$$A_{ol} = \frac{V_o}{V_s} = \left[ \frac{g_{m1} r_{01} \parallel r_{02}}{g_{m1} r_{07} \parallel R_F + 1} \right] \left[ g_{m3} r_{04} \parallel r_{03} \right] \left[ \frac{g_{m5} r_{05} \parallel r_{06} \parallel R_F + r_{07}}{g_{m5} r_{05} \parallel r_{06} \parallel R_F + r_{07} + 1} \right] = 3.89k \text{ V/V}$$

$\approx 1$

$$\beta = \frac{V_F}{V_o} = \frac{r_{07}}{r_{07} + R_F} = .875 \text{ V/V}$$

$$R_i = \infty \quad R_o = r_{05} \parallel r_{06} \parallel (R_F + r_{07}) = 29.17k \parallel 80k = 21.38k\Omega$$

b)  $A_{cl} = \frac{A_{ol}}{1 + A_{ol}\beta} = 1.14 \text{ V/V}$

$$R_{out} = \frac{R_o}{1 + A_{cl}\beta} = 6.28\Omega$$

23.15

$$A_{ol} = \left[ \frac{g_{m1} r_{o1} \parallel r_{o2}}{g_{m1} r_{o1} \parallel r_{o2} + 1} \right] \left[ \frac{g_{m3} r_{o4}}{g_{m3} r_{o4} + 1} \right] \left[ g_{m5} \left( \frac{1}{g_{m6}} \parallel r_{o6} \parallel r_{o3} \parallel (r_F + r_{L1}) \right) \right]$$


$$A_{ol} \approx \left[ \frac{g_{m1} r_{o1} \parallel r_{o2}}{g_{m1} r_{o1} \parallel r_{o2} + 1} \right] \left[ g_{m5} \left( \frac{1}{g_{m6}} \parallel (r_F + r_{L1}) \right) \right] = 82.34 \text{ V/V}$$

$$\beta = \frac{v_F}{v_2} = \frac{r_{L1}}{r_{L1} + r_{L2}} = .5 \quad \Rightarrow \quad A_{cl} = \frac{v_2}{v_{in}} = \frac{A_{ol}}{1 + A_{ol}\beta} = 1.952 \text{ V/V}$$

$$R_{out} = \frac{v_2}{i_2} = \frac{r_{o6}}{1 + A_{ol}\beta} \approx \frac{\frac{1}{g_{m6}} \parallel (r_F + r_{L1})}{1 + A_{ol}\beta} = .586 \Omega = \frac{V}{A}$$


23.16

a)

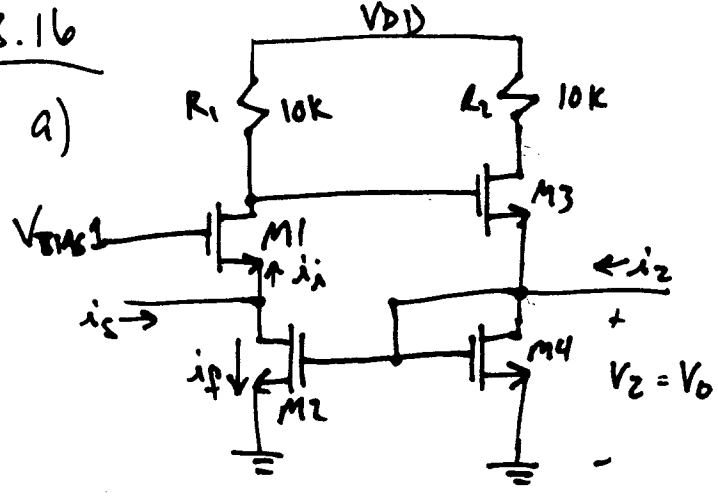

Shunt-shunt

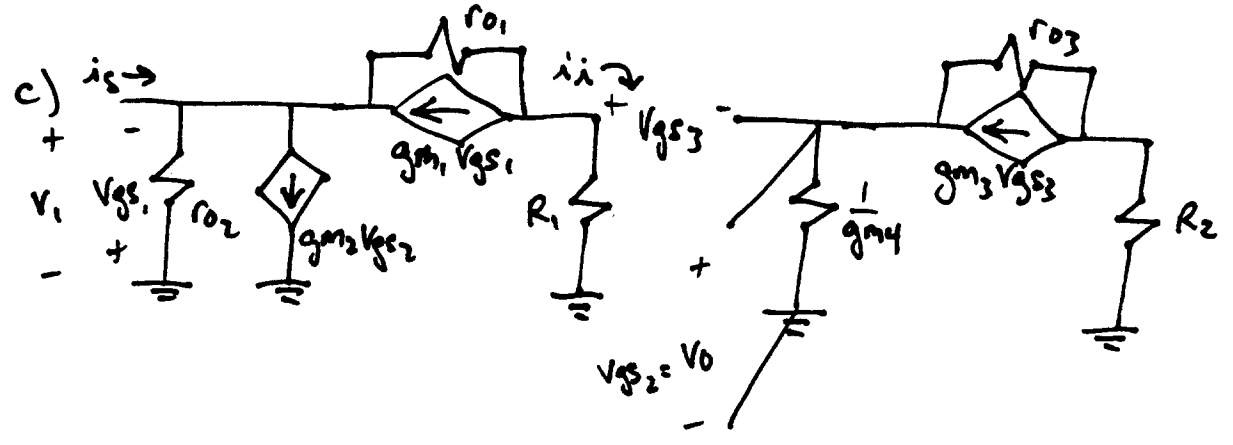
b) 1 inversions  $\Rightarrow$  (-)  $A_b$  w/ shunt mixing



d)  $R_{po} = \infty = R_{in4} \parallel R_{in2}$

$R_{pi} = r_{o2} = 70 \text{ k}\Omega$

23.17

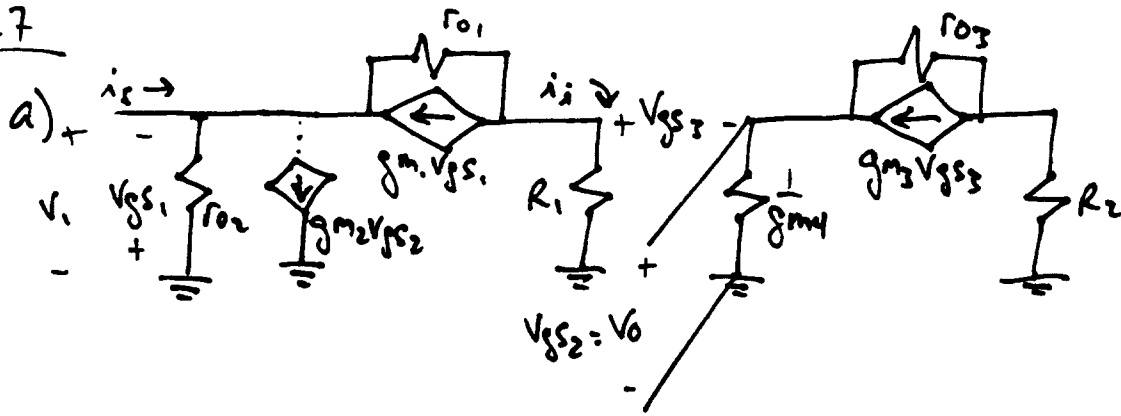

$$b) \frac{V_o}{V_i} = [C_6][C_D] = \left[ \frac{R_1}{r_{o2}} \right] \cdot \left[ \frac{g_{m3} \cdot \frac{1}{g_{m4}}}{g_{m3} \cdot \frac{1}{g_{m4}} + 1} \right] = \left[ \frac{1}{7} \right] \cdot \left[ \frac{1}{2} \right] = \frac{1}{14} = .0714 \text{ V/V}$$

$$R_i = r_{o2} \parallel R_{in1} = r_{o2} \parallel \left( \frac{1 + \frac{R_1}{r_{o1}}}{\frac{1}{r_{o1}} + g_{m1}} \right) \approx \frac{1 + \frac{1}{2}}{\frac{1}{70\Omega} + 0.06} = 19.04 \Omega = R_i$$

$$A_{oL} = \frac{V_o}{I_s} = \frac{V_o}{V_i} \cdot R_i = \left( \frac{1}{14} \right) (19.04) = 1.36 \text{ V/A} = A_{oL}$$

$$\beta = \frac{i_f}{V_o} = \frac{g_{m2} V_{gs2}}{V_{gs2}} = g_{m2} = 0.06 \text{ A/V} = \beta$$


$$R_o = \frac{1}{g_{m4}} \parallel R_{in2} = \frac{1}{g_{m4}} \parallel \left( \frac{1 + \frac{R_2}{r_{o3}}}{\frac{1}{r_{o2}} + g_{m3}} \right) = 16.67 \parallel 19.04 = 8.9 \Omega = R_o$$

$$c) A_{cL} = \frac{A_{oL}}{1 + A_{oL}\beta} = \frac{1.36 \text{ A/V}}{1 + 1.36(0.06)} = 1.26 \text{ A/V} = A_{cL}$$

$$R_{out} = \frac{R_o}{1 + A_{cL}\beta} = \frac{8.9}{1 + 1.36(0.06)} = 8.23 \Omega = R_{out}$$

$$R_{in} = \frac{R_i}{1 + A_{cL}\beta} = \frac{19.04}{1 + 1.36(0.06)} = 17.6 \Omega = R_{in}$$

23.18

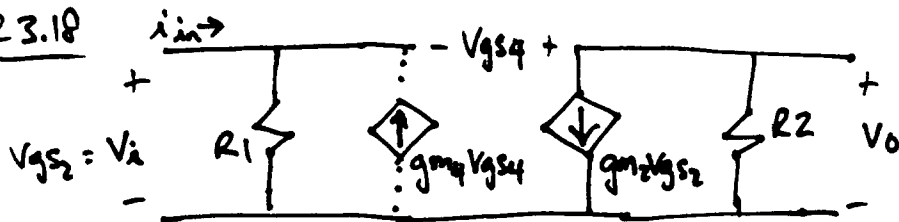

(open loop model)

$$R_1 = \frac{1}{g_{m1}} \parallel r_{o1} \parallel r_{o4}$$

$$\approx \frac{1}{g_{m1}} = 16.67 \Omega$$

$$R_2 = \frac{1}{g_{m2}} \parallel r_{o3} \parallel r_{o2}$$

$$\approx \frac{1}{g_{m2}} = 25 \Omega$$

$$A_{oc} = \frac{v_o}{v_i} \cdot R_1 = \frac{v_o}{i_{in}} = -g_{m2} \cdot R_2 \cdot R_1 = -25 \frac{V}{A}$$


$$\beta = \frac{i_A}{v_o} \approx \frac{-g_{m4}}{1 + g_{m4} R_1} = -0.03 A/V \Rightarrow A_{cl} = \frac{v_2}{i_1} = \frac{A_{oc}}{1 + A_{oc} \beta} = \boxed{-14.3 \frac{V}{A} = \frac{v_2}{i_1}}$$

$$R_{i1} = \frac{1}{g_{m1}} = 16.67 \Omega, \quad R_{in} = \frac{v_1}{i_1} = \frac{R_{i1}}{1 + A_{oc} \beta} = \boxed{9.5 \Omega = \frac{v_1}{i_1}}$$

$$R_o = \frac{1}{g_{m2}} = 25 \Omega, \quad R_{out} = \frac{v_2}{i_2} = \frac{R_o}{1 + A_{oc} \beta} = \boxed{14.3 \Omega = \frac{v_2}{i_2}}$$


$$\frac{v_2}{v_1} = \frac{v_2}{i_1} \cdot \frac{i_1}{v_1} = A_{cl} \cdot \frac{1}{R_{in}} = \boxed{-1.5 \frac{V}{V} = \frac{v_2}{v_1}}$$

23.19

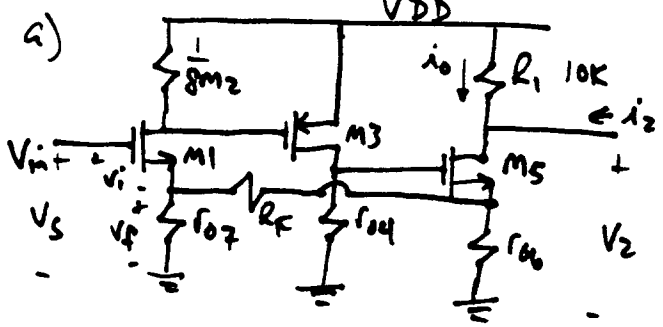


Series-Series

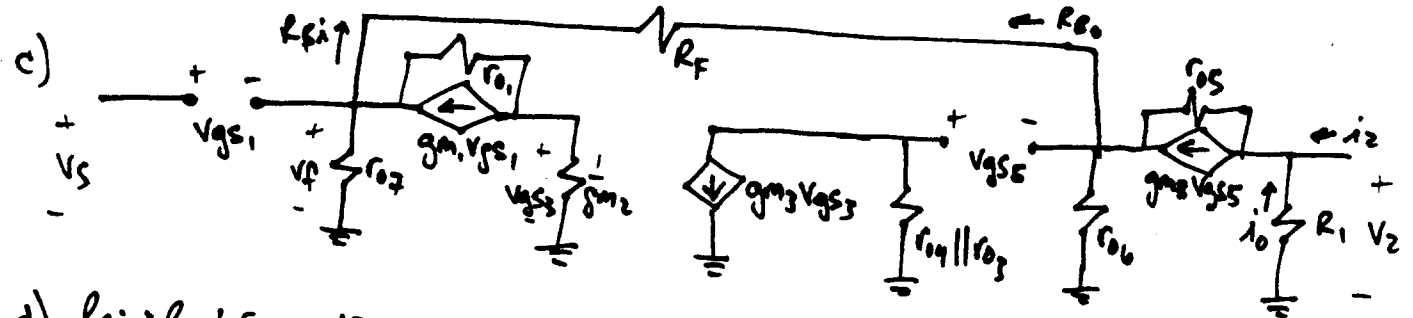b) 2 inversions  $\Rightarrow$  (-) fb w/ Series mixing



d)  $R_{pi} = R_F + r_{o6} = 120k\Omega$   
 $R_{po} = R_F + r_{o7} = 120k\Omega$

23.20

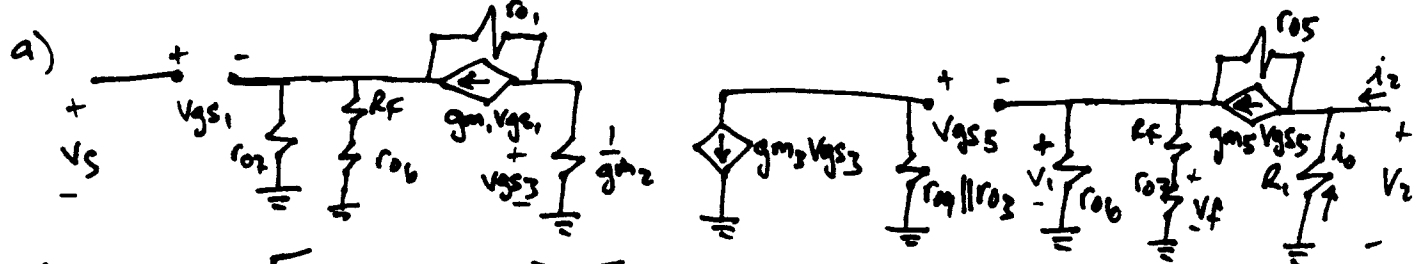

b)  $A_{ol} = \frac{i_o}{V_S} = \frac{V_2}{V_S} \cdot \frac{1}{R_1} = \left[ \frac{g_{m1} (r_{o1} \parallel \frac{1}{g_{m2}})}{g_{m1} (r_{o7} \parallel (R_F + r_{o6})) + 1} \right] \left[ g_{m3} r_{o3} \parallel r_{o4} \right] \left[ \frac{g_{m5}}{g_{m5} (r_{o6} \parallel R_F + r_{o7}) + 1} \right] = 14.924 \times 10^{-6} A/V$

$\beta = \frac{V_F}{i_o} = \left( \frac{r_{o7}}{r_{o7} + R_F} \right) \left( \frac{r_{o6} (r_{o7} + R_F)}{r_{o6} + r_{o7} + R_F} \right) = \frac{r_{o7} r_{o6}}{r_{o6} + r_{o7} + R_F} = 25.789 K \frac{V}{A}$


$R_i = \infty$        $R_o = R_1 + (r_{o6} \parallel R_F + r_{o7}) \left( \frac{r_{o5}}{r_{o5} + g_{m5} r_{o6}} \right) (1 + g_{m5} r_{o6} \parallel R_F + r_{o7}) = 186 MEG \Omega$

c)  $A_{cl} = \frac{A_{ol}}{1 + A_{ol} \beta} = 10.776 \times 10^{-6} A/V$

$R_{in} = \infty$

$R_{out} = R_1 \parallel (R_o - R_i) = 10K \parallel (186MEG - 10K) \approx R_1 = 10K$

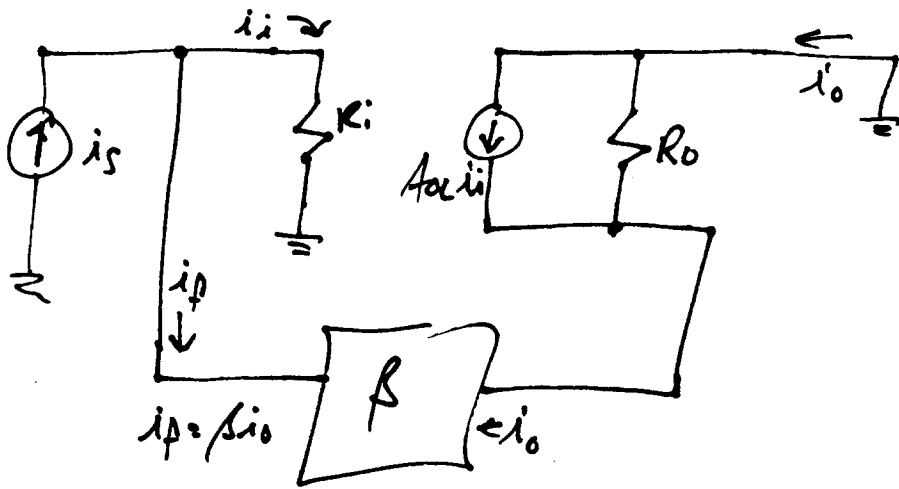23.21 Find expressions for  $A_{cc}$ ,  $R_{in}$ , and  $R_{out}$




$$A_{cc} = \frac{i_o}{i_s} = \frac{i_o}{i_i + i_p} = \frac{i_o}{i_i + \beta i_o} = \frac{i_i \cdot A_{oc}}{i_i (1 + \frac{i_o}{i_i} \beta)} \quad \left\{ \text{assuming } R_o = \infty \right\}$$

$$\Rightarrow A_{cc} = \frac{A_{oc}}{1 + A_{oc} \beta}$$

$$i_s = i_i + i_p = \frac{V_s}{R_i} + \beta i_o = \frac{V_s}{R_i} + \beta A_{oc} i_i \quad \left\{ \text{again, if } R_o = \infty \right\}$$
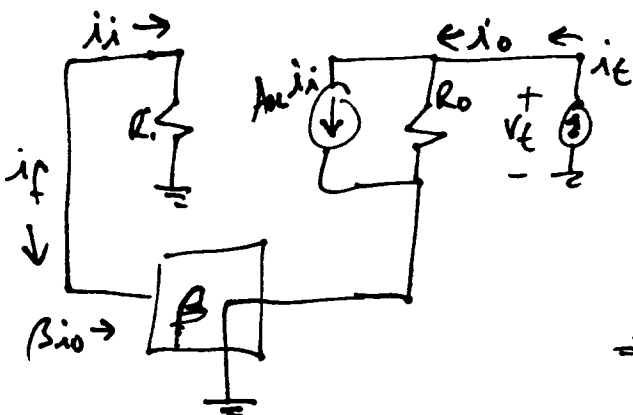
$$i_s = \frac{V_s}{R_i} (1 + A_{oc} \beta) \Rightarrow R_{in} = \frac{V_s}{i_s} = \frac{R_i}{1 + A_{oc} \beta}$$




$$i_o = A_{oc} i_i + \frac{V_t}{R_o} = A_{oc} i_p + \frac{V_t}{R_o} = -A_{oc} \beta i_o + \frac{V_t}{R_o}$$

$$\Rightarrow i_o (1 + A_{oc} \beta) = \frac{V_t}{R_o}$$


$$\Rightarrow \frac{V_t}{i_o} = R_{out} = R_o (1 + A_{oc} \beta)$$

23.22

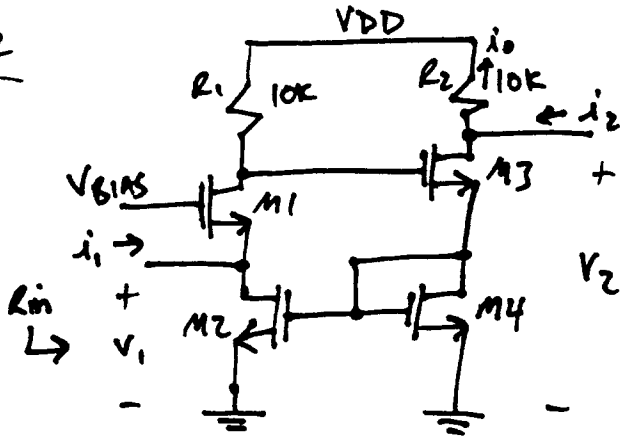

a) Shunt - series

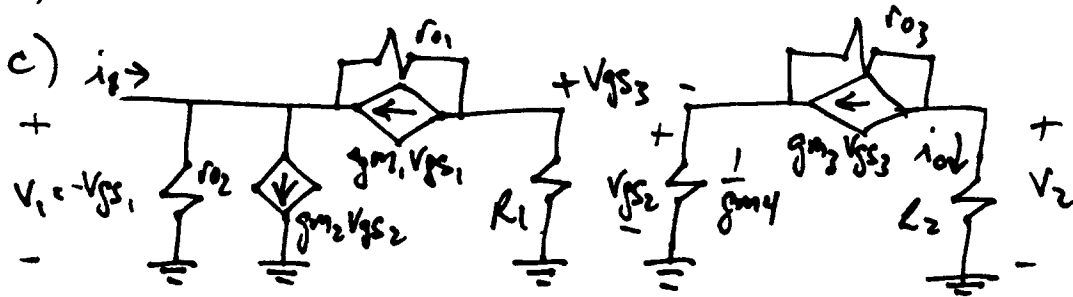
b)  $\neq$  inversion  $\Rightarrow (-)$  fb w/ shunt mixing



d)  $R_{fi} = r_{02} = 70k$

$R_{fo} = \infty$

23.23

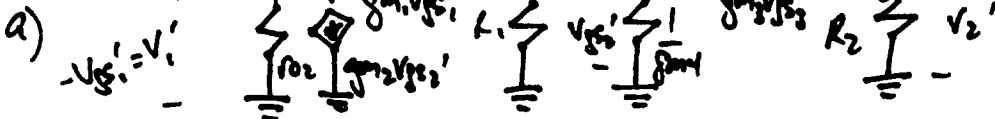

a)  $-v_{gs1}' = v_i'$

b)  $\beta = \frac{i_f}{i_o} = \frac{g_{m2} v_{gs2}'}{-v_{gs1}' \cdot (\frac{1}{g_{m4}})^{-1}} = \frac{-g_{m2}}{g_{m4}} = \boxed{-1 \text{ A/A} = \beta}$

~~$R_i = r_{02} = 70k \parallel R_1$~~   $R_i = R_{inD2} \parallel R_{inS1} = 19.04 \Omega = R_i$



$R_o = R_2 + R_{inD3} = R_2 + \frac{1}{g_{m4}} + r_{03} (1 + g_{m3}/g_{m4}) \approx R_2 + 2 \cdot r_{03} = 150k = R_o$

$A_{oL} = \frac{i_o'}{i_s'} = \frac{v_o'}{v_s'} \cdot \frac{R_i}{R_2} = (CG)(GS) \frac{R_i}{R_2} = \left(\frac{R_1}{r_{02}}\right) \left(\frac{-g_{m3} R_2 \parallel r_{03}}{g_{m3}/g_{m4} + 1}\right) \left(\frac{R_i}{R_2}\right) = \boxed{-0.0714 \text{ A/A} = A_{oL}}$

c)  $A_{cl} = \frac{A_{oL}}{1 + A_{oL}\beta} = \boxed{.06664 \text{ A/V} = A_{cl}}$

$R_{in} = \frac{R_i}{1 + A_{cl}\beta} = \boxed{18.7 \Omega = R_{in}}$        $R_{out} = R_2 \parallel [R_o(1 + A_{cl}\beta) - R_2] \approx R_2 = \boxed{10k \Omega = R_{out}}$

23.24

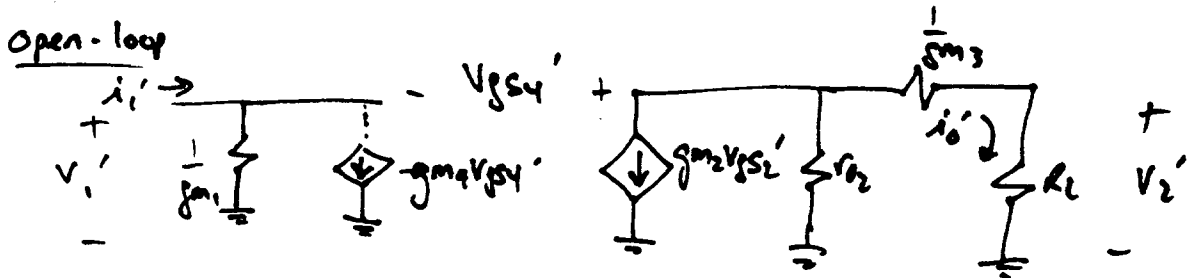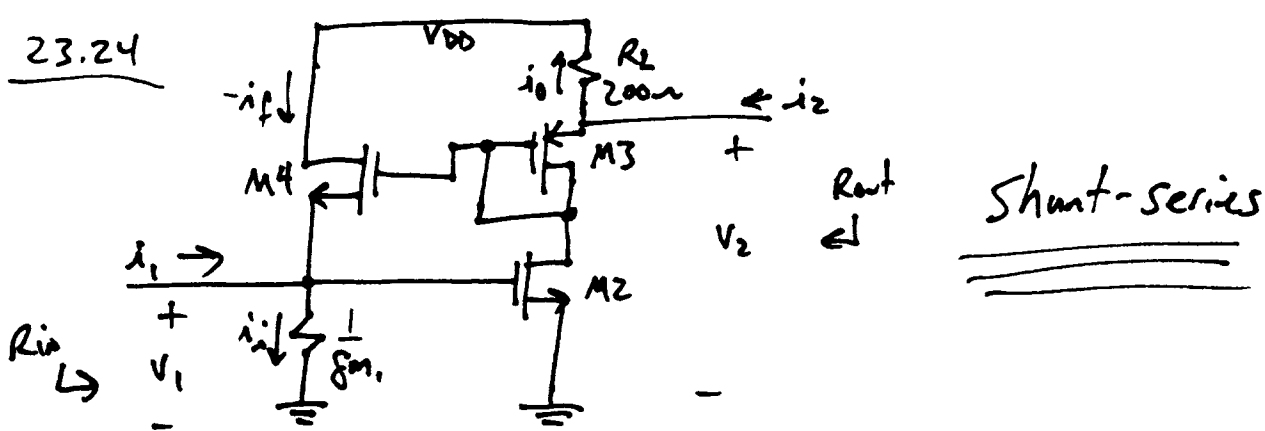

$$R_i = \frac{1}{g_{m1}} \parallel \frac{1}{g_{m4}} = 8.34 \Omega \quad R_o = R_L \parallel \left( \frac{1}{g_{m3}} + r_{o2} \right) \approx R_L = 200 \Omega$$

$$A_{oc} = \frac{i_{o2}'}{i_{i1}'} = \frac{V_{22}'}{V_{i1}'} \cdot \frac{R_i}{R_o} = \frac{R_i}{R_o} \cdot \left[ \frac{R_L}{R_L + \frac{1}{g_{m3}}} \right] \left[ -g_{m2} \left( R_L + \frac{1}{g_{m3}} \right) \right] = \frac{8.34}{200} \cdot \frac{200}{216.67} \cdot \frac{-0.6 \cdot 216.67}{1} = -5 \frac{A}{A}$$

$$\beta = \frac{i_{f1}'}{i_{o2}'} = \frac{-g_{m4} V_{gs4}}{V_{gs4} \left( 1 + \frac{g_{m4}}{g_{m1}} \right)} \cdot (R_L + g_{m1}) = -6.5 \frac{A}{A}$$


$$\Rightarrow R_{in} = \frac{R_i}{1 + A_{oc}\beta} = \frac{8.34 \Omega}{1 + 5(6.5)} = 1.96 \Omega = R_{in}$$

$$R_{out} = R_L \parallel (R_{of} - R_e) = R_L \parallel ((R_o(1 + A_{oc}\beta) - R_L)) = 200 \parallel (650) = 153 \Omega = R_{out}$$

$$A_{cl} = \frac{i_2}{i_1} = \frac{A_{oc}}{1 + A_{oc}\beta} = \frac{-5 \frac{A}{A}}{4.25} = -1.18 \frac{A}{A}$$

$$\frac{V_2}{V_1} = \frac{i_2}{i_1} \cdot \frac{R_{out}}{R_{in}} = (-1.18) \left( \frac{153}{1.96} \right) = -9.2 \frac{V}{V} = \frac{V_2}{V_1}$$

23.25

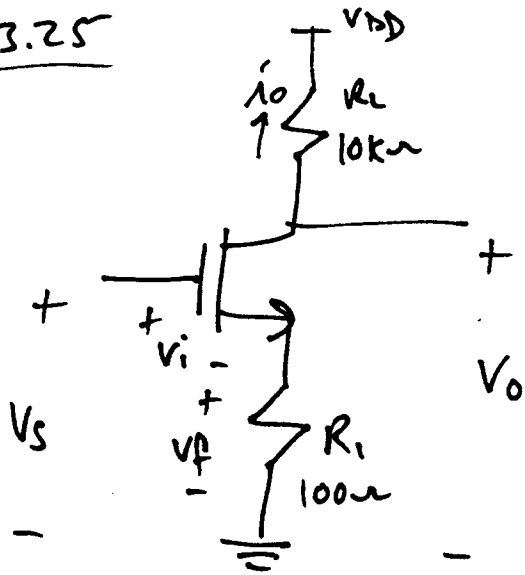

## Series-Series feedback !!


In words, any increase in  $V_s$  causes an increase in  $V_o$ . As  $V_o$  gets larger, the AC current through  $R_L$  gets larger which is also flowing through  $R_1$ . This increased current through  $R_1$  raises  $V_F$ , therefore causing the feedback.

$$A_{OL} = \frac{i_o}{V_s} = \frac{V_o}{V_s} \cdot \frac{1}{R_L} = [CS] \cdot \frac{1}{R_L} = \frac{-g_{m1} \cdot r_{o1} \parallel R_L}{g_{m1} R_1 + 1} \cdot \frac{1}{R_L} = \frac{-(0.6) \cdot 70k \parallel 10k}{61} \cdot \frac{1}{10k}$$

$$\Rightarrow A_{OL} = -860.7 \times 10^{-6} \text{ A/V}$$


$$\beta = \frac{V_F}{i_o} = \frac{-i_o \cdot R_1}{i_o} = -R_1 \Rightarrow \beta = -100 \text{ V/A}$$

23.26

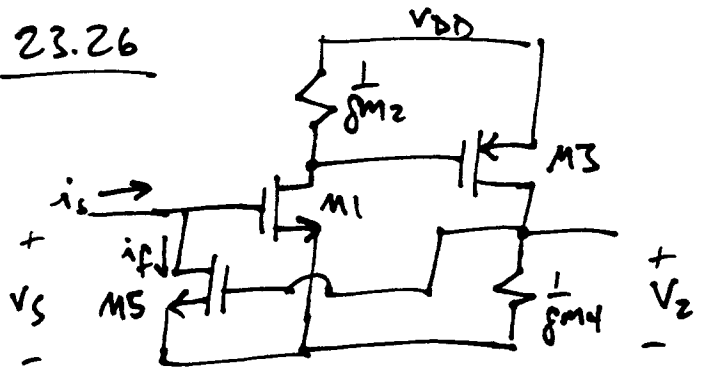

Shunt-shunt  $A_{\beta}$ !  
 3 inversions for  $(-)$   $A_{\beta}$  w/ shunt mix in

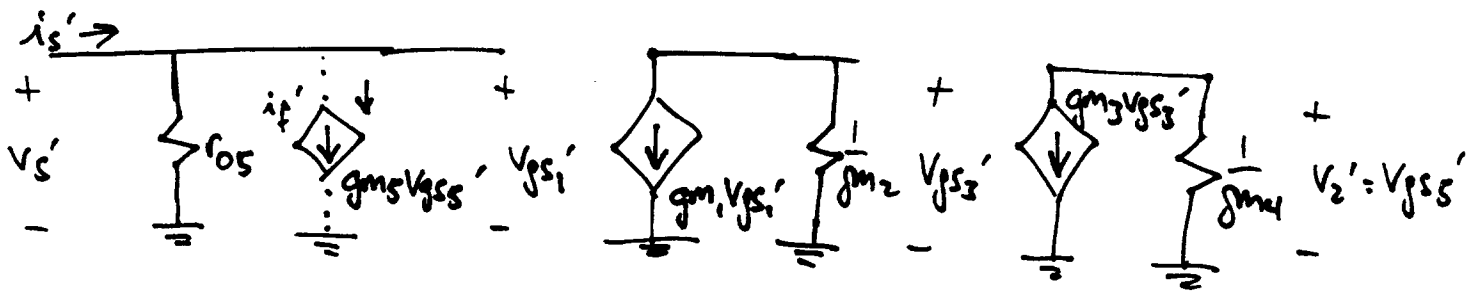$R_{o1} = \infty$      $R_{i2} = R_{inD3} = r_{o5}$



$R_i = r_{o5}$  ;  $R_o = \frac{1}{g_{m4}}$  ;  $\frac{V_2'}{V_1'} = (CS)(CS) = \left(-\frac{g_{m1}}{g_{m2}}\right)\left(-\frac{g_{m3}}{g_{m4}}\right) = 1 \text{ V/V}$


$A_{OL} = \frac{V_2'}{i_s'} = \frac{V_2'}{V_1'} \cdot R_i = 1 \cdot r_{o5} \Rightarrow A_{OL} = 70 \text{ K V/A}$   
 $\beta = \frac{i_f'}{V_2'} = \frac{g_{m5} \cdot V_{GS5}'}{V_{GS5}'} = g_{m5} \Rightarrow \beta = .06 \text{ A/V}$   
 $\Rightarrow 1 + A_{OL}\beta = 4,201 \approx A_{OL}\beta = 4200$

$R_{in} = R_{if} = \frac{R_i}{1 + A_{OL}\beta} \Rightarrow \boxed{R_{in} = 16.7 \Omega}$      $R_{out} = R_{of} = \frac{R_o}{1 + A_{OL}\beta} = \boxed{.004 \Omega = R_{of}}$

$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta} = 16.7 \text{ V/A} = \frac{V_2}{i_s}$

$\Rightarrow \frac{V_2}{V_1} = \frac{V_2}{i_s} \cdot \frac{1}{R_{in}} = \frac{16.7 \text{ V/A}}{16.7 \Omega} \Rightarrow \boxed{\frac{V_2}{V_1} = 1 \text{ V/V}}$

23.27

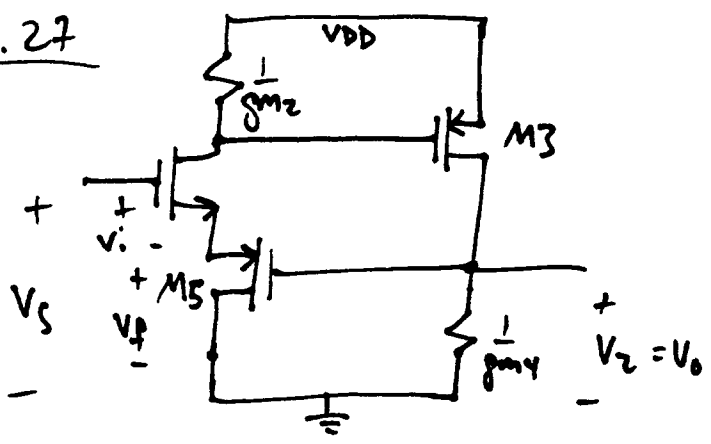

Series-Shunt

2 inversions  $\Rightarrow (-) A\beta$ .




$$A_{OL} = \frac{v_2'}{v_s'} = [CS] \cdot [CS] = \left[ \frac{-g_{m1}}{g_{m2}} \right] \cdot \left[ \frac{-g_{m3}}{g_{m4}} \right] = 333 \times 10^{-6} \text{ v/v}$$

$$\beta = \frac{v_f'}{v_2'} = \frac{v_{gs5'}}{g_{m5} v_{gs5'} \cdot r_{os}} = \frac{1}{g_{m5} \cdot r_{os}} = 500 \times 10^{-6} \text{ v/v}$$


$$\Rightarrow A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta} = \frac{v_2}{v_1} = \boxed{333 \times 10^{-6} \text{ v/v} = \frac{v_2}{v_1}}$$

$$R_o \approx \frac{1}{g_{m4}} = 16.67 \Omega \Rightarrow R_{out} = \frac{R_o}{1 + A_{OL}\beta} = \boxed{16.67 \Omega = R_{out}}$$

23.28

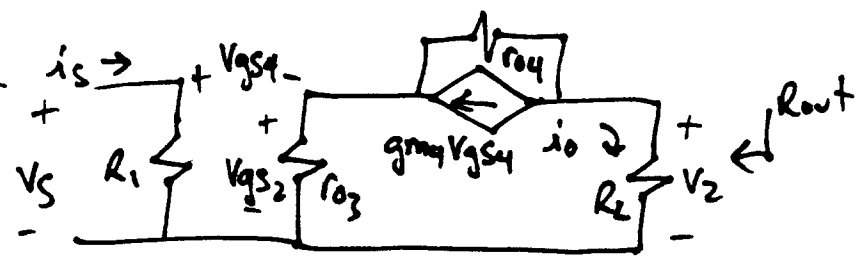
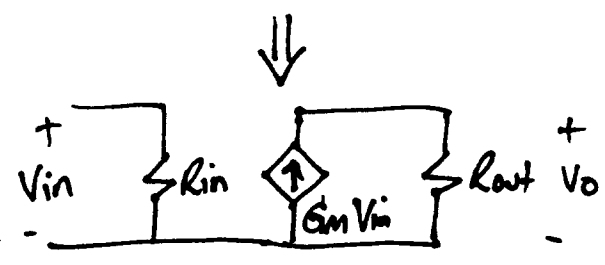
$$A_{OL} = \frac{i_o}{i_s} = \frac{V_2}{V_S} \cdot \frac{R_1}{R_L}$$



$$\frac{V_2}{V_S} = \frac{V_o}{V_{in}} = G_m R_{out}$$

$$G_m \triangleq \frac{i_o}{v_{in}} \Big|_{V_2=0}$$

$$\rightarrow R_{out} = R_L \parallel R_{inD4} = R_L \parallel (r_{O3} + r_{O4} (1 + g_{m4} r_{O3}))$$

w/  $V_2=0$

$$\textcircled{1} \quad V_{gs2} = -i_o r_{O3}$$

$$\textcircled{2} \quad \frac{V_{gs2}}{r_{O3}} = g_{m4} V_{gs1} - \frac{V_{gs2}}{r_{O4}}$$


$$\textcircled{1} \rightarrow \textcircled{2} : -i_o = g_{m4} V_{gs1} + i_o \frac{r_{O3}}{r_{O4}} \Rightarrow \frac{i_o}{V_{gs1}} = \frac{-g_{m4}}{1 + \frac{r_{O3}}{r_{O4}}}$$

$$\text{and } \frac{V_{gs1}}{V_{in}} = \frac{1 + r_{O3}/r_{O4}}{1 + \frac{r_{O3}}{r_{O4}} + g_{m4} r_{O3}} \Rightarrow G_m = \frac{i_o}{V_{in}} = \frac{i_o}{V_{gs1}} \cdot \frac{V_{gs1}}{V_{in}} = \frac{-g_{m4}}{1 + \frac{r_{O3}}{r_{O4}} + g_{m4} r_{O3}}$$

$$\Rightarrow A_{OL} = \frac{i_o}{i_s} = \frac{V_2}{V_S} \cdot \frac{R_1}{R_L} = G_m R_{out} \cdot \frac{R_1}{R_L} = \frac{-g_{m4} \cdot R_L \parallel (r_{O3} + r_{O4} (1 + g_{m4} r_{O3}))}{1 + \frac{r_{O3}}{r_{O4}} + g_{m4} r_{O3}}$$

23.29

Closed-loop

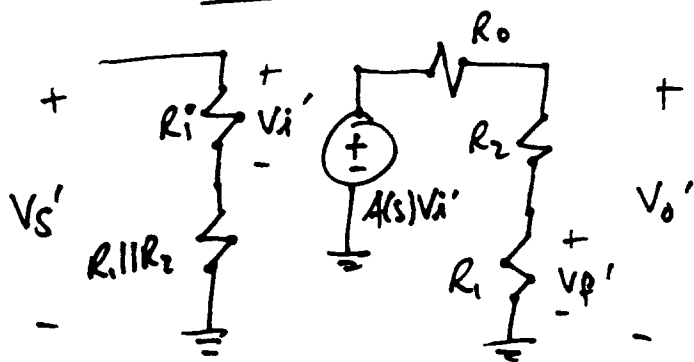

$$A(s) = \frac{100,000}{\left(\frac{s}{200} + 1\right)^3}$$

$$R_i = 10\text{M}\Omega$$

$$R_o = 100\Omega$$

$$R_1 = R_2 = 10\text{K}\Omega$$


$$A_{OL} = \frac{V_o'}{V_s'} = A(s) \cdot \left[ \frac{R_2 + R_1}{R_2 + R_1 + R_o} \right] \cdot \left[ \frac{R_i}{R_i + R_1 \parallel R_2} \right] = \frac{\cancel{994,528} 99,453}{\left(\frac{s}{200} + 1\right)^3}$$

$$\beta = \frac{R_1}{R_1 + R_2} = 0.5 \Rightarrow \text{loop gain} = A_{OL}(s)\beta = \frac{49,726}{\left(\frac{s}{200} + 1\right)^3}$$

find  $\omega_{180}$ :  $-3 \tan^{-1}\left(\frac{\omega_{180}}{200}\right) = -180 \Rightarrow \omega_{180} = 200 \tan(60) = 346.41 \text{ rad/s}$

find  $|A_{OL}(j\omega)\beta|, \text{dB} @ \omega = \omega_{180}$ :  $\Rightarrow 20 \log(49,726) - 3(20 \log \sqrt{\left(\frac{346.41}{200}\right)^2 + 1})$   
 $= 75.87 \text{ dB} > 0 \text{ dB}$

unstable

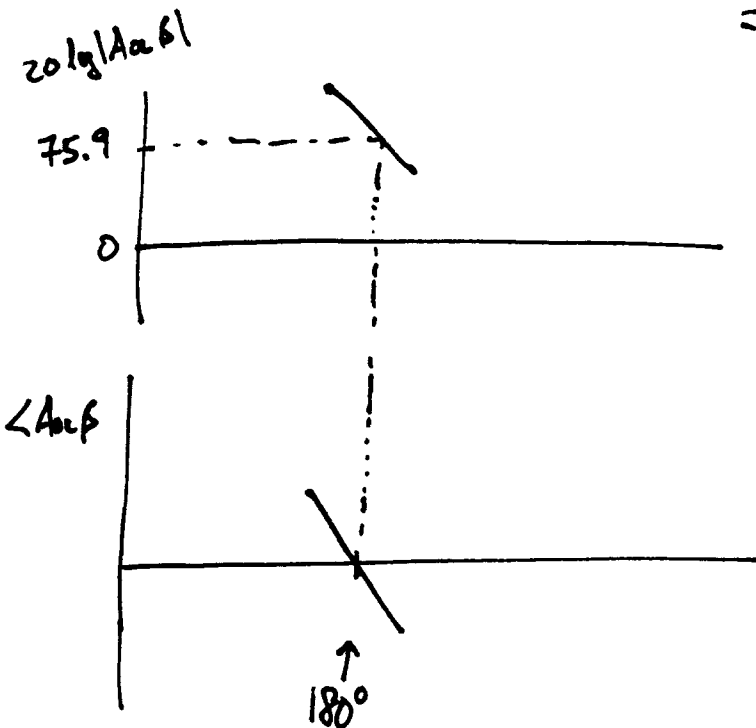

23.30

$$A_{02}(j\omega) = \frac{10,000}{\left(1 + \frac{j\omega}{100}\right)\left(1 + \frac{j\omega}{\omega_2}\right)} = A_{02}(j\omega) \cdot \beta, \text{ since } \beta = 1$$

Finding  $\omega_{0dB}$ :

$$|G| = \frac{10,000}{\sqrt{\left(1 + \left(\frac{\omega_{0dB}}{100}\right)^2\right)\left(1 + \left(\frac{\omega_{0dB}}{\omega_2}\right)^2\right)}} \Rightarrow \left(1 + \left(\frac{\omega_{0dB}}{100}\right)^2\right)\left(1 + \left(\frac{\omega_{0dB}}{\omega_2}\right)^2\right) = 10,000^2$$

$$\Rightarrow \frac{\omega_{0dB}^4}{100^2 \cdot \omega_2^2} + \omega_0^2 \left(\frac{1}{100^2} + \frac{1}{\omega_2^2}\right) - 100 \times 10^6 = 0$$

$$\Rightarrow \omega_{0dB} \approx \sqrt{\left(\left(\frac{1}{100}\right)^4 + \frac{40,000}{\omega_2^2} - \left(\frac{1}{100}\right)^2\right) \cdot (5,000 \cdot \omega_2^2)} = \text{EQN 1}$$

Finding phase margin

$$PM = \phi_m = \text{Arg}(A(j\omega)\beta) \Big|_{\omega=\omega_{0dB}} - (-180^\circ)$$


$$\Rightarrow \phi_m = -\tan^{-1}\left(\frac{\omega_{0dB}}{100}\right) - \tan^{-1}\left(\frac{\omega_{0dB}}{\omega_2}\right) + 180^\circ$$

and since 100 r/s is relatively small...

$$\phi_m \approx 90^\circ - \tan^{-1}\left(\frac{\omega_{0dB}}{\omega_2}\right) = \text{EQN 2}$$

$\omega_2$ (given)	$\omega_{0dB}$ (EQN 1)	$\phi_m$ (EQN 2)	Stable?
$10^5$ r/s	308 k r/s	$17.6^\circ$	yes
$10^6$ r/s	786 k r/s	$51.83^\circ$	yes
$10^7$ r/s	995 k r/s	$84.3^\circ$	yes
$5 \times 10^6$ r/s	981.3 k r/s	$78.9^\circ$	yes

23.31

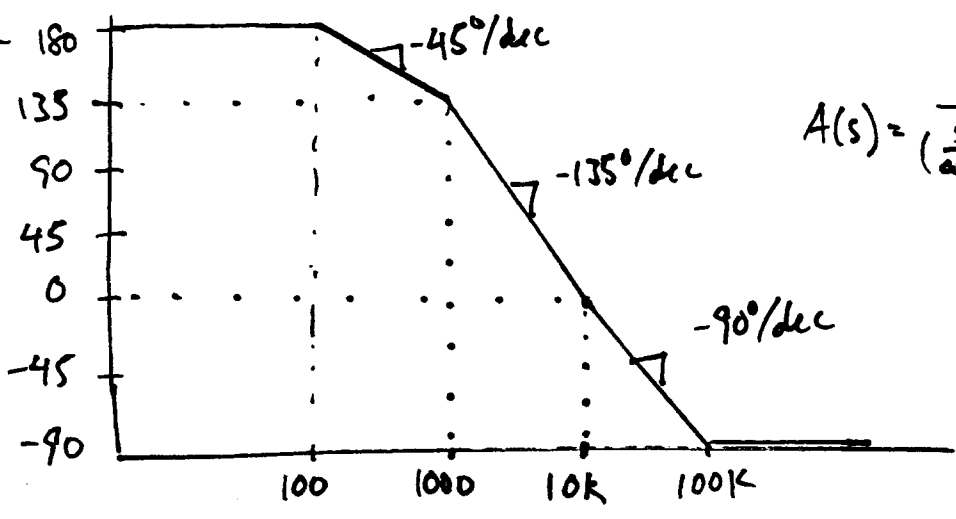

$$A(s) = \frac{-1000}{\left(\frac{s}{\omega_1} + 1\right)\left(\frac{s}{\omega_2} + 1\right)\left(\frac{s}{\omega_3} + 1\right)}$$

$\omega_1 = 1000$   
 $\omega_2 = 10K$   
 $\omega_3 = 10K$


} from given slopes      also,  $\omega_{iso} = 10K$

$$A(s) = \frac{-1000}{\left(\frac{s}{1000} + 1\right)\left(\frac{s}{10K} + 1\right)^2}$$

$\Rightarrow$  set  $|A(j\omega)\beta| = 1$  @  $\omega_{iso}$

$$\Rightarrow \frac{1000\beta}{\sqrt{\left(\frac{\omega_{iso}^2}{1000} + 1\right)\left(\frac{\omega_{iso}^2}{10K} + 1\right)^2}} = 1 \quad \Rightarrow \boxed{\beta = .0201}$$

23.32

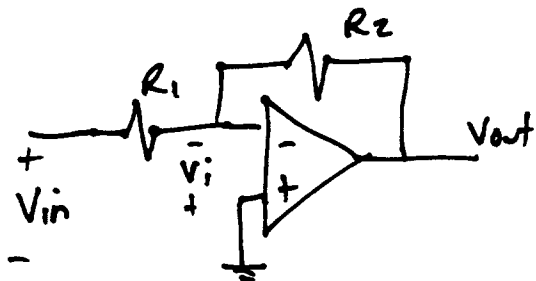


$$R_1 = 1k\Omega$$

$$R_2 = 10k\Omega$$

$$\frac{V_{out}}{V_{in}} = -5 \text{ V/V}$$

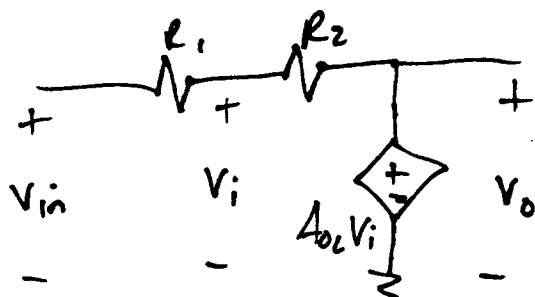↓ model (assuming  $R_i = \infty$ ,  $R_o = 0$ )



using superposition, 
$$V_i = -V_{in} \cdot \frac{R_2}{R_1 + R_2} - V_o \cdot \frac{R_1}{R_1 + R_2}$$

also, 
$$V_i = \frac{V_{out}}{A_{ol}}$$


$$\Rightarrow V_{out} \left( \frac{1}{A_{ol}} + \frac{R_1}{R_1 + R_2} \right) = -V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{-\frac{R_2}{R_1 + R_2}}{\frac{1}{A_{ol}} + \frac{R_1}{R_1 + R_2}} \Rightarrow \frac{1}{A_{ol}} = \frac{-\frac{R_2}{R_1 + R_2}}{\frac{V_{out}}{V_{in}} - \frac{R_1}{R_1 + R_2}}$$

$$\Rightarrow \frac{1}{A_{ol}} = \frac{-\frac{10}{11}}{-5} - \frac{1}{11} = -0.0909$$

$$\Rightarrow A_{ol} = 11 \text{ V/V}$$

23.33

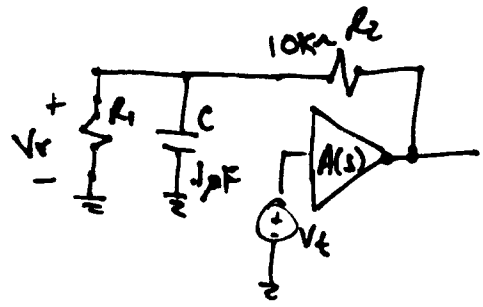

$\omega_{cut} = 8,000 \text{ rad/s}$

$\phi_m = 45^\circ$

$A(s) = \frac{-A_0}{(\frac{s}{200} + 1)(\frac{s}{10k} + 1)}$

find  $A_0$  &  $R_1$

$$\frac{V_r}{V_t} = A(s) \cdot \frac{\frac{V_c}{s + 1/R_1 C}}{\frac{V_c}{s + 1/R_1 C} + R_2} = \frac{A(s)}{R_2 C} \cdot \frac{1}{s + \frac{1}{C}(\frac{1}{R_1} + \frac{1}{R_2})} \Rightarrow \text{let } x = \frac{1}{R_1 C}$$

$$\Rightarrow \frac{V_r}{V_t} = \frac{(\frac{1000}{1000+x}) A(s)}{(\frac{s}{1000+x} + 1)} = \frac{-A_0 (\frac{1000}{1000+x})}{(\frac{s}{1000+x} + 1)(\frac{s}{200} + 1)(\frac{s}{10k} + 1)} = -A(s)\beta(s)$$

$\phi_m = \text{Arg}(A(j\omega)\beta(j\omega))|_{\omega=8k} + 180^\circ = 45^\circ \Rightarrow \text{Arg}(A(j\omega)\beta(j\omega))|_{\omega=8k} = 135^\circ$

$\Rightarrow \tan^{-1}(\frac{8k}{1000+x}) + \tan^{-1}(\frac{8k}{200}) + \tan^{-1}(\frac{8k}{10k}) = 135^\circ$

$\Rightarrow \tan^{-1}(\frac{8k}{1000+x}) = 7.772 \Rightarrow x = 57.6 \text{ K}$

$\Rightarrow R_1 = 174 \Omega$

$|A(j\omega)\beta(j\omega)||_{\omega=8k} = 1 = \frac{A_0 (.017)}{\sqrt{\frac{8k^2}{58.6k^2 + 1}} \sqrt{\frac{8k^2}{200^2 + 1}} \sqrt{\frac{8k^2}{10k^2 + 1}}}$

$\Rightarrow A_0 = 3,042 \text{ V/V}$

23.34

$$RR = -\frac{V_r}{V_t} = A_{OL}(s)\beta(s) = \frac{49,726}{\left(\frac{s}{200} + 1\right)^3} \quad \text{is it stable?}$$

first find  $\omega_{180}$ :  $-3 \tan^{-1}\left(\frac{\omega_{180}}{200}\right) = -180^\circ$

$$\Rightarrow \omega_{180} = 200 \cdot \tan(60^\circ) = 346.41 \text{ r/s}$$

now find

$$\left| A(j\omega)\beta(j\omega) \right|_{\omega=\omega_{180}} = 20 \log(49,726) - 3 \left( 20 \log \sqrt{\left(\frac{346.41}{200}\right)^2 + 1} \right)$$

$$= 75.87 \text{ dB} > 0 \text{ dB}$$

$\Rightarrow$  unstable