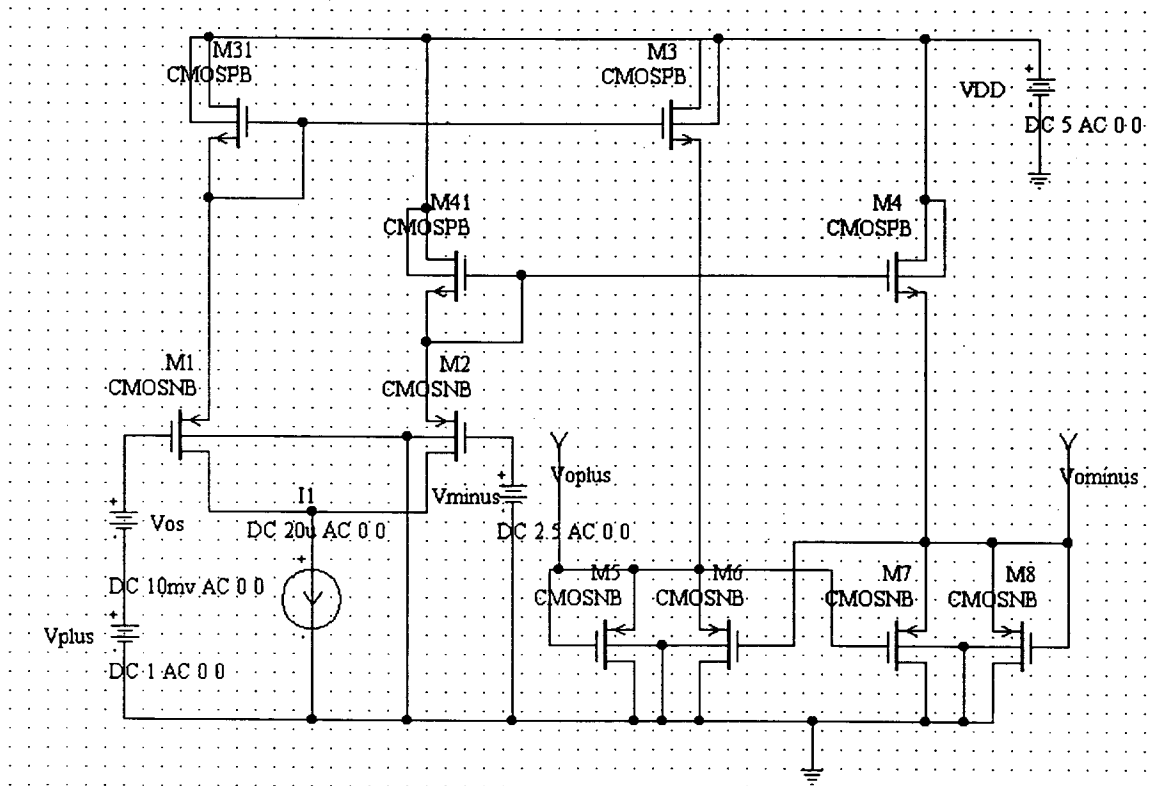


Problem 26.1



*** Top Level Netlist ***

```

I1      1 0      DC 20u AC 0 0
M1      1 10 3 0 CMOSNB L=2u W=10u
M2      1 5 6 0 CMOSNB L=2u W=10u
M3      7 3 Voplus 7 CMOSPFB L=2u W=3u
M31     7 3 3 7 CMOSPFB L=2u W=3u
M4      7 6 Vominus 7 CMOSPFB L=2u W=3u
M41     7 6 6 7 CMOSPFB L=2u W=3u
M5      0 Voplus Voplus 0 CMOSNB L=2u W=3u
M6      0 Vominus Voplus 0 CMOSNB L=2u W=3u
M7      0 Voplus Vominus 0 CMOSNB L=2u W=3u
M8      0 Vominus Vominus 0 CMOSNB L=2u W=3u
VDD     7 0      DC 5 AC 0 0
Vminus  5 0      DC 2.5 AC 0 0
Vos     10 2     DC 10mv AC 0 0
Vplus   2 0      DC 1 AC 0 0

```

***** Spice models and macro models *****

.MODEL CMOSNB NMOS LEVEL=4


.MODEL CMOSPFB PMOS LEVEL=4

***** End of spice models and macro models *****

.DC Vplus 2 3 .01

.end

The SPICE simulation result is shown below:

 

Problem 26.2

The input capacitance of the comparator of Fig 26.11 is approximately the C_{gs} of the input MOSFETs, that is,

$$C_{in} \approx C_{gs(in)} = \frac{2}{3} C_{ox}' \cdot W \cdot L$$

(Assuming input MOSFETs are in saturation region and neglecting C_{gd}).

The hysteresis of the decision circuit causes the gain of the comparator to increase.

Problem 26.3

We use the circuit of Fig 26.5.


$$V_{spH} = 100mV = \frac{I_{ss}}{g_m} \cdot \frac{\frac{\beta_B}{\beta_A} - 1}{\frac{\beta_B}{\beta_A} + 1} = \frac{20 \mu A}{71 \mu A/V} \times \frac{\frac{\beta_B}{\beta_A} - 1}{\frac{\beta_B}{\beta_A} + 1}$$

$$\Rightarrow \frac{\beta_B}{\beta_A} = 2.1$$

Set the length of all devices $2 \mu m$, $W_5 = W_8 = 3 \mu m$
resulting in $W_6 = W_7 = \underline{\underline{6 \mu m}}$.

The SPICE simulation results are shown on next page.

Problem 26.3

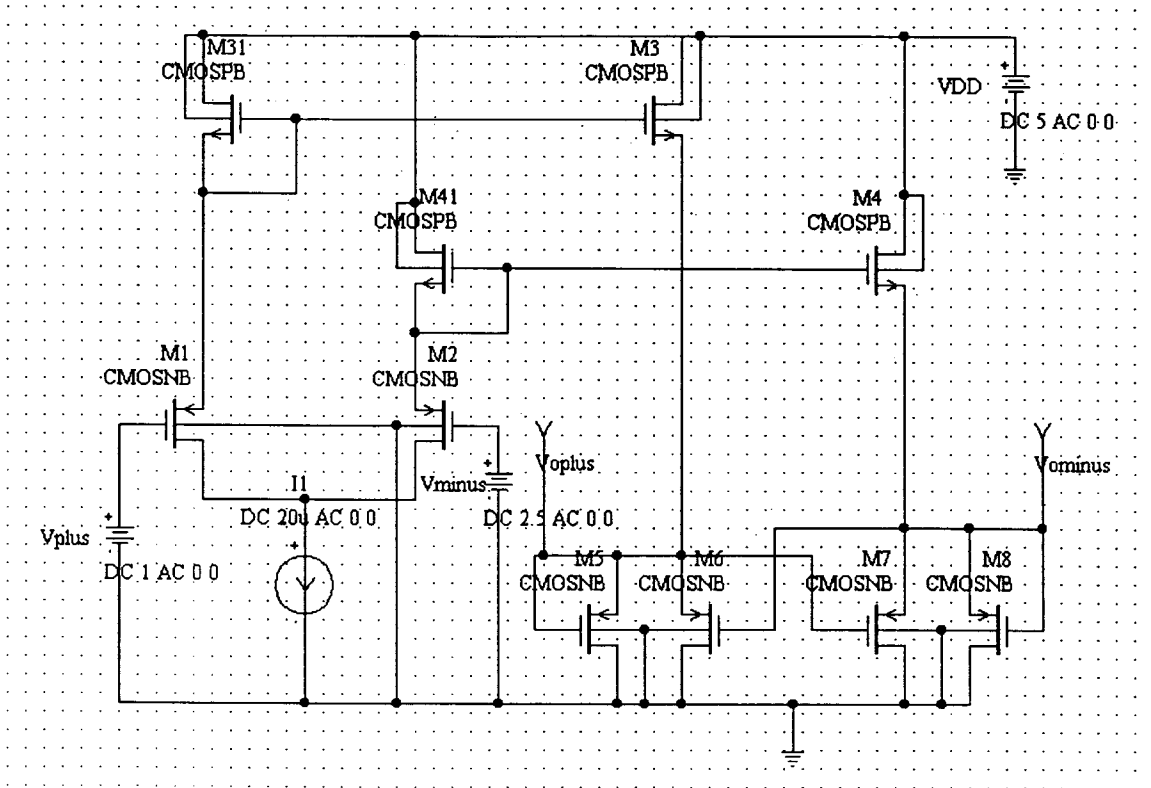

*** Top Level Netlist ***

```

I1      1 0      DC 20u AC 0 0
M1      1 2 3 0 CMOSNB L=2u W=10u
M2      1 5 6 0 CMOSNB L=2u W=10u
M3      7 3 Voplus 7 CMOSPFB L=2u W=3u
M31     7 3 3 7 CMOSPFB L=2u W=3u
M4      7 6 Vomius 7 CMOSPFB L=2u W=3u
M41     7 6 6 7 CMOSPFB L=2u W=3u
M5      0 Voplus Voplus 0 CMOSNB L=2u W=3u
M6      0 Vomius Voplus 0 CMOSNB L=2u W=6u
M7      0 Voplus Vomius 0 CMOSNB L=2u W=6u
M8      0 Vomius Vomius 0 CMOSNB L=2u W=3u
VDD     7 0      DC 5 AC 0 0
Vminus  5 0      DC 2.5 AC 0 0
Vplus   2 0      DC 1 AC 0 0

```

***** Spice models and macro models *****

.MODEL CMOSNB NMOS LEVEL=4

.MODEL CMOSPFB PMOS LEVEL=4



***** End of spice models and macro models *****

.OPTION ABSTOL=1u RELTOL=0.01 VNTOL=10mv

.DC Vplus 3 2 -.001


.end

  The SPICE simulation result is shown below:





```
.OPTION ABSTOL=1u CHGTOL=1.0E-13 ITL4=100 RELTOL=0.01 VNTOL=1mv
.probe
.tran 1n 300n 200n 1n uic
.plot tran all
.print tran all
.end
```

 
The SPICE simulation result is shown below:



The minimum sensitivity
is 3 mV

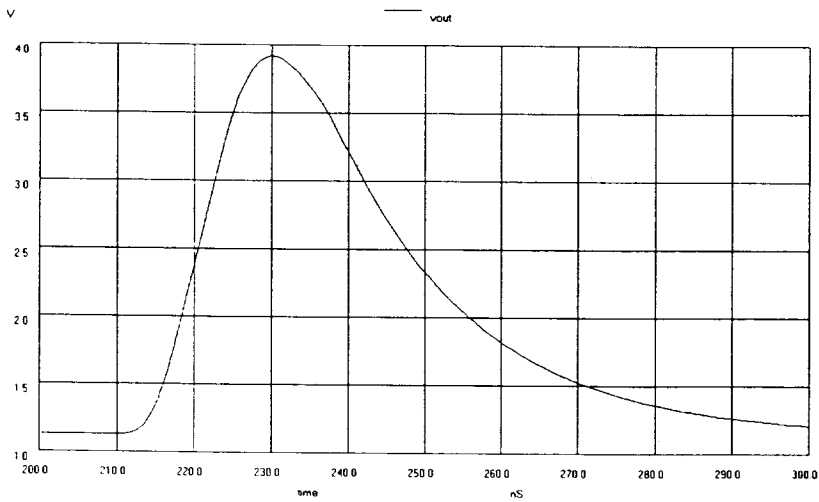

Problem 26.5

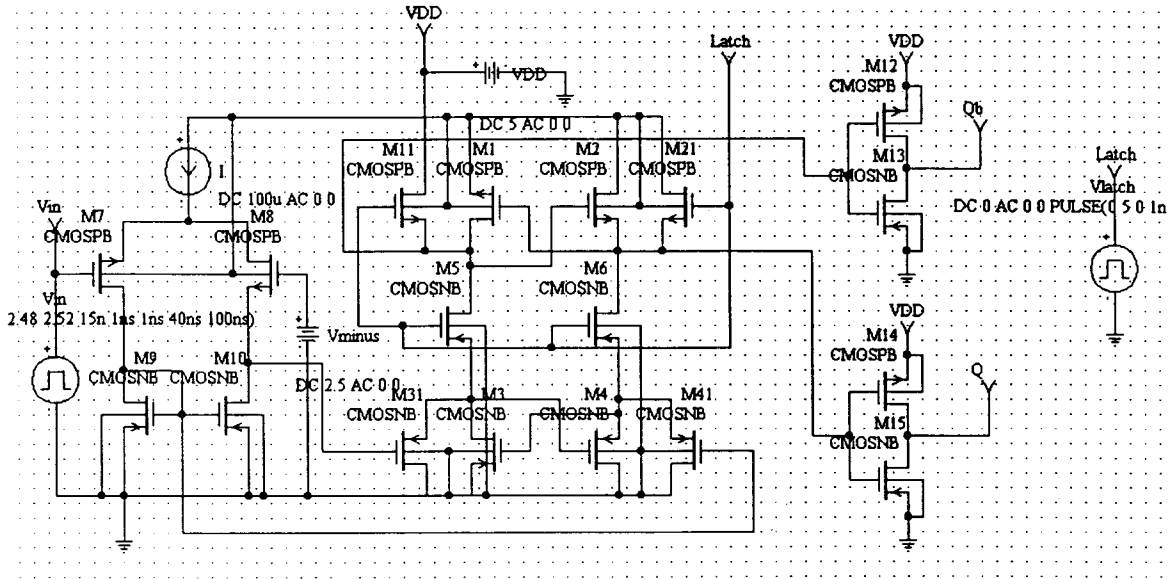

*** Top Level Netlist ***

```

I      VDD 11      DC 100u AC 0 0
M1     1 2 VDD VDD CMOSPB
M10    8 9 0 0 CMOSNB L=2u W=3u
M11    VDD Latch 1 VDD CMOSPB L=2u W=3u
M12    Qb 1 VDD VDD CMOSPB L=2u W=30u
M13    Qb 1 0 0 CMOSNB L=2u W=10u
M14    Q 2 VDD VDD CMOSPB L=2u W=30u
M15    Q 2 0 0 CMOSNB L=2u W=10u
M2     VDD 1 2 VDD CMOSPB
M21    VDD Latch 2 VDD CMOSPB L=2u W=3u
M3     4 5 0 0 CMOSNB
M31    0 8 4 0 CMOSNB L=2u W=3u
M4     0 4 5 0 CMOSNB
M41    0 9 5 0 CMOSNB L=2u W=3u
M5     1 Latch 4 0 CMOSNB L=2u W=3u
M6     2 Latch 5 0 CMOSNB L=2u W=3u
M7     9 Vin 11 VDD CMOSPB L=2u W=10u
M8     11 12 8 VDD CMOSPB L=2u W=10u
M9     9 9 0 0 CMOSNB L=2u W=3u
VDD    VDD 0 DC 5 AC 0 0
Vin    Vin 0 DC 0 AC 0 0 PULSE(2.48 2.52 15n 1ns 1ns 40ns 100ns)
Vlatch Latch 0 DC 0 AC 0 0 PULSE(0 5 0 1n 1n 20ns 40ns)
Vminus 12 0 DC 2.5 AC 0 0

```

***** Spice models and macro models *****

.MODEL CMOSPB PMOS LEVEL=4

.MODEL CMOSNB NMOS LEVEL=4


***** End of spice models and macro models *****

```

.OPTION ABSTOL=1u RELTOL=0.01 VNTOL=50mv
.tran 1n 200n 0 1n
.end


```

 The following is the SPICE simulation result:



Note: The 4 MOSFETs connected to Latch don't turn on and off at the same rate causing a glitch in the output. Sizing can minimize the glitch.

Problem 26.6

 


The advantage of this output buffer is the small layout size. The main problem of using this buffer is the low speed (caused by the small gain of the circuit). Also, this buffer does not exhibit the common mode rejection to its differential inputs.

Problem 26.7

Since the self-biased comparator (see Fig 26.19) has a wide input common-mode range, it can be used as a wide-swing op-amp. As there is only one high impedance node (output node) in this configuration, compensating the circuit is just like that of an OTA, that is, selecting a minimum load capacitance for desired f_u and phase margin, and the circuit is always stable.

Problem 26.8

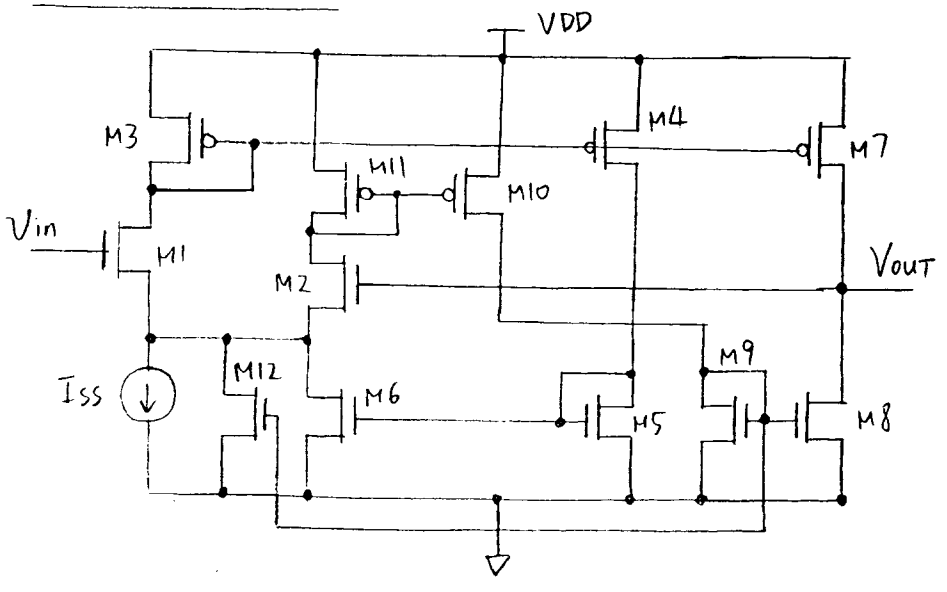


The DC biasing for this circuit is difficult to implement because of the positive feedback. One might consider the OTA of Fig 26.24 for stable biasing.

Problem 26.9

The benefits of using long channel length in the multiplying quad of Fig 26.30 is the reduced module length modulation effect, and ensuring devices operate follows Equation A.5. The long channel devices do not affect speed since they are part of the feedback of the op-amp. The problem of using long length devices, however, is that smaller W/L ratio of MOSFETs makes it more difficult to keep the quad in the triode region.

Problem 26.10

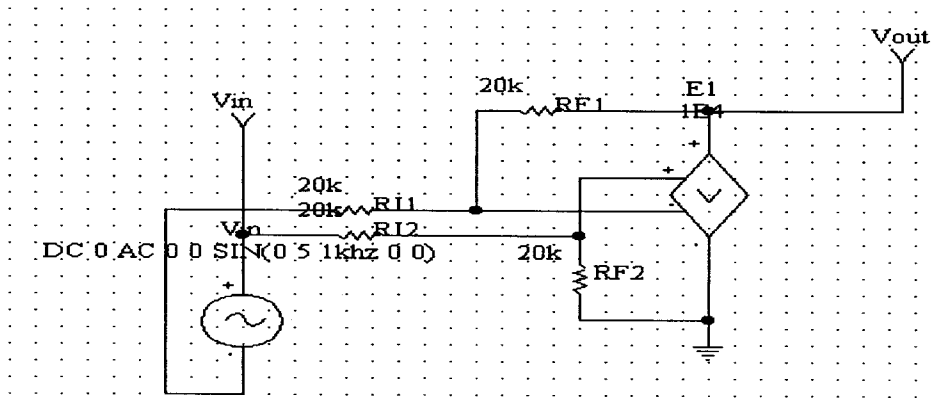

***** Top Level Netlist *****

```


E1      Vout 0 4 3      1E4
RF1     Vout 3 20k
RF2     0 4 20k
RI1     5 3 20k
RI2     4 Vin 20k
Vin     Vin 5  DC 0 AC 0 0 SIN(0.5 1kHz 0 0)
    
```

***** Spice models and macro models *****


***** End of spice models and macro models *****

```

.OPTION ABSTOL=1u RELTOL=0.01 VNTOL=1mv
.op
.tran 500n 1ms 0 500n
.end
    
```

 

Problem 26.10 (cont.)

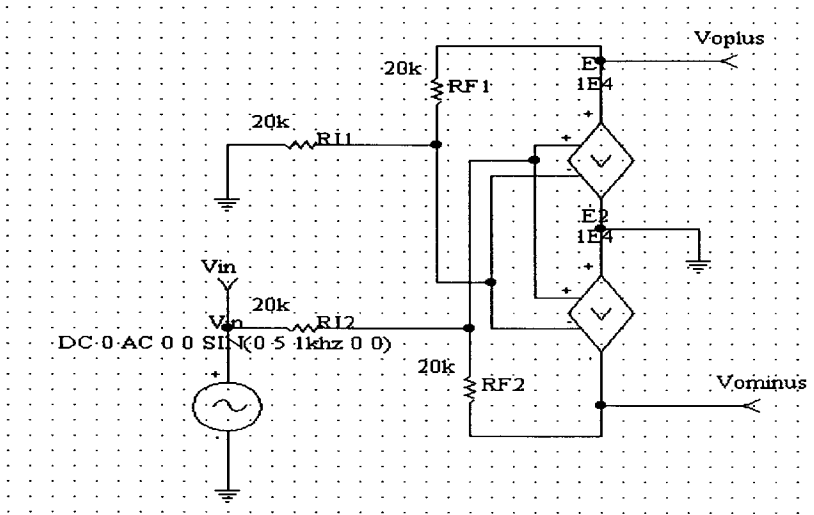


*** Top Level Netlist ***

```
E1      Voplus 0 4 5  1E4
E2      0 Vominus 4 5  1E4
RF1     Voplus 5 20k
RF2     4 Vominus 20k
RI1     0 5 20k
RI2     4 Vin 20k
Vin     Vin 0  DC 0 AC 0 0 SIN(0.5 1kHz 0 0)
```


***** Spice models and macro models *****

***** End of spice models and macro models *****

```
.OPTION ABSTOL=1u RELTOL=0.01 VNTOL=1mv
.op
.tran 500n 1ms 0 500n
.end
```

 

Problem 26.11

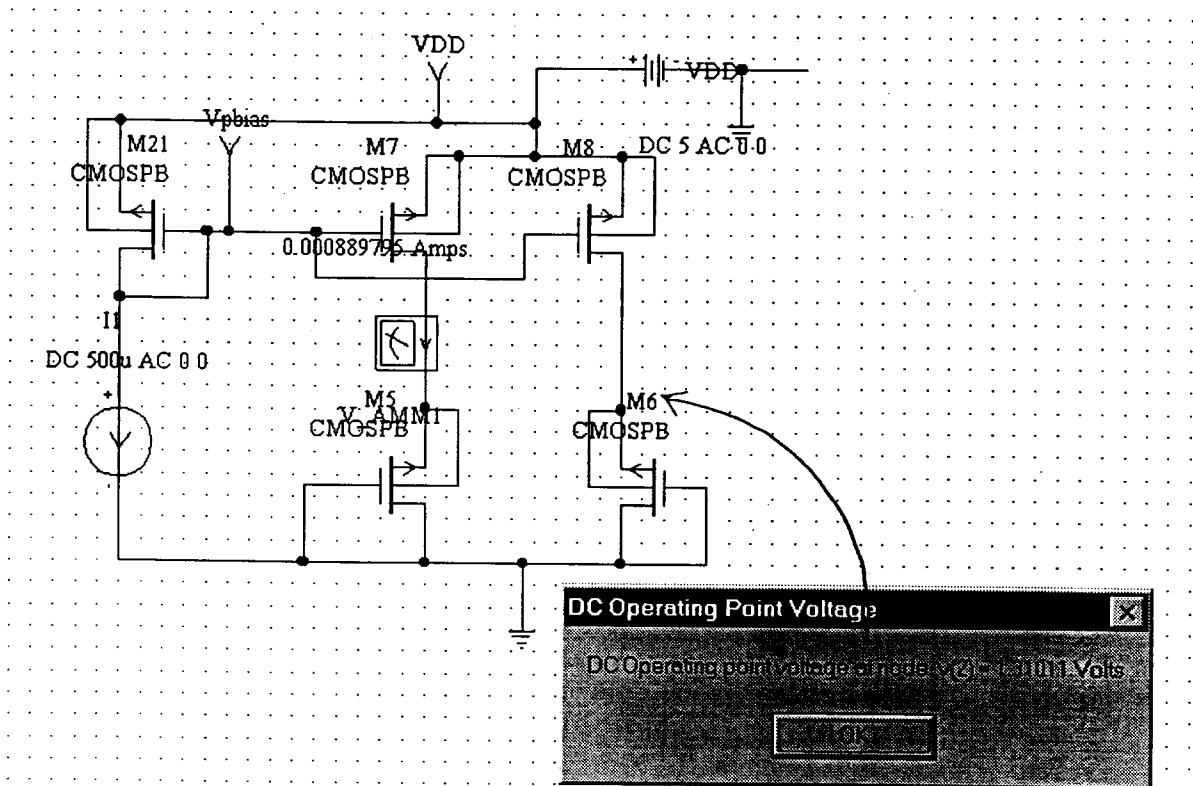

*** Top Level Netlist ***

```

I1      Vpbias 0      DC 500u AC 0 0
M21     Vpbias Vpbias VDD VDD CMOSPB L=2u W=1000u
M5      0 0 3 3 CMOSPB L=2u W=1000u
M6      0 0 2 2 CMOSPB L=2u W=1000u
M7      1 Vpbias VDD VDD CMOSPB L=2u W=1000u
M8      2 Vpbias VDD VDD CMOSPB L=2u W=1000u
V_AMM1  1 3 0V
VDD     VDD 0 DC 5 AC 0 0
    
```

***** Spice models and macro models *****

```
.MODEL CMOSPB PMOS LEVEL=4
```

***** End of spice models and macro models *****

```
.OPTION ABSTOL=1u RELTOL=0.01 VNTOL=1mv
.op
.end
```