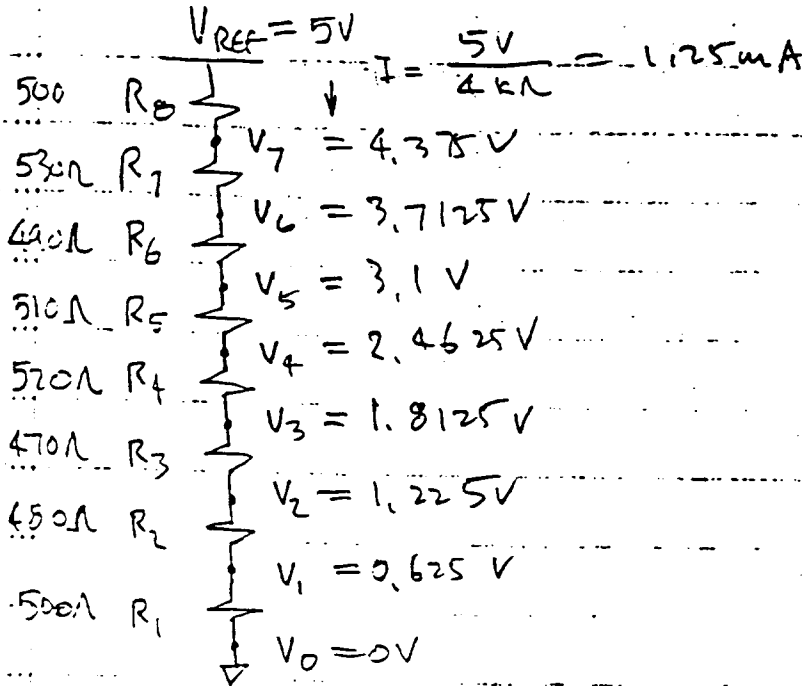


Chapter 29

29.1



Digital Input	Step Height (V)		DNL (V) (LSB)		Voltage Output (V)		INL (V)
	Actual	Ideal			Actual	Ideal	
000					0	0	0
001	0.625	0.625	0	0	0.625	0.625	0
010	0.595	"	-0.03	-0.048	1.225	1.25	-0.025
011	0.5925	"	-0.0325	-0.052	1.8125	1.875	-0.0625
100	0.65	"	0.025	0.04	2.4625	2.5	-0.0375
101	0.6375	"	0.0125	0.02	3.1	3.125	-0.025
110	0.6125	"	-0.0125	-0.02	3.7125	3.75	-0.0375
111	0.6625	"	0.0375	0.06	4.375	4.375	0

$$|DNL|_{\max} = 0.0375 \text{ V} = 0.06 \text{ LSB}$$

$$|INL|_{\max} = 0.0625 \text{ V} = 0.1 \text{ LSB}$$

29.2

$$|DNL|_{\max} = \left| \frac{V_{REF}}{2^N} \cdot \left(\frac{\Delta R}{R} \right)_{\max} \right| \text{ (V)}$$

$$= \left(\frac{\Delta R}{R} \right)_{\max} \text{ (LSB)}$$

$$= 0.01 \text{ LSB}$$


$$|INL|_{\max} = \left| \frac{V_{REF}}{2^N} \cdot 2^{N-1} \left(\frac{\Delta R}{R} \right)_{\max} \right| \text{ (V)}$$

$$= 2^{N-1} \left(\frac{\Delta R}{R} \right)_{\max} \text{ LSB}$$

$$= 1.28 \text{ LSB}$$

The effective resolution is $8 - 2 = 6$

29.4

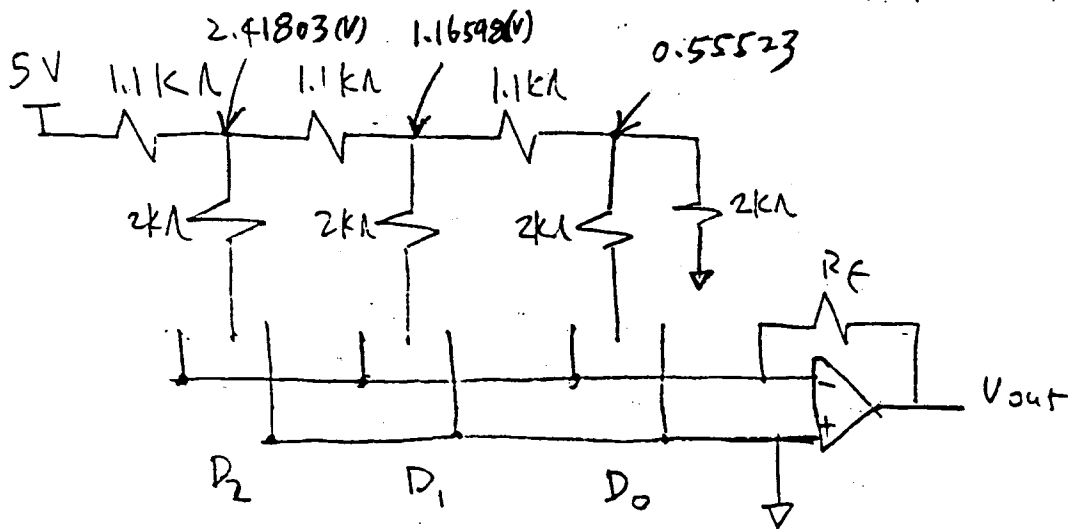

$$V_{out} = -I_{TOT} \cdot R_F$$

Digital Input			Voltage Output (V)		INL (LSB)	Step Height (V)		DN
D ₂	D ₁	D ₀	Actual	Ideal		Actual	Ideal	
0	0	0	0	0	0			
0	0	1	-0.2776 mR _F	-0.3125 mR _F	-0.11	-0.2776 mR _F	-0.3125 mR _F	-0.11
0	1	0	-0.5830 mR _F	-0.625 mR _F	-0.13	-0.3054 mR _F	"	-0.0
0	1	1	-0.8608 mR _F	-0.9375 mR _F	-0.25	-0.2778 mR _F	"	-0.11
1	0	0	-1.2090 mR _F	-1.25 mR _F	-0.13	-0.3482 mR _F	"	0.11
1	0	1	-1.4866 mR _F	-1.5625 mR _F	-0.24	-0.2776 mR _F	"	-0.11
1	1	0	-1.7920 mR _F	-1.875 mR _F	-0.27	-0.3054 mR _F	"	-0.0
1	1	1	-2.0696 mR _F	-2.1875 mR _F	-0.38	-0.2776 mR _F	"	-0.11

$$\uparrow$$

$$\frac{\text{Actual} - \text{Ideal}}{\text{}} \quad \uparrow$$

$$-0.3125 mR_F$$


$$\uparrow$$

$$-0.625 \frac{R_F}{2K}$$

$$\uparrow$$


$$\frac{\text{Actual} - \text{Ideal}}{\text{}} \quad \uparrow$$

$$-0.3125 mR_F$$

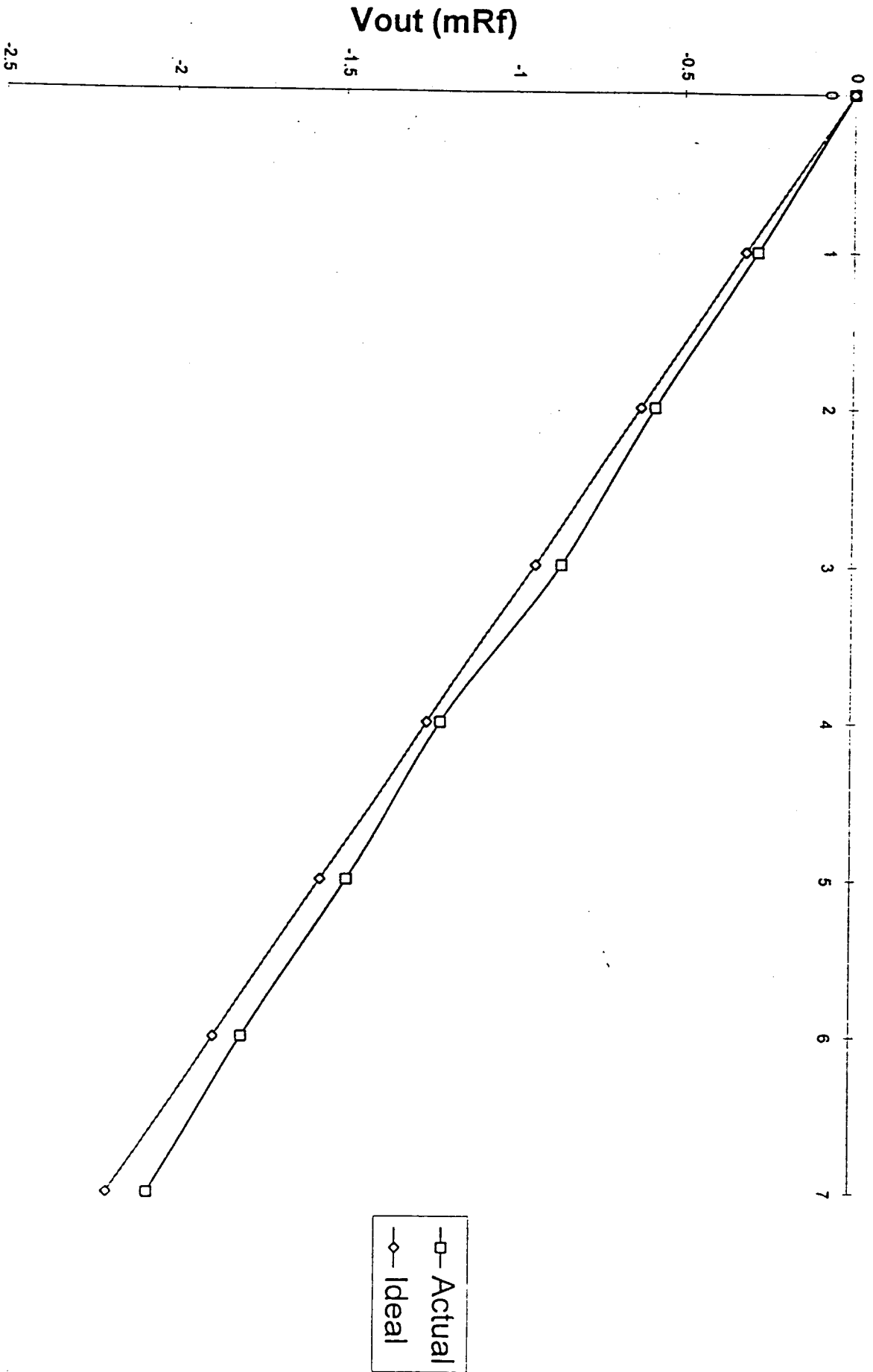


D

Prob.29.5

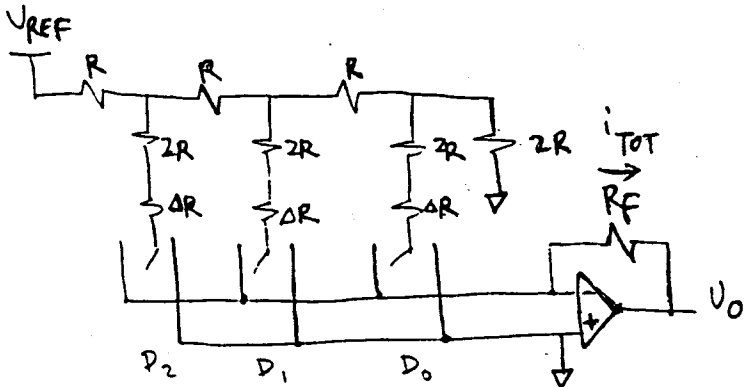

$$INL = \frac{V_{0,actual} - V_{0,ideal}}{V_{0,ideal} |_{D_2 D_1 D_0 = 001}} = \frac{(-i_{TOT,actual}) - (-i_{TOT,ideal})}{-i_{TOT,ideal} |_{D_2 D_1 D_0 = 001}} \quad (\text{LSB})$$

$$DNL = \frac{(V_{0,actual_k} - V_{0,actual_{k+1}}) - (V_{0,ideal_k} - V_{0,ideal_{k+1}})}{V_{0,ideal} |_{D_2 D_1 D_0 = 001}} = \frac{(-i_{TOT,actual_k} + i_{TOT,actual_{k+1}}) - (-i_{TOT,ideal_k} + i_{TOT,ideal_{k+1}})}{-i_{TOT,ideal} |_{D_2 D_1 D_0 = 001}} \quad (\text{LSB})$$

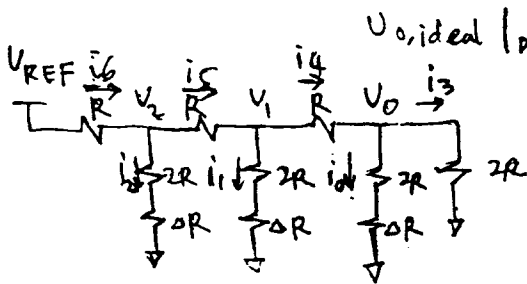

$$i_6 = i_2 + i_5 = \frac{V_{REF} - V_2}{R} = \frac{V_2 - V_1}{R} + \frac{V_2}{2R + DR} \rightarrow (2 + \frac{1}{2 + DR/R}) V_2 = V_1 + V_{REF} \quad (1)$$

$$i_3 = i_1 + i_4 = \frac{V_2 - V_1}{R} = \frac{V_1 - V_0}{R} + \frac{V_1}{2R + DR} \rightarrow (2 + \frac{1}{2 + DR/R}) V_1 = V_0 + V_2 \quad (2)$$

$$i_4 = i_0 + i_3 = \frac{V_1 - V_0}{R} = \frac{V_0}{2R} + \frac{V_0}{2R + DR} \rightarrow (1.5 + \frac{1}{2 + DR/R}) V_0 = V_1 \quad (3)$$

With Matlab, increase DR to make INL or DNL ≈ 0.5 LSB. get.

when $DR = 305 \Omega$ $|INL|_{max} = |INL_7| = 0.496 \text{ LSB}$
 $|DNL|_{max} = |DNL_4| = 0.243 \text{ LSB}$

So, $\Delta R \approx 300 \Omega$ is the upper limit to keep the DAC have 3 bit resolution

Vref := 5 DR := .305 R := 1

$$DRR := \frac{DR}{R}$$

$$\text{alfa} := 1.5 + \frac{1}{2 + DRR}$$

$$V0 := \frac{Vref}{((0.5 + \text{alfa}) \cdot ((0.5 + \text{alfa}) \cdot \text{alfa} - 1) - \text{alfa})}$$

V0 = 0.705

V1 := alfa · V0

V1 = 1.364

$$D2 := 0 \quad D1 := 0 \quad D0 := 0$$

$$iTAC0 := D0 \cdot \frac{V0}{2 \cdot R + DR} + D1 \cdot \frac{V1}{2 \cdot R + DR} + D2 \cdot \frac{V2}{2 \cdot R + DR} \quad iTAC0 = 0$$

$$iTID0 := 0$$

$$D2 := 0 \quad D1 := 0 \quad D0 := 1$$

$$iTAC1 := D0 \cdot \frac{V0}{2 \cdot R + DR} + D1 \cdot \frac{V1}{2 \cdot R + DR} + D2 \cdot \frac{V2}{2 \cdot R + DR} \quad iTAC1 = 0.306$$

$$iTID1 := .3125 \quad iLSB := iTID1$$

$$D2 := 0 \quad D1 := 1 \quad D0 := 0$$

$$iTAC2 := D0 \cdot \frac{V0}{2 \cdot R + DR} + D1 \cdot \frac{V1}{2 \cdot R + DR} + D2 \cdot \frac{V2}{2 \cdot R + DR} \quad iTAC2 = 0.592$$

$$iTID2 := .625$$

$$D2 := 0 \quad D1 := 1 \quad D0 := 1$$

$$iTAC3 := D0 \cdot \frac{V0}{2 \cdot R + DR} + D1 \cdot \frac{V1}{2 \cdot R + DR} + D2 \cdot \frac{V2}{2 \cdot R + DR} \quad iTAC3 = 0.898$$

$$iTID3 := .9375$$

$$D2 := 1 \quad D1 := 0 \quad D0 := 0$$

$$iTAC4 := D0 \cdot \frac{V0}{2 \cdot R + DR} + D1 \cdot \frac{V1}{2 \cdot R + DR} + D2 \cdot \frac{V2}{2 \cdot R + DR} \quad iTAC4 = 1.134$$

$$iTID4 := 1.25$$

$$D2 := 1 \quad D1 := 0 \quad D0 := 1$$

$$iTAC5 := D0 \cdot \frac{V0}{2 \cdot R + DR} + D1 \cdot \frac{V1}{2 \cdot R + DR} + D2 \cdot \frac{V2}{2 \cdot R + DR} \quad iTAC5 = 1.441$$

$$iTID5 := 1.5625$$

$$D2 := 1 \quad D1 := 1 \quad D0 := 0$$

$$iTAC6 := D0 \cdot \frac{V0}{2 \cdot R + DR} + D1 \cdot \frac{V1}{2 \cdot R + DR} + D2 \cdot \frac{V2}{2 \cdot R + DR} \quad iTAC6 = 1.726$$

$$iTID6 := 1.875$$

$$D2 := 1 \quad D1 := 1 \quad D0 := 1$$

$$iTAC7 := D0 \cdot \frac{V0}{2 \cdot R + DR} + D1 \cdot \frac{V1}{2 \cdot R + DR} + D2 \cdot \frac{V2}{2 \cdot R + DR} \quad iTAC7 = 2.032$$

INL and DNL

$$\text{INL}_0 := \frac{i\text{TAC}_0 - i\text{TID}_0}{i\text{LSB}}$$

$$\text{INL}_0 = 0$$

$$\text{INL}_1 := \frac{i\text{TAC}_1 - i\text{TID}_1}{i\text{LSB}}$$

$$\text{INL}_1 = -0.021$$

$$\text{INL}_2 := \frac{i\text{TAC}_2 - i\text{TID}_2}{i\text{LSB}}$$

$$\text{INL}_2 = -0.106$$

$$\text{INL}_3 := \frac{i\text{TAC}_3 - i\text{TID}_3}{i\text{LSB}}$$

$$\text{INL}_3 = -0.127$$

(LSB)

$$\text{INL}_4 := \frac{i\text{TAC}_4 - i\text{TID}_4}{i\text{LSB}}$$

$$\text{INL}_4 = -0.37$$

$$\text{INL}_5 := \frac{i\text{TAC}_5 - i\text{TID}_5}{i\text{LSB}}$$

$$\text{INL}_5 = -0.39$$

$$\text{INL}_6 := \frac{i\text{TAC}_6 - i\text{TID}_6}{i\text{LSB}}$$

$$\text{INL}_6 = -0.476$$

$$\text{INL}_7 := \frac{i\text{TAC}_7 - i\text{TID}_7}{i\text{LSB}}$$

$$\text{INL}_7 = -0.496$$

$$\text{DNL}_1 := \frac{i\text{TAC}_1 - i\text{TAC}_0 - i\text{LSB}}{i\text{LSB}}$$

$$\text{DNL}_1 = -0.021$$

$$\text{DNL}_2 := \frac{i\text{TAC}_2 - i\text{TAC}_1 - i\text{LSB}}{i\text{LSB}}$$

$$\text{DNL}_2 = -0.085$$

$$\text{DNL}_3 := \frac{i\text{TAC}_3 - i\text{TAC}_2 - i\text{LSB}}{i\text{LSB}}$$

$$\text{DNL}_3 = -0.021$$

$$\text{DNL}_4 := \frac{i\text{TAC}_4 - i\text{TAC}_3 - i\text{LSB}}{i\text{LSB}}$$

$$\text{DNL}_4 = -0.243$$

(LSB)

$$\text{DNL}_5 := \frac{i\text{TAC}_5 - i\text{TAC}_4 - i\text{LSB}}{i\text{LSB}}$$

$$\text{DNL}_5 = -0.021$$


$$\text{DNL}_6 := \frac{i\text{TAC}_6 - i\text{TAC}_5 - i\text{LSB}}{i\text{LSB}}$$

$$\text{DNL}_6 = -0.085$$

$$\text{DNL}_7 := \frac{i\text{TAC}_7 - i\text{TAC}_6 - i\text{LSB}}{i\text{LSB}}$$


$$\text{DNL}_7 = -0.021$$

29.6

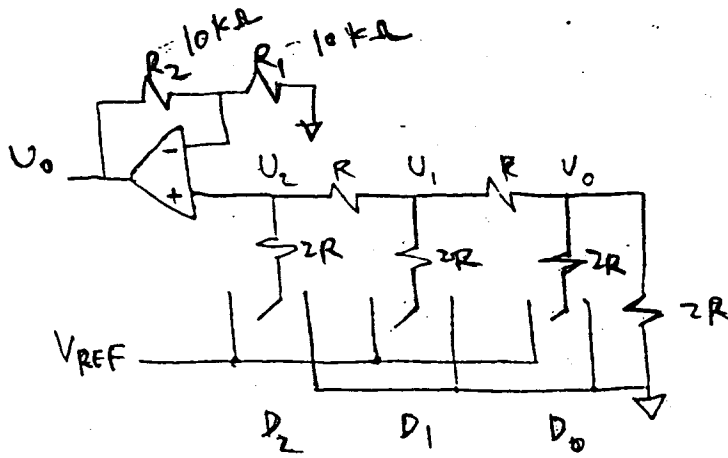

$R = 1k\Omega$
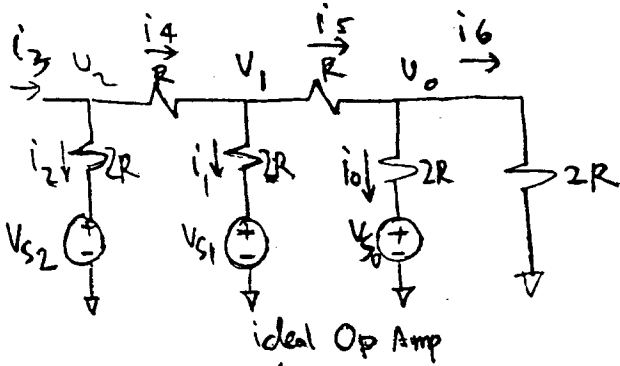
$$U_0 = \left(1 + \frac{R_2}{R_1}\right) U_2 = 2U_2$$



$$i_2 = i_2 + i_4 = 0 = \frac{U_2 - U_1}{R} + \frac{U_2 - U_{S2}}{2R} \rightarrow 1.5U_2 = U_1 + 0.5U_{S2}$$

$$i_4 = i_1 + i_5 = \frac{U_2 - U_1}{R} = \frac{U_1 - U_0}{R} + \frac{U_1 - U_{S1}}{2R} \rightarrow U_2 = 2.5U_1 - U_0 - 0.5U_{S1}$$

$$i_5 = i_0 + i_6 = \frac{U_1 - U_0}{R} = \frac{U_0}{2R} + \frac{U_0 - U_{S0}}{2R} \rightarrow U_1 = 2U_0 - 0.5U_{S0}$$

$$\Rightarrow \begin{cases} U_0 = \frac{1}{4} (0.5U_{S2} + 0.75U_{S1} + 1.375U_{S0}) \\ U_1 = 2U_0 - 0.5U_{S0} \\ U_2 = 2.5U_1 - U_0 - 0.5U_{S1} \end{cases}$$

$D_2 D_1 D_0$	U_{S2}	U_{S1}	U_{S0} (V)	U_0	U_1	U_2 (V)	$U_{out} = 2U_2$ (V)
000	0	0	0	0	0	0	0
001	0	0	5	1.719	0.938	0.625	1.25
010	0	5	0	0.938	1.875	1.25	2.5
011	0	5	5	2.656	2.813	1.85	3.75
100	5	0	0	0.625	1.25	2.5	5
101	5	0	5	2.344	2.188	3.125	6.25
110	5	5	0	1.563	3.125	3.75	7.5

Prob.29.6

D=000

$$VS2 := 0 \quad VS1 := 0 \quad VS0 := 0$$

$$V0 := \frac{1}{4} \cdot (0.5 \cdot VS2 + 0.75 \cdot VS1 + 1.375 \cdot VS0) \quad V0 = 0$$

$$V1 := 2 \cdot V0 - 0.5 \cdot VS0 \quad V1 = 0$$

$$V2 := 2.5 \cdot V1 - V0 - .5 \cdot VS1 \quad V2 = 0$$

D=001

$$VS2 := 0 \quad VS1 := 0 \quad VS0 := 5$$

$$V0 := \frac{1}{4} \cdot (0.5 \cdot VS2 + 0.75 \cdot VS1 + 1.375 \cdot VS0) \quad V0 = 1.719$$

$$V1 := 2 \cdot V0 - 0.5 \cdot VS0 \quad V1 = 0.938$$

$$V2 := 2.5 \cdot V1 - V0 - .5 \cdot VS1 \quad V2 = 0.625$$

D=010

$$VS2 := 0 \quad VS1 := 5 \quad VS0 := 0$$

$$V0 := \frac{1}{4} \cdot (0.5 \cdot VS2 + 0.75 \cdot VS1 + 1.375 \cdot VS0) \quad V0 = 0.938$$

$$V1 := 2 \cdot V0 - 0.5 \cdot VS0 \quad V1 = 1.875$$

$$V2 := 2.5 \cdot V1 - V0 - .5 \cdot VS1 \quad V2 = 1.25$$

D=011

$$VS2 := 0 \quad VS1 := 5 \quad VS0 := 5$$

$$V0 := \frac{1}{4} \cdot (0.5 \cdot VS2 + 0.75 \cdot VS1 + 1.375 \cdot VS0) \quad V0 = 2.656$$

$$V1 := 2 \cdot V0 - 0.5 \cdot VS0 \quad V1 = 2.813$$

$$V2 := 2.5 \cdot V1 - V0 - .5 \cdot VS1 \quad V2 = 1.875$$

D=100

$$VS2 := 5 \quad VS1 := 0 \quad VS0 := 0$$

$$V0 := \frac{1}{4} \cdot (0.5 \cdot VS2 + 0.75 \cdot VS1 + 1.375 \cdot VS0) \quad V0 = 0.625$$

$$V1 := 2 \cdot V0 - 0.5 \cdot VS0 \quad V1 = 1.25$$

D=101

VS2 := 5 VS1 := 0 VS0 := 5

$$V0 := \frac{1}{4} \cdot (0.5 \cdot VS2 + 0.75 \cdot VS1 + 1.375 \cdot VS0) \quad V0 = 2.344$$

$$V1 := 2 \cdot V0 - 0.5 \cdot VS0 \quad V1 = 2.188$$

$$V2 := 2.5 \cdot V1 - V0 - .5 \cdot VS1 \quad V2 = 3.125$$

D=110

VS2 := 5 VS1 := 5 VS0 := 0

$$V0 := \frac{1}{4} \cdot (0.5 \cdot VS2 + 0.75 \cdot VS1 + 1.375 \cdot VS0) \quad V0 = 1.563$$

$$V1 := 2 \cdot V0 - 0.5 \cdot VS0 \quad V1 = 3.125$$

$$V2 := 2.5 \cdot V1 - V0 - .5 \cdot VS1 \quad V2 = 3.75$$

D=111


VS2 := 5 VS1 := 5 VS0 := 5

$$V0 := \frac{1}{4} \cdot (0.5 \cdot VS2 + 0.75 \cdot VS1 + 1.375 \cdot VS0) \quad V0 = 3.281$$

$$V1 := 2 \cdot V0 - 0.5 \cdot VS0 \quad V1 = 4.063$$

$$V2 := 2.5 \cdot V1 - V0 - .5 \cdot VS1 \quad V2 = 4.375$$

29.7

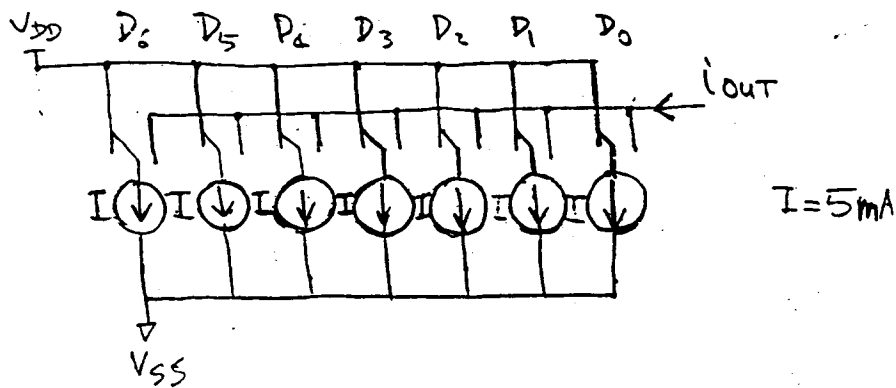

	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	i _{out}
000	0	0	0	0	0	0	0	0
001	0	0	0	0	0	0	1	I
010	0	0	0	0	0	1	1	2I
011	0	0	0	0	1	1	1	3I
100	0	0	0	1	1	1	1	4I
101	0	0	1	1	1	1	1	5I
110	0	1	1	1	1	1	1	6I
111	1	1	1	1	1	1	1	7I

29.8

for nonbinary weight current steering DAC

$$|DNL|_{max} = |\Delta I_{max}| (A) = \left(\frac{\Delta I_{max}}{I} \right) = 0.05\% \text{ (LSB) in our case}$$

$$|INL|_{max} = 2^{N-1} |\Delta I|_{max} (A) = 2^{N-1} \left(\frac{\Delta I_{max}}{I} \right) = 2^{N-1} \cdot 0.05\% \text{ (LSB) in our case}$$


$$N = \frac{\lg |INL|_{max} - \lg(0.05\%)}{\lg 2} + 1$$

Let $|INL|_{max} = 0.5 \text{ LSB}$

$$N = \frac{\lg(0.5) - \lg(0.05\%)}{\lg 2} + 1 = 10.97$$

the maximum resolution the DAC can attain using the process is 10 bit

29.9

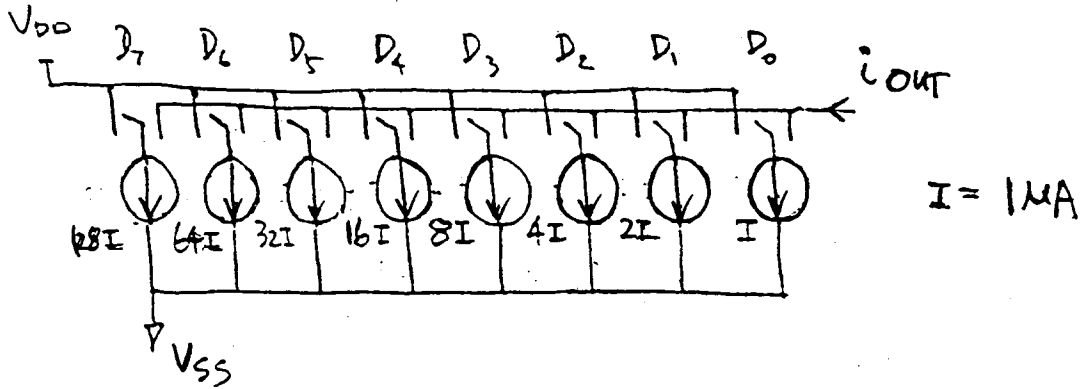

The range of values that the current source corresponding to the MS can have :

① $|INL|_{\max} \leq \frac{1}{2} \text{LSB}$

$$|\Delta I|_{\max, INL} = \frac{|INL|_{\max}}{2^{8-1}} = \frac{0.5}{2^7} = 3.906 \times 10^{-3}$$


$$I_{\text{MSB}} = 128 \pm 128 \cdot |\Delta I|_{\max, INL} = 128 \pm 0.5 \text{ mA} \quad (= 3.906 \text{ mA})$$

② $|DNL|_{\max} \leq \frac{1}{2} \text{LSB}$

$$|\Delta I|_{\max, DNL} = \frac{|DNL|_{\max}}{2^8 - 1} = \frac{0.5}{2^9 - 1} = 1.961 \times 10^{-3} \text{ LSB}$$

$$I_{\text{MSB}} = 128 \pm 128 |\Delta I|_{\max, DNL} = 128 \pm 0.25 \text{ mA} \quad (= 1.961 \text{ mA})$$

29.10

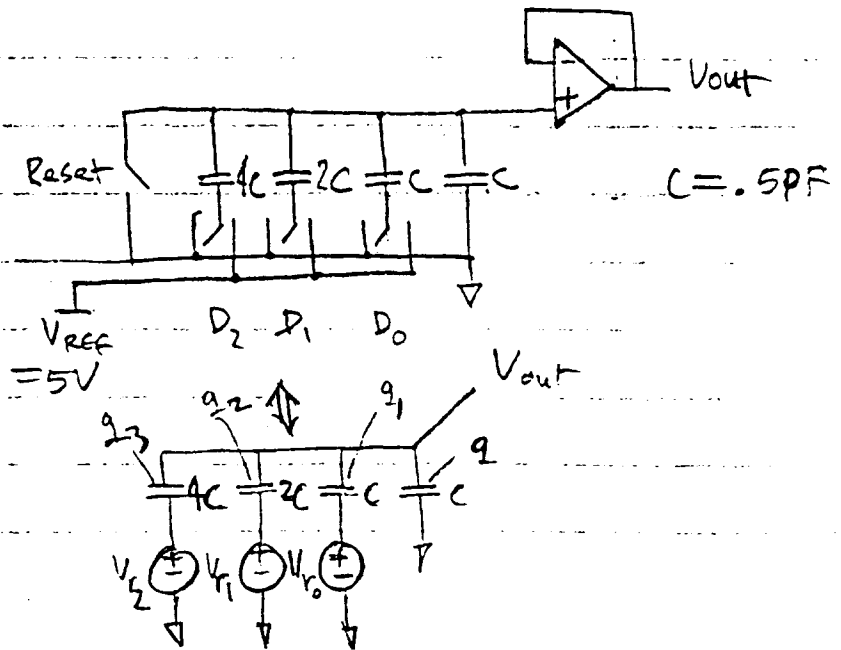


$$q_0 + q_1 + q_2 + q_3 = 0$$

$$(1+2+4+1) V_{out} = V_{r0} + 2V_{r1} + 4V_{r2}$$

$$V_{out} = \frac{1}{8} V_{r0} + \frac{1}{4} V_{r1} - \frac{1}{2} V_{r2}$$

$D_2 D_1 D_0$	$V_{r2} (V)$	$V_{r1} (V)$	$V_{r0} (V)$	$V_{out} (V)$
0 0 0	0	0	0	0
0 0 1	0	0	5	0.625
0 1 0	0	5	0	1.250
0 1 1	0	5	5	1.875
1 0 0	5	0	0	2.500
1 0 1	5	0	5	3.125
1 1 0	5	5	0	3.750
1 1 1	5	5	5	4.375


29.11 $D = 000010$
equivalent ckt:

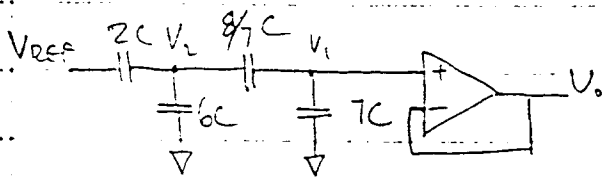

$$V_2 = \frac{2}{\left(6 + \frac{8/7 \cdot 7}{8/7 + 7}\right) + 2} V_{REF} = \frac{2}{8 + 56/57}$$

$$V_o = V_1 = \frac{8/7}{8/7 + 7} \cdot V_2 = \frac{8}{57} \cdot \frac{2}{8 + 56/57} V_{REF} = \boxed{\frac{V_{REF}}{32}}$$


$D = 001000$
equivalent ckt

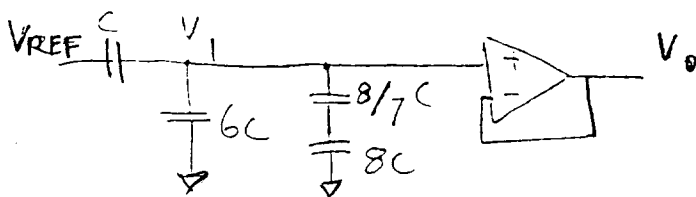

$$V_o = V_i = \frac{1}{\frac{8/7 \cdot 8}{8/7 + 8} + 6 + 1} = \boxed{\frac{V_{REF}}{8}}$$

D = 000100

equivalent CKT

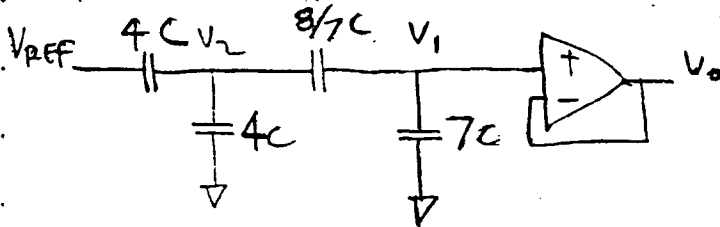


$$V_2 = \frac{4}{\left(\frac{8/7 \cdot 7}{8/7 + 7} + 4\right) + 4} V_{REF} = \frac{4}{8 + 56/57} V_{REF}$$

$$V_o = V_i = \frac{8/7}{8/7 + 7} \cdot V_2 = \frac{8}{57} \cdot \frac{4}{8 + 56/57} V_{REF} = \boxed{\frac{V_{REF}}{16}}$$


D = 0100000

equivalent CKT

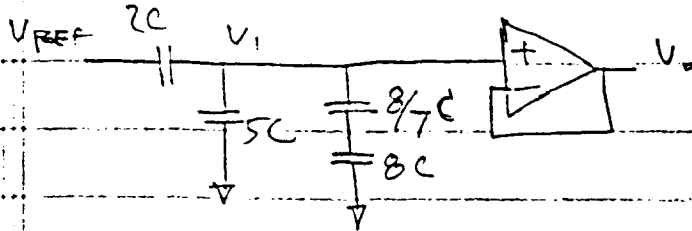


$$V_o = V_i = \frac{2C}{5 + \frac{8/7 \cdot 8}{8/7 + 8} + 2} V_{REF} = \boxed{\frac{1}{4} V_{REF}}$$

29.12

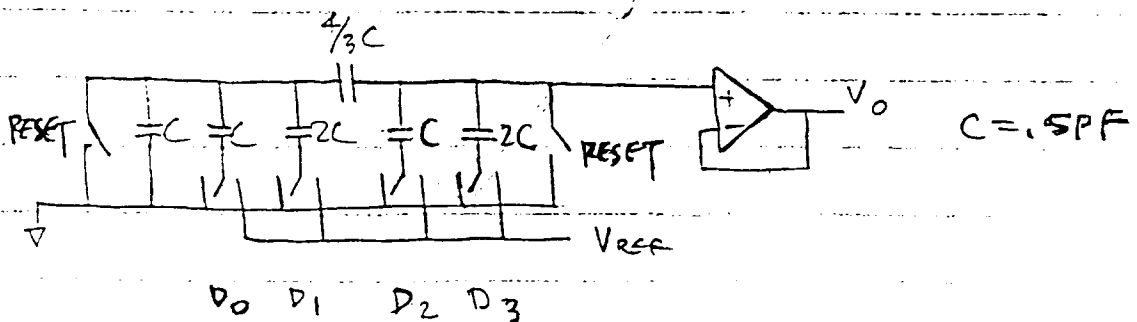


D = 0001 equivalent ckt

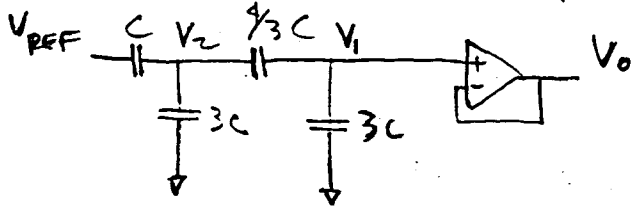

$$V_2 = \frac{1}{\left(\frac{\frac{4}{3} \cdot 3}{\frac{4}{3} + 3} + 3\right) + 1} V_{REF} = \frac{1}{4 + \frac{12}{13}} V_{REF}$$

$$V_0 = V_1 = \frac{\frac{4}{3}}{\frac{4}{3} + 3} \cdot V_2 = \frac{\frac{4}{3}}{\frac{4}{3} + 3} \cdot \frac{1}{4 + \frac{12}{13}} V_{REF} = \frac{5}{16} = \boxed{0.3125}$$


D = 0010 equivalent ckt

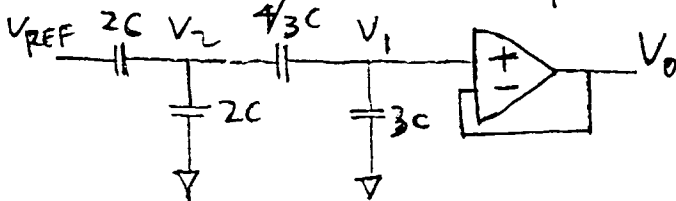

$$V_2 = \frac{2}{\left(\frac{\frac{4}{3} \cdot 3}{\frac{4}{3} + 3} + 2\right) + 2} V_{REF} = \frac{2}{4 + \frac{12}{13}} V_{REF}$$

$$V_0 = V_1 = \frac{\frac{4}{3}}{\frac{4}{3} + 3} \cdot \frac{2}{4 + \frac{12}{13}} V_{REF} = \frac{5}{8} = \boxed{0.625V}$$

D = 0100 equivalent ckt

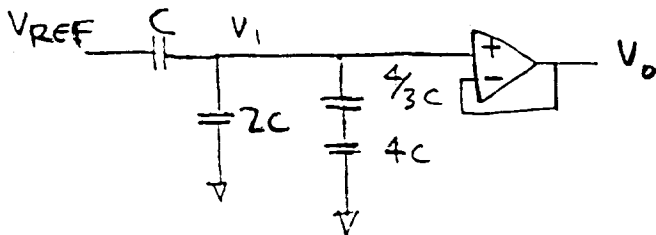


$$V_0 = V_1 = \frac{1}{\left(\frac{\frac{4}{3} \cdot 4}{\frac{4}{3} + 4} + 3\right) + 1} V_{REF} = \frac{5}{4} = \boxed{1.25V}$$

D = 1000 equivalent ckt



29.13.

Input	D2	D1	D0	Vout,ideal(v)	Vout,actual(v)	Vout,nogain(v)	INL(v)	INL(LSBs)	DNL(v)	DNL(LSBs)
0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0.625	0.455625	0.536119516	-0.08888	-0.142209	-0.08888	-0.1422088
2	0	1	0	1.25	1.0125	1.191376702	-0.058623	-0.093797	0.030257	0.0484115
3	0	1	1	1.875	1.468125	1.727496218	-0.147504	-0.236006	-0.08888	-0.1422088
4	1	0	0	2.5	2.25	2.647503782	0.147504	0.2360061	0.295008	0.4720121
5	1	0	1	3.125	2.705625	3.183623298	0.058623	0.0937973	-0.08888	-0.1422088
6	1	1	0	3.75	3.2625	3.838880484	0.08888	0.1422088	0.030257	0.0484115
7	1	1	1	4.375	3.718125	4.375	8.88E-16	1.421E-15	-0.08888	-0.1422088
MAXIMUM							0.147504	0.2360061	0.08888	0.1422088

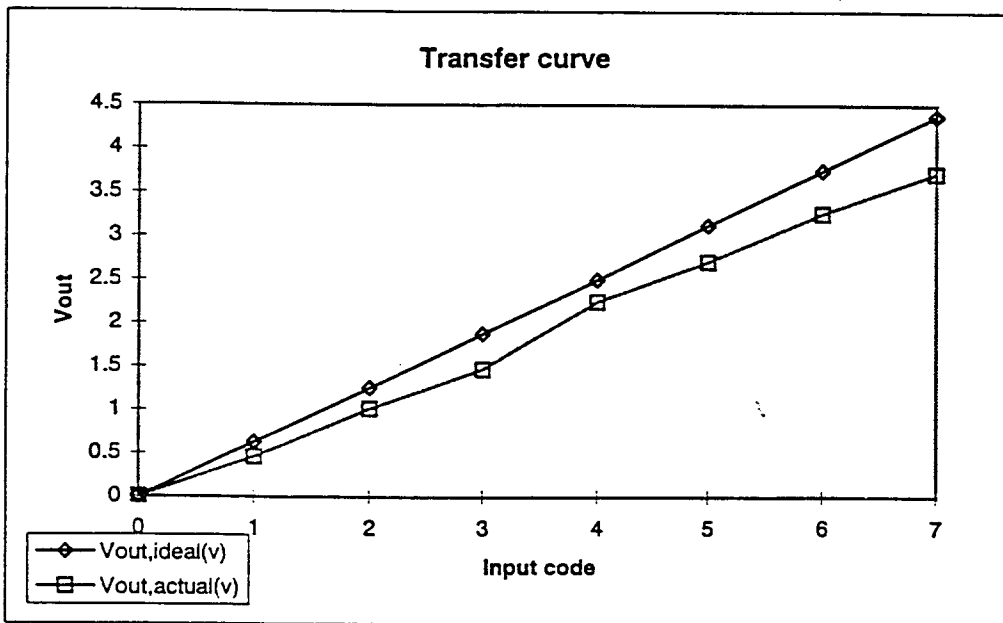

$$V_{out,actual} = V_{REF} \sum_{k=0}^M A^{N-k} \cdot D_k = V_{REF} [A \cdot D_2 + A^2 \cdot D_1 + A^1 \cdot D_0]$$

$$\text{offset} = 0$$

$$A = 0.45$$

$$\text{Gain error} = \text{Gain}_{ideal} - \text{Gain}_{actual}$$

$$= 1 - \frac{3.718125/0.625}{7} = 1 - 0.85 = 0.15 \frac{\text{LSB}}{\text{LSB}}$$

After removing offset, gain error


$$|INL|_{max} = 0.236 \text{ LSBs} = 0.1475 \text{ V}$$

$$|DNL|_{max} = 0.472 \text{ LSBs} = 0.295 \text{ V}$$

29.14

Input	D2	D1	D0	Vout,ideal(v)	Vout,actual(v)	Vout,nooff(v)	INL(v)	INL(LSBs)	DNL(v)	DNL(LSBs)
0	0	0	0	0	0.175	0	0	0	0	0
1	0	0	1	0.625	0.8	0.625	0	0	0	0
2	0	1	0	1.25	1.425	1.25	0	0	0	0
3	0	1	1	1.875	2.05	1.875	0	0	0	0
4	1	0	0	2.5	2.675	2.5	0	0	0	0
5	1	0	1	3.125	3.3	3.125	0	0	0	0
6	1	1	0	3.75	3.925	3.75	0	0	0	0
7	1	1	1	4.375	4.55	4.375	0	0	0	0
MAXIMUM							0	0	0	0

Offset=0.175v

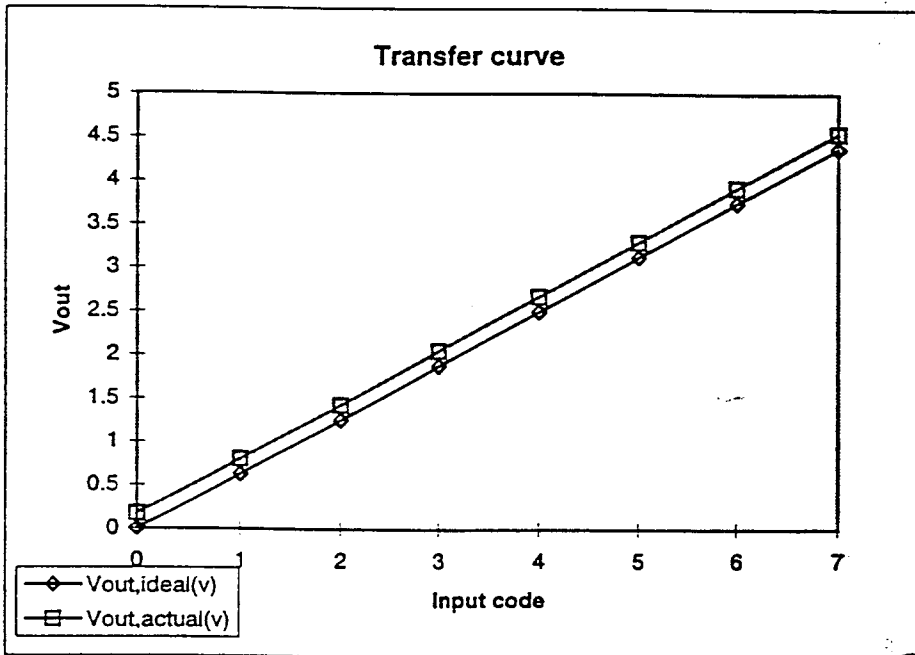

Assume: $V_{off} = 0.2V$

$$V_{out} = V_{ref} \sum_{k=0}^{M-1} A^{M-k} \cdot D_k + \sum_{k=0}^{M-1} A^{M-k} \cdot V_{off}$$

$A = 0.5$
 $V_{off} = 0.2V$

$$= V_{REF} [A \cdot D_2 + A^2 \cdot D_1 + A^3 \cdot D_0] + V_{off} [A + A^2 + A^3]$$

$$= V_{out,ideal} + 0.175V$$

offset = 0.175V

gain error = 0

After removing offset, gain error.

$$|INL|_{max} = 0$$

$$|DNL|_{max} = 0$$


29.15

Input	D2	D1	D0	Vout,ideal(v)	Vout,actual(v)	Vout,nooff(v)	Vout,nogain(v)	INL(v)	INL(LSBs)	DNL(v)	DNL(LSBs)
0	0	0	0	0	0.148725	0	0	0	0	0	0
1	0	0	1	0.625	0.60435	0.455625	0.536119516	-0.08888	-0.14221	-0.08888	-0.14221
2	0	1	0	1.25	1.161225	1.0125	1.191376702	-0.05862	-0.0938	0.030257	0.048411
3	0	1	1	1.875	1.61685	1.468125	1.727496218	-0.1475	-0.23601	-0.08888	-0.14221
4	1	0	0	2.5	2.398725	2.25	2.647503782	0.147504	0.236006	0.295008	0.472012
5	1	0	1	3.125	2.85435	2.705625	3.183623298	0.058623	0.093797	-0.08888	-0.14221
6	1	1	0	3.75	3.411225	3.2625	3.838880484	0.08888	0.142209	0.030257	0.048411
7	1	1	1	4.375	3.86685	3.718125	4.375	0	0	-0.08888	-0.14221

MAXIMUM

0.147504 0.236006 ~~0.08888~~ ~~0.142209~~
 0.295008 0.472012

Offset=0.175v

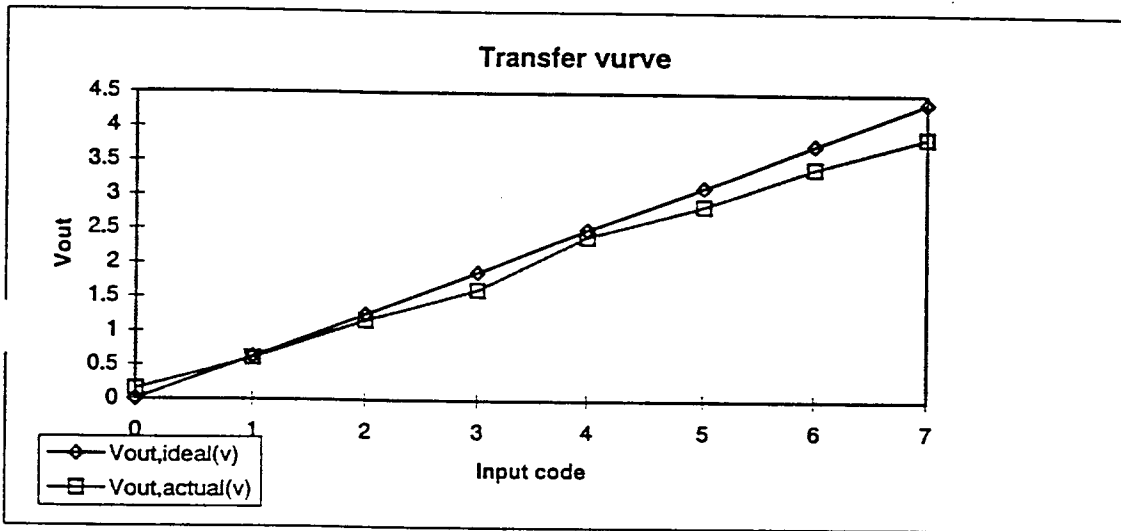

$$V_{out} = V_{ref} [A \cdot D_2 + A^2 \cdot D_1 + A^3 \cdot D_0] + V_{off} [A + A^2 + A^3]$$

$$A = 0.45$$

$$\text{offset} = 0.148725 \text{ V} = 0.23796 \text{ LSBs}$$

$$V_{off} = 0.2 \text{ V}$$


$$\text{gain error} = 1 - \frac{3.718125 / 0.625}{7} = 1 - 0.85 = 0.15 \text{ LSB/LSB}$$

after removing offset, gain error.

$$|INL|_{max} = 0.1475 \text{ V} = 0.236 \text{ LSBs}$$

$$|DNL|_{max} = 0.295 \text{ V} = 0.472 \text{ LSBs}$$

29.16.

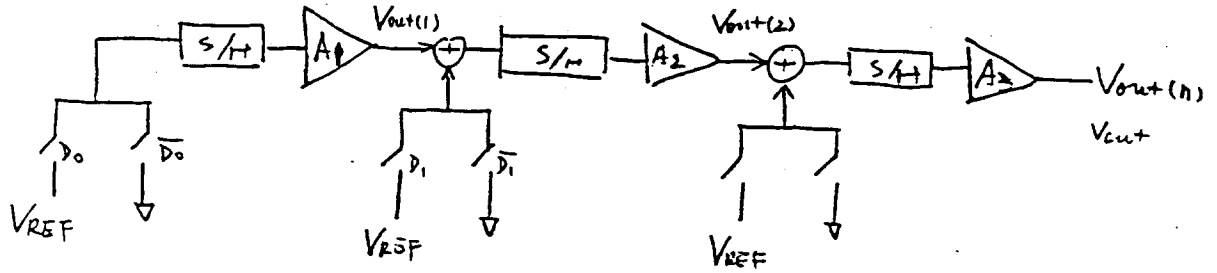

$A_{ideal} = \frac{1}{2}$, $V_{REF} = 1V$

a) $A_2 = A_3 = A_{ideal} = \frac{1}{2} = A$.

$V_{out(1)} = D_0 \cdot V_{REF} \cdot A_1$

$V_{out(2)} = (D_1 \cdot V_{REF} + D_0 \cdot V_{REF} \cdot A_1) A_2$

$V_{out(3)} = (D_2 \cdot V_{REF} + (D_1 \cdot V_{REF} + D_0 \cdot V_{REF} \cdot A_1) A_2) A_3$
 $= V_{REF} (D_0 \cdot A_1 A_2 A_3 + D_1 \cdot A_2 \cdot A_3 + D_2 \cdot A_3)$

In this case, $V_{out, actual} = V_{REF} (D_2 \cdot \frac{1}{2} + D_1 \cdot \frac{1}{4} + D_0 \cdot \frac{A_1}{4})$

Input	$V_{out, actual}$	DNL (no offset)	offset = 0
000	0	0	gain error factor = α
001	$V_{REF} (\frac{A_1}{4})$	$\alpha \cdot V_{REF} (\frac{A_1}{4}) - \frac{V_{REF}}{8}$	$\alpha = \frac{\frac{7}{8} V_{REF}}{V_{REF} (\frac{1}{2} + \frac{1}{4} + \frac{A_1}{4})} = \frac{7}{2(3+A_1)}$
010	$V_{REF} (\frac{1}{4})$	$\alpha \cdot V_{REF} (\frac{1-A_1}{4}) - \frac{V_{REF}}{8}$	
011	$V_{REF} (\frac{1}{4} + \frac{A_1}{4})$	$\alpha \cdot V_{REF} (\frac{A_1}{4}) - \frac{V_{REF}}{8}$	
100	$V_{REF} (\frac{1}{2})$	$\alpha \cdot V_{REF} (\frac{1-A_1}{4}) - \frac{V_{REF}}{8}$	
101	$V_{REF} (\frac{1}{2} + \frac{A_1}{4})$	$\alpha \cdot V_{REF} (\frac{A_1}{4}) - \frac{V_{REF}}{8}$	
110	$V_{REF} (\frac{1}{2} + \frac{1}{4})$	$\alpha \cdot V_{REF} (\frac{1-A_1}{4}) - \frac{V_{REF}}{8}$	
111	$V_{REF} (\frac{1}{2} + \frac{1}{4} + \frac{A_1}{4})$	$\alpha \cdot V_{REF} (\frac{A_1}{4}) - \frac{V_{REF}}{8}$	

Set $|DNL| \leq \frac{1}{2} LSBs = \frac{1}{2} \cdot \frac{V_{REF}}{8} = \frac{1}{16} V_{REF}$

$\left| \frac{7 \cdot A_1}{2 \cdot (3+A_1) \cdot 4} - \frac{1}{8} \right| \leq \frac{1}{16} \Rightarrow \frac{3}{13} \leq A_1 \leq \frac{9}{11}$
 $\left| \frac{7}{2 \cdot (3+A_1) \cdot 4} - \frac{1}{8} \right| \leq \frac{1}{16} \Rightarrow \frac{5}{17} \leq A_1 \leq \frac{11}{15}$
 $\Rightarrow \frac{5}{17} \leq A_1 \leq \frac{11}{15}$
 $0.294 \leq A \leq 0.733$

In order to let the DAC have $\leq \pm \frac{1}{2} LSBs$ of DNL, the gain of first stage should be:

$0.294 < A < 0.733$

$$b) \quad V_{out, actual} = V_{REF} \left(D_2 \cdot \frac{1}{2} + D_1 \cdot \frac{A_2}{2} + D_0 \cdot \frac{A_2}{4} \right)$$

Input	$V_{out, actual}$	DNL	offset = 0
000	0	0	gain error factor γ
001	$V_{REF} \left(\frac{A_2}{4} \right)$	$\gamma \cdot V_{REF} \left(\frac{A_2}{4} \right) - \frac{1}{8} V_{ref}$	$\gamma = \frac{\frac{7}{8} V_{ref}}{V_{ref} \left(\frac{1}{2} + \frac{3}{4} A_2 \right)} = \frac{7}{2(2+3A_2)}$
010	$V_{REF} \left(\frac{A_2}{2} \right)$	$\gamma \cdot V_{REF} \left(\frac{A_2}{2} \right) - \frac{1}{8} V_{ref}$	
011	$V_{REF} \left(\frac{3A_2}{4} \right)$	$\gamma \cdot V_{REF} \left(\frac{A_2}{4} \right) - \frac{1}{8} V_{ref}$	
100	$V_{REF} \left(\frac{1}{2} \right)$	$\gamma \cdot V_{REF} \left(\frac{1}{2} - \frac{3A_2}{4} \right) - \frac{1}{8} V_{ref}$	
101	$V_{REF} \left(\frac{1}{2} + \frac{A_2}{4} \right)$	$\gamma \cdot V_{REF} \left(\frac{1}{4} \right) - \frac{1}{8} V_{ref}$	
110	$V_{REF} \left(\frac{1}{2} + \frac{A_2}{2} \right)$	$\gamma \cdot V_{REF} \left(\frac{A_2}{2} \right) - \frac{1}{8} V_{ref}$	
111	$V_{REF} \left(\frac{1}{2} + \frac{3A_2}{4} \right)$	$\gamma \cdot V_{REF} \left(\frac{A_2}{4} \right) - \frac{1}{8} V_{ref}$	

$$\text{Set } |DNL| \leq \frac{1}{16} V_{REF}$$

$$\left. \begin{aligned} \left| \frac{7}{2(2+3A_2)} \left(\frac{A_2}{4} \right) - \frac{1}{8} \right| &\leq \frac{1}{16} \Rightarrow \frac{2}{11} A_2 \leq \frac{6}{5} \\ \left| \frac{7}{2(2+3A_2)} \left(\frac{1}{2} - \frac{3A_2}{4} \right) - \frac{1}{8} \right| &\leq \frac{1}{16} \Rightarrow \frac{22}{51} A_2 \leq \frac{26}{45} \end{aligned} \right\} \Rightarrow \frac{22}{51} A_2 \leq \frac{26}{45}$$

$$\boxed{0.4314 \leq A_2 \leq 0.5778}$$

$$c) \quad V_{out, actual} = V_{REF} \left(D_2 \cdot A_3 + D_1 \cdot \frac{A_3}{2} + D_0 \cdot \frac{A_3}{4} \right)$$

Input	$V_{out, actual}$	DNL	offset = 0
000	0	0	gain error factor γ
001	$V_{REF} \left(\frac{A_3}{4} \right)$	$\gamma \cdot V_{REF} \left(\frac{A_3}{4} \right) - \frac{1}{8} V_{ref}$	$\gamma = \frac{\frac{7}{8} V_{ref}}{V_{ref} \left(\frac{7}{8} A_3 \right)} = \frac{1}{2A_3}$
010	$V_{REF} \left(\frac{A_3}{2} \right)$	$\gamma \cdot V_{REF} \left(\frac{A_3}{2} \right) - \frac{1}{8} V_{ref}$	
011	$V_{REF} \left(\frac{3A_3}{4} \right)$	$\gamma \cdot V_{REF} \left(\frac{A_3}{4} \right) - \frac{1}{8} V_{ref}$	
100	$V_{REF} \left(A_3 \right)$	$\gamma \cdot V_{REF} \left(\frac{3A_3}{4} \right) - \frac{1}{8} V_{ref}$	
101	$V_{REF} \left(\frac{5A_3}{4} \right)$	$\gamma \cdot V_{REF} \left(\frac{1}{4} A_3 \right) - \frac{1}{8} V_{ref}$	
110	$V_{REF} \left(\frac{6A_3}{4} \right)$	$\gamma \cdot V_{REF} \left(\frac{A_3}{2} \right) - \frac{1}{8} V_{ref}$	
111	$V_{REF} \left(\frac{7A_3}{4} \right)$	$\gamma \cdot V_{REF} \left(\frac{A_3}{4} \right) - \frac{1}{8} V_{ref}$	

$$\text{Set } |DNL| \leq \frac{1}{16} V_{REF}$$

$$\left| \frac{1}{2A_3} \cdot \frac{A_3}{4} - \frac{1}{8} \right| = |0| \leq \frac{1}{16} V_{ref}$$

In this case, no restriction for A_3 but there will be gain error

29.17 a) $V_{\text{off}} = 0.25$ $A_1 = A_2 = A_3 = A = \frac{1}{2}$

$$V_{\text{out}1} = (D_0 \cdot V_{\text{REF}} + V_{\text{off}}) A_1$$

$$V_{\text{out}2} = (D_1 \cdot V_{\text{REF}} + (D_0 \cdot V_{\text{REF}} + V_{\text{off}}) \cdot A_1) A_2$$

$$V_{\text{out}3} = (D_2 \cdot V_{\text{REF}} + (D_1 \cdot V_{\text{REF}} + (D_0 \cdot V_{\text{REF}} + V_{\text{off}}) A_1) A_2) A_3$$

$$= V_{\text{REF}} (D_2 \cdot A_3 + D_1 \cdot A_2 \cdot A_3 + D_0 \cdot A_1 \cdot A_2 \cdot A_3) + V_{\text{off}} \cdot A_1 \cdot A_2 \cdot A_3$$

$$= V_{\text{REF}} (D_2 \cdot A + D_1 \cdot A^2 + D_0 \cdot A^3) + 0.03125 \text{V} = V_{i, \text{ideal}} + 0.5125 \text{V}$$

offset = $0.03125 \text{V} = 0.05 \text{ LSBs}$

After removing offset. $V_{\text{out, no offset}} = V_{i, \text{ideal}}$

$$|INL|_{\text{max}} = 0$$

$$|DNL|_{\text{max}} = 0$$

b) $V_{\text{out}} = V_{\text{REF}} (D_2 \cdot A + D_1 \cdot A^2 + D_0 \cdot A^3) + V_{\text{off}} \cdot A_2 \cdot A_3$

$$= V_{i, \text{ideal}} + 0.0625 \text{V}$$

offset = $0.0625 \text{V} = 0.1 \text{ LSBs}$

$$|INL|_{\text{max}} = 0, \quad |DNL|_{\text{max}} = 0$$

c) $V_{\text{out}} = V_{\text{REF}} (D_2 \cdot A + D_1 \cdot A^2 + D_0 \cdot A^3) + V_{\text{off}} \cdot A_3$


$$= V_{i, \text{ideal}} + 0.125 \text{V}$$

offset = $0.125 \text{V} = 0.2 \text{ LSBs}$

$$|INL|_{\text{max}} = 0 \quad |DNL|_{\text{max}} = 0$$

29.18

3-bit flash ADC

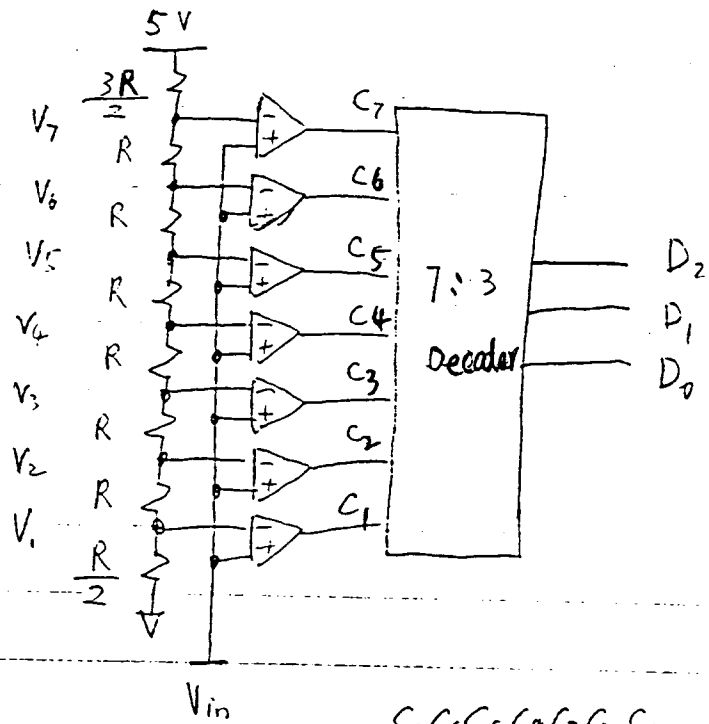

V_{in}	$C_7, C_6, C_5, C_4, C_3, C_2, C_1$	D_2, D_1, D_0
$0 \leq V_{in} < 0.3125$	0000000	000
$0.3125 \leq V_{in} < 0.9375$	0000001	001
$0.9375 \leq V_{in} < 1.5625$	0000011	010
$1.5625 \leq V_{in} < 2.1875$	0000111	011
$2.1875 \leq V_{in} < 2.8125$	0001111	100
$2.8125 \leq V_{in} < 3.4375$	0011111	101
$3.4375 \leq V_{in} < 4.0625$	0111111	110
$4.0625 \leq V_{in}$	1111111	111

$$|DNL|_{max} = \frac{5V}{8} \times 0.05 = 31.25 mV = 0.05 \text{ LSB}$$

$$|INL|_{max} = \frac{5}{2} \times 0.05 = 125 mV = 0.2 \text{ LSB}$$


2

29.19 $1LSB = \frac{5}{8} V = 625 mV$

$$|DNL|_{max} = \frac{V_{REF}}{2^N} \left| \frac{\Delta R}{R} \right|_{max} + 2 |V_{OS}|_{max} \leq \frac{625 mV}{2}$$

$$\therefore |V_{OS}|_{max} \leq \frac{(625 mV - 31.25 mV)}{2} = \boxed{140.625 mV}$$

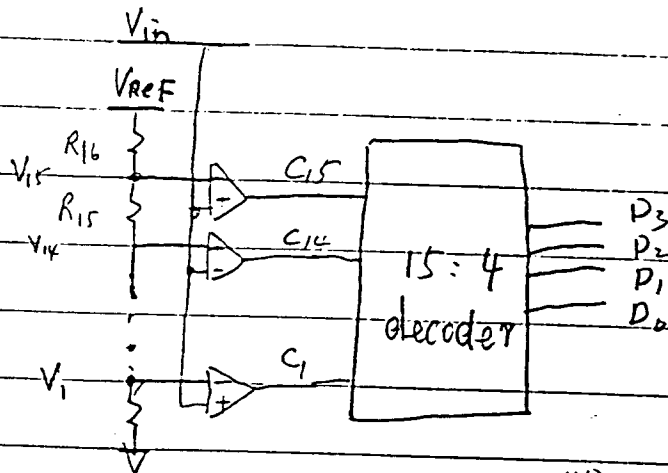29.20 $\sum_{i=1}^{16} \left(\frac{\Delta R}{R} \right)_i = (2 + 1.5 + 0 - 1 - 0.5 + 1 + 1.5 + 3 + 2.5 + 1 - 0.5 - 1.5 - 2 + 0 + 1 + 1) \% = 8 \% \neq 0$



n	R	$V_n (V)$	$V_{n,ideal} (V)$	$V_n, no-of (V)$	$V_n, multilevel (V)$	INL(mv)	DNL(mv)
1	1.02	0.317	0.3125	0.3125	0.31290	0.4	0.6
2	1.015	0.633	0.625	0.625	0.6293	4.3	3.9
3	1	0.944	0.9375	0.9395	0.9407	3.2	-1.1
4	0.99	1.252	1.2500	1.2475	1.2491	0.9	-4.1
5	0.995	1.561	1.5625	1.5565	1.5585	-4.0	-3.1
6	1.01	1.875	1.8750	1.8705	1.8729	-2.1	-1.9
7	1.015	2.191	2.1875	2.1865	2.1893	-1.8	-2.5
8	1.02	2.508	2.5000	2.5035	2.5067	-6.7	4.9
9	1.025	2.826	2.8125	2.8215	2.8251	12.6	4.9
10	1.01	3.141	3.1250	3.1365	3.1405	15.5	2.9
11	0.995	3.450	3.4375	3.4455	3.4499	12.4	-3.1
12	0.985	3.756	3.7500	3.7515	3.7563	-6.3	-6.1
13	0.98	4.061	4.0625	4.0565	4.0617	-0.8	-7.1
14	1	4.372	4.3725	4.3675	4.3731	-0.6	-1.1
15	1.01	4.686	4.6875	4.6815	4.6875	0	1.0

3


$$|INL|_{max} = 15.5 \text{ mV} \leq \frac{5}{2^{N+1}}$$

$$N = \log_2 \left(\frac{5}{15.5 \times 10^{-3}} \right) - 1 = 7.333 \approx 7$$

This converter possesses 7-bit resolution

29.21

$$A_{CL} \approx \frac{1}{\beta} = 2^{N/2} \quad |A_{OL}| \geq \frac{2^{N+1}}{\beta} = 2^{\frac{3N}{2}+1}$$

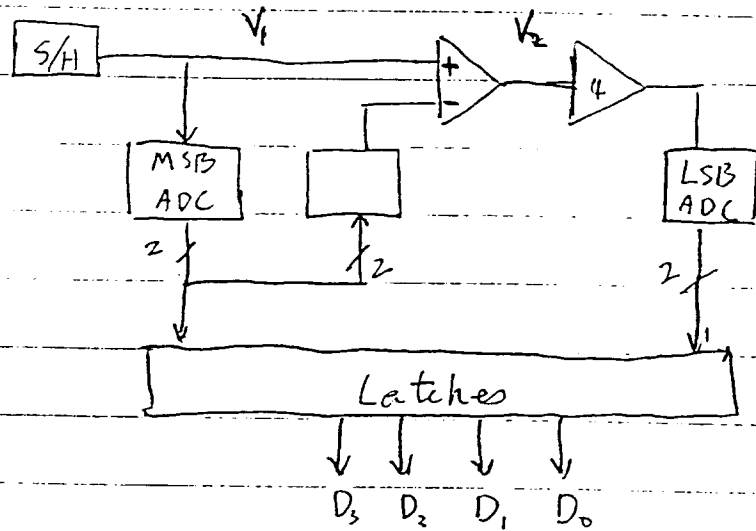

$$|A_{OL}| = \frac{1}{\beta} (2^{N+1} + 1) \geq \frac{2^{N+1}}{\beta}$$


(a) For $N=4$ $|A_{OL}| \geq 2^7 = 128$

(b) For $N=8$ $|A_{OL}| \geq 2^{13} = 8192$

(c) For $N=10$ $|A_{OL}| \geq 2^{16} = 65536$

29.22

4-bit, two step flash ADC

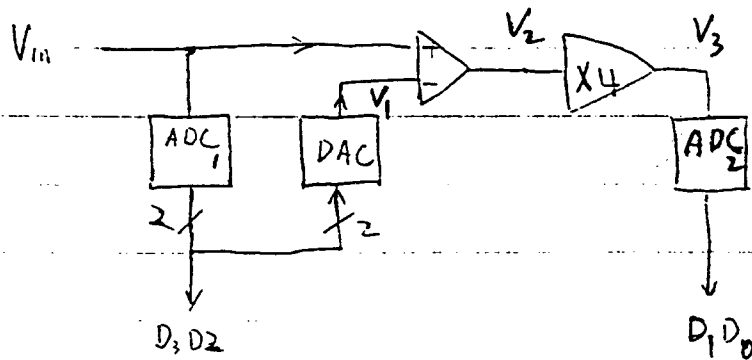

If ADC_2 has an accuracy of $\frac{1}{2^{N_2}}$

$$\Delta V_3 = \frac{V_{REF}}{2^{N_2+1}} \quad \Delta V_2 = \frac{\Delta V_3}{4} = \frac{V_{REF}}{2^{N_2+3}}$$

Assume ADC_1 is ideal, then

$$\Delta V_{in} = \Delta V_2 = \frac{V_{REF}}{2^{N_2+3}} \leq \frac{V_{REF}}{2^{4+1}} \Rightarrow N_2 \geq 2$$

So ADC_2 has 2-bit accuracy at least.

If ADC_1 has an accuracy of $\frac{1}{2^{N_1}}$

$$\Delta V_{in} = \Delta V_1 = \frac{V_{REF}}{2^{N_1+1}} = \Delta V_2 \Rightarrow \Delta V_3 = \frac{4 V_{REF}}{2^{N_1+1}} \leq \frac{V_{REF}}{2^{2+1}}$$

$$\Rightarrow N_1 = 4$$


So ADC_1 has 4-bit accuracy at least.

∴ The first flash converter needs to be more accurate than the second one


(5)

29.23. $V_{in} = 3, 5, 7.5, 14.75V$

V_{in}	V_1	V_2	V_3	$D_3 D_2 D_1 D_0$
3	0	3	12	0011
5	4	1	4	0101
7.5	4	3.5	14	0111
14.75	12	2.75	11	1110

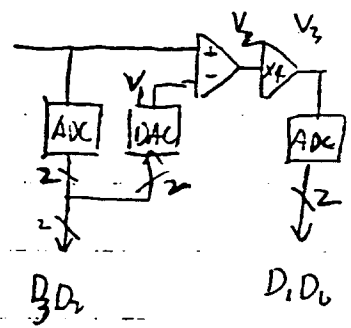

29.24 $V_{REF} = 8V$

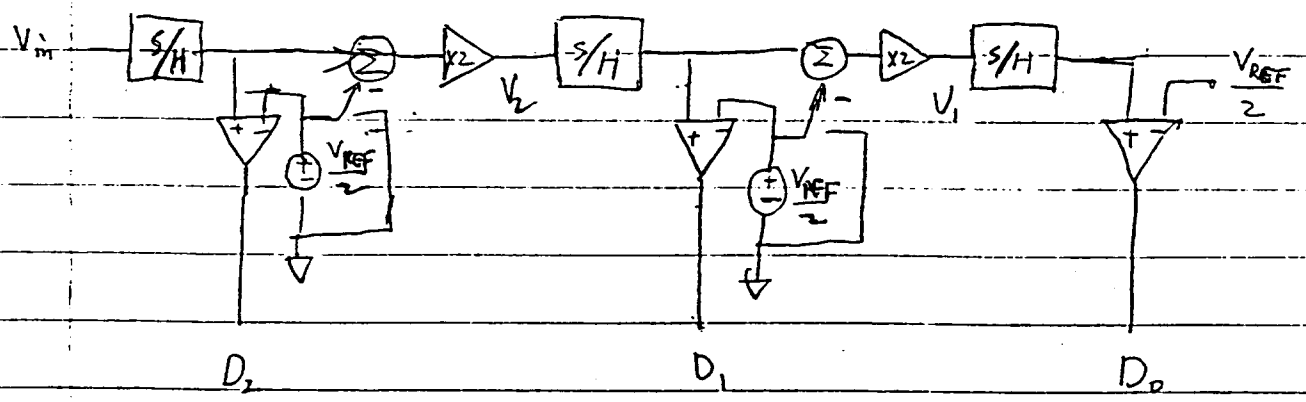

V_{in}	V_2	V_1	$D_2 D_1 D_0$
1	2	4	0 0 1
4	0	0	1 0 0
6	4	0	1 1 0
7	6	4	1 1 1

29.25

For 8 bits, it is best to write a program that generates the transfer curve, for increasing values of V_{IN} . INL & DNL can be determined from the resulting data.

29.26

Use eqs. 29.61, 29.62 & 29.63 to calculate the values of V_{IN} that cause the digital output to change.

For a 3 bit pipeline, there are only two residue amplifiers.

When the 1st residue amp. has a gain of 2.2 the new switch points occur at

$$V_{IN,1} = 2.5V$$

$$V_{p2} = 2.5V = \left[V_{IN} - \frac{1}{2} D_{N-1} \cdot V_{REF} \right] \cdot 2.2$$

gain of 1st residue amp.

$$\text{or } V_{IN} = \frac{2.5}{2.2} + \frac{1}{2} D_{N-1} \cdot V_{REF}$$

MSB
where $D_{N-1} = D_2$ & can be either 0 or 1.

$\therefore D_1$ switches when

$$V_{IN} = 1.136V, 3.636V$$

$$\text{since } V_{p3} = 2.5 = \left[\left[V_{IN} - \frac{1}{2} \cdot D_2 \cdot V_{REF} \right] A_2 - \left[\frac{1}{2} \cdot D_1 \cdot V_{REF} \right] A_1 \right]$$

gain of 1st residue amp. gain of the 2nd residue amp.

$\therefore D_0$ switches when

$$V_{IN} = \frac{\frac{2.5}{2} + 2.5 D_1}{2.2} + 2.5 D_2$$

for $D_2 D_1$ 4 combinations

$$\text{or } V_{IN} = 0.5682, 3.068, 1.7045, 4.2045$$

29.26 cont.

\therefore when A_2 (the 1st residue amp) has a gain of 2.2, V_{IN} switches at:

$A_2=2.2$		Ideal	DNL (V)	INL (V)
0	000	0		
0.5682	001	0.625	-0.0568	-0.0568
1.136	010	1.25	-0.0572	-0.114
1.7045	011	1.875	-0.0565	-0.1705
2.5	100	2.5	0	0
3.068	101	3.125	-0.057	-0.057
3.6364	110	3.75	-0.0566	-0.1136
4.2045	111	4.375	-0.0569	-0.1705

INL + DNL can be calculated by comparing the new switching pts to the ideal case, as see above.

Now perform same analysis using $A_1 = 2.2$, while $A_2 = 2.0$. This yields,

$$V_{IN} = \frac{\frac{2.5}{2.2} + 2.5 D_1}{2.0} + 2.5 D_2 \quad \text{or}$$

$$V_{IN} = 0.5682, 1.818, 3.0682, 4.3182$$

Note that since the 1st residue is now ideal (gain of 2), all the other switching points are ideal (eq. 29.63, 29.61)

$A_1 = 2.2$ yields the following switch points,

V_{IN}	DNL	INL
0	-	0
0.5682	-0.0568	-0.0568
1.25	0.0568	0
1.818	-0.057	-0.057
2.5	0.057	0
3.0682	-0.0568	-0.0568
3.75	0.0568	0
4.3182	-0.0568	-0.0568

Compare these values to the previous case shows both DNL + INL are improved!

29.27

$t_c(\text{max}) \Rightarrow$ occurs when $V_{in} = V_{FS}$

\therefore eqs. (29.8) and (29.79)

$$\begin{aligned} t_c &= \frac{V_{FS}}{V_{REF}} \cdot 2^N \cdot T_{CLK} \\ &= \frac{2^N - 1}{2^N} \cdot \frac{V_{REF}}{V_{REF}} \cdot 2^N \cdot T_{CLK} \\ &= (255)(1\mu\text{s}) = 255\mu\text{s}. \end{aligned}$$

eq. (29.80) $f_{\text{max}} = \frac{f_{\text{sample}}}{2} = \frac{V_{REF}}{V_{FS} \cdot 2^{NH}} \cdot 1\text{MHz} = \frac{1\text{MHz}}{510} = \underline{\underline{1.96\text{ kHz}}}$!

$$V_{\text{max}} = V_{FS} = \frac{255}{256} \cdot V_{REF} = \underline{\underline{4.98\text{ V}}}$$

29.28

eq. (29.81) $\Rightarrow V_C = \frac{V_{REF} \cdot t_c}{RC}$

since the conversion time, t_c , is dependent on the value of V_{in} , for the worst case of $V_{in} = V_{FS} = V_C$

$$V_{C(\text{ideal})} = \frac{V_{REF} \cdot (2^N - 1) T_{CLK}}{RC} = \frac{2^N - 1}{2^N} V_{REF}$$

\therefore The RC time constant must be:

$$RC = 2^N T_{CLK} = \underline{\underline{256\mu\text{s}}}$$

Tolerance on clock (Assume $V_{in} = 2.5\text{ V}$ worst-case)

$$\begin{aligned} V_{C,\text{ideal}} &= 2.5\text{ V} \\ \text{for } \frac{1}{2} \text{ LSB INL, } V_{C,\text{actual}} - 2.5 &= \frac{5}{2^9} = \pm 9.765\text{ mV} \\ \text{or } V_{C,\text{actual}} &= 2.5 \pm 9.765\text{ mV} \quad \& \quad f_{\text{clk}} = \frac{2^N \cdot 2.5}{V_{C,\text{actual}} \cdot RC} \quad (29.82) \\ &+ 996.11\text{ kHz} \leq f_{\text{clk}} \leq 1.0389\text{ MHz} \end{aligned}$$

29.29

Max Conversion time:

1st integration takes 2^N clock cycles

2nd integration takes $2^N - 1$ maximum clock cycles. (when $V_{IN} = V_{FS}$)

\therefore Max conversion time is,

$$t_{c(max)} = (2^N + 2^N - 1) \mu s \text{ or } 511 \mu s$$

Minimum conversion time still requires the

1st integration of 2^N clock cycles

If $V_{IN} = 0$, then $t_{c(min)} = 256 \mu s$

For $V_{IN} = 2.5 \text{ V}$,

$$t_c = 2^N + \frac{1}{2} (2^N) = 256 + 128 = \underline{\underline{384 \mu s}}$$

\uparrow 1st int. \uparrow 2nd

$\swarrow \frac{V_{IN}}{V_{REF}}$

29.30

Advantages: Dual slope removes nonidealities of R, C, & F_{CLK}

so is the more accurate of two converters

Disadvantage: The first integration can be considered as a calibration

phase which requires a hefty 2^N clock cycle overhead for each conversion.

29.31

$$V_{REF} = 5V, \quad V_{IN} = 1V$$

Step	$B_3 B_2 B_1 B_0$	$D_3' D_2' D_1' D_0'$	V_{OUT}	Comp-Out	$D_3 D_2 D_1 D_0$
1	1000	1000	$\frac{1}{2} V_{REF} = 2.5V$	1	0000
2	0100	0100	$\frac{1}{4} V_{REF} = 1.25V$	1	0000
3	0010	0010	$\frac{1}{8} V_{REF} = 0.625V$	0	0010
4	0001	0011	$\frac{3}{16} V_{REF} = 0.9375V$	0	0011

$$V_{IN} = 3V$$

Step	$B_3 B_2 B_1 B_0$	$D_3' D_2' D_1' D_0'$	V_{OUT}	Comp-Out	$D_3 D_2 D_1 D_0$
1	1000	1000	2.5V	0	1000
2	0100	1100	3.75V	1	1000
3	0010	1010	3.125V	1	1000
4	0001	1001	2.8125V	0	1001

$$V_{IN} = V_{FS} = 4.6875$$

Step	$B_3 B_2 B_1 B_0$	$D_3' D_2' D_1' D_0'$	V_{OUT}	Comp-Out	$D_3 D_2 D_1 D_0$
1	1000	1000	2.5V	0	1000
2	0100	1100	3.75V	0	1100
3	0010	1110	4.375V	0	1110
4	0011	1111	4.6875V	0	1111

29.32

Refer to Fig. 29.36 This problem refers to the 4bit ADC used in P29.31

$$V_{IN} = 2.49$$

Because of offset, Comp-out = 0 (wrong decision)

step	$D_3 D_2 D_1 D_0$	V_{out}	Comp-out	$D_3 D_2 D_1 D_0$
1	1 0 0 0	2.5V	0	1 0 0 0
2	1 1 0 0	3.75V	1	1 0 0 0
3	1 0 1 0	3.125V	1	1 0 0 0
4	1 0 0 1	2.8125V	1	1 0 0 0

The answer should be 0111


$$V_{IN} = 0.3625$$

step	$D_3 D_2 D_1 D_0$	V_{out}	Comp-out	$D_3 D_2 D_1 D_0$
1	1 0 0 0	2.5	1	0 0 0 0
2	0 1 0 0	1.25	1	0 0 0 0
3	0 0 1 0	0.625	1	0 0 0 0
4	0 0 0 1	0.3125	0	0 0 0 1


The answer should be 0000 since

$$V_{IN} < 1 \text{ LSB!}$$


29.33

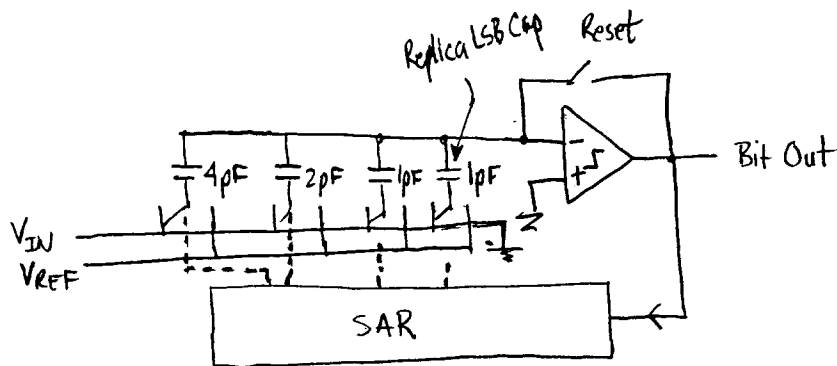


Sampling

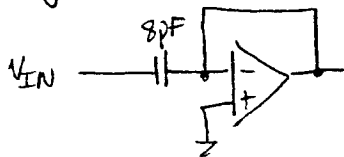


MSB (D_2 Comparison)

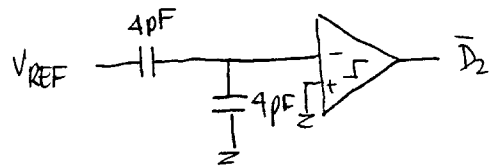

D_1 Comparison ($D_2 = 0$)

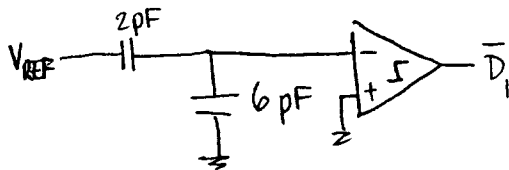

D_0 Comparison ($D_2 + D_1 = 0$)

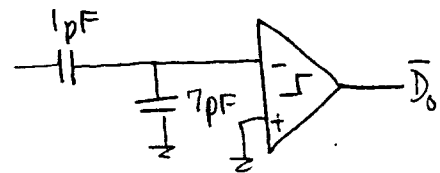

Note that after sampling, the bottom plate of the replica LSB capacitor always stays on ground.

For $V_{IN} = 2V$,

Step	$D_2 D_1 D_0$	V_{TOP}
1	000	-2V
2	010	$-2V + \frac{V_{REF}}{4} = -0.75V$
3	011	$-2V + \frac{V_{REF}}{4} + \frac{V_{REF}}{8} = -0.125V$

see eq. (29.89)

29.33 (Cont)

For $V_{IN} = 3V$

Step	$D_2 D_1 D_0$	V_{TOP}
1	1 0 0	$-3 + \frac{V_{REF}}{2} = -0.5$
2	1 0 0	$-0.5V$
3	1 0 0	$-0.5V$

For $V_{IN} = 4V$

Step	$D_2 D_1 D_0$	V_{TOP}
1	1 0 0	$-3 + \frac{V_{REF}}{2} = -0.5$
2	1 1 0	$-3 + \frac{V_{REF}}{2} + \frac{V_{REF}}{4} = -0.25V$
3	1 1 0	$-0.25V$

Note that once V_{TOP} is within $\pm 1LSB$, that the converted digital output doesn't change.

29.34

$$\text{eq. (29.91)} \quad \text{INL}_{\text{max}} = 4 \cdot (0.01) = \underline{\underline{0.04}}$$

$$\text{eq. (29.93)} \quad \text{DNL}_{\text{max}} = (7)(0.01) = \underline{\underline{0.07}}$$

Note that the INL & DNL are independent of the absolute size of the capacitor.

29.35

See problem 29.33


If $V_{OS} = 0.3$ Then, for $V_{IN} = 2.0V$

Step	D_2	D_1	D_0	V_{TOP}
1	0	0	0	$-2 + 0.3 = -1.7V$
2	0	1	0	$-2 + \frac{V_{REF}}{4} + 0.3 = -0.45$
3	0	1	1	$-2 + \frac{V_{REF}}{4} + \frac{V_{REF}}{8} + 0.3 = 0.175$

Even though V_{TOP} is now positive, because of the comparator's offset, the output stays the same. The comparator doesn't switch states until the plus input is 0.3V above ground.

29.36 See sec. 29.2.6

Problem 29.38

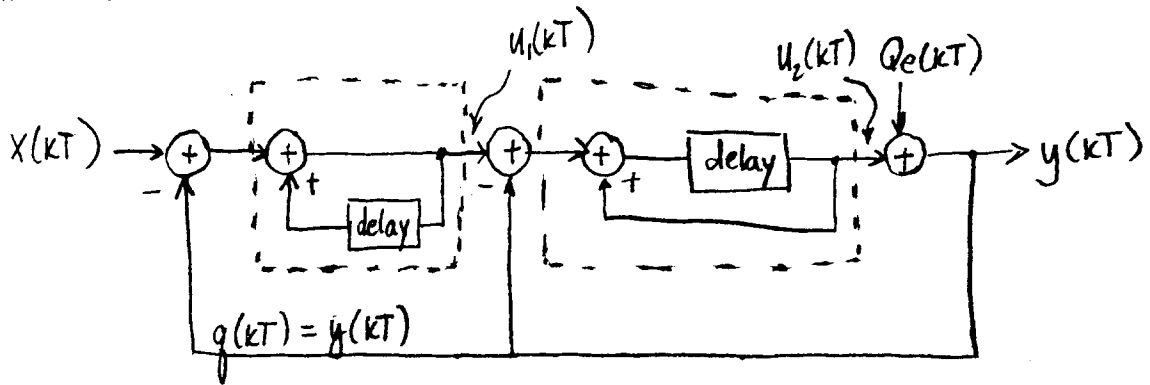

$$1.) u_2(kT) = u_1(kT-T) - y(kT-T) + u_2(kT-T)$$

$$2.) u_1(kT) = X(kT) - y(kT) + u_1(kT-T)$$

$$3.) = 2.) \rightarrow 1.) \quad u_2(kT) = X(kT-T) - y(kT-T) + u_1(kT-2T) - \underbrace{y(kT-T)}_{-Q_e(kT-T)} + u_2(kT-T)$$

$$4.) y(kT) = Q_e(kT) + u_2(kT)$$

plugging 3.) \rightarrow 4.) $= X(kT-T) - y(kT-T) + u_1(kT-2T) + Q_e(kT) - Q_e(kT-T)$

from 1), we know

$$u_1(kT-2T) = u_2(kT-T) + y(kT-2T) - u_2(kT-2T)$$

+ 4.) becomes,

$$y(kT) = X(kT-T) - \underbrace{y(kT-T)}_{-Q_e(kT-T)} + u_2(kT-T) + \underbrace{y(kT-2T) - u_2(kT-2T)}_{Q_e(kT-2T)} + Q_e(kT) - Q_e(kT-T)$$

$$\therefore y(kT) = X(kT-T) + Q_e(kT) - 2Q_e(kT-T) + Q_e(kT-2T)$$