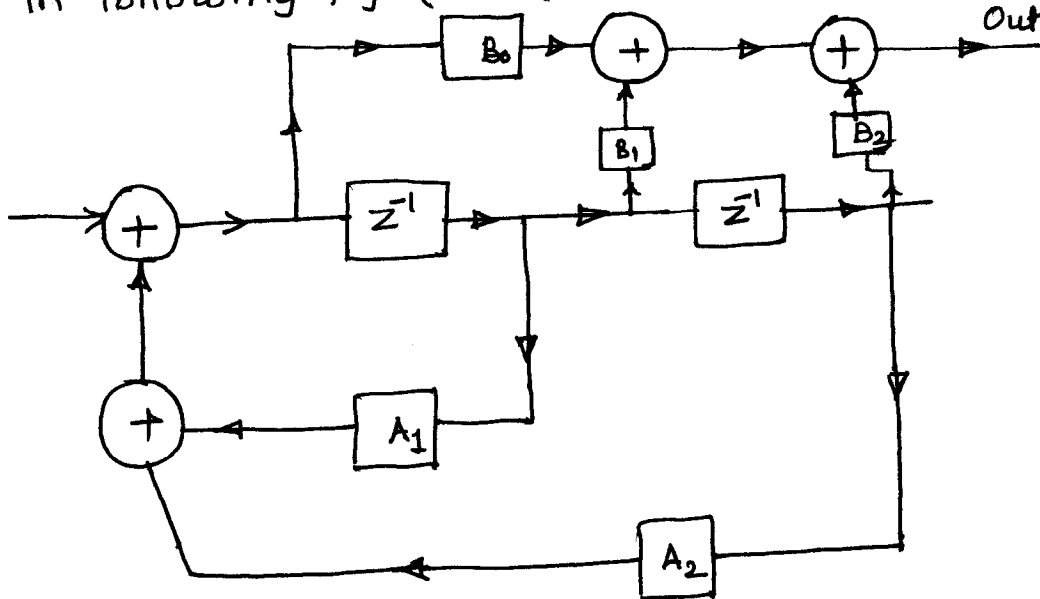


Solution for 35.29 by Pandurang IrkarProb. 35.29

Repeat Ex. 35.14 using a digital filter.

Soln : Referring to Ex. 35.14 (~~35.11~~ 35.13), We have to design a digital band pass filter with center frequency  $f_0 = 1.59 \text{ MHz}$  and  $Q = 20$ , It can be done with digital Biquad form shown in following fig. (35.64)



Writing the transfer function

$$H(f) = \frac{a_1 s}{s^2 + \left(\frac{2\pi f_0}{Q}\right)s + (2\pi f_0)^2} \quad \text{---} \quad (*)$$

The equation from 35.110 to 35.116 gives that

$$a_2 = B_0$$

$$a_1 = f_s (2B_0 + B_1)$$

$$a_0 = f_s^2 (B_0 + B_1 + B_2)$$

$$\frac{2\pi f_0}{Q} = f_s (2 - A_1)$$

$$f_0 = \frac{f_s}{2\pi} \sqrt{(1 - A_1 - A_2)}$$

from (\*)

$$a_2 = B_0 = 0$$

$$a_0 = 0 \Rightarrow B_0 + B_1 + B_2 = 0$$

$$B_1 = -B_2$$

$$a_1 = f_s \cdot B_1 \rightarrow \text{Pass Band gain.}$$

For the center frequency  $\Rightarrow 1.59 \text{ MHz}$ , we can take sampling frequency  $10000 \text{ Hz}$  which can satisfy the Nyquist criteria completely.

We need to calculate the coefficients  $A_1$ ,  $A_2$  and  $B_1$  with the specifications  $f_0 = 1.59 \text{ MHz}$  and  $Q = 20$

from equation 35.115

$$\frac{2\pi f_0}{Q} = f_s (2 - A_1)$$

$$\frac{2\pi \times 1.59}{20 \times 10} = 2 - A_1$$

$$A_1 = 1.9950$$

from equation 35.116

$$f_0 = \frac{f_s}{2\pi} \cdot \sqrt{(1 - A_1 - A_2)}$$

putting the above value of  $A_1$  in 35.116

We get

$$A_2 = 1.0049$$



## Biquad Bandpass Digital filter

```
.control  
destroy all  
run  
set units=degrees  
plot dB(vout) ylimit 25 -25  
.endc
```

```
.AC DEC 100 10k 200MEG
```

```
*Input Signal  
Vin Vin 0 DC 0 AC 1
```


```
*Adders  
Eadd1 Voadd1 0 Vin Voadd2 1  
Eadd2 0 Voadd2 Voal Voa2 1  
Eadd3 Vout 0 Vob1 Vob2 1
```

```
*Delays Using transmission line and termination  
TZ1 Vod1 0 Voadd1 0 TD=10n ZO=50  
RZ1 Vod1 0 50
```

```
*Add buffer to avoid loading  
Ebuf1 Vod11 0 Vod1 0 1  
TZ2 Vod2 0 Vod11 0 TD=10n ZO=50  
RZ2 Vod2 0 50
```

```
*multipliers  
EA1 Voa1 0 Vod1 0 1.9950  
EA2 Voa2 0 Vod2 0 1.0049  
EB1 Vob1 0 Vod1 0 0.099  
EB2 Vob2 0 Vod2 0 0.099
```
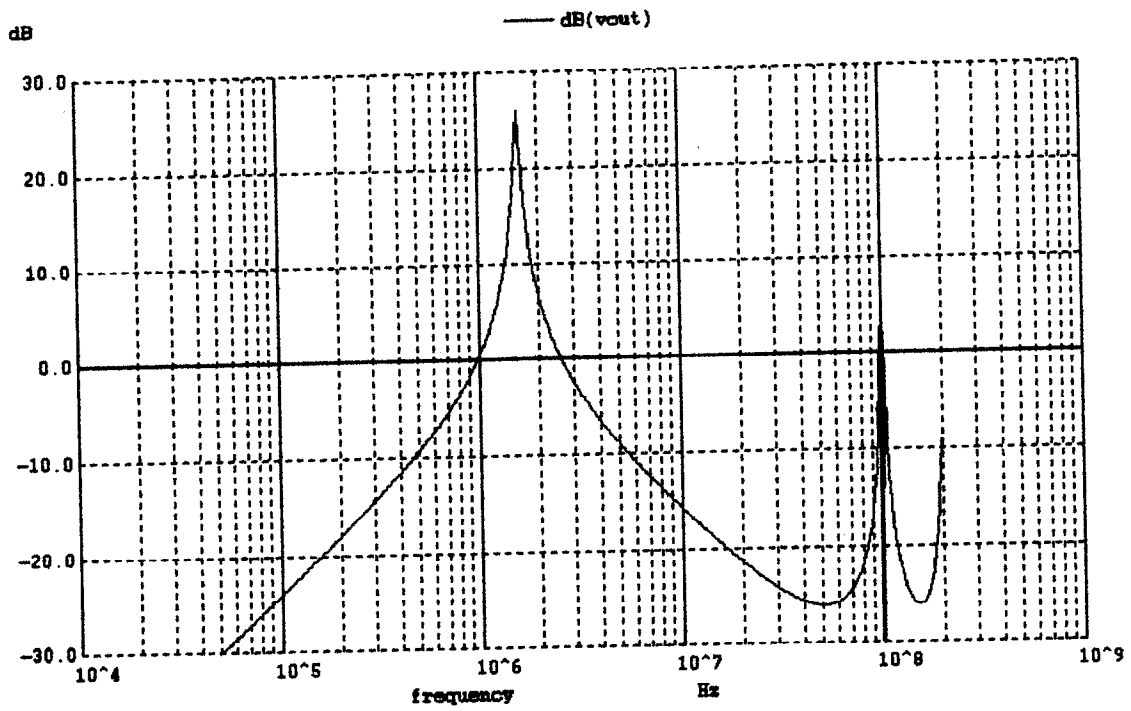
```
* Load resistors  
RL Vout 0 1G  
Radd1 Voadd1 0 1G  
Radd2 Voadd2 0 1G  
Roal Voa1 0 1G  
Roa2 Voa2 0 1G  
.end
```



With  $Q=20$  and Gain of Passband=20, we have here Gain =26dB at center frequency