

$$\textcircled{1} \textcircled{a} \quad G_m \cong \sqrt{50\mu \cdot 100\mu \cdot 12.5} = 250\mu\text{S}$$

$$r_{o8} = \frac{1}{0.1 \cdot 25\mu} = 400\text{k}\Omega$$

$$g_{m6} = \sqrt{50\mu \cdot 200\mu \cdot 40} = 632\mu\text{S}$$

$$r_{o6} = \frac{1}{0.02 \cdot 25\mu} = 2\text{M}\Omega$$

$$r_{o4} = \frac{1}{0.05 \cdot 50\mu} = 400\text{k}\Omega$$

$$\Rightarrow A_{dmo} = 250\mu\text{S} \cdot 400\text{k} \parallel \frac{632\mu\text{S} \cdot 2\text{M}\Omega \cdot 400\text{k}}{505\text{M}\Omega}$$


$$A_{dmo} = 100$$

$$A_{dmo} \hat{=} 40\text{dB}$$

$$f_{p1} = \frac{1}{2\pi C_L r_{o8}} = \frac{1}{2\pi \cdot 0.2\text{p} \cdot 400\text{k}} = 2\text{MHz}$$

$$f_{p2} = \frac{g_{m5}}{2\pi C_{gs5}} = \boxed{30.2\text{MHz}}$$
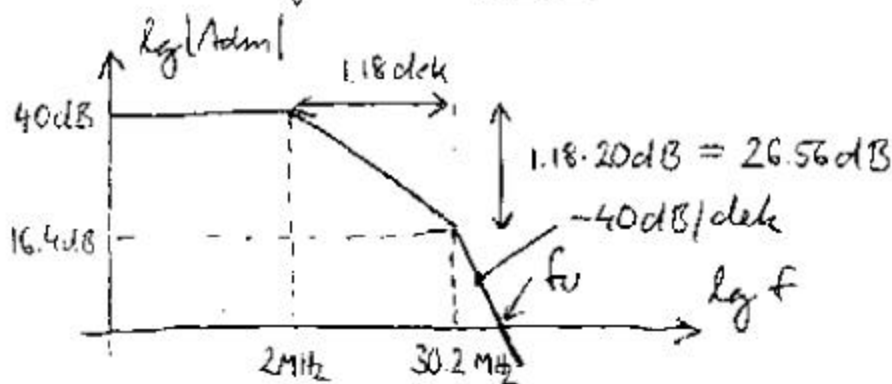
$$C_{gs5} = \frac{2}{3} \cdot 1000 \cdot 5\text{fF} = 3.33\text{pF}$$




$$f_u \cong \underbrace{10^{\left(\frac{16.4}{40}\right)}}_{2.57} \cdot 30.2\text{MHz} = \boxed{77.6\text{MHz}}$$

① b) phase shift from $p_1 \cong -90^\circ$
 phase shift from p_2 : $\arctan\left(\frac{f_u}{f_{p2}}\right) = -\arctan\left(\frac{7.6\text{MHz}}{32\text{MHz}}\right) = -67.6^\circ$

$\Rightarrow \varphi_m = 180^\circ - 90^\circ - 67.7^\circ = \underline{\underline{22.3^\circ}}$ POOR!

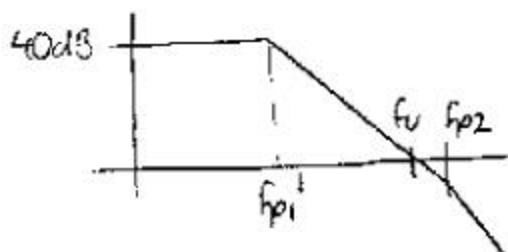c) For $\varphi_m = 60^\circ$:

$f_u \stackrel{!}{=} \frac{1}{2} f_{p2}$ and f_u caused by dominant pole f_{p1}'



$f_{p1}' = \frac{1}{2} \cdot \frac{1}{100} \cdot 30.2\text{MHz}$

$f_{p1}' = 151.1\text{kHz}$

$\Rightarrow C_L' = \frac{1}{2\pi f_{p1}' \cdot r_{o8}} = \frac{1}{2\pi \cdot 151\text{k} \cdot 400\Omega} = \underline{\underline{264\text{pF}}}$

d) $G_m \sim I_0 \Rightarrow f_u \sim I_0$
 $g_{m5} \sim I_0 \Rightarrow f_{p2} \sim I_0$ } $\frac{f_{p2}}{f_u} = \text{const.}!$

\Rightarrow THE PHASE MARGIN DOES NOT CHANGE WHEN I_0 IS CUT IN HALF!

e) $W_{i,2} \uparrow 2x \Rightarrow G_m \uparrow \sqrt{2} \Rightarrow f_u \uparrow \sqrt{2}$
 and $f_{p2} = \text{const.} \Rightarrow \frac{f_{p2}}{f_u} \downarrow \times 1/\sqrt{2}$



\rightarrow THE PHASE MARGIN WILL DECREASE IN THIS CASE, BY

$\arctan 2 - \arctan\left(\frac{2}{\sqrt{2}}\right) = \underline{\underline{8.7^\circ}}$

(1) f) see attached plot

	<u>CALC</u>	<u>SIM</u>	<u>ERR</u>
$f_m (L_L = 0.2p)$	22.3°	16.8°	30%
$f_m (L_L = 2.6p)$	$\cong 60^\circ$	63°	4.7%

→ good agreement

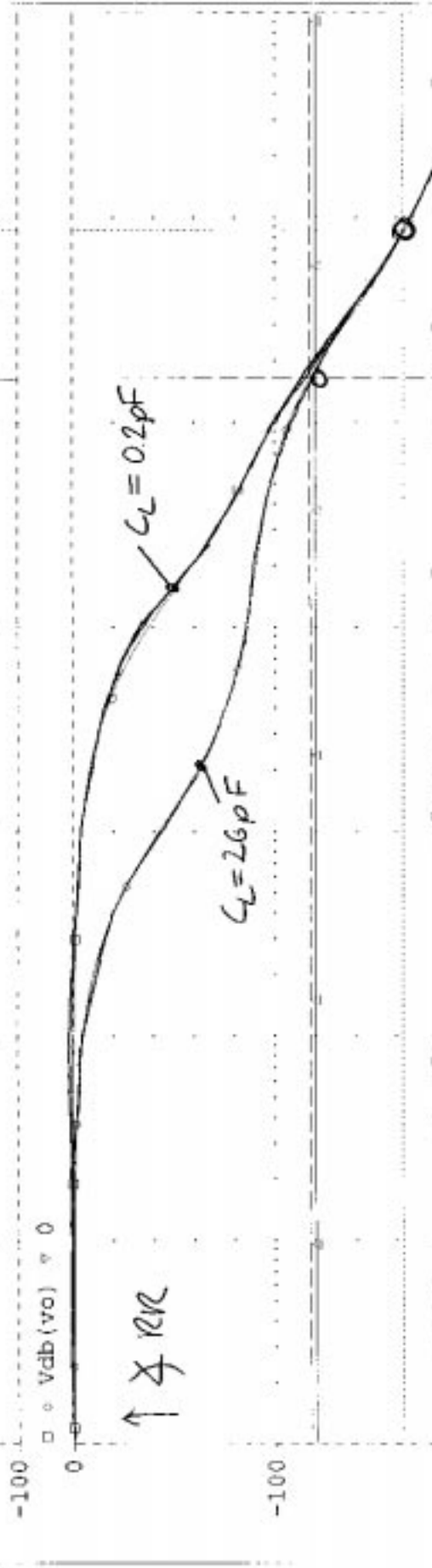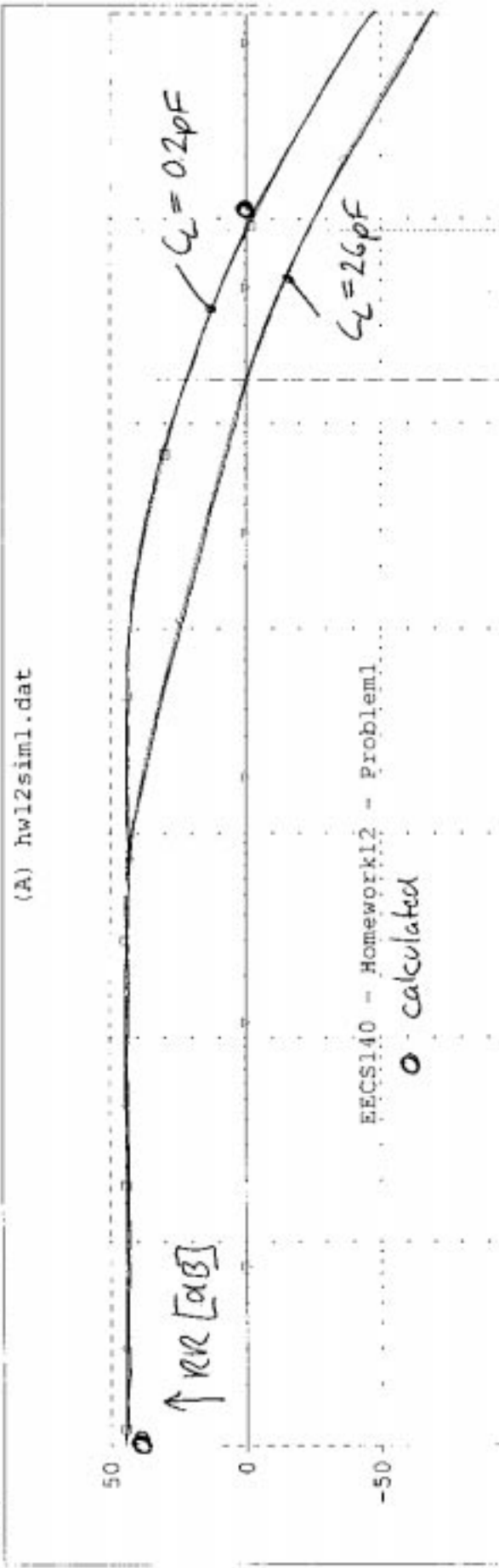

SEL>>
 -200 +
 100Hz 1.0KHz 10KHz 100KHz 1.0MHz 10MHz 100MHz 1.0GHz
 □ |Vp(vo) -180 -120
 Frequency
 A1: (86.767M, -163.124) A2: (16.305M, -117.317) DIFF(A): (70.462M, -45.807)
 Date: November 23, 1999 Page 1
 Time: 00:08:40

$$\textcircled{2} \text{ a) } g_{m8} = \sqrt{2I_{D8} \mu_n' \frac{W}{L}} = \sqrt{200 \mu\text{A} \cdot 200 \mu\text{m} \cdot 25} = 1 \text{ mS}$$

$$R_z = \frac{1}{g_{m8}} = \underline{\underline{1 \text{ k}\Omega}}$$

$$\textcircled{b) } \omega_u \cong \frac{g_{m1}}{C_L} \quad g_{m1} = \sqrt{100 \mu\text{A} \cdot 100 \mu\text{m} \cdot 50} = 707 \mu\text{S}$$

$$f_u \cong \frac{1}{2\pi} \frac{707 \mu\text{S}}{5 \text{ pF}} = \underline{\underline{22.5 \text{ MHz}}}$$

$$f_{p2} \cong \frac{1}{2\pi} \frac{g_{m8}}{C_L} \geq 2 \cdot f_u \text{ for } 60^\circ \text{ phase margin}$$

$$\Rightarrow C_{L\text{max}} = \frac{g_{m8}}{2 \cdot 2\pi f_u} = \frac{1 \text{ mS}}{2 \cdot 2\pi \cdot 22.5 \text{ MHz}} = \underline{\underline{3.5 \text{ pF}}}$$

$$\textcircled{c) } \left. \begin{array}{l} \omega_{1,2} \uparrow 2x \Rightarrow g_{m1} \uparrow \sqrt{2} \\ \omega_5 \uparrow 2x \Rightarrow I_{D1} \uparrow 2x \Rightarrow g_{m1} \uparrow \sqrt{2} \end{array} \right\} g_{m1} \uparrow 2x$$

$$\Rightarrow \omega_u \uparrow 2x \rightarrow \omega_u' = \underline{\underline{44.5 \text{ MHz}}} = f_{p2}$$

$$\Rightarrow \text{since } \omega_u = f_{p2} \Rightarrow \underline{\underline{P_m' = 45^\circ}}$$

$$\textcircled{d) } \left. \begin{array}{l} I_{D8} \uparrow 2x \\ W_8 \uparrow 2x \end{array} \right\} \Rightarrow g_{m8} \uparrow 2x \quad \begin{array}{l} g_{m8}' = 2 \text{ mS} \\ (R_z' = 500 \Omega) \end{array}$$

→ unity gain frequency does not change! ($f_u = 22.5 \text{ MHz}$)

$$f_{p2} \text{ doubles} \Rightarrow f_{p2} = 4f_u$$

$$\Rightarrow P_m = \arctan 4 = \underline{\underline{76^\circ}}$$

$$e) \quad \left. \begin{array}{l} g_{m1} \uparrow \sqrt{2} \\ g_{m2} \uparrow \sqrt{2} \end{array} \right\} P_{in} = \text{const}$$

$$f_c' - \sqrt{2} f_c = \underline{\underline{31.8 \text{ MHz}}}$$


$$\underline{\underline{P_{in} \approx 60^\circ}}$$

$$f) \quad f_{p2} = 45 \text{ MHz}$$

$$\text{from class: } A(s) = \frac{N(s)}{D(s)} = \frac{N(s)}{D(s)}$$

$$N(s) = 0 = g_{m2} - sC_c$$
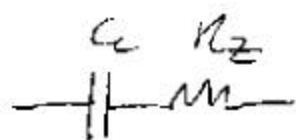
$$\text{replace } sC_c \text{ with } \frac{1}{\frac{1}{sC_c} + R_z}$$



$$= \frac{sC_c}{1 + sR_zC_c}$$

$$0 = \frac{g_{m2} + s g_{m2} R_z C_c - sC_c}{1 + sR_zC_c}$$

$$0 = g_{m2} + sC_c \left(g_{m2} R_z - 1 \right)$$

$$0 = 1 + sC_c \left(R_z - \frac{1}{g_{m2}} \right) \quad \text{zero: } z = - \frac{1}{C_c \left(R_z - \frac{1}{g_{m2}} \right)}$$

$$z = \frac{1}{s} p_2 = -2\pi \cdot 45 \text{ MHz} = - \frac{1}{C_c \left(R_z - \frac{1}{g_{m2}} \right)}$$



$$R_z = \frac{1}{\omega_{p2} C_c} + \frac{1}{g_{m2}} = \frac{1}{2\pi \cdot 45 \text{ MHz} \cdot 2 \text{ pF}} + \frac{1}{1 \text{ mS}} = \underline{\underline{2.768 \text{ k}}}$$

$$\Rightarrow \underline{\underline{P_{in} = 90^\circ}}$$

g) → see attached plot


	<u>CALC</u>	<u>SIM</u>	<u>ERR</u>
f_u	22.5 MHz	23.7 MHz	4%
$\phi_m (R_z = 1k)$	$\approx 60^\circ$	62°	3%
$\phi_m (R_z = 0)$	—	24.5°	—

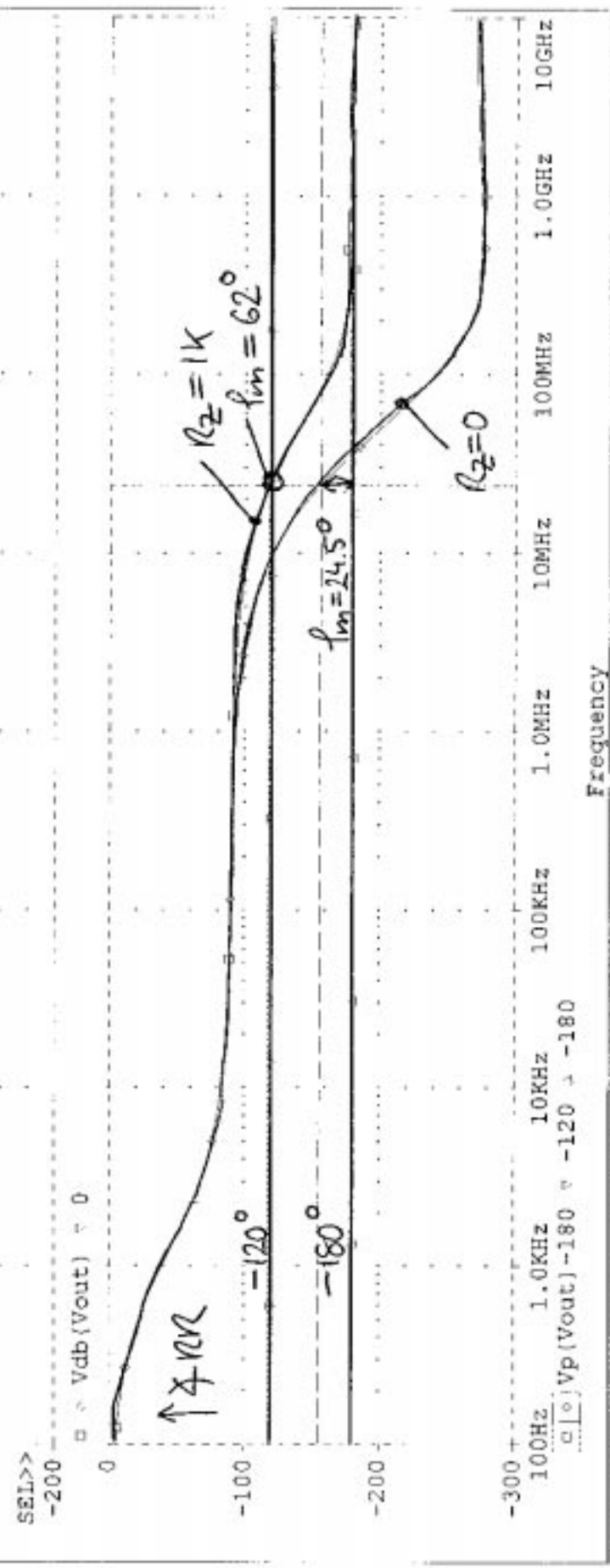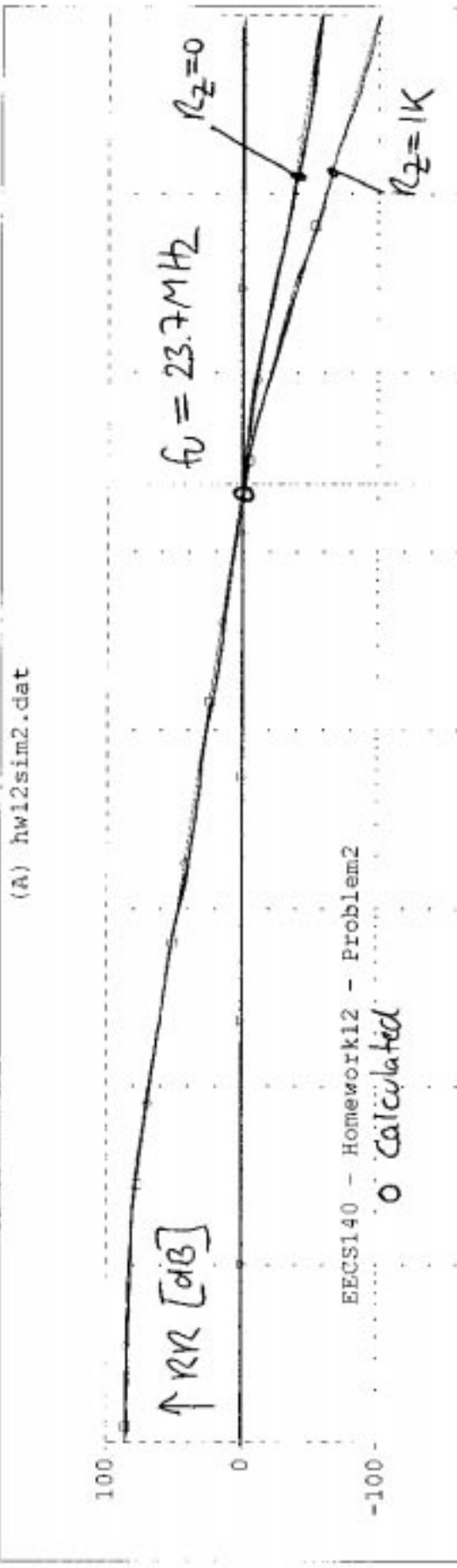↓
due to additional phase
shift from RHP zero!



8/18

3 a

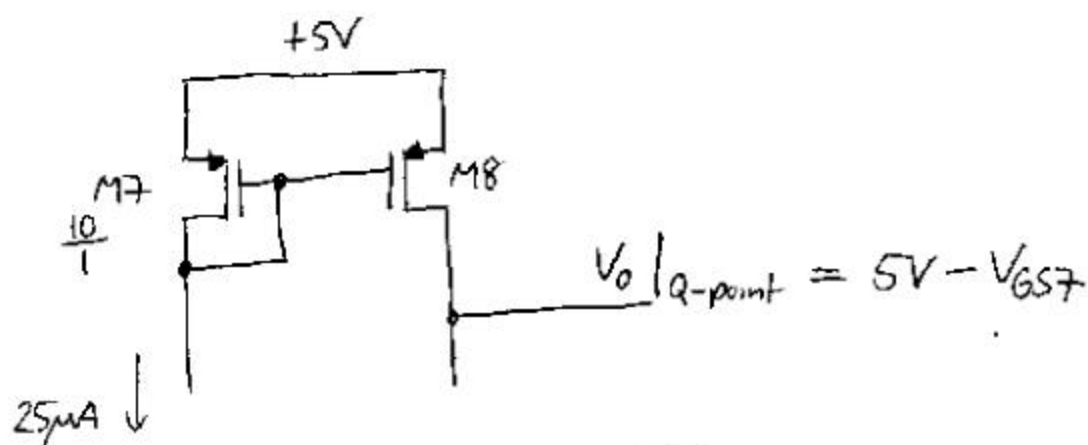

$$V_{dsat7} = \sqrt{\frac{2I_D}{\mu' \frac{W}{L}}} = \sqrt{\frac{50\mu A}{100\mu \cdot 10}} = 223 \text{ mV}$$

$$\Rightarrow V_{DQ} = 5V - 1.223V = \underline{\underline{3.77V}}$$

$$\rightarrow \text{for } V_0 \stackrel{!}{=} 0 \text{ need } V_{os} = V_{id} |_{V_0=0} = \frac{V_{DQ}}{A_{dcm}}$$

$$\Rightarrow V_{os} = \frac{-3.86V}{100} = \underline{\underline{-38.7 \text{ mV}}}$$

$$b) \epsilon_s = \frac{1}{T_0} = \frac{1}{a_0} = \frac{1}{100} = \underline{\underline{1\%}}$$

$$c) SR = \frac{2I_0}{C_L} = \frac{50\mu A}{10pF} = \underline{\underline{5V/\mu s}}$$

$$\tau = \frac{1}{\omega_0(\text{NR})} = \frac{C_L}{g_{m1}} = \frac{10pF}{250\mu S} = \underline{\underline{40ns}}$$

$$d) (i) \text{ double } \left(\frac{W}{L}\right)_g \Rightarrow I_0 \uparrow 2x \Rightarrow SR \uparrow 2x \quad \left(\left(\frac{W}{L}\right)_g \stackrel{!}{=} \frac{100}{2}\right)$$

$$(ii) \tau \sim \frac{1}{g_{m1}} \rightarrow \text{e.g. double } g_{m1} \text{ by increasing } \left(\frac{W}{L}\right)_{1,2} \text{ by a factor of 2 and } I_{D1} \uparrow 2x$$


$$\rightarrow \left(\frac{W}{L}\right)_{1,2} \stackrel{!}{=} \frac{50}{2} \quad \left(\frac{W}{L}\right)_g \stackrel{!}{=} \frac{100}{2} \quad 9/18 \text{ HW1}$$

$$e) \quad V_{dsat1} = \sqrt{\frac{50\mu}{100\mu \cdot 12.5}} = 200\text{mV}$$

$$\Delta V_i = 50\text{mV} < 200\text{mV} \Rightarrow \text{LINEAR SETTling}$$

$$t_s \cong 6.9 \tau = 4.6 \cdot 40\text{ns} = \underline{\underline{276\text{ns}}}$$
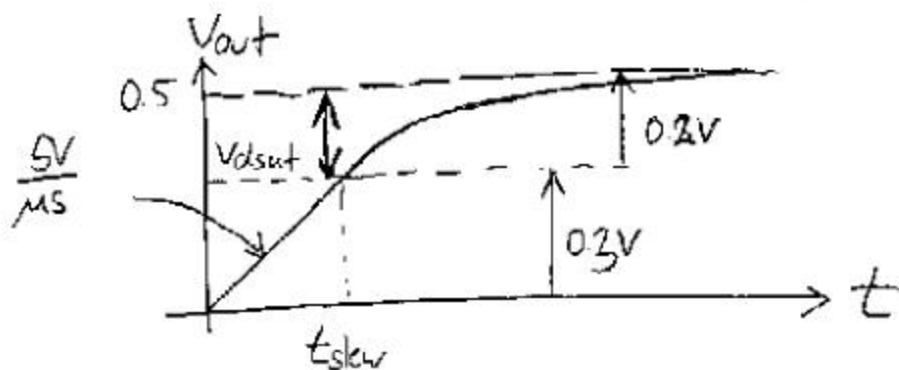
$$f) \quad \Delta V_i = 500\text{mV} > 200\text{mV}$$



$$- t_{SLEW} = \frac{V_{dsat}}{SR} = \frac{0.2}{5} \mu s = 60\text{ns}$$

$$- \text{exponential needs to settle within } 0.1\% \text{ of } 0.5\text{V} \\ = 0.5\text{mV}$$

$$\Rightarrow (200\text{mV} - 0.5\text{mV}) = 200\text{mV} (1 - e^{-t/\tau})$$

$$t_{lin} = -\tau \cdot \ln\left(1 - \frac{200 - 0.5}{200}\right)$$

$$t_{lin} = -40\text{ns} \ln(0.16667\%)$$

$$t_{lin} = 239\text{ns}$$

$$\Rightarrow t_s = t_{lin} + t_{slew} = 60\text{ns} + 239\text{ns} = \underline{\underline{299\text{ns}}}$$

g) i) see attached plot
 $V_{OS} = -19.715 \text{ mV}$ (calculated -38.6 mV
 \rightarrow discrepancy due to underestimated A_{dm})

ii) see attached plot
settling voltages: (after cancelling V_{OS})

V_i	V_o
-25 mV	-24.931 mV
$+25 \text{ mV}$	$+24.906 \text{ mV}$
-250 mV	-249.218 mV
$+250 \text{ mV}$	$+249.142 \text{ mV}$

iii) see attached plot

iv) see attached plot

DISCREPANCIES (COMPARED TO HAND ANALYSIS)
ARE DUE TO :

— LARGE $V_{DS}'_S \Rightarrow$ large $\lambda V_{DS} \rightarrow$ difference in I_D
 $g_{m1}, r_{o1}, \text{ etc.}$

— LARGE SIGNAL EFFECTS SHOW UP IN NEG.
TRANSIENT OF -500 mV STEP (SEE P.17)

\rightarrow TO BE EXAMINED !!

\rightarrow LOOK AT V_{I1} DURING NEG. SLEWING
M7 IS OFF \Rightarrow IMPEDANCE LOOKING INTO
SOURCE OF M5 IS LARGE \rightarrow LOW FREQUENCY


$f_{P2} \Rightarrow$ INSTABILITY EFFECTS ...
(CAN BE FIXED BY SIZING M5-6 TO $\frac{40}{1}$)

U:\Ee140\spice\hw12sim3.sch

Date/Time run: 11/23/99 17:44:20

Temperature: 27.0

(A) hw12sim3.dat

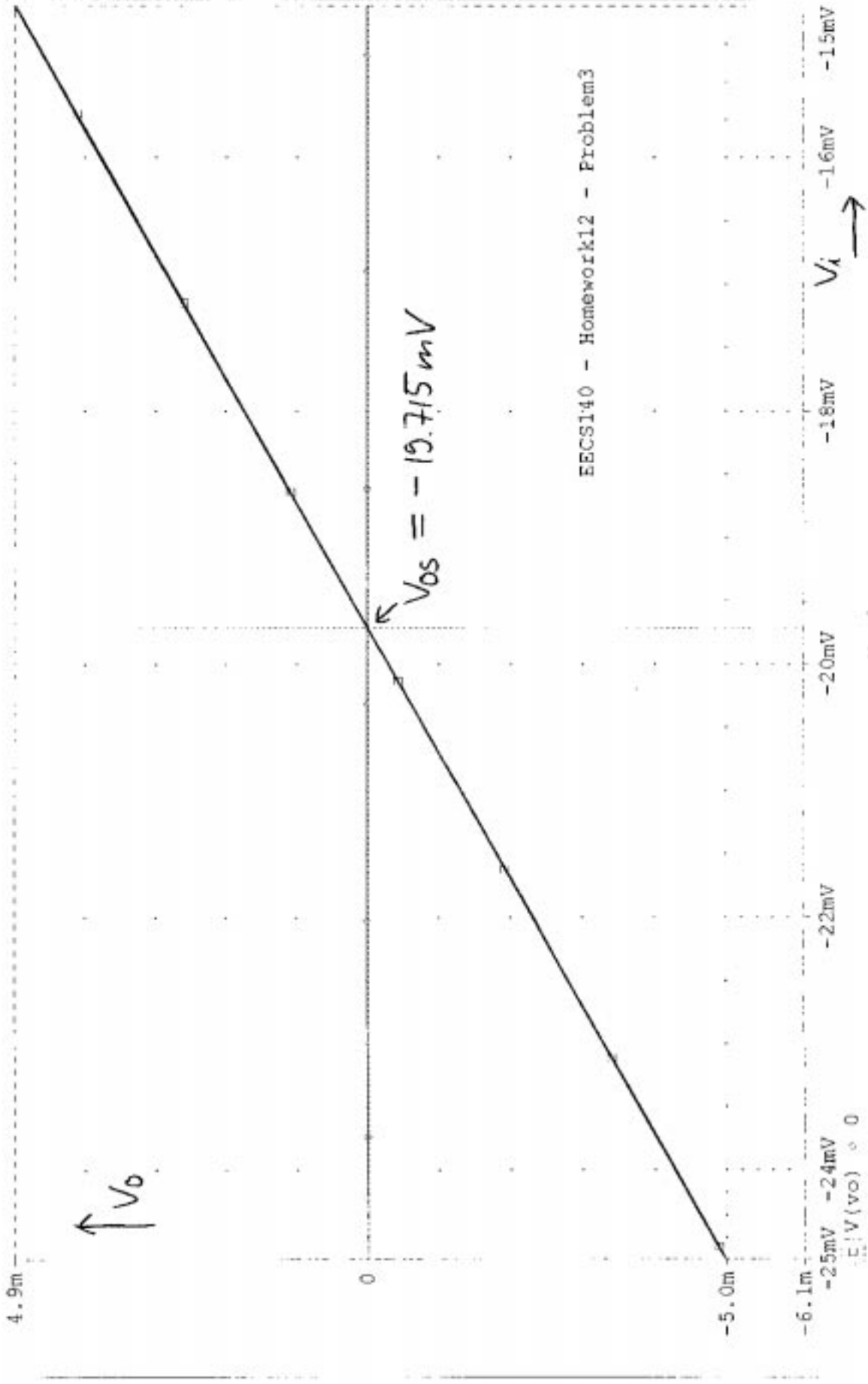

A1: (-19.715m, -12.636u) A2: (-50.000m, -30.198m) DIFF(A): (30.285m, 30.186m)


Date: November 23, 1999

Page 1

Time: 17:46:51

12/18

(A) hw12sim3.dat

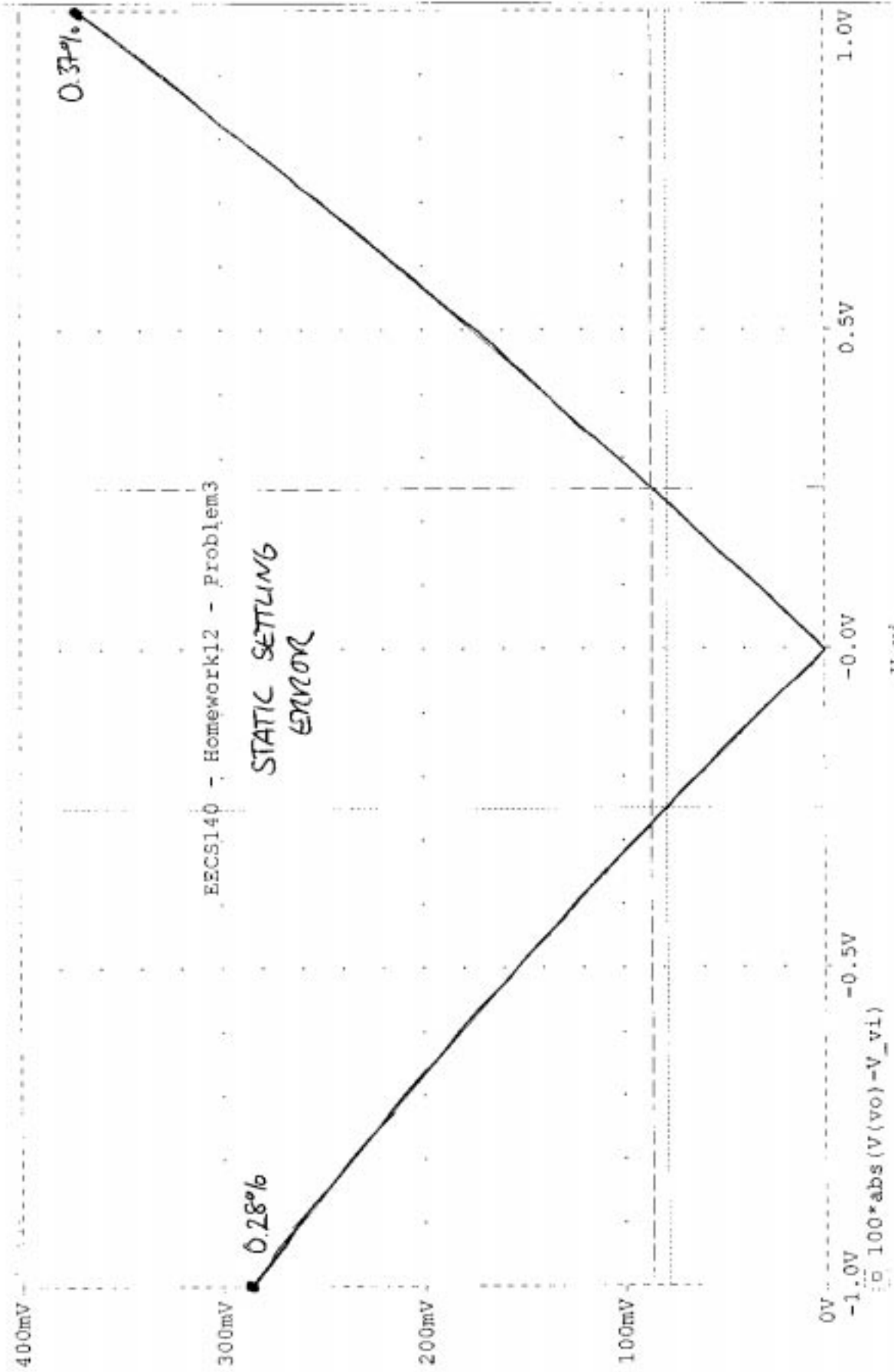

A1: (-250.900m, 78.507m) A2: (251.000m, 86.127m) DIFF(A): (-501.900m, -7.6205m)

13/1

* U:\Ee140\spice\hw12sim3.sch

Date/Time run: 11/23/99 18:45:46

Temperature: 27.0

(A) hw12sim3.dat

EECS140 - Homework12 - Problem3

500mV

+0.1%

0V

-0.1%

$t_s = 172\text{ns}$

$\Delta V_i = 50\text{mV}$, pos. edge.

-500mV

100.00000ns

200.00000ns

400.00000ns

500.00000ns

100*(V(vo)-24.906m)/25m * 0.1 * -0.1

Time

A1:(272.727n,-99.810m) A2:(600.505n,481.392u) DIFF(A):(-327.778n,-100.291m)


Date: November 23, 1999

Page 1

Time: 18:54:34

14/18

EECS140 - Homework12 - Problem3

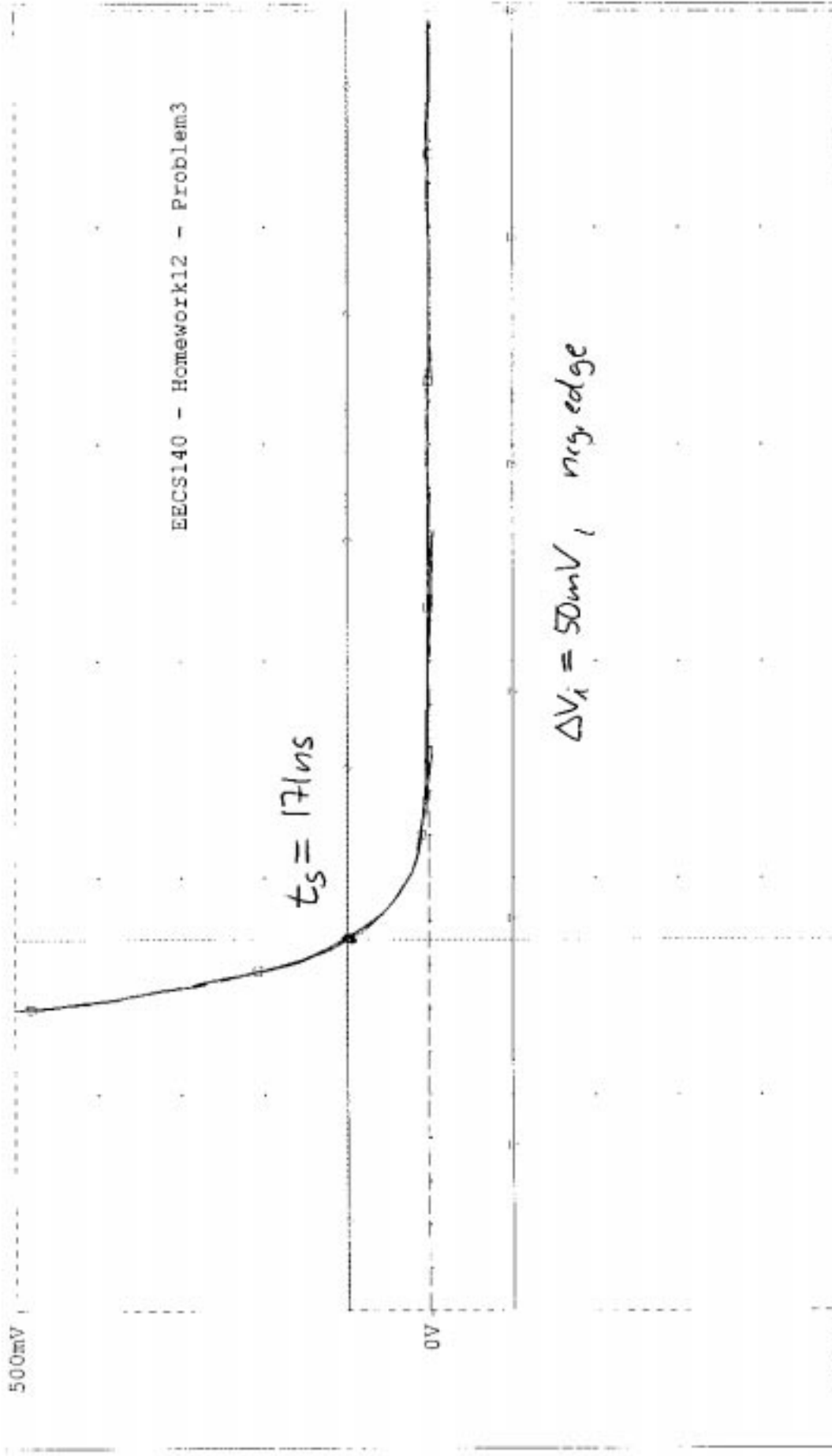

$\Delta V_i = 50mV$, $r_{ig, edge}$

	Time
-500mV	
2.000000us	2.100000us
2.000000us	2.200000us
2.300000us	2.400000us
2.500000us	2.500000us

Time

A1: (2.1714u, 100.987m) A2: (2.6006u, 2.2852m) DIFF(A): (-429.175n, 98.702m)

15/18


* U:\Eel140\spice\hw12sim3.sch

Temperature: 27.0

Date/Time run: 11/23/99 19:06:39

(A) hw12sim3.dat

EECS140 - Homework12 - Problem3

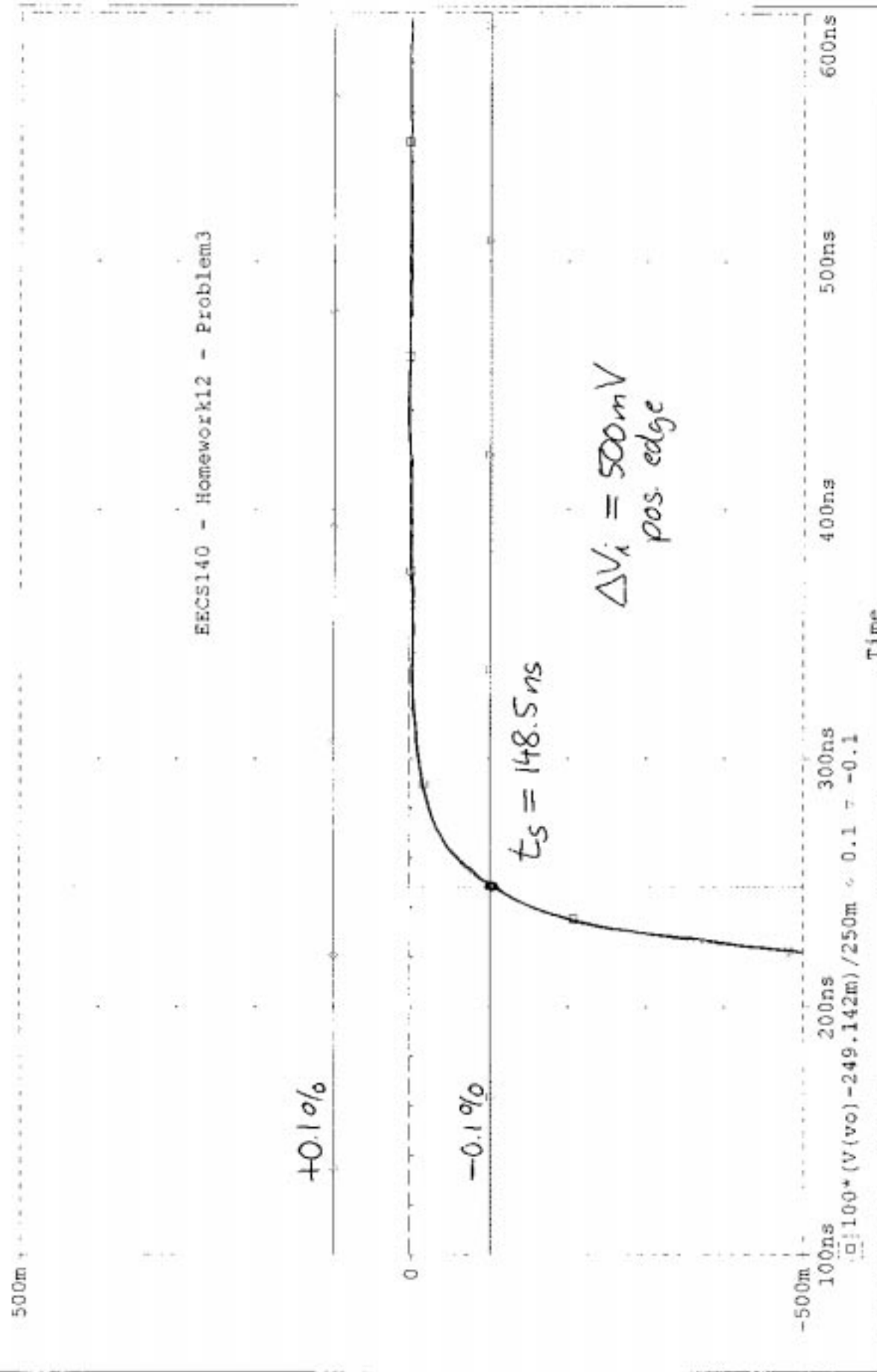

500m
100ns
-500m
□: 100*(V(vo)-249.142m)/250m < 0.1 & -0.1

Time

A1:(248.500n,-100.673m) A2:(600.000n,3.0977m) DIFF(A):(-351.500n,-103.770m)


Date: November 23, 1999

Page 1

Time: 19:07:51

16/18

(A) hw12sim3.dat

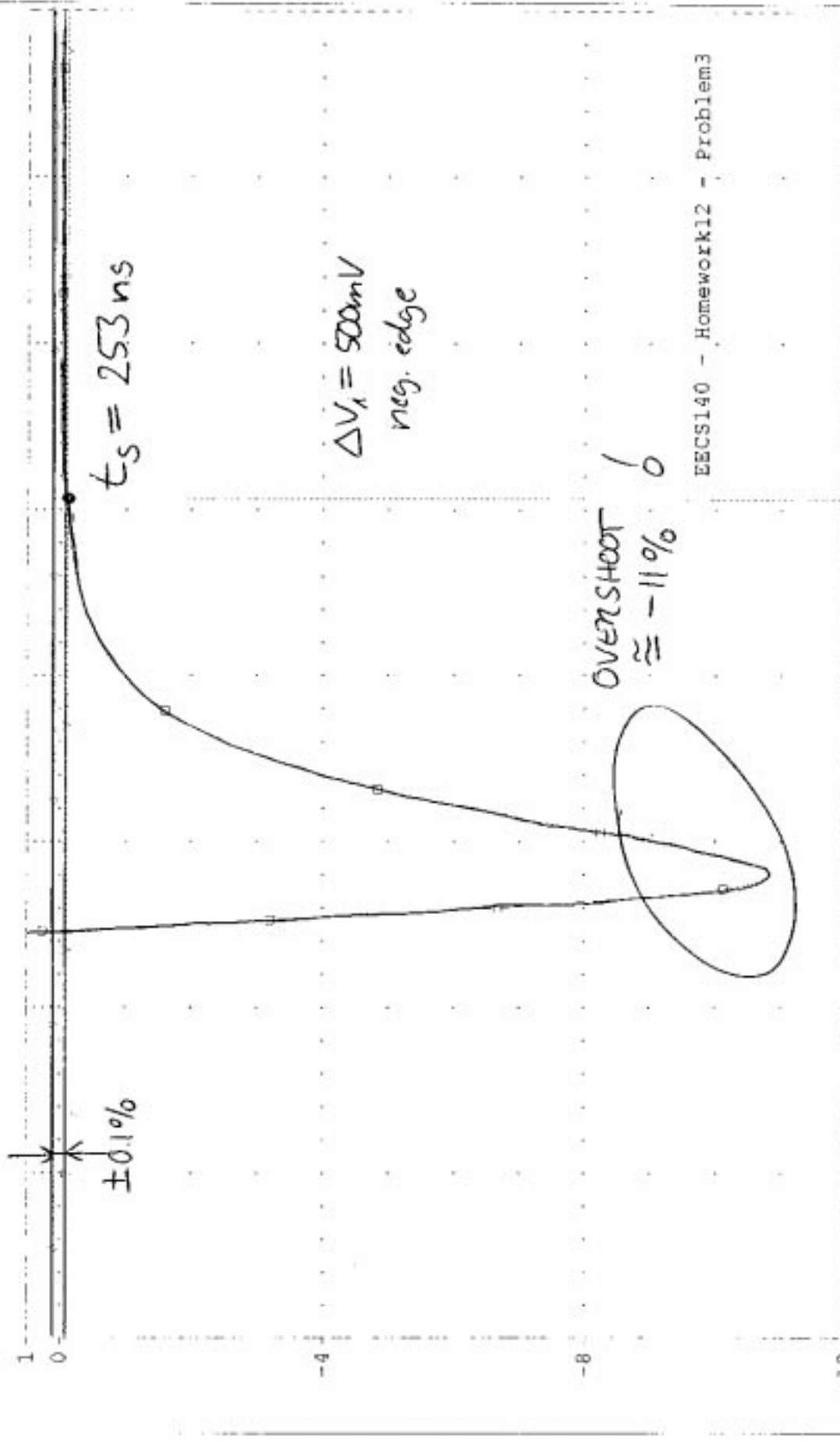

EECS140 - Homework12 - Problem3

Time	2.00us	2.05us	2.10us	2.15us	2.20us	2.25us	2.30us	2.35us	2.40us
Value	$100 \cdot (V(vo) + 249.142 \text{ m}) / 250 \text{ m} \diamond 0.1 = -0.1$								


A1: (2.2532u, -100.715m) A2: (2.0000u, 199.316) DIFF(A): (253.150n, -199.417)

17/18


$$(4) \quad a) \quad SR = \frac{I_{D5}}{C_C} = \frac{100 \mu A}{5 pF} = \underline{\underline{20 V/\mu s}}$$

$$b) \quad SR = \frac{I_{D7}}{C_C + C_L} = \frac{100 \mu A}{5 pF + 15 pF} = \underline{\underline{6.66 V/\mu s}}$$

c) (i) pos. slewing:

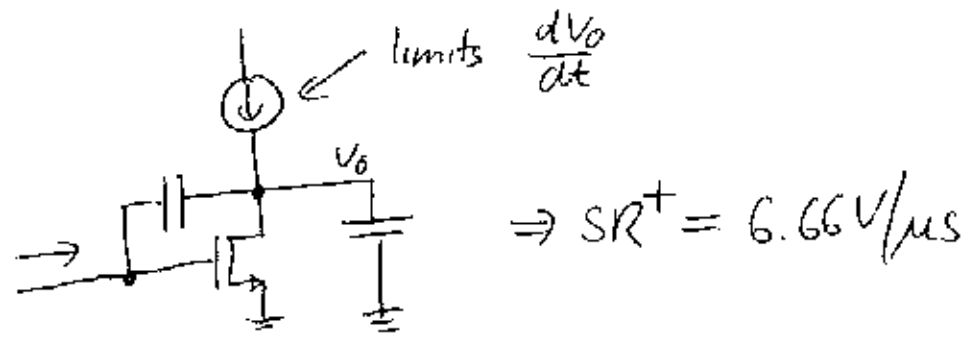

(ii) neg. slewing:

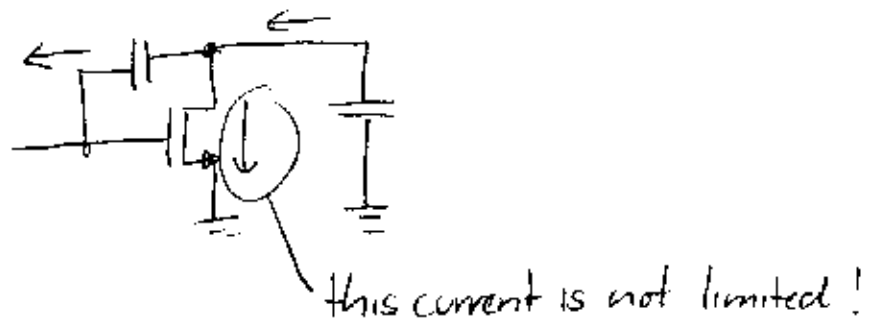

$$\Rightarrow SR^- = \frac{I_{D5}}{C_C} = \underline{\underline{20 V/\mu s}}$$

$$d) \quad \frac{I_{D5}}{C_C} = \frac{I_{D7}}{C_C + C_L}$$

$$\frac{100 \mu}{5 pF} = \frac{100 \mu}{5 pF + C_L} \Rightarrow \underline{\underline{C_L = \phi !}}$$