

$$\textcircled{1} \text{ a) } |V_{BE}| = V_t \ln \frac{I_{out}}{I_S} = 26 \text{ mV} \cdot \ln \frac{100 \mu\text{A}}{1 \text{ fA}} = 658.5 \text{ mV}$$

$$R = \frac{|V_{BE}|}{I_{out}} = \frac{658.5 \text{ mV}}{100 \mu\text{A}} = \underline{\underline{6.585 \text{ k}\Omega}}$$

$$\text{b) } I_{out} = \frac{V_t}{R} \ln \frac{I_{out}}{I_S} ; \quad S_{I_S}^{I_{out}} = \frac{I_S}{I_{out}} \frac{dI_{out}}{dI_S}$$

→ need to find derivative of implicit function

$$f(I_{out}, I_S) = I_{out} - \frac{V_t}{R} \ln \frac{I_{out}}{I_S} = 0$$

$$\frac{dI_{out}}{dI_S} = \frac{-\partial f / \partial I_S}{\partial f / \partial I_{out}} = \frac{\frac{V_t}{R} \frac{I_S}{I_{out}} \cdot \left(-\frac{I_{out}}{I_S^2}\right)}{1 - \frac{V_t}{R} \frac{I_S}{I_{out}} \cdot \frac{1}{I_S}}$$

$$\frac{dI_{out}}{dI_S} = \frac{V_t}{RI_S - V_t \frac{I_S}{I_{out}}} \quad \text{small} \quad RI_S \approx 6 \cdot 10^{-12}$$

$$V_t \frac{I_S}{I_{out}} \approx 3 \cdot 10^{-13}$$

$$\Rightarrow S_{I_S}^{I_{out}} = \frac{I_S}{I_{out}} \cdot \frac{V_t}{RI_S} = \frac{V_t}{R I_{out}} = \frac{26 \text{ mV}}{6.585 \text{ k} \cdot 100 \mu\text{A}} = \underline{\underline{3.95\%}}$$

So, for a 10% in I_S :

$$\frac{\Delta I_{out}}{I_{out}} \bigg|_{\frac{\Delta I_S}{I_S} = 10\%} = 3.95\% \cdot 10\% = \underline{\underline{0.395\%}} \quad (\text{only!})$$

$$\textcircled{c) } TCF = \frac{1}{I_{out}} \frac{\partial I_{out}}{\partial T} = \frac{1}{I_{out}} \frac{\partial}{\partial T} \left(\frac{V_{BE}}{R} \right)$$

$$= \frac{1}{I_{out}} \frac{\frac{\partial V_{BE}}{\partial T} \cdot R - V_{BE} \frac{\partial R}{\partial T}}{R^2}$$

$$= \frac{1}{100 \mu\text{A}} \frac{-2 \text{ mV}/^\circ\text{C} \cdot 6.585 \text{ k} - 658.5 \text{ mV} \cdot (1200 \cdot 10^{-6} / ^\circ\text{C} \cdot 6.585 \text{ k})}{(6.585 \text{ k})^2}$$

$$TCF = \underline{\underline{-0.424\%}}$$

$$\textcircled{2} \quad \text{a) } |V_{GS1}| = |V_{TH}| + \sqrt{\frac{2I_{OUT}}{k'w/L}} = 1.1V + \sqrt{\frac{2 \cdot 100\mu A}{100 \frac{mA}{V^2} \cdot 200}} = 1.1V$$

$$\Rightarrow R = \frac{|V_{GS1}|}{I_{OUT}} = \frac{1.1V}{100\mu A} = \underline{\underline{11k\Omega}}$$

$$\text{b) } I_{OUT} = \frac{V_{TH}}{R} + \frac{1}{R} \sqrt{\frac{2I_{OUT}}{k'w/L}}; \quad S_{V_{TH}}^{I_{OUT}} = \frac{I_{OUT}}{V_{TH}} \cdot \frac{dI_{OUT}}{dV_{TH}}$$

$$f(I_{OUT}, V_{TH}) = \frac{V_{TH}}{R} + \frac{1}{R} \sqrt{\frac{2I_{OUT}}{k'w/L}} - I_{OUT} = 0$$

$$\frac{\partial f}{\partial I_{OUT}} = 0 + \frac{1}{R} \frac{1}{\sqrt{\frac{2I_{OUT}}{k'w/L}}} \cdot \frac{1}{2\sqrt{\frac{2I_{OUT}}{k'w/L}}} - 1$$

$$\frac{\partial f}{\partial V_{TH}} = \frac{1}{R}$$

$$\Rightarrow \frac{dI_{OUT}}{dV_{TH}} = - \frac{\partial f / \partial V_{TH}}{\partial f / \partial I_{OUT}} = \frac{1}{R - \frac{1}{\sqrt{2I_{OUT}k'w/L}}}$$

small $\approx 500\Omega$, $R=11k$

$$\Rightarrow S_{V_{TH}}^{I_{OUT}} = \frac{I_{OUT}}{V_{TH}} \cdot \frac{1}{R} = \frac{1V}{100\mu A \cdot 11k\Omega} = \underline{\underline{0.909}}$$

So, for a 100 mV change in V_{TH} :

$$\left. \frac{\Delta I_{OUT}}{I_{OUT}} \right|_{\Delta V_{TH}=0.1} = \frac{0.1}{1} \cdot 0.909 = \underline{\underline{9.09\%}}$$

which is large compared to $\textcircled{1}$ (b)!

$$\textcircled{c) } TC_F = \frac{1}{I_{OUT}} \frac{\partial I_{OUT}}{\partial T} = \frac{1}{I_{OUT}} \frac{\partial}{\partial T} \left(\frac{V_{TH} + \sqrt{\frac{2I_{OUT}}{k'w/L}}}{R} \right)$$

neglect

$$TC_F = \frac{1}{I_{OUT}} \frac{\frac{\partial V_{TH}}{\partial T} \cdot R - V_{TH} \frac{\partial R}{\partial T}}{R^2} = \frac{-2 \frac{mV}{^\circ C} \cdot 11k - 1V \cdot 1200 \cdot 10^{-6} / ^\circ C \cdot 11k}{100\mu A \cdot (11k)^2}$$

$$TC_F = \underline{\underline{-0.291\%}}$$