
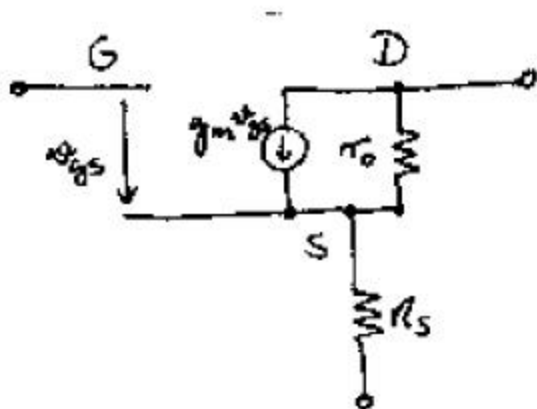


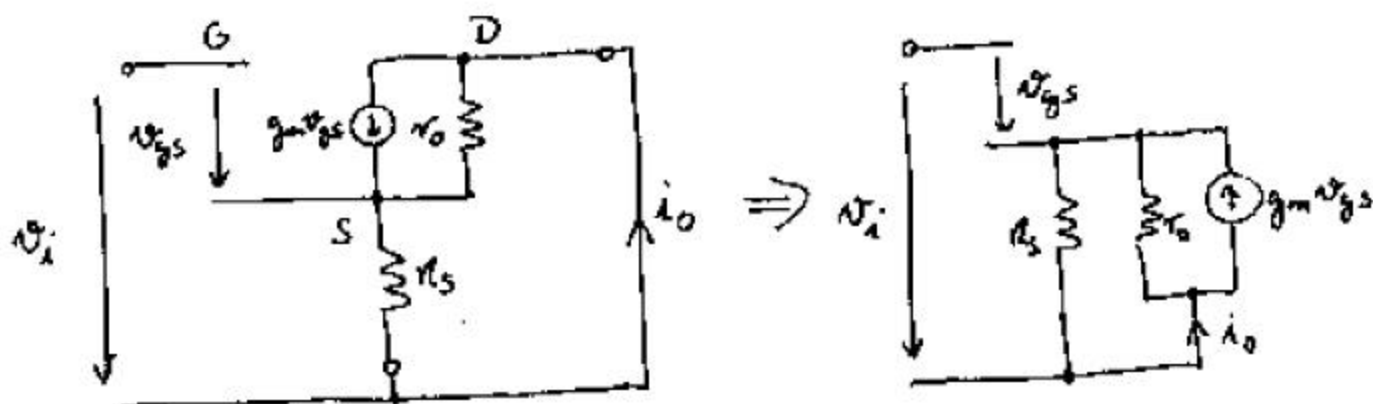① a) small signal model for compound device:



→ to find  $G_m$ , short output:  $G_m = \frac{i_o}{v_i}$



$$\Rightarrow v_i = v_{gs} + g_m v_{gs} (r_o \parallel R_s) \quad r_o \parallel R_s \stackrel{!}{=} R_p$$

$$i_o = g_m v_{gs} + g_m v_{gs} R_p / r_o$$


$$\Rightarrow \frac{i_o}{v_i} = G_m = \frac{g_m v_{gs} + g_m v_{gs} R_p / r_o}{v_{gs} + g_m v_{gs} R_p} = \frac{1 + \frac{R_p}{r_o}}{\frac{1}{g_m} + R_p}$$

$$\text{Since } R_s \ll r_o \Rightarrow R_p \approx R_s \\ \Rightarrow R_p / r_o \rightarrow 0$$

$$\Rightarrow \underline{\underline{G_m \approx \frac{1}{R_s + 1/g_m}}}$$

① a) ckt.

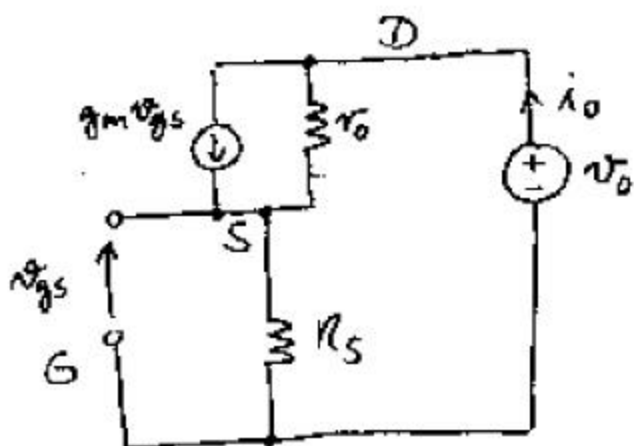→ to find  $R_o$ , short input and analyze  $\frac{v_o}{i_o}$



$$\Rightarrow v_o = i_o R_s + r_o (i_o - g_m v_{gs})$$

$$= i_o R_s + r_o (i_o + g_m i_o R_s)$$

$$\Rightarrow \frac{v_o}{i_o} = R_o = \overset{\ll r_o}{R_s} + \underline{\underline{r_o (1 + g_m R_s)}}$$

$$b) a_{vo} = -G_m R_o = - \frac{r_o (1 + g_m R_s)}{R_s + 1/g_m} = \underline{\underline{-g_m r_o}}$$

$$f_p = \frac{1}{2\pi R_o C_L} = \frac{1}{2\pi C_L r_o (1 + g_m R_s)} //$$

$$f_u = \frac{1}{2\pi} \frac{G_m}{C_L} = \frac{1}{2\pi C_L (R_s + 1/g_m)} = \frac{1}{2\pi} \frac{g_m}{C_L (1 + g_m R_s)} //$$

→ note that both  $f_p$  and  $f_u$  are reduced by the factor  $\frac{1}{1 + g_m R_s}$  compared to a non-degenerated amplifier.

	$R_s = 0$		$R_s = 500\Omega$	
① ②				
$a_{vo}$	50	no change!	50	
$f_p$	1.59 MHz	$\cdot 0.8$	1.27 MHz	
$f_u$	79.6 MHz	$\cdot 0.8$	63.7 MHz	

$$\frac{1}{1 + g_m R_s} = \frac{1}{1 + 500\mu\text{S} \cdot 500\Omega} = \underline{\underline{0.8}}$$

$$\text{d) } g_m \approx \sqrt{2I_D k_n' \frac{W}{L}} = \sqrt{1\text{mA} \cdot 200 \frac{\mu\text{A}}{\text{V}^2} \cdot 10} = 1.414 \text{ mS}$$


$$f_u(R_s=0) = \frac{1}{2\pi} \frac{g_m}{C_L} = \frac{1.414 \text{ mS}}{2\pi \cdot 1\text{pF}} = 225 \text{ MHz}$$

$$\frac{f_u(R_s=0)}{f_u(R_s=500\Omega)} = \frac{1}{1 + g_m R_s} = \frac{1}{1 + 1.414 \text{ mS} \cdot 500\Omega} = \underline{\underline{0.93}}$$

$$\rightarrow f_u(R_s=500\Omega) = 210 \text{ MHz}$$

→ Lost about 7% in bandwidth due to insufficient number of source contacts...

2 a)

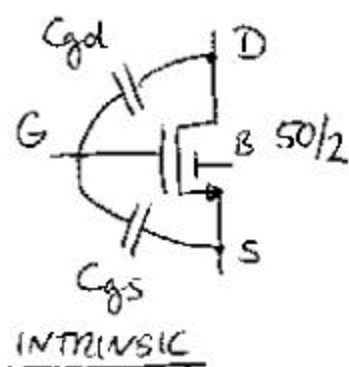

forward active:

$$C_{gs} \approx \frac{2}{3} W L C_{ox} = \frac{2}{3} \cdot 100(\mu\text{m})^2 \frac{5\text{fF}}{(\mu\text{m})^2} = \underline{\underline{333\text{fF}}}$$

$$C_{gd} \approx \underline{\underline{0}}$$

triode:

$$C_{gs} \approx C_{gd} \approx \frac{1}{2} W L C_{ox} = \underline{\underline{250\text{fF}}}$$

b) HSPICE printout see attached

	SIM	CALC		SIM	CALC
$C_{gs}$	333fF	333fF		296fF	250fF
$C_{gd}$	2fF	0		185fF	250fF
	SAT			TRIODE	


→ discrepancies:

1) SAT, TRIODE: HSPICE uses by default more accurate expressions than the one we used in our hand analysis. → see next page  
Especially in the triode region, our equation  $C_{gs} = \frac{1}{2} W L C_{ox}$  assumes that D and S have about the same potential → which is not true for this case...

For the forward active region, the agreement is good enough to predict the frequency response through hand analysis!

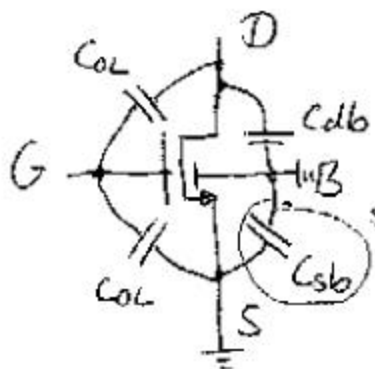c) EXTRINSIC:

$$C_{OL} = C_{OL}' \cdot W = \underline{\underline{25\text{fF}}}$$



$$C_{db} = A D \frac{C_{db0}}{\sqrt{1 + \frac{V_{db}}{V_0}}} \Rightarrow C_{db}|_{(V_{db}=1V)} = \underline{\underline{28.9\text{fF}}}$$

$$C_{db}|_{(V_{db}=3V)} = \underline{\underline{18.9\text{fF}}}$$

$$C_{sb} = A S \frac{C_{sb0}}{\sqrt{1 + \frac{V_{sb}}{V_0}}} = \underline{\underline{50\text{fF}}}$$

$$V_{sb} = 0$$

EECS140 HW4 Problem 2b -> HSPICE output



```

***** Transistor bias info for VG=1.5V, VD=3V
element 0:m1
  del 0:nmos2
  _d 718.7500u
  ibs 0.
  ibd -30.0000f
  vgs 1.5000
  vds 3.0000
  vbs 0.
  vth 1.0000
  vdsat 500.0000m
  beta 5.7500m
  gam_eff 500.0000m
  gm 2.8750m
  gds 31.2500u
  gmb 927.9023u
  cdtot 2.0018f
  cgtot 340.3371f
  cstot 333.6388f
  cbtot 4.6966f
  cgs 333.6388f
  cgd 2.0018f
  
```

Our cap model:

HSPICE default:

"smooth" transition

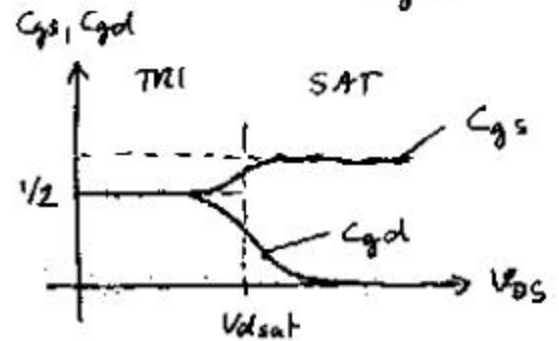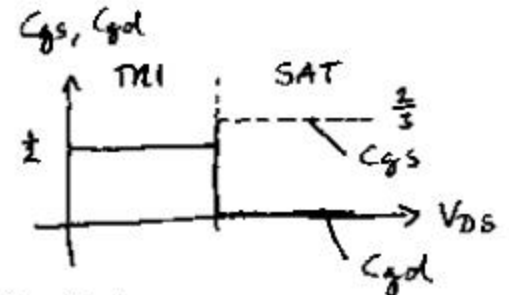

→ you get zero here if you set "capop = 0" in the device model (or "capop = 4")


```

***** Transistor bias info for VG=3V, VD=3V
element 0:m1
  model 0:nmos2
  id 7.8750m
  ibs 0.
  ibd -10.0000f
  vgs 3.0000
  vds 1.0000
  vbs 0.
  vth 1.0000
  vdsat 1.0000
  beta 5.2500m
  gam_eff 500.0000m
  gm 5.2500m
  gds 5.6250m
  gmb 1.6944m
  cdtot 185.3549f
  cgtot 483.1317f
  cstot 296.5678f
  cbtot 1.2090f
  cgs 296.5678f
  cgd 185.3549f
  
```

→ difference cgs - cgd due to different potential

② d) → HSPICE deck see attached

e)

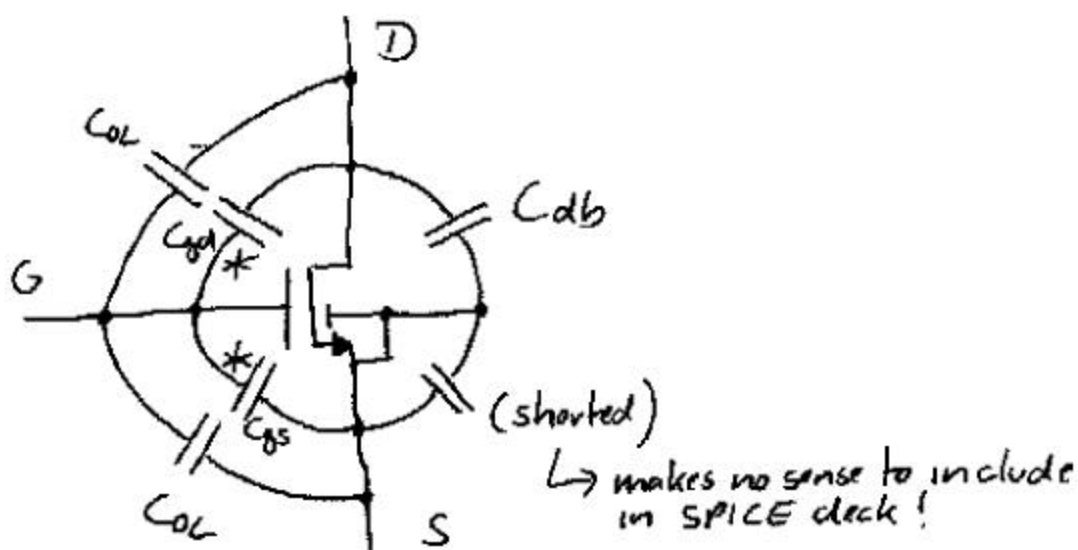

\* these capacitors are automatically modeled through SPICE.

We added  $C_{OL}$ ,  $C_{db}$  manually to complete the model.

③ a)  $C_{OL} = C_{OL}' \cdot W = 0.5 \text{ fF}/\mu\text{m} \cdot 40 \mu\text{m} = \underline{\underline{20 \text{ fF}}}$

$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_A - V_{TH})^2 (1 + \lambda V_{DS}) ; \lambda = 0.05$$
$$0.5 \text{ mA} = 2 \frac{\text{mA}}{\text{V}^2} (V_A - 1)^2 (1 + 0.15)$$

$$\Rightarrow \underline{\underline{V_A = 1.466 \text{ V}}} ; C_{gs} = \frac{2}{3} W L C_{ox} = \frac{2}{3} 80 \cdot 5 \text{ fF} = \underline{\underline{267 \text{ fF}}}$$

b)  $g_m = \frac{2 I_D}{V_{dsat}} = \frac{1 \text{ mA}}{0.466 \text{ V}} = 2.145 \text{ mS}$

$$r_o \approx \frac{1}{\lambda I_D} = \frac{1}{0.05 \cdot 0.5 \text{ mA}} = 40 \text{ k}\Omega \rightarrow \text{"large error"}$$

$$r_o = \frac{2}{k_n' \frac{W}{L} (V_{GS} - V_{TH})^2 \lambda} = \underline{\underline{46 \text{ k}\Omega}} \rightarrow \text{better}$$

EECS140 HW2 - Problem 2d

\*\*\*\* circuit description

m1 vd vg 0 0 nmos2 w=50um l=2um

\*\*\*\* the above line for M1 automatically takes care of the intrinsic caps,  
\*\*\*\* the following lines are for the extrinsic caps:

COL1 vg 0 25fF

COL2 vg vd 25fF

CDB vd 0 18.9fF

\*\*\*\* sources

vi 1 vg ac 1

vg 1 0 dc 1.5

vd vd 0 dc 3

\*\*\*\* analyses

.ac dec 10 1k 10k

\*\*\*\* model


.model nmos2 nmos level=1 vto=1 tox=6.9n kp=200u lambda=0.05 gamma=0.5 phi=0.6

.options brief


.end

③ b) ctd.  $|a_{v0}| = g_m r_o = 2.145 \text{ mS} \cdot 46 \text{ k}\Omega = \underline{\underline{98.67}}$

Small-signal circuit:

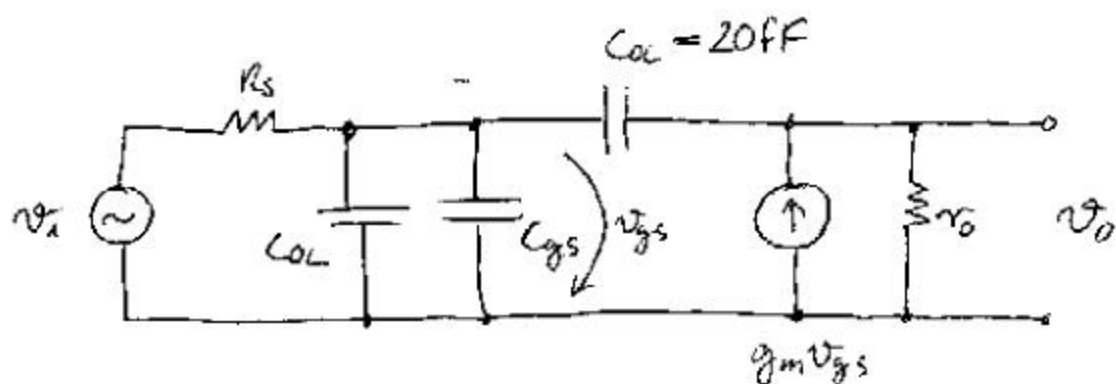

⇓ MILLER

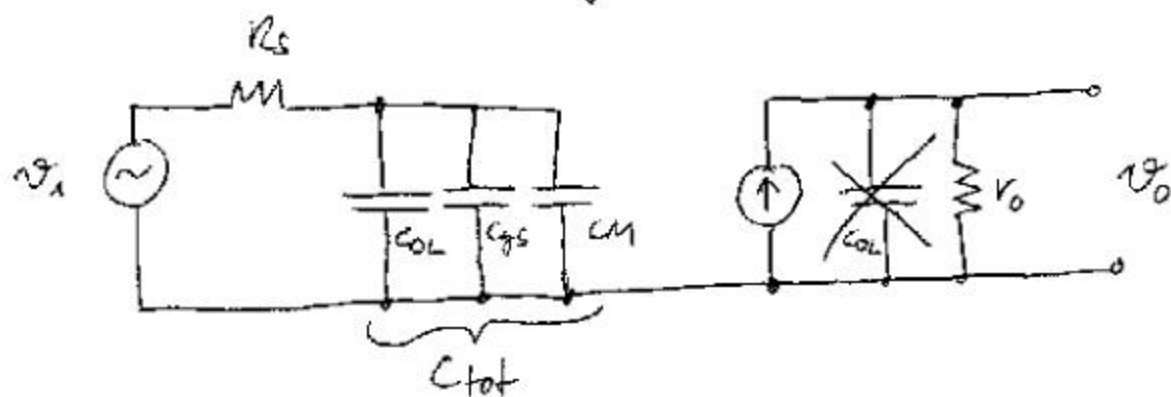

$$C_M = (1 + |a_{v0}|) C_{OL} = 1.97 \text{ pF} ! \Rightarrow C_{TOT} = \underline{\underline{2.25 \text{ pF}}}$$

$$\Rightarrow f_{p1} = \frac{1}{2\pi R_s C_{TOT}} = \frac{1}{2\pi \cdot 500 \text{ k} \cdot 2.25 \text{ pF}} = 141 \text{ kHz}$$

$$\Rightarrow f_u \approx f_{p1} |a_{v0}| = \underline{\underline{13.9 \text{ MHz}}}$$

④ Include  $C_{cb} = 30.23 \text{ pF}$


→ simulation plot see attached

\* C:\Dater\Berkeley\3E140\spice\hw4sim2.sch

Date/time run: 09/14/99 08:52:30

Temperature: 27.0

(A) hw4sim2.sac

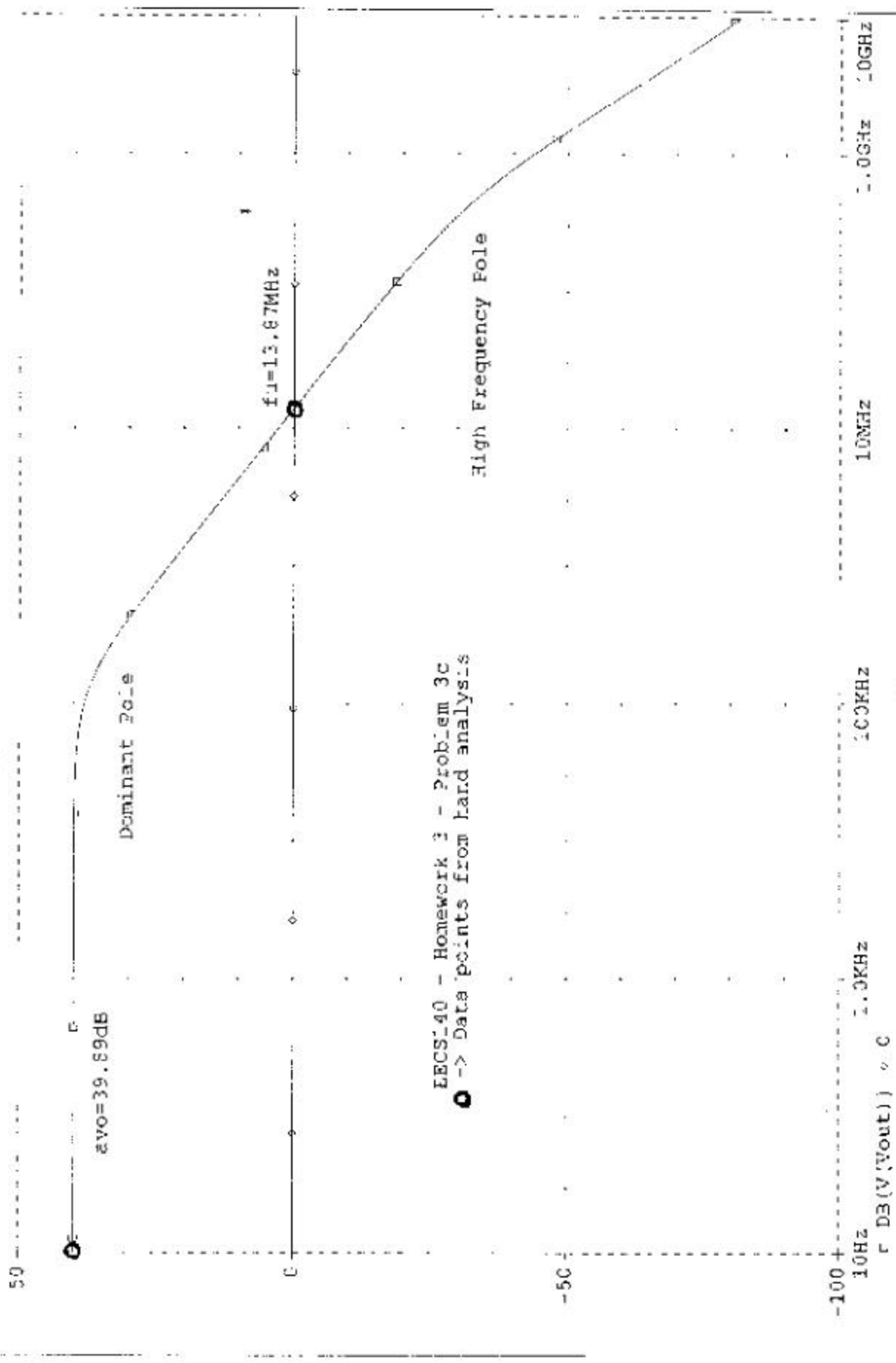

Frequency

48

③ d)

HSPICE

hand analysis

$|a_{v0}|$

39.8 dB  $\hat{=} 58.7$

98.7

$f_u$


13.87 MHz

13.9 MHz

→ exact match!

⇒ Miller approximation seems valid!

Verify pole frequency at output node:

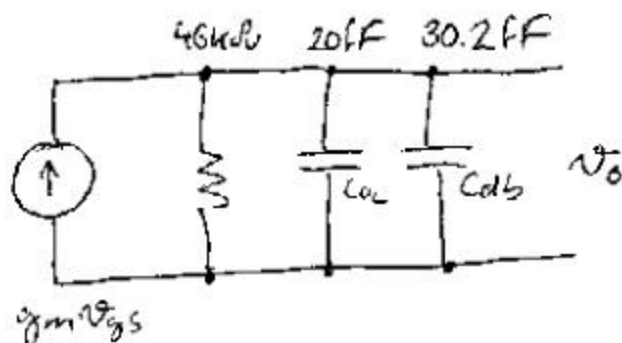

$$f_{p2} \approx \frac{1}{2\pi \cdot 50pF \cdot 46k} = \underline{\underline{69 \text{ MHz}}}$$

$$\underline{\underline{69 \text{ MHz} \gg \gg 141 \text{ kHz} = f_{p1}}}$$

→ That's why the Miller approximation works here!