

$$(1) a) I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$I_D = \frac{V_{DD} - V_O}{R_L} \quad V_{GS} = V_O - V_I \quad V_{DS} = V_O$$

$$\Rightarrow V_I = V_O - V_{TH} - \sqrt{\frac{2(V_{DD} - V_O)}{R_L (1 + \lambda V_O)} k_n' \frac{W}{L}}$$

→ for the circuit of Fig. 1b,  $V_{TH}$  depends on  $V_O$

$$|V_{SB}| = V_{DD} - V_O, \quad V_{TH} = V_{T0} + \gamma \left( \sqrt{V_{SB} + 2\phi_f} - \sqrt{2\phi_f} \right)$$

$$V_O = 5V: \quad V_{TH} = 1 + 0.5 \left( \sqrt{5+0.6} - \sqrt{0.6} \right) = 1.796V$$

$$V_O = 9V: \quad V_{TH} = 1 + 0.5 \left( \sqrt{1+0.6} - \sqrt{0.6} \right) = 1.245V$$

⇒ For circuit 1a:

$R_L$	$V_O$	$V_I$	$\frac{\Delta V_O}{\Delta V_I}$
1kΩ	5V	2.174V	$\frac{4}{5.101} = 0.784$
	9V	7.275V	
1MΩ	5V	3.942V	$\frac{4}{4.35} = 0.991$
	9V	7.977V	

⇒ For circuit 1b:

$R_L$	$V_O$	$V_{TH}$	$V_I$	$\frac{\Delta V_O}{\Delta V_I}$
1kΩ	5V	1.796V	1.378V	$\frac{4}{5.657} = 0.708$
	9V	1.245V	7.029V	
1MΩ	5V	1.796V	3.146	$\frac{4}{4.586} = 0.872$
	9V	1.245V	7.732	

① a) ctd. Analysis:


$$\rightarrow R_L \rightarrow \infty \Rightarrow \frac{\Delta V_o}{\Delta V_I} \rightarrow 1$$

$\rightarrow \frac{\Delta V_o}{\Delta V_I}$  decreases for small  $R_L$

$\rightarrow$  Including the body effect (Fig. 1b):

$\frac{\Delta V_o}{\Delta V_I} \neq 1$  even for large  $R_L$ , due to the change in  $V_{TH}$ ! (True for large signal swing at the output)

b)

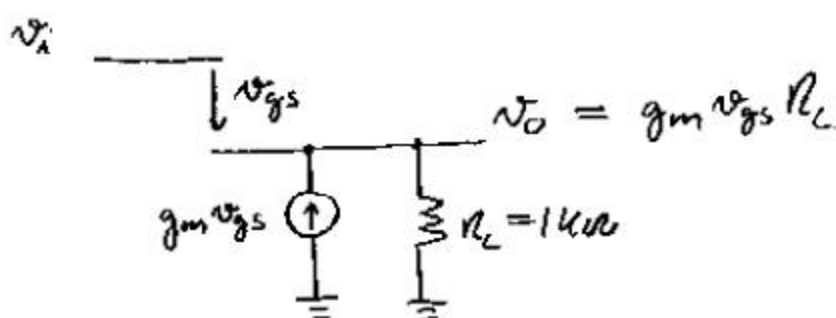

$$v_{gs} = v_i - v_o \Rightarrow v_o = (v_i - v_o) g_m R_L$$

$$\Rightarrow a_v = \frac{g_m R_L}{1 + g_m R_L} \quad ; \quad g_m = \sqrt{2 I_D k'_n \frac{W}{L}}$$

bias:  $I_D = \frac{V_{DD} - V_o}{R_L} \Rightarrow g_m = \sqrt{\frac{2(V_{DD} - V_o) k'_n \frac{W}{L}}{R_L}}$

$$\Rightarrow a_v = \frac{1}{1 + \frac{1}{\sqrt{2 R_L k'_n \frac{W}{L} (V_{DD} - V_o)}}} = f(R_L, V_o, \dots)$$

$$a_v(V_o = 5V) = \frac{1}{1 + \frac{1}{\sqrt{2 \cdot 1 \cdot 2 \cdot 5}}} = \underline{\underline{0.817}} \quad \left. \vphantom{a_v(V_o = 5V)} \right\} -18.4\%$$

$$a_v(V_o = 5V) = \frac{1}{1 + \frac{1}{\sqrt{2 \cdot 1 \cdot 2 \cdot 1}}} = \underline{\underline{0.667}}$$

① ② from DC sweep: ( $\lambda=0$ )

$$V_I (V_o = 5V) = 1.764V$$

$$V_I (V_o = 9V) = 7.000V$$

→ .tf results (see attached):

$$a_v (V_o = 5V) = 0.817$$

$$a_v (V_o = 9V) = 0.667$$

→ -18.4%

→ Simulation results match hand analysis

---

EECS140 - Homework 5 - Problem 1c

\*\*\*\* mosfet bias

```

element 0:m1
model 0:pmos1
id -4.9999m
ibs 0.
ibd 50.0000f
vgs -3.2361
vds -5.0001
vbs 0.
vth -1.0000
vdsat -2.2361
beta 2.0000m
gam_eff 500.0000m
gm 4.4721m
gds 0.
gmb 1.4434m
    
```

\*\*\*\* small-signal transfer characteristics

```

v(vo)/vi = 817.2552m
input resistance at vi = 1.000e+20
output resistance at v(vo) = 182.7448
    
```

\*\*\*\* mosfet bias

```


element 0:m1
model 0:pmos1
id -1.0000m
ibs 0.
ibd 90.0000f
vgs 2.0000
vds -9.0000
vbs 0.
vth 1.0000
vdsat -1.0000
beta 2.0000m
gam_eff 500.0000m
gm 2.0000m
gds 0.
gmb 645.4972u
    
```

\*\*\*\* small-signal transfer characteristics

```

v(vo)/vi = 666.6667m
input resistance at vi = 1.000e+20
output resistance at v(vo) = 333.3333
    
```

(2) a)

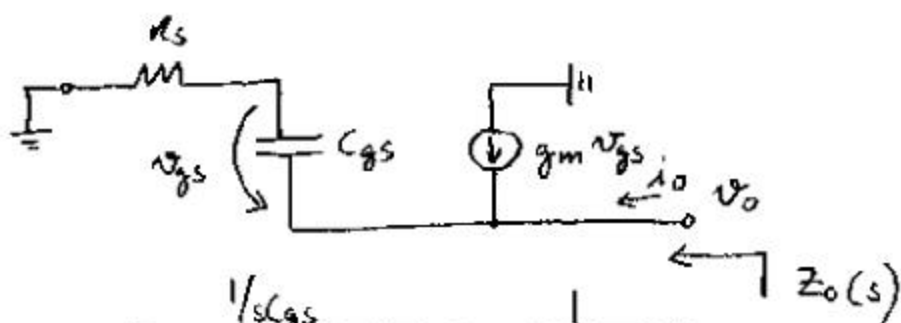

$$v_{gs} = -v_o \frac{1/sC_{gs}}{1/sC_{gs} + r_s} = \frac{1}{1 + s r_s C_{gs}}$$

$$i_o = v_o \left( \frac{1}{r_s + 1/C_{gs}} \right) + g_m v_o \left( \frac{1}{1 + s r_s C_{gs}} \right)$$

$$\Rightarrow Y_o = \frac{i_o}{v_o} = \frac{g_m + s C_{gs}}{1 + s r_s C_{gs}} = g_m \frac{1 + s \frac{C_{gs}}{g_m}}{1 + s r_s C_{gs}}$$

$$\Rightarrow Z_o(s) = \frac{1}{g_m} \cdot \frac{1 + s r_s C_{gs}}{1 + s \frac{C_{gs}}{g_m}} //$$

$$\begin{aligned} \text{b) } Z_{RL}(s) &= \frac{(R_1 + sL)R_2}{R_1 + R_2 + sL} \approx \frac{(R_1 + sL)R_2}{R_2 + sL} \quad \text{for } R_2 \gg R_1 \\ &= R_1 \frac{1 + s \frac{L}{R_1}}{1 + s \frac{L}{R_2}} \end{aligned}$$

→ compare with  $Z_o(s)$

$$\Rightarrow R_1 = \frac{1}{g_m}; \quad R_2 = r_s; \quad L = \frac{r_s C_{gs}}{g_m} //$$

→ see also reader pp. 7T14.

$$\text{c) } g_m = \sqrt{2I_D k' \frac{W}{L}} = 2.82 \frac{\text{mA}}{\text{V}}; \quad C_{gs} = \frac{2}{3} 20 \mu\text{m}^2 \cdot 5 \text{fF}/\mu\text{m}^2 = 66.$$

$$\begin{aligned} \Rightarrow R_1 &= \frac{1}{g_m} = \underline{\underline{356.6 \Omega}} \\ R_2 &= r_s = \underline{\underline{1 \text{M}\Omega}} \end{aligned} \quad \left. \vphantom{\begin{aligned} R_1 \\ R_2 \end{aligned}} \right\} \Rightarrow R_s \gg \frac{1}{g_m} \text{ holds } \checkmark$$

$$L = \frac{r_s C_{gs}}{g_m} = \underline{\underline{23.6 \mu\text{H}}}$$

- ② d) → see attached plot  
→ no discrepancies, exact match between model and real circuit!  
(at least after setting copop = 0!)

e) → see attached plot

→ Extracted from plot:

$$T \approx 21.8 \text{ ns} \Rightarrow f \approx \underline{\underline{45.87 \text{ MHz}}} \text{ (ringing frequency)}$$


→ Expected:

$$f_0 = \frac{1}{2\pi\sqrt{LC_L}} = \frac{1}{2\pi\sqrt{23.6\mu\text{H} \cdot 0.5\text{pF}}} = \underline{\underline{46.3 \text{ MHz}}}$$

⇒ Ringing frequency observed on plot is close to resonant frequency of an ideal LC resonator!

---

eecs140 hw5 - problem 2d

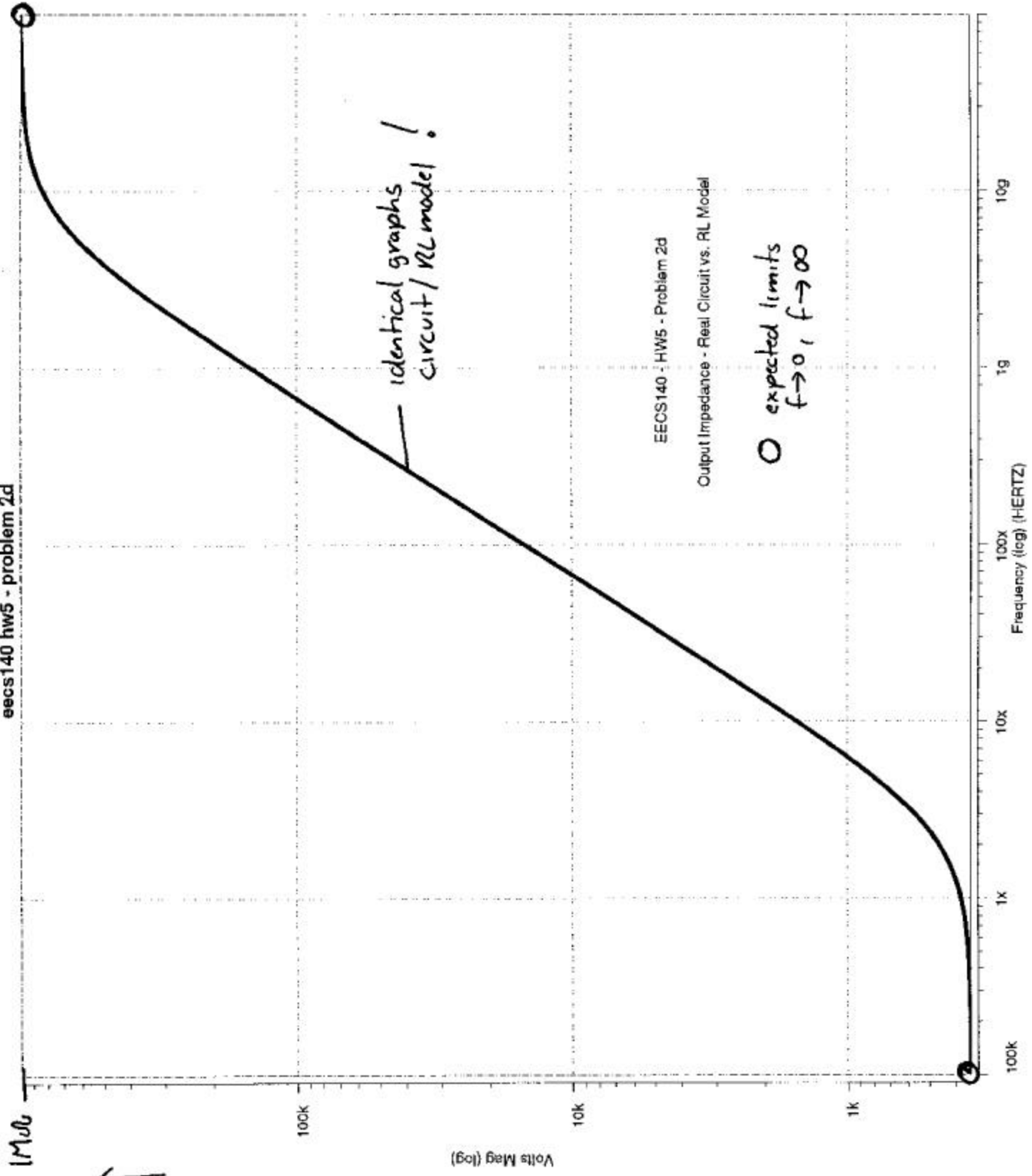

eeCS140 hw5 - problem 5e

