
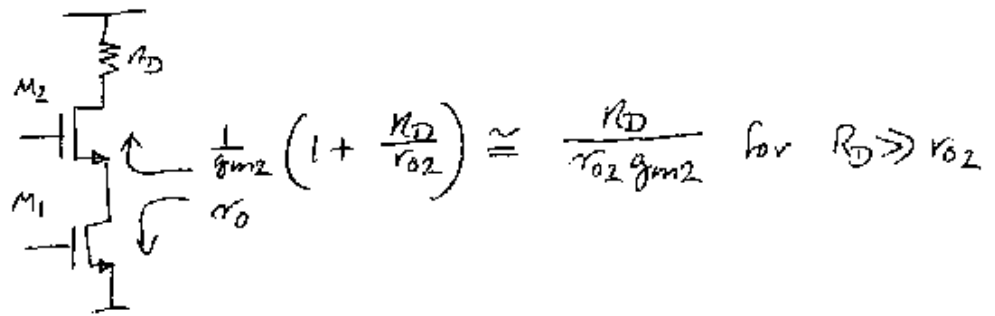


(1) a)

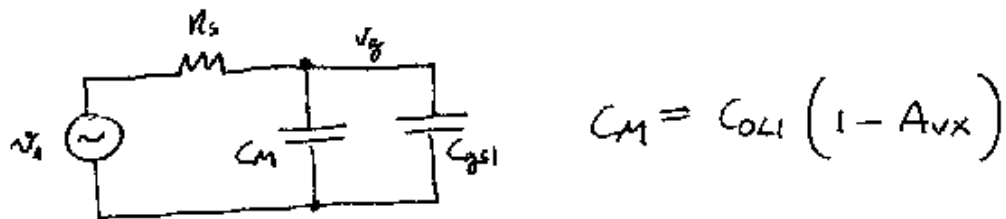

$$\Rightarrow R_x = \frac{1}{\frac{1}{r_{o1}} + \frac{g_{m2} r_{o2}}{R_D}} ; \quad A_{vX} = \frac{-g_{m1}}{\frac{1}{r_{o1}} + \frac{g_{m2} r_{o2}}{R_D}} //$$

b)



$$C_M = C_{o1} (1 - A_{vX})$$

$$\Rightarrow f_{p1} = \frac{1}{2\pi} \frac{1}{R_s [C_{o1} + C_{o1} (1 - A_{vX})]} //$$

$$c) \quad g_{m2} \approx \sqrt{2I_D k'_n \left(\frac{W}{L}\right)_2} = \sqrt{2\text{mA} \cdot 1\text{m}} = 1.41 \text{ mS}$$

$$g_{m1} \approx \sqrt{2I_D k'_n \left(\frac{W}{L}\right)_1} = \sqrt{2\text{mA} \cdot 20\text{m}} = 6.32 \text{ mS}; \quad C_{gs1} = \frac{2}{3} \cdot 100 \cdot 5 = 666 \text{ fF}$$

$$r_{o1} \approx r_{o2} \approx \frac{1}{\lambda I_D} = \frac{1}{0.1 \cdot 1\text{mA}} = 10 \text{ k}\Omega ; \quad C_{o1} = 100 \cdot 0.5 \text{ fF} = 50 \text{ fF}$$

$$\Rightarrow R_x = 10 \text{ k}\Omega \parallel \left(\frac{1 \text{ M}\Omega}{1.41 \text{ mS} \cdot 10 \text{ k}\Omega} \right) = 8.76 \text{ k}\Omega$$

$$\Rightarrow A_{vX} = -g_{m1} \cdot R_x = 6.32 \text{ mS} \cdot 8.76 \text{ k}\Omega = \underline{\underline{-55.39}}$$

$$\Rightarrow f_{p1} = \frac{1}{2\pi} \frac{1}{500 \text{ k} (50 \text{ fF} + 50 \text{ fF} \cdot 56.39)} = \underline{\underline{95.89 \text{ kHz}}}$$

$$f_{p1}^i = \frac{1}{2\pi} \frac{1}{500 \text{ k} \cdot 666 \text{ fF}} = 954.9 \text{ kHz}$$

$$\frac{f_{p1}}{f_{p1}^i} = \frac{95.89}{954.9} = \underline{\underline{15.1\%}} !$$

1/8

① d) → see attached plots

DC: found $V_{B1} = 1.3049 \text{ V} \Rightarrow V_o = 5.015 \text{ V}$


<u>AC</u> :	<u>SIMULATED</u>	<u>CALCULATED</u>
A_{vxo}	$34.97 \text{ dB} \hat{=} 56.0$	$55.39 \hat{=} 34.86 \text{ dB}$
($C_{OL} = 0$) f_{p1}	954.8 kHz	954.9 kHz
($C_{OL} = 50 \text{ fF}$) f_{p1}	99 kHz	95.89 kHz

→ good agreement

e) → decrease $R_D \Rightarrow$ "less" Miller effect, but also less gain a_{vo} !

→ increase g_{m2} by making $\left(\frac{W}{L}\right)_2$ larger
 \Rightarrow reduced Miller effect

(A) hw6sim1.dat

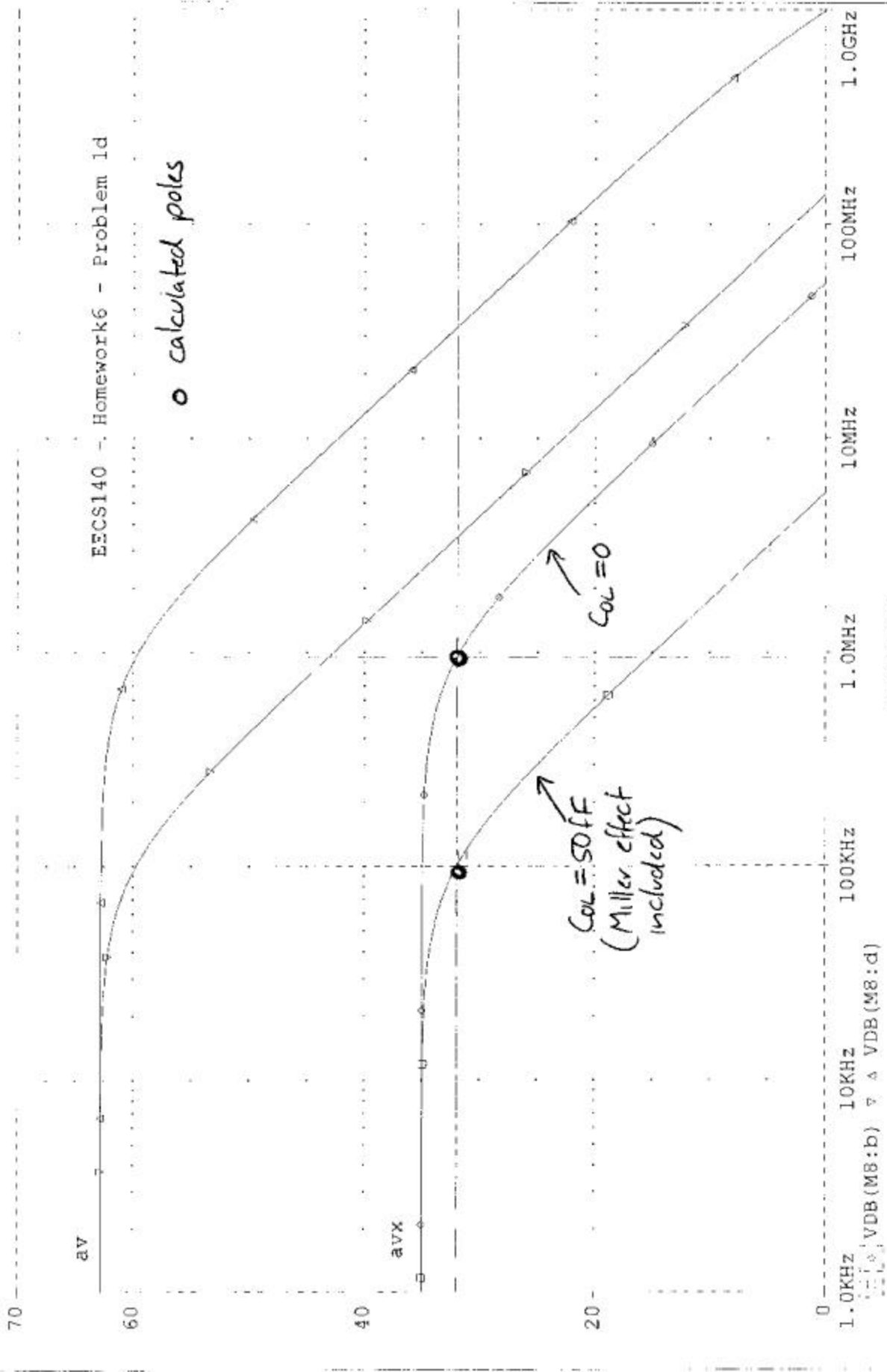

A1: (100.000K, 31.960) A2: (955.855K, 31.963) DIFF(A): (-855.855K, -2.9684m)


(2) a) $a_{voad} = -g_{m1} r_{o1}$

$a_{vob} = -g_{m1} (r_{o2} [1 + g_{m2} r_{o1}]); \quad g_{m2} r_{o1} \gg 1$

$\Rightarrow a_{vob} \approx -g_{m1} r_{o1} r_{o2} g_{m2}$

$\Rightarrow \frac{a_{vob}}{a_{voad}} = \underline{\underline{g_{m2} r_{o2}}}$

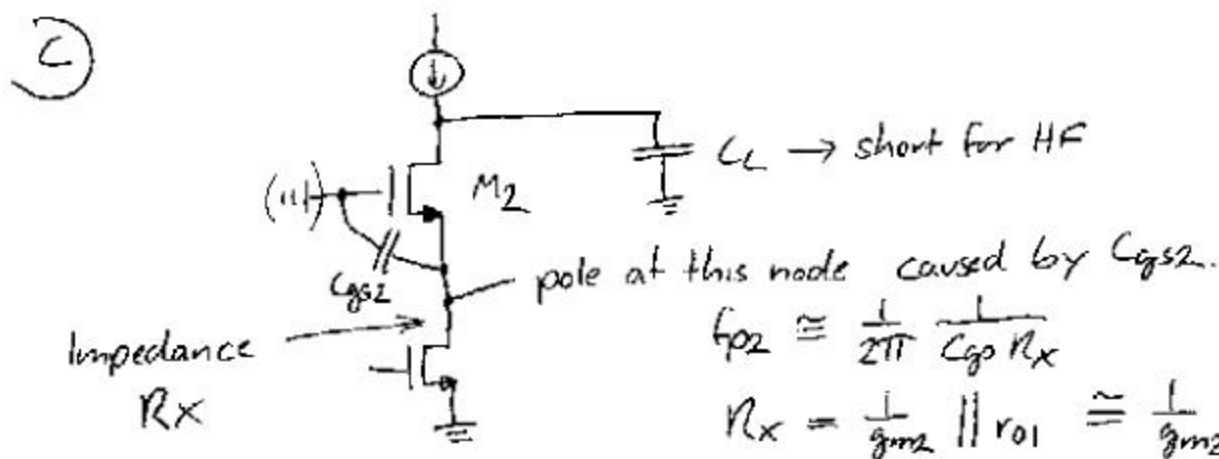b) $f_{p1a} = \frac{1}{2\pi} \frac{1}{r_{o1} C_L}$
 $f_{p1b} = \frac{1}{2\pi} \frac{1}{g_{m2} r_{o2} r_{o1} C_L}$ } $\frac{f_{p1a}}{f_{p1b}} = \underline{\underline{g_{m2} r_{o2}}}$



$\Rightarrow \underline{\underline{f_{p2} \approx \frac{1}{2\pi} \frac{g_{m2}}{C_{gs2}}}}$

\rightarrow this pole will typically occur at several GHz and is thus irrelevant!

d) $f_{ua} \approx a_{voad} \cdot f_{p1a}$
 $f_{ub} \approx a_{vob} \cdot f_{p1a}$ } $\Rightarrow \underline{\underline{\frac{f_{ub}}{f_{ua}} = 1}}$!

$$e) (a) g_{m1} \approx g_{m2} \approx \sqrt{2I_D k' \frac{W}{L}} = \sqrt{1m \cdot 4m} = 2mS = g_m$$

$$r_{o1} \approx r_{o2} \approx \frac{1}{\lambda I_D} = \frac{1}{0.1 \cdot 0.5mA} = 20k\Omega = r_o$$

$$\Rightarrow a_{voo} = -g_m r_o = \underline{40}$$

$$a_{vob} = -g_m^2 r_o^2 = \underline{1600} \quad \left. \vphantom{a_{vob}} \right\} \frac{a_{vob}}{a_{voo}} = 40$$

$$(b) f_{p1a} = \frac{1}{2\pi} \frac{1}{r_o C_L} = \frac{1}{2\pi \cdot 20k \cdot 0.5p} = \underline{15.92MHz}$$

$$f_{p1b} = \frac{1}{2\pi} \frac{1}{g_m r_o^2 C_L} = \underline{397.89kHz}$$

$$\left. \vphantom{f_{p1a}} \right\} \frac{f_{p1a}}{f_{p1b}} = 40$$

$$(c) f_{p2b} \approx \frac{1}{2\pi} \frac{g_{m2}}{C_{gs2}} \quad ; \quad C_{gs2} = \frac{2}{3} \cdot 20 \cdot 5FF = 66fF$$

$$\Rightarrow f_{p2b} \approx \frac{1}{2\pi} \frac{2mS}{66fF} = \underline{4.823GHz}$$

$$(d) f_{u1a} \approx f_{u1b} \approx a_{voo} \cdot f_{p1a} = \underline{636.8MHz}$$

f) \rightarrow see attached plot

DC: found $V_{B1} = 1.465V \Rightarrow V_o = 4.901V$

AC:

	SIMULATED	CALCULATED
a_{voo}	37.34dB	$40 \hat{=} 32dB$
a_{vob}	69.87dB	$1600 \hat{=} 64dB$
f_{p1a}	10.6MHz	15.9MHz
f_{p1b}	218kHz	397kHz
f_{u1a}	783MHz	637MHz
f_{u1b}	665MHz	637MHz

② f) continued:


→ large discrepancies between simulation and hand analysis! The discrepancies are due to neglecting the finite λ in the g_m and r_o calculations!

	calculated	simulated (SPICE listing)	
g_m	2mS	$M_{1b}: 2.15mS$ $M_{2b}: 2.31mS$	$M_{1a}: 2.45mS$
r_o	20k Ω	$M_{1b}: 23.1k\Omega$ $M_{2b}: 26.7k\Omega$	$M_{1a}: 30k\Omega$

→ this is a good example on how using the approximate equations $r_o \approx \frac{1}{\lambda I_D}$ and $g_m = \sqrt{2I_D \mu_n C_{ox} \frac{W}{L}}$ can introduce large discrepancies for "large" λ (short channel).

→ There is an exact agreement between hand calculations and simulation if the effect of λ is included into the hand calculations!

(B) hw62.dat

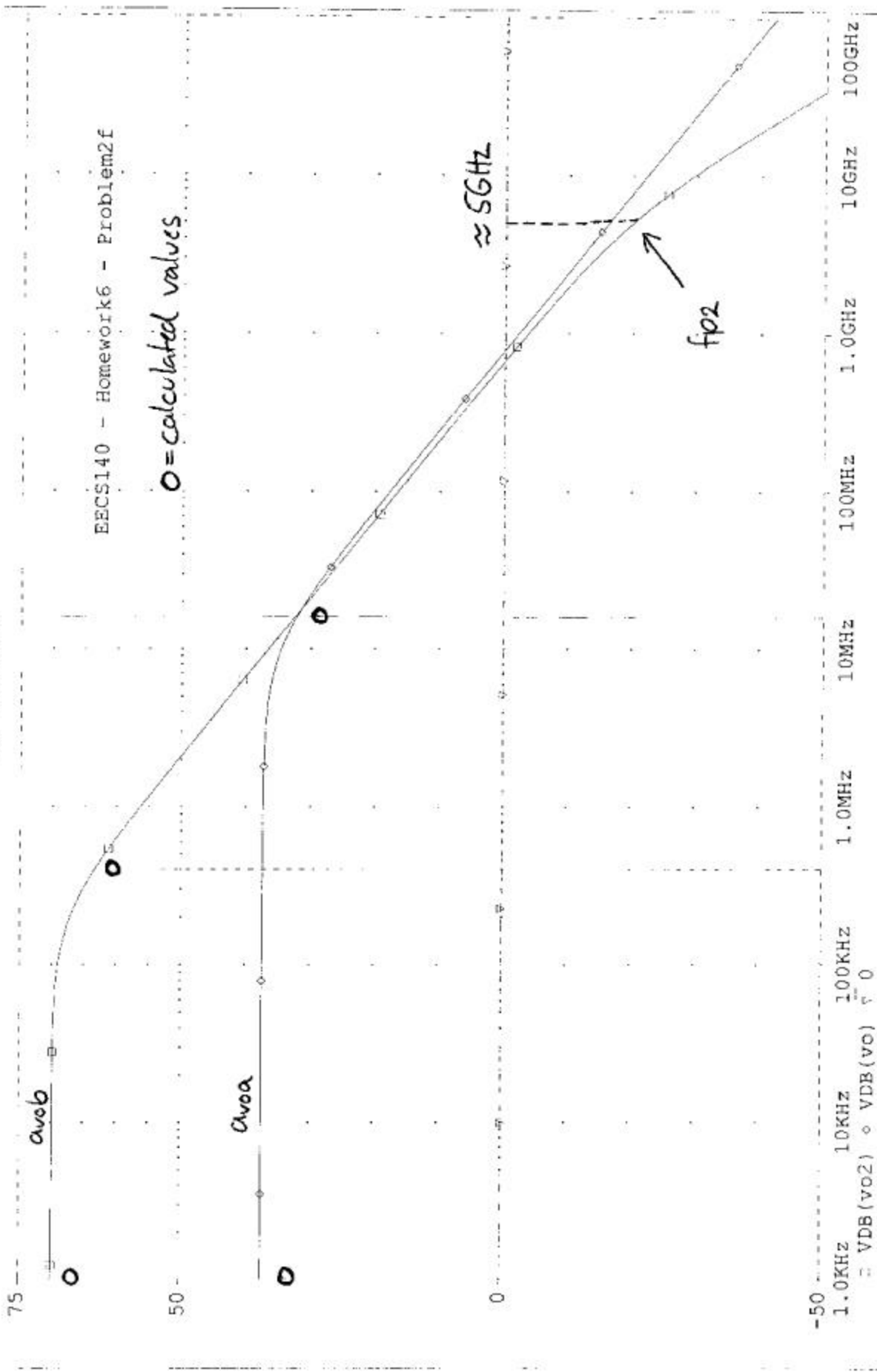

B1: (399.733K,0.000) B2: (15.979M,0.000) DIFF(B): (-15.579M,0.000)
 Date: October 04, 1999 Page 1

7/2

③ a) single devices: $V_{min} = V_{dsat}$
 $C_{out} = A\beta_2 \frac{C_{olbo}}{\sqrt{1 + \frac{V_{dsb}}{V_0}}} \propto W_2$

cascode: $V_{min} = V_{ds1}^{sat} + V_{ds2}^{sat} = 2V_{ds1}^{sat}$
 $C_{out} = A\beta_1 \frac{C_{olbo}}{\sqrt{1 + \frac{V_{dsb}}{V_0}}} \propto W_1$

$$\Rightarrow \underline{W_2 = W_1} \text{ for same } C_{out}$$

$$I_{D1} = I_{D2} \text{ and } 2V_{ds1}^{sat} = V_{ds2}^{sat}; W_2 = W_1$$

$$\Rightarrow \frac{1}{2} \mu_n \left(\frac{W_1}{L_1}\right) (V_{ds1}^{sat})^2 = \frac{1}{2} \mu_n \left(\frac{W_2}{L_2}\right) (2V_{ds1}^{sat})^2$$

$$\Rightarrow \underline{L_2 = 4L_1}$$

b) $R_{o1} \approx g_{m1} r_{o1}^2$; $R_{o2} = 4r_{o1}$ since $\lambda_2 = \frac{1}{4}\lambda_1$

$$\Rightarrow \frac{R_{o1}}{R_{o2}} = \frac{g_{m1} r_{o1}}{4}$$

c) $\left(\frac{W}{L}\right)_1 = \frac{10\mu}{2\mu} \rightarrow \left(\frac{W}{L}\right)_2 = \frac{10\mu}{8\mu}$

$$V_{min} = V_{dsat2} \approx \sqrt{\frac{2I_D}{\mu_n \left(\frac{W}{L}\right)_2}} = \sqrt{\frac{200\mu A}{200\mu A/V^2 \cdot \frac{10}{8}}} = \underline{894mV}$$

$$g_{m1} \approx \sqrt{2I_D \mu_n \left(\frac{W}{L}\right)_1} = \sqrt{2 \cdot 100\mu \cdot 1m} = 0.447mS$$

$$R_{o2} = \frac{1}{\lambda_2 I_D} = \frac{1}{\frac{0.1}{8} \cdot 100\mu} = \underline{800k\Omega}$$

$$r_{o1} \approx \frac{1}{\lambda_1 I_D} = \frac{1}{\frac{0.1}{2} \cdot 100\mu} = 200k\Omega$$

$$R_{o1} \approx g_{m1} r_{o1}^2 = \underline{17.88M\Omega}$$