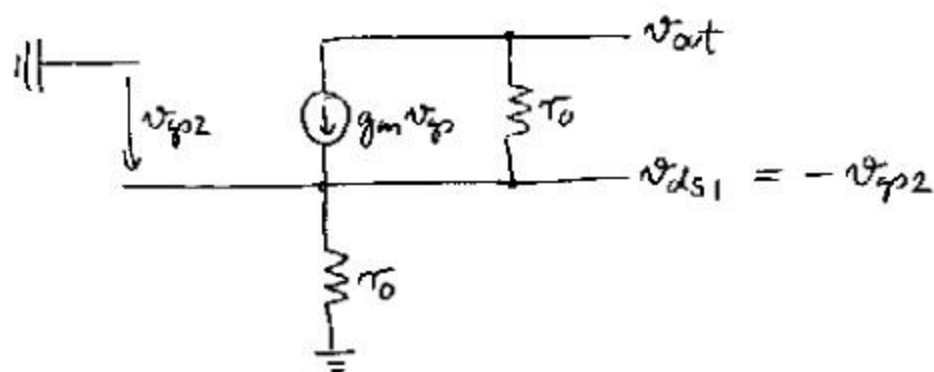


① a)



$$0 = -v_{ds1} \left( \frac{1}{r_o} + \frac{1}{r_o} + g_m \right) + \frac{1}{r_o} v_{out}$$

$$\Rightarrow \frac{v_{ds1}}{v_{out}} = \frac{1}{r_o \left( \frac{1}{r_o} + \frac{1}{r_o} + g_m \right)} \approx \frac{1}{g_m r_o}$$

$$\epsilon = \lambda (v_{ds1} - v_{ds3})$$

small signal:

$$\epsilon = \lambda (v_{ds1} - v_{ds3}) = \lambda \frac{v_{out}}{g_m r_o} \quad v_{in} = 0$$

$$\epsilon = \frac{\lambda (v_{out} - v_{in})}{g_m r_o} \xrightarrow{x} \frac{\lambda (v_{out} - v_{in})}{g_m r_o}$$

$$\epsilon = \frac{\lambda \Delta V}{g_m r_o}$$

$$\begin{array}{l} \text{b) simple mirror: } \epsilon_s = \lambda \Delta V \\ \text{cascode: } \epsilon_c = \frac{\lambda \Delta V}{g_m r_o} \end{array} \left. \vphantom{\begin{array}{l} \epsilon_s \\ \epsilon_c \end{array}} \right\} \frac{\epsilon_s}{\epsilon_c} = \frac{1}{g_m r_o}$$

$$\text{c) } \lambda = 0.05; \quad g_m = \sqrt{0.4 \text{ mA} \cdot 1 \text{ mA}} = 0.632 \text{ mS}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.05 \cdot 0.2 \text{ mA}} = 100 \text{ k}\Omega$$

$$\text{simple mirror: } \epsilon = \lambda \Delta V = 0.05 \cdot 2 \text{ V} = \underline{\underline{10\%}}$$

$$\text{cascode: } \epsilon = \frac{10\%}{0.632 \cdot 100} = \underline{\underline{0.16\%}}$$

2

$$I_{out} r_s = \sqrt{\frac{2I_w}{k'(\frac{W}{L})}} - \sqrt{\frac{2I_{out}}{k'(\frac{W}{L})}} \quad \text{let } x = \sqrt{I_{out}}$$

$$k = \sqrt{\frac{2}{k'(\frac{W}{L})}}$$

$$0 = x^2 + \frac{k}{r_s} x - \frac{k}{r_s} \sqrt{I_w}$$

$$x_{1,2} = -\frac{k}{2r_s} \pm \sqrt{\frac{k^2}{4r_s^2} + \frac{k}{r_s} \sqrt{I_w}}$$

$$\Rightarrow \sqrt{I_{out}} = \sqrt{\frac{k^2}{4r_s^2} + \frac{k}{r_s} \sqrt{I_w}} - \frac{k}{2r_s} \quad \frac{k}{r_s} = \frac{\sqrt{\frac{2}{20\text{m}}}}{100}$$

$$\frac{k}{r_s} = 0.1$$

$$\sqrt{I_{out}} = \sqrt{\frac{1}{4} \cdot 0.01 + 0.1 \sqrt{0.2\text{m}}} - 0.05$$

$$\sqrt{I_{out}} = 12.564 \quad \sqrt{A} \Rightarrow I_{out} = 157.8 \mu A$$

$$\Rightarrow \epsilon = \frac{157.8}{200} - 1 = \underline{\underline{-21.1\%}}$$

$$\Delta V_{GS} = I_{out} r_s = \sqrt{\frac{0.4}{20}} - \sqrt{\frac{0.3152}{20}} = \underline{\underline{15.8\text{mV}}}$$

3

a)  $V_{min} = 2V_{dsat} = 400\text{mV} \Rightarrow V_{dsat} = 200\text{mV}$


$$V_{dsat} = \sqrt{\frac{2I_D}{k'(\frac{W}{L})}} = \left(\frac{W}{L}\right) = \frac{2I_D}{V_{dsat}^2 k'} = \frac{0.2\text{m}}{0.04\text{m} \cdot 0.1\text{m}} = \underline{\underline{50}}$$

Can choose all  $\left(\frac{W}{L}\right) = 50$ , except  $\left(\frac{W}{L}\right)_5 = \frac{1}{3} \frac{W}{L} = \underline{\underline{16.67}}$ \*

\* in practice, you would use 3 devices in series:



3 b

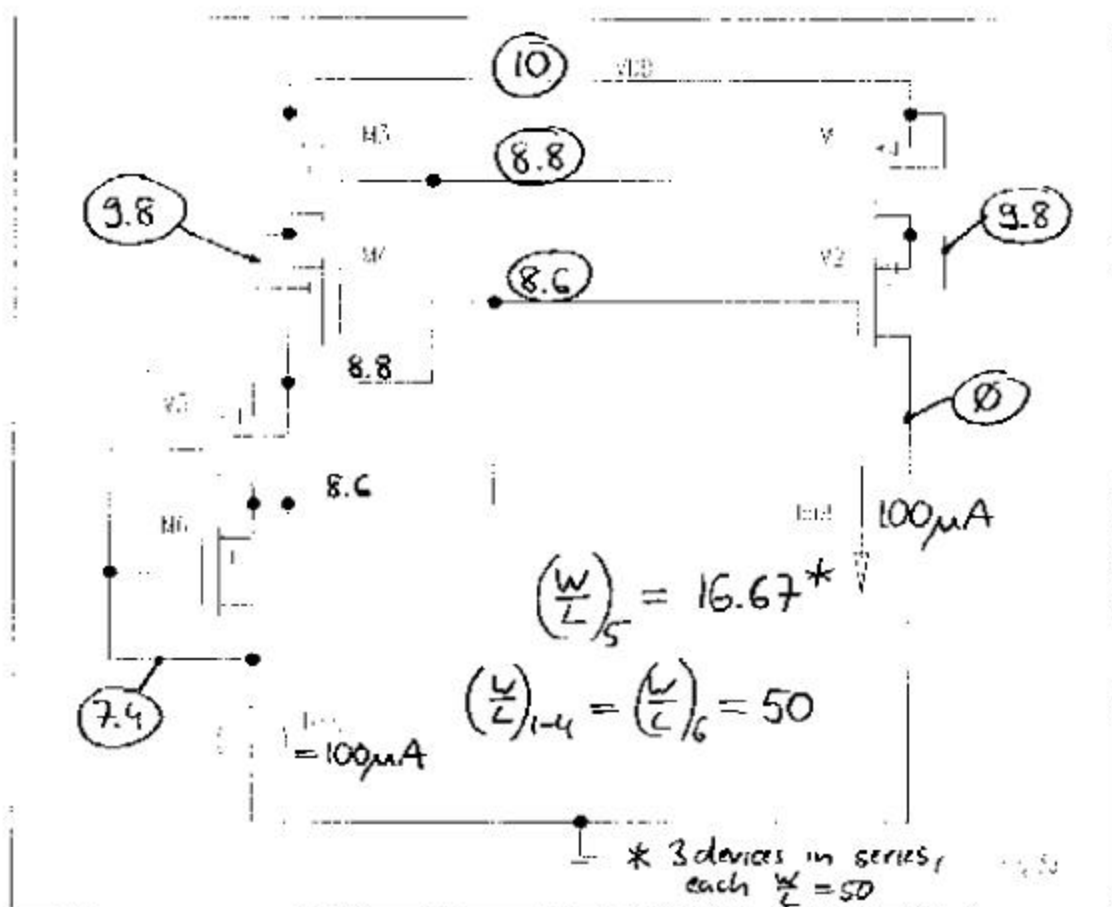

check ROP for M4:  $V_{DS} = 9.8 - 8.8 = 1V \geq V_{DSsat} = 0.2V \checkmark$   
 $\Rightarrow$  SAT

c) •  $\epsilon = 0$  with M4! (since  $V_{DS3} = V_{DS1}$ )

• without M4:  $V_{DS3} = V_{TH} + V_{DSsat}$   
 $V_{DS4} = V_{DSsat}$

$$\Rightarrow \underline{\underline{\epsilon = -\lambda V_{TH}}}$$

So, say I used  $L = 1\mu m$  in my design  $\Rightarrow \epsilon = -10\%$ !

$L = 2\mu m \Rightarrow \epsilon = 5\%$

$L = 3\mu m \Rightarrow \epsilon = 3.3\%$

$\rightarrow$  better  $\epsilon$  for longer channels!

3/6

4) a) → see text pp 3T.36

$$\Delta I_D = \frac{1}{2} k'_n \frac{W}{L} V_{id} \sqrt{\frac{4I_{SS}}{k'_n \frac{W}{L}} - V_{id}^2} \quad (3.162)$$

from Fig. 4:  $V_{od} = R_D \Delta I_D$ ;  $\Delta I_D = I_{D1} - I_{D2}$

$$\Rightarrow V_{od} = \frac{1}{2} k'_n \frac{W}{L} R_D V_{id} \sqrt{\frac{4I_{SS}}{k'_n \frac{W}{L}} - V_{id}^2}$$

$$\frac{dV_{od}}{dV_{id}} = \frac{1}{2} k'_n \frac{W}{L} R_D \left( \sqrt{\frac{4I_{SS}}{k'_n \frac{W}{L}} - V_{id}^2} + \frac{-2V_{id}^2}{2\sqrt{\frac{4I_{SS}}{k'_n \frac{W}{L}} - V_{id}^2}} \right)$$

$$\therefore A_{dm\phi} = \frac{1}{2} k'_n \frac{W}{L} R_D \sqrt{\frac{4I_{SS}}{k'_n \frac{W}{L}} - V_{id}^2} \left( 1 - \frac{V_{id}^2}{\frac{4I_{SS}}{k'_n \frac{W}{L}} - V_{id}^2} \right)$$

b) for  $V_{id}=0$ :  $A_{dm\phi} = \frac{1}{2} k'_n \frac{W}{L} R_D \sqrt{\frac{4I_{SS}}{k'_n \frac{W}{L}}}$

$$A_{dm\phi} = R_D \cdot \sqrt{I_{SS} k'_n \frac{W}{L}}; \quad I_{SS} = 2I_D$$

$$A_{dm\phi} = g_m R_D \quad !! \quad g_m = \sqrt{0.2 \text{mA} \cdot 10 \text{mA}} = 1.41 \text{mA/V}$$

$$\Rightarrow A_{dm\phi} = 1.41 \cdot 30 = \underline{\underline{42.42}}$$

for  $V_{id} = 100 \text{mV}$ :

$$A_{dm\phi} = 150 \sqrt{\frac{0.8 \text{mA}}{10 \text{mA}} - 0.01} \left( 1 - \frac{0.01}{\frac{0.8 \text{mA}}{10 \text{mA}} - 0.01} \right) = \underline{\underline{34.01}}$$

c) see attached plot:

(i) for  $V_{id} = 100 \text{mV} \rightarrow V_{od} = \underline{\underline{3.97 \text{V}}}$

(ii) max at  $V_{id} = 0 \rightarrow A_{dm\phi} = \underline{\underline{42.4 \text{ MAX}}}$

4) c) ii) cont.

min: @  $V_{od} = 5.5 \rightarrow V_{id} = 155\text{mV} \rightarrow A_{dm} = 20.3$

@  $V_{od} = -5.5 \rightarrow V_{id} = -155\text{mV} \rightarrow A_{dm} = 20.3$

$\Rightarrow$  minimum small signal gain 20.3! MIN

$$\frac{A_{dm\phi}(\text{max}) - A_{dm\phi}(\text{min})}{A_{dm\phi}(\text{max})} = \frac{42.4 - 20.3}{20.3} = \underline{\underline{52\%}}!$$

$\rightarrow$  The gain changes about 50% over a reasonable output swing! In practice, if the amplifiers output swings from  $-5.5$  to  $+5.5\text{V}$ , the lowest gain in this operating range should be quoted in a specification!

d)  $\rightarrow$  see text p. 3T.44

$$A_{cm} \approx \frac{g_m R_D}{1 + 2g_m R_x} = \frac{R_D}{\frac{1}{g_m} + 2R_x}$$

$$\underline{\underline{A_{cm} \approx \frac{1}{2} \frac{R_D}{R_x}}}$$

e)  $g_m = 1.41\text{mS} = \frac{1}{700\Omega}$  O.K.

$R_x = 100\text{k}\Omega$ :  $A_{cm} = \frac{1}{2} \frac{30}{100} = \underline{\underline{0.15}} \hat{=} -16.5\text{dB}$

$R_x = 10\text{M}\Omega$ :  $A_{cm} = \frac{1}{2} \frac{30}{10000} = \underline{\underline{1.5 \cdot 10^{-3}}} \hat{=} -56.5\text{dB}$

eecs140 hw7 - problem 4

