
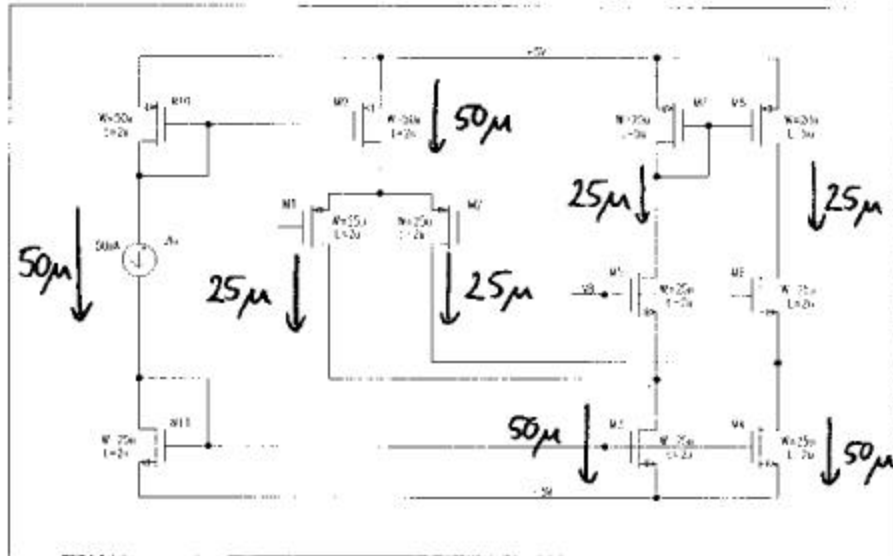



(1) a) (i)

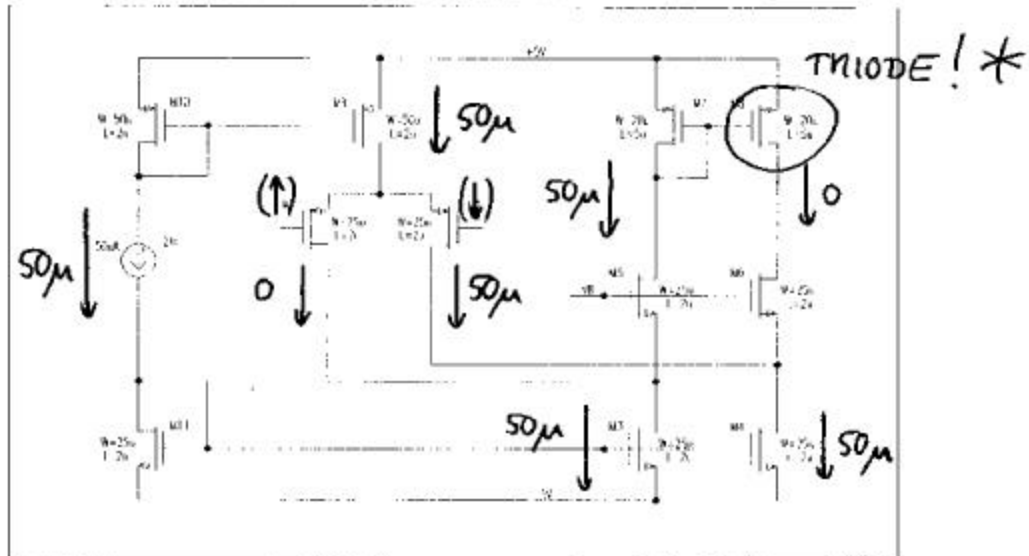

(ii)



(iii)

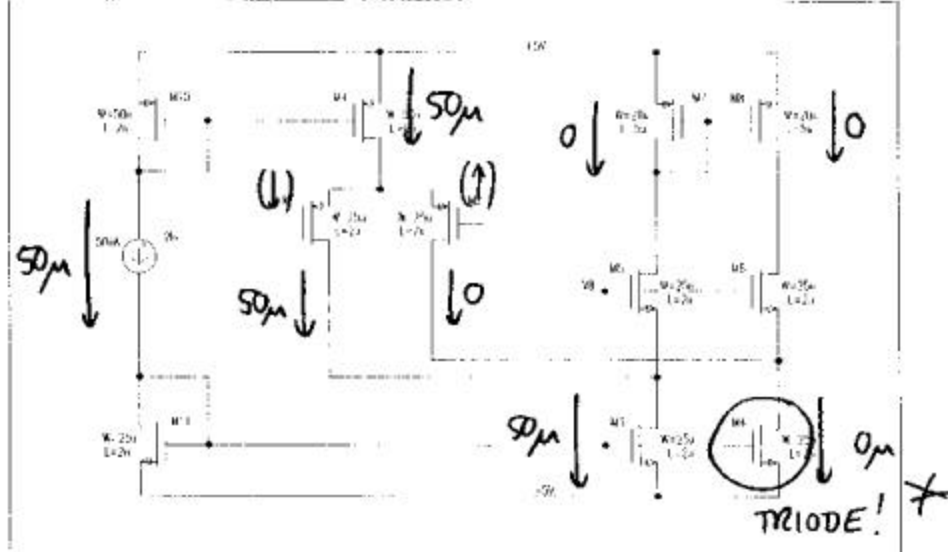

\* If the output is connected to ground, these devices stay forward active and carry 50µA, which then flows into the output... (another possible solution)

$$\textcircled{1} \textcircled{b} \text{ for } M3 \& M4: V_{dsat3} = \sqrt{\frac{2I_D}{\mu_n' \frac{W}{L}}} = \sqrt{\frac{2.50 \mu}{200 \mu \cdot 12.5}} = 200 \text{ mV}$$

for  $M4 \& M5$  we have to consider the max. drain current,  
i.e.  $I_{Dmax} = 2I_D$

$$\Rightarrow V_{dsat5}^{(max)} = \sqrt{\frac{2.50 \mu}{200 \mu \cdot 12.5}} = 200 \text{ mV}$$


$$\Rightarrow V_{Bmin} = V_{TH} + V_{dsat3} + V_{dsat5} = \underline{\underline{-3.6 \text{ V}}}$$

$$\textcircled{c} \text{ neg. swing: } V_{dsat5} = \sqrt{\frac{2.25 \mu}{200 \mu \cdot 12.5}} = 141 \text{ mV} = V_{dsat3}$$

$$\Rightarrow V_{omin} = V_{SS} + V_{dsat3} + V_{dsat5} = \underline{\underline{-4.72 \text{ V}}}$$

$$\text{pos. swing: } V_{dsat8} = \sqrt{\frac{2.25 \mu}{100 \mu \cdot 4}} = 353 \text{ mV}$$
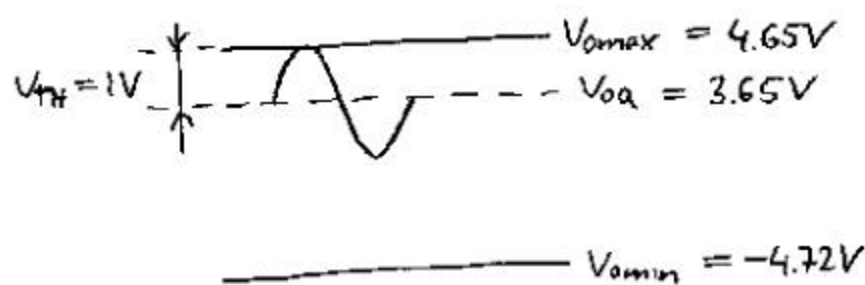
$$\Rightarrow V_{omax} = 5 \text{ V} - 353 \text{ mV} = \underline{\underline{4.65 \text{ V}}}$$



Bias voltage at output:  $V_{oq} = 5 \text{ V} - V_{dsat7} = 3.65 \text{ V}$   
(symmetry)

$\Rightarrow$  max output amplitude before clipping:

$$\hat{V}_o = V_{omax} - V_{oq} = V_{TH} = \underline{\underline{1 \text{ V}}}$$

$$d) G_m = g_{m1} = \sqrt{2I_D k' \frac{W}{L}} = \sqrt{50\mu \cdot 100\mu \cdot 12.5} = 250\mu S$$

$$R_o = r_{o8} \parallel g_{m6} r_{o6} r_{o4}$$

$$r_{o8} = \frac{1}{\lambda I_D} = \frac{1}{0.02 \cdot 25\mu} = 2M\Omega$$

$$r_{o6} = \frac{1}{0.05 \cdot 25\mu} = 800k\Omega$$

$$r_{o4} = \frac{1}{0.05 \cdot 50\mu A} = 400k\Omega$$

$$g_{m6} = \sqrt{100\mu \cdot 200\mu \cdot 12.5} = 500\mu S$$

$$\Rightarrow R_o = 2M\Omega \parallel 160M\Omega \approx 2M\Omega \quad \left( R_o \text{ dominated by } r_{o8} \dots \right)$$

$$\Rightarrow A_{dmo} = G_m R_o = 250\mu S \cdot 2M\Omega = \underline{\underline{500}}$$

$$e) V_{OQ} = 3.65V \text{ at bias point}$$

$$\text{middle of operating range: } \frac{V_{omax} + V_{omin}}{2} = \frac{4.65 - 4.72}{2} = 35mV \approx 0V$$

$$\Rightarrow \Delta V_o = 3.65V \text{ required at the output}$$

$$\Rightarrow \Delta V_{id} = \frac{\Delta V_o}{A_{dmo}} = \frac{3.65V}{500} = \underline{\underline{7.3mV}}$$

$$f) f_u = \frac{G_m}{2\pi C_L} = \frac{250\mu S}{2\pi 10pF} = \underline{\underline{4MHz}}$$

non-dominant pole due to current mirror M7-M8:

$$f_{p2} = \frac{1}{2\pi} \frac{g_{m7}}{2C_{gs7}}$$

$$g_{m7} = \sqrt{50\mu \cdot 100\mu \cdot 4} = 141\mu S$$

$$C_{gs7} = \frac{2}{3} \cdot 100 \cdot 51fF = 333fF$$

$$\Rightarrow f_{p2} = \underline{\underline{33.6MHz}}$$

f) ctd:

(check for second pole due to cascode M5-M6)

$$f_{p3} = \frac{1}{2\pi} \frac{\sqrt{25\mu \cdot 200\mu \cdot 12.5}}{\frac{2}{3} \cdot 50 \cdot 5 \text{ fF}} = \frac{250\mu\text{s}}{2\pi \cdot 166.7 \text{ fF}} = 238 \text{ MHz}$$

$$f_{p3} \gg f_{p2} \checkmark$$


g) → see attached plots. (used  $V_{in} = 0V$ )

	<u>CALCULATED:</u>	<u>SIMULATED:</u>	( <u>ERROR</u> )
Aclimo	<u>500</u> $\hat{=}$ 54dB	57dB $\hat{=}$ <u>707</u>	-30%
$f_u$	<u>4MHz</u>	<u>4.7MHz</u>	-15%
$f_{p2}$	<u>33MHz</u>	<u><math>\approx</math> 40MHz</u>	

→ reasonable agreement, discrepancies due to neglecting  $\lambda$  in the hand analysis

---

(A) hw9sim2

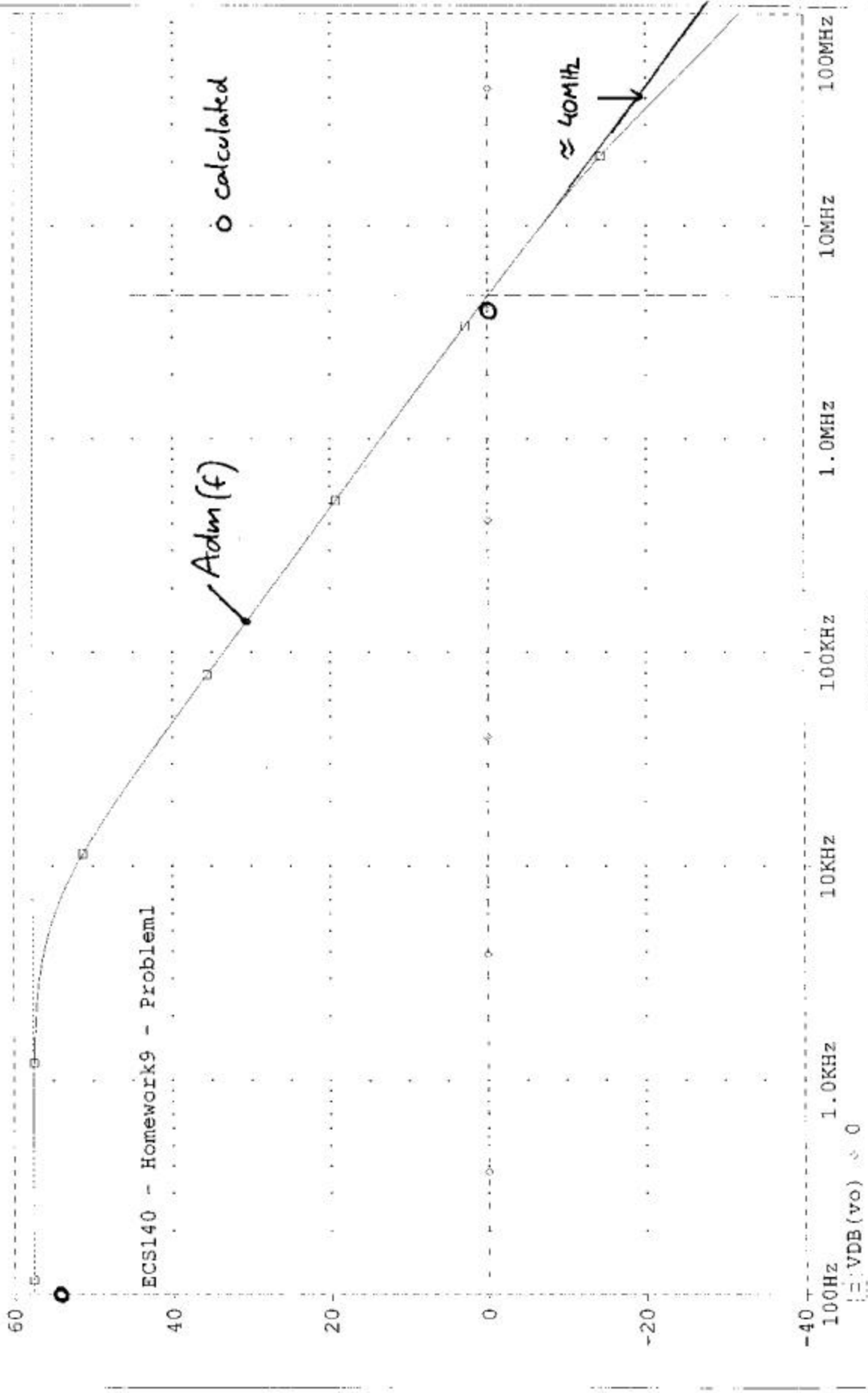

5/5