

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering**  
**and Computer Sciences**

**B. E. Boser**

**Midterm I**  
 - closed book, 5.5" x 8.5" summary ok -

**EECS 140**  
**Fall 1999**

Device Parameters (except where otherwise noted):

Parameter	Unit	NMOS	PMOS
Threshold voltage, $V_{TH}$	V	1	-1
Gate capacitance, $C_{ox}$	fF/ $\mu\text{m}^2$	5	5
Transconductance coefficient, $k_p = \mu C_{ox}$	$\mu\text{A}/\text{V}^2$	200	100
Channel length modulation, $\lambda(L)$ , L in $\mu\text{m}$	$\text{V}^{-1}$	0.1/L	0.1/L
Body effect coefficient, $\gamma$	$\sqrt{V}$	0.5	0.5
Surface potential, $2\phi_f$	V	0.6	0.6
Overlap Capacitances	$C_{ov} = W \cdot 0.5 \text{ fF}/\mu\text{m}$		
Drain and source area	$A_S = A_D = W \cdot 1 \mu\text{m}$		
Zero bias junction capacitance	$C_{j0} = C_{j00} = 1 \text{ fF}/\mu\text{m}^2$		
Built-in junction potential	$\psi_0 = 0.5 \text{ V}$		
Fractional temperature coefficient of resistors	$TCF = \frac{1}{R} \frac{\partial R}{\partial T} = -1000 \text{ ppm}/^\circ\text{C}$		
Base-Emitter voltage temperature dependence	$\frac{dV_{BE}}{dT} = -1.5 \text{ mV}/^\circ\text{C}$		

- Show your calculations on exam sheets (no credit for numerical result only) -

Name: Solution (5 points)


Result summary: (5 points)

- Problem 1 a)  $R = \underline{239.5 \Omega}$   
 b)  $TCF = \underline{4333 \text{ ppm}/^\circ\text{C}}$
- Problem 2  $I_{D1} = \underline{4.675 \mu\text{A}}$
- Problem 3 a)  $a_{v0} = \underline{-42.16}$   
 b)  $f_p = \underline{2.39 \text{ MHz}}$
- Problem 4 a)  $C_x = \underline{51.7 \text{ fF}}$   
 b)  $f_{p1} = \underline{711.7 \text{ MHz}}$
- Problem 5 a)  $V_T = \underline{1.979 \text{ V}}$   
 b)  $C_L = \underline{46.3 \text{ fF}}$

- Each Problem is worth 18 points-

**Problem 1**

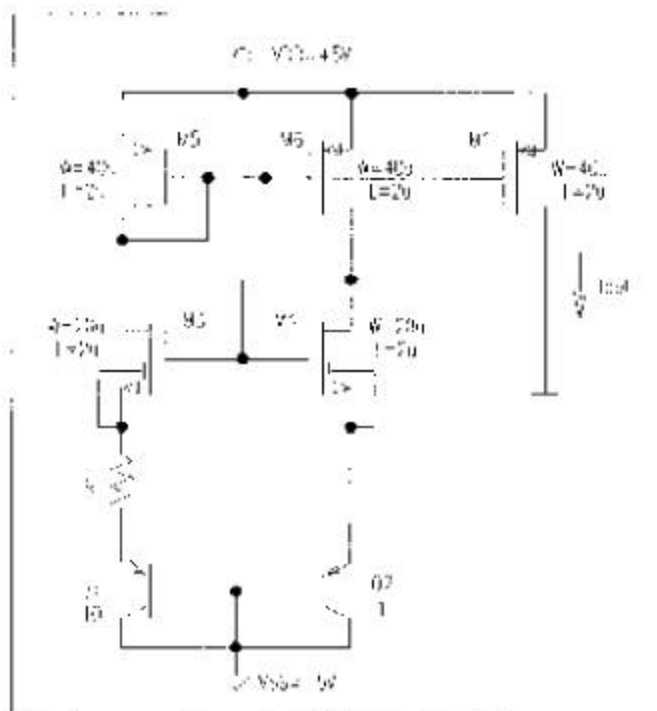- a) Find the value of R such that  $I_{out} = 250 \mu A$  at room temperature. Assume  $\lambda = 0$  and  $\beta \rightarrow \infty$ .  
 b) Find  $TC_F$  of  $I_{out}$  for  $R = 1 k\Omega$  (this is not the correct answer for (a)!) )



$$a) \quad I_{out} = \frac{V_t}{R} \ln n$$


$$R = \frac{V_t}{I_{out}} \ln n = \frac{26mV}{0.25mA} \cdot \ln 10 = \underline{\underline{239.5 \Omega}}$$

$$b) \quad TC_F = \frac{1}{I_{out}} \frac{\partial I_{out}}{\partial T} = \frac{1}{T} - \frac{1}{R} \frac{\partial R}{\partial T}$$

$$TC_F = 3333 \text{ ppm}/^\circ C + 1000 \text{ ppm}/^\circ C = \underline{\underline{4333 \text{ ppm}/^\circ C}}$$
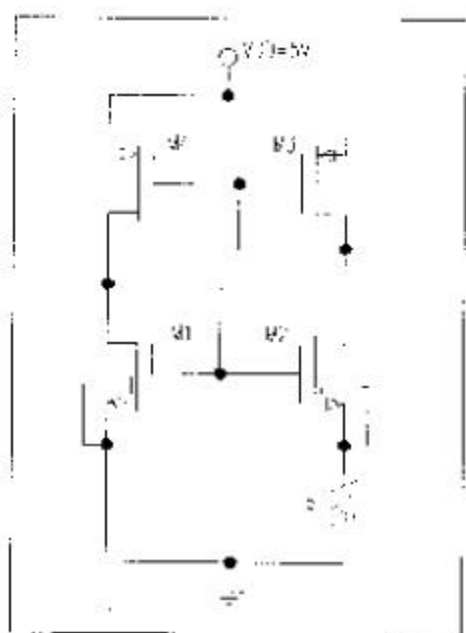
### Problem 2

Find the drain current  $I_{D1}$  in M1. Assume that all devices operate in the forward active region and  $\lambda=0$ .  $(W/L)_1=10$ ,  $(W/L)_2=100$ ,  $(W/L)_3=(W/L)_4$ ,  $R=10k\Omega$ .



$$R I_{D1} + \sqrt{\frac{2 I_{D1}}{\mu' \left(\frac{W}{L}\right)_2}} - \sqrt{\frac{2 I_{D1}}{\mu' \left(\frac{W}{L}\right)_1}} = 0$$

$$R \sqrt{I_{D1}} \left( \sqrt{I_{D1}} + \frac{1}{R} \left[ \sqrt{\frac{2}{\mu' \left(\frac{W}{L}\right)_2}} - \sqrt{\frac{2}{\mu' \left(\frac{W}{L}\right)_1}} \right] \right) = 0 ; \sqrt{I_{D1}} \neq 0$$


$$\Rightarrow \sqrt{I_{D1}} = \frac{1}{R} \left( \sqrt{\frac{2}{\mu' \left(\frac{W}{L}\right)_1}} - \sqrt{\frac{2}{\mu' \left(\frac{W}{L}\right)_2}} \right)$$

$$\sqrt{I_{D1}} = \frac{1}{10k} \left( \sqrt{\frac{2}{2mA/V^2}} - \sqrt{\frac{2}{20mA/V^2}} \right) \Rightarrow I_{D1} = \underline{\underline{4.675 \mu A}}$$

### Problem 3

In the circuit below, the DC value of  $V_i$  is adjusted such that  $V_o = 2V$

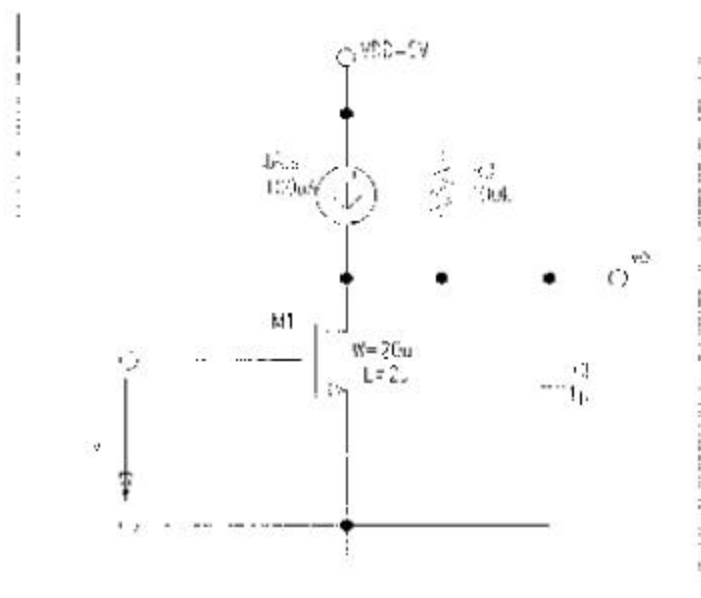- a) What is the low frequency small signal voltage gain  $A_{vo} = v_o/v_i$ ?
- b) Find the pole frequency  $f_p$  of  $A_{v(s)} = V_o(s)/V_i(s)$ .



$$a) \quad r_{o1} = \frac{1}{\lambda I_D} = \frac{1}{0.05 \cdot 0.1\text{mA}} = 200\text{k}\Omega$$


$$g_{m1} = \sqrt{2I_D k' \frac{W}{L}} = \sqrt{0.2\text{mA} \cdot 2\text{mA}} = 632.5\text{mS}$$

$$A_{vo} = -g_{m1} (r_{o1} \parallel R_D) = -632.5\text{mS} \cdot 66\text{k}\Omega = \underline{\underline{-42.16}}$$

$$b) \quad f_p = \frac{1}{2\pi} \frac{1}{(r_{o1} \parallel R_D) C_L} = \frac{1}{66\text{k}\Omega \cdot 1\text{pF}} \cdot \frac{1}{2\pi} = \underline{\underline{239\text{MHz}}}$$

#### Problem 4

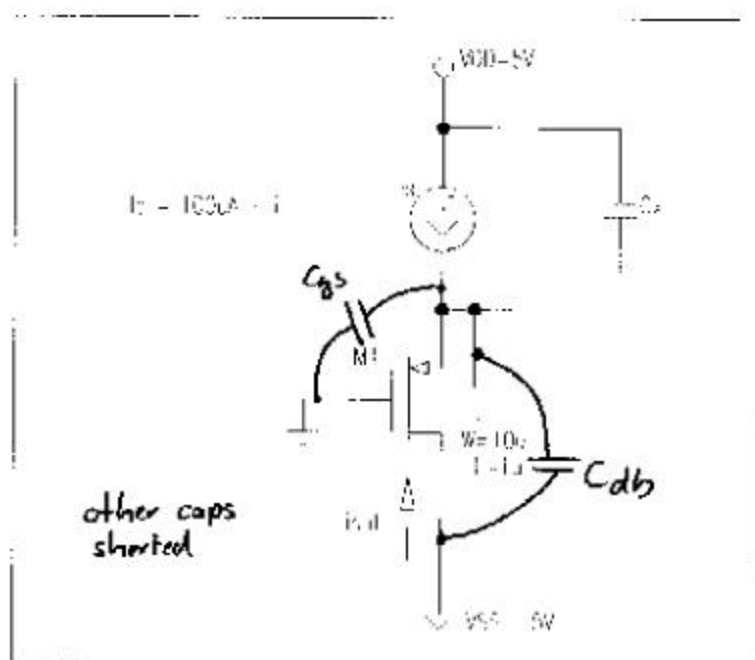- a) In the circuit below,  $C_x$  represents the intrinsic and extrinsic capacitances associated with M1. Find the value of  $C_x$ . Hint: Draw the small signal model for the circuit. Use  $AS=AD= W \cdot 5\mu\text{m}$ .
- b) Assuming  $C_x=100\text{fF}$  (not the correct answer for (a)!), find the pole frequency  $f_{p1}$  of the small signal current gain  $A_i(s)=i_{\text{out}}(s)/i_s(s)$ .



$$a) \quad C_x = C_{gs} + C_{db} ; \quad C_{gs} = \frac{2}{3}WL C_{ox} + C_{ol} = 33.3\text{fF} + 5\text{fF} = 38.3\text{fF}$$

$$V_{db} = 5V + V_{GS} ; \quad V_{GS} \cong 1V + \sqrt{\frac{2 \cdot 100\mu}{1\text{m}}} = 1.447V$$

$$\Rightarrow V_{db} = 5V + 1.447V = 6.447V \quad C_{db} = AD \frac{C_{db0}}{\sqrt{1 + \frac{V_{db}}{V_0}}}$$

$$\Rightarrow C_{db} = 50\mu\text{m}^2 \frac{1\text{fF}/\mu\text{m}^2}{\sqrt{1 + \frac{6.447}{0.5}}} = 13.41\text{fF}$$


$$\Rightarrow C_x = 38.3\text{fF} + 13.41\text{fF} = \underline{\underline{51.7\text{fF}}}$$

$$b) \quad f_{p1} = \frac{1}{2\pi} \frac{g_m}{C_x} ; \quad g_m = \sqrt{2 \cdot 100\mu \cdot 1\text{m}} = 0.447\text{mS}$$

$$f_{p1} = \frac{1}{2\pi} \frac{0.447\text{mS}}{100\text{fF}} = \underline{\underline{711.7\text{MHz}}}$$

**Problem 5**

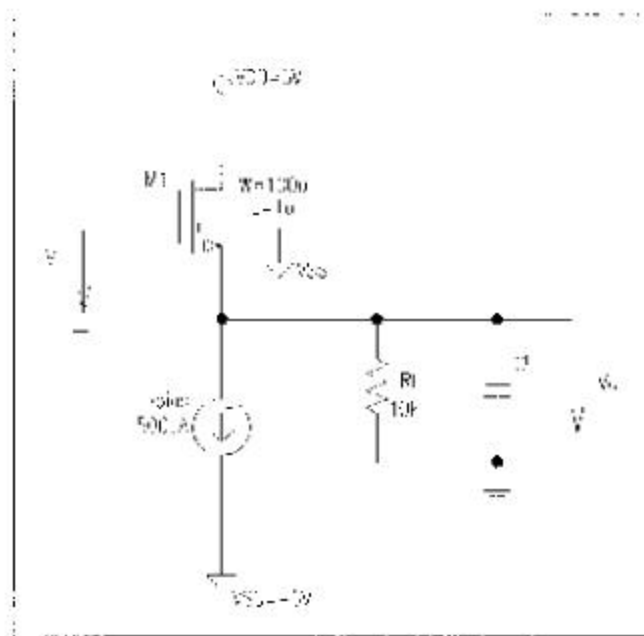- a) Find the large signal value of  $V_I$  for  $V_O = 0V$ . Beware: M1 has body effect!  
 b) Find the value of  $C_L$  for which the bandwidth of the circuit goes to infinity (i.e. all poles and zeros cancel).



$$a) V_{TH} = V_{T0} + \gamma \left( \sqrt{V_{SB} + 2\phi_f} - \sqrt{2\phi_f} \right)$$

$$V_{TH} = 1V + 0.5V \left( \sqrt{5 + 0.6} - \sqrt{0.6} \right) = 1.796V$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_I - V_{TH})^2 (1 + \lambda V_{DS})$$

$$0.5 = 10 (V_I - 1.796)^2 (1 + 0.5) \Rightarrow \underline{\underline{V_I = 1.979V}}$$

$$b) z = \frac{g_m}{C_{gs}} ; p = \frac{g_m + \frac{1}{r_o}}{C_{gs} + C_L} \quad r_o^L = r_o \parallel \frac{1}{g_{mb}} \parallel r_o$$

$$g_m = \sqrt{2 \cdot 500 \mu \cdot 20 m} = 4.472 \text{ mS} ; C_{gs} = \frac{2}{3} W L \cdot 5 \text{ fF} / \mu m^2 = 333 \text{ fF}$$

$$g_{mb} = g_m \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}} = 4.472 \text{ mS} \frac{0.5}{2\sqrt{0.6 + 5}} = 0.472 \text{ mS} = \frac{1}{2.117k}$$

$$r_o = \frac{1}{\lambda I_D} = 204k$$

$$z = p \Rightarrow C_L = \frac{1}{g_m r_o^L} C_{gs} = \frac{1}{4.472 \text{ mS} \cdot (10k \parallel 2.117k \parallel 204k)} \cdot 333 \text{ fF}$$

$$\underline{\underline{C_L = 46.3 \text{ fF}}}$$