

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering**  
**and Computer Sciences**

**Midterm 2**

**EECS 140**

**B. E. Boser**

- closed book, one 5.5"x 8.5" summary ok -

**Fall 1999**

Device Parameters (except where otherwise noted):

Parameter	Unit	NMOS	PMOS
Threshold voltage, $V_{TH}$	V	1	-1
Gate capacitance, $C_{ox}$	$fF/\mu m^2$	5	5
Transconductance coefficient, $k_p = \mu C_{ox}$	$\mu A/V^2$	200	100
Channel length modulation, $\lambda(L)$ , L in $\mu m$	$V^{-1}$	$0.1/L$	$0.1/L$
Overlap Capacitances	$C_{OL} = W \cdot 0.5 fF/\mu m$		

*- Show your calculations on exam sheets (no credit for numerical result only) -*

Name: Solution (2 points)

Student-ID: \_\_\_\_\_ (3 points)

Result summary: \_\_\_\_\_ (5 points)

a)  $V_{omin} = \underline{894 mV}$  \_\_\_\_\_ (10 points)

$V_{omax} = \underline{4.106 V}$

b)  $W_{17} = \underline{25 \mu m}$  \_\_\_\_\_ (10 points)

$V_{omax}' = \underline{4.434 V}$

c)  $G_m = \underline{1 mS}$  \_\_\_\_\_ (10 points)

d)  $R_o = \underline{10 M\Omega}$  \_\_\_\_\_ (10 points)

e)  $A_{dm} = \underline{80.0 dB}$  \_\_\_\_\_ (10 points)

f)  $f_0 = \underline{31.83 MHz}$  \_\_\_\_\_ (10 points)

g)  $f_{p2} = \underline{478 MHz}$  \_\_\_\_\_ (10 points)

h)  $f_{pm} = \underline{119 MHz}$  \_\_\_\_\_ (10 points)


$f_{zm} = \underline{238 MHz}$

i)  $C_{i1} = \underline{3.3 pF}$  \_\_\_\_\_ (10 points)

Total: \_\_\_\_\_ (100 points)

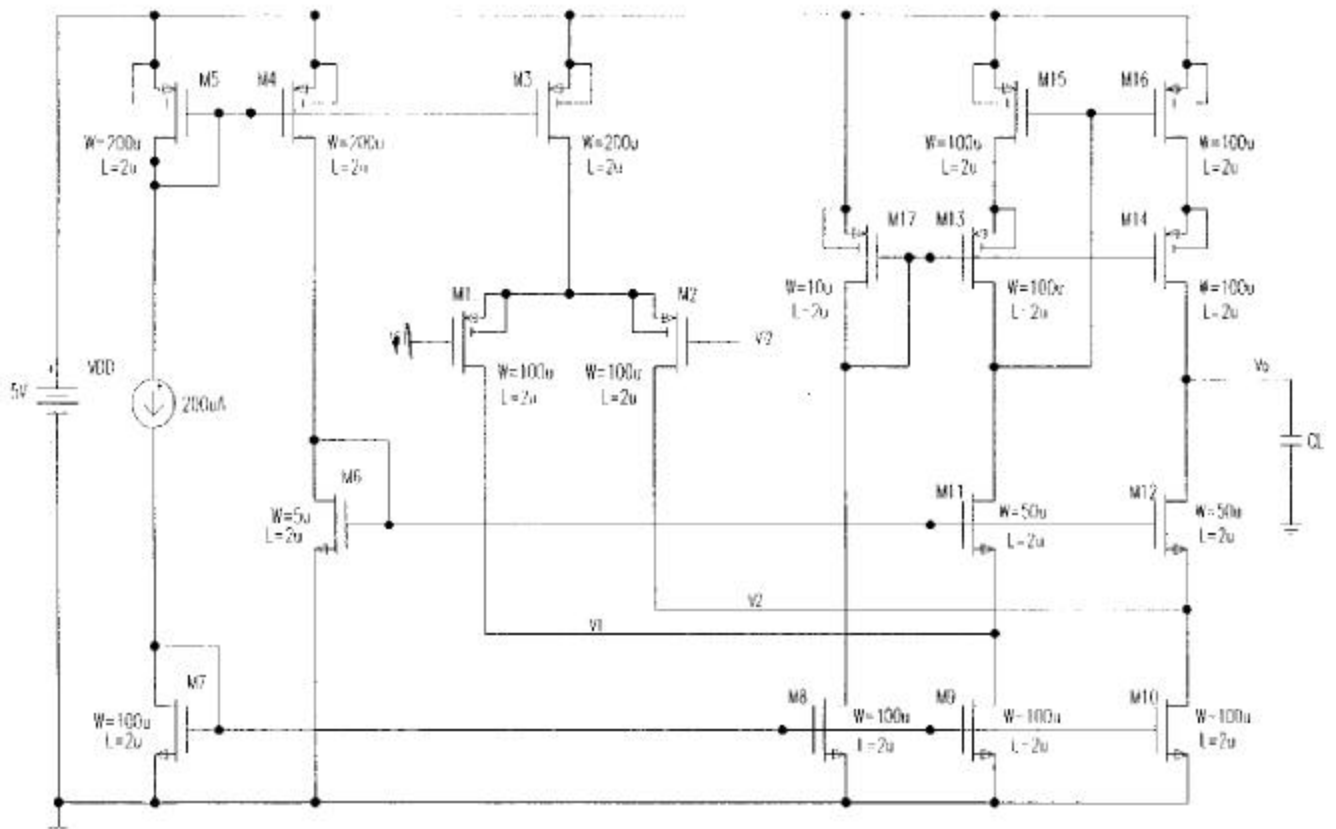**Problem:** Consider the Folded Cascode Amplifier shown below.

- Neglect channel length modulation in DC calculations. (large signal)
  - Neglect extrinsic parasitic capacitances in parts a) through h)
  - Neglect body effect
- a) Determine the minimum and maximum output voltages,  $V_{omin}$  and  $V_{omax}$ , that are required to operate the amplifier in its high gain regime.
  - b) Change  $W$  of M17 to *maximize* the output range while keeping all devices in the forward active region (assume maximum output current). Calculate the corresponding maximum output voltage  $V_{omax}$ . Verify that M13 and M15 are indeed in saturation
  - c) Calculate the amplifier's differential mode transconductance  $G_m$ .
  - d) Calculate the amplifier's output resistance  $R_o$ .
  - e) Calculate the low frequency differential gain  $A_{dm}$  in dB.
  - f) Calculate the unity gain frequency  $f_u$  of the circuit for  $C_L=5pF$ . Assume that all non-dominant poles are at higher frequencies than  $f_u$ .
  - g) Estimate the pole frequency  $f_{p2}$  caused by the cascode device M11 (node V1).
  - h) Estimate the pole frequency  $f_{pm}$  and the zero frequency  $f_{zm}$  caused by the current mirror M13-M16.
  - i) Estimate the *low frequency* input capacitance  $C_{i2}$  looking into node V<sub>i2</sub>. Include the gate to drain overlap capacitance of M2 in your analysis – neglect the parasitic junction capacitances. Hint: Include the Miller effect at node V2 and assume that  $C_L$  is an open circuit for the frequencies of interest. ( $C_{i1}$  at GND)



$$a) V_{dsat6} = \sqrt{\frac{2 \cdot 200 \mu}{200 \mu \cdot 2.5}} = 894 \text{ mV}$$

$$V_{dsat12} = \sqrt{\frac{2 \cdot 200 \mu}{200 \mu \cdot 2.5}} = 283 \text{ mV (max.)}$$

$$\Rightarrow V_{omin} = V_{dsat6} - \cancel{V_{dsat12}} + \cancel{V_{dsat12}} = \underline{\underline{894 \text{ mV}}}$$

$$V_{dsat17} = V_{dsat6} = 894 \text{ mV}$$

$$\Rightarrow V_{omax} = V_{DD} - V_{dsat17} = \underline{\underline{4.106 \text{ V}}}$$

$$b) \text{ for max output range: } \left(\frac{W}{L}\right)_{17} = \frac{1}{4} \left(\frac{W}{L}\right)_{13-16} = \frac{25 \mu\text{m}}{2 \mu\text{m}}$$

$$\Rightarrow W_{17} = \underline{\underline{25 \mu\text{m}}}$$

$$\Rightarrow V_{omax}' = V_{DD} - 2V_{dsat16} = V_{DD} - 2V_{dsat17}$$

$$V_{dsat17}' = \sqrt{\frac{2 \cdot 200 \mu}{100 \mu \cdot 2.5}} = 566 \text{ mV}$$

$$V_{dsat16} = V_{dsat12} = 282 \text{ mV}$$

$$V_{omax}' = 5 \text{ V} - 2 \cdot 283 \text{ mV} = 5 \text{ V} - 566 \text{ mV} = \underline{\underline{4.434 \text{ V}}}$$

$$c) G_m = g_{mi} = \sqrt{2I_D k_i' \frac{W}{L}} = \sqrt{200 \mu \cdot 100 \mu \cdot 50} = \underline{\underline{1 \text{ mS}}}$$

$$d) R_o = g_{m14} r_{o14} r_{o16} \parallel g_{m12} r_{o12} (r_{o10} \parallel r_{o2})$$

$$r_{o14} = r_{o16} = \frac{1}{\lambda I_D} = \frac{1}{0.05 \cdot 100 \mu\text{A}} = 200 \text{ k}\Omega = r_{o12} = r_{o2}$$

$$g_{m14} = g_{m1} = 1 \text{ mS} = g_{m12}$$

$$r_{o10} = \frac{1}{0.05 \cdot 200 \mu\text{A}} = 100 \text{ k}\Omega$$

$$\Rightarrow R_o = 1 \text{ mS} \cdot 200 \text{ k} \cdot 200 \text{ k} \parallel 1 \text{ mS} \cdot 200 \text{ k} (100 \text{ k} \parallel 200 \text{ k}) = \underline{\underline{10 \text{ M}\Omega}}$$

$$e) A_{dm} = G_m R_o = 1 \text{ mS} \cdot 10 \text{ M}\Omega = 10000 \hat{=} \underline{\underline{80 \text{ dB}}}$$

$$f) f_u = \frac{1}{2\pi} \frac{G_m}{C_L} = \frac{1}{2\pi} \frac{1 \text{ mS}}{5 \text{ pF}} = \underline{\underline{31.83 \text{ MHz}}}$$


$$g) f_{p2} \approx \frac{1}{2\pi} \frac{g_{m11}}{C_{gs11}} \quad \begin{aligned} g_{m11} &= g_{m1} = 1 \text{ mS} \\ C_{gs11} &= \frac{2}{3} \cdot 50 \cdot 2 \cdot 5 \text{ fF} = 333 \text{ fF} \end{aligned}$$

$$\Rightarrow \underline{\underline{f_{p2} = 478 \text{ MHz}}}$$

$$h) f_{pm} \approx \frac{g_{m15}}{C_{gs15} + C_{gs16}} \quad \begin{aligned} C_{gs15} &= C_{gs16} = 666 \text{ fF} \\ g_{m15} &= g_{m1} = 1 \text{ mS} \end{aligned}$$


$$\underline{\underline{f_{pm} = 119 \text{ MHz}}}$$
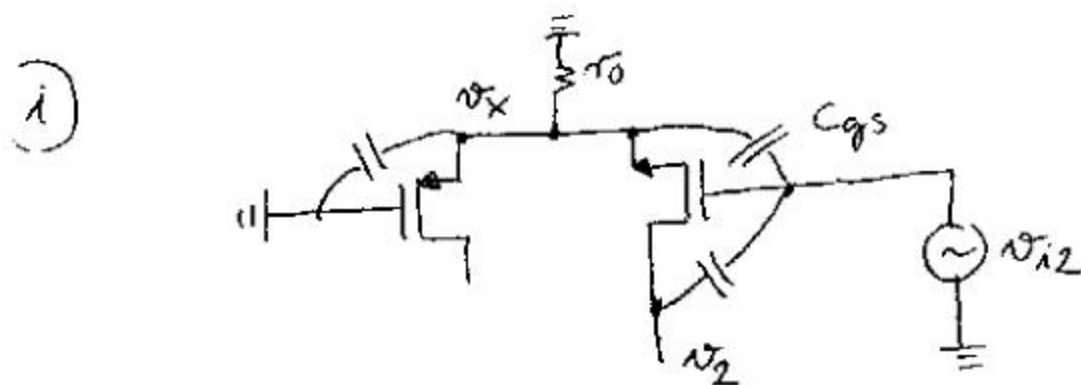
$$f_{zm} = 2 f_{pm} = \underline{\underline{238 \text{ MHz}}}$$



→ there is a common mode and diff mode input component!

$$v_x \neq \text{AC ground}$$

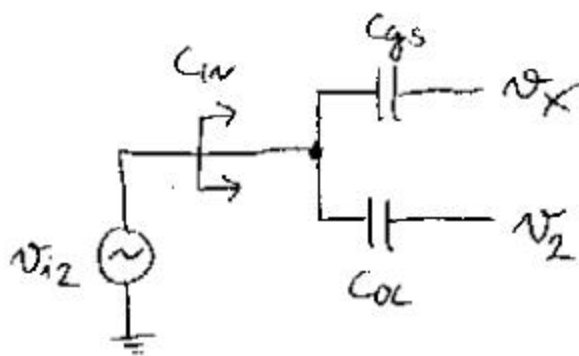


$$C_{1W} = C_{gs} \left(1 - \frac{v_x}{v_{i2}}\right) + C_{ol} \left(1 - \frac{v_2}{v_{i1}}\right)$$

→ find  $\frac{v_x}{v_{i2}}$ :



$$v_{icm} = \frac{1}{2} (v_{i1} + v_{i2}) = \frac{1}{2} v_{i2}$$

CM half circuit:
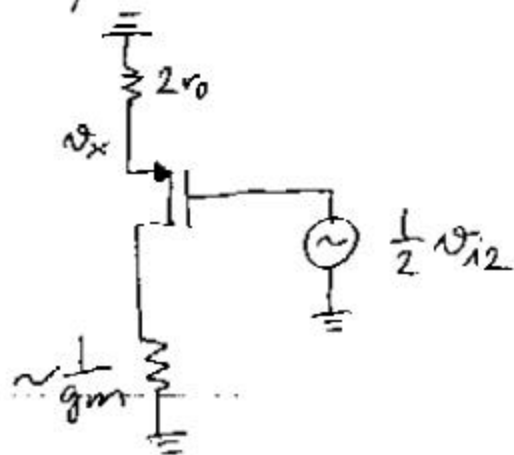
$$\Rightarrow \frac{v_x}{v_{i2}} \approx \frac{1}{2}$$



→ find  $\frac{v_2}{v_{i2}}$ :

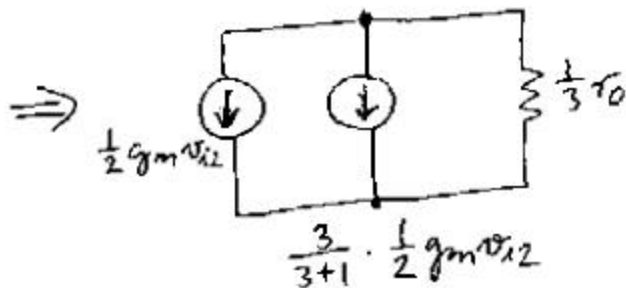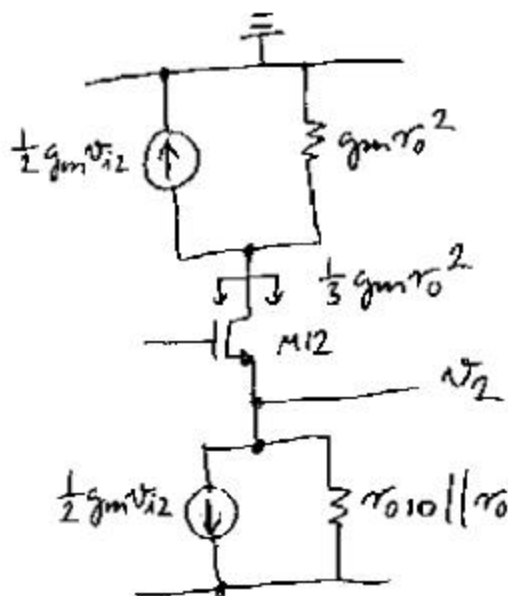

$$\Rightarrow \frac{v_2}{v_{i2}} = -\left(\frac{1}{2} + \frac{3}{8}\right) g_m \cdot \frac{1}{3} r_o = -\frac{7}{24} g_m r_o$$

$$= -\frac{7}{24} \cdot 1 \text{mS} \cdot 200\text{k} = \underline{\underline{-58.3}}$$

$$\Rightarrow C_{in} = C_{gs} \left(1 - \frac{v_x}{v_{i2}}\right) + C_{ol} \left(1 - \frac{v_2}{v_{i1}}\right)$$

$$C_{in} = 666\text{fF} \left(1 - \frac{1}{2}\right) + 50\text{fF} \left(1 - (-58.3)\right)$$

$$\underline{\underline{C_{in} = 3.3\text{pF}}}$$