

UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering
and Computer Sciences

Homework #3

EECS 140

B. E. Boser

Due 09/15/99 before noon in 497 Cory


Fall 1999

Note: Use the device parameters given in the class handout “Device Parameters & SPICE Models” and also available on the EECS 140 website, <http://kowloon.eecs.berkeley.edu/~courses/140>.


Grading: Problem 1: 10% Problem 2: 40% Problem 3: 50%

- 1) Consider the PMOS transistor shown in Fig.1.
- Assuming the device is on, what are the signs of the quantities V_{GS} , V_{DS} and I_D ?
 - Write out the equations for I_D as a function of V_{GS} and V_{DS} , for both the triode and forward active region of the device.
 - The table below shows three different biasing conditions for a PMOS transistor. For each situation, determine the transistor’s region of operation and its drain current. Assume that the device is on, $(W/L) = 10$ and $\lambda=0.1$.

$ V_{GS} $	$ V_{DS} $	Region of Operation	I_D
3V	3V		
5V	0V		
1.5V	2.5V		

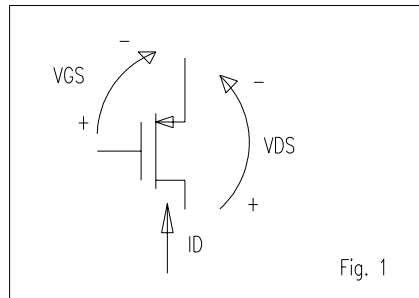

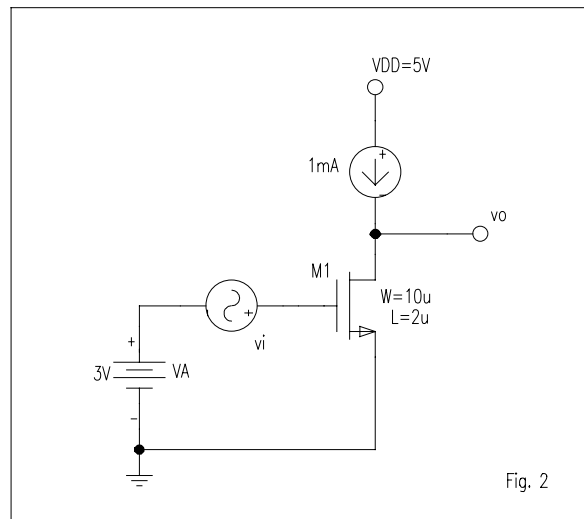- 2) Figure 2 shows a common source amplifier with resistive load. The transistor M1 is biased to operate in the *triode* region.
- Derive a small signal transistor model for a device operating the triode region, i.e. find expressions for its small signal output resistance and transconductance. Call these parameters r_o' and g_m' .
 - Verify that M1 operates in the triode region. Calculate r_o' and g_m' for M1 and draw the small signal equivalent circuit for the amplifier circuit. Calculate the low frequency voltage gain $a_{v0}' = v_o/v_i$.
 - Now assume that V_A is lowered until the device operates in the forward active region. Calculate r_o , g_m and a_{v0} using the expressions established in class. Assume $V_{DS}=3V$.
 - Compare the results obtained in (b) and (c). Why are amplifier devices usually operated in the forward active region ?
 - Derive analytical expressions for $a_{v0} = f(V_{GS}, V_{DS})$ for both regions of operation and compare.



- 3) Consider the common source amplifier with capacitive load in Figure 3.
- a) Use the parameters given in the schematic to analyze the circuit as follows.
 - i) Calculate V_A such that the bias point at the output node $V_O = 3V$. Calculate the small signal parameters g_m and r_o for M1. Calculate the low frequency gain a_{v0} , the pole frequency f_0 and the unity gain frequency f_U .
 - ii) Find the *precise* value for V_A by performing a DC analysis using SPICE. Compare with your result from (i). Use at least 5 significant digits and explain why this is necessary.
 - iii) Setting V_A to the value obtained in (ii), run a .OP analysis. Extract V_{DS} , V_{GS} , g_m and r_o from the SPICE listing file. Verify that the device operates in the forward active region and compare the simulation results for the small signal parameters with (i).
 - iv) Perform a .AC analysis and printout a Bode plot for the magnitude of the transfer function v_o/v_i . Mark the results from part (i) in your plot with three circles. Comment on discrepancies
 - b) Double the device width W and the channel length L . Repeat (i) through (iv).
 - c) Double the current I and double the device width W . Repeat (i) through (iv).
 - d) Compare the values for gain and bandwidth obtained in (a) through (c). Create a printout that contains all three Bode plots in one diagram. Explain.

