

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering**  
**and Computer Sciences**

**Homework #6**

**EECS 140**

**B. E. Boser**

Due 10/08/99 before noon in 497 Cory

**Fall 1999**

**Note:** Use the device parameters given in the class handout “Device Parameters & SPICE Models” and also available on the EECS 140 website, <http://kowloon.eecs.berkeley.edu/~courses/140>. Use the following parameters to calculate parasitic capacitors:  $C_{ox}=5\text{fF}/\mu\text{m}$ ,  $C_{OL}=W\cdot 0.5\text{fF}/\mu\text{m}$ ,  $C_{sb0}=C_{db0}=1\text{fF}/\mu\text{m}^2$ ,  $\psi_0=0.5\text{V}$ ,  $AS=AD=W\cdot 1\mu\text{m}$ .


**Grading:** Problem 1: 40% Problem 2: 40% Problem 3: 20%

1) Cascode amplifier stages are often used to eliminate bandwidth reduction due to Miller multiplication of the parasitic gate to drain capacitance. The following problem examines a case in which a poorly designed cascode amplifier circuit still suffers from bandwidth degradation due to the Miller effect. Consider the circuit shown in Fig.1. For the analysis, neglect all parasitic junction capacitances.



- a) Derive analytical expressions for the small signal resistance  $R_x$  at node  $v_x$  and the DC voltage gain  $A_{v_x} = v_x/v_i$ . Assume  $R_D \gg r_{o2}$ .
- b) Find an expression for the pole frequency  $f_{p1}$  that is present at node  $v_g$  using the Miller approximation.
- c) Using the results from (b), find  $A_{v_x}$ , and  $f_{p1}$  for  $I_{bias}=1\text{mA}$ ,  $R_D=1\text{M}\Omega$ ,  $R_S=500\text{k}\Omega$ ,  $W_2=5\mu\text{m}$ ,  $W_1=100\mu\text{m}$  and  $L_1=L_2=1\mu\text{m}$ . Compare  $f_{p1}$  with the pole frequency  $f_{p1}'=1/R_S C_{gs1}$ , i.e. find  $f_{p1}/f_{p1}'$ . Note that  $f_{p1}'$  approximately represents the expected pole frequency at node  $v_g$  neglecting the Miller effect.
- d) Verify your results from part (c) using SPICE. Use  $V_{B2}=3\text{V}$  and run a DC analysis to find  $V_{B1}$  such that  $V_O=5\text{V}$  at the operating point. Use 5 significant digits when extracting  $V_{B1}$ .

Next, perform an AC analysis and printout a Bode plot for the voltage gains  $a_{v_x}=v_x/v_i$  and  $a_v=v_o/v_i$ . In the same diagram, plot  $a_{v_x}$  and  $a_v$  after setting  $C_{OL1}=0$ , thus neglecting the Miller effect. Compare the observed pole frequencies  $f_{p1}$  and  $f_{p1}'$  and their ratio with your hand calculations. Mark the calculated pole frequencies in your plot.

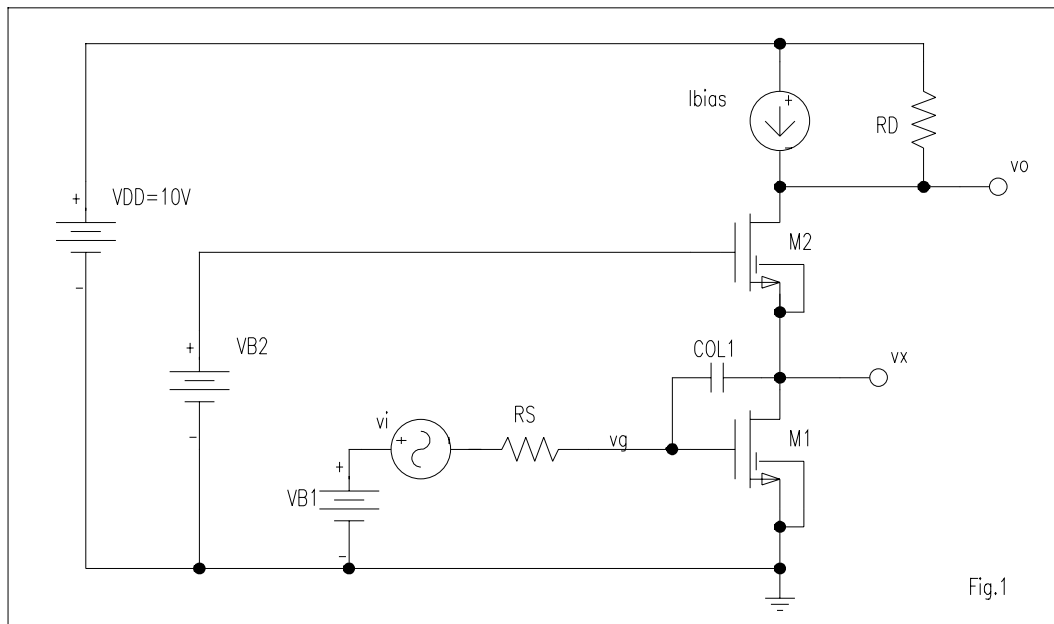- e) The result from the above analysis suggests that the Miller effect *can* cause bandwidth degradation in a cascode amplifier stage. Referring to the topology of the circuit in Fig.1 and for  $R_S=\text{constant}$ , what must be done to avoid the Miller effect? What are the tradeoffs?



  - 2) Fig. 2a and Fig. 2b show common source amplifiers before and after the insertion of a cascode device. For the analysis of these circuits, neglect all extrinsic parasitic capacitances.
- Find an analytical expression for the the DC voltage gains  $a_{voa}$  and  $a_{vob}$  and their ratio  $a_{vob}/a_{voa}$ , where the indices a and b correspond to the circuits in Fig. 2a and Fig. 2b, respectively.
  - Find an expression for the pole frequencies  $f_{p1a}$  and  $f_{p1b}$  and their ratio  $f_{p1a}/f_{p1b}$  caused by a fixed load capacitor  $C_L$ .
  - The insertion of M2 causes another pole to appear in the transfer function  $v_o/v_i$  of the circuit in Fig. 2b. Briefly explain the origin of this pole using appropriate circuit diagrams. Find an expression for its pole frequency  $f_{p2b}$ .
  - Find an expression for the unity gain frequencies  $f_{ua}$  and  $f_{ub}$  and their ratio  $f_{ua}/f_{ub}$ . Assume that  $f_{p2b} \gg f_{ub}$ .
  - Calculate numerical values for all expressions found in (a) through (d) using  $I_{bias}=500\mu A$ ,  $(W/L)_1=(W/L)_2=20\mu m/1\mu m$  and  $C_L=0.5pF$ .
  - Verify your results from part (d) using SPICE. Use  $V_{DD}=10V$  and  $V_{B2}=3V$ . For both circuits, run a DC analysis to find  $V_{B1}$  such that  $V_O=5V$  at the operating point. Use 5 significant digits when extracting  $V_{B1}$ . Perform AC analyses to printout the frequency response of  $v_o/v_i$  for both circuits in the same diagram. Mark the calculated DC voltage gains, pole frequencies and unity gain frequencies in your plot. Comment on discrepancies.



3) Fig. 3 shows a cascode current source consisting of M1A and M1B, and a single transistor current source consisting of M2. Assume that the cascode current source is optimally biased, i.e.  $V_{B1B}$  is chosen such that  $V_{DS1a} = V_{d1A}(\text{sat})$ . Assume also that both current sources supply the same current  $I_D$ .

a) Find relationships between  $W_1, L_1$  and  $W_2, L_2$  such that both current sources have the same parasitic output capacitance, and the same minimum output voltage  $V_{\min}$ . Assume  $\lambda=0$  in this part of the analysis.

b) Using the result from (a), show that: 
$$\frac{R_{O1}}{R_{O2}} \cong \frac{g_{m1} \cdot r_{o1}}{4}$$

where  $R_{O1}$  and  $R_{O2}$  are the output resistances of each current source, as indicated in Fig. 3.

c) Calculate  $V_{\min}, R_{O1}$  and  $R_{O2}$  for  $I_D = 100 \mu\text{A}$  and  $(W/L)_1 = 10 \mu\text{m}/2 \mu\text{m}$ .

