

UNIVERSITY OF CALIFORNIA AT BERKELEY
College of Engineering
Department of Electrical Engineering and Computer Science

R.W. Brodersen
Mike Chen

Homework #4
(Due 2/19/04)

EECS 140
Spring 2004

- 1) Given the differential amplifier in figure 1, $(W/L)_{3,4}=5\mu/1\mu$, $(W/L)_{1,2}=10\mu/1\mu$, $(W/L)_5=20\mu/1\mu$, $R1=1\text{ M}\Omega$, input common mode voltage, $V_{ic} = 0.9\text{ V}$, $V_{dd}=1.8\text{ V}$. Answer the following questions, assuming $V_{bs}=0$ for all transistors:
- Calculate the voltage, V_b , such that the tail current is $10\text{ }\mu\text{A}$. And compute all the DC biasing voltage of all the nodes.
 - Plot V_{oc} vs. V_{ic} , as V_{ic} sweeps from 0 to V_{dd} , and $V_{id}=0\text{ V}$. Label all the breakpoints, and indicate operation regions of all the transistors. [Def: $V_{oc}=(V_{o1}+V_{o2})/2$, $V_{ic}=(V_{i1}+V_{i2})/2$]
 - Plot V_{od} vs. V_{id} , as V_{id} sweeps from $-V_{dd}$ to V_{dd} , and $V_{ic}=0.9\text{ V}$. Label all the breakpoints. [Def: $V_{od}=(V_{o1}-V_{o2})$, $V_{id}=(V_{i1}-V_{i2})$]
 - Calculate output common mode resistance, R_{oc} , and common mode gain, A_{cm} .
 - Calculate output differential mode resistance, R_{od} , and differential mode gain, A_{dm} .
 - Use HSPICE to verify (a)-(e), and print out the results.

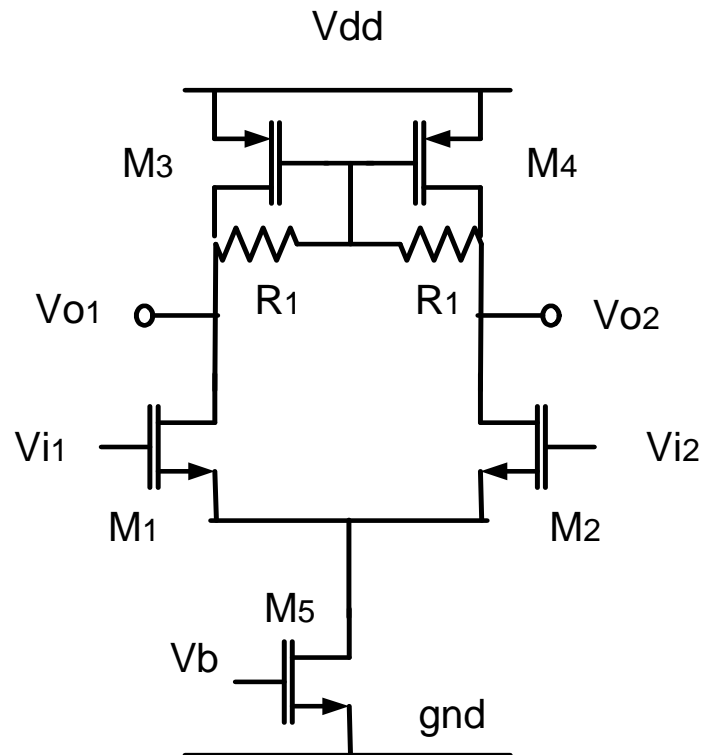


Figure 1

Device model for problem (1):

```
.model nch nmos LEVEL=1 TOX=25 VTO=0.4 KP=100.0e-6 LAMBDA=0.2  
+GAMMA=0.01 PHI=0.6
```

```
.model pch pmos LEVEL=1 TOX=25 VTO=-0.4 KP=60.0e-6 LAMBDA=0.15  
+GAMMA=0.01 PHI=0.6
```

[SPICE hint: 'e' element (voltage control voltage source) can be used to sweep a differential voltage. 'e1 out1 out2 in1 in2 gain']

- 2) A current source is shown in figure 2, with $(W/L)_{1,2}=10\mu/1\mu$, $V_{bs}=0$, $V_{dd}=1.8V$.
 - a) Choose R_1 and R_2 , such that $I_{out} = 100 \mu A$, and $I_{in} = 400 \mu A$.
 - b) Calculate the output resistance of this current source, R_{out} .
 - c) Plot I_{out} vs. V_{out} , which is the voltage at the output node. Label the breakpoints and indicate operation region of M_2 .
 - d) Use HSPICE to verify (a)-(c), and print out the results.

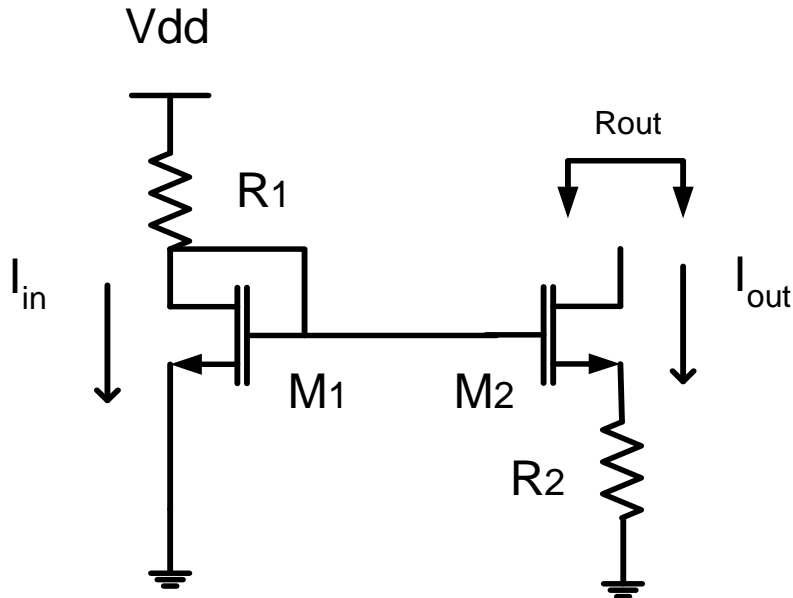


Figure 2

Device model for problem (2):

```
.model nch nmos LEVEL=1 TOX=25 VTO=0.4 KP=100.0e-6 LAMBDA=0.1  
+GAMMA=0.01 PHI=0.6
```

[SPICE hint: Put a voltage source V_{out} at output node to sweep output voltage, and '.tf i(M2) Vout' gives the output resistance.]