

University of California  
Berkeley  
College of Engineering  
Department of Electrical Engineering  
and Computer Science



Robert W. Brodersen  
EECS140

Analog Circuit Design


**Lectures  
on  
CURRENT SOURCES**

**Current Sources**

CS-1

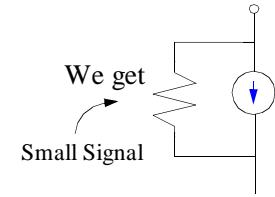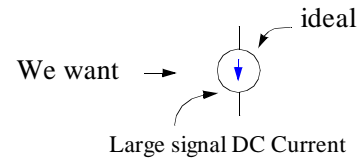

**Simple Source**

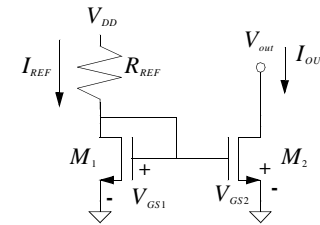


$$V_{OUT} > V_{GS} - V_T = V_{DSAT}$$


$$V_{DSAT} = \left( \frac{2 \cdot I_{DS}}{k' \cdot \frac{W}{L}} \right)^{\frac{1}{2}} \approx 0.1$$

**Ideal Current Source**



CS-1a

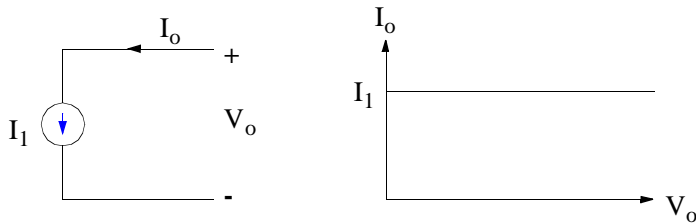

**Real Current Source**

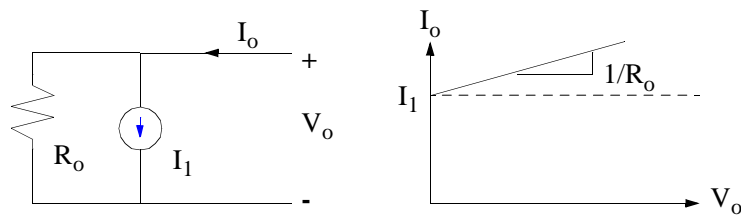

CS-2

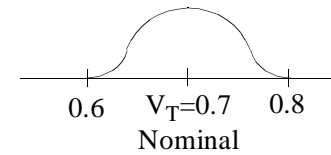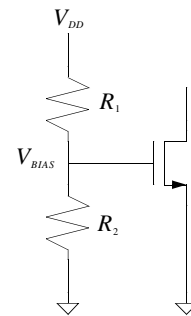


$$I_{DS1} = \frac{W}{L} \cdot \frac{k'}{2} \cdot (V_{BIAS} - V_T)^2$$

**Simple Source (Cont.)**

CS-3

**Diode Connected Transistor :**

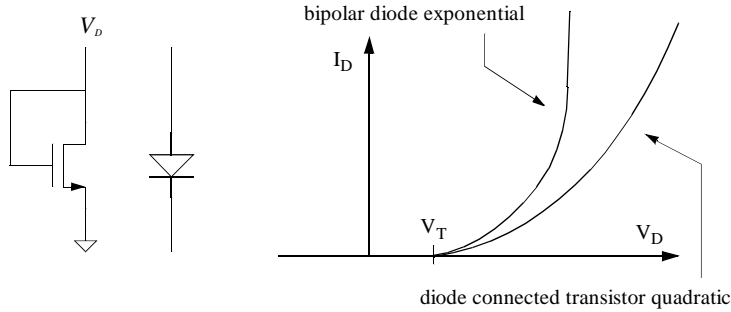

$V_{DS} > V_{GS} - V_T$  } After we reach the point  $V_D > V_T$ , the transistor will always be in Sat.

**Simple Source (Cont.)**

CS-5

**Current Calculation :**


Analysis :

$$I_{DS1} = I_{REF} = \frac{V_{DD} - V_{GS1}}{R_{REF}}$$

$$V_{GS1} = V_T + \left( \frac{2 \cdot I_{DS1}}{k' \cdot \frac{W}{L}} \right)^{\frac{1}{2}} = V_T + \Delta V$$

$$I_{REF} = V_{DD} - V_T - \left( \frac{2 \cdot I_{REF}}{k' \cdot \frac{W}{L}} \right)^{\frac{1}{2}}$$

Iterative Solution !

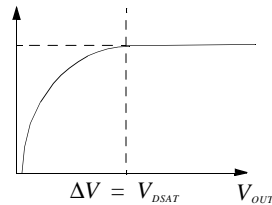

**Simple Source (Cont.)**

CS-4

$$I_{DS1} = \left( \frac{W}{L} \right)_1 \cdot \frac{k'}{2} \cdot (V_{GS1} - V_T)^2$$

$$I_{DS2} = \left( \frac{W}{L} \right)_2 \cdot \frac{k'}{2} \cdot (V_{GS2} - V_T)^2$$

if  $\left( \frac{W}{L} \right)_1 = \left( \frac{W}{L} \right)_2$ , then  $I_{DS1} = I_{DS2}$

otherwise  $I_{OUT} = I_{REF} \cdot \left[ \frac{\left( \frac{W}{L} \right)_2}{\left( \frac{W}{L} \right)_1} \right]$

$$I_{REF} = I_{DS1} , I_{OUT} = I_{DS2}$$

**Simple Source (Cont.)**

CS-6

Design :

$$R_{REF} = \frac{V_{DD} - V_{GS1}}{I_{REF}} = \frac{V_{DD} - V_T - \left( \frac{2 \cdot I_{REF}}{k' \cdot \frac{W}{L}} \right)^{\frac{1}{2}}}{I_{REF}}$$

$$I_{REF} = 10\mu A , V_{DD} = 5 , V_T = 0.7$$


$$k' = 90 \times 10^{-6}$$

$$R_{REF} = 415k\Omega \quad (\text{Pretty Big!})$$

**Simple Source (Cont.)**

CS-7

**Small Signal :**

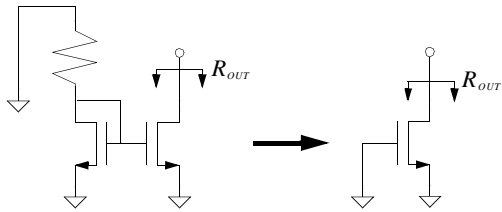


$$R_{OUT} = r_o = \frac{1}{\lambda \cdot I_{OUT}}$$

$$I_{OUT} = 10\mu A$$

$$\lambda = 0.01$$

$$R_{OUT} = 10M\Omega$$

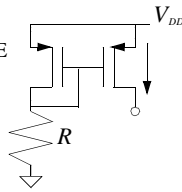
NMOS → current SINK  
PMOS → current SOURCE



**Simple Source (Cont.)**

CS-8

**Bipolar :**

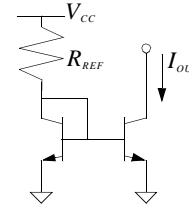

$$I_{OUT} \approx \frac{V_{CC} - V_{BE(ON)}}{R_{REF}}$$


$$V_{BE(ON)} \approx 0.6$$

$$R_{OUT} = \frac{V_A}{I_{OUT}}$$

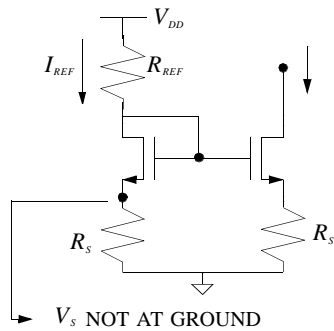**Simple Source (Cont.)**

CS-9

How to make  $R_{OUT}$  better (ie. larger) ?  
Degeneration?



$$V_{OUT} > V_{DSAT} + I_{OUT} \cdot R_S$$


$$R_{OUT} = r_o \cdot [1 + (1 + x) \cdot g_m \cdot R_S]$$

$$V_T = V_{T0} + \gamma \cdot [(V_{SB} + 2 \cdot \phi_f)^{\frac{1}{2}} - (2 \cdot \phi_f)^{\frac{1}{2}}]$$

Not a very efficient way to get high  $R_{OUT}$  too much area for resistor.  
Better method is to use transistors instead of resistors.

**Cascode Source**

CS-10

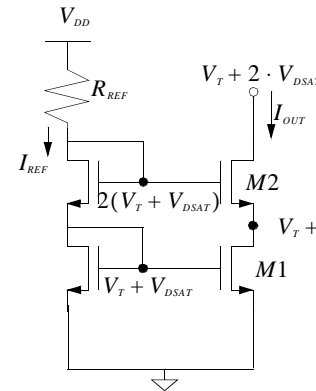

Let  $\gamma = 0$  or tie all wells to sources  
 $V_T + V_{DSAT}$  for EOS


**Cascode Source (Cont.)**

CS-11

$$V_{GS} = V_T + V_{DSAT}$$

$$\Delta V = \left( \frac{2 \cdot I_{DS}}{k' \cdot \frac{W}{L}} \right)^{\frac{1}{2}}$$

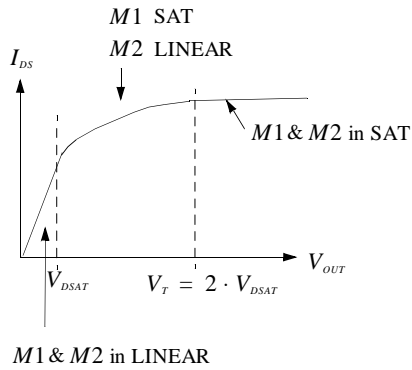
$$I_{REF} = \frac{V_{DD} - 2 \cdot (V_T - V_{DSAT})}{R_{REF}}$$



**Cascode Source (Cont.)**

CS-12

**Rout for Cascode Source :**

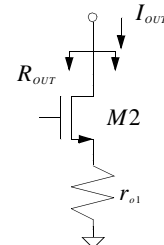

$$\lambda = 0.01$$

$$\gamma = 0$$

$$I_{DS} = 10\mu A$$

$$\frac{W}{L} = 5$$

$$R_{OUT} = r_{o2} \cdot [1 + (1 + \chi_2) \cdot g_{m2} \cdot r_{o1}]$$

$$\approx (1 + \chi_2) \cdot g_{m2} \cdot r_{o1} \cdot r_{o2}$$

$$r_o = \frac{1}{\lambda \cdot I_{DS}} \quad g_{m2} = \left( 2 \cdot k' \cdot \frac{W}{L} \cdot I_{DS} \right)^{\frac{1}{2}} \approx 10^{-4}$$

$$R_{OUT} \approx 10^{-4} \cdot \left( \frac{1}{0.1 \cdot 10^{-5}} \right)^2 \approx 10^{10} \Omega$$


$$g_{m2} = \frac{2 \cdot I_{OUT}}{V_{DSAT}} \quad V_{DSAT} \approx 0.2V$$

$$R_{OUT} = \frac{(1 + \chi_2)}{\lambda^2} \cdot \frac{2}{(V_{DSAT}) \cdot (I_{OUT})}$$

**Cascode Source (Cont.)**

CS-13

**Triple Cascode :**

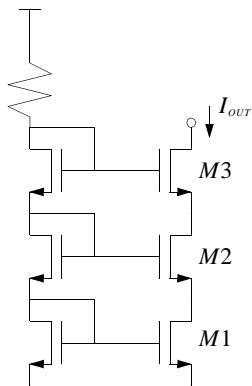



$$R_{OUT} = (1 + \chi_2) \cdot (1 + \chi_3) \cdot g_{m2} \cdot g_{m3} \cdot r_{o1} \cdot r_{o2} \cdot r_{o3}$$

**HUGE!!**

**Cascode Source (Cont.)**

CS-14

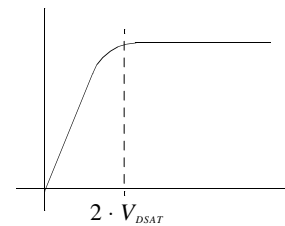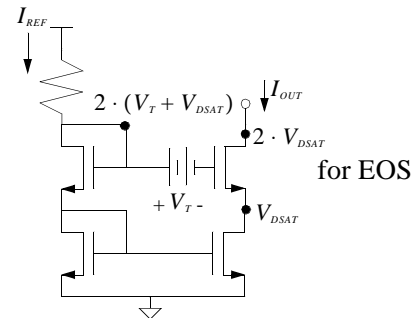
Problem with Cascode is the  $V_T + 2 \cdot V_{DSAT}$  drop required for saturation.  
**High Swing Cascode** is the solution



**Cascode Source (Cont.)**

CS-15


**How to implement Battery?**

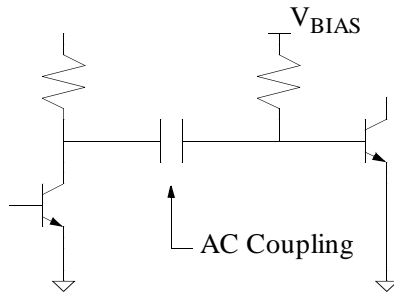

**Cascode Source (Cont.)**

CS-17

**Power Reduction :**

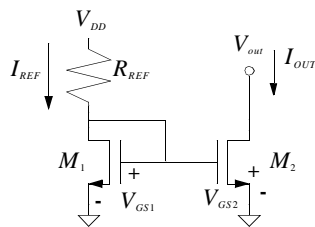


If we want  $I_{out} = 1\text{mA}$ ,  
 then we can either:  
 a) Set  $(W/L)_1 = (W/L)_2$   
 and  $I_{REF} = I_{out}$   
 b) Ratio  $(W/L)_1$  and  $(W/L)_2$   
 so that  $I_{REF} < I_{out}$ , e.g. set  
 $(W/L)_2 = 100(W/L)_1$  so that  
 $I_{REF} = 10\mu\text{A}$

The tradeoff is between power and area.

**Cascode Source (Cont.)**

CS-16

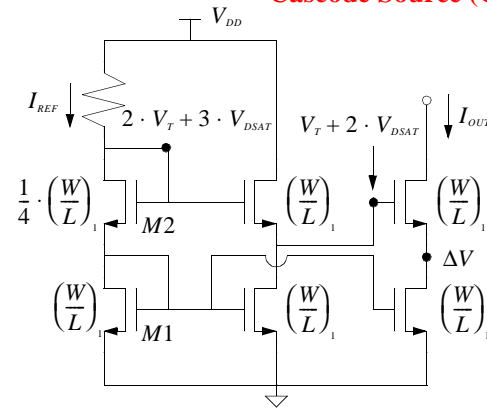

$$V_{DSAT1} = \left( \frac{2 \cdot I_{REF}}{k' \cdot \left(\frac{W}{L}\right)_1} \right)^{1/2}$$


$$V_{DSAT2} = \left( \frac{2 \cdot I_{REF}}{k' \cdot \frac{\left(\frac{W}{L}\right)_1}{4}} \right)^{1/2}$$

$$= 2 \cdot V_{DSAT1}$$

$$\approx 2 \cdot V_{DSAT}$$

**Wilson Source**

CS-18

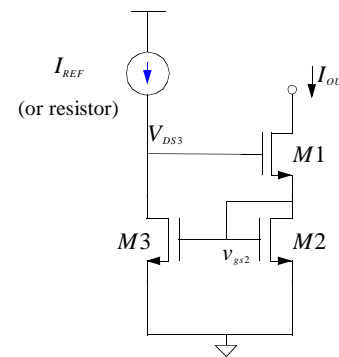

Assume  $\gamma = 0$

$$I_{OUT} = I_{REF}$$


$$V_{DS3} = 2 \cdot (V_T + V_{DSAT})$$

Equivalent to Cascode

**Wilson Source (Cont)**

CS-19

**Small Signal Analysis :**

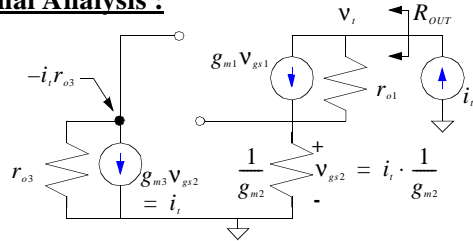

$$g_{m1} = g_{m2} = g_{m3} = g_m$$

$$v_i = i_i \cdot r_o - g_m \cdot v_{gs1} \cdot r_{o1} + i_i \cdot \frac{1}{g_{m3}}$$

$$v_{gs1} = -i_i \cdot r_{o3} - i_i \cdot \frac{1}{g_{m2}}$$


$$v_i = i_i \cdot (r_{o1} + g_m \cdot r_{o1} \cdot r_{o3}) \quad ; \quad R_{OUT} = r_{o1} \cdot (1 + g_m \cdot r_{o3})$$

**Wilson Current Source (Cont)**

CS-22

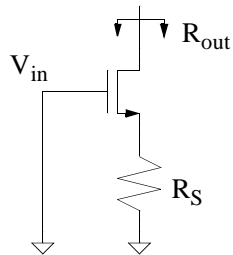**Rout :**

For this we must apply the small signal analysis, it is not correct to calculate  $R_{out}$  as for a common source with degeneration :




NO!

$$R_{OUT} = r_o \cdot (1 + g_m \cdot R_s)$$

**Wilson Current Source**

CS-21

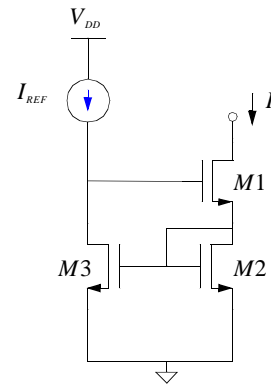

$$I_{DS1} = \frac{1}{2} \cdot \mu \cdot C_{OX} \cdot \frac{W}{L} \cdot (V_{GS} - V_T)^2 \cdot (1 + \lambda \cdot V_{DS})$$

with  $\lambda = 0$


$$I_O = I_{REF}$$

assuming same W/L and


$$V_{GS3} = V_{GS2}$$

**Wilson Current Source (Cont)**

CS-23

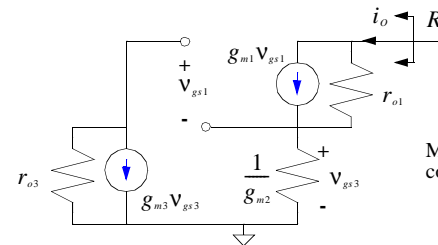

assume  $g_{m1} = g_{m2} = g_{m3} = g_m$

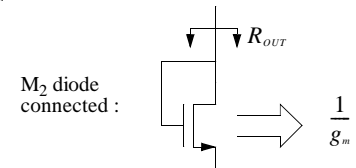

$$i_o = g_m \cdot v_{gs1} + \frac{v_o - v_{gs3}}{r_{o1}}$$


$$g_m \cdot v_{gs1} + \frac{v_o - v_{gs3}}{r_{o1}} = v_{gs3} \cdot g_{m2}$$

$$\frac{v_{gs1} + v_{gs3}}{r_{o3}} + g_m \cdot v_{gs3} = 0$$

$$\Rightarrow \frac{v_o}{i_o} = r_{o1} \cdot (2 + g_m \cdot r_{o3})$$

**Wilson Current Source (Cont)**

CS-24

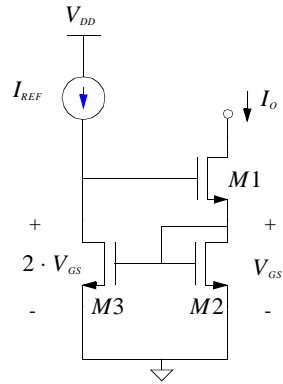

$$I_{DS1} = \frac{1}{2} \cdot \mu \cdot C_{ox} \cdot \frac{W}{L} \cdot (V_{GS} - V_T)^2 \cdot (1 + \lambda \cdot V_{DS})$$

with  $\lambda \neq 0$

$$V_{DS2} = V_{GS2} = V_{GS}$$

$$V_{DS3} = 2 \cdot V_{GS}$$


$$\frac{I_{DS2}}{I_{DS3}} = \frac{1 + \lambda \cdot V_{DS2}}{1 + \lambda \cdot V_{DS3}} = \frac{1 + \lambda \cdot V_{GS}}{1 + 2 \cdot \lambda \cdot V_{GS}}$$

$$I_O \neq I_{REF}$$

**Wilson Current Source (Cont)**

CS-25

To solve the matching problem,

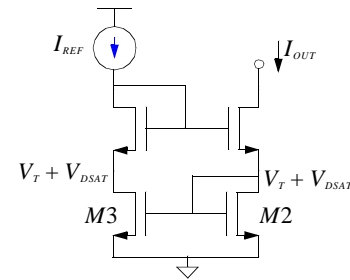


$$I_O = I_{REF}$$

$R_O =$  same as before

**Widlar Current Source**

CS-26

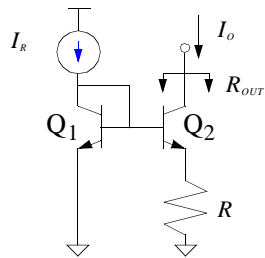

$$I_O =$$

$$V_{BE1} = V_{BE2} + I_O \cdot R$$

for BJT

$$V_{BE} = V_T \cdot \ln \frac{I_C}{I_S} \text{ so,}$$

$$V_T \cdot \ln \frac{I_R}{I_{S1}} = V_T \cdot \ln \frac{I_O}{I_{S2}} + I_O \cdot R$$

$$I_O \cdot R = V_T \cdot \ln \left( \frac{I_R \cdot I_{S2}}{I_O \cdot I_{S1}} \right)$$

$$I_O = \frac{V_T}{R} \cdot \ln \frac{I_R}{I_O} \text{ solve iteratively}$$


$$R_{OUT} =$$

for emitter degenerated BJT

$$R_{OUT} = r_o \cdot [1 + g_m \cdot (R \parallel r_\pi)]$$

**Low Current Bias Circuit (bipolar)**

CS-27

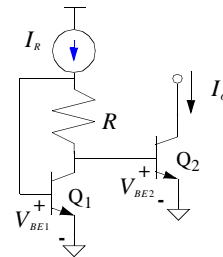

Very low  $I_O \sim$  nanoamps

$$V_{BE1} = V_{BE2} + I_R \cdot R$$

$$V_T \cdot \ln \frac{I_R}{I_{S1}} = V_T \cdot \ln \frac{I_O}{I_{S2}} + I_R \cdot R$$

let  $I_{S1} = I_{S2}$

$$I_O = I_R \cdot \exp \left( -\frac{I_R \cdot R}{V_T} \right)$$

for  $I_R = 10 \mu A$   $R = 12 k\Omega$


$$I_O = 100 nA$$

allows low  $I_O$  with reasonable values of R

$$R_{OUT} = r_{o2}$$

### Supply Independent Biasing

CS-28

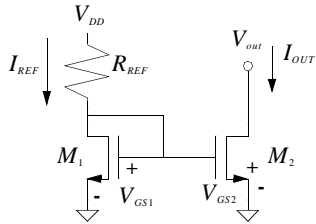

$$I_{OUT} = I_{REF}$$


$$I_{REF} = \frac{V_{DD} - V_{GS}}{R}$$

Hence,  $I_{REF}$  depends on the supply voltage  $V_{DD}$ . If the supply is a battery or similar device, then this will change over time, causing the reference current to also vary with time

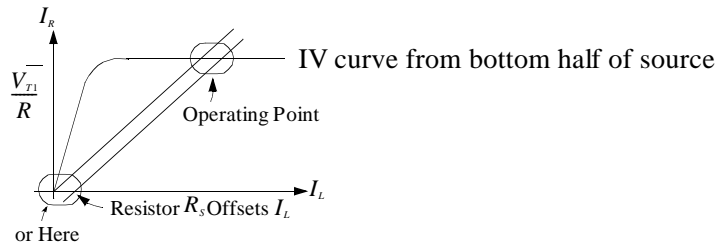
### Supply Independent Biasing (Cont.)

CS-30

For most self-biased circuits, there is a startup problem:



Soln : add  $R_s$  to top mirror

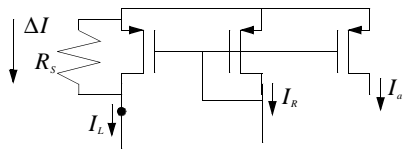


$$I_L = I_R + \Delta I$$

### Supply Independent Biasing (Cont.)

CS-29
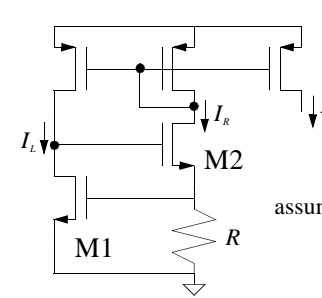
#### Vt - Referenced Self-Biased Circuit :



$$V_{GS1} = I_R \cdot R = V_{DSAT}$$

$$= \sqrt{\frac{2 \cdot I_L}{\mu \cdot C_{ox} \cdot \left(\frac{W}{L}\right)_1}} + V_{T1}$$

assume  $\left(\frac{W}{L}\right)_1 \gg 1$ ,  $V_{dsat}$  is then negligible

$$I_L = I_R$$


$$I_R \approx \frac{V_{T1}}{R}$$

$$I_o = I_R = \frac{V_{T1}}{R}$$

### Supply Independent Biasing (Cont.)

CS-31

#### Vbe referenced

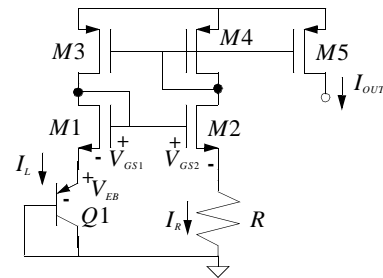

$$I_{OUT} = I_L$$

$$V_{EB1} + V_{GS1} = V_{GS2} + I_R \cdot R$$

M1 & M2 matched

$$V_{GS1} = V_{GS2}$$

$$V_{EB1} = I_R \cdot R$$

$$I_R = I_{OUT}$$

$$I_{OUT} = \frac{V_{EB}}{R} = \frac{\left(V_{thermal} \ln \frac{I_{out}}{I_S}\right)}{R} \approx \frac{\dot{I}}{R}$$

**Supply Independent Biasing (Cont.)** CS-32

With Temperature Fluctuation

$$TC = \text{parts per million/degree C} = \text{ppm}/^\circ\text{C} = \frac{\left(\frac{\Delta I}{I}\right)}{\Delta T} = \left(\frac{1}{I_{OUT}} \cdot \frac{\partial I_{OUT}}{\partial T}\right)$$


$$I_{OUT} = \frac{V_{EB1}}{R}$$

$$\frac{\partial I_{OUT}}{\partial T} = \frac{1}{R} \cdot \frac{\partial V_{EB}}{\partial T} - \frac{V_{EB}}{R^2} \cdot \frac{\partial R}{\partial T}$$

$$TC = \frac{1}{V_{EB}} \cdot \frac{\partial V_{EB}}{\partial T} - \frac{1}{R} \cdot \frac{\partial R}{\partial T}$$

**Supply Independent Biasing (Cont.)** CS-33

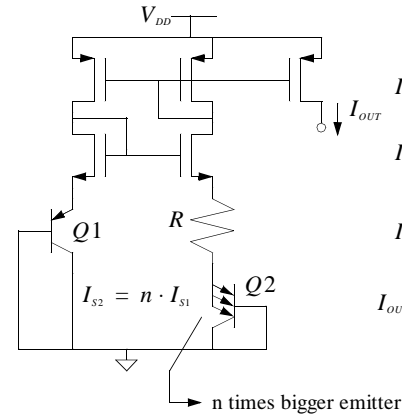$V_{thermal}$  referenced Self-Biased Circuit :




$$I_{OUT} \cdot R + V_{EB2} = V_{EB1}$$

$$I_{OUT} \cdot R + V_T \cdot \ln\left(\frac{I_{OUT}}{n \cdot I_{S1}}\right) = V_T \cdot \ln\left(\frac{I_{OUT}}{I_{S1}}\right)$$

$$I_{OUT} = \frac{V_T}{R} \cdot \ln(n)$$

$$I_{OUT} \cdot R = V_{Thermal} \cdot \ln(n)$$


**Cascode - Self-Biased Source** CS-34

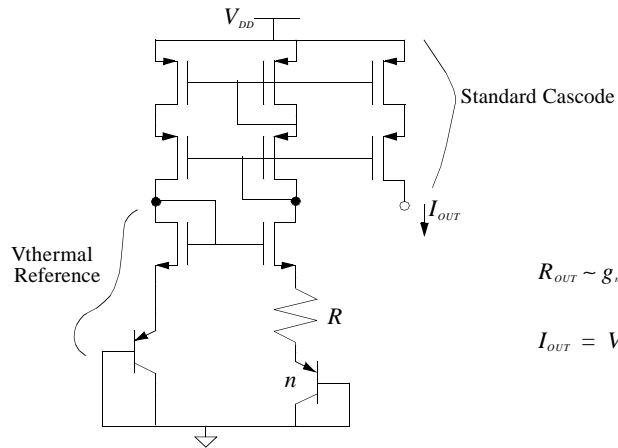

$$R_{OUT} \sim g_m \cdot r_o^2$$

$$I_{OUT} = V_T \cdot \frac{\ln(n)}{R}$$

**Current Source Load** CS-35

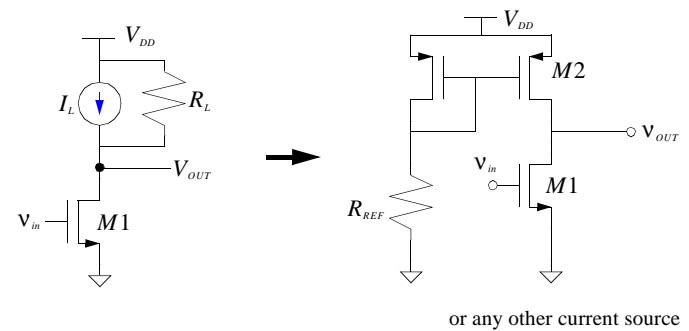

**Current Source Load (Cont.)**

CS-36

$$R_L = r_{o2} = \frac{1}{\lambda_p \cdot I_L} \quad r_{o1} = \frac{1}{\lambda_n \cdot I_L}$$

$$R_{OUT} = R_L \parallel r_{o1} = r_{o2} \parallel r_{o1}$$

$$A_v = -g_m \cdot (r_{o1} \parallel r_{o2}) \quad \text{If } \lambda_n = \lambda_p$$


$$g_m = \frac{2 \cdot I_{DS}}{V_{DSAT}} \quad \leftarrow \quad \text{Handy Formula}$$

$$A_v = -\frac{2 \cdot I_L}{V_{DSAT}} \cdot \frac{1}{2 \cdot \lambda \cdot I_L} = -\frac{1}{\lambda \cdot V_{DSAT}} \propto \frac{1}{I_L^2}$$

**Differential Pair with Current Source Load**

CS-37

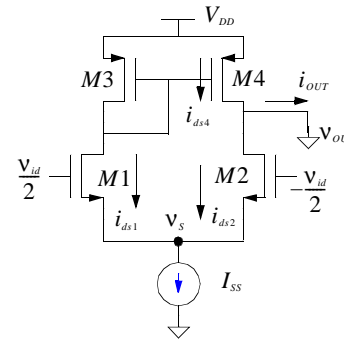**Double to single ended conversion without loss :**



Calculate  $GM$


$$\begin{aligned} \left(\frac{v_{id}}{2} - v_s\right) \cdot g_m &= i_{ds1} = i_{ds3} = i_{ds4} \\ i_{ds2} &= \left(-\frac{v_{id}}{2} - v_s\right) \cdot g_m \\ i_{OUT} &= i_{ds4} - i_{ds2} = \left(\frac{v_{id}}{2} - v_s\right) \cdot g_m - \left(-\frac{v_{id}}{2} - v_s\right) \cdot g_m \\ i_{OUT} &= g_m \cdot v_{id} \\ GM &= \frac{i_{OUT}}{v_{id}} = g_m \end{aligned}$$

by current source connection  
↓

**Differential Pair with Current Source Load (Cont.)**

CS-38

**Rout for Differential Pair :**

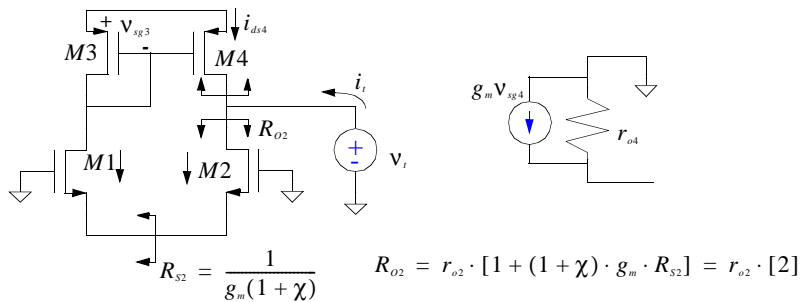

**Differential Pair with Current Source Load (Cont.)**

CS-39

$$\begin{aligned} i_i &= i_{ds2} - i_{ds4} \\ i_{ds4} &= g_m \cdot v_{sg4} - \frac{v_i}{r_{o4}} \\ v_{sg4} &= v_{sg3} = \left(\frac{1}{g_m}\right) \cdot i_{ds1} = -i_{ds2} \cdot \left(\frac{1}{g_m}\right) \\ -g_m \cdot v_{sg4} &= -g_m \cdot \frac{v_i}{2 \cdot r_{o2}} \cdot \frac{1}{g_m} = -\frac{v_i}{2 \cdot r_{o2}} \\ i_{ds4} &= -\frac{v_i}{2 \cdot r_{o2}} - \frac{v_i}{r_{o4}} \\ i_i &= i_{ds2} - i_{ds4} = \frac{v_i}{2 \cdot r_{o2}} + \frac{v_i}{2 \cdot r_{o2}} + \frac{v_i}{r_{o4}} \\ R_{OUT} &= \frac{v_i}{i_i} = r_{o2} \parallel r_{o4} \end{aligned}$$