

University of California
Berkeley
College of Engineering
Department of Electrical Engineering
and Computer Science


Robert W. Brodersen
EECS140

Analog Circuit Design

Lectures
on
OP AMPS


Miller Op Amp

OP-1

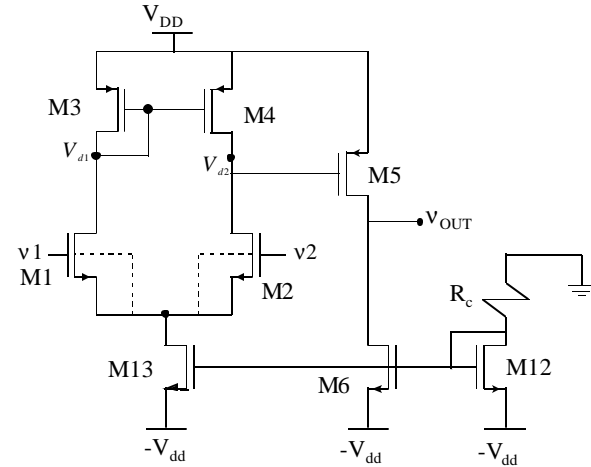

Miller Op Amp (Cont.)

OP-2

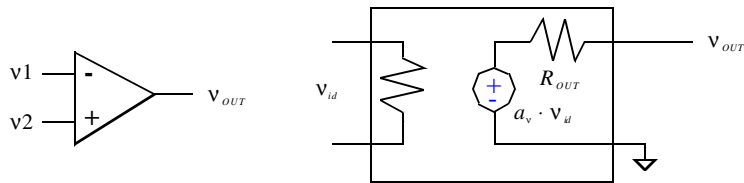

$$R_{ii} = \infty$$

$$R_{OUT} = r_{o5} \parallel r_{o6}$$

$$\frac{v_{d2}}{v_{id}} \cdot \frac{v_{OUT}}{v_{d2}} = \frac{v_{OUT}}{v_{id}}$$

$$g_{m2} \cdot (r_{o2} \parallel r_{o4}) \quad \quad \quad g_{m5} \cdot R_{OUT}$$

Miller Op Amp (Cont.)

OP-3

What is the DC voltage at V_{d2} ?

$$I_{DS1} = I_{DS2} = I_{DS3} = I_{DS4}$$

$$I_{DS3} = \frac{k'}{2} \cdot \frac{W}{L} \cdot (V_{SG3} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD3})$$

$$I_{DS4} = \frac{k'}{2} \cdot \frac{W}{L} \cdot (V_{SG4} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD4})$$

$$I_{DS3} = I_{DS4}$$

$$(V_{SG3} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD3}) = (V_{SG4} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD4})$$

$$V_{SG3} = V_{SG4}$$

~~$$(V_{SG3} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD3}) = (V_{SG3} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD4})$$~~


$$V_{SD3} = V_{SD4} = V_{SG3} = V_T + V_{DSAT3}$$

$$V_{D1} = V_{DD} - V_{SG3} = V_{DD} - V_T - V_{DSAT3} = V_{D2}$$

Miller Op Amp (Cont.)

OP-4

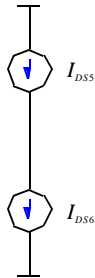To set offset at output or 2nd stage M5, M6 to near zero, set $I_{DS5} = I_{DS6}$



$$I_{SD5} = \frac{k'}{2} \cdot \left(\frac{W}{L}\right)_5 \cdot (V_{SG5} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD5})$$

$$I_{SD6} = \frac{k'}{2} \cdot \left(\frac{W}{L}\right)_6 \cdot (V_{GS6} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD6})$$

Since $V_{SD4} = V_{SG3} = V_{SG5}$

$$I_{SD5} = I_{DS3} \quad \text{if} \quad \left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_3$$

$$I_{SD6} = \frac{1}{2} \cdot I_{SD13} \quad \text{if} \quad \left(\frac{W}{L}\right)_{13} = 2 \cdot \left(\frac{W}{L}\right)_6$$


then $I_{DS6} = I_{DS5}$ or,

$$\frac{I_{DS5}}{I_{DS3}} = \frac{\left(\frac{W}{L}\right)_5}{\left(\frac{W}{L}\right)_3} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_{13}} = \frac{2 \cdot \left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_{13}}$$

Miller Op Amp (Cont.)

OP-5

What happens if $I_1 = \alpha \cdot I_2$

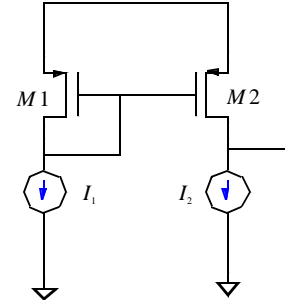

$$\frac{k'}{2} \cdot \left(\frac{W}{L}\right)_1 \cdot (V_{SG1} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD1})$$

$$= \alpha \cdot \frac{k'}{2} \cdot \left(\frac{W}{L}\right)_2 \cdot (V_{SG2} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD2})$$

$$1 + \lambda \cdot V_{SD1} = \alpha \cdot (1 + \lambda \cdot V_{SD2})$$

$$V_{SD2} = \frac{\frac{1}{\lambda} + V_{SD1}}{\alpha} - \frac{1}{\lambda}$$

$$\alpha = 1 \quad V_{SD2} = V_{SD1}$$

$$\alpha = \frac{1}{2} \quad V_{SD2} = \frac{100 + V_{SD1}}{1/2} - 100$$

$$\lambda = 0.01 \quad = 100 + 2 \cdot V_{SD1} \quad \text{Big Offset}$$

Miller Op Amp (Cont.)

OP-6

Gain :

First Stage

$$\frac{v_{ds}}{v_{id}} = -g_{m1} \cdot (r_{o4} \parallel r_{o2})$$

Second Stage

$$\frac{V_{OUT}}{V_{d2}} = -g_{m5} \cdot (r_{o6} \parallel r_{o5})$$

Overall

$$A_v = g_{m1} \cdot g_{m5} \cdot (r_{o4} \parallel r_{o2}) \cdot (r_{o5} \parallel r_{o6})$$

Miller Op Amp (Cont.)

OP-7

$$A_v = \frac{2 \cdot I_{DS1}}{V_{DSAT1}} \cdot \left(\frac{2 \cdot I_{DS5}}{V_{DSAT5}}\right) \cdot \frac{1}{(\lambda_n + \lambda_p) \cdot I_{DS1}} \cdot \frac{1}{(\lambda_n + \lambda_p) \cdot I_{DS5}}$$

$$= \frac{4}{(V_{DSAT1}) \cdot (V_{DSAT5}) \cdot (\lambda_n + \lambda_p)^2}$$

$$A_v = \frac{4}{\left(k'_n \cdot \frac{2 \cdot I_{SD1}}{(W/L)_1}\right)^{\frac{1}{2}} \cdot \left(k'_p \cdot \frac{2 \cdot I_{DS5}}{(W/L)_3}\right)^{\frac{1}{2}} \cdot (\lambda_n + \lambda_p)^2}$$


$$= \frac{2 \cdot (k'_n \cdot k'_p)^{\frac{1}{2}} \cdot \left(\frac{W}{L}\right)_1^{\frac{1}{2}} \cdot \left(\frac{W}{L}\right)_3^{\frac{1}{2}}}{(\lambda_n + \lambda_p)^2 \cdot (I_{SD1} \cdot I_{DS5})^{\frac{1}{2}}}$$

Miller Op Amp (Cont.)

OP-8

$$R_{OUT} = r_{o5} \parallel r_{o6} = \frac{1}{(\lambda_p + \lambda_n) \cdot I_{D55}}$$

Add output stage if this is too high.

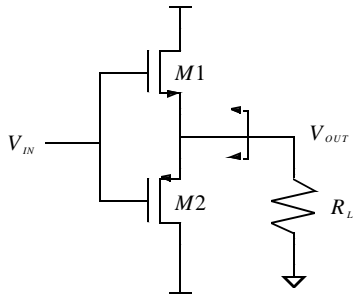

What is the output resistance of this ?

OP-10
Empty Slide

Miller Op Amp (Cont.)

OP-9

You need to choose an operating point since the R_{out} is very non-linear.


$$R_{OUT} = \frac{1}{g_{m1}} \Big|_{V_{IN} > V_{IN}} = \frac{1}{g_{m2}} \Big|_{V_{IN} < -V_{IN}}$$

$$g_m = \left(2 \cdot \frac{W}{L} \cdot k' \cdot I_{DS} \right)^{\frac{1}{2}} = \left(2 \cdot \frac{W}{L} \cdot k' \cdot I_{OUT} \right)^{\frac{1}{2}}$$

$$= \left(2 \cdot \frac{W}{L} \cdot k' \cdot \frac{V_{OUT}}{R_L} \right)^{\frac{1}{2}}$$

OP-11

You could use a level shifter

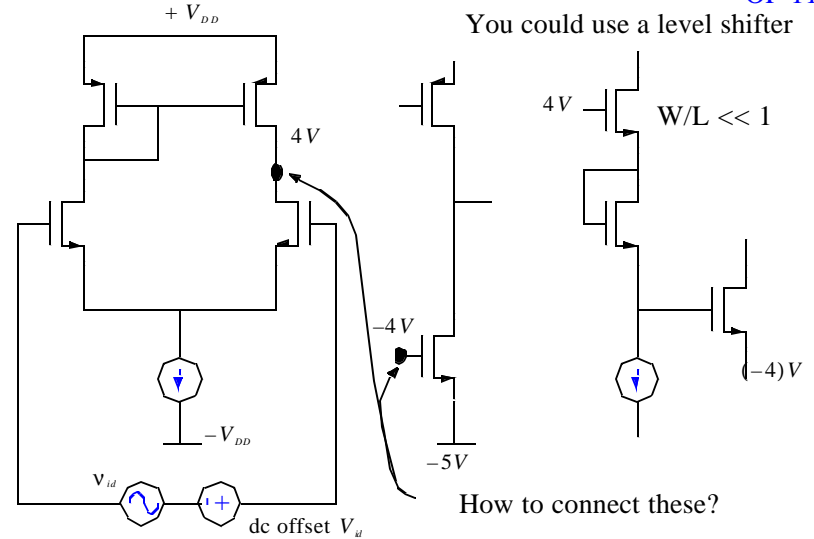

How to connect these?

