

EE140 HW#2 Solution

①

1.

$$V_{SG2} = V_{R1}$$

$$V_{SD2} = V_{R1} + V_{R2}$$


$\therefore V_{SG2} < V_{SD2} \Rightarrow M2$ either in cut-off or saturation region.

When $V_{in} < V_{to(nmos)} = 0.5V$, $M1$ is cut-off

$$I_{DS1} = I_{DS2} = I_{R1} = I_{R2} = 0 \quad \therefore V_{out} = V_{DD}$$

When $V_{R1} = V_{R2} \geq |V_{to(pmos)}| = 0.6V$, $M2$ is in the saturation region.
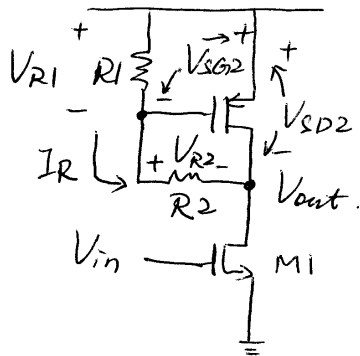
$$\text{When } V_{R1} = V_{R2} = 0.6V \quad V_{out} = V_{DD} - V_{R1} - V_{R2} = 1.8V$$



Assume $M1$ is in the saturation region:

KCL @ output

$$I_{SD2} + I_R = I_{DS1} \quad \text{①}$$

(2)

$$I_{SD2} = \frac{1}{2} K'_p \left(\frac{W}{L}\right)_p (V_{SG2} - |V_{tp}|)^2 \quad (2)$$

$$I_R = \frac{0.6V}{R_2} = \frac{0.6V}{10K\Omega} = 60\mu A. \quad (3)$$

$$I_{DS1} = \frac{1}{2} K'_n \left(\frac{W}{L}\right)_n (V_{GS1} - |V_{tn}|)^2 \quad V_{GS1} = V_{in}$$

$$\therefore I_{DS1} = \frac{1}{2} K'_n \left(\frac{W}{L}\right)_n (V_{in} - |V_{tn}|)^2 \quad (4) \quad V_{SG2} = 0.6V$$

Substitute (2), (3), (4) in (1).

$$\frac{1}{2} \times 3mA/V^2 \times (0.6V - 0.6V)^2 + 60\mu A = \frac{1}{2} \times 8mA/V^2 \times (V_{in} - 0.5)^2$$

Solve $V_{in} = 0.62V$.

* Check the operation region of M1:

$$V_{GS1} = V_{in} = 0.62V$$

$$V_{DS1} = V_{out} = 1.8V \quad \left. \begin{array}{l} V_{GS1} = 0.62V \\ V_{DS1} = 1.8V \end{array} \right\} V_{DS1} > V_{GS1} - V_{t1}$$

M1 is in the sat. region. Assumption is correct.

Another breaking point is when M1 goes into linear region. (boundary point).

$$I_{DS1} = K'_n \left(\frac{W}{L}\right)_n \left[(V_{GS1} - V_{t1}) \cdot V_{DS1} - \frac{V_{DS1}^2}{2} \right] \quad (5)$$

$$V_{GS1} = V_{in} \quad V_{DS1} = V_{out}$$

$$I_D = (V_{DD} - V_{out}) / \dots \quad (6)$$

$$V_{SG2} = \frac{V_{DD} - V_{out}}{2} \quad (3)$$


$$V_{in} - V_{t1} = V_{GS1} \quad (7)$$

Substitute (2), (5), (6), (7), (8) into (1).

$$\frac{1}{2} \times 3 \text{mA/V}^2 \times \left(\frac{3V - V_{out}}{2} - 0.6 \right)^2 +$$

$$\frac{3V - V_{out}}{20 \text{k}\Omega} = 8 \text{mA/V}^2 \times \left[V_{out}^2 - \frac{V_{out}^2}{2} \right]$$

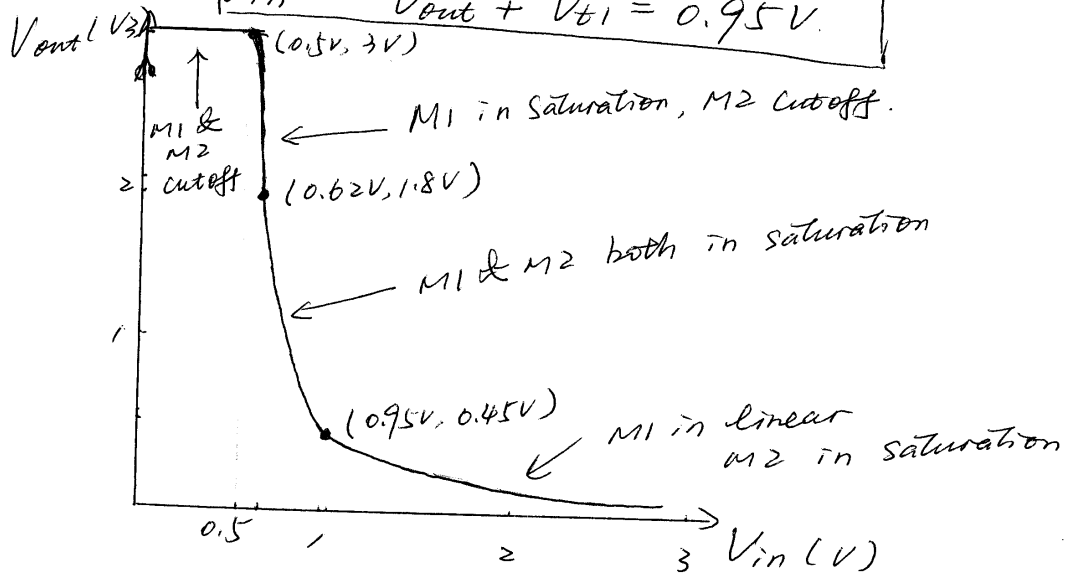Solve $V_{out} = 0.45 \text{V}$
 $V_{in} = V_{out} + V_{t1} = 0.95 \text{V}$



2.

④

$$a) \frac{\text{First circuit}}{V_{out} = 1.5V.}$$

$$I_{DS} = \frac{V_{DD} - V_{out}}{R_{L1}} = \frac{3V - 1.5V}{10k\Omega}$$

$$= \boxed{150\mu A}$$

$V_D = 1.5V, V_G = 1.2V \Rightarrow$ Transistor must be in sat. region.

$$\therefore I_{DS} = \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) \quad (1)$$

$$V_{GS} = V_G - V_S = 1.2V - V_S \quad (2)$$

$$V_{DS} = V_D - V_S = 1.5V - V_S \quad (3)$$

$$V_t = V_{t0} + \gamma (\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f}) \quad (4)$$

$$V_{SB} = V_S - V_B = V_S \quad (5)$$

Substitute (2), (3) into (1) and (5) into (4).

We get:

$$150\mu A = \frac{1}{2} \times 8m \times (1.2V - V_S - V_t)^2 [1 + 0.1(1.5 - V_S)] \quad (6)$$

$$V_t = 0.5 + 0.2 (\sqrt{0.6 + V_S} - \sqrt{0.6}) \quad (7)$$

Use iteration to solve ⑥ & ⑦: ⑤

first guess $V_s \approx 0.5V$:

V_s V_t

0.5V $\xrightarrow{\text{use ⑦}}$ 0.55V

$\xleftarrow{\text{use ⑥}}$

0.462 $\xrightarrow{\text{use ⑦}}$ 0.551V

The V_t difference between the first & second iteration is only 0.001V, enough accuracy.

So $V_s \approx 0.462V$. $V_t \approx 0.551V$

$$V_{in} = V_s - R_s \cdot I_{os} = 0.462V - 0.2k\Omega \times 0.15mA$$
$$= \underline{\underline{0.432V}}$$

Second circuit ..

$$V_{out} = 1.5V$$

$$\therefore I_{os} = \frac{V_{out}}{R_{L2}} = \frac{1.5V}{10k\Omega} = 0.15mA$$

$$V_{in, \max} = 3V$$

⑥

$$\therefore V_{GS, \max} = 3V - 1.5V = 1.5V$$

$$V_{DS} = V_{DD} - V_{out} = 1.5V$$

Therefore, transistor must be in saturation region.

$$I_{DS} = \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) \quad \text{⑧}$$

$$V_{GS} = V_G - V_S = V_{in} - 1.5V \quad \text{⑨}$$

$$V_{DS} = V_{DD} - V_{out} = 1.5V \quad \text{⑩}$$

$$V_t = V_{t0} + \gamma (\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f})$$

$$V_{SB} = V_S - V_B = 1.5V$$

$$\therefore V_t = 0.5V + 0.2 \times (\sqrt{0.6V + 1.5V} - \sqrt{0.6V})$$

$$= \boxed{0.635V} \quad \text{⑪}$$

Sub. ⑨, ⑩, ⑪ into ⑧.

$$0.15mA = \frac{1}{2} \times 8m \times (V_{in} - 1.5 - 0.635)^2 (1 + 0.1 \times 1.5)$$

$$\therefore \boxed{V_{in} = 2.32V}$$

3

b) First circuit.

$$I_{D3} = 150 \mu A.$$

$$V_T = 0.551 V$$

$$\begin{aligned} V_{dsat} &= V_{GS} - V_t \\ &= 1.2V - 0.462V - 0.551V \\ &= 0.187 V. \end{aligned}$$

$$\begin{aligned} g_m &= \frac{2I_D}{V_{dsat}} \\ &= \frac{2 \times 150 \mu A}{0.187 V} \approx 1.6 \text{ ms} \end{aligned}$$

$$\begin{aligned} r_o &= \frac{1}{\lambda I_{D3}} \\ &= \frac{1}{0.11 \times 150 \mu A} = 66.7 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} g_{mbs} &= g_m \cdot \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}} \\ &= 1.6 \text{ ms} \cdot \frac{0.2}{2\sqrt{0.6 + 0.462}} \\ &= 0.155 \text{ ms} \end{aligned}$$

Second circuit.

$$I_{D3} = 150 \mu A$$

$$V_T = 0.635 V$$

$$\begin{aligned} V_{dsat} &= V_{GS} - V_t \\ &= 2.32V - 1.15V \\ &\quad - 0.635V \\ &= 0.185 V. \end{aligned}$$

$$\begin{aligned} g_m &= \frac{2I_D}{V_{dsat}} \\ &= \frac{2 \times 150 \mu A}{0.185 V} \\ &\approx 1.6 \text{ ms} \end{aligned}$$

$$\begin{aligned} r_o &= \frac{1}{\lambda I_{D3}} \\ &= \frac{1}{0.11 \times 150 \mu A} \\ &= 66.7 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} g_{mbs} &= g_m \cdot \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}} \\ &= 1.6 \text{ ms} \cdot \frac{0.2}{2\sqrt{0.6 + 1.15}} \\ &= 0.11 \text{ ms} \end{aligned}$$