

# HOME WORK #5 SOLUTION

1) NMOS:  $k' \frac{W}{L_{eff}} = 16.6 \text{ mA/V}^2$

circuit (a)  $V_{GS} = V_T + \sqrt{\frac{I_{DS}}{\frac{k' W}{2 L_{eff}} (1 + \lambda V_{GS})}}$

$I_{DS} = 200 \mu\text{A}$

By solving for  $V_{GS}$  iteratively:  
(assume an initial value for  $V_{GS}$ , e.g.  $V_{GS} = 0$ ,  
fill it in in the RHS of the equation,  
compute the new value of  $V_{GS}$  and repeat)

$V_{GS} = 0 \rightarrow V_{GS} = 455 \text{ mV} \rightarrow V_{GS} = 449 \text{ mV}$   
 $\rightarrow V_{GS} = 449 \text{ mV}$

$R_{REF} = \frac{V_{DD} - V_{GS}}{I_{DS}} = \frac{1.2\text{V} - 449 \text{ mV}}{200 \mu\text{A}} = 3755 \Omega$

$r_o \approx \frac{1}{\lambda I_{DS}} = 25 \text{ k}\Omega$

$V_{DSat} = 149 \text{ mV}$

→ saturation range is  $[V_{DSat}, V_{DD}] = [149 \text{ mV}, 1.2\text{V}]$

$R_{out} = r_o \approx 25 \text{ k}\Omega$

(SPICE: 27.2 kΩ)

(SPICE: [160 mV, 1.2V])

circuit

ⓑ

$$V_{SB} = R_S I = 200 \text{ mV}$$

$$V_T = V_{T0} + \gamma (\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f}) \\ = 324 \text{ mV}$$

$$V_{GS} - V_T = 149 \text{ mV} \text{ (identical to circuit ⓐ)}$$

$$V_{GS} = (V_{GS} - V_T) + V_T = 149 \text{ mV} + 324 \text{ mV} = 473 \text{ mV}$$

$$R_{REF} = \frac{V_{DD} - V_{GS} - \Delta V_{RS}}{I} = \frac{1.2 \text{ V} - 473 \text{ mV} - 200 \text{ mV}}{200 \mu\text{A}}$$

$$R_{REF} = 2635 \Omega$$

$$r_o \approx \frac{1}{\lambda I_{DS}} = 25 \text{ k}\Omega$$

$$g_m = \frac{2 I_{DS}}{V_{GS} - V_T} = 2.68 \text{ mS}$$

$$\alpha = \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}} = 0.11$$

$$R_{out} = R_S + r_o + (1 + \alpha) g_m r_o R_S$$

$$R_{out} \approx 100 \text{ k}\Omega \text{ (SPICE: } 103 \text{ k}\Omega)$$

$$\text{saturation range: } [\Delta V_{RS} + V_{Dsat}, V_{DD}] \\ = [349 \text{ mV}, 1.2 \text{ V}]$$

$$\text{(SPICE: } [360 \text{ mV}, 1.2 \text{ V}]$$

circuit

©

$$V_{GS2} = 449 \text{ mV} \quad (\text{cfr. circuit } \textcircled{a})$$

$$V_{SB4} = V_{GS2} = 449 \text{ mV}$$

$$V_{T4} = V_{T0} + \gamma (\sqrt{2\phi_f + V_{SB4}} - \sqrt{2\phi_f}) \\ = 350 \text{ mV}$$

$$V_{GS4} - V_{T4} = 149 \text{ mV}$$

$$V_{GS4} = (V_{GS4} - V_{T4}) + V_{T4} = 149 \text{ mV} + 350 \text{ mV} \\ = 449 \text{ mV}$$

$$R_{REF} = \frac{V_{DD} - V_{GS4} - V_{GS2}}{I} = \frac{1.2 \text{ V} - 449 \text{ mV} - 449 \text{ mV}}{200 \mu\text{A}}$$

$$R_{REF} = 1.26 \text{ k}\Omega$$

$$r_o \approx \frac{1}{\lambda I_{D5}} = 25 \text{ k}\Omega$$

$$g_m = \frac{2I_{D5}}{V_{Dsat}} = 268 \text{ mS}$$

$$x_4 = \gamma / (2\sqrt{2\phi_f + V_{SB4}}) = 0.1$$

$$R_{out} = 2r_o + (1+x)g_m r_o^2 \approx (1+x)g_m r_o^2$$

$$R_{out} \approx 1.8 \text{ M}\Omega \quad (\text{SPICE: } 2 \text{ M}\Omega)$$

$$\text{Saturation range: } [V_{GS1} + V_{Dsat3}, V_{DD}] \\ = [648 \text{ mV}, 1.2 \text{ V}]$$

$$(\text{SPICE: } [610 \text{ mV}, 1.2 \text{ V}])$$

$$(V_{D1} = V_{S3} = V_{G3} - V_{GS3} = V_{G4} - V_{GS3} = V_{S4} + V_{GS4} - V_{GS3} \\ = V_{S4} = V_{G2} = V_{GS2})$$

circuit d) The DC-problem is identical to that of circuit c):

$$R_{REF} = 1.26 \text{ k}\Omega$$


(Both problems have 2 stacked diode-connected transistors between  $R_{REF}$  and GND:  $M_4$  and  $M_2$  for problem 1.c,  $M_4$  and  $M_1$  for problem 1.d)

Because of the same reason, the output range will be the same:

$$\text{saturation range: } [V_{GS}, +V_{DSat_3}, V_{DD}] = [648 \text{ mV}, 1.2 \text{ V}]$$

(SPICE:  $[610 \text{ mV}, 1.2 \text{ V}]$ )

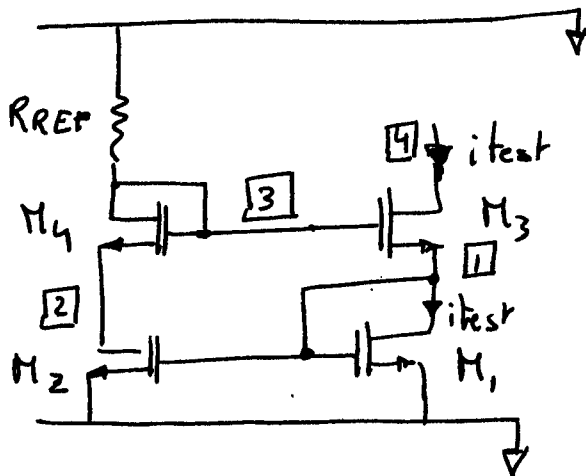For the output resistance, we inject a test current into the drain of  $M_3$  and calculate all the small signal voltages caused by this current



The boxed numbers refer to the nodes, and their voltages will be called  $v_1, v_2, v_3, v_4$

- $i_{test}$  will flow through  $M_3$  into  $M_1$ , which is diode connected

$$\Rightarrow v_1 = \frac{i_{test}}{g_m}$$

- $v_{gs2} = v_1 \Rightarrow g_m \frac{i_{test}}{g_m} = i_{test}$  will flow

out of node 2 into the dependent current source of  $M_2$


- Looking down from node 2, we see  $r_{o2}$ . Looking up from node 2, we see approximately  $\frac{1}{g_m} + R_{REF} \ll r_o$

Therefore, all of the  $i_{test}$  current flowing out of node 2, will come from  $M_3$  and  $R_{REF}$ .

(If you would take the bulk effect into account, you get  $\frac{R_{REF} + 1/g_m}{1+x}$  looking up from node 2)

- $v_3 = -R_{REF} \cdot i_{test}$
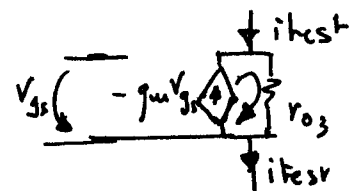
$$v_{gs3} = -\left(R_{REF} + \frac{1}{g_m}\right) i_{test}$$



- $v_{ds3} = r_o \left( \underset{\substack{\uparrow \\ \text{original } i_{test}}}{i_{test}} + \underbrace{i_{test} \left(R_{REF} + \frac{1}{g_m}\right) g_m}_{-g_m v_{gs}} \right)$

- $\Delta V = v_{ds3} + v_{ds1} = \frac{1}{g_m} + 2r_o + g_m r_o R_{REF}$

$R_{out} \approx 2r_o + g_m r_o R_{REF} = 117 \text{ k}\Omega \quad (\text{SPICE: } 134 \text{ k}\Omega)$

```

.title homework 5 - problem 1a

.option nomod post
.include ../models.sp

m1 out in 0 0 nmos w=4u l=0.13u
m2 in in 0 0 nmos w=4u l=0.13u
rref vdd in r=3.755k
vdd vdd 0 dc=1.2
vout out 0 dc=0.5

.op
.tf i(m1) vout

.dc vout start=0 stop=1.2 step=0.01

.end

```

```

.title homework 5 - problem 1b

.option nomod post
.include ../models.sp

m1 out in s1 0 nmos w=4u l=0.13u
rs1 s1 0 r=1k
rs2 s2 0 r=1k
m2 in in s2 0 nmos w=4u l=0.13u
rref vdd in r=2.635k
vdd vdd 0 dc=1.2
vout out 0 dc=0.7

.op
.tf i(m1) vout

.dc vout start=0 stop=1.2 step=0.01

.end

```

```

.title homework 5 - problem 1c

.option nomod post
.include ../models.sp

m1 out1 in1 0 0 nmos w=4u l=0.13u
m2 in1 in1 0 0 nmos w=4u l=0.13u
m3 out in out1 0 nmos w=4u l=0.13u
m4 in in in1 0 nmos w=4u l=0.13u
rref vdd in r=1.26k
vdd vdd 0 dc=1.2
vout out 0 dc=1

.op
.tf i(m3) vout

.dc vout start=0 stop=1.2 step=0.01

.end

```

```

.title homework 5 - problem 1d

.option nomod post
.include ../models.sp

m1 out1 out1 0 0 nmos w=4u l=0.13u
m2 in1 out1 0 0 nmos w=4u l=0.13u
m3 out in out1 0 nmos w=4u l=0.13u
m4 in in in1 0 nmos w=4u l=0.13u
rref vdd in r=1.26k
vdd vdd 0 dc=1.2
vout out 0 dc=1

.op
.tf i(m3) vout

.dc vout start=0 stop=1.2 step=0.01

.end

```

```
*****
homework 5 - problem 1a
```

```
****      small-signal transfer characteristics
```

```
  i(m1)/vout          = 36.7195u
input resistance at   vout      = 27.2335k
output resistance at i(m1)      = 27.2335k
```

```
*****
homework 5 - problem 1b
```

```
****      small-signal transfer characteristics
```

```
  i(m1)/vout          = 9.0106u
input resistance at   vout      = 110.9810k
output resistance at i(m1)      = 110.9810k
```

```
*****
homework 5 - problem 1c
```

```
****      small-signal transfer characteristics
```


```
  i(m3)/vout          = 435.4626n
input resistance at   vout      = 2.2964x
output resistance at i(m3)      = 2.2964x
```

```
*****
homework 5 - problem 1d
```


```
****      small-signal transfer characteristics
```

```
  i(m3)/vout          = 6.8154u
input resistance at   vout      = 146.7259k
output resistance at i(m3)      = 146.7259k
```

# homework 5 - problem 1

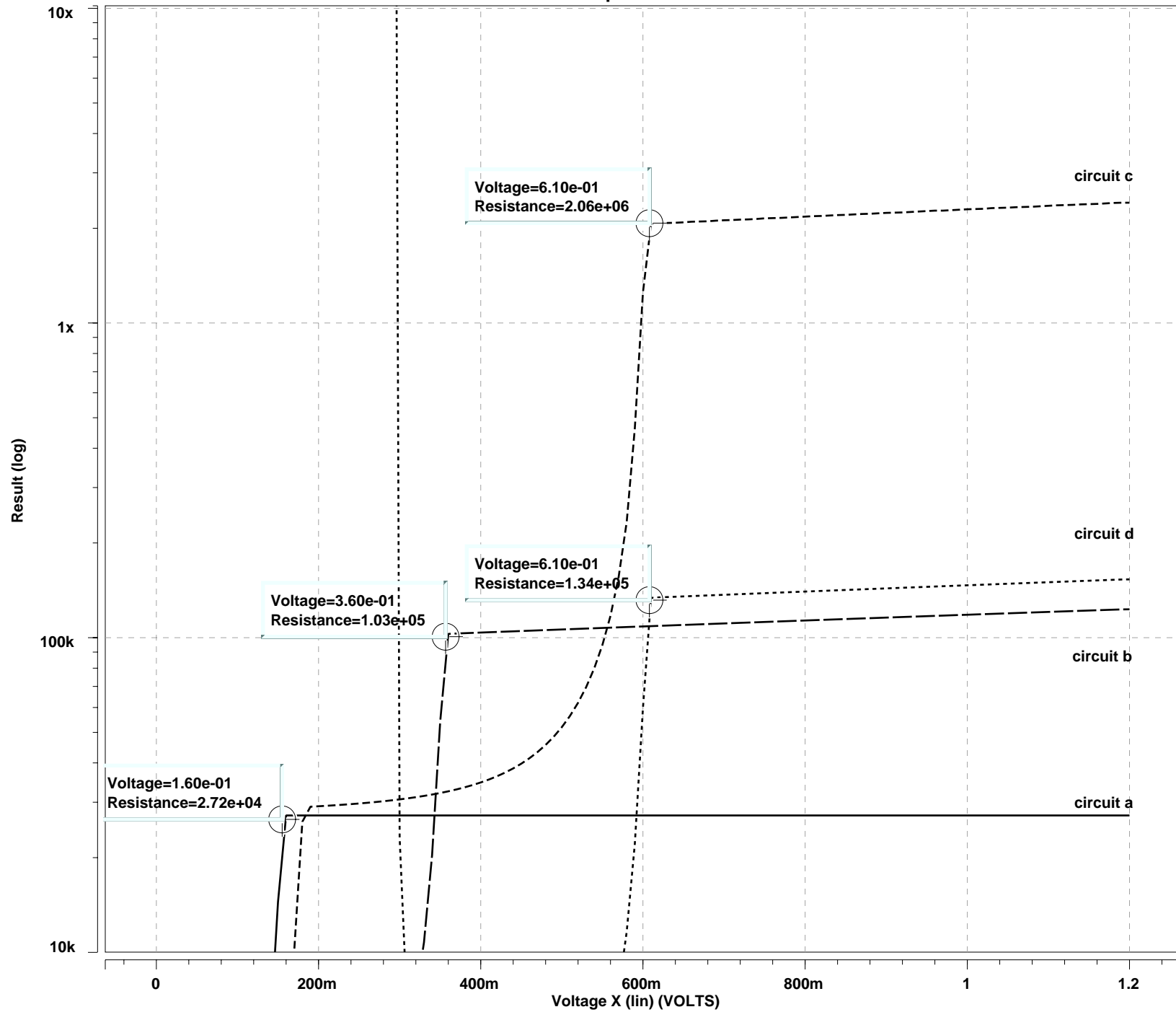

2)

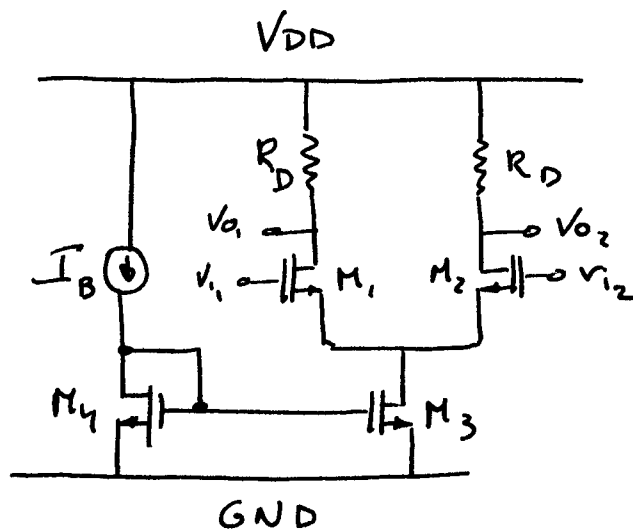


$$V_{DD} = 1.2V$$

$$R_D = 1k\Omega$$

$$I_B = 400\mu A$$

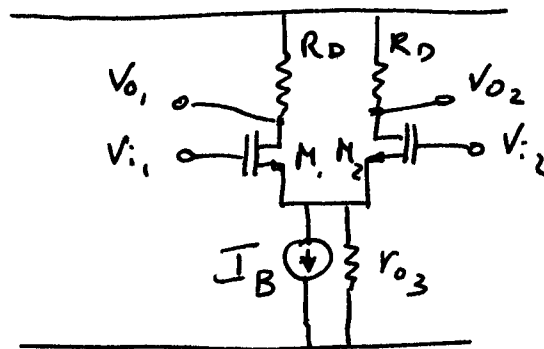Ⓐ Assuming  $M_3$  is in saturation, the circuit can be simplified as follows:



$$I_{DS_{1,2}} = 200\mu A$$


$$V_{DSat_{1,2}} = \sqrt{\frac{2I_{DS_{1,2}}}{k' W/L}} = 155\text{ mV}$$

$$g_{m_{1,2}} = \frac{2I_{DS}}{V_{DSat}} = 2.58\text{ mS}$$

$$r_{o_{1,2}} \approx \frac{1}{\lambda I_{DS_{1,2}}} = 25\text{ k}\Omega \quad (I_{DS_{1,2}} = 200\mu A)$$

$$r_{o3} \approx 1/\lambda I_{DS3} = 12.5\text{ k}\Omega \quad (I_{DS3} = 400\mu A)$$

differential-mode half-circuit:

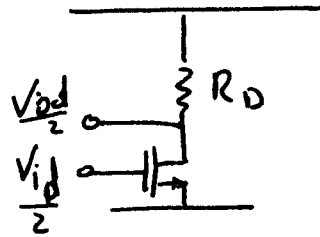

(SPICE: 1.93kΩ)


$$R_{out, dm} = 2R_D \parallel 2r_{o_{1,2}} = 1.92k\Omega$$

$$A_{dm} = -g_{m_{1,2}} R_D \parallel r_{o_{1,2}} = -2.48$$

(SPICE = -2.61)

(Note: this is a small-signal circuit, where the transistor stands for its small-signal model)

common-mode half-circuit:

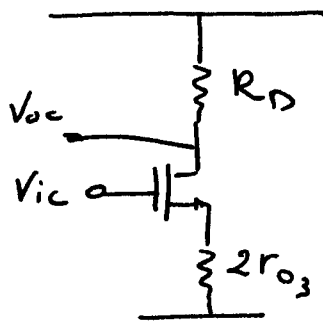

$$R_{out, cm} = R_D \parallel [g_{m_{1,2}} r_{o_{1,2}} 2r_{o_3} + r_{o_{1,2}} + 2r_{o_3}] \approx R_D = 1k\Omega$$

(SPICE: 999.5Ω)

$$A_{cm} = \frac{-g_{m_{1,2}} R_D}{1 + g_{m_{1,2}} 2r_{o_3}} \approx -\frac{R_D}{2r_{o_3}} = 0.04$$

(SPICE: 0.035)

⑤ • lower range of common mode input:  
 point where  $V_{DS3} = V_{DSat3} = \sqrt{\frac{2 I_{DS3}}{k'W/L}} = 220 \text{ mV}$

$$\begin{aligned} V_{IC, \min} &= V_{DSat3} + V_{GS,2} \\ &= V_{DSat3} + V_{T,1,2} + V_{DSat,2} \\ &= 220 \text{ mV} + 0.3 \text{ V} + 155 \text{ mV} \\ &= 675 \text{ mV} \end{aligned}$$

• higher range of common mode input:  
 point where  $V_{DS,1,2} = V_{DSat,1,2}$   
 (when  $M_1$  and  $M_2$  go out of saturation)

Once  $M_3$  is in saturation, the current through each leg is approximately fixed at  $200 \mu\text{A}$ .

This means that  $V_{D,1,2}$  is fixed at

$$\begin{aligned} V_{D,1,2} &= V_{DD} - I \cdot R_D = 1.2 \text{ V} - 200 \mu\text{A} \cdot 1 \text{ k}\Omega \\ &= 1 \text{ V} \end{aligned}$$

$M_1$  and  $M_2$  will go out of saturation when

$$V_{DS,1,2} \leq V_{DSat,1,2} = V_{GS,1,2} - V_T$$

$$\Leftrightarrow V_{D,1,2} \leq V_{G,1,2} - V_T$$

$$\Leftrightarrow V_{G,1,2} \geq V_{D,1,2} + V_T = 1 \text{ V} + 0.3 \text{ V} = 1.3 \text{ V}$$

$$\bullet \quad V_{IC} \in [675 \text{ mV}, 1.3 \text{ V}]$$

© For  $V_{ID} = 0V$  (and assuming  $M_3$  is in saturation) there will be  $\frac{400\mu A}{2} = 200\mu A$  flowing through each leg<sup>2</sup> of the differential pair.

For  $V_{ID} \neq 0$ , one of the diff pair transistors  $M_1$  &  $M_2$  will have more current than the other one; the difference in current will get larger when  $|V_{ID}|$  gets larger. This can continue until all the  $400\mu A$  flows in one of the legs of the diff pair and the other leg will be shut off.

This happens for

$$|V_{ID}| = (V_{GS_{max}} - V_T) - (V_{GS_{min}} - V_T)$$

$$= \sqrt{\frac{2 \cdot 400\mu A}{\mu' W/L}} - 0 = 220mV$$

Then  $V_{i,max} = 0.9V + \frac{220mV}{2} = 1.01V$

( $V_D$  will be  $1.2V - \frac{1k\Omega \cdot 400\mu A}{2} = 1.2V - 400mV = 0.8V$

and  $V_G < V_D + V_T = 1.1V$ , so still saturation)

$$V_{i,min} = 0.9 - \frac{220mV}{2} = 0.79V$$

Saturation range :  $V_{ID} \in [-220mV, +220mV]$

④ . Vod versus Vid - plot

The theoretical shape of this curve is derived on page 220 of the textbook:

$$V_{od} = -R_D \frac{k'_n}{2} \frac{W}{L} V_{id} \sqrt{\frac{4I_{B3}}{k'_n W/L} - V_{id}^2}$$

. Voc versus Vic - plot

Notice how it is impossible to figure out from this plot when  $M_1$ ,  $M_2$  go into the linear region:

$V_D$  will remain approximately constant since there will be still  $200\mu A$  flowing through each diff pair leg, regardless of whether  $M_1$  &  $M_2$  are in the saturation or linear region.

```

.title homework 5 - problem 2

.option nomod post
.include ../models.sp

* main circuit

m1 vo1 vi1 com com nmos w=4u l=0.13u
m2 vo2 vi2 com com nmos w=4u l=0.13u
m3 com bias 0 0 nmos w=4u l=0.13u
m4 bias bias 0 0 nmos w=4u l=0.13u
rd1 vo1 vdd r=1k
rd2 vo2 vdd r=1k

* input network

vic vic 0 dc=0.9
vid vid 0 dc=0
edi1 vi1 vic vid 0 0.5      $ +vid/2 to positive input
edi2 vic vi2 vid 0 0.5      $ -vid/2 to negative input

* output network

eco1 voc_1 voc_2 vo1 0 0.5    $ construct (vo1+vo2)/2
eco2 voc voc_1 vo2 0 0.5
voc voc_2 0 0                $ current probe (0V v source)
fco1 vo1 gnd voc -1          $ feed current back to circuit
fco2 vo2 gnd voc -1

* supply and bias

ibias vdd bias dc=400u
vdd vdd 0 dc=1.2

* analysis statements

.op

.probe dc vod=v(vo1,vo2) voc=v(voc)
.dc vid start=-1.2 stop=+1.2 step=0.01
.dc vic start=0 stop=1.5 stop=0.01

.tf v(vo1,vo2) vid
*.tf v(voc) vic

.end

```

```

*****
homework 5 - problem 2

****      small-signal transfer characteristics
           (differential mode)

v(vo1,vo2)/vid          = -2.6078
input resistance at    vid      = 1.000e+20
output resistance at v(vo1,vo2) = 1.9311k


****      small-signal transfer characteristics
           (common mode)

v(voc)/vic              = -35.3444m
input resistance at    vic      = 1.000e+20
output resistance at v(voc) = 999.5331

```

Wave	Symbol
D4:A0:v(vod)	X

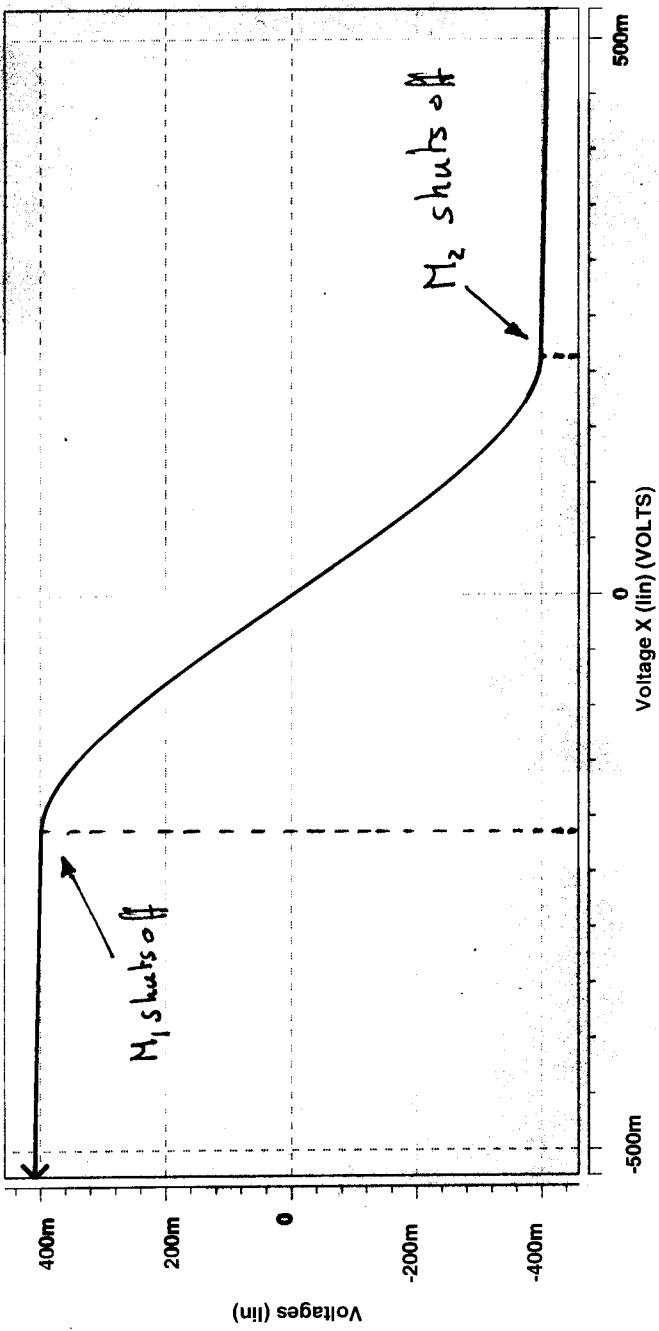homework 5 - problem 2 - differential mode output



Wave	Symbol
D4:A1:v(voc)	X

homework 5 - problem 2 - common mode output

