

2) For the circuit shown in figure 2:

$$V_{DD} = 1.2 \text{ V}, R_{LOAD} = 1 \text{ K}\Omega, I_B = 9.375 \text{ }\mu\text{A}.$$

$$(W/L)_{1a} = (W/L)_{2a} = 7.2 \text{ }\mu\text{m} / 0.13 \text{ }\mu\text{m} \quad (W/L)_{1b} = (W/L)_{2b} = 18 \text{ }\mu\text{m} / 0.13 \text{ }\mu\text{m}$$

$$(W/L)_3 = 0.4 \text{ }\mu\text{m} / 0.35 \text{ }\mu\text{m} \quad (W/L)_{4a} = (W/L)_{4b} = 1 \text{ }\mu\text{m} / 0.35 \text{ }\mu\text{m}$$

V_{in} is referenced to the negative supply rail.

- a) Calculate the V_{Dsat} 's for all the transistors, assuming the output is at 0 V.
- b) Calculate the value of V_{IN} so that the output is at 0 V.
- c) Calculate the range of output voltages so the active transistors remain in saturation. (e.g. for a negative output voltage, M1b, M2b, M3 have to remain in saturation).
- d) Verify part (a)-(c) with SPICE:
 - i) Do a DC sweep with a small step size around the calculated value of V_{IN} to verify the range of output voltages and to determine the real value of V_{IN} for which the output becomes 0 V.
Use this experimentally determined voltage V_{IN} , for which the output becomes 0 V, as the input bias voltage.
 - ii) Do an operating point analysis to verify the V_{Dsat} 's.
- e) Calculate the sine wave efficiency (power into load / total power) for a full swing sine wave at the output ('full swing' meaning the range of output voltages calculated in part (c) and verified in part (d))
- f) Verify the efficiency with SPICE:
 - i) Make your input voltage source a sine wave source:
`vin in1 in2 sin(<dc-voltage> <amplitude> <freq>)`
Use the value for <dc-voltage> from part (d). Set <amplitude> to get the full output swing. Set <freq> to 1K (= 1 KHz)
 - ii) Do a transient analysis (time domain analysis) for one period of the sine wave and measure the power into the load and the total supply power:
`.meas tran p_load avg p(rload)`
`.meas tran p_supply_p avg p(vddp)`
`.meas tran p_supply_n avg p(vddn)`
`.meas tran p_supply param='-p_supply_p-p_supply_n'`
`.meas tran p_eff param='100*p_load/p_supply'`
`.tran 1u 1m`
where 'rload' is the load resistance, 'vddp' is the positive supply and 'vddn' is the negative supply. The measured values will be listed in your output file.
'p_eff' is the efficiency.

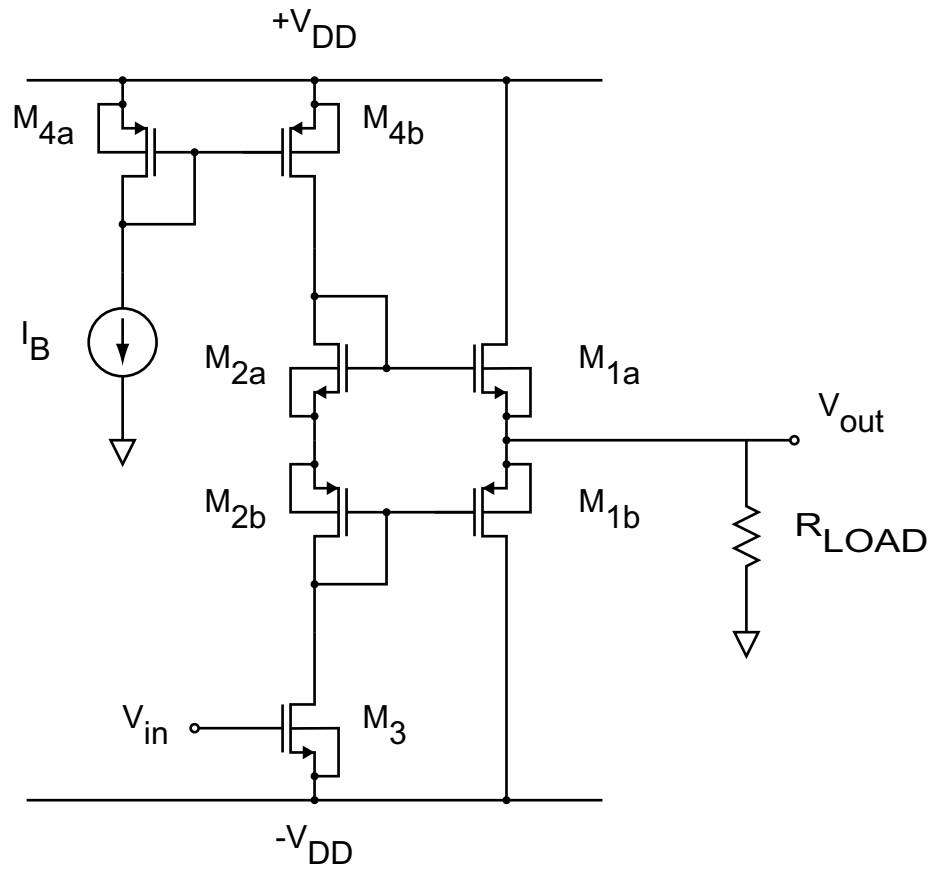


Figure 2.