

UNIVERSITY OF CALIFORNIA AT BERKELEY
College of Engineering
Department of Electrical Engineering and Computer Science

R.W. Brodersen
Mike Chen

Homework #7
(Due 4/27/04)

EECS 140
Spring 2004

- 1) Do problem 9.21 in G&M textbook with our device model and following changes.
 - a) $V_{dd}=1.2V$, and $V_{ss}=0V$.
 - b) (W/L) of M3 and M4 are $5\mu m/0.13\mu m$, and the rest of device are $10\mu m/0.13\mu m$. (Note: you should derive your own (W/L) for M9)
 - c) $V_{ic}=0.6V$. V_{sb} of M9 = 0.

Device model:

```
.model nch nmos LEVEL=1 tox=2.6n vt0=0.3 gamma=0.2 phi=0.6 u0=250 ld=0.025u
+ capop=0 acm=3 ldif=0 hdif=0.2u cj=8e-4 cjsw=8e-12 cjgate=8e-11
+ lambda=0.2
```

```
.model pch pmos LEVEL=1 tox=2.6n vt0=-0.3 gamma=0.2 phi=0.6 u0=100 ld=0.025u
+ capop=0 acm=3 ldif=0 hdif=0.2u cj=8e-4 cjsw=8e-12 cjgate=8e-11
+ lambda=0.15
```

- 2) Given the circuits in Figure 1 and 2, answer the following questions in terms of g_m , r_o of transistors, capacitors and resistors denoted in the figures.
 - a) Identify the feedback loop and type.
 - b) Find out forward gain A, feedback gain f, and loop gain T.
 - c) Find out closed loop gain, input and output impedance.

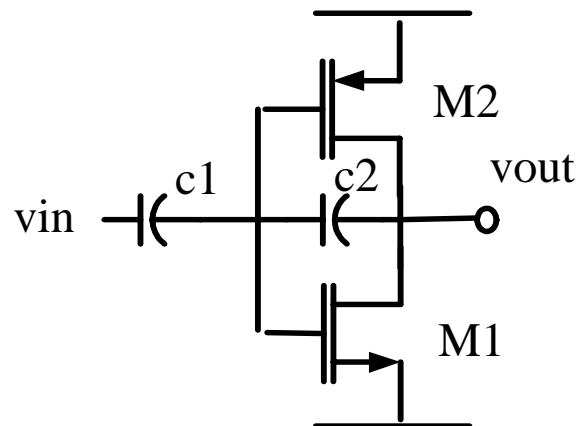


Figure 1

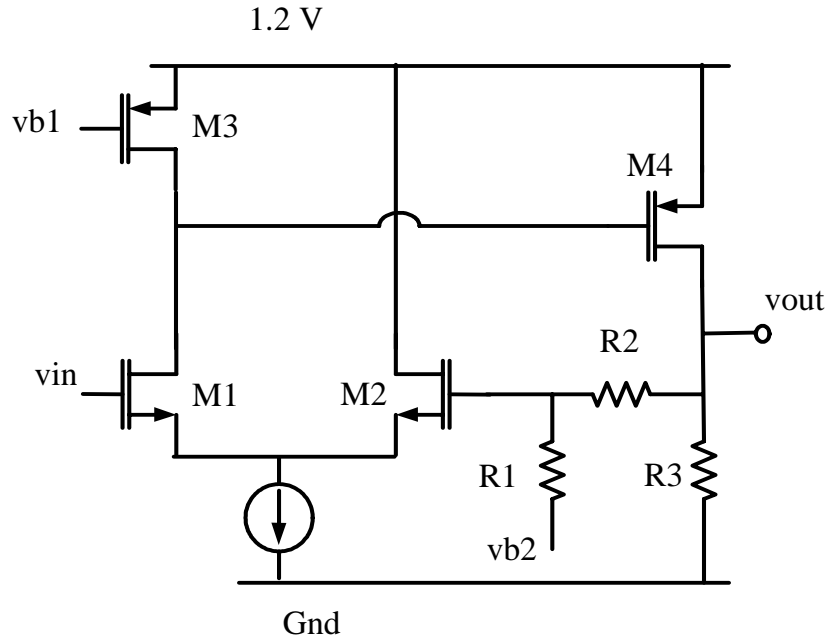


Figure 2

- 3) Using feedback analysis, identify the type of feedback, and calculate the closed loop gain, input and output impedance. How does this compare to a traditional common drain stage? At what frequency range the circuit lost its advantage

compared to common drain? Assume $A(S) = \frac{K}{1 + S/\omega_p}$

