

# LECTURE 170 – TEMPERATURE STABLE REFERENCES

## LECTURE ORGANIZATION

### Outline

- Principles of temperature stable references
- Examples of temperature stable references
- Design of bias voltages for a chip
- Summary

***CMOS Analog Circuit Design, 2<sup>nd</sup> Edition Reference***

Pages 153-159

## PRINCIPLES OF TEMPERATURE STABLE REFERENCES

### Temperature Stable References

- The previous reference circuits failed to provide small values of temperature coefficient although sufficient power supply independence was achieved.
- This section introduces a temperature stable reference that cancels a positive temperature coefficient with a negative temperature coefficient. The technique is sometimes called the *bandgap reference* although it has nothing to do with the bandgap voltage.

### Principle

$$V_{REF}(T) = V_{PTAT}(T) + K \cdot V_{CTAT}(T)$$


where

$V_{PTAT}(T)$  is a voltage that is *proportional to absolute temperature* (PTAT)

$V_{CTAT}(T)$  is a voltage that is *complimentary to absolute temperature* (CTAT)

and

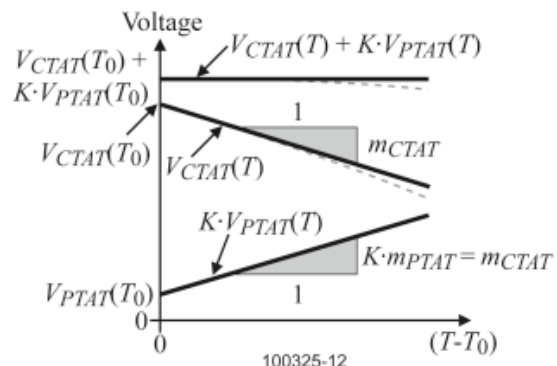
$K$  is a temperature independent constant that makes  $V_{REF}(T)$  independent of temperature



## PTAT Voltage

The principle illustrated on the last slide requires perfectly linear positive and negative temperature coefficients to work properly. We will now show a technique of generating PTAT voltages that are linear with respect to temperature.

Implementation of a PTAT voltage:

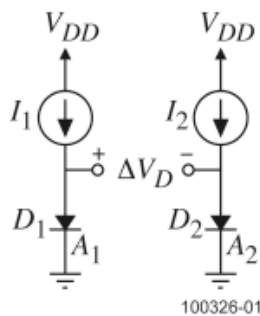

$$\begin{aligned}
 V_{PTAT} = \Delta V_D &= V_{D1} - V_{D2} = V_t \ln\left(\frac{I_1}{I_{S1}}\right) - V_t \ln\left(\frac{I_2}{I_{S2}}\right) \\
 &= V_t \ln\left(\frac{I_1}{I_2} \frac{I_{S2}}{I_{S1}}\right) = V_t \ln\left(\frac{I_{S2}}{I_{S1}}\right) = V_t \ln\left(\frac{A_2}{A_1}\right) = \frac{kT}{q} \ln\left(\frac{A_2}{A_1}\right)
 \end{aligned}$$

if  $I_1 = I_2$ .


Therefore, if  $A_2 = 10A_1$ ,  $\Delta V_D$  at room temperature becomes,

$$\Delta V_D = \left[ \frac{k}{q} \ln\left(\frac{A_2}{A_1}\right) \right] T = \left[ \frac{1.381 \times 10^{-23} \text{ J/K}}{1.6 \times 10^{-19} \text{ Coul}} \ln(10) \right] T = (+0.086 \text{ mV/}^\circ\text{C}) T$$

$$\therefore V_{PTAT} = V_t \ln\left(\frac{A_2}{A_1}\right)$$
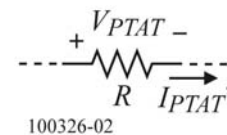
## Pseudo-PTAT Currents

In developing temperature independent voltages, it is useful to show how to generate PTAT currents. A straight-forward method is to superimpose  $V_{PTAT}$  across a resistor as shown:



Because  $R$  is always dependent on temperature, this current is called a *pseudo-PTAT current* and is designated by  $I_{PTAT}$ .

When a pseudo-PTAT current flows through a second resistor with the same temperature characteristics as the first, it creates a new  $V_{PTAT}$  voltage.


The new  $V_{PTAT}$  voltage,  $V_{PTAT2}$  is equal to,

$$V_{PTAT2} = \frac{R_2}{R_1} V_{PTAT1}$$

Differentiating with respect to temperature gives


$$\frac{dV_{PTAT2}}{dT} = \frac{R_2}{R_1} \left( \frac{dR_2}{R_2 dT} - \frac{dR_1}{R_1 dT} \right) + \frac{dV_{PTAT1}}{dT}$$

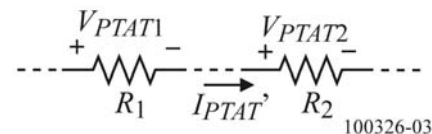Therefore, if the temperature coefficient of  $R_1$  and  $R_2$  are equal, then the temperature dependence of  $V_{PTAT2}$  is the same as  $V_{PTAT1}$ .



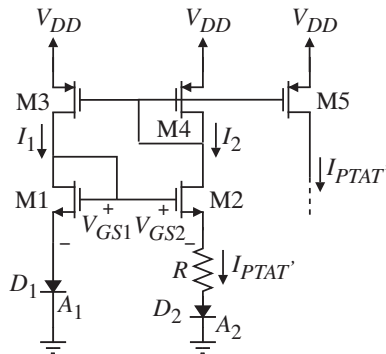
## Pseudo-PTAT Currents - Continued

This can be done through the circuits below which use only MOSFETs and *pn* junctions or MOSFETs, an op amp and *pn* junctions.



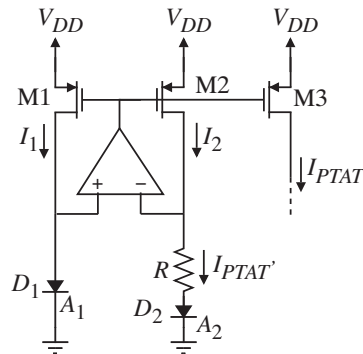Pseudo-PTAT current generator using only MOSFETs and *pn* junctions.



Pseudo-PTAT current generator using MOSFETs, an op amp and *pn* junctions.  
100326-04

In these circuits,  $I_1 = I_2$  and the voltage across  $D_1$  is made equal to the voltage across the series combination of  $R$  and  $D_2$  to create the pseudo-PTAT current,

$$I_{PTAT}' = \frac{V_{D1} - V_{D2}}{R} = \frac{kT}{Rq} \ln\left(\frac{A_2}{A_1}\right)$$

where  $V_{GS1} = V_{GS2}$  for the MOSFET only version.

## CTAT Voltage

This becomes more challenging because a true CTAT voltage does not exist. The best approach is to examine the *pn* junction (can be a diode or BJT).

The current through a *pn* junction shown can be written as,

$$J_D = \left[ \frac{qD_n n_i^2}{L_n N_A} + \frac{qD_p p_{no}}{L_p} \right] \left( \frac{v_D - V_{G0}}{V_t} \right) = AT^\gamma \exp\left(\frac{v_D - V_{G0}}{V_t}\right)$$

Consider the circuit shown. It can be shown, that  $v_D(T)$  can be given as,

$$v_D(T) = V_{G0} \left( 1 - \frac{T}{T_0} \right) + v_{D0} \left( \frac{T}{T_0} \right) + \frac{\gamma kT}{q} \ln\left(\frac{T}{T_0}\right) + \frac{kT}{q} \ln\left(\frac{J_D}{J_{D0}}\right)$$

where,

$V_{G0}$  = bandgap voltage of silicon (1.205V)


$T_0$  = a reference temperature about which  $T$  varies

$\gamma$  = a temperature coefficient for the *pn* junction saturation current ( $\gamma \approx 3$ )

$J_D$  = *pn* junction current density

In the above expression for  $v_D(T)$  the term  $\frac{\gamma kT}{q} \ln\left(\frac{T}{T_0}\right)$  is not linear with  $T$ !!

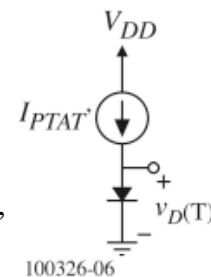
This term will create a problem called “bandgap curvature problem” because a perfectly linear PTAT function cannot be cancelled by a term that is not truly CTAT.



100326-06
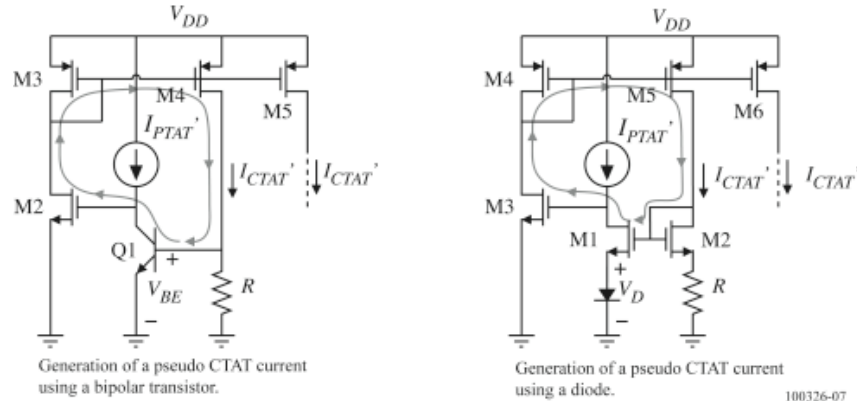
## Pseudo CTAT Currents

The circuits below show two ways of creating a pseudo CTAT current using negative feedback:<sup>†</sup>




The negative feedback loop shown causes the current designated as  $I_{CTAT}'$  to be,

$$I_{CTAT}' = \frac{V_{BE}}{R} = \frac{V_D}{R}$$

<sup>†</sup> I.M. Gunawan, G.C.M. Jeijer, J. Fonderie, and J.H. Huijsing, "A Curvature-Corrected Low-Voltage Bandgap Reference, *IEEE J. Solid-state Circuits*, vol. SC-28, No. 6, June 1993, pp. 677-670.

## Temperature Independent Voltage References

Basic structures:

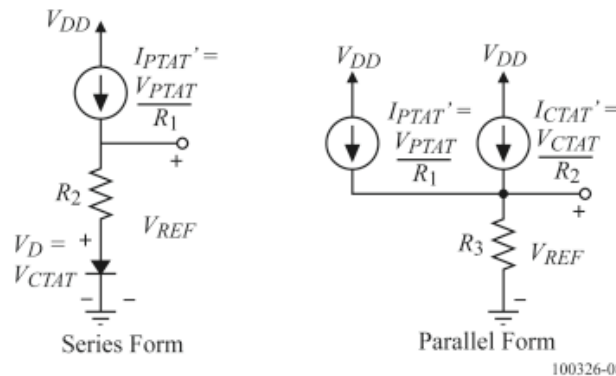

Series form:

$$V_{REF} = I_{PTAT}'R_2 + V_D = \left(\frac{R_2}{R_1}\right)V_{PTAT} + V_{CTAT}$$

Parallel form:

$$V_{REF} = (I_{PTAT}' + I_{CTAT}')R_3 + V_D = \left(\frac{R_3}{R_1}\right)V_{PTAT} + \left(\frac{R_3}{R_2}\right)V_{CTAT} = \left(\frac{R_3}{R_2}\right)\left[\left(\frac{R_2}{R_1}\right)V_{PTAT} + V_{CTAT}\right]$$

To achieve temperature independence,  $V_{REF}$  must be differentiated with respect to temperature and set equal to zero. The resistor ratios and other parameters can be used to achieve temperature independence.

### Conditions for Temperature Independence

Differentiating either the series or parallel form with respect to temperature and equating to zero gives,

$$K = \frac{R_2}{R_1} = - \frac{dV_{CTAT}/dT}{dV_{PTAT}/dT}$$

The slopes of  $V_{CTAT}$  and  $V_{PTAT}$  at a given temperature,  $T_0$ , are:

$$m_{CTAT} = \left. \frac{dV_{CTAT}}{dT} \right|_{T=T_0} = \frac{V_D - V_{GO}}{T_0} + (\alpha - \gamma) \left( \frac{k}{q} \right) = \frac{V_{CTAT} - V_{GO}}{T_0} + (\alpha - \gamma) \left( \frac{V_{t0}}{T_0} \right)$$

where  $\alpha$  = temperature dependence of  $J_D$  [ $J_D(T) \propto T^\alpha$ , where  $\alpha = 1$  for PTAT current flowing through the pn junction]

and

$$m_{PTAT} = \left. \frac{dV_{PTAT}}{dT} \right|_{T=T_0} = \frac{k}{q} \ln \left( \frac{J_{D2}}{J_{D1}} \right) = \frac{k}{q} \ln \left( \frac{A_2}{A_1} \right) = \frac{V_{t0}}{T_0} \ln \left( \frac{A_2}{A_1} \right) = \frac{V_{PTAT}}{T_0}$$

Therefore, the temperature independent constant multiplying  $V_{PTAT}$  is

$$\text{Temp. independent constant} = K = \frac{R_2}{R_1} = \frac{V_{GO} - V_{CTAT} + (\gamma - \alpha)V_{t0}}{V_{PTAT}}$$

Therefore,

$$V_{REF} = V_{GO} - V_{CTAT} + (\gamma - \alpha)V_{t0} + V_{CTAT} = V_{GO} + (\gamma - \alpha)V_{t0} \approx 1.205\text{V} + 0.057 = 1.262\text{V}$$

### Example 170-1 – Temp. Independent Constant for Series and Parallel References

(a.) Design the ratio of  $R_2/R_1$  for the series configuration if  $V_{CTAT} = 0.6\text{V}$  and  $A_2/A_1 = 10$  for room temperature ( $V_t = 0.026\text{V}$ ). Assume  $\gamma = 3.2$  and  $\alpha = 1$ . Find the value of  $V_{REF}$ .

$$\frac{R_2}{R_1} = \frac{V_{GO} - V_{CTAT} + (\gamma - \alpha)V_{t0}}{V_{PTAT}} = \frac{1.205 - 0.6 + 2.2(0.026)}{0.026(2.3026)} = 11.06$$

$$V_{REF} = 1.205 + 2.2(0.026) = 1.262\text{V}$$

(b.) For the parallel configuration find the values of  $R_2/R_1$  and  $R_3/R_2$  if  $V_{REF} = 0.5\text{V}$ .

From (a.) we know that  $R_2/R_1 = 11.05$ . We also know that,

$$\begin{aligned} V_{REF} &= \left( \frac{R_3}{R_1} \right) V_{PTAT} + \left( \frac{R_3}{R_2} \right) V_{CTAT} = \left( \frac{R_3}{R_2} \right) \left[ \left( \frac{R_2}{R_1} \right) V_{PTAT} + V_{CTAT} \right] \\ &= (R_3/R_2)[11.05 \ln(10)(0.026) + 0.6] = (R_3/R_2)1.262 = 0.5 \end{aligned}$$

$$\therefore (R_3/R_2) = 0.3963$$

If  $R_1 = 1\text{k}\Omega$ , then  $R_2 = 11.05\text{k}\Omega$  and  $R_3 = 4.378\text{k}\Omega$

### A Series Temperature Independent Voltage Reference

An early realization of the series form is shown below†:

Assuming  $V_{OS} = 0$ , then  $V_{R1}$  is

$$\begin{aligned} V_{R1} &= V_{EB2} - V_{EB1} = V_t \ln\left(\frac{J_2}{J_{s2}}\right) - V_t \ln\left(\frac{J_1}{J_{s1}}\right) \\ &= V_t \ln\left(\frac{I_2 A_{E1}}{I_1 A_{E2}}\right) = V_t \ln\left(\frac{R_2 A_{E1}}{R_1 A_{E2}}\right) \end{aligned}$$

The op amp forces the relationship  $I_1 R_2 = I_2 R_3$


$$\therefore V_{REF} = V_{EB2} + I_2 R_3 = V_{EB2} + V_{R1} \left(\frac{R_2}{R_1}\right) = V_{EB2} + \left(\frac{R_2}{R_1}\right) V_t \ln\left(\frac{R_2 A_{E1}}{R_1 A_{E2}}\right) = V_{CTAT} + \left(\frac{R_2}{R_1}\right) \ln\left(\frac{R_2 A_{E1}}{R_1 A_{E2}}\right) V_t$$

Differentiating the above with respect to temperature and setting the result to zero, gives

$$\left(\frac{R_2}{R_1}\right) \ln\left(\frac{R_2 A_{E1}}{R_1 A_{E2}}\right) = \frac{V_{GO} - V_{CTAT} + (\gamma - \alpha) V_{t0}}{V_t}$$

If  $V_{OS} \neq 0$ , then  $V_{REF}$  becomes,
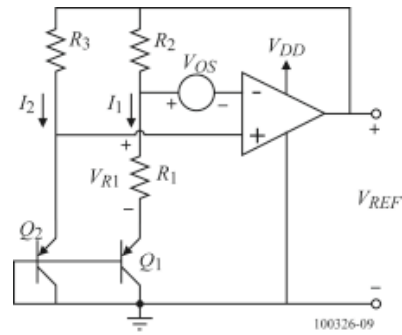
$$V_{REF} = V_{EB2} - \left(1 + \frac{R_2}{R_1}\right) V_{OS} + \frac{R_2}{R_1} V_t \ln\left[\frac{R_2 A_{E1}}{R_1 A_{E2}} \left(1 - \frac{V_{OS}}{I_1 R_2}\right)\right]$$



† K.E. Kujik, "A Precision Reference Voltage Source," *IEEE Journal of Solid-State Circuits*, Vol. SC-8, No. 3 (June 1973) pp. 222-226.

### Example 170-2 – Design of the Previous Temperature Independent Reference

Assume that  $A_{E1} = 10 A_{E2}$ ,  $V_{EB2} = 0.7$  V,  $R_2 = R_3$ , and  $V_t = 0.026$  V at room temperature for temperature independent reference on the previous slide. Find  $R_2/R_1$  to give a zero temperature coefficient at room temperature. If  $V_{OS} = 10$  mV, find the change in  $V_{REF}$ . Note that  $I_1 R_2 = V_{REF} - V_{EB2} - V_{OS}$ .

Evaluating the temperature independent constant gives

$$\left(\frac{R_2}{R_1}\right) \ln\left(\frac{R_2 A_{E1}}{R_3 A_{E2}}\right) = \frac{V_{GO} - V_{CTAT} + (\gamma - \alpha) V_{t0}}{V_{PTAT}} = \frac{1.205 - 0.7 + (2.2)(0.026)}{0.026} = 21.62$$



Therefore,  $R_2/R_1 = 9.39$ . In order to use the equation for  $V_{REF}$  with  $V_{OS} \neq 0$ , we must know the approximate value of  $V_{REF}$  and iterate if necessary because  $I_1$  is a function of  $V_{REF}$ . Assuming  $V_{REF}$  to be 1.262, we obtain from

$$V_{REF} = V_{EB2} - \left(1 + \frac{R_2}{R_1}\right) V_{OS} + \frac{R_2}{R_1} V_t \ln\left[\frac{R_2 A_{E1}}{R_1 A_{E2}} \left(1 - \frac{V_{OS}}{V_{REF} - V_{EB2} - V_{OS}}\right)\right]$$

a new value  $V_{REF} = 1.153$  V. The second iteration makes little difference on the result because  $V_{REF}$  is in the argument of the logarithm
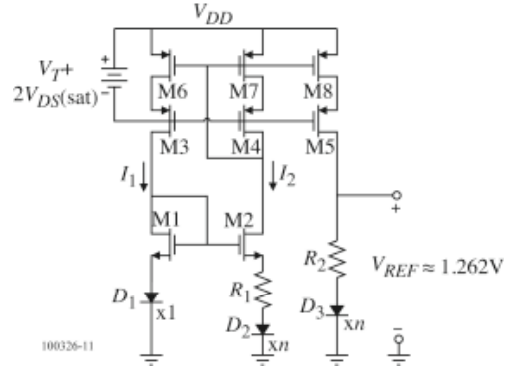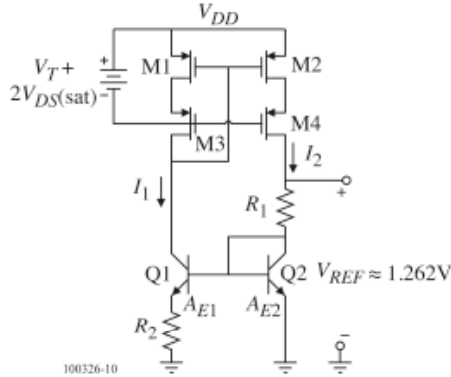
### Series Temperature Independent Voltage References

The references shown do not use an op amp and avoid the issues with offset voltage and PSRR.



$$I_1 = I_{PTAT}' = \frac{V_{BE2} - V_{BE1}}{R_2} = \frac{V_t}{R_2} \left[ \ln\left(\frac{I_2}{I_{S2}}\right) - \ln\left(\frac{I_1}{I_{S1}}\right) \right]$$

$$= \frac{V_t}{R_2} \ln\left(\frac{I_{S1}}{I_{S2}}\right) = \frac{V_t}{R_2} \ln\left(\frac{A_{E1}}{A_{E2}}\right)$$

Since  $I_1 = I_2$ ,  $V_{REF} = V_{BE2} + I_1 R_1 = V_{BE1} + \left(\frac{R_1}{R_2} \ln\left(\frac{A_{E1}}{A_{E2}}\right)\right) V_t$

$$= V_{CTAT} + \left(\frac{R_1}{R_2} \ln\left(\frac{A_{E1}}{A_{E2}}\right)\right) V_{PTAT}$$

$$V_{D1} = I_2 R_1 + V_{D2}$$


$$I_3 = I_2 = I_{PTAT}' = \frac{V_t}{R} \ln(n)$$

$$V_{REF} = V_{D3} + I_3(kR) = V_{D3} + kV_t \ln(n)$$

$$= V_{CTAT} + k \ln(n) V_{PTAT}$$
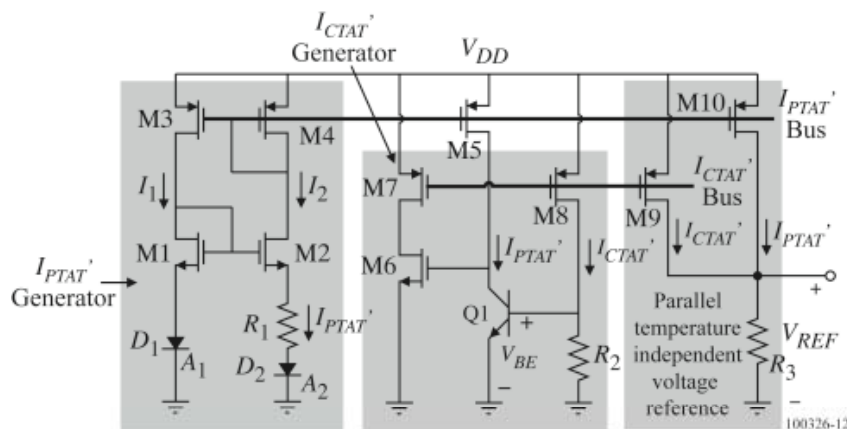
### Parallel Temperature Independent Voltage Reference

A parallel form of the temperature independent voltage reference is shown below:




$$V_{REF} = \left(\frac{R_3}{R_1}\right) V_{PTAT} + \left(\frac{R_3}{R_2}\right) V_{CTAT}$$

Comments:

- The BJT of the  $I_{CTAT}'$  generator can be replaced with an MOSFET-diode equivalent
- Any value of  $V_{REF}$  can be achieved
- Part (b.) of Example 170-1 showed how to design the resistors of this implementation
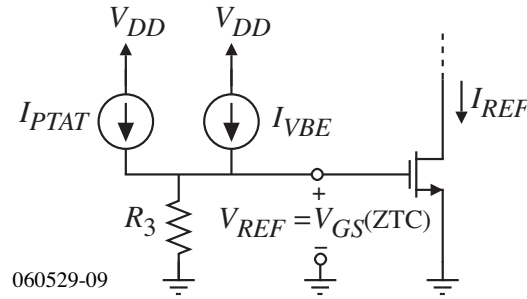
### How Can a Bandgap “Current” Reference be Obtained?



Use a MOSFET under ZTC operation and design the parallel form of the bandgap voltage reference to give a value of  $V_{ZTC}$ .


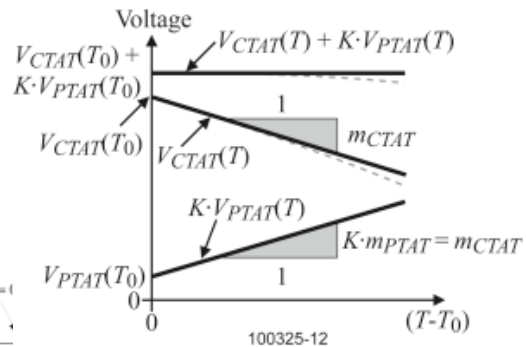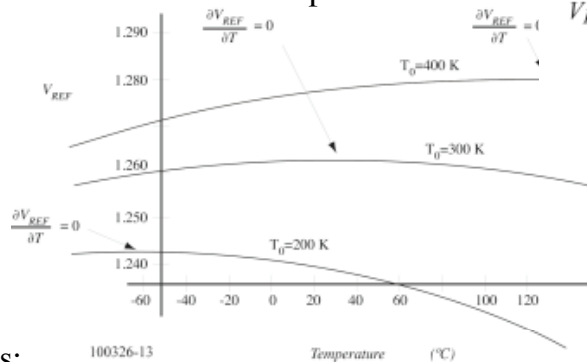
### Bandgap Curvature Problem

Unfortunately, the  $\frac{\gamma k T}{q} \ln\left(\frac{T_0}{T}\right)$  term of the  $pn$  junction contributed a nonlinearity to the CTAT realization. This is illustrated by the dashed lines in the plot shown.

The result is shown below where the reference voltage is not constant with temperature.




#### Comments:

- True temperature independence is only achieved over a small range of temperatures
- References that do not correct this problem have a temperature dependence of 10 ppm/°C to 50 ppm/°C over 0°C to 70°C.
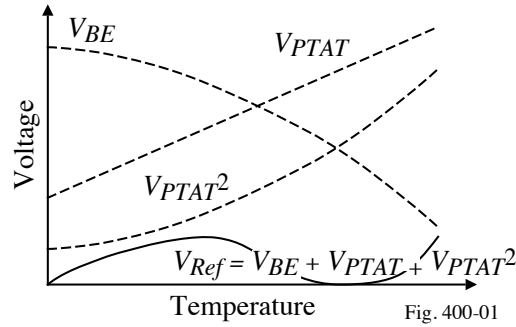
## Some Curvature Correction Techniques

- Squared PTAT Correction:  
Temperature coefficient  $\approx 1\text{-}20\text{ ppm}/^\circ\text{C}$



- $V_{BE}$  loop

M. Gunaway, *et. al.*, “A Curvature-Corrected Low-Voltage Bandgap Reference,” *IEEE Journal of Solid-State Circuits*, vol. 28, no. 6, pp. 667-670, June 1993.

- $\beta$  compensation


I. Lee *et. al.*, “Exponential Curvature-Compensated BiCMOS Bandgap References,” *IEEE Journal of Solid-State Circuits*, vol. 29, no. 11, pp. 1396-1403, Nov. 1994.

- Nonlinear cancellation

G.M. Meijer *et. al.*, “A New Curvature-Corrected Bandgap Reference,” *IEEE Journal of Solid-State Circuits*, vol. 17, no. 6, pp. 1139-1143, December 1982.

## $V_{BE}$ Loop Curvature Correction Technique

Circuit:

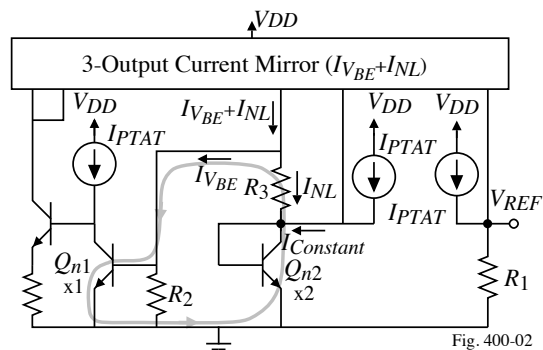

Operation:

$$I_{NL} = \frac{V_{BE1} - V_{BE2}}{R_3} = \frac{V_t}{R_3} \ln \left( \frac{I_{C1} A_2}{A_1 I_{C2}} \right)$$

$$= \frac{V_t}{R_3} \ln \left( \frac{2 I_{PTAT}}{I_{NL} + I_{Constant}} \right)$$

where

$$I_{constant} = I_{NL} + I_{PTAT} + I_{VBE}$$

$$\approx I_{NL} + \frac{V_t}{R_x} + \frac{V_{BE}}{R_2}$$

(a quasi-temperature independent current subject to the  $TC_F$  of the resistors)

where

$$V_t = kT/q$$

$I_{C1}$  and  $I_{C2}$  are the collector currents of  $Q_{n1}$  and  $Q_{n2}$ , respectively

$R_x$  is a resistor used to define  $I_{PTAT}$

$$\therefore V_{REF} = \left[ \frac{V_{BE}}{R_2} + \frac{V_t}{R_3} \ln \left( \frac{2 I_{PTAT}}{I_{NL} + I_{constant}} \right) + I_{PTAT} \right] R_1$$

Temperature coefficient  $\approx 3\text{ ppm}/^\circ\text{C}$  with a total quiescent current of  $95\mu\text{A}$ .

### $\beta$ Compensation Curvature Correction Technique

Circuit:

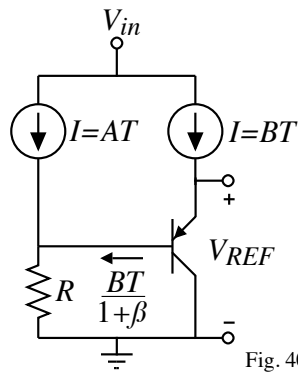


Fig. 400-0

Operation:

$$V_{REF} = V_{BE} + \left( AT + \frac{BT}{(1+\beta)} \right) R \approx V_{BE} + \left( AT + \frac{BT}{\beta} \right) R$$

where

$A$  and  $B$  are constant

$T$  = temperature

The temperature dependence of  $\beta$  is

$$\beta(T) \propto e^{-1/T} \Rightarrow \beta(T) = Ce^{-1/T}$$

$$\therefore V_{REF} = V_{BE}(T) + \left( AT + \frac{BTe^{1/T}}{C} \right)$$

Not good for small values of  $V_{in}$ .

$$V_{in} \geq V_{REF} + V_{sat.} = V_{GO} + V_{sat.} = 1.4V$$

### Series Temperature Independent Voltage Reference with Curvature Correction

Objective: Eliminate nonlinear term from  $V_{CTAT}$ .

Result: 0.5 ppm/°C from -25°C to 85°C.

Operation:

$$V_{REF} = V_{PTAT} + 3V_{CTAT} - 2V_{Constant}$$

Note that,  $I_{PTAT} \Rightarrow I_c \propto T^1 \Rightarrow \alpha = 1$

and  $I_{Constant} \Rightarrow I_c \propto T^0 \Rightarrow \alpha = 0$ ,

Previously we found,

$$V_{CTAT}(T) \approx V_{GO} - \frac{T}{T_0} [V_{GO} - V_{CTAT}(T_0)] - (\gamma - \alpha) V_t \ln\left(\frac{T}{T_0}\right)$$

so that

$$V_{CTAT}(I_{PTAT}) = V_{GO} - \frac{T}{T_0} [V_{GO} - V_{BE}(T_0)] - (\gamma - 1) V_t \ln\left(\frac{T}{T_0}\right)$$


and

$$V_{CTAT}(I_{Constant}) = V_{GO} - \frac{T}{T_0} [V_{GO} - V_{CTAT}(T_0)] - \gamma V_t \ln\left(\frac{T}{T_0}\right)$$

Combining the above relationships gives,


$$V_{REF}(T) = V_{PTAT} + V_{GO} - \frac{T}{T_0} [V_{GO} - V_{CTAT}(T_0)] - [\gamma - 3] V_t \ln\left(\frac{T}{T_0}\right)$$

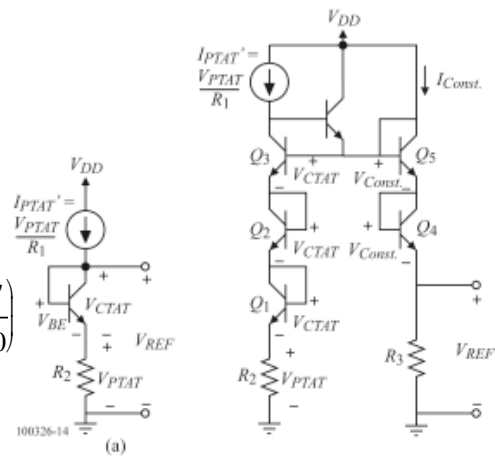If  $\gamma \approx 3$ , then  $V_{REF}(T) \approx V_{PTAT} + V_{GO}(1 - (T/T_0)) + V_{CTAT}(T_0)(T/T_0)$


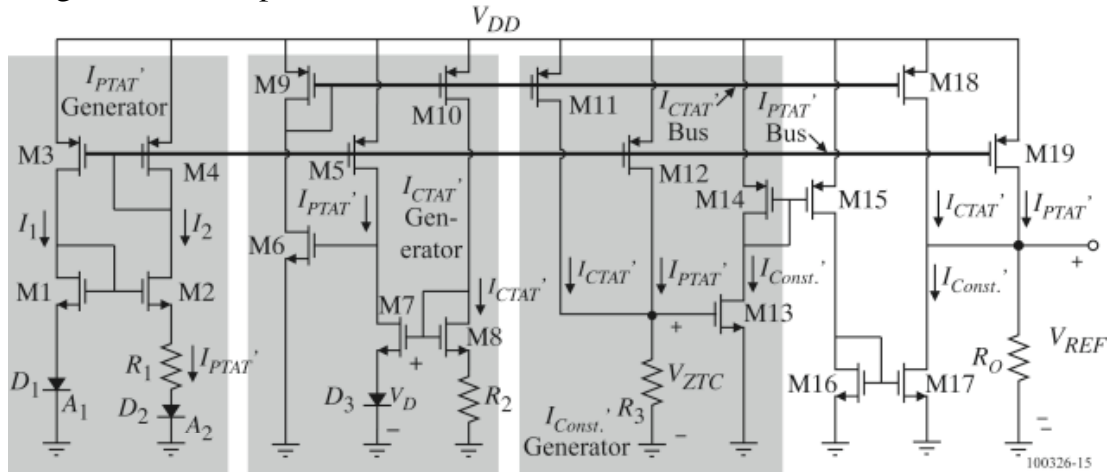
### A Parallel Version of the Nonlinear Curvature Correction Technique

The last idea was good in concept but not appropriate for CMOS implementation. The following is a better implementation.



$$V_{REF} = R_0[I_{PTAT}' + I_{CTAT}' - I_{const.}] = \frac{R_0}{R_1} V_{PTAT} + \frac{R_0}{R_2} V_{CTAT} - \frac{R_0}{R_3} V_{const.}$$

Use the resistor ratios to eliminate the nonlinear term given  $\gamma$  and  $\alpha$ .

### Parallel Curvature Correction Reference - Continued

Substitute for  $V_{CTAT}$  and  $V_{const.}$  in the expression for  $V_{REF}$ .

$$V_{REF} = \frac{R_0}{R_1} V_{PTAT} + \frac{R_0}{R_2} \left[ V_{GO} - \frac{T}{T_0} [V_{GO} - V_{CTAT}(T_0)] - (\gamma - 1) V_t \ln\left(\frac{T}{T_0}\right) \right] - \frac{R_0}{R_3} \left[ V_{GO} - \frac{T}{T_0} [V_{GO} - V_{CTAT}(T_0)] - \gamma V_t \ln\left(\frac{T}{T_0}\right) \right]$$

To cancel the nonlinear CTAT term, we want the following relationship to hold:

$$\frac{R_0}{R_2} (\gamma - 1) = \frac{R_0}{R_3} \gamma \quad \Rightarrow \quad \frac{R_2}{R_3} = \frac{(\gamma - 1)}{\gamma} \quad (\text{Fortunately } \gamma \text{ is always greater than } 1)$$

With these constraints, we find the voltage reference to be,

$$\begin{aligned} V_{REF} &= \frac{R_0}{R_1} V_{PTAT} + \left( \frac{R_0}{R_2} - \frac{R_0}{R_3} \right) \left[ V_{GO} - \frac{T}{T_0} [V_{GO} - V_{CTAT}(T_0)] \right] \\ &= \frac{R_0}{R_1} V_{PTAT} + \frac{1}{\gamma} \frac{R_0}{R_2} \left[ V_{GO} - \frac{T}{T_0} [V_{GO} - V_{CTAT}(T_0)] \right] \\ &= \frac{R_0}{\gamma R_2} \left\{ \frac{\gamma R_2}{R_1} V_{PTAT} + \left[ V_{GO} - \frac{T}{T_0} [V_{GO} - V_{CTAT}(T_0)] \right] \right\} = \frac{R_0}{\gamma R_2} \left[ \frac{\gamma R_2}{R_1} V_{PTAT} + V_{CTAT}(T_0) \right], (T = T_0) \end{aligned}$$

Design  $\gamma R_2/R_1$  to achieve temperature independence and  $R_0/R_2$  to get  $V_{REF}$ .

### Example 170-3 – Design of a Zero Temperature Coefficient Voltage Reference

Assume that  $V_{CTAT} = 0.7 \text{ V}$ ,  $R_3 = 10\text{k}\Omega$ ,  $\gamma = 3.2$ ,  $A_2 = 10A_1$ , and  $V_t = 0.026 \text{ V}$  at room temperature for the parallel curvature correction circuit. Find  $R_2$  and  $R_3$  to give a zero temperature coefficient at room temperature and a reference voltage of  $1.0\text{V}$ .

To eliminate the nonlinear CTAT term,

$$\frac{R_2}{R_3} = \frac{(\gamma-1)}{\gamma} = \frac{(2.2)}{3.2} = 0.6875 \quad \Rightarrow \quad R_2 = 6.88\text{k}\Omega$$

To cancel the temperature dependence,

$$\text{Temp. independent constant} = K = \frac{\gamma R_2}{R_1} = \frac{V_{GO} - V_{CTAT} + (\gamma - \alpha)V_{t0}}{V_{PTAT}}$$

or

$$\frac{\gamma R_2}{R_1} = \frac{V_{GO} - V_{CTAT} + (\gamma - \alpha)V_{t0}}{V_{PTAT}} = \frac{(1.205 - 0.7 + (3.2-1)(0.026)}{(0.026)(2.3026)} = 9.3907 \Rightarrow R_1 = 2.34\text{k}\Omega$$

The reference voltage can be written as,

$$V_{REF} = \frac{R_0}{\gamma R_2} \left[ \frac{\gamma R_2}{R_1} V_{PTAT} + V_{CTAT}(T_0) \right] = \frac{R_0}{\gamma R_2} [9.3907(0.026)(2.3026) + 0.7]$$

$$\frac{R_0}{R_2} = \frac{(3.2)}{1.262} = 2.535 \quad \Rightarrow \quad R_0 = 2.535R_2 = 17.44\text{k}\Omega$$

### Other Characteristics of Bandgap Voltage References

#### Noise

Voltage references for high-resolution ADCs are particularly sensitive to noise.

Noise sources: Op amp, resistors, switches, etc.

#### PSRR

Maximize the PSRR of the op amp.

#### Offset Voltages

Becomes a problem when op amps are used.

$$V_{BE2} = V_{BE1} + V_{R1} + V_{OS}$$

$$\Delta V_{BE} = V_{BE2} - V_{BE1} = V_{R1} + V_{OS} = V_t \ln \left( \frac{i_{C2} A_{E1}}{i_{C1} A_{E2}} \right)$$

Since  $i_{C2} R_3 = i_{C1} R_2 - V_{OS}$

$$\text{then } \frac{i_{C2}}{i_{C1}} = \frac{R_2}{R_3} - \frac{V_{OS}}{i_{C1} R_3} = \frac{R_2}{R_3} \left( 1 + \frac{V_{OS}}{i_{C1} R_2} \right)$$

Therefore,

$$V_{R1} = -V_{OS} + V_t \ln \left[ \frac{R_2 A_{E1}}{R_3 A_{E2}} \left( 1 + \frac{V_{OS}}{i_{C1} R_2} \right) \right]$$

$$V_{REF} = V_{BE2} - V_{OS} + i_{C1} R_2 = V_{BE2} - V_{OS} + \left( \frac{V_{R1}}{R_1} \right) R_2 = V_{BE2} - V_{OS} + \left( \frac{R_2}{R_1} \right)$$

$$\therefore \quad V_{REF} = V_{BE2} - V_{OS} \left( 1 + \frac{R_2}{R_1} \right) + \frac{R_2}{R_1} V_t \ln \left[ \frac{R_2 A_{E1}}{R_3 A_{E2}} \left( 1 + \frac{V_{OS}}{i_{C1} R_2} \right) \right]$$

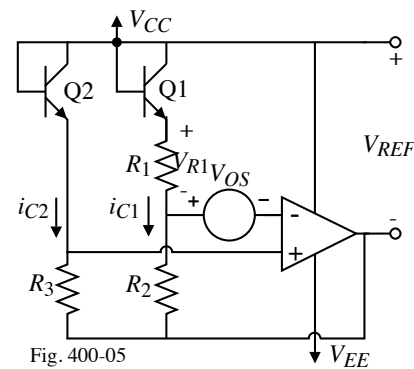


Fig. 400-05

## Noise Analysis of a Bandgap Reference

Consider the simple classical BG reference shown ( $R_2 = 10 R_1 = 10k\Omega$ ):

The open-circuit output noise voltage squared is found as,

$$e_{no}^2 = [e_{n1}^2/R_1^2 + e_{n2}^2/R_1^2 + g_{m5}^2 e_{n3}^2 + g_{m5}^2 e_{n4}^2 + g_{m5}^2 e_{n5}^2 + i_{nd1}^2/(g_{m1}^2 R_1^2) + i_{nd2}^2 + i_{nd3}^2 + i_{nr1}^2 + i_{nr2}^2] R_2^2$$

Assuming the MOSFETs are matched and the dc currents in  $D_1$ ,  $D_2$ , and  $D_3$  are equal gives,


$$e_{no}^2 \approx [g_{m5}^2(e_{n3}^2 + e_{n4}^2 + e_{n5}^2) + i_{nd2}^2 + i_{nd3}^2 + i_{nr1}^2 + i_{nr2}^2] R_2^2$$

Thermal noise gives ( $g_{m5} = 400\mu S$ ),

$$e_{no}^2 = 8kTg_{m5}^2 R_2^2 + 4qI_1 + \left(\frac{4kT}{R_1} + \frac{4kT}{R_2}\right) R_2^2 \approx 5.3 \times 10^{-19} + 6.4 \times 10^{-23} + 1.7 \times 10^{-15} (\text{V}^2/\text{Hz})$$

1/f noise gives,

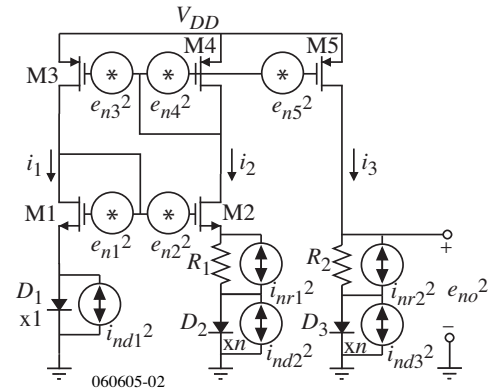
$$e_{no}^2 = 3g_{m5}^2 \frac{KF}{2fC_{ox}WLK'}$$



## DESIGN OF BIAS VOLTAGES FOR A CHIP
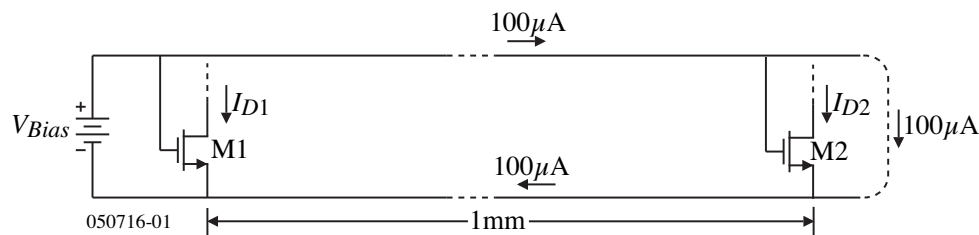
### Distributing Bias Voltages over a Distance

The major problem is the  $IR$  drops in busses. For example,




If the bus metal is  $50\text{m}\Omega/\text{sq.}$  and is  $5\mu\text{m}$  wide, the resistance of the bus in one direction is  $(50\text{m}\Omega/\text{sq.}) \times (1000\mu\text{m}/5\mu\text{m}) = 10\Omega$ . The difference in drain currents for an overdrive of  $0.1\text{V}$  is,

$$V_{GS1} = 1\text{mV} + V_{GS2} + 1\text{mV} = V_{GS2} + 2\text{mV}$$

$$\frac{I_{D1}}{I_{D2}} = \frac{(V_{GS1} - V_{TN})^2}{(V_{GS2} - V_{TN})^2} = \frac{(V_{GS2} - V_{TN} + 2\text{mV})^2}{(V_{GS2} - V_{TN})^2} = \left(\frac{0.1 + 0.002}{0.1}\right)^2 = 1.04$$


## Use Current to Avoid $IR$ Drops in Long Metal Lines

Example:

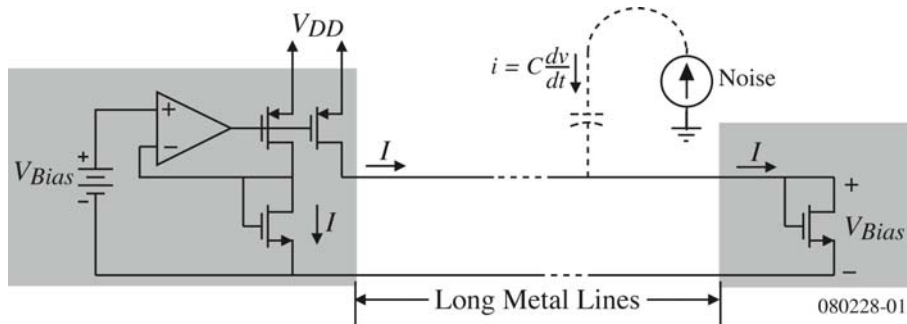
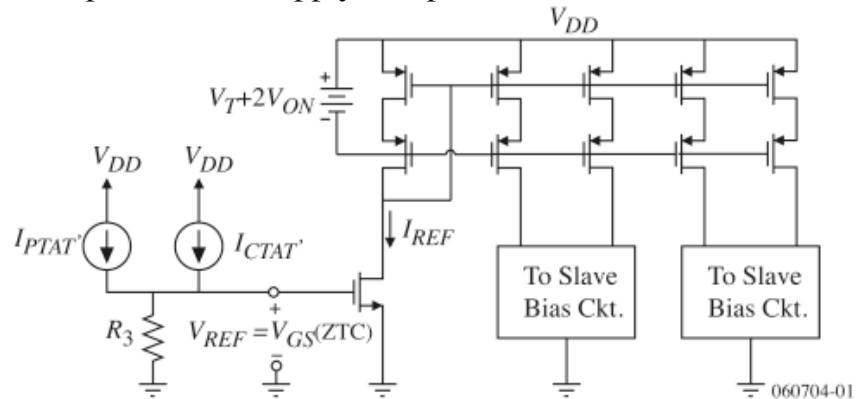
## Practical Aspects of Temperature-Independent and Supply-Independent Biasing

A temperature-independent and supply-independent current source and its distribution:




The currents are used to distribute the bias voltages to remote sections of the chip.

## Practical Aspects of Bias Distribution Circuits - Continued

Distribution of the current avoids change in bias voltage due to  $IR$  drop in bias lines.

Slave bias circuit:

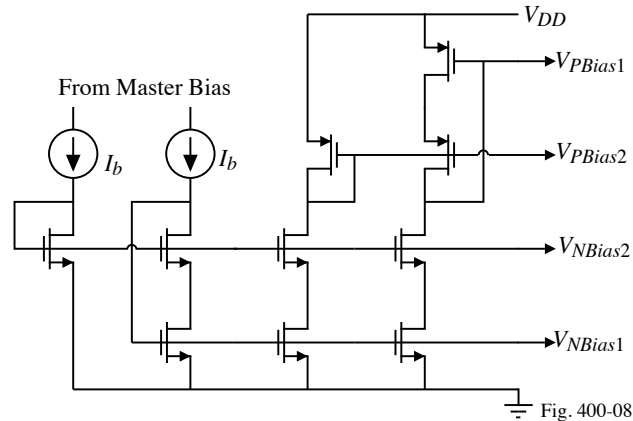

From here on out in these notes,

$$V_{PBias1} = V_{PB1} = V_{DD} - |V_{TP}| - V_{SD}(sat) \quad V_{PBias2} = V_{PB2} = V_{DD} - |V_{TP}| - 2V_{SD}(sat)$$

and

$$V_{NBias1} = V_{NB1} = V_{TN} + V_{DS}(sat) \quad V_{NBias2} = V_{NB2} = V_{TN} + 2V_{DS}(sat)$$

## SUMMARY OF TEMPERATURE STABLE REFERENCES

- The classical form of the temperature stable reference has a value of voltage close to the bandgap voltage and is called the “bandgap voltage reference”.
- Bandgap voltage references can achieve temperature dependence less than 50 ppm/°C
- Correction of second-order effects in the bandgap voltage reference can achieve very stable (1 ppm/°C) voltage references.
- Watch out for second-order effects such as noise when using the bandgap voltage reference in sensitive applications.
- Distribution of bias voltages over a long distance should be done by current rather than voltage.