

# Lecture 11: Cascode and Buffered Operational Amplifiers

November 27, 2007

# Cascode Op Amps


## Why Cascode Op Amps?

- Control of the frequency behavior
- Can get more gain by increasing the output resistance of a stage
- In the past section,  $PSRR$  of the two-stage op amp was insufficient for many applications
- A two-stage op amp can become unstable for large load capacitors (if nulling resistor is not used)
- The cascode op amp leads to wider  $ICMR$  and/or smaller power supply requirements

## Where Should the Cascode Technique be Used?

- First stage -
  - Good noise performance
  - Requires level translation to second stage
  - Degrades the Miller compensation
- Second stage -
  - Self compensating
  - Increases the efficiency of the Miller compensation
  - Increases  $PSRR$

# Simple Single Stage Cascode Op Amp

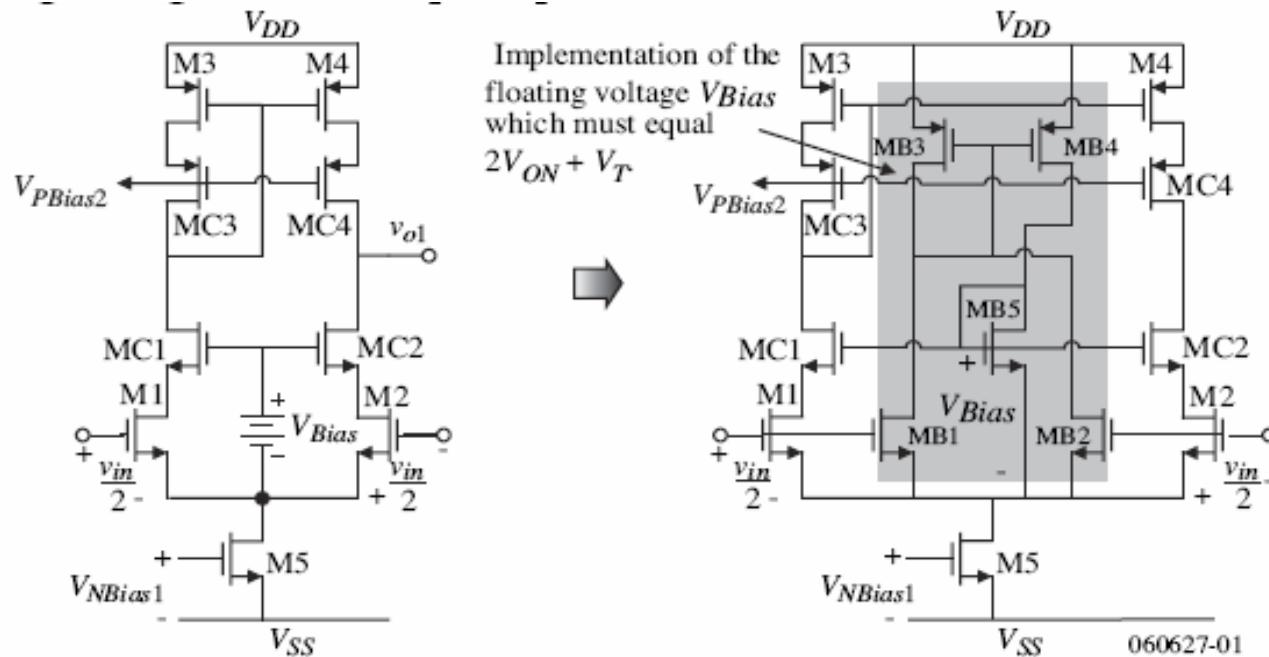

$R_{out}$  of the first stage is  $R_I \approx (g_{mC2}r_{dsC2}r_{ds2}) \parallel (g_{mC4}r_{dsC4}r_{ds4})$

Voltage gain =  $\frac{v_{o1}}{v_{in}} = g_{m1}R_I$  [The gain is increased by approximately  $0.5(g_{mC}r_{dsC})$ ]

As a single stage op amp, the compensation capacitor becomes the load capacitor.

# Example: Single-Stage, Cascode Op Amp Performance

Assume that all  $W/L$  ratios are  $10 \mu\text{m}/1 \mu\text{m}$ , and that  $I_{DS1} = I_{DS2} = 50 \mu\text{A}$  of single stage op amp. Find the voltage gain of this op amp and the value of  $C_I$  if  $GB = 10 \text{ MHz}$ . Use the model parameters of Table 3.1-2.

## Solution

The device transconductances are

$$g_{m1} = g_{m2} = g_{mI} = 331.7 \mu\text{S}$$

$$g_{mC2} = 331.7 \mu\text{S}$$

$$g_{mC4} = 223.6 \mu\text{S}.$$

The output resistance of the NMOS and PMOS devices is  $0.5 \text{ M}\Omega$  and  $0.4 \text{ M}\Omega$ , respectively.

$$\therefore R_I = 25 \text{ M}\Omega$$


$$A_v(0) = 8290 \text{ V/V}.$$

For a unity-gain bandwidth of  $10 \text{ MHz}$ , the value of  $C_I$  is  $5.28 \text{ pF}$ .


What happens if a  $100 \text{ pF}$  capacitor is attached to this op amp?

$GB$  goes from  $10 \text{ MHz}$  to  $0.53 \text{ MHz}$ .
 
# Two-Stage Op Amp with a Cascoded First-Stage



 - MT1 and MT2 are required for level shifting from the first-stage to the second.
- The  $PSRR^+$  is improved by the presence of MT1
- Internal loop pole at the gate of M6 may cause the Miller compensation to fail.
- The voltage gain of this op amp could easily be 100,000V/V



# Two-Stage Op Amp with a Cascode Second-Stage

$$A_v = g_{mI} g_{mII} R_I R_{II}$$

where  $g_{mI} = g_{m1} = g_{m2}$ ,  $g_{mII} = g_{m6}$ ,

$$R_I = \frac{1}{g_{ds2} + g_{ds4}} = \frac{2}{(\lambda_2 + \lambda_4) I_{D5}}$$

and

$$R_{II} = (g_{mC6} r_{dsC6} r_{ds6}) \parallel (g_{mC7} r_{dsC7} r_{ds7})$$


 


Fig. 6.5-3

Comments:

- The second-stage gain has greatly increased improving the Miller compensation
- The overall gain is approximately  $(g_m r_{ds})^3$  or very large
- Output pole,  $p_2$ , is approximately the same if  $C_c$  is constant
- The zero RHP is the same if  $C_c$  is constant
- PSRR is poor unless the Miller compensation is removed (then the op amp becomes self compensated)
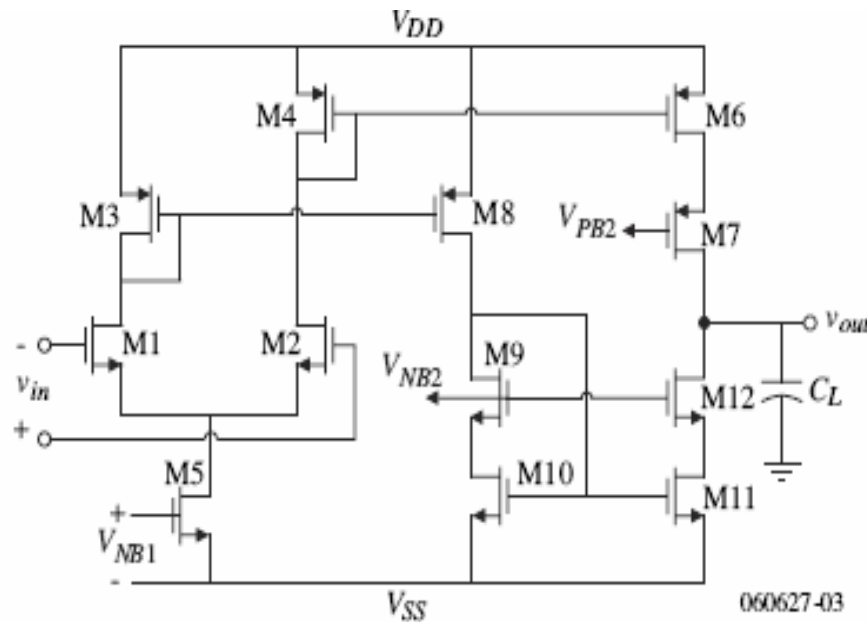
# A Balanced, Two-Stage Op Amp using a Cascode Output Stage



$$v_{out} = \left( \frac{g_{m1}g_{m8}}{g_{m3}} \frac{v_{in}}{2} + \frac{g_{m2}g_{m6}}{g_{m4}} \frac{v_{in}}{2} \right) R_{II}$$

$$= \left( \frac{g_{m1}}{2} + \frac{g_{m2}}{2} \right) k v_{in} R_{II} = g_{m1} \cdot k \cdot R_{II} v_{in}$$

where

$$R_{II} = (g_{m7}r_{ds7}r_{ds6}) \parallel (g_{m12}r_{ds12}r_{ds11})$$

and

$$k = \frac{g_{m8}}{g_{m3}} = \frac{g_{m6}}{g_{m4}}$$

This op amp is balanced because the drain-to-ground loads for M1 and M2 are identical.

# Design Relationships for Balanced, Cascode Output Stage Op Amp.

---

$$\text{Slew rate} = \frac{I_{\text{out}}}{C_L} \quad GB = \frac{g_{m1}g_{m8}}{g_{m3}C_L} \quad A_v = \frac{1}{2} \left( \frac{g_{m1}g_{m8}}{g_{m3}} + \frac{g_{m2}g_{m6}}{g_{m4}} \right) R_{II}$$
$$V_{in}(\text{max}) = V_{DD} - \left[ \frac{I_5}{\beta_3} \right]^{1/2} - |V_{TO3}|(\text{max}) + V_{T1}(\text{min}) \quad V_{in}(\text{min}) = V_{SS} + V_{DSS} + \left[ \frac{I_5}{\beta_1} \right]^{1/2} + V_{T1}(\text{min})$$

---

# Design of Balanced, Cascoded Output Stage Op Amp

The balanced, cascoded output stage op amp is a useful alternative to the two-stage op amp. Its design will be illustrated by this example. The pertinent design equations for the op amp were given above. The specifications of the design are as follows:

$$V_{DD} = -V_{SS} = 2.5 \text{ V} \quad \text{Slew rate} = 5 \text{ V}/\mu\text{s} \text{ with a } 50 \text{ pF load}$$

$$GB = 10 \text{ MHz with a } 25 \text{ pF load} \quad A_v \geq 5000$$

$$\text{Input CMR} = -1 \text{ V to } +1.5 \text{ V} \quad \text{Output swing} = \pm 1.5 \text{ V}$$

Use the parameters of Table 3.1-2 and let all device lengths be  $1 \mu\text{m}$ .

## Solution

While numerous approaches can be taken, we shall follow one based on the above specifications. The steps will be numbered to help illustrate the procedure.

1.) The first step will be to find the maximum source/sink current. This is found from the slew rate.

$$I_{\text{source}}/I_{\text{sink}} = C_L \times \text{slew rate} = 50 \text{ pF}(5 \text{ V}/\mu\text{s}) = 250 \mu\text{A}$$

2.) Next some  $W/L$  constraints based on the maximum output source/sink current are developed. Under dynamic conditions, all of  $I_5$  will flow in M4; thus we can write

$$\text{Max. } I_{\text{out}}(\text{source}) = (S_6/S_4)I_5 \quad \text{and} \quad \text{Max. } I_{\text{out}}(\text{sink}) = (S_8/S_3)I_5$$

The maximum output sinking current is equal to the maximum output sourcing current if

$$S_3 = S_4, \quad S_6 = S_8, \quad \text{and} \quad S_{10} = S_{11}$$

# Design of Balanced, Cascoded Output Stage Op Amp (cont)

3.) Choose  $I_5$  as  $100 \mu\text{A}$ . This current (which can be changed later) gives

$$S_6 = 2.5S_4 \text{ and } S_8 = 2.5S_3$$

Note that  $S_8$  could equal  $S_3$  if  $S_{11} = 2.5S_{10}$ . This would minimize the power dissipation.

4.) Next design for  $\pm 1.5 \text{ V}$  output capability. We shall assume that the output must source or sink the  $250 \mu\text{A}$  at the peak values of output. First consider the negative output peak. Since there is  $1 \text{ V}$  difference between  $V_{SS}$  and the minimum output, let  $V_{DS11}(\text{sat}) = V_{DS12}(\text{sat}) = 0.5 \text{ V}$  (we continue to ignore the bulk effects). Under the maximum negative peak assume that  $I_{11} = I_{12} = 250 \mu\text{A}$ . Therefore

$$0.5 = \sqrt{\frac{2I_{11}}{K'_N S_{11}}} = \sqrt{\frac{2I_{12}}{K'_N S_{12}}} = \sqrt{\frac{500 \mu\text{A}}{(110 \mu\text{A}/\text{V}^2)S_{11}}}$$

which gives  $S_{11} = S_{12} = 18.2$  and  $S_9 = S_{10} = 18.2$ . For the positive peak, we get

$$0.5 = \sqrt{\frac{2I_6}{K'_P S_6}} = \sqrt{\frac{2I_7}{K'_P S_7}} = \sqrt{\frac{500 \mu\text{A}}{(50 \mu\text{A}/\text{V}^2)S_6}}$$

which gives  $S_6 = S_7 = S_8 = 40$  and  $S_3 = S_4 = (40/2.5) = 16$ .

# Design of Balanced, Cascoded Output Stage Op Amp (cont)

5.) Now we must consider the possibility of conflict among the specifications.

First consider the input CMR.  $S_3$  has already been designed as 16. Using ICMR relationship, we find that  $S_3$  should be at least 4.1. A larger value of  $S_3$  will give a higher value of  $V_{in(max)}$  so that we continue to use  $S_3 = 16$  which gives  $V_{in(max)} = 1.95V$ .

Next, check to see if the larger W/L causes a pole below the gainbandwidth. Assuming a  $C_{ox}$  of  $0.4fF/\mu m^2$  gives the first-stage pole of

$$p_3 = \frac{-g_{m3}}{C_{gs3} + C_{gs8}} = \frac{-\sqrt{2K'_p S_3 I_3}}{(0.667)(W_3 L_3 + W_8 L_8) C_{ox}} = 33.15 \times 10^9 \text{ rads/sec or } 5.275 \text{ GHz}$$

which is much greater than  $10GB$ .

6.) Next we find  $g_{m1}$  ( $g_{m2}$ ). There are two ways of calculating  $g_{m1}$ .

(a.) The first is from the  $A_v$  specification. The gain is

$$A_v = (g_{m1}/2g_{m4})(g_{m6} + g_{m8}) R_{II}$$

Note, a current gain of  $k$  could be introduced by making  $S_6/S_4$  ( $S_8/S_3 = S_{11}/S_3$ ) equal to  $k$ .

$$\frac{g_{m6}}{g_{m4}} = \frac{g_{m11}}{g_{m3}} = \sqrt{\frac{2K'_p \cdot S_6 \cdot I_6}{2K'_p \cdot S_4 \cdot I_4}} = k$$

Calculating the various transconductances we get  $g_{m4} = 282.4 \mu S$ ,  $g_{m6} = g_{m7} = g_{m8} = 707 \mu S$ ,  $g_{m11} = g_{m12} = 707 \mu S$ ,  $r_{ds6} = r_{d7} = 0.16 M\Omega$ , and  $r_{ds11} = r_{ds12} = 0.2 M\Omega$ .

Assuming that the gain  $A_v$  must be greater than 5000 and  $k = 2.5$  gives  $g_{m1} > 72.43 \mu S$ .

# Design of Balanced, Cascoded Output Stage Op Amp (cont)

(b.) The second method of finding  $g_{m1}$  is from the  $GB$  specifications. Multiplying the gain by the dominant pole ( $1/C_{II}R_{II}$ ) gives

$$GB = \frac{g_{m1}(g_{m6} + g_{m8})}{2g_{m4}C_L}$$

Assuming that  $C_L = 25$  pF and using the specified  $GB$  gives  $g_{m1} = 251 \mu S$ .

Since this is greater than  $72.43 \mu S$ , we choose  $g_{m1} = g_{m2} = 251 \mu S$ . Knowing  $I_5$  gives  $S_1 = S_2 = 5.7 \approx 6$ .

8.) The next step is to check that  $S_1$  and  $S_2$  are large enough to meet the  $-1V$  input CMR specification. Use the saturation formula we find that  $V_{DS5}$  is  $0.261$  V. This gives  $S_5 = 26.7 \approx 27$ . The gain becomes  $A_v = 6,925V/V$  and  $GB = 10$  MHz for a  $25$  pF load. We shall assume that exceeding the specifications in this area is not detrimental to the performance of the op amp.

9.) Knowing the currents and  $W/L$  values, the bias voltages  $V_{NB1}$ ,  $V_{NB2}$  and  $V_{PB2}$  can be designed.

The  $W/L$  values resulting from this design procedure are shown below. The power dissipation for this design is seen to be  $2$  mW. The next step would be simulation.

$$\begin{array}{lll} S_1 = S_2 = 6 & S_3 = S_4 = 16 & S_5 = 27 \\ S_6 = S_7 = S_8 = 40 & S_9 = S_{10} = S_{11} = S_{12} = 18.2 & \end{array}$$

# Technological Implications of the Cascode Configuration

 


Fig. 6.5-5

If a double poly CMOS process is available, internode parasitics can be minimized. As an alternative, one should keep the drain/source between the transistors to a minimum area.


 


Fig. 6.5-5A

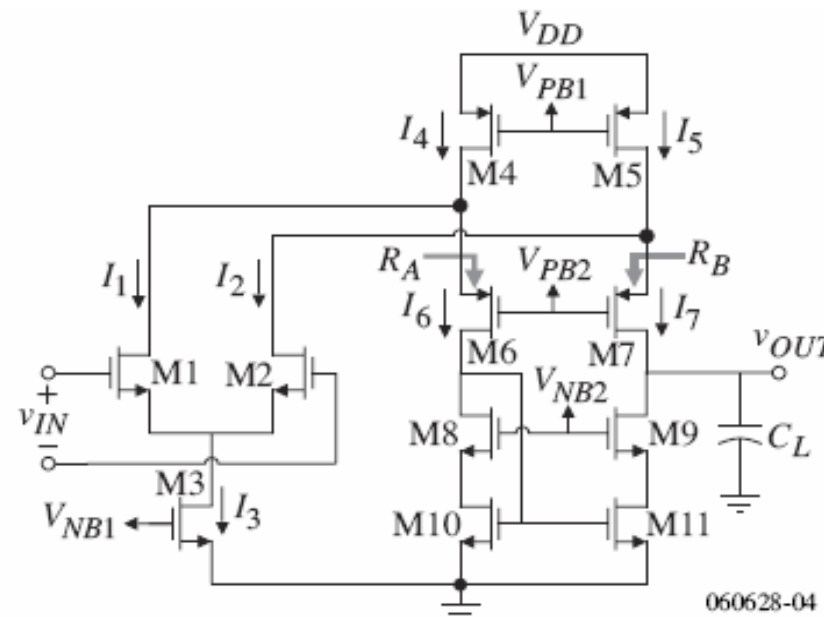

# The Folded Cascode Op Amp




Comments:

- $I_4$  and  $I_5$ , should be designed so that  $I_6$  and  $I_7$  never become zero (i.e.  $I_4=I_5=1.5I_3$ )
- This amplifier is nearly balanced (would be exactly if  $R_A$  was equal to  $R_B$ )
- Self compensating
- Poor noise performance, the gain occurs at the output so all intermediate transistors contribute to the noise along with the input transistors. (Some first stage gain can be achieved if  $R_A$  and  $R_B$  are greater than  $g_{m1}$  or  $g_{m2}$ .)
 
# Small-Signal Analysis of the Folded Cascode Op Amp

Model:

Recalling what we learned about the resistance looking into the source of the cascode transistor;



$$R_A = \frac{r_{ds6} + (1/g_{m10})}{1 + g_{m6}r_{ds6}} \approx \frac{1}{g_{m6}} \quad \text{and} \quad R_B = \frac{r_{ds7} + R_{II}}{1 + g_{m7}r_{ds7}} \approx \frac{R_{II}}{g_{m7}r_{ds7}} \quad \text{where} \quad R_{II} \approx g_{m9}r_{ds9}r_{ds11}$$

The small-signal voltage transfer function can be found as follows. The current  $i_{10}$  is written as

$$i_{10} = \frac{-g_{m1}(r_{ds1} || r_{ds4})v_{in}}{2[R_A + (r_{ds1} || r_{ds4})]} \approx \frac{-g_{m1}v_{in}}{2}$$

and the current  $i_7$  can be expressed as

$$i_7 = \frac{g_{m2}(r_{ds2} || r_{ds5})v_{in}}{2\left[\frac{R_{II}}{g_{m7}r_{ds7}} + (r_{ds2} || r_{ds5})\right]} = \frac{g_{m2}v_{in}}{2\left(1 + \frac{R_{II}(g_{ds2} + g_{ds5})}{g_{m7}r_{ds7}}\right)} = \frac{g_{m2}v_{in}}{2(1+k)} \quad \text{where} \quad k = \frac{R_{II}(g_{ds2} + g_{ds5})}{g_{m7}r_{ds7}}$$

The output voltage,  $v_{out}$ , is equal to the sum of  $i_7$  and  $i_{10}$  flowing through  $R_{out}$ . Thus,

$$\frac{v_{out}}{v_{in}} = \left(\frac{g_{m1}}{2} + \frac{g_{m2}}{2(1+k)}\right)R_{out} = \left(\frac{2+k}{2+2k}\right)g_{m1}R_{out}$$

# Frequency Response of the Folded Cascode Op Amp

The frequency response of the folded cascode op amp is determined primarily by the output pole which is given as

$$p_{out} = \frac{-1}{R_{out}C_{out}}$$

where  $C_{out}$  is all the capacitance connected from the output of the op amp to ground.

All other poles must be greater than  $GB = g_{m1}/C_{out}$ . The approximate expressions for each pole is

- 1.) Pole at node A:  $p_A \approx -g_{m6}/C_A$
- 2.) Pole at node B:  $p_B \approx -g_{m7}/C_B$
- 3.) Pole at drain of M6:  $p_6 \approx -g_{m10}/C_6$
- 4.) Pole at source of M8:  $p_8 \approx -(g_{m8}r_{ds8}g_{m10})/C_8$
- 5.) Pole at source of M9:  $p_9 \approx -g_{m9}/C_9$

where the approximate expressions are found by the reciprocal product of the resistance and parasitic capacitance seen to ground from a given node. One might feel that because  $R_B$  is approximately  $r_{ds}$  that this pole might be too small. However, at frequencies where this pole has influence,  $C_{out}$ , causes  $R_{out}$  to be much smaller making  $p_B$  also non-dominant.

# Example: Folded Cascode, CMOS Op Amp

Assume that all  $g_{mN} = g_{mP} = 100\mu\text{S}$ ,  $r_{dsN} = 2\text{M}\Omega$ ,  $r_{dsP} = 1\text{M}\Omega$ , and  $C_L = 10\text{pF}$ . Find all of the small-signal performance values for the folded-cascode op amp.

$$R_{II} = 0.4\text{G}\Omega, R_A = 10\text{k}\Omega, \text{ and } R_B = 4\text{M}\Omega \quad \therefore k = \frac{0.4 \times 10^9 (0.3 \times 10^{-6})}{100} = 1.2$$

$$\frac{v_{out}}{v_{in}} = \left( \frac{2+1.2}{2+2.4} \right) (100)(57.143) = 4,156\text{V/V}$$

$$R_{out} = R_{II} \parallel [g_{m7} r_{ds7} (r_{ds5} \parallel r_{ds2})] = 400\text{M}\Omega \parallel [(100)(0.667\text{M}\Omega)] = 57.143\text{M}\Omega$$

$$|p_{out}| = \frac{1}{R_{out} C_{out}} = \frac{1}{57.143\text{M}\Omega \cdot 10\text{pF}} = 1,750 \text{ rads/sec.} \Rightarrow 278\text{Hz} \Rightarrow GB = 1.21\text{MHz}$$

# PSRR of the Folded Cascode Op Amp

Consider the following circuit used to model the  $PSRR^-$ :

 


Fig. 6.5-9A

This model assumes that gate, source and drain of M11 and the gate and source of M9 all vary with  $V_{SS}$ .

We shall examine  $V_{out}/V_{SS}$  rather than  $PSRR^-$ . (Small  $V_{out}/V_{SS}$  will lead to large  $PSRR^-$ .)

The transfer function of  $V_{out}/V_{SS}$  can be found as

$$\frac{V_{out}}{V_{SS}} \approx \frac{sC_{gd9}R_{out}}{sC_{out}R_{out}+1} \quad \text{for } C_{gd9} < C_{out}$$

The approximate  $PSRR^-$  is sketched on the next page.

# Frequency Response of the PSRR- of the Folded Cascode Op Amp

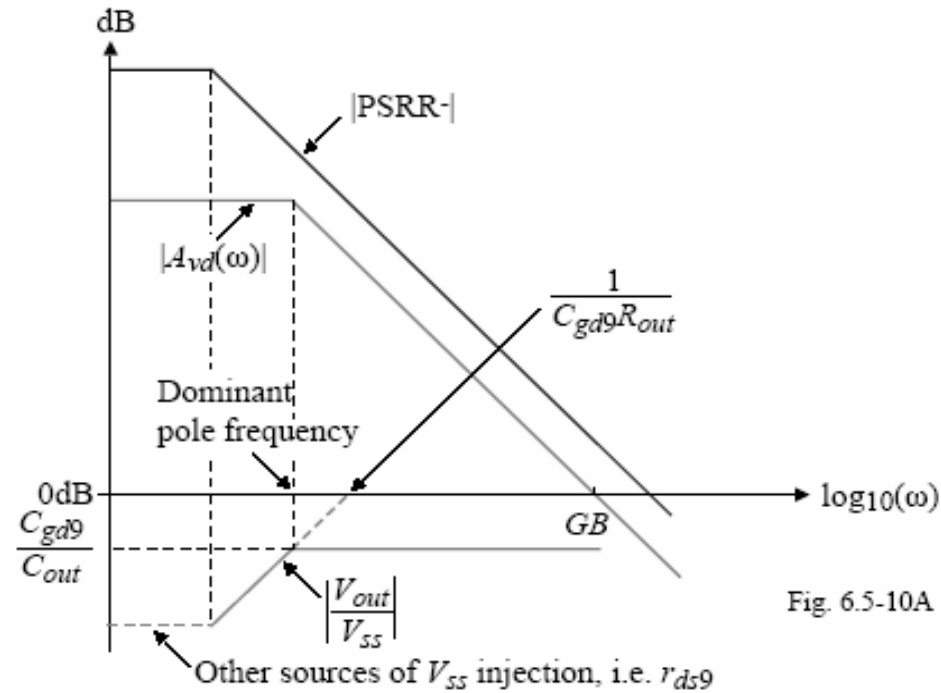


Fig. 6.5-10A

We see that the PSRR of the cascode op amp is much better than the two-stage op amp.

# Design Approach for the Folded-Cascode Op Amp

Step	Relationship	Design Equation/Constraint	Comments
1	Slew Rate	$I_3 = SR \cdot C_L$	
2	Bias currents in output cascodes	$I_4 = I_5 = 1.2I_3$ to $1.5I_3$	Avoid zero current in cascodes
3	Maximum output voltage, $v_{out(max)}$	$S_5 = \frac{2I_5}{K_P \cdot V_{SD5}^2}$ , $S_7 = \frac{2I_7}{K_P \cdot V_{SD7}^2}$ , ( $S_4 = S_5$ and $S_6 = S_7$ )	$V_{SD5(sat)} = V_{SD7(sat)} = 0.5[V_{DD} - v_{out(max)}]$
4	Minimum output voltage, $v_{out(min)}$	$S_{11} = \frac{2I_{11}}{K_N \cdot V_{DS11}^2}$ , $S_9 = \frac{2I_9}{K_N \cdot V_{DS9}^2}$ , ( $S_{10} = S_{11}$ and $S_8 = S_9$ )	$V_{DS9(sat)} = V_{DS11(sat)} = 0.5[v_{out(min)} - V_{SS}]$
5	$GB = \frac{g_{m1}}{C_L}$	$S_1 = S_2 = \frac{g_{m1}^2}{K_N \cdot I_3} = \frac{GB^2 \cdot C_L^2}{K_N \cdot I_3}$	
6	Minimum input CM	$S_3 = \frac{2I_3}{K_N \cdot (V_{in(min)} - V_{SS} - \sqrt{(I_3/K_N \cdot S_1)} - V_{T1})^2}$	
7	Maximum input CM	$S_4 = S_5 = \frac{2I_4}{K_P \cdot (V_{DD} - V_{in(max)} + V_{T1})^2}$	$S_4$ and $S_5$ must meet or exceed value in step 3
8	Differential Voltage Gain	$\frac{v_{out}}{v_{in}} = \left( \frac{g_{m1}}{2} + \frac{g_{m2}}{2(1+k)} \right) R_{out} = \left( \frac{2+k}{2+2k} \right) g_{m1} R_{out}$	$k = \frac{R_{II}(g_{ds2} + g_{ds4})}{g_{m7} r_{ds7}}$
9	Power dissipation	$P_{diss} = (V_{DD} - V_{SS})(I_3 + I_{10} + I_{11})$	

# Example: Design of a Folded-Cascode Op Amp

Follow the procedure given to design the folded-cascode op amp when the slew rate is  $10\text{V}/\mu\text{s}$ , the load capacitor is  $10\text{pF}$ , the maximum and minimum output voltages are  $\pm 2\text{V}$  for  $\pm 2.5\text{V}$  power supplies, the  $GB$  is  $10\text{MHz}$ , the minimum input common mode voltage is  $-1.5\text{V}$  and the maximum input common mode voltage is  $2.5\text{V}$ . The differential voltage gain should be greater than  $5,000\text{V}/\text{V}$  and the power dissipation should be less than  $5\text{mW}$ . Use channel lengths of  $1\mu\text{m}$ .

## Solution

Following the approach outlined above we obtain the following results.

$$I_3 = SR \cdot C_L = 10 \times 10^6 \cdot 10^{-11} = 100\mu\text{A}$$

Select  $I_4 = I_5 = 125\mu\text{A}$ .

Next, we see that the value of  $0.5(V_{DD} - V_{out(\text{max})})$  is  $0.5\text{V}/2$  or  $0.25\text{V}$ . Thus,

$$S_4 = S_5 = \frac{2 \cdot 125\mu\text{A}}{50\mu\text{A}/\text{V}^2 \cdot (0.25\text{V})^2} = \frac{2 \cdot 125 \cdot 16}{50} = 80$$

and assuming worst case currents in M6 and M7 gives,

$$S_6 = S_7 = \frac{2 \cdot 125\mu\text{A}}{50\mu\text{A}/\text{V}^2 \cdot (0.25\text{V})^2} = \frac{2 \cdot 125 \cdot 16}{50} = 80$$

The value of  $0.5(V_{out(\text{min})} - |V_{SS}|)$  is also  $0.25\text{V}$  which gives the value of  $S_8, S_9, S_{10}$  and

$$S_{11} \text{ as } S_8 = S_9 = S_{10} = S_{11} = \frac{2 \cdot I_8}{K_N' V_{DS8}^2} = \frac{2 \cdot 125}{110 \cdot (0.25)^2} = 36.36$$

# Example: Design of a Folded-Cascode Op Amp (cont)

In step 5, the value of  $GB$  gives  $S_1$  and  $S_2$  as

$$S_1 = S_2 = \frac{GB^2 \cdot C_L^2}{K_N' I_3} = \frac{(20\pi \times 10^6)^2 (10^{-11})^2}{110 \times 10^{-6} \cdot 100 \times 10^{-6}} = 35.9$$

The minimum input common mode voltage defines  $S_3$  as

$$S_3 = \frac{2I_3}{K_N' \left( V_{in(\min)} - V_{SS} - \sqrt{\frac{I_3}{K_N' S_1}} - V_{T1} \right)^2} = \frac{200 \times 10^{-6}}{110 \times 10^{-6} \left( -1.5 + 2.5 - \sqrt{\frac{100}{110 \cdot 35.9}} - 0.7 \right)^2} = 91.6$$

We need to check that the values of  $S_4$  and  $S_5$  are large enough to satisfy the maximum input common mode voltage. The maximum input common mode voltage of 2.5 requires

$$S_4 = S_5 \geq \frac{2I_4}{K_P' [V_{DD} - V_{in(\max)} + V_{T1}]^2} = \frac{2 \cdot 125 \mu\text{A}}{50 \times 10^{-6} \mu\text{A/V}^2 [0.7\text{V}]^2} = 10.2$$

which is much less than 80. In fact, with  $S_4 = S_5 = 80$ , the maximum input common mode voltage is 3V.

The power dissipation is found to be

$$P_{diss} = 5\text{V}(125 \mu\text{A} + 125 \mu\text{A}) = 1.25\text{mW}$$

# Example: Design of a Folded-Cascode Op Amp (cont)

The small-signal voltage gain requires the following values to evaluate:

$$S_4, S_5: g_m = \sqrt{2 \cdot 125 \cdot 50 \cdot 80} = 1000 \mu\text{S} \quad \text{and} \quad g_{ds} = 125 \times 10^{-6} \cdot 0.05 = 6.25 \mu\text{S}$$

$$S_6, S_7: g_m = \sqrt{2 \cdot 75 \cdot 50 \cdot 80} = 774.6 \mu\text{S} \quad \text{and} \quad g_{ds} = 75 \times 10^{-6} \cdot 0.05 = 3.75 \mu\text{S}$$

$$S_8, S_9, S_{10}, S_{11}: g_m = \sqrt{2 \cdot 75 \cdot 110 \cdot 36.36} = 774.6 \mu\text{S} \quad \text{and} \quad g_{ds} = 75 \times 10^{-6} \cdot 0.04 = 3 \mu\text{S}$$

$$S_1, S_2: g_{mI} = \sqrt{2 \cdot 50 \cdot 110 \cdot 35.9} = 628 \mu\text{S} \quad \text{and} \quad g_{ds} = 50 \times 10^{-6} (0.04) = 2 \mu\text{S}$$

Thus,

$$R_{II} \approx g_{m9} r_{ds9} r_{ds11} = (774.6 \mu\text{S}) \left( \frac{1}{3 \mu\text{S}} \right) \left( \frac{1}{3 \mu\text{S}} \right) = 86.07 \text{M}\Omega$$

$$R_{out} \approx 86.07 \text{M}\Omega \parallel (774.6 \mu\text{S}) \left( \frac{1}{3.75 \mu\text{S}} \right) \left( \frac{1}{2 \mu\text{S} + 6.25 \mu\text{S}} \right) = 19.40 \text{M}\Omega$$

$$k = \frac{R_{II}(g_{ds2} + g_{ds4})}{g_{m7} r_{ds7}} = \frac{86.07 \text{M}\Omega (2 \mu\text{S} + 6.25 \mu\text{S}) (3.75 \mu\text{S})}{774.6 \mu\text{S}} = 3.4375$$

The small-signal, differential-input, voltage gain is

$$A_{vd} = \left( \frac{2+k}{2+2k} \right) g_{mI} R_{out} = \left( \frac{2+3.4375}{2+6.875} \right) 0.628 \times 10^{-3} \cdot 19.40 \times 10^6 = 7,464 \text{ V/V}$$


The gain is larger than required by the specifications which should be okay.

# Comments on Folded Cascode Op Amps

- Good PSRR
- Good ICMR
- Self compensated
- Can cascade an output stage to get extremely high gain with lower output resistance (use Miller compensation in this case)
- Need first stage gain for good noise performance
- Widely used in telecommunication circuits where large dynamic range is required
 
# Enhanced-Gain, Folded Cascode Op Amps

If more gain is needed, the folded cascode op amp can be enhanced to boost the output impedance even higher as follows.



Voltage gain =  $g_{m1}R_{out}$ ,

where

$$R_{out} \approx [A r_{ds7} g_{m7} (r_{ds1} \parallel r_{ds5})] \parallel (A r_{ds9} g_{m9} r_{ds11})$$

Since  $A \approx g_m r_{ds}$  the voltage gain would be in the range of 100,000 to 500,000.


Note that to achieve maximum output swing, it will be necessary to make sure that M5 and M11 are biased with  $V_{DS} = V_{DS}(\text{sat})$ .

# What are the Enhancement Amplifiers?

Requirements:

- 1.) Need a gain of  $g_m r_{ds}$ .
- 2.) Must be able to set the dc voltage at its input to get wide-output voltage swing.

Possible Enhancement Amplifiers:

 


# Frequency Response of the Enhanced Gain Cascode Op Amps

Normally, the frequency response of the cascode op amps would have one dominant pole at the output. The frequency response would be,

$$A_v(s) = g_{m1} \left( \frac{R_{out}(1/sC_{out})}{R_{out} + 1/sC_{out}} \right) = \frac{g_{m1}R_{out}}{sR_{out}C_{out} + 1} = \frac{g_{m1}R_{out}}{1 - \frac{s}{p_1}}$$

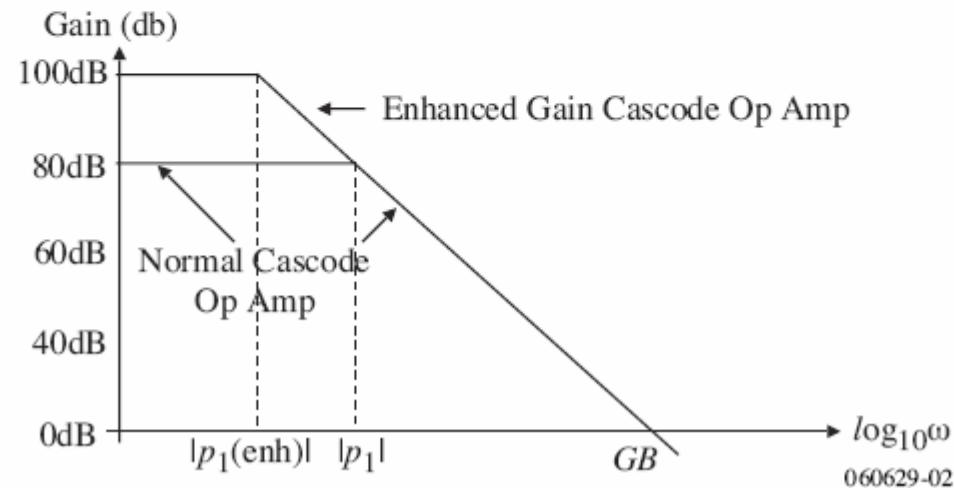If the amplifier used to boost the output resistance had no frequency dependence then the frequency response would be as follows.



# Frequency Response of the Enhanced Gain Cascode Op Amps (cont)

- Does the pole in the feedback amplifier  $A$  have an influence?

Although the output resistance can be modeled as,

$$R_{out}' \approx R_{out} A_o \left( \frac{1 - \frac{s}{p_2 A_o}}{1 - \frac{s}{p_2}} \right)$$

it has no influence on the frequency response because  $C_{out}$  has shorted out any influence a change in  $R_{out}$  might have.

- Higher order poles come from a diversion of the current flow in the op amp to ground rather than the intended destination of the current to the output. These poles that divert the current are:
  - Pole at the source of M6 ( $A g_{m6}/C_6$ )      - Pole at the source of M7 ( $A g_{m7}/C_7$ )
  - Pole at the drain of M8 ( $A g_{m10}/C_8$ )      - Pole at the source of M9 ( $A g_{m9}/C_6$ )
  - Pole at the drain of M10 ( $g_{m8} r_{ds8} g_{m10}/C_{10}$ )

Note that the enhancement amplifiers cause all higher-order poles to be moved out by  $|A|$ . Therefore, the  $GB$  of the enhanced gain cascode op amp should be able to be increased by  $|A|$ .

# Buffered Op Amps

# Buffered Op Amps

- Illustrate the method of lowering the output resistance of simple op amps
  - Open-loop MOSFET buffered op amps
  - Closed-loop MOSFET buffered op amps (shunt negative feedback)
  - BJT output op amps
- Show examples

# What is a Buffered Op Amp?

- A buffered op amp is an op amp with a low value of output resistance,  $R_o$ .

$$10\Omega \leq R_o \leq 1000\Omega$$

- The result is a voltage-controlled, voltage-source amplifier.
  - Requirements are generally the same as for the output amplifier:
    - Low output resistance
    - Large output signal swing
    - Low distortion
    - High efficiency

# The Source Follower as a Buffer

Class-A Follower:

- Simple, gain < 1
- Lower efficiency
- $R_{out} = \frac{1}{g_m + g_{mbs}} \approx 500$  to  $1000\Omega$
- Level shift from input to output

Push-Pull Follower:



- Voltage loss from 2 cascaded followers
- Higher efficiency
- Current in M1 and M2 determined by:

$$V_{GS4} + V_{SG3} = V_{GS1} + V_{SG2}$$


$$\sqrt{\frac{2I_6}{K_n'(W_4/L_4)}} + \sqrt{\frac{2I_5}{K_p'(W_3/L_3)}}$$

$$= \sqrt{\frac{2I_1}{K_n'(W_1/L_1)}} + \sqrt{\frac{2I_2}{K_p'(W_2/L_2)}}$$

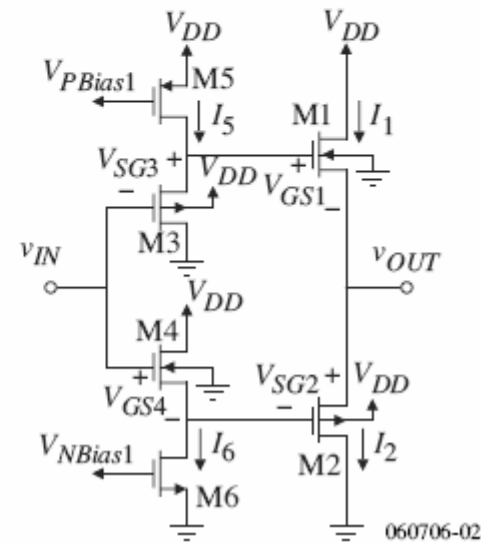 Use the  $W/L$  ratios to define  $I_1$  and  $I_2$  from  $I_5$  and  $I_6$



# Two-Stage Op Amp with Follower

 

Power dissipation now becomes  $(I_5 + I_7 + I_9)V_{DD}$

Gain becomes,

$$A_v = \left( \frac{g_{m1}}{g_{ds2} + g_{ds4}} \right) \left( \frac{g_{m6}}{g_{ds6} + g_{ds7}} \right) \left( \frac{g_{m8}}{g_{m8} + g_{mbs8} + g_{ds8} + g_{ds9}} \right)$$

# Source-Follower, Push-Pull Output Op Amp

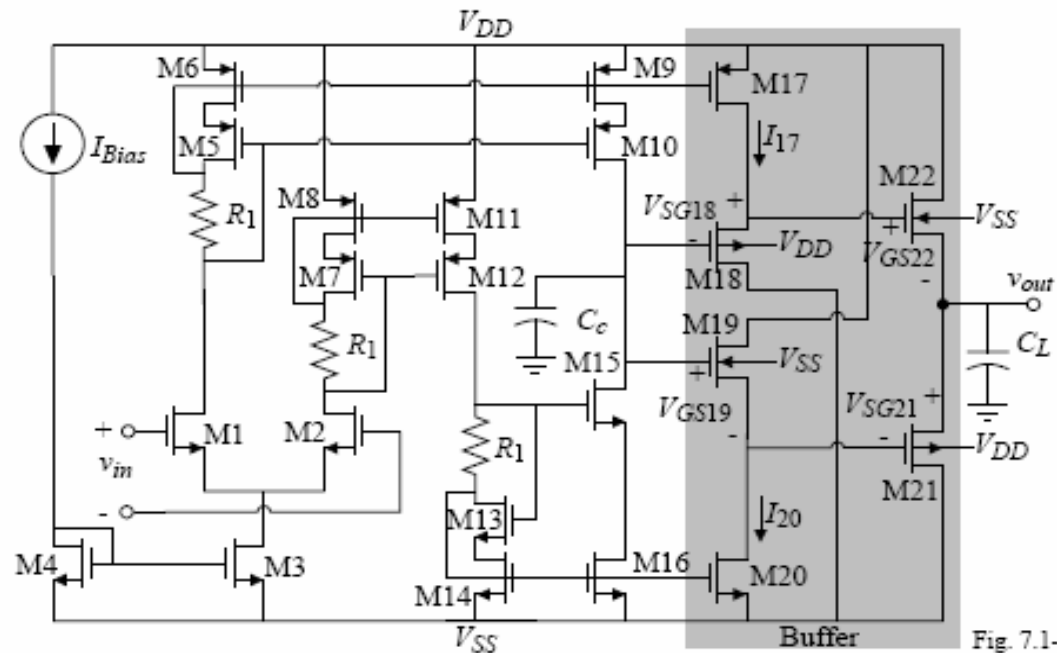


Fig. 7.1-1

$$R_{out} \approx \frac{1}{g_{m21} + g_{m22}} \leq 1000\Omega, A_v(0) = 65\text{dB} (I_{Bias} = 50\mu\text{A}), \text{ and } GB = 60\text{MHz for } C_L = 1\text{pF}$$

# Compensation of Op Amps with Output Amplifiers

Compensation of a three-stage amplifier:

This op amp introduces a third pole,  $p'_3$  (what about zeros?)

With no compensation,

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-A_{vo}}{\left(\frac{s}{p'_1} - 1\right)\left(\frac{s}{p'_2} - 1\right)\left(\frac{s}{p'_3} - 1\right)}$$



 


Illustration of compensation choices:

 

Miller compensation applied around both the second and the third stage.

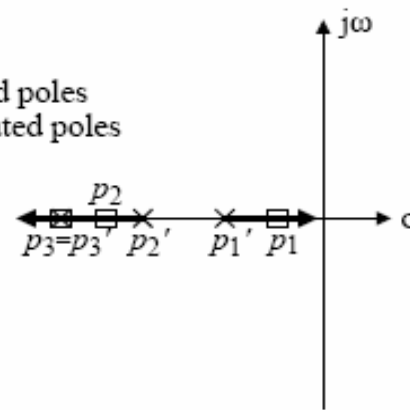□ Compensated poles  
× Uncompensated poles




Miller compensation applied around the second stage only.

Fig. 7.1-5
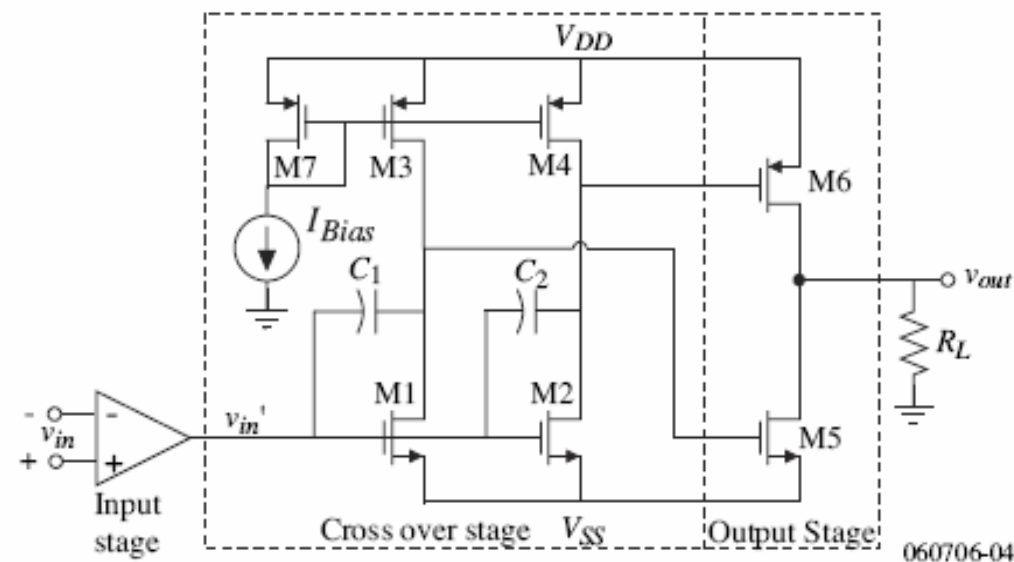
# Crossover-Inverter, Buffer Stage Op Amp

Principle: If the buffer has high output resistance and voltage gain (common source), this is okay if when loaded by a small  $R_L$  the gain of this stage is approximately unity.




This op amp is capable of delivering 160mW to a  $100\Omega$  load while only dissipating 7mW of quiescent power!

# Crossover-Inverter, Buffer Stage Op Amp - Continued

How does the output buffer work?

The two inverters, M1-M3 and M2-M4 are designed to work over different regions of the buffer input voltage,  $v_{in}'$ .

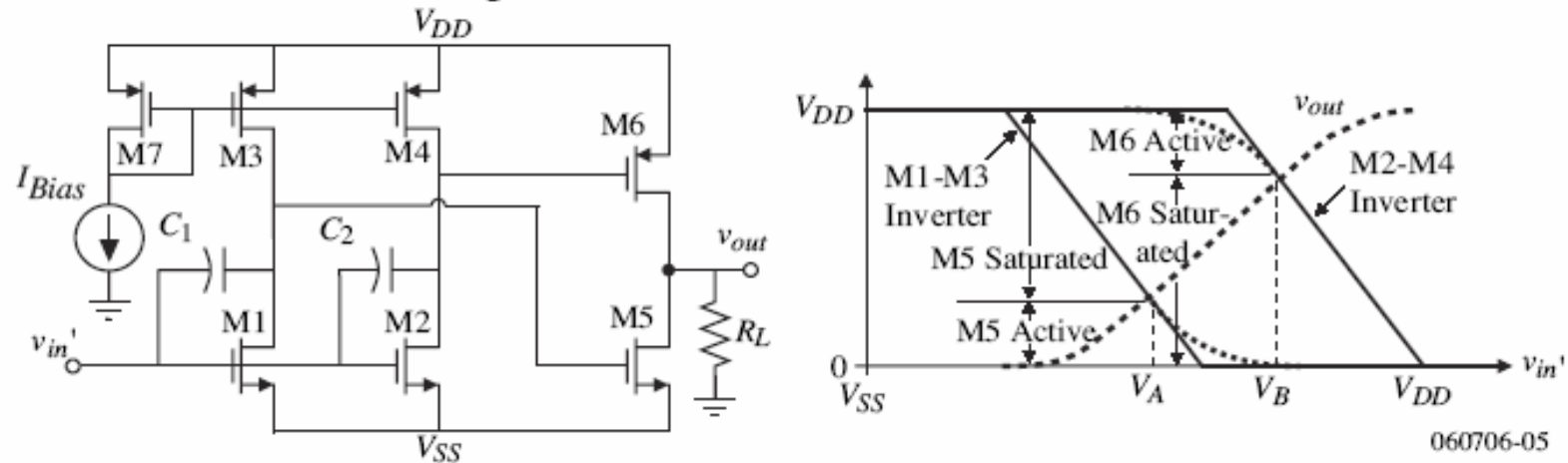Consider the idealized voltage transfer characteristic of the crossover inverters:




$$\text{Crossover voltage} \equiv V_C = V_B - V_A \geq 0$$

$V_C$  is designed to be small and positive for worst case variations in processing.

# Low Output Resistance Op Amp

To get low output resistance using MOSFETs, negative feedback must be used.

Ideal implementation:

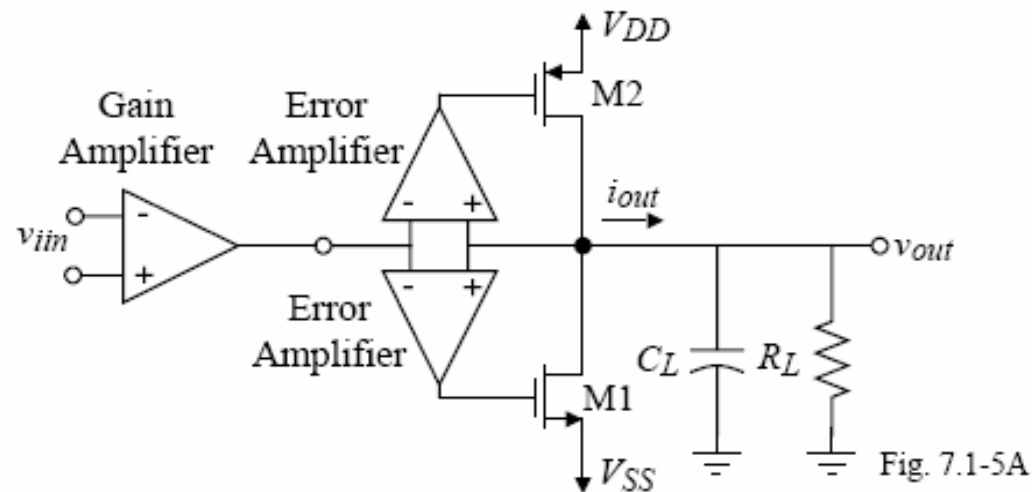


Comments:

- The output resistance will be equal to  $r_{ds1} || r_{ds2}$  divided by the loop gain
- If the error amplifiers are not perfectly matched, the bias current in M1 and M2 is not defined

# Low Output Resistance Op Amp - Continued

Offset correction circuitry:

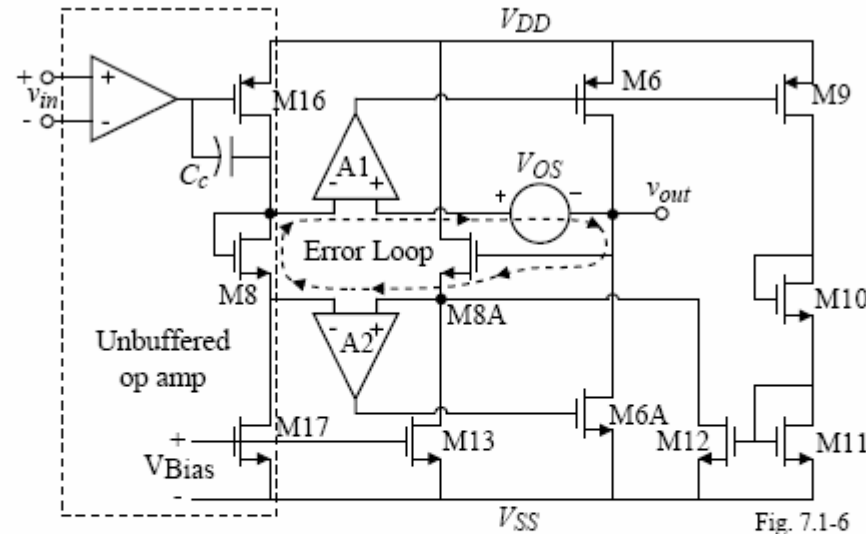


The feedback circuitry of the two error amplifiers tries to insure that the voltages in the loop sum to zero. Without the M9-M12 feedback circuit, there is no way to adjust the output for any error in the loop. The circuit works as follows:


When  $V_{OS}$  is positive, M6 tries to turn off and so does M6A.  $I_{M9}$  reduces thus reducing  $I_{M12}$ . A reduction in  $I_{M12}$  reduces  $I_{M8A}$  thus decreasing  $V_{GS8A}$ .  $V_{GS8A}$  ideally decreases by an amount equal to  $V_{OS}$ . A similar result holds for negative offsets and offsets in EA2.

# Low Output Resistance Op Amp - Continued

Error amplifiers:

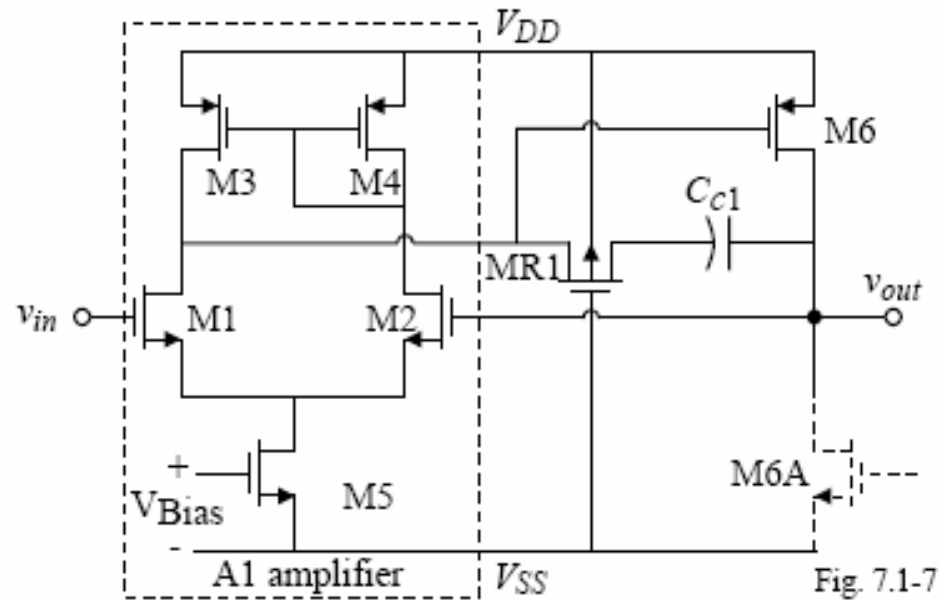
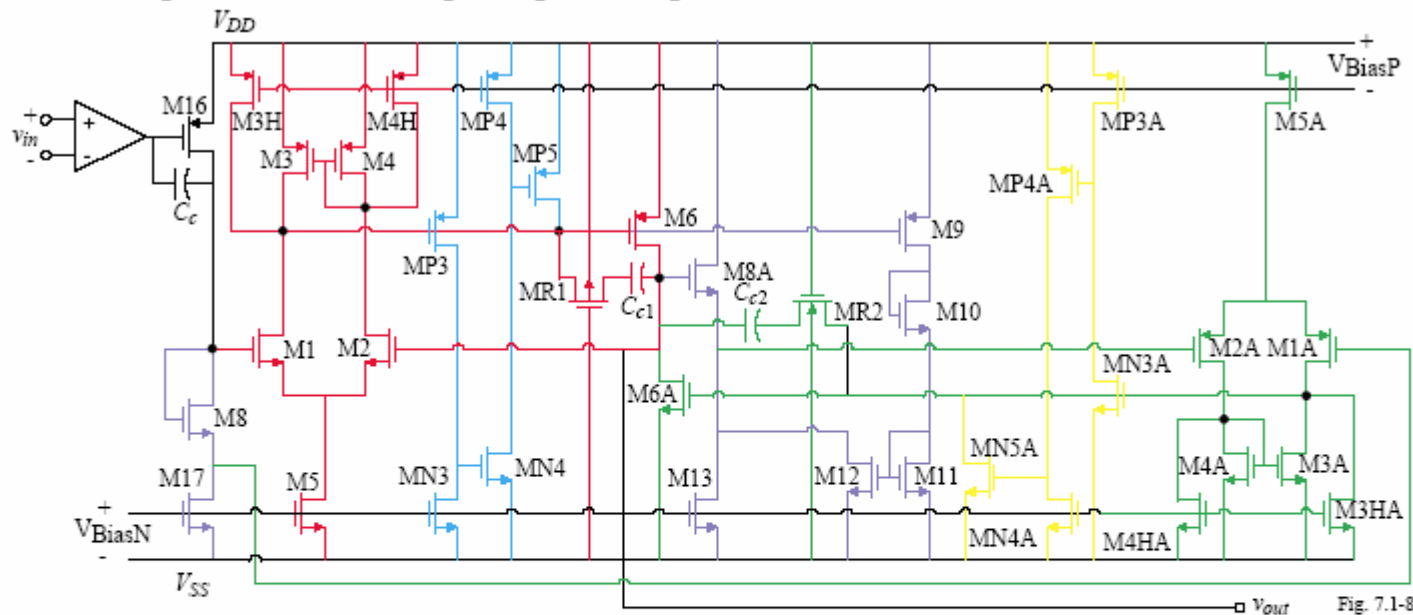
# Low Output Resistance Op Amp – Complete Schematic




Short circuit protection(max. output  $\pm 60\text{mA}$ ):

MP3-MN3-MN4-MP4-MP5

MN3A-MP3A-MP4A-MN4A-MN5A

$$R_{out} \approx \frac{r_{ds6} || r_{ds6A}}{\text{Loop Gain}} \approx \frac{50\text{k}\Omega}{5000} = 10\Omega$$

 

# Simpler Implementation of Negative Feedback to Achieve Low Output Resistance

 


Fig. 7.1-9

Output Resistance:

$$R_{out} = \frac{R_o}{1+LG}$$

where

$$R_o = \frac{1}{g_{ds6}+g_{ds7}}$$

and

$$|LG| = \frac{g_{m2}}{2g_{m4}} (g_{m6}+g_{m7})R_o$$

Therefore, the output resistance is:

$$R_{out} = \frac{1}{(g_{ds6}+g_{ds7}) \left[ 1 + \left( \frac{g_{m2}}{2g_{m4}} \right) (g_{m6}+g_{m7})R_o \right]}$$

# Example - Low Output Resistance Using Shunt Negative Feedback Buffer

Find the output resistance of above op amp using the model parameters of Table 3.1-2.

Solution

The current flowing in the output transistors, M6 and M7, is 1mA which gives  $R_o$  of

$$R_o = \frac{1}{(\lambda_N + \lambda_P) 1\text{mA}} = \frac{1000}{0.09} = 11.11\text{k}\Omega$$

To calculate the loop gain, we find that

$$g_{m2} = \sqrt{2K_N \cdot 10 \cdot 100\mu\text{A}} = 469\mu\text{S}$$

$$g_{m4} = \sqrt{2K_P \cdot 1 \cdot 100\mu\text{A}} = 100\mu\text{S}$$

and

$$g_{m6} = \sqrt{2K_P \cdot 10 \cdot 1000\mu\text{A}} = 1\text{mS}$$

Therefore, the loop gain is

$$|LG| = \frac{469}{100} \cdot 12 \cdot 11.11 = 104.2$$

Solving for the output resistance,  $R_{out}$ , gives

$$R_{out} = \frac{11.11\text{k}\Omega}{1 + 104.2} = 106\Omega \text{ (Assumes that } R_L \text{ is large)}$$

# BJTs Available in CMOS Technology

Illustration of an NPN substrate BJT available in a p-well CMOS technology:

 



Fig. 7.1-10

Comments:

- $g_m$  of the BJT is larger than the FET so that the output resistance w/o feedback is lower
- Can use the lateral or substrate BJT but since the collector is on ac ground, the substrate BJT is preferred
- Current is required to drive the BJT
 
# Two-Stage Op Amp with a Class-A BJT Output Buffer Stage

Purpose of the M8-M9 source follower:  
 1.) Reduce the output resistance  
 (includes whatever is seen from the base to ground divided by  $1+\beta_F$ )  
 2.) Reduces the output load at the drains of M6 and M7



Small-signal output resistance :

$$R_{out} \approx \frac{r_{\pi 10} + (1/g_{m9})}{1+\beta_F} = \frac{1}{g_{m10}} + \frac{1}{g_{m9}(1+\beta_F)}$$

$$= 51.6\Omega + 6.7\Omega = 58.3\Omega \text{ where } I_{10}=500\mu\text{A}, I_8=100\mu\text{A}, W_9/L_9=100 \text{ and } \beta_F \text{ is } 100$$

$$v_{OUT}(\text{max}) = V_{DD} - V_{SD8}(\text{sat}) - v_{BE10} = V_{DD} - \sqrt{\frac{2K_p'}{I_8(W_8/L_8)}} - V_t \ln\left(\frac{I_{c10}}{I_{s10}}\right)$$

Voltage gain:

$$\frac{v_{out}}{v_{in}} \approx \left(\frac{g_{m1}}{g_{ds2}+g_{ds4}}\right) \left(\frac{g_{m6}}{g_{ds6}+g_{ds7}}\right) \left(\frac{g_{m9}}{g_{m9}+g_{mbs9}+g_{ds8}+g_{\pi 10}}\right) \left(\frac{g_{m10}R_L}{1+g_{m10}R_L}\right)$$

Compensation will be more complex because of the additional stages.

# Example - Designing the Class-A, Buffered Op Amp

Use the parameters of Table 3.1-2 along with the BJT parameters of  $I_s = 10^{-14}\text{A}$  and  $\beta_F = 100$  to design the class-A, buffered op amp to give the following specifications.

Assume the channel length is to be  $1\mu\text{m}$ .

$$V_{DD} = 2.5\text{V} \quad V_{SS} = -2.5\text{V} \quad \text{GB} = 5\text{MHz} \quad A_{vd}(0) \geq 5000\text{V/V} \quad \text{Slew rate} \geq 10\text{V}/\mu\text{s}$$
$$R_L = 500\Omega \quad R_{out} \leq 100\Omega \quad C_L = 100\text{pF} \quad \text{ICMR} = -1\text{V to } 2\text{V}$$

## Solution

Because the specifications above are similar to the two-stage design of Ex. 6.3-1, we can use these results for the first two stages of our design. However, we must convert the results of Ex. 6.3-1 to a PMOS input stage. The results of doing this give  $W_1 = W_2 = 6\mu\text{m}$ ,  $W_3 = W_4 = 7\mu\text{m}$ ,  $W_5 = 11\mu\text{m}$ ,  $W_6 = 43\mu\text{m}$ , and  $W_7 = 34\mu\text{m}$ .

BJT follower:

$$\text{SR} = 10\text{V}/\mu\text{s} \text{ and } 100\text{pF} \text{ capacitor give } I_{11} = 1\text{mA}.$$

$$\therefore \text{ If } W_{13} = 44\mu\text{m}, \text{ then } W_{11} = 44\mu\text{m}(1000\mu\text{A}/30\mu\text{A}) = 1467\mu\text{m}.$$

$$I_{11} = 1\text{mA} \Rightarrow 1/g_{m10} = 0.0258\text{V}/1\text{mA} = 25.8\Omega$$

MOS follower:

To source 1mA, the BJT requires  $20\mu\text{A}$  ( $\beta = 100$ ) from the MOS follower.

Therefore, select a bias current of  $100\mu\text{A}$  for M8.

$$\text{ If } W_{12} = 44\mu\text{m}, \text{ then } W_8 = 44\mu\text{m}(100\mu\text{A}/30\mu\text{A}) = 146\mu\text{m}.$$

# Example - Designing the Class-A, Buffered Op Amp

If  $1/g_{m10}$  is  $25.8\Omega$ , then design  $g_{m9}$  as

$$\frac{1}{g_{m10}} = \frac{1}{g_{m9}(1+\beta_F)} = 25.8\Omega \quad \rightarrow \quad g_{m9} = \frac{1}{(25.8\Omega)(1+\beta_F)} = \frac{1}{25.8 \cdot 101} = 384\mu S$$

$$\therefore g_{m9} \text{ and } I_9 \Rightarrow W/L = 6.7$$

To calculate the voltage gain of the MOS follower we need to find  $g_{mbs9}$ .

$$\therefore g_{mbs9} = \frac{g_{m9} \gamma_N}{2\sqrt{2\phi_F + V_{BS9}}} = \frac{384 \cdot 0.4}{2\sqrt{0.7+2}} = 46.7\mu S$$

where we have assumed that the value of  $V_{SB9}$  is approximately 2V.

$$\therefore A_{MOS} = \frac{384\mu S}{384\mu S + 46.7\mu S + 4\mu S + 5\mu S} = 0.873$$

The voltage gain of the BJT follower is

$$A_{BJT} = \frac{500}{25.8+500} = 0.951 \text{ V/V}$$

Thus, the gain of the op amp is

$$A_{vd}(0) = (7777)(0.873)(0.951) = 6459 \text{ V/V}$$

The power dissipation of this amplifier is,

$$P_{diss.} = 5V(1255\mu A) = 6.27\text{mW}$$

# Summary

- A buffered op amp requires an output resistance between  $10\Omega \leq R_o \leq 1000\Omega$
- Output resistance using MOSFETs only can be reduced by,
  - Source follower output ( $1/g_m$ )
  - Negative shunt feedback (frequency is a problem in this approach)
- Use of substrate (or lateral) BJT's can reduce the output resistance because  $g_m$  is larger than the  $g_m$  of a MOSFET
- Adding a buffer stage to lower the output resistance will most likely complicate the compensation of the op amp

# High Frequency Op Amps

# HIGH SPEED/FREQUENCY OP AMPS


- Increase the GB of operational amplifiers
  - Extending the GB of conventional op amps
- Cascading of Amplifiers
  - Voltage amplifiers
  - Voltage amplifiers using current feedback

# INCREASING THE GB OF OP AMPS

## What is the Influence of $GB$ on the Frequency Response?

The unity-gainbandwidth represents a limit in the trade-off between closed loop voltage gain and the closed-loop -3dB frequency.

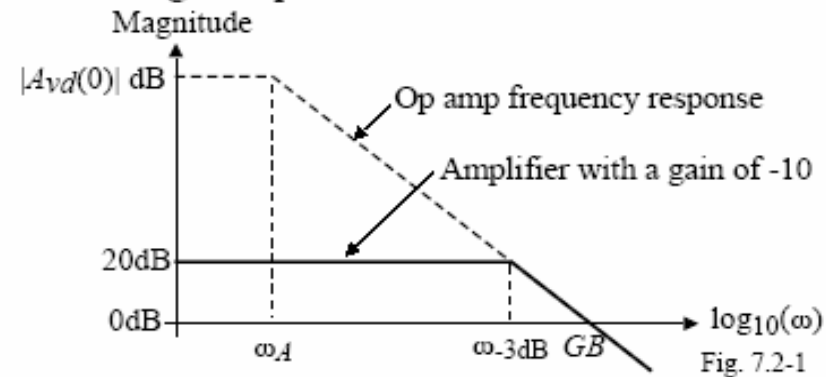Example of a gain of -10 voltage amplifier:



What causes the  $GB$ ?

We know that

$$GB = \frac{g_m}{C}$$

where  $g_m$  is the transconductance that converts the input voltage to current and  $C$  is the capacitor that causes the dominant pole.


This relationship assumes that all higher-order poles are greater than  $GB$ .

# What is the Limit of Gain-Bandwidth?

The following illustrates what happens when the next higher pole is not greater than  $GB$ :


For a two-stage op amp, the poles and zeros are:

 - 1.) Dominant pole  $p_1 = \frac{-g_{m1}}{A_v(0)C_c}$
- 2.) Output pole  $p_2 = \frac{-g_{m6}}{C_L}$
- 3.) Mirror pole  $p_3 = \frac{-g_{m3}}{C_{gs3}+C_{gs4}}$  and  $z_3 = 2p_3$
- 4.) Nulling pole  $p_4 = \frac{-1}{R_z C_I}$
- 5.) Nulling zero  $z_1 = \frac{-1}{R_z C_c - (C_c/g_{m6})}$


 
# Higher Poles

For reasonable phase margin, the smallest higher-order pole should be 2-3 times larger than  $GB$  if all other higher-order poles are larger than  $10GB$ .



If the higher-order poles are not greater than  $10GB$ , then the distance from  $GB$  to the smallest non-dominant pole should be increased for reasonable phase margin.

# Increasing the $GB$ of a Two-Stage Op Amp

- 1.) Use the nulling zero to cancel the closest pole beyond the dominant pole.
- 2.) The maximum  $GB$  would be equal to the magnitude of the second closest pole beyond the dominant pole.
- 3.) Adjust the dominant pole so that  $2.2GB \approx$  (second closest pole beyond the dominant pole)

Illustration which assumes that  $p_2$  is the next closest pole beyond the dominant pole:

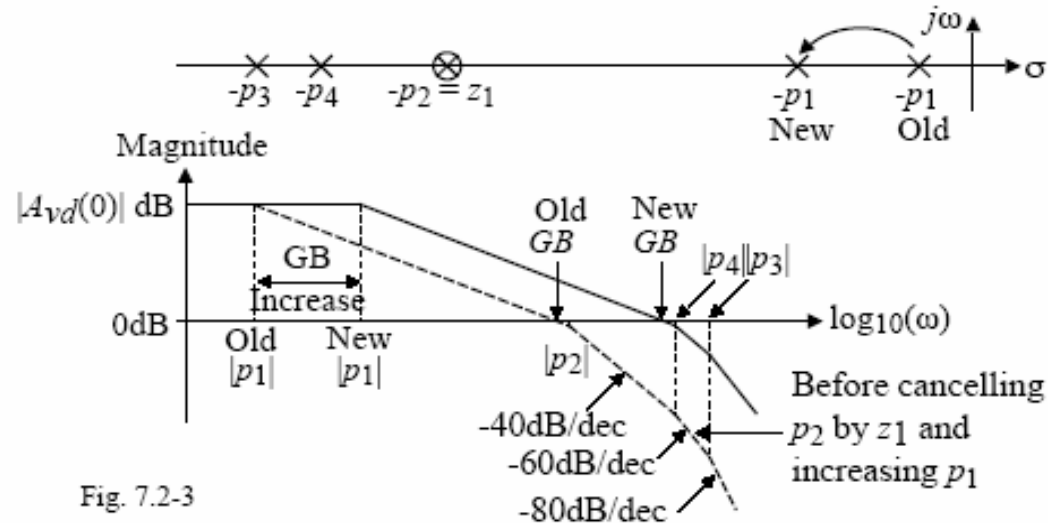


Fig. 7.2-3

# Example - Increasing the $GB$ of the Two-Stage Op Amp Design

Use the two-stage op amp designed in Example 6.3-1 and apply the above approach to increase the gainbandwidth as much as possible.

## Solution

1.) First find the values of  $p_2$ ,  $p_3$ , and  $p_4$ .

(a.) From Ex. 6.3-2, we see that

$$p_2 = -94.25 \times 10^6 \text{ rads/sec.}$$

(b.)  $p_3$  was found in Ex. 6.3-1 as

$$p_3 = -2.81 \times 10^9 \text{ rads/sec. (also there is a zero at } -5.62 \times 10^9 \text{ rads/sec.)}$$

(c.) To find  $p_4$ , we must find  $C_I$  which is the output capacitance of the first stage of the op amp.  $C_I$  consists of the following capacitors,

$$C_I = C_{bd2} + C_{bd4} + C_{gs6} + C_{gd2} + C_{gd4}$$

For  $C_{bd2}$  the width is  $3\mu\text{m} \Rightarrow L1+L2+L3=3\mu\text{m} \Rightarrow AS/AD=9\mu\text{m}^2$  and  $PS/PD=12\mu\text{m}$ .

For  $C_{bd4}$  the width is  $15\mu\text{m} \Rightarrow L1+L2+L3=3\mu\text{m} \Rightarrow AS/AD=45\mu\text{m}^2$  and  $PS/PD=36\mu\text{m}$ .

From Table 3.2-1:

$$C_{bd2} = (9\mu\text{m}^2)(770 \times 10^{-6} \text{F/m}^2) + (12\mu\text{m})(380 \times 10^{-12} \text{F/m}) = 6.93 \text{fF} + 4.56 \text{fF} = 11.5 \text{fF}$$

$$C_{bd4} = (45\mu\text{m}^2)(560 \times 10^{-6} \text{F/m}^2) + (36\mu\text{m})(350 \times 10^{-12} \text{F/m}) = 25.2 \text{fF} + 12.6 \text{fF} \approx 37.8 \text{fF}$$

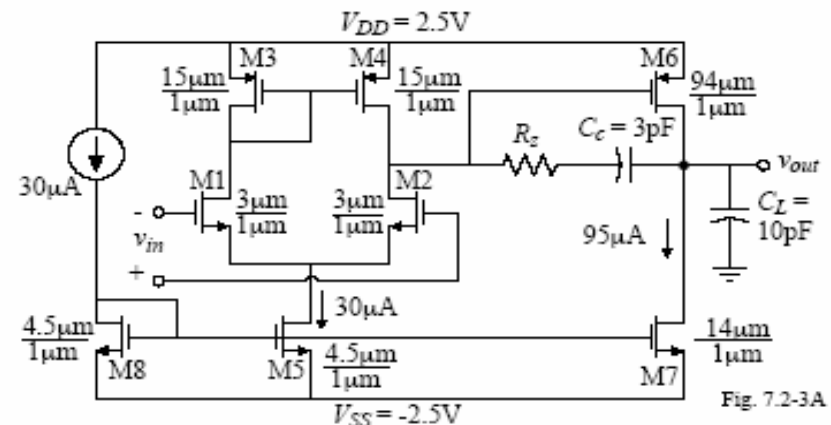


Fig. 7.2-3A

# Example - Increasing the $GB$ of the Two-Stage Op Amp Design

$C_{gs6}$  is given by Eq. (10b) of Sec. 3.2 and is

$$\begin{aligned} C_{gs6} &= CGDO \cdot W_6 + 0.67(C_{ox}W_6L_6) = (220 \times 10^{-12})(94 \times 10^{-6}) + (0.67)(24.7 \times 10^{-4})(94 \times 10^{-12}) \\ &= 20.7 \text{fF} + 154.8 \text{fF} = 175.5 \text{fF} \end{aligned}$$

$$C_{gd2} = 220 \times 10^{-12} \times 3 \mu\text{m} = 0.66 \text{fF} \quad \text{and} \quad C_{gd4} = 220 \times 10^{-12} \times 15 \mu\text{m} = 3.3 \text{fF}$$

Therefore,  $C_T = 11.5 \text{fF} + 37.8 \text{fF} + 175.5 \text{fF} + 0.66 \text{fF} + 3.3 \text{fF} = 228.8 \text{fF}$ . Although  $C_{bd2}$  and  $C_{bd4}$  will be reduced with a reverse bias, let us use these values to provide a margin. In fact, we probably ought to double the whole capacitance to make sure that other layout parasitics are included. Thus let  $C_T$  be 300fF.

In Ex. 6.3-2,  $R_z$  was 4.591k $\Omega$  which gives  $p_4 = -0.726 \times 10^9$  rads/sec.

2.) Using the nulling zero,  $z_1$ , to cancel  $p_2$ , gives  $p_4$  as the next smallest pole.

For 60° phase margin  $GB = |p_4|/2.2$  if the next smallest pole is more than 10GB.

$$\therefore GB = 0.726 \times 10^9 / 2.2 = 0.330 \times 10^9 \text{ rads/sec. or } 52.5 \text{MHz.}$$

This value of  $GB$  is designed from the relationship that  $GB = g_{m1}/C_c$ . Assuming  $g_{m1}$  is constant, then  $C_c = g_{m1}/GB = (94.25 \times 10^{-6}) / (0.330 \times 10^9) = 286 \text{fF}$ . It might be useful to increase  $g_{m1}$  in order to keep  $C_c$  above the surrounding parasitic capacitors ( $C_{gd6} = 20.7 \text{fF}$ ). The success of this method assumes that there are no other roots with a magnitude smaller than 10GB.

# Example - Increasing the $GB$ of the Folded Cascode Op Amp

Use the folded-cascode op amp designed in Example 6.5-3 and apply the above approach to increase the gainbandwidth as much as possible. Assume that the drain/source areas are equal to  $2\mu\text{m}$  times the width of the transistor and that all voltage dependent capacitors are at zero voltage.

Solution

The poles of the folded cascode op amp are:


$$p_A \approx \frac{-1}{R_A C_A} \quad (\text{the pole at the source of M6})$$

$$p_B \approx \frac{-1}{R_B C_B} \quad (\text{the pole at the source of M7})$$

$$p_6 \approx \frac{-g_{m10}}{C_6} \quad (\text{the pole at the drain of M6})$$

$$p_8 \approx \frac{-g_{m8} r_{ds8} g_{m10}}{C_8} \quad (\text{the pole at the source of M8})$$
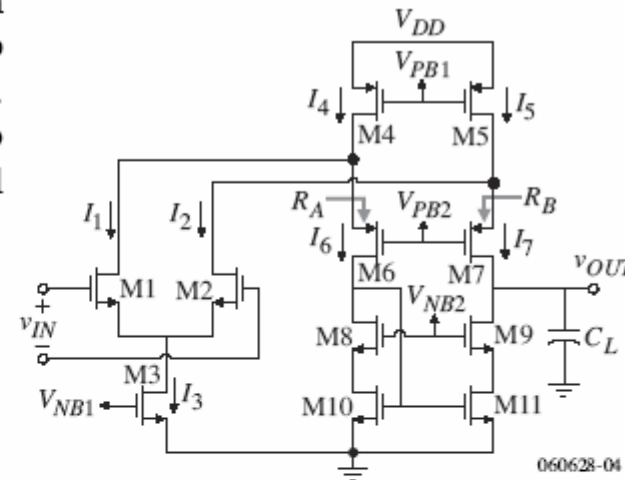
$$p_9 \approx \frac{-g_{m9}}{C_9} \quad (\text{the pole at the source of M9})$$



# Example - Increasing the $GB$ of the Folded Cascode Op Amp (cont)

Let us evaluate each of these poles.

1.) For  $p_A$ , the resistance  $R_A$  is approximately equal to  $g_{m6}$  and  $C_A$  is given as

$$C_A = C_{gs6} + C_{bd1} + C_{gd1} + C_{bd4} + C_{bs6} + C_{gd4}$$

From Ex. 6.5-3,  $g_{m6} = 744.6\mu\text{S}$  and capacitors giving  $C_A$  are found using the parameters of Table 3.2-1 as,

$$C_{gs6} = (220 \times 10^{-12} \cdot 80 \times 10^{-6}) + (0.67)(80 \times 10^{-6} \cdot 10^{-6} \cdot 24.7 \times 10^{-4}) = 149 \text{fF}$$

$$C_{bd1} = (770 \times 10^{-6})(35.9 \times 10^{-6} \cdot 2 \times 10^{-6}) + (380 \times 10^{-12})(2 \cdot 37.9 \times 10^{-6}) = 84 \text{fF}$$

$$C_{gd1} = (220 \times 10^{-12} \cdot 35.9 \times 10^{-6}) = 8 \text{fF}$$

$$C_{bd4} = C_{bs6} = (560 \times 10^{-6})(80 \times 10^{-6} \cdot 2 \times 10^{-6}) + (350 \times 10^{-12})(2 \cdot 82 \times 10^{-6}) = 147 \text{fF}$$

and

$$C_{gd4} = (220 \times 10^{-12})(80 \times 10^{-6}) = 17.6 \text{fF}$$

Therefore,

$$C_A = 149 \text{fF} + 84 \text{fF} + 8 \text{fF} + 147 \text{fF} + 17.6 \text{fF} + 147 \text{fF} = 0.553 \text{pF}$$

Thus,

$$p_A = \frac{-744.6 \times 10^{-6}}{0.553 \times 10^{-12}} = -1.346 \times 10^9 \text{ rads/sec.}$$

2.) For the pole,  $p_B$ , the capacitance connected to this node is

$$C_B = C_{gd2} + C_{bd2} + C_{gs7} + C_{gd5} + C_{bd5} + C_{bs7}$$

# Example - Increasing the *GB* of the Folded Cascode Op Amp (cont)

The various capacitors above are found as

$$C_{gd2} = (220 \times 10^{-12} \cdot 35.9 \times 10^{-6}) = 8 \text{ fF}$$

$$C_{bd2} = (770 \times 10^{-6})(35.9 \times 10^{-6} \cdot 2 \times 10^{-6}) + (380 \times 10^{-12})(2 \cdot 37.9 \times 10^{-6}) = 84 \text{ fF}$$

$$C_{gs7} = (220 \times 10^{-12} \cdot 80 \times 10^{-6}) + (0.67)(80 \times 10^{-6} \cdot 10^{-6} \cdot 24.7 \times 10^{-4}) = 149 \text{ fF}$$

$$C_{gd5} = (220 \times 10^{-12})(80 \times 10^{-6}) = 17.6 \text{ fF}$$

and

$$C_{bd5} = C_{bs7} = (560 \times 10^{-6})(80 \times 10^{-6} \cdot 2 \times 10^{-6}) + (350 \times 10^{-12})(2 \cdot 82 \times 10^{-6}) = 147 \text{ fF}$$

The value of  $C_B$  is the same as  $C_A$  and  $g_{m6}$  is assumed to be the same as  $g_{m7}$  giving  $p_B = p_A = -1.346 \times 10^9$  rads/sec.

3.) For the pole,  $p_6$ , the capacitance connected to this node is

$$C_6 = C_{bd6} + C_{gd6} + C_{gs8} + C_{gs9}$$

The various capacitors above are found as

$$C_{bd6} = (560 \times 10^{-6})(80 \times 10^{-6} \cdot 2 \times 10^{-6}) + (350 \times 10^{-12})(2 \cdot 82 \times 10^{-6}) = 147 \text{ fF}$$

$$C_{gs8} = (220 \times 10^{-12} \cdot 36.4 \times 10^{-6}) + (0.67)(36.4 \times 10^{-6} \cdot 10^{-6} \cdot 24.7 \times 10^{-4}) = 67.9 \text{ fF}$$

and

$$C_{gs9} = C_{gs8} = 67.9 \text{ fF} \quad C_{gd6} = C_{gd5} = 17.6 \text{ fF}$$

Therefore,

$$C_6 = 147 \text{ fF} + 17.6 \text{ fF} + 67.9 \text{ fF} + 67.9 \text{ fF} = 0.300 \text{ pF}$$

# Example - Increasing the $GB$ of the Folded Cascode Op Amp (cont)

From Ex. 6.5-3,  $g_{m6} = 744.6 \times 10^{-6}$ . Therefore,  $p_6$ , can be expressed as

$$-p_6 = \frac{744.6 \times 10^{-6}}{0.300 \times 10^{-12}} = 2.482 \times 10^9 \text{ rads/sec.}$$

4.) Next, we consider the pole,  $p_8$ . The capacitance connected to this node is

$$C_8 = C_{bd10} + C_{gd10} + C_{gs8} + C_{bs8}$$

These capacitors are given as,

$$C_{bs8} = C_{bd10} = (770 \times 10^{-6})(36.4 \times 10^{-6} \cdot 2 \times 10^{-6}) + (380 \times 10^{-12})(2 \cdot 38.4 \times 10^{-6}) = 85.2 \text{ fF}$$

$$C_{gs8} = (220 \times 10^{-12} \cdot 36.4 \times 10^{-6}) + (0.67)(36.4 \times 10^{-6} \cdot 10^{-6} \cdot 24.7 \times 10^{-4}) = 67.9 \text{ fF}$$

and

$$C_{gd10} = (220 \times 10^{-12})(36.4 \times 10^{-6}) = 8 \text{ fF}$$

The capacitance  $C_8$  is equal to

$$C_8 = 67.9 \text{ fF} + 8 \text{ fF} + 85.2 \text{ fF} + 85.2 \text{ fF} = 0.246 \text{ pF}$$

Using the values of Ex. 6.5-3 of  $774.6 \mu\text{S}$ , the pole  $p_8$  is found as,

$$-p_8 = g_{m8} r_{ds8} g_{m10} / C_8 = -774.6 \mu\text{S} \cdot 774.6 \mu\text{S} / 3 \mu\text{S} \cdot 0.246 \text{ pF} = -812.4 \times 10^9 \text{ rads/sec.}$$

5.) The capacitance for the pole at  $p_9$  is identical with  $C_8$ . Therefore, since  $g_{m9}$  is  $774.6 \mu\text{S}$ , the pole  $p_9$  is found to be  $-p_9 = 3.149 \times 10^9 \text{ rads/sec.}$

# Example - Increasing the $GB$ of the Folded Cascode Op Amp (cont)

The poles are summarized below:

$$p_A = -1.346 \times 10^9 \text{ rads/sec} \quad p_B = -1.346 \times 10^9 \text{ rads/sec} \quad p_6 = -2.482 \times 10^9 \text{ rads/sec}$$
$$p_8 = -812.4 \times 10^9 \text{ rads/sec} \quad p_9 = -3.149 \times 10^9 \text{ rads/sec}$$

The smallest of these poles is  $p_A$  or  $p_B$ . Since  $p_6$  and  $p_9$  are not much larger than  $p_A$  or  $p_B$ , we will find the new  $GB$  by dividing  $p_A$  or  $p_B$  by 6 (rather than 2.2) to get  $224 \times 10^6 \text{ rads/sec} \approx 200 \times 10^6$ . Thus the new  $GB$  will be  $200/2\pi$  or 32MHz. The magnitude of the dominant pole is given as

$$p_{\text{dominant}} = \frac{GB}{A_{vd}(0)} = \frac{200 \times 10^6}{7,464} = 26,795 \text{ rads/sec.}$$


The value of load capacitor that will give this pole is

$$C_L = \frac{1}{p_{\text{dominant}} R_{\text{out}}} = \frac{1}{26.795 \times 10^3 \cdot 19.4 \text{M}\Omega} \approx 1.9 \text{pF}$$

Therefore, the new  $GB = 32\text{MHz}$  compared with the old  $GB = 10\text{MHz}$ .
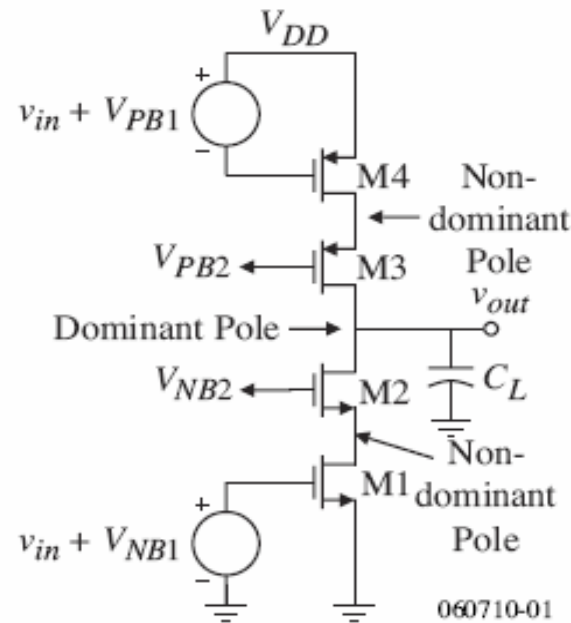
# Elimination of Higher-Order Poles

The minimum circuitry for a cascode op amp is shown below:



If the source-drain area between M1 and M2 and M3 and M4 can be minimized, the non-dominant poles will be quite large.

# CASCADED AMPLIFIERS USING CURRENT FEEDBACK AMPLIFIERS

## Advantages of Using Current Feedback

Why current feedback:

- Higher  $GB$
- Less voltage swing  $\Rightarrow$  more dynamic range

What is a current amplifier?

 


Fig. 7.2-8A

Requirements:

$$i_o = A_i(i_1 - i_2)$$

$$R_{i1} = R_{i2} = 0\Omega$$

$$R_o = \infty$$

Ideal source and load requirements:

$$R_{source} = \infty$$

$$R_{Load} = 0\Omega$$

# Bandwidth Advantage of a Current Feedback Amplifier

Consider the inverting voltage amplifier shown using a current amplifier with negative current feedback:

The output current,  $i_o$ , of the current amplifier can be written as

$$i_o = A_i(s)(i_1 - i_2) = -A_i(s)(i_{in} + i_o)$$

The closed-loop current gain,  $i_o/i_{in}$ , can be found as

$$\frac{i_o}{i_{in}} = \frac{-A_i(s)}{1 + A_i(s)}$$

However,  $v_{out} = i_o R_2$  and  $v_{in} = i_{in} R_1$ . Solving for the voltage gain,  $v_{out}/v_{in}$  gives

$$\frac{v_{out}}{v_{in}} = \frac{i_o R_2}{i_{in} R_1} = \left( \frac{-R_2}{R_1} \right) \left( \frac{A_i(s)}{1 + A_i(s)} \right)$$

If  $A_i(s) = \frac{A_o}{\frac{s}{\omega_A} + 1}$ , then

$$\frac{v_{out}}{v_{in}} = \left( \frac{-R_2}{R_1} \right) \left( \frac{A_o}{1 + A_o} \right) \left( \frac{\omega_A(1 + A_o)}{s + \omega_A(1 + A_o)} \right) \Rightarrow A_v(0) = \frac{-R_2 A_o}{R_1(1 + A_o)} \quad \text{and} \quad \boxed{\omega_{3dB} = \omega_A(1 + A_o)}$$

 


Fig. 7.2-9

# Bandwidth Advantage of a Current Feedback Amplifier (continued)


The unity-gainbandwidth is,

$$GB = |A_v(0)| \omega_{-3dB} = \frac{R_2 A_o}{R_1(1+A_o)} \cdot \omega_A(1+A_o) = \frac{R_2}{R_1} A_o \omega_A = \frac{R_2}{R_1} GB_i$$

where  $GB_i$  is the unity-gainbandwidth of the current amplifier.

*Note that if  $GB_i$  is constant, then increasing  $R_2/R_1$  (the voltage gain) increases  $GB$ .*

Illustration:

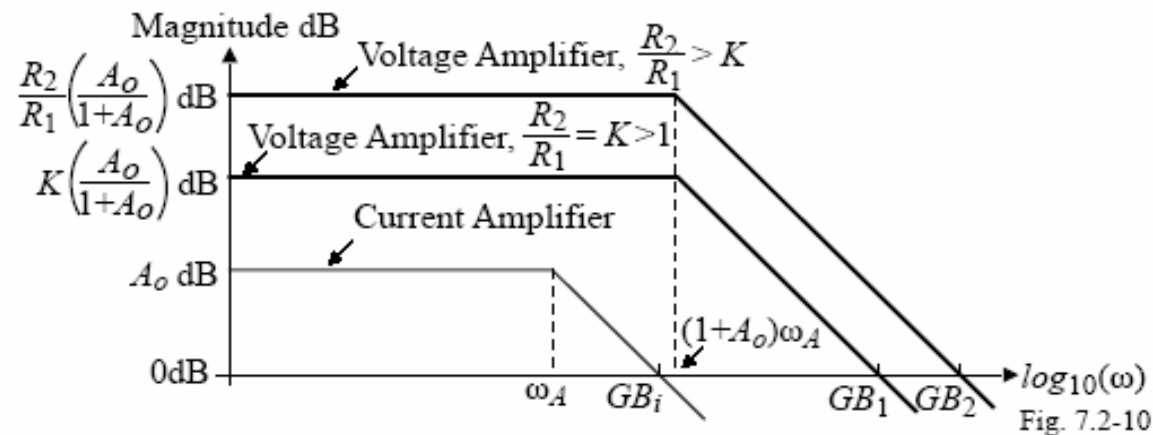


Note that  $GB_2 > GB_1 > GB_i$

The above illustration assumes that the  $GB$  of the voltage amplifier realizing the voltage buffer is greater than the  $GB$  achieved from the above method.
 
# A Wide-Swing, Cascode Current Mirror as a High Frequency Amplifier

The current mirror shown below increases the value of  $R_2$  by increasing the output resistance of the current mirror.



Limitations:

$$R_1 > \frac{1}{g_{m1}} \text{ and } R_2 < g_{m4}r_{ds4}r_{ds2} \parallel g_{m6}r_{ds6}r_{ds8} \Rightarrow \frac{R_2}{R_1} \ll g_{m1}(g_{m4}r_{ds4}r_{ds2} \parallel g_{m6}r_{ds6}r_{ds8})$$

# Example - Design of a High $GB$ Voltage Amplifier using Current Feedback

Design the wide-swing, cascode voltage amplifier to achieve a gain of  $-10V/V$  and a  $GB$  of  $500\text{MHz}$  which corresponds to a  $-3\text{dB}$  frequency of  $50\text{MHz}$ .

## Solution

Since we know what the gain is to be, let us begin by assuming that  $C_o$  will be  $100\text{fF}$ . Thus to get a  $GB$  of  $500\text{MHz}$ ,  $R_1$  must be  $3.2\text{k}\Omega$  and  $R_2 = 32\text{k}\Omega$ . Therefore,  $1/g_{m1}$  must be less than  $3200\Omega$  (say  $300\Omega$ ). Therefore we can write

$$g_{m1} = \sqrt{2KI'(W/L)} = \frac{1}{300\Omega} \rightarrow 5.56 \times 10^{-6} = K' \cdot I \cdot \frac{W}{L} \rightarrow 0.0505 = I \cdot \frac{W}{L}$$

At this point we have a problem because if  $W/L$  is small to minimize  $C_o$ , the current will be too high. If we select  $W/L = 200\mu\text{m}/1\mu\text{m}$  we will get a current of  $0.25\text{mA}$ . However, using this  $W/L$  for  $M4$  and  $M6$  will give a value of  $C_o$  that is greater than  $100\text{fF}$ .

Therefore, select  $W/L = 200$  for  $M1$ ,  $M3$ ,  $M5$  and  $M7$  and  $W/L = 20\mu\text{m}/1\mu\text{m}$  for  $M2$ ,  $M4$ ,  $M6$ , and  $M8$  which gives a current in these transistors of  $25\mu\text{A}$ .

Since  $R_2/R_1$  is multiplied by  $1/11$  let  $R_2$  be  $110$  times  $R_1$  or  $352\text{k}\Omega$ .

Now select a  $W/L$  for  $M12$  of  $20\mu\text{m}/1\mu\text{m}$  which will now permit us to calculate  $C_o$ . We will assume zero-bias on all voltage dependent capacitors. Furthermore, we will assume the diffusion area as  $2\mu\text{m}$  times the  $W$ .  $C_o$  can be written as

$$C_o = C_{gd4} + C_{bd4} + C_{gd6} + C_{bd6} + C_{gs12}$$

# Example - Design of a High $GB$ Voltage Amplifier using Current Feedback

The information required to calculate these capacitors is found from Table 3.2-1.

The various capacitors are,

$$C_{gd4} = C_{gd6} = CGDO \times 10 \mu\text{m} = (220 \times 10^{-12})(20 \times 10^{-6}) = 4.4 \text{fF}$$

$$\begin{aligned} C_{bd4} &= CJ \times AD_4 + CJSW \times PD_4 = (770 \times 10^{-6})(20 \times 10^{-12}) + (380 \times 10^{-12})(44 \times 10^{-6}) \\ &= 15.4 \text{fF} + 16.7 \text{fF} = 32.1 \text{fF} \end{aligned}$$

$$C_{bd6} = (560 \times 10^{-6})(20 \times 10^{-12}) + (350 \times 10^{-12})(44 \times 10^{-6}) = 26.6 \text{fF}$$

$$C_{gs12} = (220 \times 10^{-12})(20 \times 10^{-6}) + (0.67)(20 \times 10^{-6} \cdot 10^{-6} \cdot 24.7 \times 10^{-4}) = 37.3 \text{fF}$$


Therefore,

$$C_o = 4.4 \text{fF} + 32.1 \text{fF} + 4.4 \text{fF} + 26.6 \text{fF} + 37.3 \text{fF} = 105 \text{fF}$$

Note that if we had not reduced the  $W/L$  of M2, M4, M6, and M8 that  $C_o$  would have easily exceeded 100fF. Since 105fF is close to our original guess of 100fF, let us keep the values of  $R_1$  and  $R_2$ . If this value was significantly different, then we would adjust the values of  $R_1$  and  $R_2$  so that the  $GB$  is 500MHz. One must also check to make sure that the input pole is greater than 500MHz.

The design is completed by assuming that  $I_{Bias} = 100 \mu\text{A}$  and that the current in M9 through M12 be  $100 \mu\text{A}$ . Thus  $W_{13}/L_{13} = W_{14}/L_{14} = 20 \mu\text{m}/1 \mu\text{m}$  and  $W_9/L_9$  through  $W_{12}/L_{12}$  are  $20 \mu\text{m}/1 \mu\text{m}$ .
 
# Example - Design of a High $GB$ Voltage Amplifier using Current Feedback



Simulation Results:

$$f_{-3\text{dB}} \approx 38\text{MHz} \quad GB \approx 300\text{MHz} \quad \text{Closed-loop gain} = 18\text{dB}$$

(Loss of -2dB is attributed to source follower and  $R_1$ )


Note second pole at about 1GHz. To get these results, it was necessary to bias the input at -1.7VDC using  $\pm 3\text{V}$  power supplies.

If  $R_1$  is decreased to  $1\text{k}\Omega$  results in:

$$\text{Gain of } 26.4\text{dB}, f_{-3\text{dB}} = 32\text{MHz}, \text{ and } GB = 630\text{MHz}$$
 
# Current Feedback Amplifier

The difficulties of making the input resistance of the current amplifier small compared to  $R_1$  can be solved with the following block diagram:



$$\frac{V_{out}}{V_{in}} = \frac{-G_M R_F A_i}{1 + A_i}$$

