



## Process parameters for the AMI 0.5 micron process.

$$V_{TN} := 0.88V \quad V_{TP} := -1.0V \quad n := 1.4$$

$$K_{PN} := 110 \frac{\mu A}{V^2} \quad K_{PP} := 32 \frac{\mu A}{V^2} \quad R := \frac{K_{PN}}{K_{PP}} = 3.438$$

$$C_{OX} := 2.5 \cdot 10^{-15} \frac{F}{\mu m^2} \quad C_{ol} := 0.25 \cdot 10^{-15} \frac{F}{\mu m} \quad C_{xb} := 0.2 \cdot 10^{-15} \frac{F}{\mu m}$$

## Flicker noise parameters (current noise)

$$K_{aP} := 3.8 \cdot 10^{-30} A \cdot F \quad K_{aN} := 6.3 \cdot 10^{-26} A \cdot F$$

Flicker noise current density

$$i_{n2} := \frac{K_a \cdot I_B}{C_{OX} \cdot L^2} \cdot \frac{df}{f}$$

Input referred flicker noise voltage density

$$v_{n2} := \frac{i_{n2}}{g_m} \rightarrow \frac{I_B \cdot K_a \cdot df}{C_{OX} \cdot L^2 \cdot f \cdot g_m^2}$$

If the device is strongly inverted then we can write

$$v_{n2} := v_{n2} \text{ substitute, } g_m = \sqrt{\frac{2 \cdot I_B \cdot S \cdot K_P}{n_{sub}}} \rightarrow \frac{K_a \cdot df \cdot n_{sub}}{2 \cdot C_{OX} \cdot K_P \cdot L^2 \cdot S \cdot f}$$

$$v_{n2} := v_{n2} \text{ substitute, } S = \frac{W}{L} \rightarrow \frac{K_a \cdot df \cdot n_{sub}}{2 \cdot C_{OX} \cdot K_P \cdot L \cdot W \cdot f}$$

$$v_{n2} := v_{n2} \text{ substitute, } \frac{K_a \cdot n_{\text{sub}}}{2 \cdot K_P} = K_V \rightarrow \frac{K_V \cdot df}{C_{OX} \cdot L \cdot W \cdot f}$$

So let us compute

$$K_{vP} := \frac{K_{aP} \cdot n}{2 \cdot K_{PP}} = 8.312499999999998 \times 10^{-26} \text{ J}$$

$$K_{vN} := \frac{K_{aN} \cdot n}{2 \cdot K_{PN}} = 4.009090909090909 \text{E-022 J}$$

## Other parameters

Thermal voltage:  $U_T := 26 \cdot 10^{-3} \text{ V}$

Electronic charge:  $q_e := 1.602 \cdot 10^{-19} \text{ C}$

## IMPORTANT FUNCTIONS

$$\text{THETA}_N(I, S) := \frac{I}{2 \cdot n \cdot S \cdot K_{PN} \cdot U_T^2}$$

$$\text{THETA}_P(I, S) := \frac{I}{2 \cdot n \cdot S \cdot K_{PP} \cdot U_T^2}$$

$$\text{VSAT}(I, g_m) := 2 \cdot \frac{I}{g_m}$$

$$\text{RO}(I, V_E) := \frac{V_E}{I}$$

$$\text{GMN}(I, S) := \left[ \left[ \left( \theta \leftarrow \frac{I}{2 \cdot n \cdot S \cdot K_{PN} \cdot U_T^2} \right) \right] \right. \\ \left. \left[ \text{out} \leftarrow \frac{1 - e^{-\sqrt{\theta}}}{\sqrt{\theta}} \cdot \frac{I}{n \cdot U_T} \right] \right. \\ \left. \left[ \text{return out} \right] \right]$$

$$\text{GMP}(I, S) := \left[ \left[ \left( \theta \leftarrow \frac{I}{2 \cdot n \cdot S \cdot K_{PP} \cdot U_T^2} \right) \right] \right. \\ \left. \left[ \text{out} \leftarrow \frac{1 - e^{-\sqrt{\theta}}}{\sqrt{\theta}} \cdot \frac{I}{n \cdot U_T} \right] \right. \\ \left. \left[ \text{return out} \right] \right]$$



$$C_{Lmin} := 10 \cdot 10^{-12} \text{F} \quad C_{Lmax} := 15 \cdot 10^{-12} \text{F} \quad V_{pk} := 1.3 \text{V}$$

$$T_{settle} := 10 \mu\text{s}$$

Slew rate calculations

$$SR = \frac{I_o}{C_L} \text{ solve, } I_o \rightarrow C_L \cdot SR$$

$$\text{Also } SR := \frac{2 \cdot V_{pk}}{5 \mu\text{s}} = 5.2 \times 10^5 \frac{\text{m}^2 \cdot \text{kg}}{\text{A} \cdot \text{s}^4}$$

Use the maximum  $C_L$

$$I_o := C_{Lmax} \cdot SR = 7.8 \times 10^{-6} \text{A}$$

Since I have a 5 uA current source at my disposal lets use

$$I_o := 10 \mu\text{A}$$

Compute how long we will slew

$$SR := \frac{I_o}{C_{Lmax}} = 6.667 \times 10^5 \frac{\text{m}^2 \cdot \text{kg}}{\text{A} \cdot \text{s}^4} \quad T_{slew} := 2 \cdot \frac{V_{pk}}{SR} = 3.9 \times 10^{-6} \text{s}$$

We want linear settling to occur in about 5  $\mu\text{s}$  and to within 0.01%

NumTimeConst := 12      Nine or ten time constants would be enough ...

$$t_{linear} = 12 \cdot \tau \text{ solve, } \tau \rightarrow \frac{t_{linear}}{12} \quad t_{linear} := T_{settle} - T_{slew} = 6.1 \times 10^{-6} \text{s}$$

$$\tau := \frac{t_{linear}}{\text{NumTimeConst}} = 5.083 \times 10^{-7} \text{s} \quad \omega_u := \frac{1}{\tau} = 1.967 \times 10^6 \frac{1}{\text{s}}$$

$$f_u := \frac{\omega_u}{2 \cdot \pi} = 3.131 \times 10^5 \frac{1}{\text{s}}$$

$$\omega_u = \frac{g_{mi}}{C_L} \left| \begin{array}{l} \text{explicit} \\ \text{solve, } g_{mi} \end{array} \right. \rightarrow C_L \cdot \omega_u \quad g_{mi} := C_{Lmax} \cdot \omega_u = 2.951 \times 10^{-5} \frac{1}{\Omega}$$


$$g_m = \alpha \cdot \frac{I_B}{n \cdot U_T} \quad \left| \begin{array}{l} \text{explicit} \\ \text{solve, } \alpha \end{array} \right. \rightarrow \frac{U_T \cdot g_m \cdot n}{I_B}$$

Bias current for input device is 1/2 I<sub>o</sub>.

$$\alpha := \frac{U_T \cdot g_{mi} \cdot n}{\frac{I_o}{2}} = 0.215$$

$$\alpha(\theta) := \frac{1 - e^{-\sqrt{\theta}}}{\sqrt{\theta}}$$

$\theta := 0.05, 0.1 \dots 100$

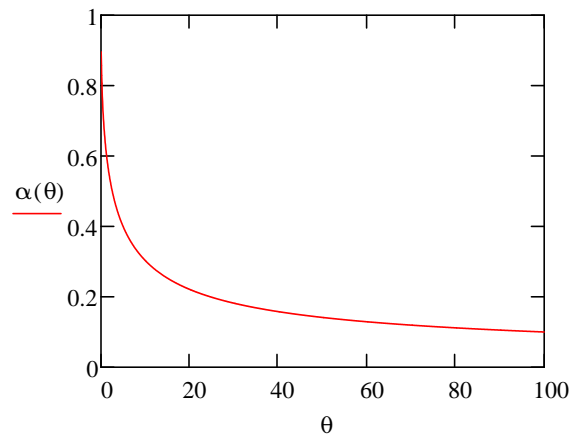

$$\theta_{\text{sym}} = \frac{I_B}{2 \cdot n \cdot S_1 \cdot K_{PP} \cdot U_T^2} \quad \left| \begin{array}{l} \text{explicit} \\ \text{solve, } S_1 \end{array} \right. \rightarrow \frac{I_B}{2 \cdot K_{PP} \cdot U_T^2 \cdot n \cdot \theta_{\text{sym}}}$$

So choose  $\theta$  of about 3  $\theta := 3$

$$S_1 := \frac{\frac{I_o}{2}}{(2 \cdot K_{PP} \cdot U_T^2 \cdot n \cdot \theta)} = 27.517$$

$$K_{OS} := 20 \text{mV} \cdot \mu\text{m} \quad \sigma_{OS} = \frac{K_{OS}}{\sqrt{A}} \quad \left| \begin{array}{l} \text{solve, } A \\ \text{explicit} \end{array} \right. \rightarrow \frac{K_{OS}^2}{\sigma_{OS}^2}$$

$$\sigma_{OS} := 2.5 \text{mV} \quad A_1 := \frac{K_{OS}^2}{\sigma_{OS}^2} = 6.4 \times 10^{-11} \text{ m}^2$$

$$A_1 = W_1 \cdot L_1 \left| \begin{array}{l} \text{explicit} \\ \text{solve, } W_1 \rightarrow \end{array} \right. \frac{A_1}{L_1}$$

$$S_1 = \frac{W_1}{L_1} \left| \begin{array}{l} \text{explicit} \\ \text{solve, } W_1 \rightarrow \end{array} \right. L_1 \cdot S_1$$

$$L_1 \cdot S_1 = \frac{A_1}{L_1} \left| \begin{array}{l} \text{explicit} \\ \text{solve, } L_1 \rightarrow \end{array} \right. \left( \begin{array}{c} \frac{\sqrt{A_1 \cdot S_1}}{S_1} \\ \frac{\sqrt{A_1 \cdot S_1}}{S_1} \end{array} \right)$$

$$L_1 := \sqrt{\frac{A_1}{S_1}} = 1.525 \times 10^{-6} \text{ m}$$

$$W_1 := \frac{A_1}{L_1} = 4.196 \times 10^{-5} \text{ m}$$

$$g_{m1} := \text{GMP}\left(\frac{I_o}{2}, S_1\right) = 6.528 \times 10^{-5} \frac{1}{\Omega}$$

Recall we wanted:  $g_{mi} = 2.951 \times 10^{-5} \frac{1}{\Omega}$

Having a bit more than what we wanted is a good thing ....

Compute the output resistance.

$$V_{E1} := 15\text{V} \quad r_{ds1} := \text{RO}\left(\frac{I_o}{2}, V_{E1}\right) = 3 \times 10^6 \Omega \quad g_{ds1} := \frac{1}{r_{ds1}} = 3.333 \times 10^{-7} \frac{1}{\Omega}$$

Check the thermal noise

$$\text{NBW} := \frac{\pi}{2} \cdot f_u = 4.918 \times 10^5 \frac{1}{\text{s}}$$

$$v_t := \sqrt{2} \cdot \sqrt{4 \cdot U_T \cdot q_e \cdot \frac{2}{3} \cdot \frac{1}{g_{m1}} \cdot \text{NBW}} = 1.294 \times 10^{-5} \text{V}$$

Check the 1/f noise

$$v_f := \sqrt{2} \cdot \sqrt{\frac{K_{vP}}{C_{ox} \cdot W_1 \cdot L_1} \cdot \ln\left(\frac{f_u}{1\text{Hz}}\right)} = 3.626 \times 10^{-6} \text{V}$$

Choose transconductance of load devices 2 times smaller than input transconductance. The load device is biased at a \* I<sub>o</sub>.

$$a := 1.5$$

$$g_{m3} := \frac{1}{2} \cdot g_{m1} = 3.264 \times 10^{-5} \frac{1}{\Omega} \quad S_3 := \frac{g_{m3}^2 \cdot n}{2 \cdot a \cdot I_O \cdot K_{PN}} = 0.452$$

Choose  $W_3 := 6 \mu\text{m}$   $L_3 := \frac{W_3}{S_3} = 1.328 \times 10^{-5} \text{m}$

Compute output resistance

$$V_{E3} := 120\text{V} \quad r_{ds3} := \text{RO}\left(\frac{3 \cdot I_O}{2}, V_{E3}\right) = 8 \times 10^6 \Omega \quad g_{ds3} := \frac{1}{r_{ds3}} = 1.25 \times 10^{-7} \frac{1}{\Omega}$$

Check the saturation voltage on the input and load devices

$$V_{ds1\_sat} := \text{VSAT}\left(\frac{I_O}{2}, g_{m1}\right) = 0.153 \text{V}$$

$$V_{ds3\_sat} := \text{VSAT}(a \cdot I_O, g_{m3}) = 0.919 \text{V}$$

Looks reasonable.

Size the transistor that provides the tail current (M11)

Choose a saturation voltage of 250 mV.

$$V_{ds11\_sat} = \sqrt{\frac{2 \cdot I_O \cdot n}{S_{11} \cdot K_{PP}}} \Bigg|_{\text{explicit solve, } S_{11}} \rightarrow \frac{2 \cdot I_O \cdot n}{K_{PP} \cdot V_{ds11\_sat}^2}$$

$$V_{ds11\_sat} := 0.75\text{V}$$

$$S_{11} := \frac{2 \cdot I_O \cdot n}{K_{PP} \cdot V_{ds11\_sat}^2} = 1.556$$

Choose  $L_{11} := 8 \mu\text{m}$   $W_{11} := S_{11} \cdot L_{11} = 1.244 \times 10^{-5} \text{m}$

Compute output resistance.

$$V_{E11} := 55\text{V} \quad r_{ds11} := \text{RO}(I_O, V_{E11}) = 5.5 \times 10^6 \Omega$$

Compute CMRR.

$$\text{CMRR} := 1 + 2 \cdot g_{m1} \cdot r_{ds11} = 719.029 \quad \text{CMRR\_DB} := 20 \cdot \log(\text{CMRR}) = 57.135$$

A little shy but not bad .. we will leave it ride for the moment.

Might make sense to see what simulator says before we worry about this.

Compute transconductance.

$$g_{m11} := \text{GMP}(I_o, S_{11}) = 2.667 \times 10^{-5} \frac{1}{\Omega}$$

Make M9 saturation voltage match that of M3.

$$\sqrt{\frac{2 \cdot I_o \cdot n}{S_9 \cdot K_{PP}}} = \sqrt{\frac{2 \cdot \left(\frac{3}{2} \cdot I_o\right) \cdot n}{S_3 \cdot K_{PN}}} \left| \begin{array}{l} \text{explicit} \\ \text{solve, } S_9 \end{array} \right. \rightarrow \frac{2 \cdot K_{PN} \cdot S_3}{3 \cdot K_{PP}}$$

$$S_9 := \frac{2 \cdot K_{PN} \cdot S_3}{3 \cdot K_{PP}} = 1.036$$

Choose  $L_9 := 10 \mu\text{m}$   $W_9 := S_9 \cdot L_9 = 1.036 \times 10^{-5} \text{ m}$

Find output resistance.

$$V_{E9} := 65\text{V} \quad r_{ds9} := \text{RO}(I_o, V_{E9}) = 6.5 \times 10^6 \Omega \quad g_{ds9} := \frac{1}{r_{ds9}} = 1.538 \times 10^{-7} \frac{1}{\Omega}$$

Choose a saturation voltage of about 200 mV for M7 so as to meet our swing requirement.

$$V_{ds7\_sat} = \sqrt{\frac{2 \cdot I_o \cdot n}{S_7 \cdot K_{PP}}} \left| \begin{array}{l} \text{explicit} \\ \text{solve, } S_7 \end{array} \right. \rightarrow \frac{2 \cdot I_o \cdot n}{K_{PP} \cdot V_{ds7\_sat}^2}$$

$$V_{ds7\_sat} := 200\text{mV}$$

$$S_7 := \frac{2 \cdot I_o \cdot n}{K_{PP} \cdot V_{ds7\_sat}^2} = 21.875$$

Choose  $L_7 := 2 \mu\text{m}$   $W_7 := S_7 \cdot L_7 = 4.375 \times 10^{-5} \text{ m}$

Compute the output resistance and transconductance.

$$V_{E7} := 20V \quad r_{ds7} := RO(I_0, V_{E7}) = 2 \times 10^6 \Omega \quad g_{ds7} := \frac{1}{r_{ds7}} = 5 \times 10^{-7} \frac{1}{\Omega}$$

$$g_{m7} := GMP(I_0, S_7) = 9.359 \times 10^{-5} \frac{1}{\Omega}$$

Make M5 and M7 have the same saturation voltage

$$S_5 := \frac{2 \cdot I_0 \cdot n}{K_{PN} \cdot V_{ds7\_sat}^2} = 6.364$$

Choose  $L_5 := 4\mu\text{m}$   $W_5 := S_5 \cdot L_5 = 2.545 \times 10^{-5} \text{m}$

Compute transconductance and output resistance.

$$g_{m5} := GMN(I_0, S_5) = 9.359 \times 10^{-5} \frac{1}{\Omega}$$

$$V_{E5} := 65V \quad r_{ds5} := RO(I_0, V_{E5}) = 6.5 \times 10^6 \Omega \quad g_{ds5} := \frac{1}{r_{ds5}} = 1.538 \times 10^{-7} \frac{1}{\Omega}$$

Let us turn our attention to the biasing circuits.

We need the following to be true.

$$\sqrt{\frac{2 \cdot I_0 \cdot n}{S_{16} \cdot K_{PP}}} = \sqrt{\frac{2 \cdot I_0 \cdot n}{S_7 \cdot K_{PP}}} + \sqrt{\frac{2 \cdot I_0 \cdot n}{S_9 \cdot K_{PP}}} \quad \left| \begin{array}{l} \text{explicit} \\ \text{solve, } S_{16} \end{array} \right. \rightarrow \frac{I_0 \cdot n}{K_{PP} \cdot \left( \sqrt{\frac{I_0 \cdot n}{K_{PP} \cdot S_7}} + \sqrt{\frac{I_0 \cdot n}{K_{PP} \cdot S_9}} \right)^2}$$

$$S_{16} := \frac{1}{\left( \sqrt{\frac{1}{S_7}} + \sqrt{\frac{1}{S_9}} \right)^2} = 0.699$$

Choose  $L_{16} := 10\mu\text{m}$   $W_{16} := S_{16} \cdot L_{16} = 6.986 \times 10^{-6} \text{m}$

Actually made if 7 over 12 for safety.

For completeness compute transconductance and output resistance.

$$g_{m16} := \text{GMP}(I_o, S_{16}) = 1.787 \times 10^{-5} \frac{1}{\Omega}$$

We also need

$$\sqrt{\frac{2 \cdot I_o \cdot n}{S_{19} \cdot K_{PN}}} = \sqrt{\frac{2 \cdot \left(\frac{3 \cdot I_o}{2}\right) \cdot n}{S_3 \cdot K_{PN}}} + \sqrt{\frac{2 \cdot I_o \cdot n}{S_5 \cdot K_{PN}}} \quad \left| \begin{array}{l} \text{explicit} \\ \text{solve, } S_{19} \end{array} \right. \rightarrow \frac{I_o \cdot n}{K_{PN} \cdot \left( \sqrt{\frac{I_o \cdot n}{K_{PN} \cdot S_5}} + \frac{\sqrt{2} \cdot \sqrt{3} \cdot \sqrt{\frac{I_o \cdot n}{K_{PN} \cdot S_3}}}{2} \right)^2}$$

$$S_{19} := \frac{I_o \cdot n}{K_{PN} \cdot \left( \sqrt{\frac{I_o \cdot n}{K_{PN} \cdot S_5}} + \frac{\sqrt{2} \cdot \sqrt{3} \cdot \sqrt{\frac{I_o \cdot n}{K_{PN} \cdot S_3}}}{2} \right)^2} \quad \left| \begin{array}{l} \text{explicit} \\ \text{simplify} \end{array} \right. \rightarrow \frac{4 \cdot I_o \cdot n}{K_{PN} \cdot \left( 2 \cdot \sqrt{\frac{I_o \cdot n}{K_{PN} \cdot S_5}} + \sqrt{\frac{6 \cdot I_o \cdot n}{K_{PN} \cdot S_3}} \right)^2}$$

$$S_{19} := \frac{4 \cdot I_o \cdot n}{K_{PN} \cdot \left( 2 \cdot \sqrt{\frac{I_o \cdot n}{K_{PN} \cdot S_5}} + \sqrt{\frac{6 \cdot I_o \cdot n}{K_{PN} \cdot S_3}} \right)^2} = 0.203$$

Choose  $L_{19} := 20 \mu\text{m}$   $W_{19} := S_{19} \cdot L_{19} = 4.064 \times 10^{-6} \text{ m}$

Actually made it 4.1 over 22 for safety.

$$g_{m19} := \text{GMN}(I_o, S_{19}) = 1.787 \times 10^{-5} \frac{1}{\Omega}$$

$$V_{ds19\_sat} := \text{VSAT}(I_o, g_{m19}) = 1.119 \text{ V}$$

Compute output resistance for OTA.

$$R_{on} := (g_{m5} \cdot r_{ds5}) \cdot \frac{1}{g_{ds1} + g_{ds3}} = 1.327 \times 10^9 \Omega$$

$$G_{on} := \frac{1}{R_{on}} = 7.534 \times 10^{-10} \frac{1}{\Omega}$$

$$R_{op} := (g_{m7} \cdot r_{ds7}) \cdot r_{ds9} = 1.217 \times 10^9 \Omega$$

$$G_{op} := \frac{1}{R_{op}} = 8.219 \times 10^{-10} \frac{1}{\Omega}$$

$$R_{out} := \frac{1}{G_{on} + G_{op}} = 6.348 \times 10^8 \Omega$$

Compute the low-frequency imbalance factor.

$$k := \frac{(r_{ds7} \cdot g_{m7} \cdot r_{ds9}) \cdot (g_{ds1} + g_{ds3})}{g_{m5} \cdot r_{ds5}} = 0.917$$

$$A_o := \left( \frac{2+k}{2+2 \cdot k} \right) \cdot g_{m1} \cdot R_{out} = 3.153 \times 10^4$$

$$A_{dB} := 20 \cdot \log(A_o) = 89.974$$

We easily met the open-loop gain spec.

Compute the dominant pole frequency.

$$\omega_d := \frac{1}{R_{out} \cdot C_{Lmax}} = 105.023 \frac{1}{s}$$

$$f_d := \frac{\omega_d}{2 \cdot \pi} = 16.715 \frac{1}{s}$$

$$f_u := \frac{g_{m1}}{2 \cdot \pi \cdot C_{Lmax}} = 6.926 \times 10^5 \frac{1}{s}$$

Acually about ten times faster than we need. It was because of the severe slew rate requirement we had.

$$C_{db1} := C_{xb} \cdot W_1 = 8.393 \times 10^{-15} F$$

$$C_{db3} := C_{xb} \cdot W_3 = 1.2 \times 10^{-15} \text{ F}$$

$$C_{gs5} := \frac{2}{3} \cdot C_{ox} \cdot W_5 \cdot L_5 = 169.697 \times 10^{-15} \text{ F}$$

$$C_{db5} := C_{xb} \cdot W_5 = 5.091 \times 10^{-15} \text{ F}$$

$$C_{gd5} := C_{ol} \cdot W_5 = 6.364 \times 10^{-15} \text{ F}$$

$$C_x := C_{db1} + C_{db3} + C_{gs5} + C_{db5} + 2 \cdot C_{gd5} = 1.971 \times 10^{-13} \text{ F}$$

Just guessing that this might be the most important parasitic pole.

$$\omega_p := \frac{g_{m5}}{C_x} = 4.748 \times 10^8 \frac{1}{\text{s}}$$

$$f_p := \frac{\omega_p}{2 \cdot \pi} = 7.557 \times 10^7 \frac{1}{\text{s}}$$

The phase margin should be near 90 degrees.