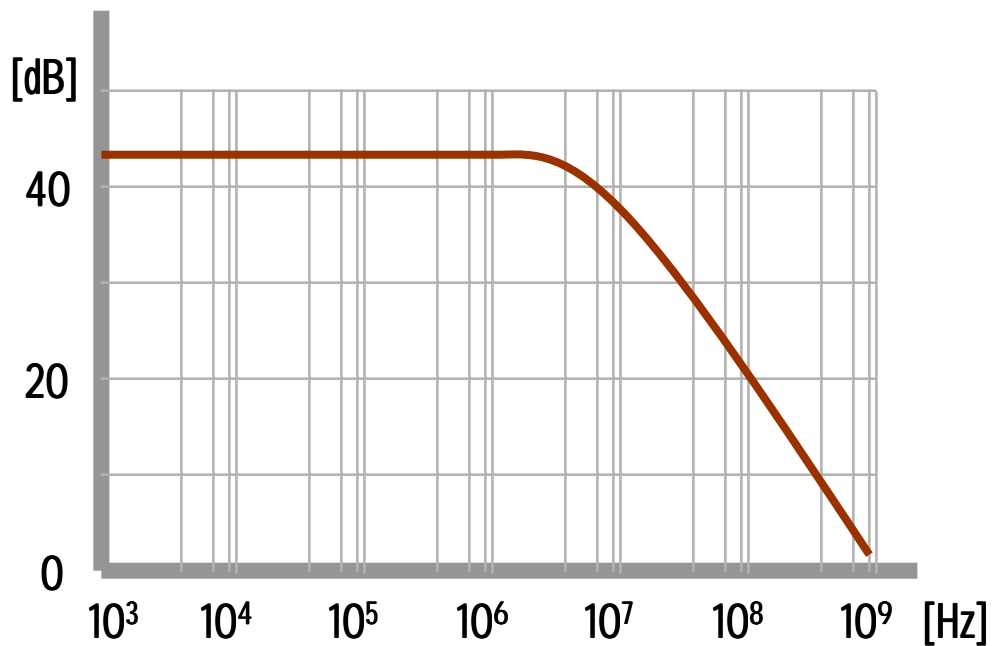


VLSI Design II

Frequency Response of Single Stage Amplifiers



Circuit Analysis

- ◆ *the precise way*: solving complex equations
- ◆ *the approximate way*: find the dominant pole
- ◆ *the handy way*: let Spice do it precisely

Goal: You are able to identify the dominant pole in a transistor circuit. You can approximately determine the contribution of each node in a circuit to the total frequency response.

Outline

- ◆ Frequency response
 - ◆ common-source amplifier
 - ◆ source-follower amplifier
 - ◆ source-follower amplifier with compensation technique
 - ◆ cascode gain stage

- ◆ Johns&Martin
 - ◆ frequency response (chap 3.11)

- ◆ Gray&Meyer
 - ◆ estimation of dominant poles
 - ◆ zero-Value Time Constant Analysis (pp500 ff)
(Analysis and Design of Analog Integrated Circuits, 3rd edition, Wiley and Sons, ISBN-0471-59984-0)

- ◆ Exercises
 - ◆ hand calculations
 - ◆ spice simulations

Frequency Response

Dominant Pole Approximation

- ◆ precise calculation of frequency response is a complex task and thus different approximation methods exist
- ◆ one method is the zero-value time constant analysis
- ◆ first some ideas about dominant-pole approximation are developed

transfer function by small-signal analysis

$$A(s) = \frac{N(s) a_0 + a_1 s + a_2 s^2 + \dots + a_m s^m}{D(s) 1 + b_1 s + b_2 s^2 + \dots + b_n s^n}$$

very often the zeros are unimportant, thus

$$A(s) = \frac{K}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \dots \left(1 - \frac{s}{p_n}\right)}$$

Where K is a constant and $p_1, p_2 \dots$ are poles of the transfer function,

thus
$$b_1 = \sum_{i=1}^n \left(-\frac{1}{p_i} \right)$$

Dominant Pole Approximation (con't 2)

$$b_1 = \sum_{i=1}^n \left(-\frac{1}{p_i} \right)$$

an important practical case occurs when one pole is dominant

$$|p_1| \ll |p_2|, |p_3|, \dots \quad \left| \frac{1}{p_1} \right| \gg \left| \sum_{i=2}^n \left(-\frac{1}{p_i} \right) \right|$$

$$\text{thus } b_1 \cong \left| \frac{1}{p_1} \right|$$

the gain magnitude in the frequency domain is

$$A(j\omega) = \frac{K}{\sqrt{\left(1 + \left(\frac{\omega}{p_1} \right)^2 \right) \left(1 + \left(\frac{\omega}{p_2} \right)^2 \right) \cdots \left(1 + \left(\frac{\omega}{p_n} \right)^2 \right)}}$$

with a dominant pole we simply get

$$|A(j\omega)| \cong \frac{K}{\sqrt{\left(1 + \left(\frac{\omega}{p_1} \right)^2 \right)}}$$


Dominant Pole Approximation (con't 3)

this approximation will be quite accurate as long as $\omega \cong |p_1|$

thus for a dominant pole situation the -3dB frequency is

$$\omega_{-3dB} \cong |p_1| \qquad \omega_{-3dB} \cong \frac{1}{b_1}$$

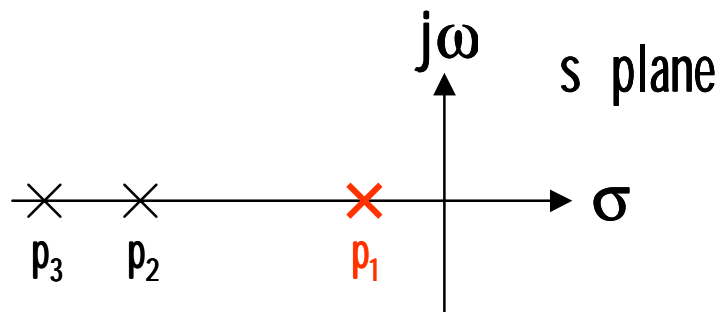pole plot for a circuit with a dominant pole



Zero-Value Time Constant


Method for finding the time constant associated with a capacitor in the small signal equivalent circuit

- ◆ replace the capacitor C_x by a voltage source V_x
- ◆ set all independent sources to ground
- ◆ set all other network capacitors to zero
- ◆ find admittance $Y_x (=1/R_x)$ which is driven by a voltage source V_x
- ◆ the time constant τ_x is given by:

$$\tau_x = R_x C_x$$

Frequency Response

Zero-Value Time Constant

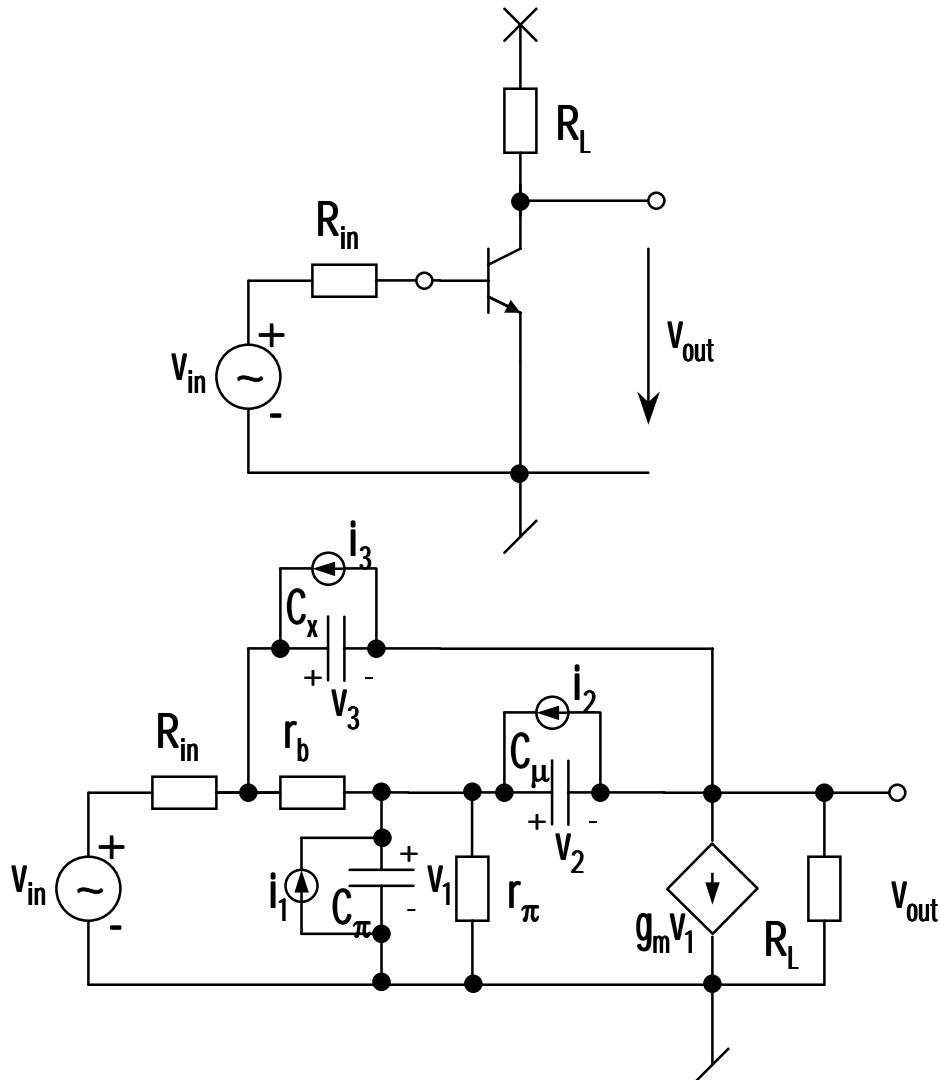

We can show that with this choice of variables the circuit equations are of the form:

$$i_1 = (g_{11} + sC_{\pi})v_1 + g_{12}v_2 + g_{13}v_3$$

$$i_2 = g_{21}v_1 + (g_{22} + sC_{\mu})v_2 + g_{23}v_3$$

$$i_3 = g_{31}v_1 + g_{32}v_2 + (g_{33} + sC_x)v_3$$

Zero-Value Time Constant (con't 1)

The poles of the transfer function are the zeros of the determinant Δ of the circuit equations, which can be written in the form:

$$\Delta(s) = K_0 + K_1s + K_2s^2 + K_3s^3$$

$$\Delta(s) = K_0 (1 + b_1s + b_2s^2 + b_3s^3)$$

If all capacitors are zero:

$$K_0 = \Delta|_{C_\pi=C_\mu=C_x=0} \equiv \Delta_0$$

Consider now the term K_1s , this is the sum of the terms involving s that are obtained when the system determinant is evaluated. However it is apparent, that s only occurs when associated with a capacitance:

$$K_1s = h_1sC_\pi + h_2sC_\mu + h_3sC_x$$

The terms are constants. h_1 can be evaluated by expanding the determinant about the first row:

$$\Delta(s) = (g_{11} + sC_\pi)\Delta_{11} + g_{12}\Delta_{12} + g_{13}\Delta_{13}$$

With cofactors Δ_{xx} of the determinant. The term sC_π is found by evaluating Δ_{11} with C_μ and C_x equal zero

$$h_1 = \Delta_{11}|_{C_\mu=C_x=0}$$

Zero-Value Time Constant (con't 2)

Now consider expansion of the determinant about the second row.

$$\Delta(s) = g_{21}\Delta_{21} + (g_{22} + sC_{\mu})\Delta_{22} + g_{23}\Delta_{23}$$

With cofactors Δ_{xx} of the determinant. The term sC_{μ} is found by evaluating Δ_{22} with C_{π} and C_x equal zero

$$h_2 = \Delta_{22} \Big|_{C_{\pi}=C_x=0}$$

similarly

$$h_3 = \Delta_{33} \Big|_{C_{\mu}=C_{\pi}=0}$$

Combining these equations gives:

$$K_1 = \Delta_{11} \Big|_{C_{\mu}=C_x=0} C_{\pi} + \Delta_{22} \Big|_{C_{\pi}=C_x=0} C_{\mu} + \Delta_{33} \Big|_{C_{\mu}=C_{\pi}=0} C_x$$

and:

$$b_1 = \frac{K_1}{K_0} = \frac{\Delta_{11} \Big|_{C_{\mu}=C_x=0}}{\Delta_0} C_{\pi} + \frac{\Delta_{22} \Big|_{C_{\pi}=C_x=0}}{\Delta_0} C_{\mu} + \frac{\Delta_{33} \Big|_{C_{\mu}=C_{\pi}=0}}{\Delta_0} C_x$$

Zero-Value Time Constant (con't 3)

Now consider putting $i_2 = i_3 = 0$ and solving for v_1

$$\frac{v_1}{i_1} = \frac{\Delta_{11}}{\Delta(s)}$$

The driving-point resistance at the C_π node pair with all capacitors equal to zero:

$$\frac{\Delta_{11} \Big|_{C_\mu = C_x = 0}}{\Delta_0} = \frac{\Delta_{11}}{\Delta} \Big|_{C_\mu = C_\pi = C_x = 0}$$

We now define

$$R_{\pi 0} = \frac{\Delta_{11}}{\Delta_0} \Big|_{C_\mu = C_x = 0}$$

We can write now:

$$b_1 = R_{\pi 0} C_\pi + R_{\mu 0} C_\mu + R_{x 0} C_x$$

Thus:

$$\omega_{-3\text{dB}} \cong \frac{1}{b_1} \qquad \omega_{-3\text{dB}} \cong \frac{1}{\sum T_0}$$

Thus the sum of the zero-value time constants leads to the -3dB frequency

Summary: Frequency Analysis Methods

The precise way:

- ◆ Add the parasitic capacitors to the equivalent circuit. Use nodal analysis for evaluating the transfer function.

The approximate way:

- ◆ if there exists a pole $p_1 \ll p_2, p_3, \dots$, and the transfer function is already given by the transfer function $A(s) = N(s)/D(s)$

with
$$D(s) = 1 + b_1s + b_2s^2 + \dots + b_ns^n$$

the pole p_1 is given by: $p_1 = 1/b_1$


- ◆ the dominant pole may be found directly in the circuit diagram by looking for the node with the largest impedance. Take care of the Miller Effect.
- ◆ The time constant (and its influence on the frequency response) associated with a single parasitic capacitor can be estimated with the zero value time constant method:
 - ◆ set all independent sources to zero
 - ◆ replace the interesting capacitor C_x by a voltage source V_x
 - ◆ set all other capacitors to zero
 - ◆ evaluate the impedance R_x seen by the voltage source V_x
 - ◆ the time constant is equal to C_xR_x

The handy way:

- ◆ AC analysis with Spice

Frequency Response Common-Source Amplifier

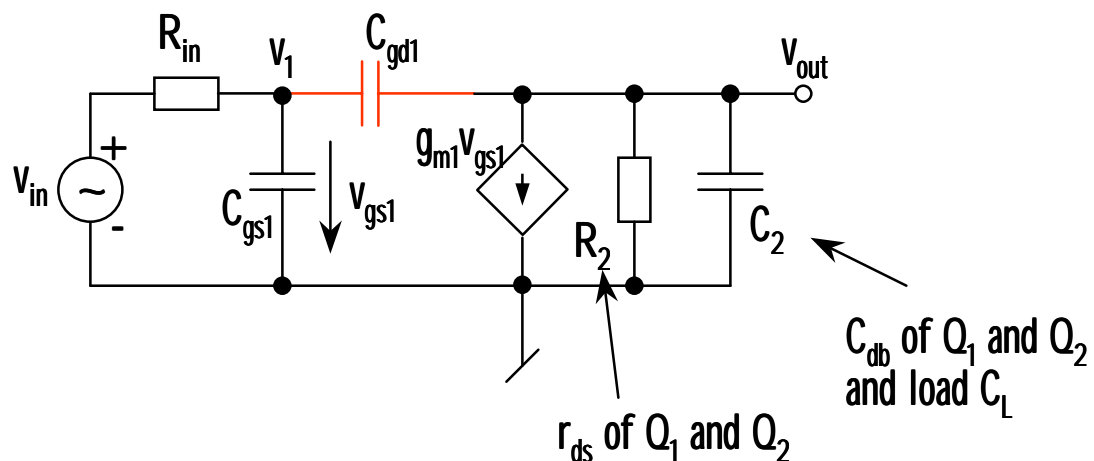- ◆ precise calculation of frequency response is most often left to computer simulations
- ◆ much insight can be obtained by finding the dominant frequency effects (dominant poles, zeros)



nodal analysis ...

Frequency Analysis (con't)

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m1}R_2 \left(1 - s \frac{C_{gd1}}{g_{m1}}\right)}{1 + sa + s^2b}$$

at frequencies where gain has just started to decrease

$$a = R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1}R_2)] + R_2 (C_{gd1} + C_2)$$

$$b = R_{in}R_2 (C_{gd1}C_{gs1} + C_{gs1}C_2 + C_{gd1}C_2)$$

$$\omega_{-3db} = \frac{1}{a}$$

$$\omega_{-3db} = \frac{1}{R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1}R_2)] + R_2 (C_{gd1} + C_2)}$$

Miller capacitance

for $R_{in} \gg R_2$



analysis for high frequencies for widely separated poles

$$D(s) = \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \cong 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1}\omega_{p2}}$$


$$\omega_{p2} \cong \frac{g_{m1}C_{gd1}}{C_{gs1}C_{gd1} + C_{gs1}C_2 + C_{gd1}C_2}$$

Frequency Response Source-Follower Amplifier

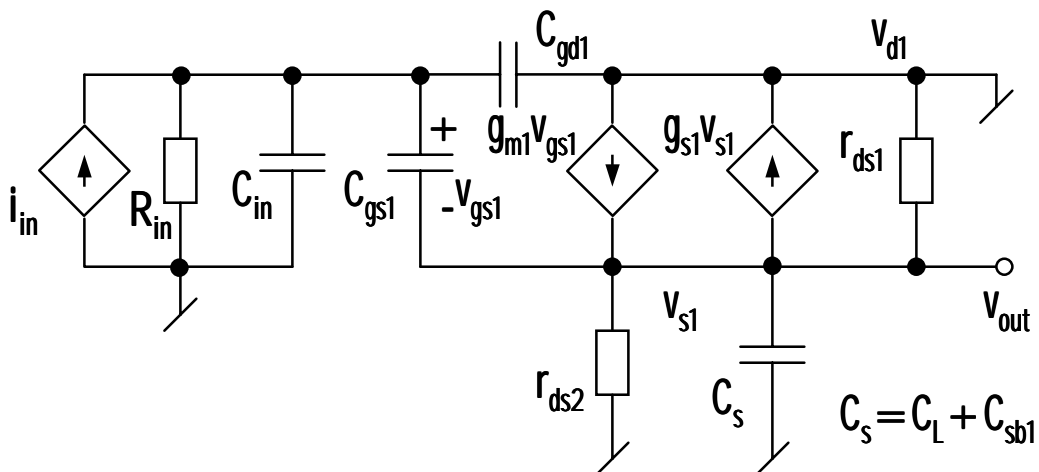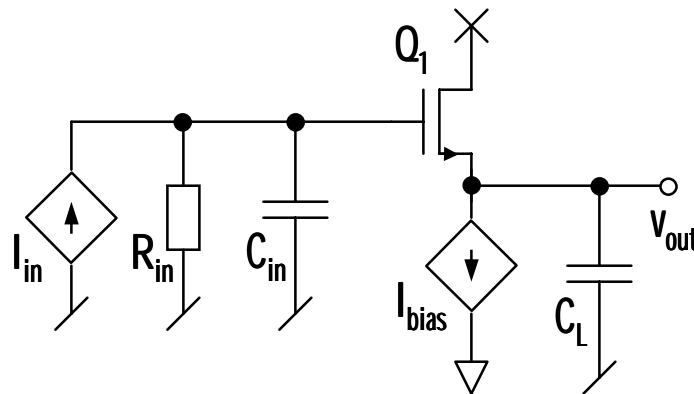- ◆ source followers can have complex poles and thus exhibit overshoot
- ◆ a compensation technique resulting in only real axis poles is shown, resulting in no overshooting



Source-Follower Amplifier (con't 1)

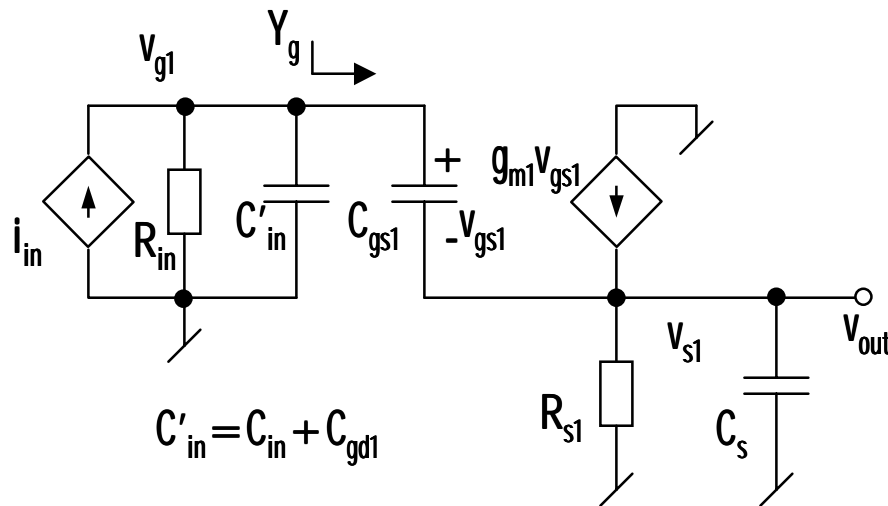

$$R_{s1} = r_{ds1} \parallel r_{ds2} \parallel (1/g_{s1})$$

1. gain from v_{g1} to v_{out} is found
2. admittance Y_g looking into gate of Q_1 without considering C_{gd1} is found
3. Gain from i_{in} to v_{g1} is found
4. overall gain from v_{in} to v_{out} is found and results interpreted

1. gain from v_{g1} to v_{out} is found

$$V_{out} (sC_s + sC_{gs1} + G_{s1}) - v_{g1} sC_{gs1} - g_{m1} (v_{g1} - v_{out}) = 0$$

$$\frac{V_{out}}{v_{g1}} = \frac{sC_{gs1} + g_{m1}}{s(C_{gs1} + C_s) + g_{m1} + G_{s1}}$$

Source-Follower Amplifier (con't 2)

1. gain from v_{g1} to v_{out} is found
2. admittance Y_g looking into gate of Q_1 without considering C_{gd1} is found
3. Gain from i_{in} to v_{g1} is found
4. overall gain from v_{in} to v_{out} is found and results interpreted

2. admittance Y_g looking into gate of Q_1 without considering C_{gd1} is found

$$Y_g = \frac{i_{g1t}}{v_{g1}} = \frac{sC_{gs1}(sC_s + G_{sq})}{s(C_{gs1} + C_s) + g_{m1} + G_{s1}}$$

3. Gain from i_{in} to v_{g1} is found

$$\frac{v_{g1}}{i_{in}} = \frac{s(C_{gs1} + C_s) + g_{m1} + G_{s1}}{a + sb + s^2c}$$

4. overall gain from v_{in} to v_{out} is found and results interpreted

$$A(s) = \frac{v_{out}}{i_{in}} = \frac{sC_{gs1} + g_{m1}}{a + sb + s^2c}$$

Source-Follower Amplifier (con't 3)

ω_0 is the pole frequency
Q is the Q factor

$$A(s) = A(0) \frac{N(s)}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}}$$

There is no peaking and the transfer functions maximum is at dc if:

$$Q < \sqrt{1/2} \cong 0.707$$

ω_0 is the -3dB frequency if:

$$Q = \sqrt{1/2}$$

Step input function:

no peaking for $Q \leq 0.5$

peaking for
(complex conjugate poles)

$Q > 0.5$

$$\% \text{ overshoot} = 100e^{-\pi/\sqrt{4Q^2-1}}$$

For the source follower:


$$\omega_z = \frac{-g_{m1}}{C_{gs1}} \quad \omega_0 = \sqrt{\frac{G_{in}(g_{m1} + G_{s1})}{C_{gs1}C_s + C'_{in}(C_{gs1} + C_s)}}$$

$$Q = \frac{\sqrt{G_{in}(g_{m1} + G_{s1})[C_{gs1}C_s + C'_{in}(C_{gs1} + C_s)]}}{G_{in}C_s + C'_{in}(g_{m1} + G_{s1}) + C_{gs1}G_{s1}}$$

Source follower circuits can exhibit large amounts of overshoot under certain conditions. In practical uE circuits the parasitic capacitances and the output capacitance results in only moderate overshoot for worst-case conditions.

Source-Follower Amplifier Compensation Technique

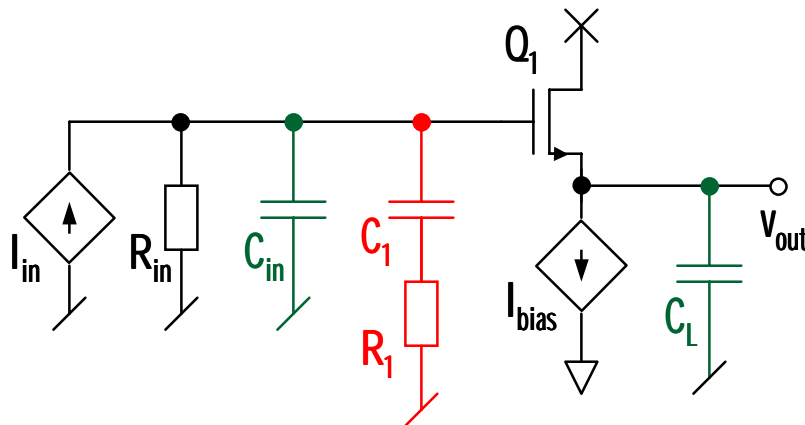- ◆ source followers can have complex poles and thus exhibit overshoot
- ◆ overshooting may be reduced by:
 - ◆ increasing C_{in} or C_s or both
 - ◆ adding a **compensation network**



$$C_1 = \frac{C_{gs1}(C_s g_{m1} - C_{gs1} G_{s1})}{(g_{m1} + G_{s1})(C_{gs1} + C_s)} \cong \frac{g_{m1} C_{gs1} C_s}{(g_{m1} + G_{s1})(C_{gs1} + C_s)}$$


$$R_1 = \frac{(C_{gs1} + G_s)^2}{C_{gs1}(C_s g_{m1} - C_{gs1} G_{s1})} \cong \frac{(C_{gs1} + G_s)^2}{C_{gs1} C_s g_{m1}}$$

$$C_2 = \frac{C_{gs1} C_s}{C_{gs1} + C_s}$$

(see Johns/Martin pp160-162)

Frequency Response Common-Gate Amplifier

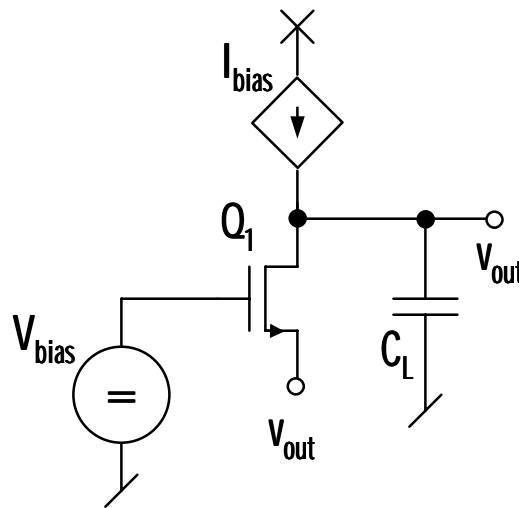- ◆ The frequency response of the common-gate stage is usually superior to that of the common-source stage due to the low impedance, r_{in} , at the source node, assuming $G_L = (sC_L + g_{ds2})$ is not considerably smaller than g_{ds1} .




(see Johns/Martin pp160-162)

Frequency Response

High-Output Impedance Mirrors

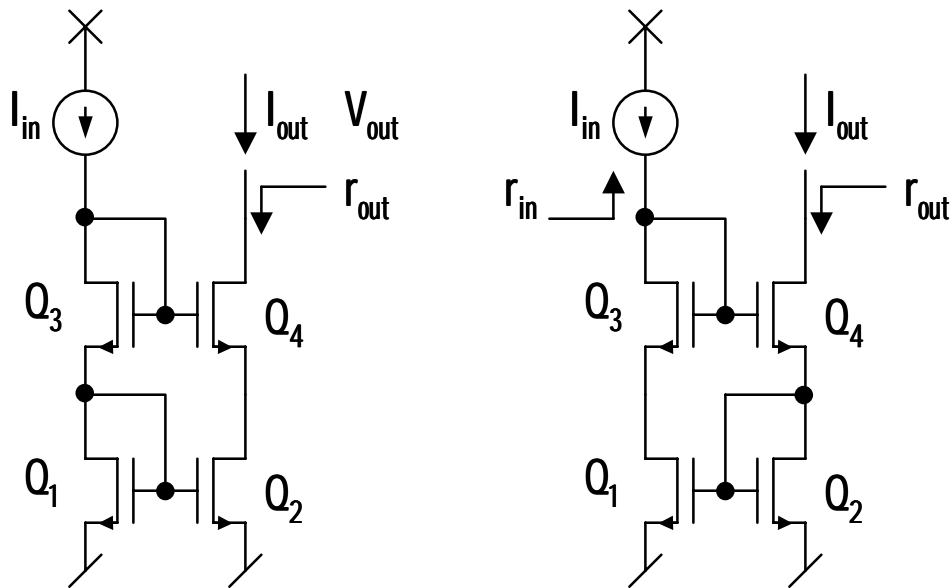
- ◆ Both the Wilson and the cascode current mirrors introduce high-frequency poles into the signal transfer function.
- ◆ The approximate time constant of these poles is C_{gs}/g_m , the roof of this statement can be found by doing high-frequency, small-signal analysis.



(see Johns/Martin pp163)

Frequency Response Cascode Gain Stage

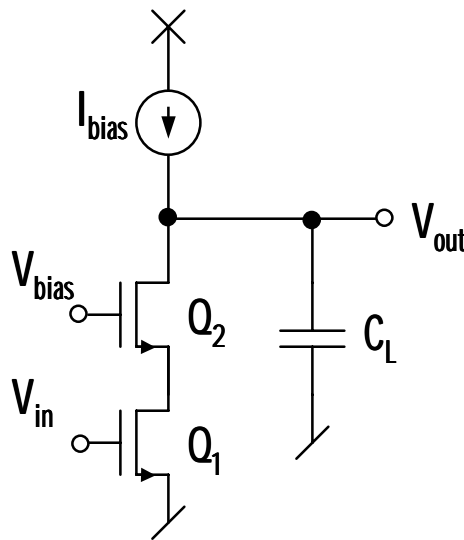
- ◆ The exact high-frequency analysis of a cascode gain stage is usually left to simulation on a computer.
- ◆ at high-frequencies, the time constant due to the output node almost always dominates since the impedance is so large at that node:
 - ◆ $C_{out} = (C_{gd2} + C_{db2}) + C_L + C_{bias}$
 - ◆ C_L is normally the major contributor



$$\omega_{-3dB} \cong \frac{1}{R_{out} C_L} \cong \frac{2g_{ds}^2}{g_m C_L}$$

Cascode Gain Stage (con't 1)

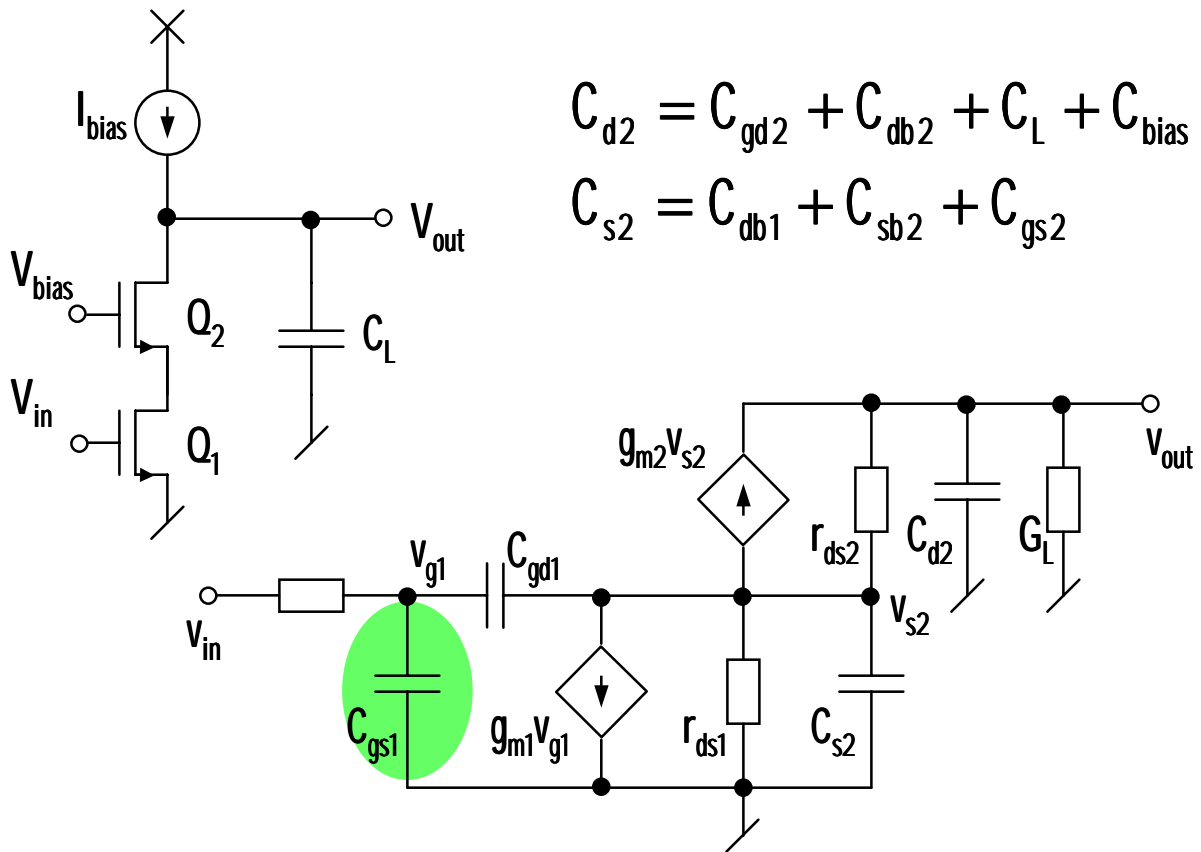
- ◆ Zero-value time constant analysis method used




- ◆ All independent sources have to be set to zero ($v_{in} = 0$)

node v_{g1} $\tau_{C_{gs1}} = C_{gs1} R_{in}$

Cascode Gain Stage (con't 2)

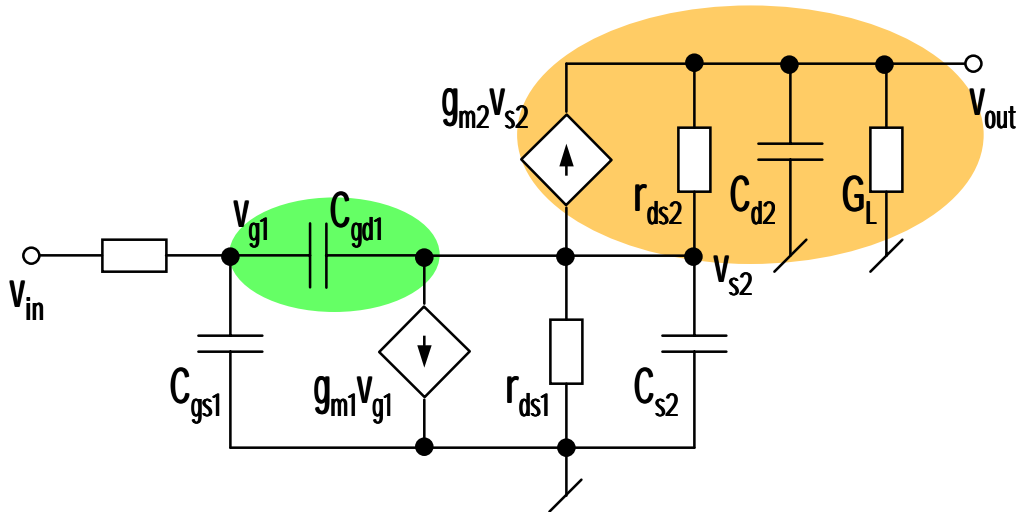

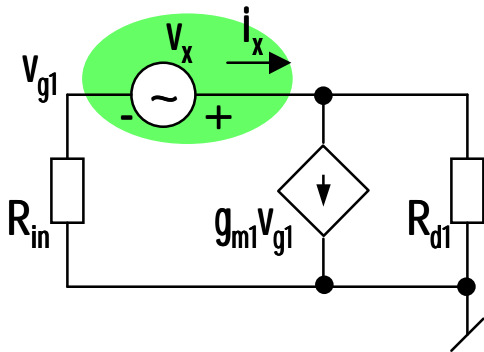nodes v_{g1}, v_{s2} the capacitor C_{gd1} is replaced by a voltage source v_x in order to calculate the input resistance seen from that node.




$$G_{d1} = g_{ds1} + Y_{s2}$$

admittance looking into the source of a cascode transistor is Y_{s2}

$$\tau_{C_{gd1}} = C_{gd1} R_{d1} (1 + R_{in} [G_{d1} + g_{m1}])$$

Cascode Gain Stage (con't 3)

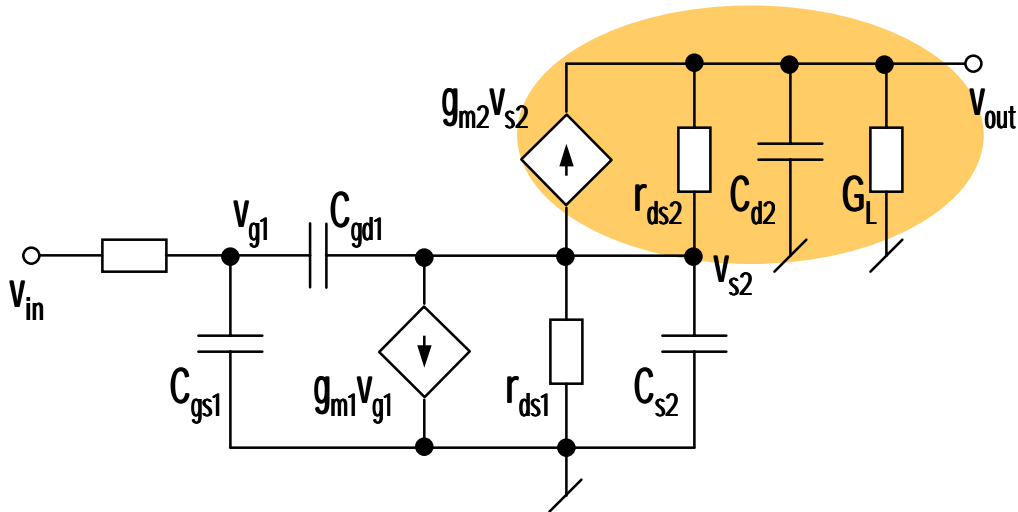

$$G_{d1} = g_{ds1} + Y_{s2}$$

admittance looking into the source
of a cascode transistor is Y_{s2}

$$Y_{s2} = i_s / v_{s2}$$

for

$$g_{ds} \ll g_m$$

$$R_L \cong g_m r_{ds}^2$$


(see cascode current mirror
impedance, pp137, vlsi-25/17)

$$Y_{s2} \cong g_{ds}$$


$$\tau_{Cgd1} \cong C_{gd1} \frac{r_{ds}}{2} (1 + g_m R_{in})$$

$$\tau_{Cgd1} \cong C_{gd1} \frac{g_m r_{ds}^2}{2}$$

for R_{in} is large and equal r_{ds}

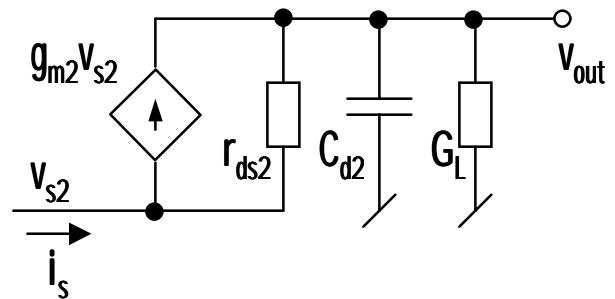

Cascode Gain Stage (con't 4)

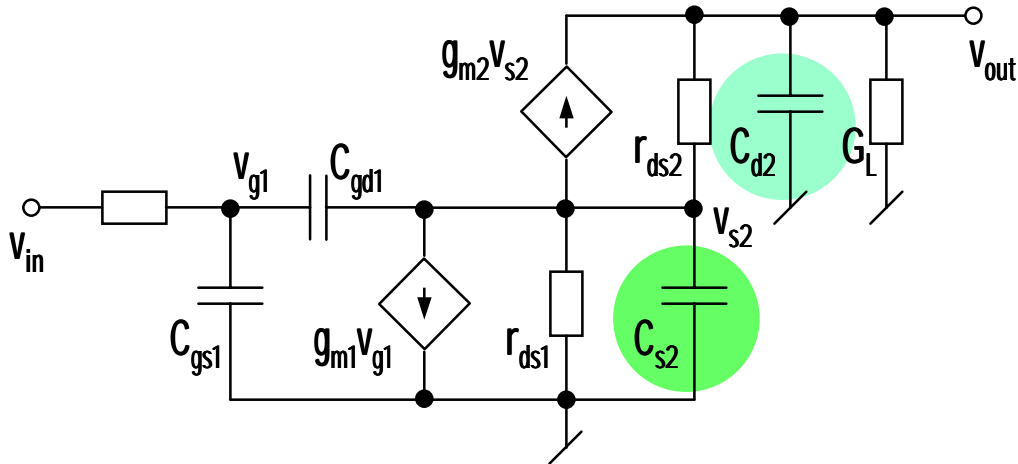

node v_{s2}

the resistance seen by the capacitor C_{s2} is r_{ds1} in parallel with the impedance seen looking in the source of Q_2 which is approximately r_{ds} , thus:

$$\tau_{C_{s2}} \cong C_{s2} \frac{r_{ds}}{2}$$

node v_{out}

The resistance seen by C_{d2} is the output impedance of the cascode amplifier, thus:


$$\tau_{C_{d2}} \cong C_{d2} \frac{g_m r_{ds}^2}{2}$$

$$\tau_{total} \cong \tau_{C_{gs1}} + \tau_{C_{gd1}} + \tau_{C_{s1}} + \tau_{C_{d1}}$$

$$\tau_{total} \cong C_{gs1} R_{in} + C_{gd1} \frac{g_m r_{ds}^2}{2} + C_{s2} \frac{r_{ds}}{2} + C_{d2} \frac{g_m r_{ds}^2}{2}$$

Cascode Gain Stage Comments

◆ High frequencies considerations

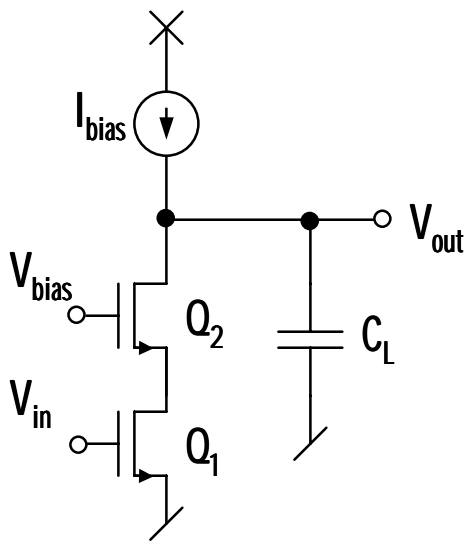

one pole dominates, thus the gain is:

$$A(s) = \frac{A_v}{1 + s / \omega_{-3dB}}$$

at frequencies substantial larger than ω_{-3dB} :

$$A(s) \cong \frac{A_v}{s / \omega_{-3dB}} \cong -\frac{g_{m1}}{sC_L}$$

◆ upper limit of the unity-gain frequency of an amplifier that uses a cascode gain stage is limited by source node of Q_2 :

$$\omega_{p2} = \frac{1}{\tau_{s2}} > \frac{3\mu_p V_{eff2}}{2L_2^2}$$

Coming Up...

- ◆ Next topic...
Basic OpAmp design and compensation
- ◆ Readings for next time...
Johns&Martin. Sections 3.11
- ◆ Exercises:
Have a look at the exercises in *Johns&Martin*.

Exercises VLSI-26 #1

Johns&Martin chap 3.11 pp156: 3.8 (difficulty: easy):

Consider the common-source amplifier shown on transparency vlsi-26/6 where $I_{in} = 100\mu A$ and all transistors have $W = 100\mu m$ and $L = 1.6\mu m$. Given $R_{in} = 180k\Omega$, $C_L = 0.3pF$, $C_{gs1} = 0.2pF$, $C_{gd1} = 15fF$, $C_{db1} = 20fF$, $C_{db2} = 36fF$, $\mu_n C_{ox} = 90\mu A/V^2$, $\mu_p C_{ox} = 30\mu A/V^2$, and $r_{ds-n} = 8000 [L (\mu m)]/[ID (mA)]$, $r_{dsp} = 12000 [L (\mu m)]/[ID (mA)]$. Estimate the 3db frequency response.

Result: $f_{-3db} = 554kHz$

Johns&Martin chap 3.11 pp160: 3.9 (difficulty: easy):

Analyse the source follower and assume that $I_{bias} = 100\mu A$ and all transistors have $W = 100\mu m$ and $L = 1.6\mu m$. Given $R_{in} = 180k\Omega$, $C_L = 10pF$, $C_{gs1} = 0.2pF$, $C_{gd1} = 15fF$, $C_{sb1} = 40fF$, $C_{in} = 30fF$, $\mu_n C_{ox} = 90\mu A/V^2$, $\mu_p C_{ox} = 30\mu A/V^2$, and $r_{ds-n} = 8000 [L (\mu m)]/[ID (mA)]$. Find ω_0 , Q , and ω_z of the source follower.

Result: $\omega_0 = 52MHz$, $Q = 0.8$, % overshoot = 8.1%,
 $\omega_z = 5.3GHz$

Exercises VLSI-26 #2

Johns&Martin chap 3.11 pp166:3.11 (difficulty: easy):

Assume that for the input transistors and the cascode transistors, $g_m = 1\text{mA/V}$, $r_{ds} = 100\text{k}\Omega$, $R_{in} = 180\text{k}\Omega$, $C_L = 5\text{pF}$, $C_{gs} = 0.2\text{pF}$, $C_{gd} = 15\text{fF}$, $C_{sb} = 40\text{fF}$, $C_{db} = 20\text{fF}$, $C_{bias} = 20\text{fF}$, Estimate the -dB frequency of the cascode amplifier (transparency 19).

Result: $\omega_{-3\text{dB}} = 2\pi \cdot 6.3\text{MHz}$

Johns&Martin chap 3.11 pp168: 3.12 (difficulty: easy):

Estimate the lower bound on the frequency of the second pole of a folded-cascode amplifier for a $0.8\mu\text{m}$ technology, where a typical value of 0.25V is chosen for $V_{\text{eff}2}$. $L_2 = 1.5L_{\text{min}}$, $\mu_p = 0.02\text{m}^2/\text{Vs}$.

Result: $\omega_{p2} = 2\pi \cdot 414\text{MHz}$