

Analog Microelectronics

Advanced Current Mirrors and OpAmp Design



Today's handouts:
(1) Lecture Slides

Outline

◆ Johns&Martin

◆ advanced current mirrors (chap 6.1)

- ◆ wide-swing current mirrors
- ◆ wide-swing constant-transconductance bias circuit
- ◆ enhanced output-impedance current mirrors (not yet)
- ◆ wide-swing current mirror with enhanced output impedance (not yet)

◆ folded-cascode OpAmp (chap 6.2)

- ◆ small signal analysis
- ◆ slew rate


◆ Exercises (6.8 & 6.10)

- ◆ spice simulations
- ◆ problems

Advanced current mirrors *wide-swing current mirrors*

- ◆ The classical two-stage OpAmp was discussed in vlsi27.
- ◆ Recently a number of alternate OpAmps designs have been gaining in popularity. They make use of more advanced current mirrors.
- ◆ **Wide-swing current mirror:**
 - ◆ as shorter channel lengths are used, it becomes more difficult to achieve reasonable OpAmp gains due to transistor output-impedance degradation caused to short-channel effects.
 - ◆ Conventional cascode current mirrors limit the signal swings available.
 - wide-swing current mirror

Wide-swing current mirrors


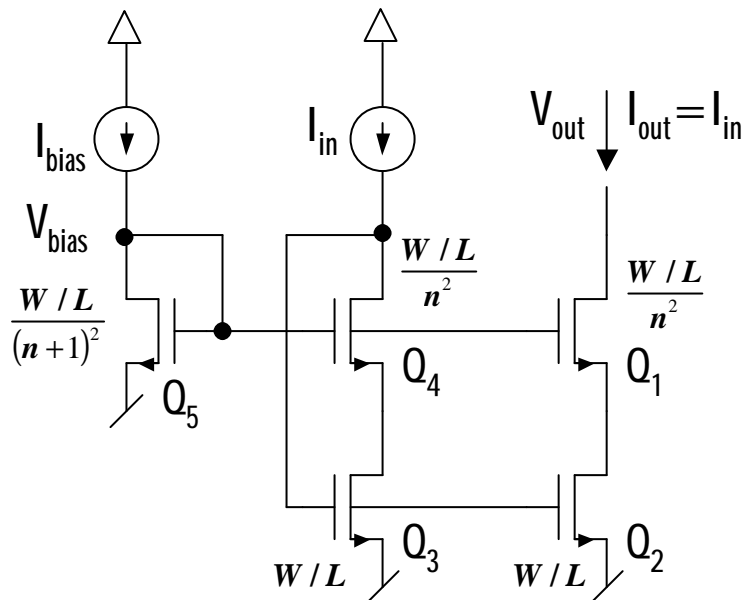


$$V_{out} > (n + 1)V_{eff}$$

$$\text{for } Q_4: V_{tn} > nV_{eff}$$

- ◆ The basic idea is to bias the drain-source voltages of transistors Q_2 and Q_3 to be close to the minimum possible without them going to triode region.
- ◆ Choice of I_{bias} :
 - ◆ I_{bias} equal to maximum of I_{in} (all fets in saturation)
 - ◆ I_{bias} equal to nominal of I_{in} (for larger I_{in} , fets in triode, but probably only during slew-rate)
- ◆ Design hints:
 - ◆ a common choice for n is unity
 - ◆ Q_5 larger (0,1V to 0.15V) in order to offset the increased threshold voltages for Q_1 and Q_4 due to their body effects
 - ◆ L of Q_1 , Q_4 and Q_5 are twice minimal channel length, L of Q_2 and Q_3 are just slightly larger than minimal channel length (high frequency poles)

 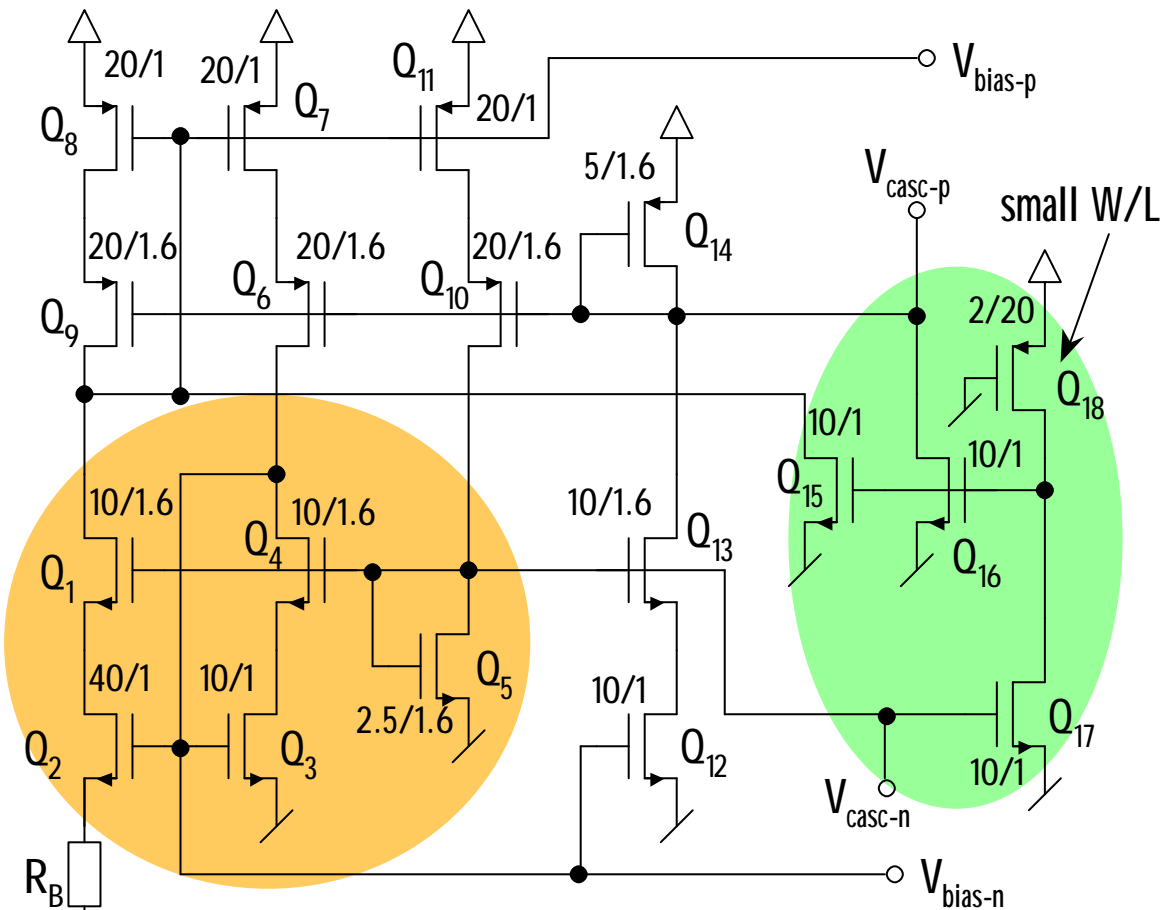Wide-swing constant-transconductance bias circuit



bias loop

see vlsi-27
slide 29

cascode bias


start-up circuitry

injects current as long
as $I_{D's}$ are zero

Enhanced output-impedance current mirror

- ◆ Another variation of the cascode current mirror is the enhanced output-impedance current mirror shown as simplified version
- ◆ basic idea: use of feedback amplifier to keep the drain-source voltage across Q_2 stable, irrespective of the output voltage
- ⇒ the additional amplifier increases the output impedance (see classical cascode current mirror, vlsi-25 slides 16, 17)
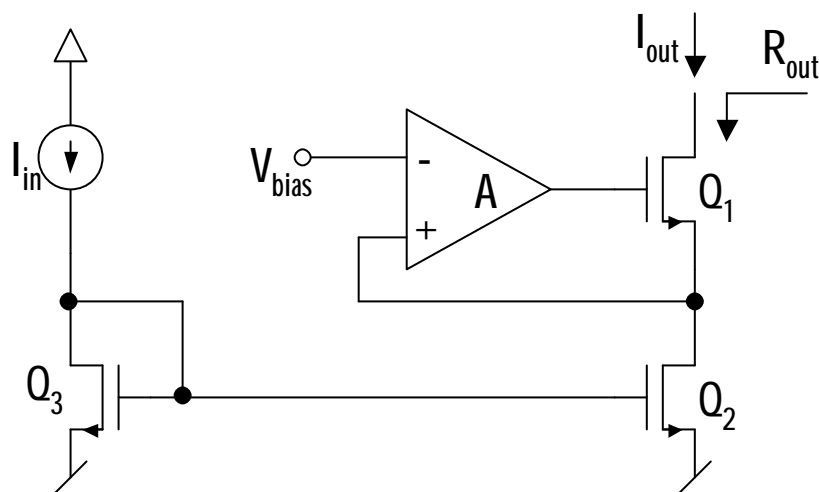
$$R_{out} \cong g_{m1} r_{ds1} r_{ds2} (1 + A)$$




Folded-cascode OpAmp

- ◆ many modern integrated CMOS OpAmps are designed to drive only capacitive loads
- ◆ capacitive-only loads do not need voltage buffers to obtain low output impedance of the OpAmp
- ◆ thus it is possible to realize OpAmps having higher speed and larger signal swings than those who must drive resistive loads
- ◆ these improvements are obtained by having only one single high-impedance node at the OpAmp output that drives only capacitive loads
- ◆ all internal nodes have relatively low impedance (around g_m) thus the speed is optimized
- ◆ the compensation is usually achieved by the load capacitance
- ◆ the most important parameter is their transconductance:
operational transconductance amplifier OTA

Folded-cascode OpAmp *con't*

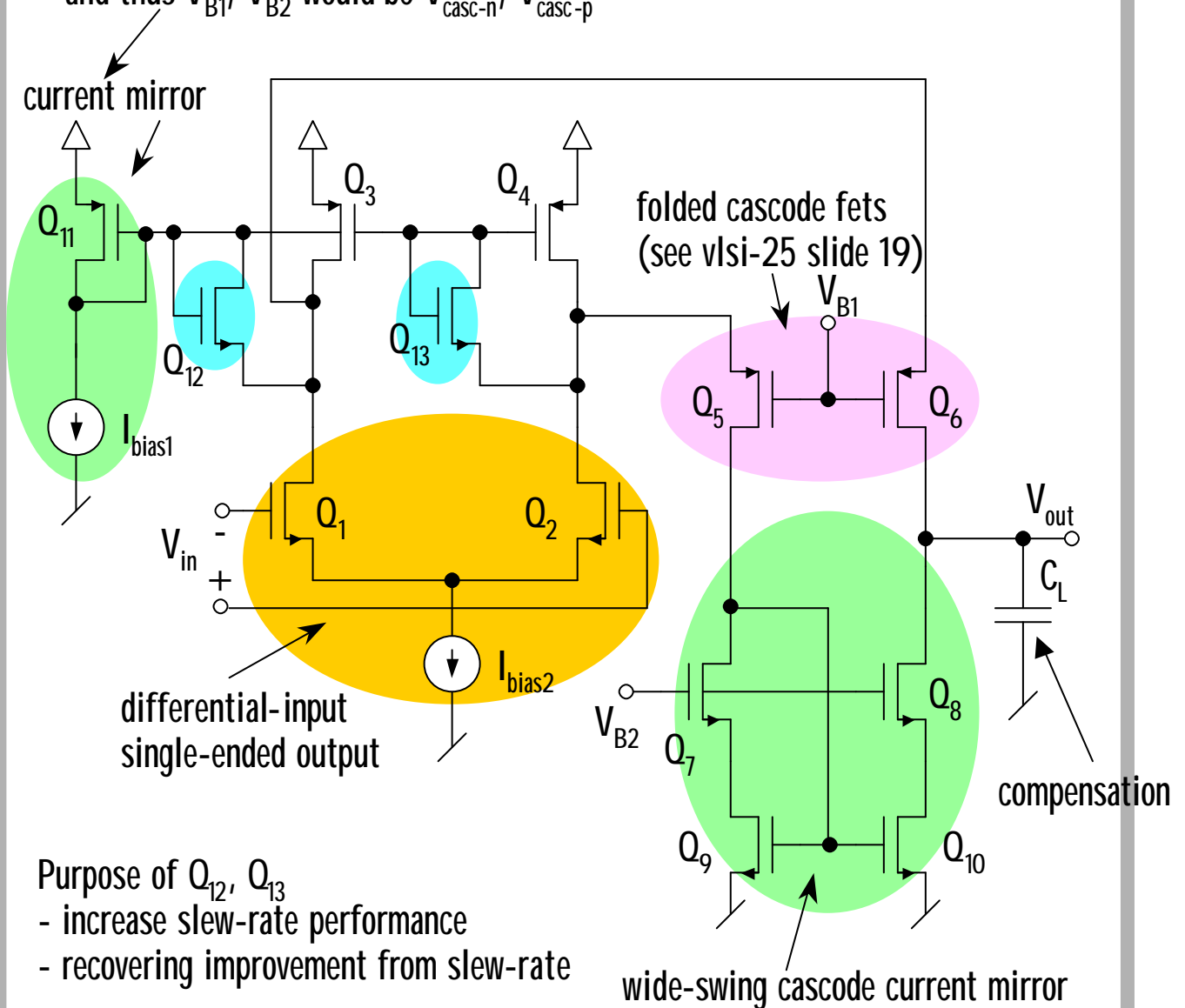may be replaced by a wide-swing constant-transconductance bias network and thus V_{B1} , V_{B2} would be V_{casc-n} , V_{casc-p}



Design hints:

- I_{bias1} and I_{bias2} should be derived from a single bias network
- any current mirrors should be designed by parallel combination of unit size fets

Folded-cascode OpAmp small-signal analysis

Assumption: g_{m5} and g_{m6} are much larger than g_{ds3} and g_{ds4}

- differential output current from drains of differential pair Q_1 and Q_2 is applied to the load capacitance
- the small-signal current from Q_1 passes directly from source to drain of Q_6 and thus to C_L (indirect for Q_2 to Q_5 and C_L)

$$A_v = \frac{V_{out}(s)}{V_{in}(s)} = g_{m1} Z_L(s) \quad (\text{for } g_{m1} = g_{m2})$$

$$A_v(s) = \frac{g_{m1} r_{out}}{1 + s r_{out} C_L} \quad r_{out} \cong \frac{g_m r_{ds}^2}{2}$$

(see vlsi-25 slide 20)

for mid-band and high frequencies $A_v \cong \frac{g_{m1}}{s C_L}$ thus the unity-gain frequency is $W_t \cong \frac{g_{m1}}{C_L}$

Design hint:

- for large load capacitances a maximal transconductance of input fets maximizes band width, use n-channel fets
- input bias current 4 times larger than cascode current (maximizing dc gain)

Lead compensation (series resistance R_C to C_L)

$$A_v(s) = \frac{g_{m1}}{\frac{1}{r_{out}} + \frac{1}{R_C + 1/sC_L}} \cong \frac{g_{m1}(1 + sR_C C_L)}{sC_L}$$

R_C can be chosen to place a zero at 1.2 times unity-gain frequency

Folded-cascode OpAmp slew-rate

- ◆ The diode connected fets Q_{12} and Q_{13} are turned off during normal operation and have almost no effect
- ◆ slew-rate limiting behavior:
 - ◆ assume there is a large differential input voltage that causes Q_1 to be turned on hard and Q_2 to be turned off
 - ◆ since Q_2 is off, all of the bias current of Q_4 will be directed to through cascode fet Q_5 through n-channel current mirror and out of the load capacitance
 - ◆ the output voltage will decrease linearly with a slew-rate given by:

$$SR \cong \frac{I_{d4}}{C_L}$$

- ◆ Q_1 and current source I_{bias} will go into triode region, moving the drain voltage of Q_1 to the negative power supply
- ◆ Q_{12} and Q_{13} clamp the drain voltages so they don't change as much during slew-rate limitation
- ◆ in addition Q_{12} and Q_{13} increase the bias currents for Q_3 and Q_4 and thus for C_L

Exercises VLSI-28

Ex ana6.2 (difficulty: medium): find reasonable fet sizes for the folded-cascode OpAmp: Assume pos/neg 2.5V power supply, power dissipation maximal 2mW, current ratio 4:1 between input and cascode fets, bias current or Q_{11} is 1/30 of Q_3 (thus ignoring it for power dissipation), maximum fet width is 300um, $L=1.6\mu\text{m}$ and $V_{\text{eff}}=0.25\text{V}$ for all except input fets, $W_1=W_2=300\mu\text{m}$, rounding widths to 10um, $CL=10\text{pF}$, $\mu_n C_{\text{ox}} = 3\mu_p C_{\text{ox}} = 96\mu\text{A}/\text{V}^2$

- find all fet sizes, unity gain frequency,
- slew-rate with and without clamp fets
- reasonable lead compensation R_C

Result: a) Q_1 to $Q_4 = 300\mu\text{m}$, $Q_5, Q_6 = 60\mu\text{m}$, Q_7 to $Q_{10} = 20\mu\text{m}$, Q_{11} to $Q_{12} = 10\mu\text{m}$, $w_t = 2\text{p}$ 38MHz

b) $SR = 32\text{V}/\mu\text{s}$,

c) $RC = 347\text{W}$ (see Johns/Martin pp271-273)

Coming Up...

- ◆ Next topic...
Comparators
- ◆ Readings for next time...
Johns&Martin: Sections 6.1 and 6.2
- ◆ Exercises:
Have a look at the exercises in *Johns&Martin*.