


# CH5 Differential amplifier

5.0 differential signal

5.1 R-load differential amplifier


5.2 Active load differential amplifier
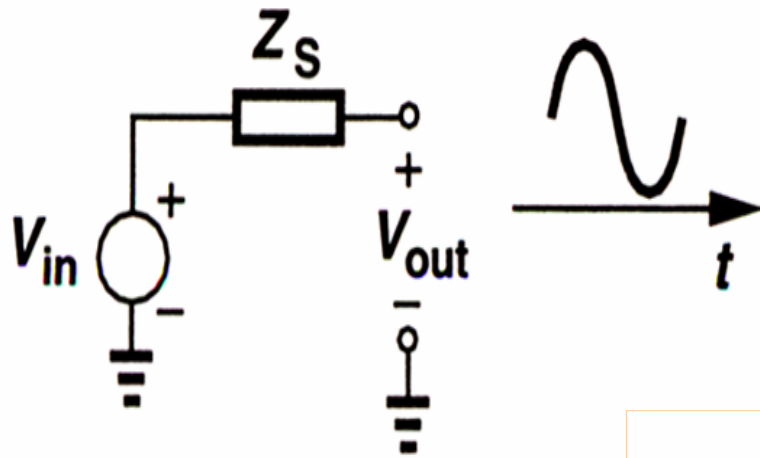
## Differential Signal versus Single Ended Signal




Single ended

Differential

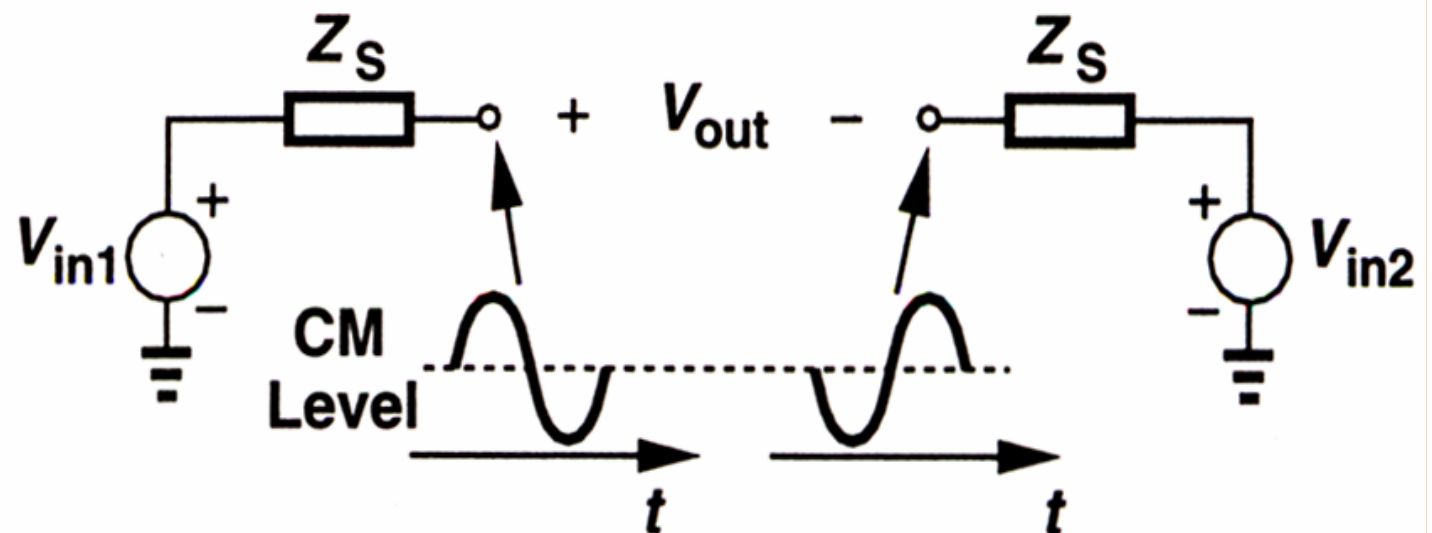

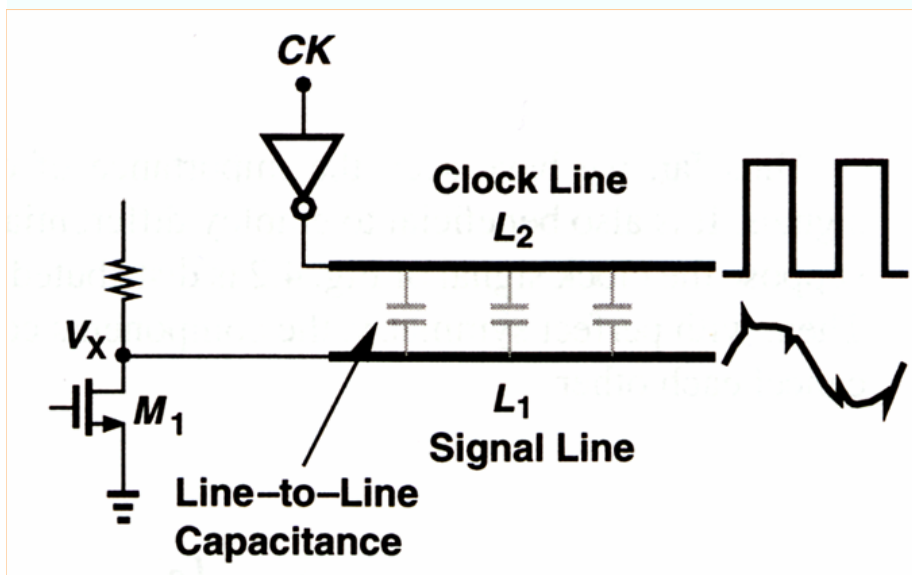
## Differential Signal

Highly immune to environmental noise (1) Digital noise  
 environmental noise => common mode => rejected by diff amp




Single ended

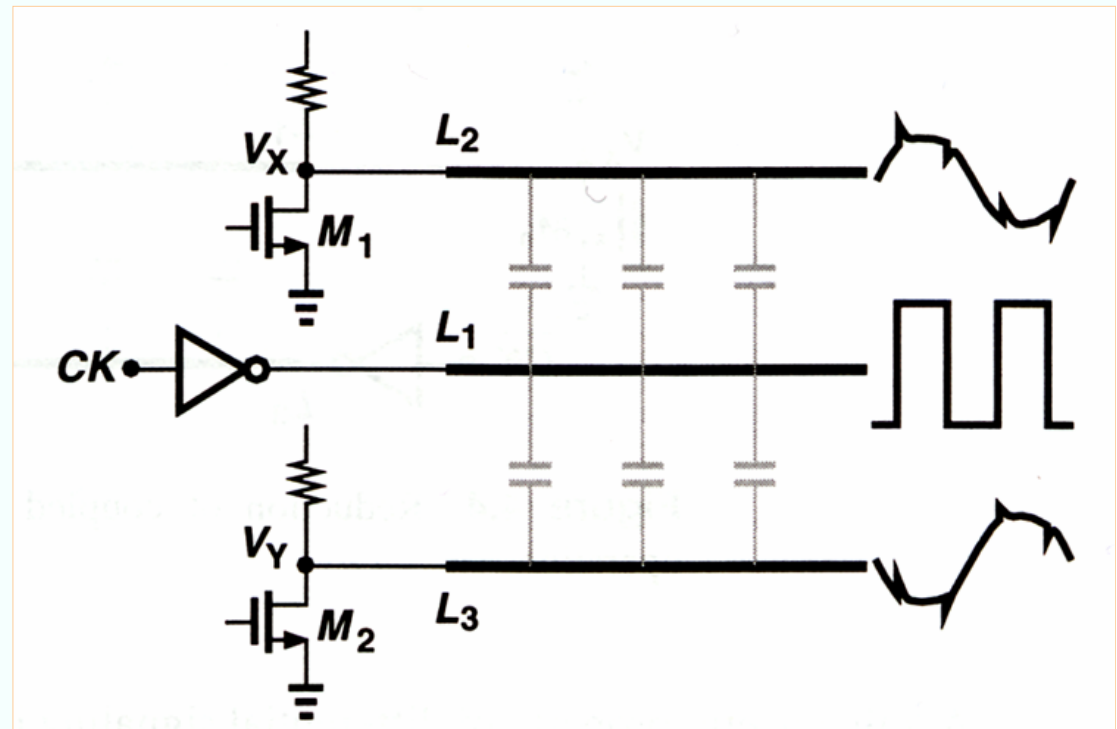


Differential
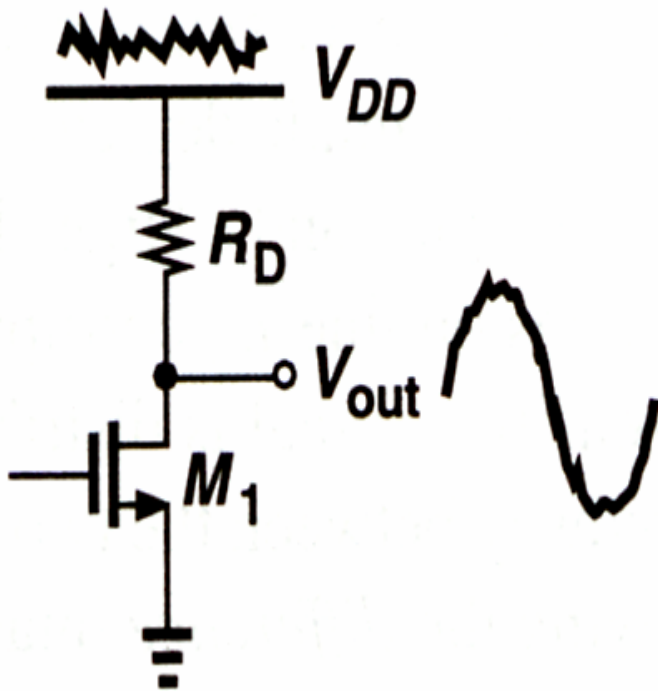
## Differential Signal


Highly immune to environmental noise (2) Supply noise



Single ended


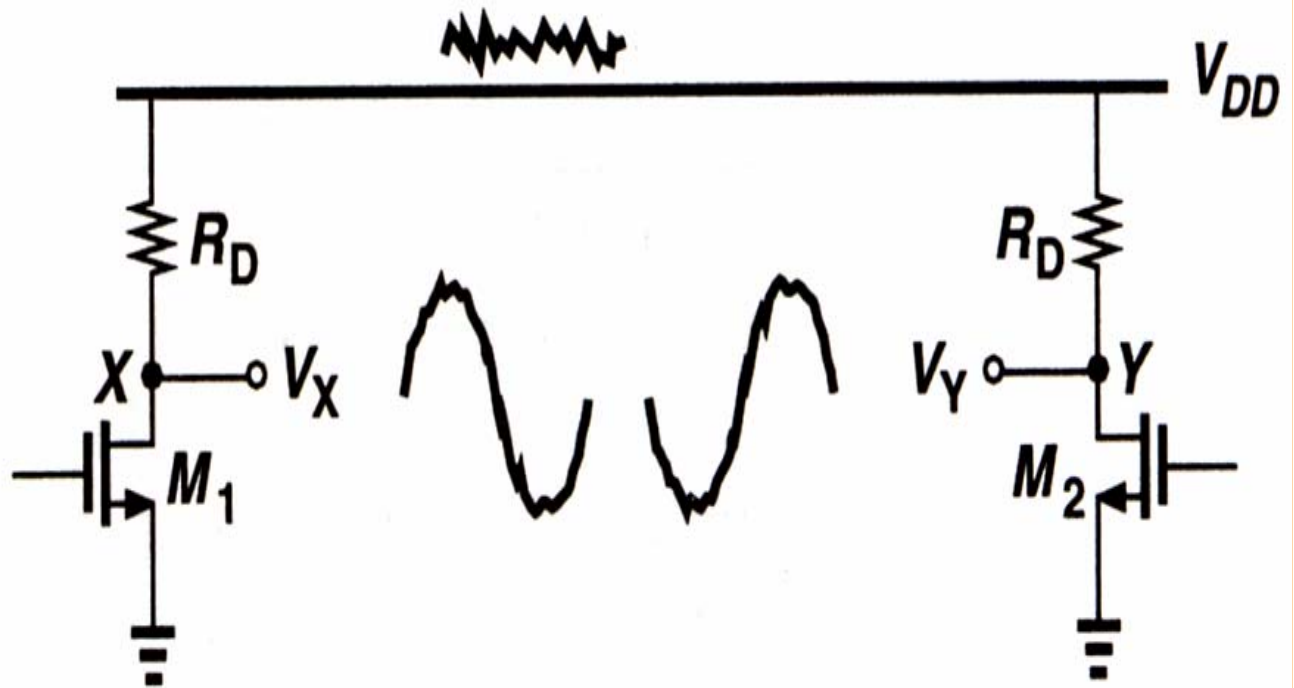



Differential

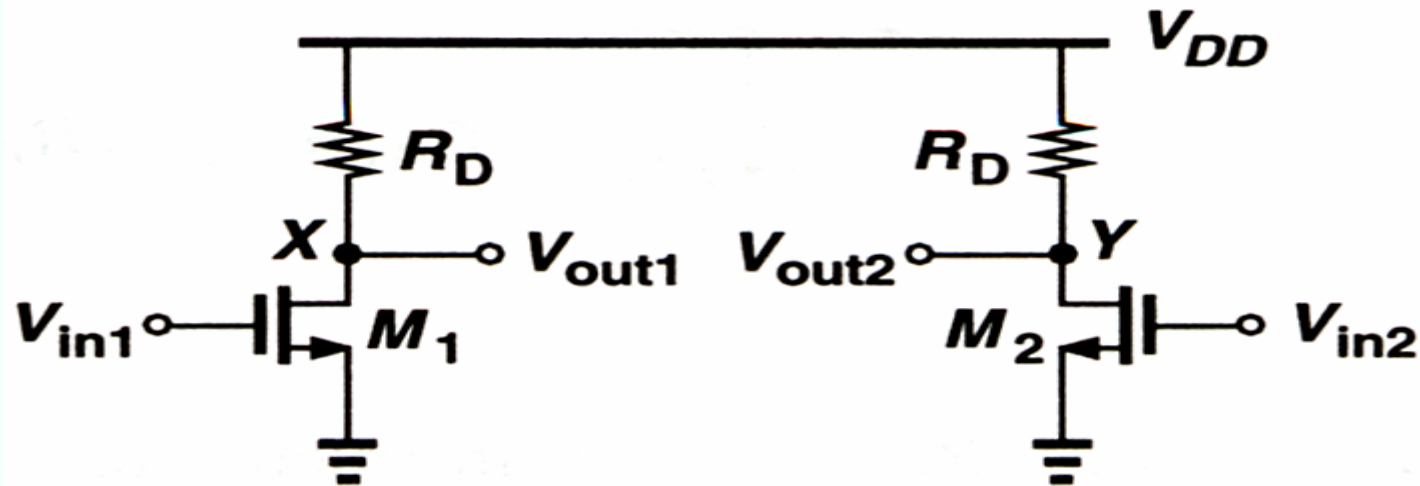

Advantage

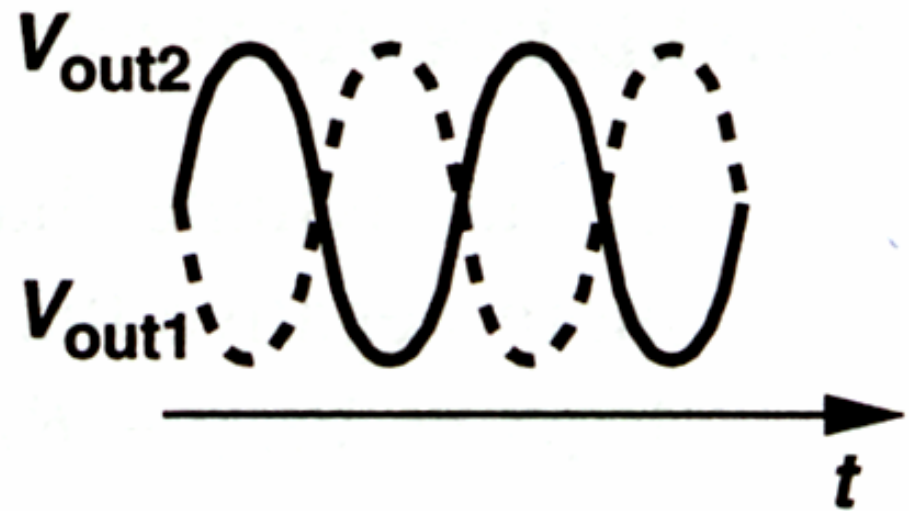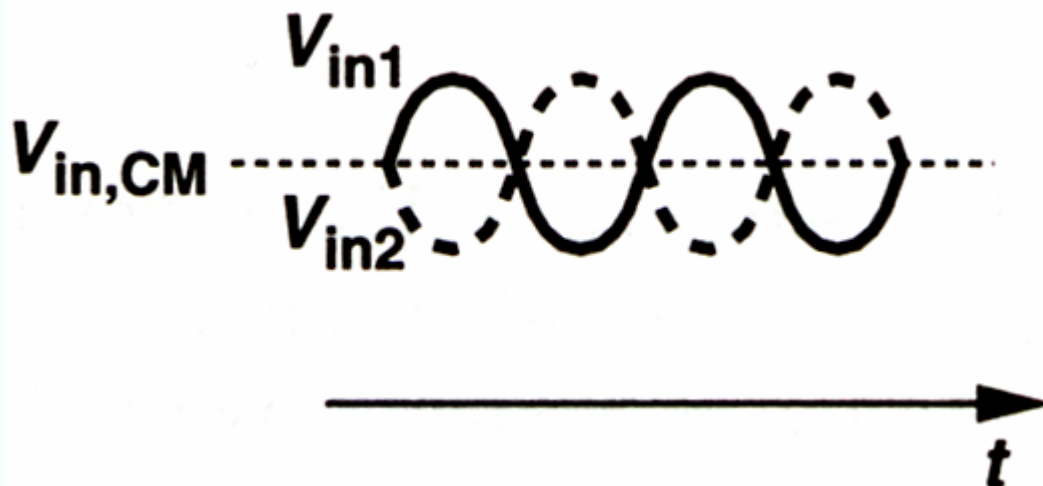
High rejection of environmental noise (digital & supply noise)



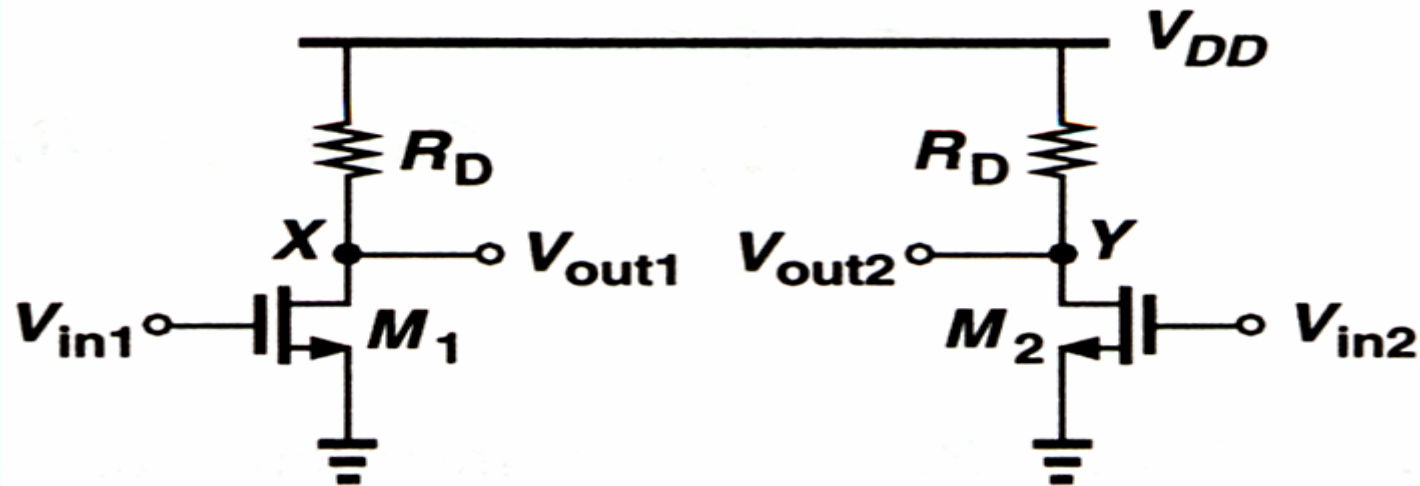


Disadvantage

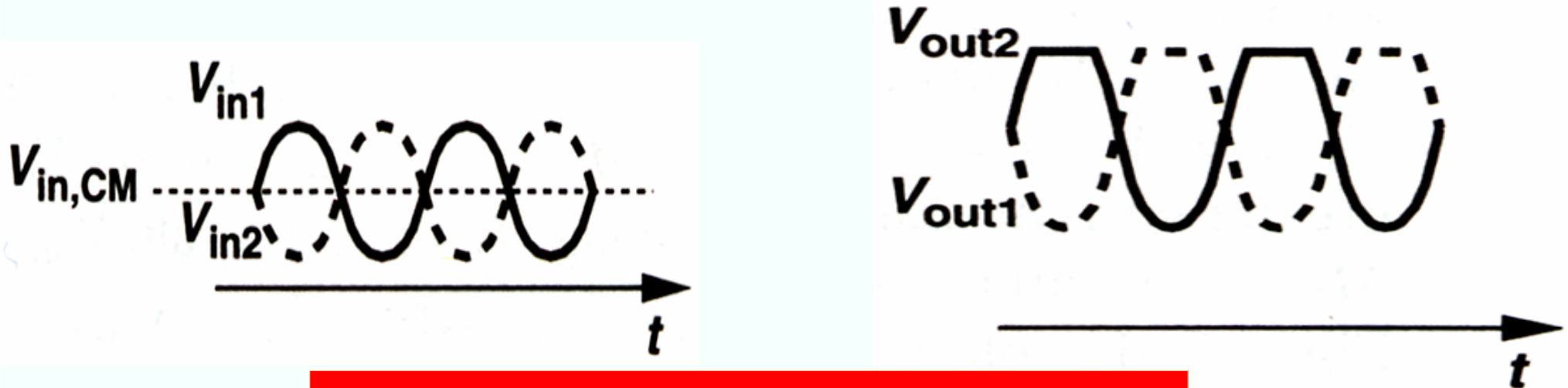Change in input common mode level ( $V_{in,cm}$ )  $\Rightarrow$  change in bias  $I$ ,  $g_m$  or clipping







$V_{out,cm}$ : sensitive to  $V_{in,cm}$

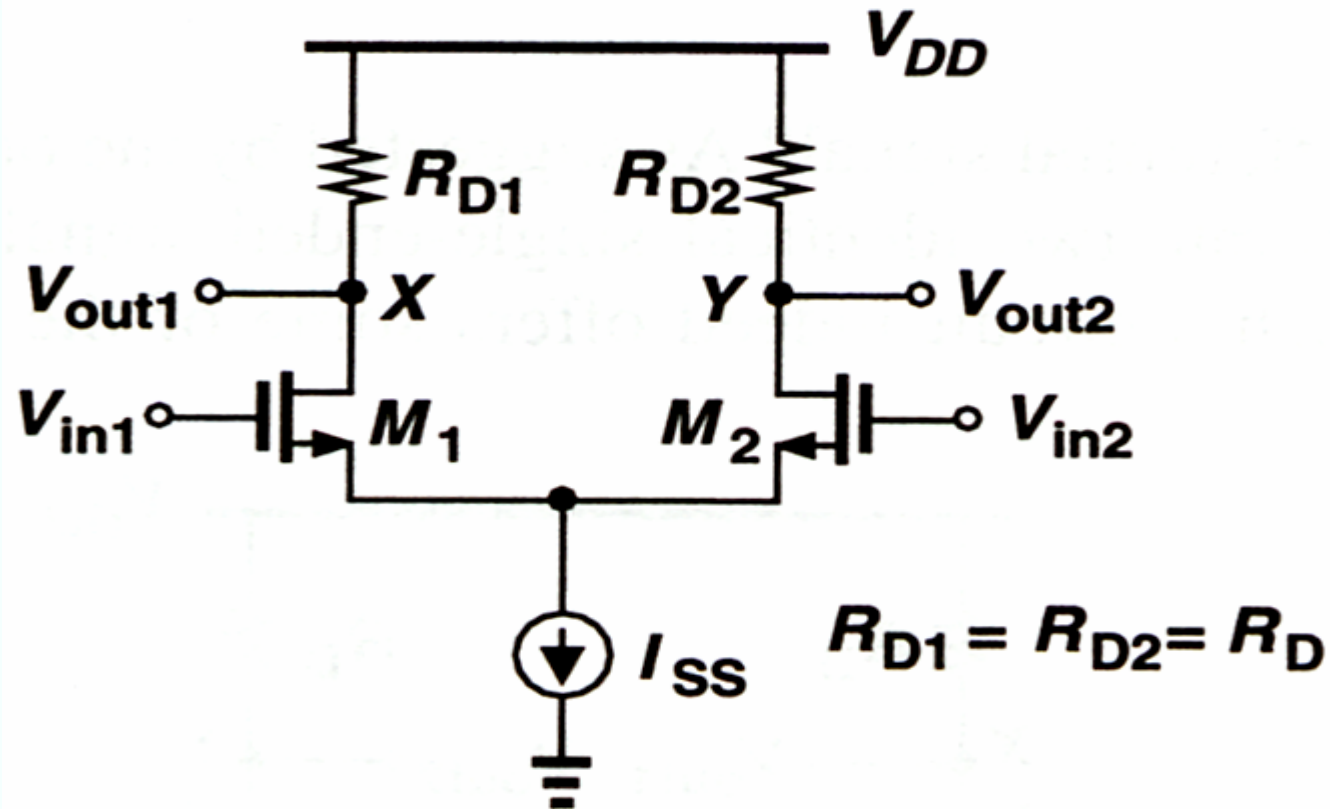

$V_{out.cm} = V_{DD} - 0.5 \times I_{SS} \times R_D$  : independent of  $V_{in.cm}$

( $V_{out.max} = V_{DD}$ ,  $V_{out.min} = V_{DD} - I_{SS} \times R_D$  : both independent of  $V_{in.cm}$ )

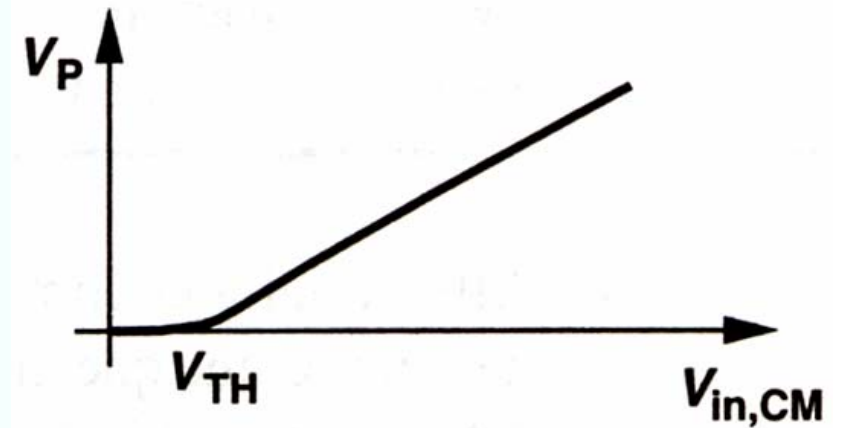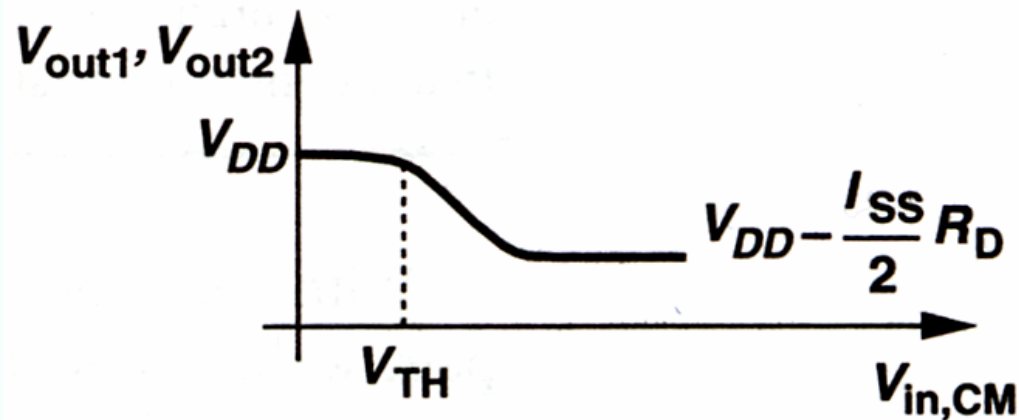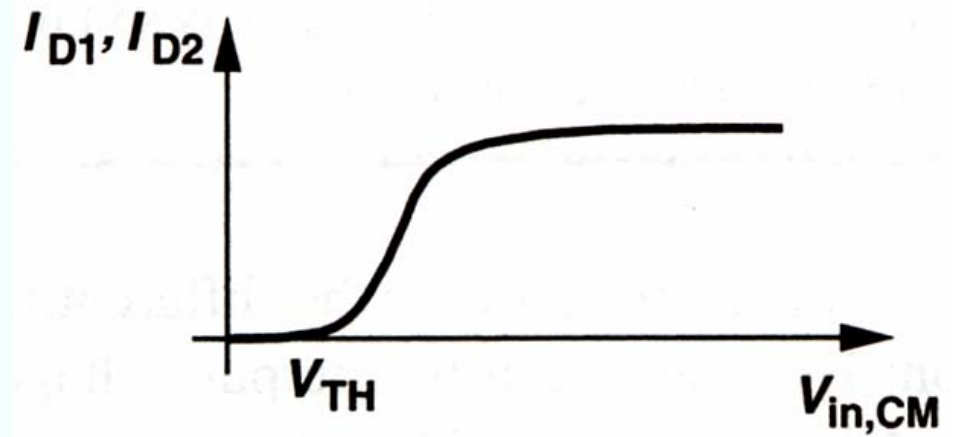
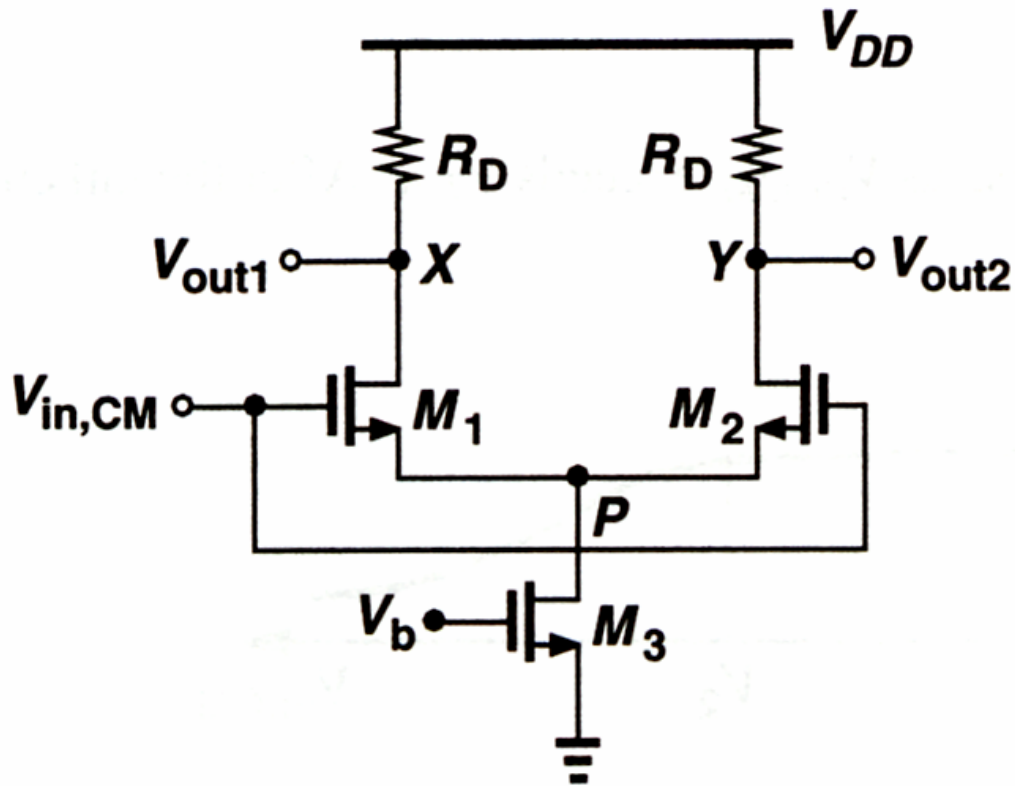
Small-signal common mode gain  $A_{vc} = 0$



Active input CM V range

**Active input common mode range:**  
range of  $V_{in,cm}$  with all MOS in saturation  $\rightarrow$  High  $A_{vd}$
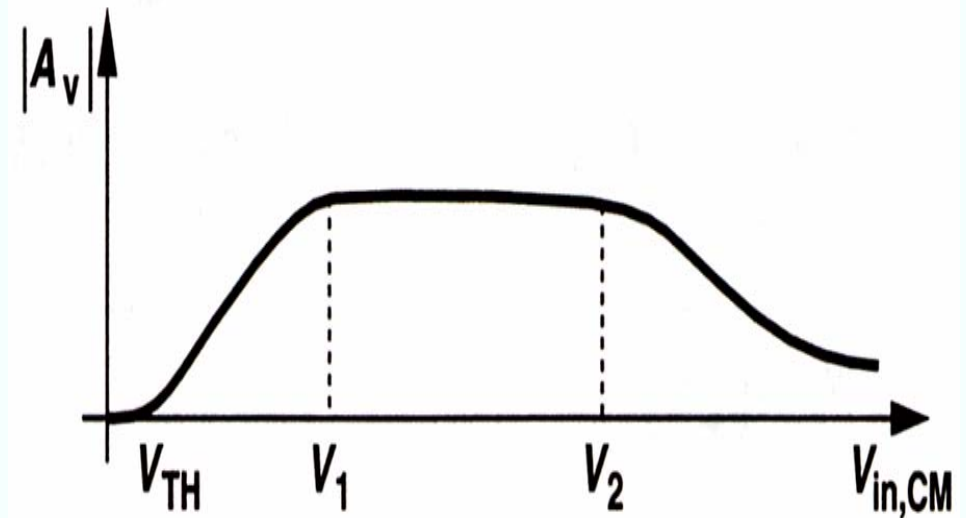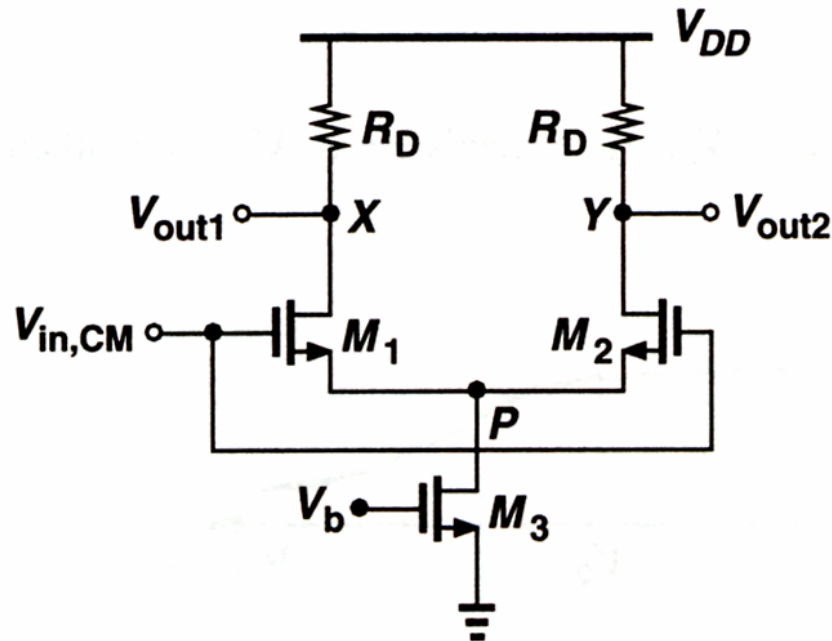
$$V_{GS1} + (V_{GS3} - V_{TH3}) \leq V_{in,CM} \leq \min \left[ V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH}, V_{DD} \right]$$



Small-signal diff mode voltage gain

Razavi