
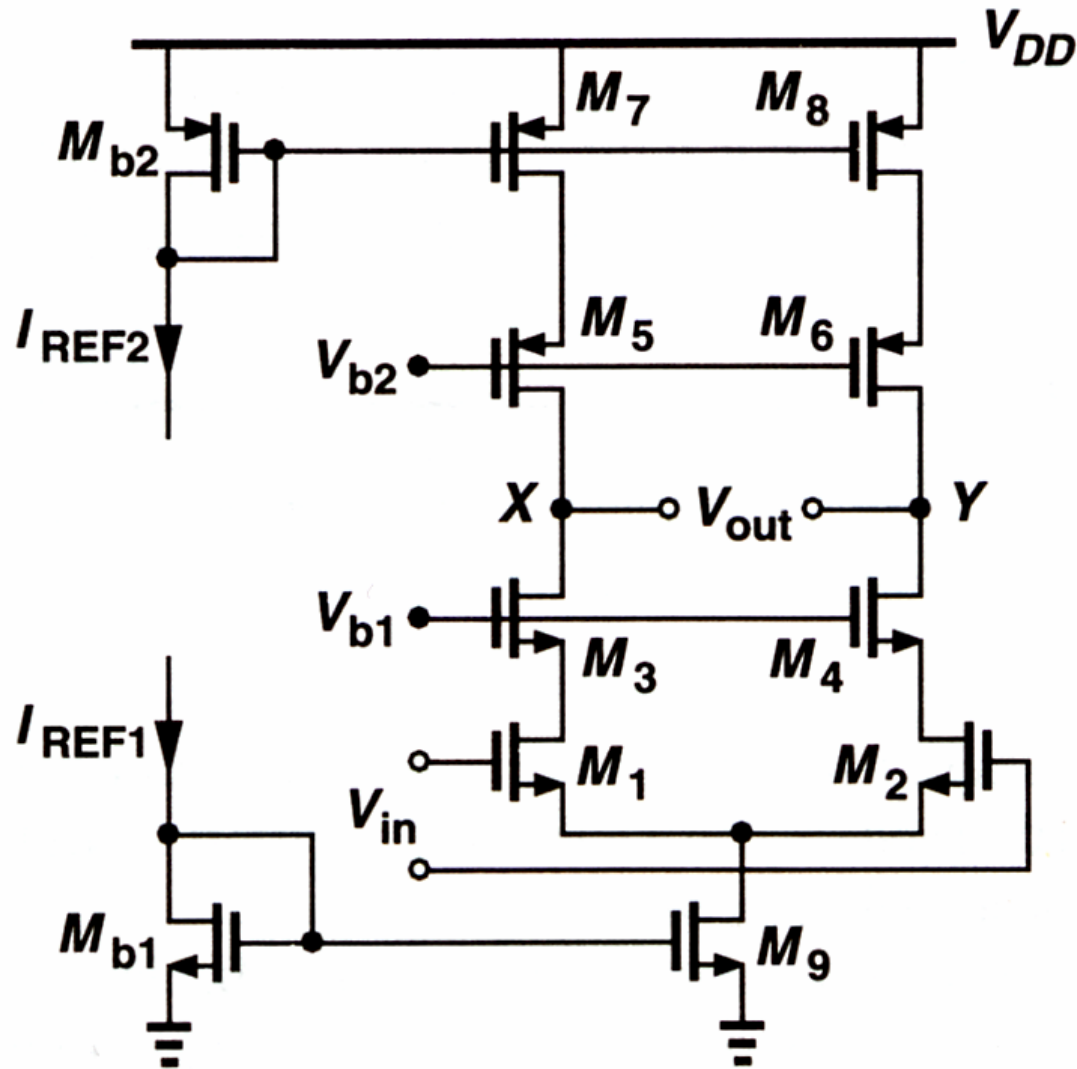


3. Folded Cascode OP amp

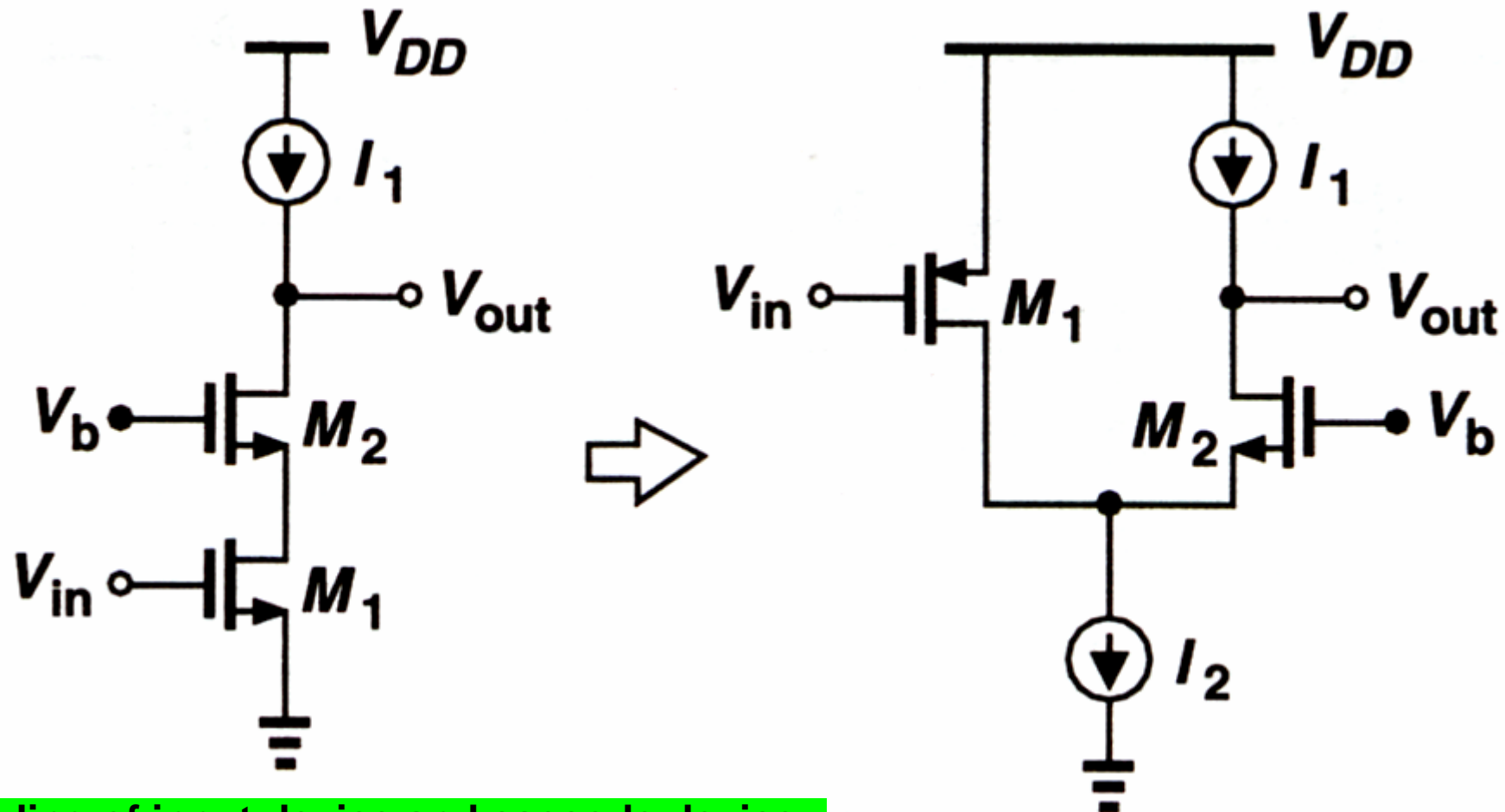

Telescopic OP amp:

- (1) Large gain
- (2) High speed
small parasitic cap \rightarrow high freq non-dominant pole
- (3) Small ICMR
- (4) Small OVR
- (5) Not suitable for unity gain buffer




cascading of input device and cascode device


V_b affects both max V_{in} and min V_{out}
 (max $V_{in} = V_b - V_{dsat}$, min $V_{out} = V_b - V_{th}$)
 Tradeoff between V_{in} and V_{out} ranges

NO cascading of input device

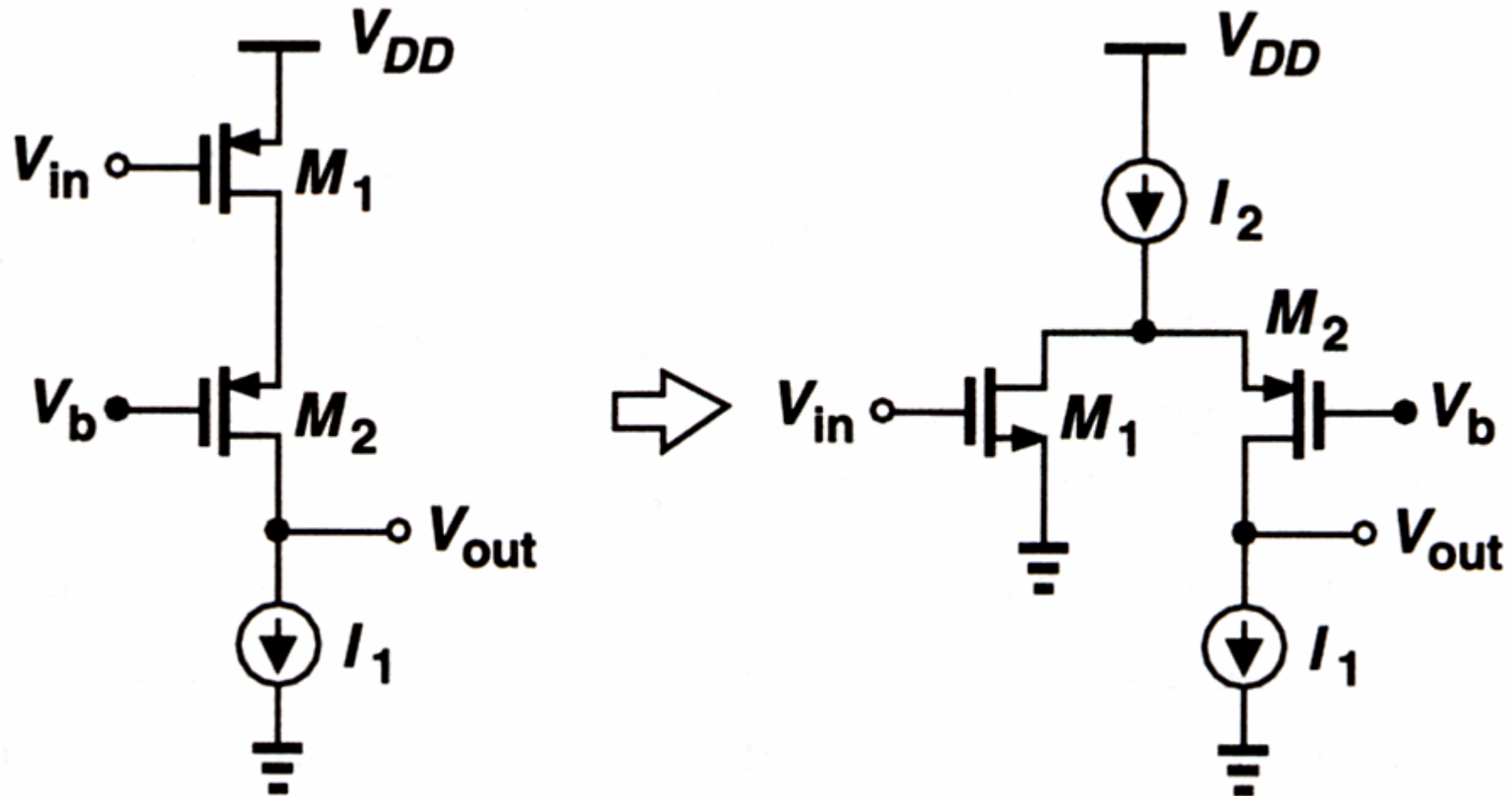V_b affects V_{out} range only
 (min V_{in} : $V_{dsat} - V_{th}$,
 min $V_{out} = V_b - V_{th} = 2 V_{dsat}$), no tradeoff



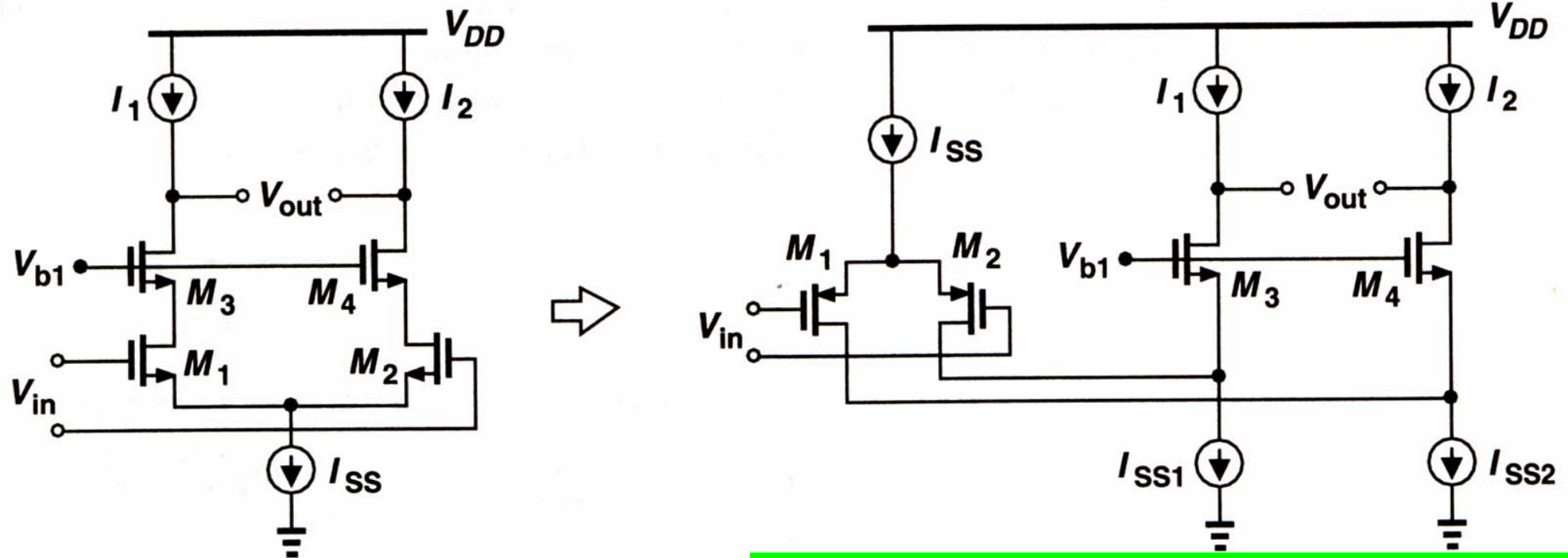$A_v = g_{m1} \times R_{out}$
(about the same in both cases)



NO cascading of input device and cascode device

**V_{b1} affects both max V_{in} and min V_{out}
 (max $V_{in} = V_b - V_{dsat}$, min $V_{out} = V_b - V_{th}$)
 Tradeoff between V_{in} and V_{out} ranges**



**V_{b1} affects V_{out} range only
 (min V_{in} : $V_{dsat} - V_{th}$,
 min $V_{out} = V_b - V_{th} = 2 V_{dsat}$), no tradeoff**


$A_v = g_{m1} \times R_{out}$ (about the same in both cases)

$R_{out}(\text{left}) = g_{m3} r_{o3} r_{o1}$, $R_{out}(\text{right}) = g_{m3} r_{o3} (r_{o2} \parallel r_{oSS1})$


Telescopic OP amp의 단점:

- (1) limited output swing, limited input CM range
- (2) limited swing in unity-gain feedback configuration

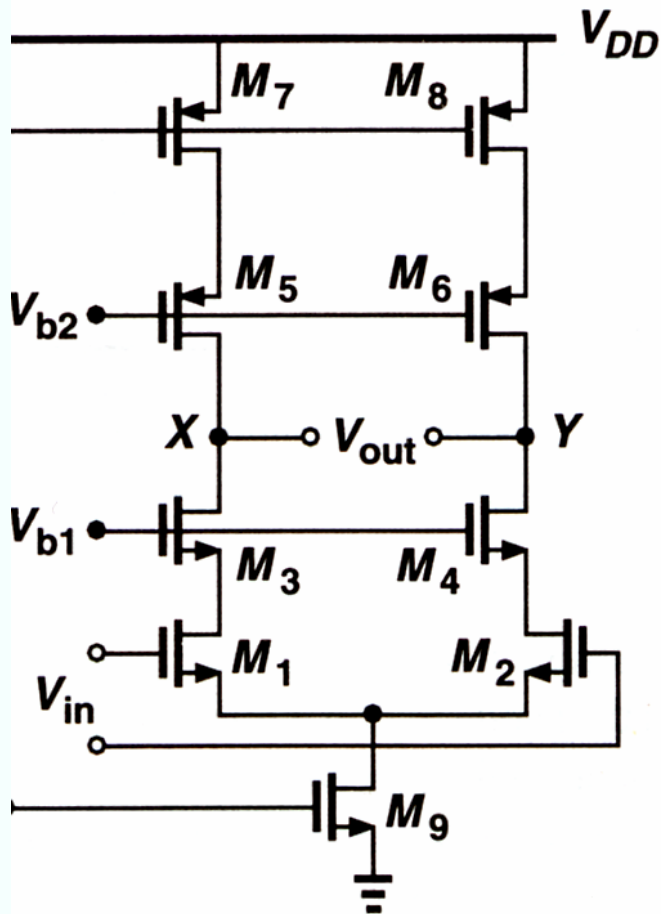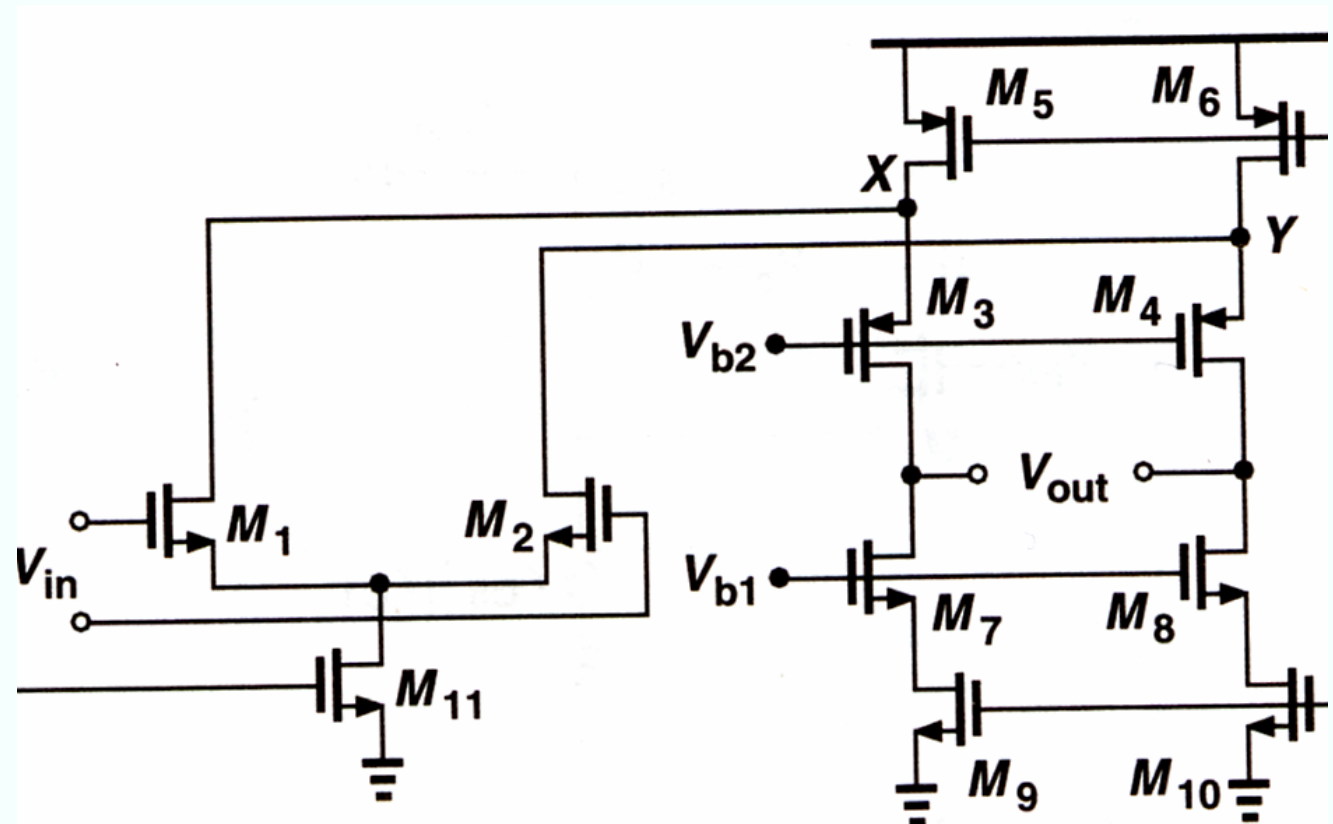**Telescopic****Folded cascode**

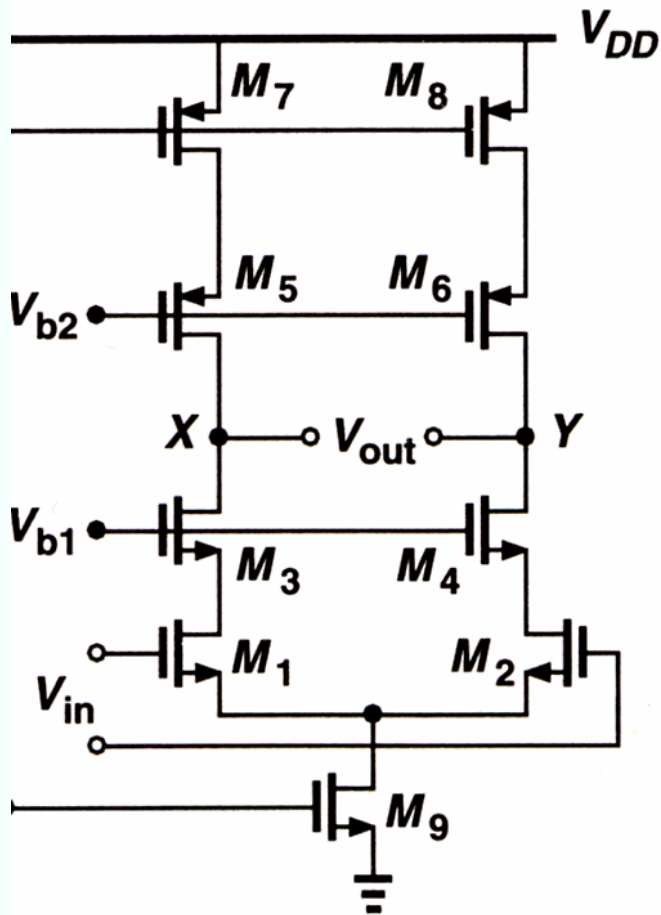


Telescopic

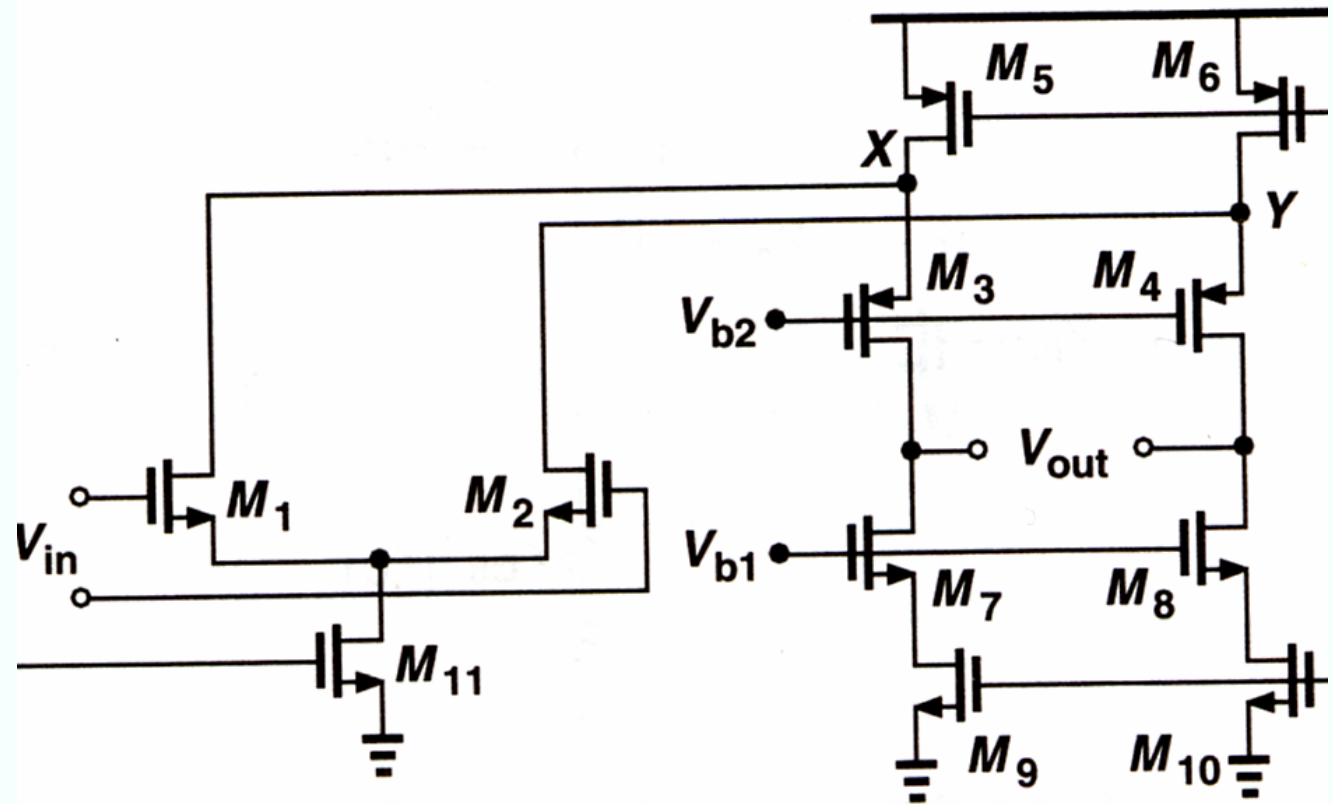


Folded cascode

Input Common mode voltage range

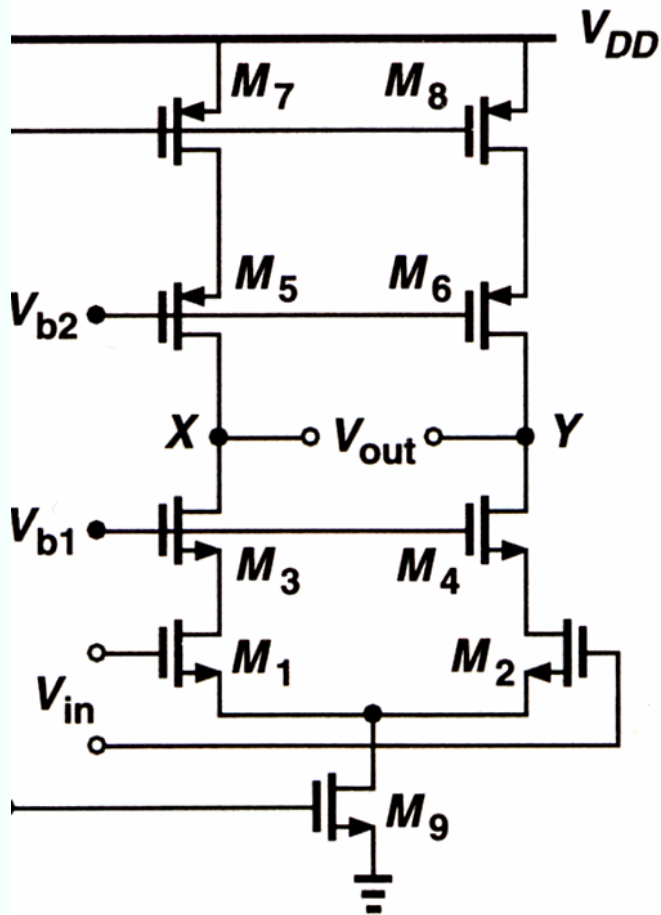- (1) Telescopic: $2 V_{DSAT} + V_{TH}$, $V_{b1} - V_{DSAT}$ ($2 V_{DSAT} + V_{TH}$)
- (2) Folded cascode: $2 V_{DSAT} + V_{TH}$, $V_{G56} + V_{TH}$ ($V_{DD} - V_{DSAT}$)




Telescopic

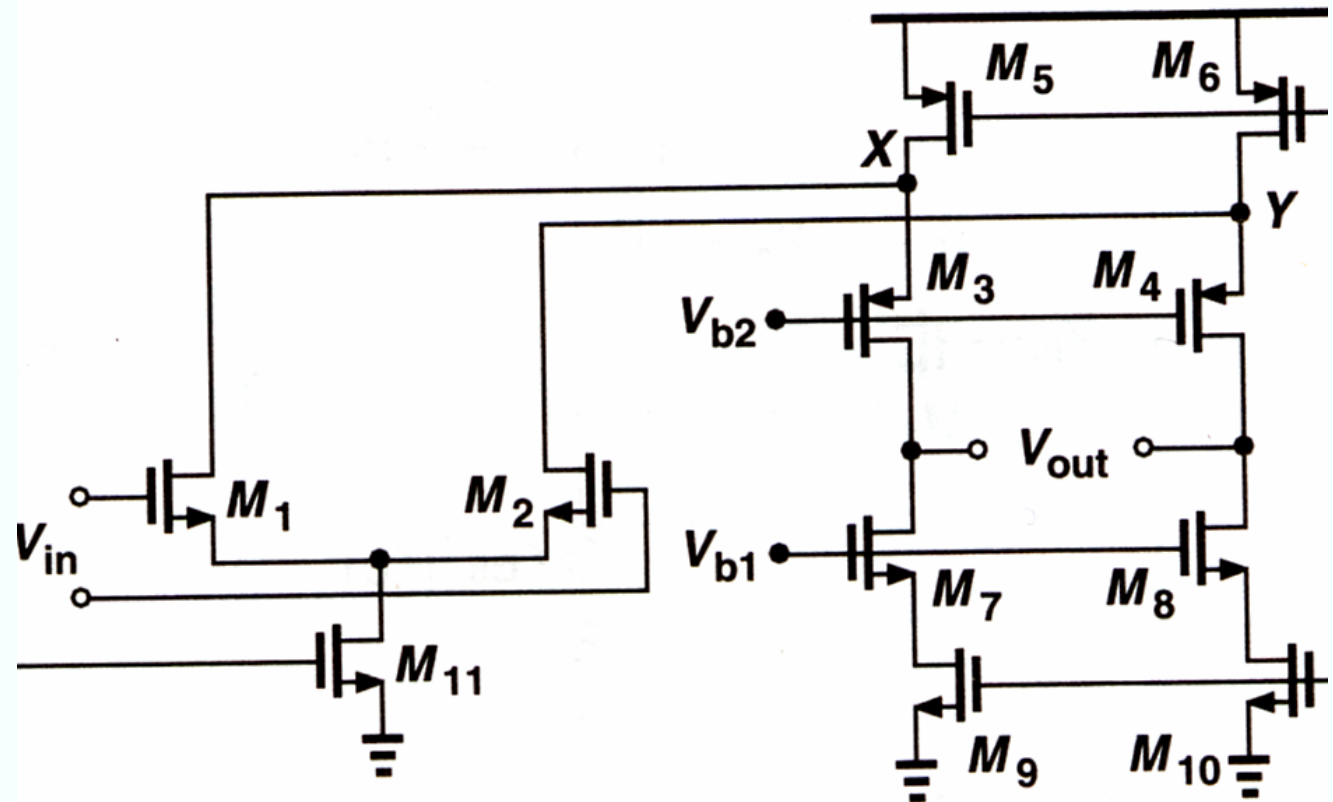


Folded cascode

Output voltage range

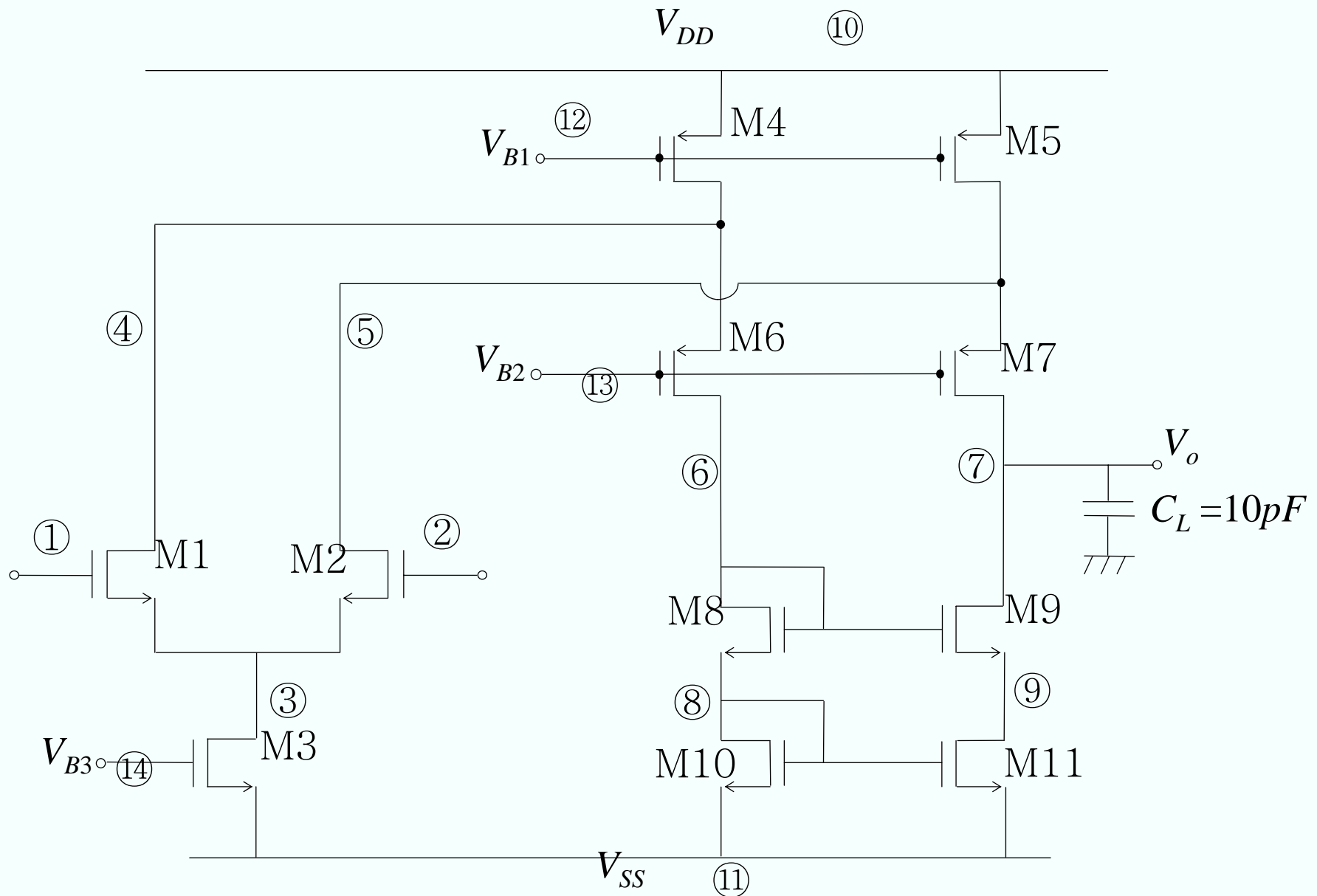- (1) Telescopic: $V_{b1} - V_{th}$, $V_{b2} + V_{th}$ ($3 V_{dsat} + V_{th}$, $V_{DD} - 2 V_{dsat}$)
- (2) Folded cascode: $V_{b1} - V_{th}$, $V_{b2} + V_{th}$ ($2 V_{dsat}$, $V_{DD} - 2 V_{dsat}$)




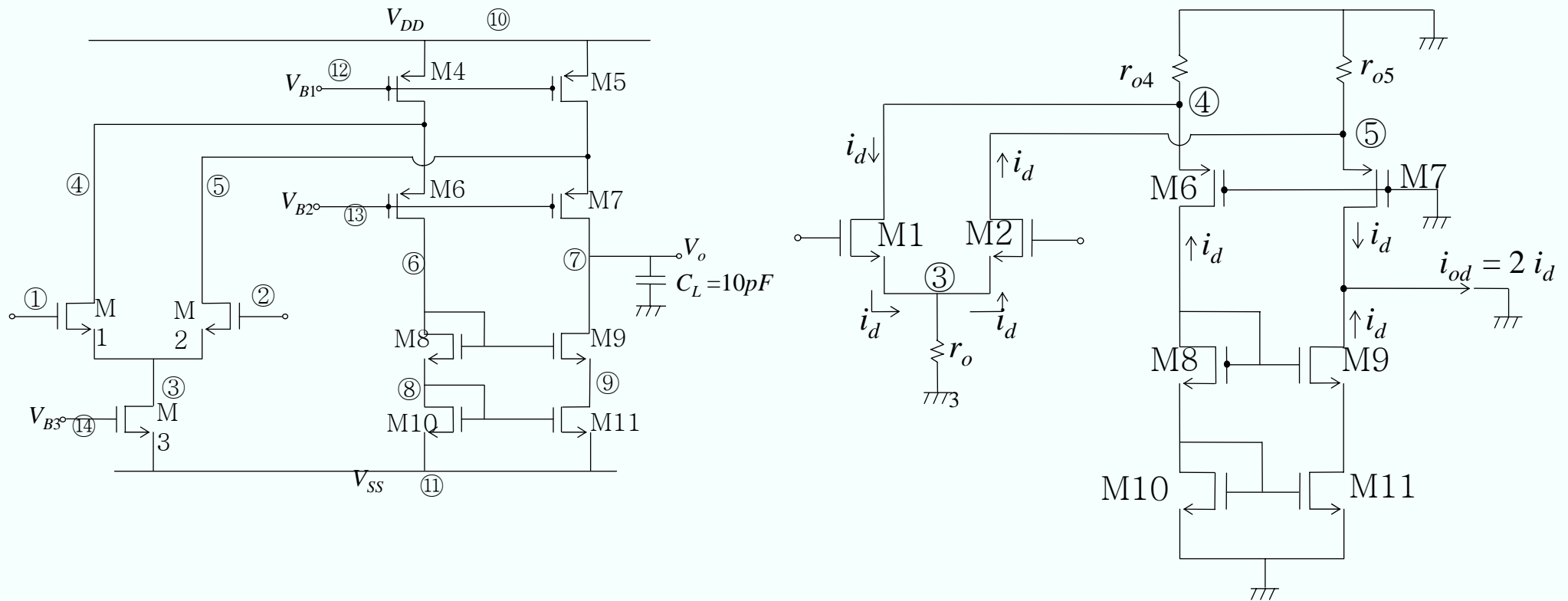


Small-signal analysis

$$i_d = \frac{v_{id}}{r_{s1} + r_{s2}} = \frac{1}{2} g_{m1} v_{id}$$
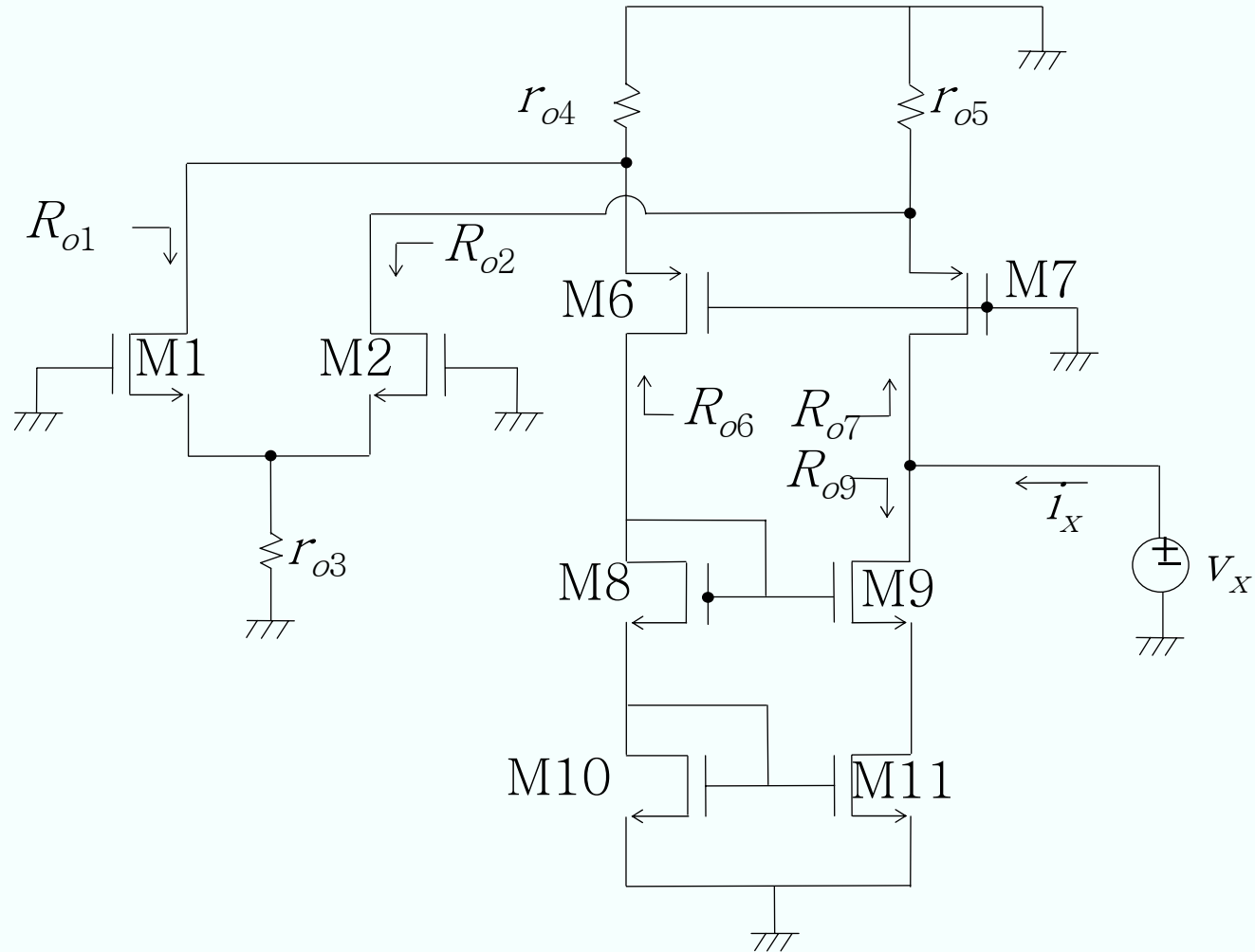
$$G_{md} = \frac{i_{od}}{v_{id}} = \frac{2i_d}{v_{id}} = g_{m1}$$


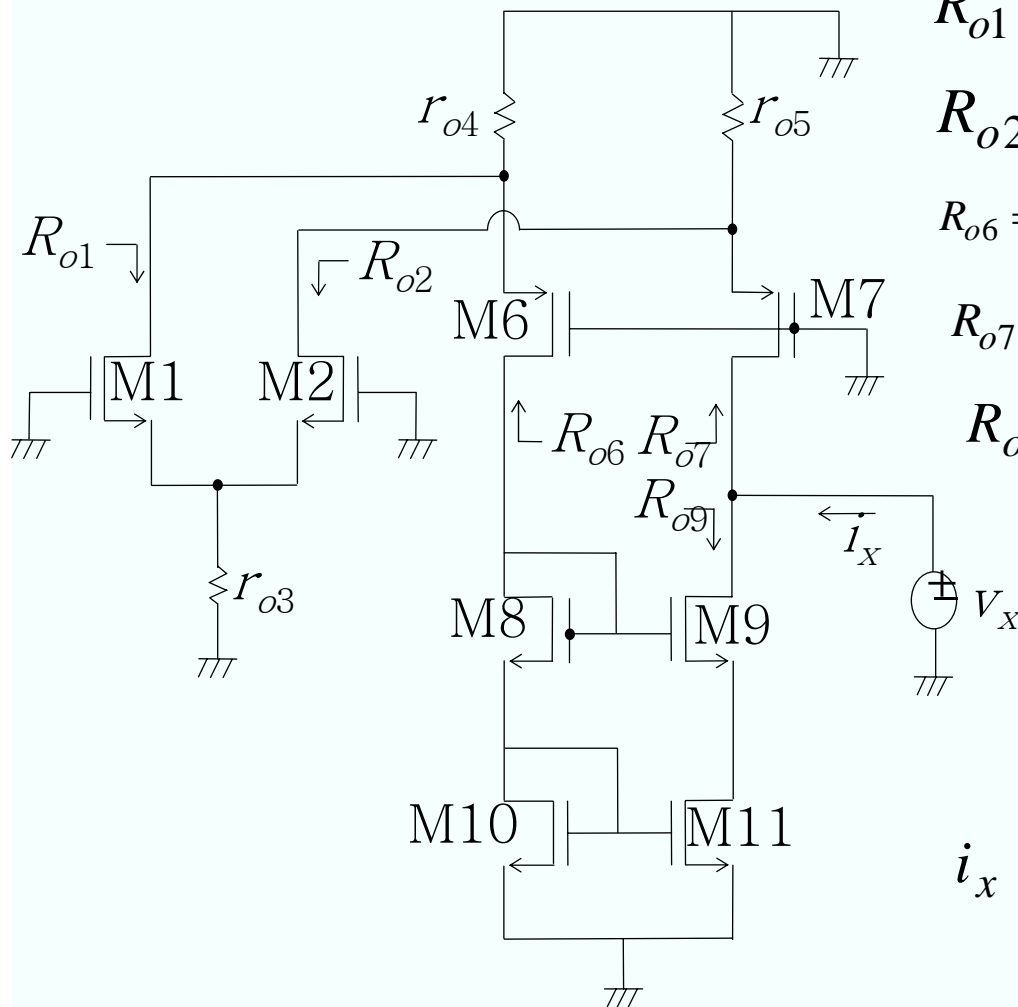
$$R_o = \frac{v_x}{i_x} = \left\{ g_{m7} r_{o7} \cdot (r_{o2} \parallel r_{o5}) \right\} \parallel \left\{ g_{m9} r_{o9} \cdot r_{o11} \right\}$$



$$R_{o1} = g_{m1}r_{o1} \cdot (r_{s2} \parallel r_{o3}) + r_{o1} + (r_{s2} \parallel r_{o3}) \approx 2r_{o1}$$

$$R_{o2} = 2r_{o2}$$

$$R_{o6} = g_{m6}r_{o6} \cdot (R_{o1} \parallel r_{o4}) + r_{o6} + (R_{o1} \parallel r_{o4}) \approx g_{m6}r_{o6} \cdot (R_{o1} \parallel r_{o4})$$

$$R_{o7} = g_{m7}r_{o7} \cdot ((2r_{o2}) \parallel r_{o5}) = R_{o6}$$

$$R_{o9} = g_{m9}r_{o9} \cdot r_{o11} + r_{o9} + r_{o11} \approx g_{m9}r_{o9} \cdot r_{o11}$$

$$i_x = i_{x7} + i_{x9}$$


$$i_{x9} = \frac{v_x}{R_{o9}}$$

$$i_{x7} = \frac{v_x}{R_{o7}} \cdot \left(1 + \frac{r_{o5}}{r_{o5} + R_{o2}} \right) \approx \frac{v_x}{(g_{m7}r_{o7}) \cdot (r_{o2} \parallel r_{o5})}$$

$$i_x = i_{x7} + i_{x9} = \frac{v_x}{(g_{m7}r_{o7}) \cdot (r_{o2} \parallel r_{o5})} + \frac{v_x}{g_{m9}r_{o9} \cdot r_{o11}}$$

$$= \frac{v_x}{\{g_{m7}r_{o7} \cdot (r_{o2} \parallel r_{o5})\} \parallel \{g_{m9}r_{o9} \cdot r_{o11}\}}$$

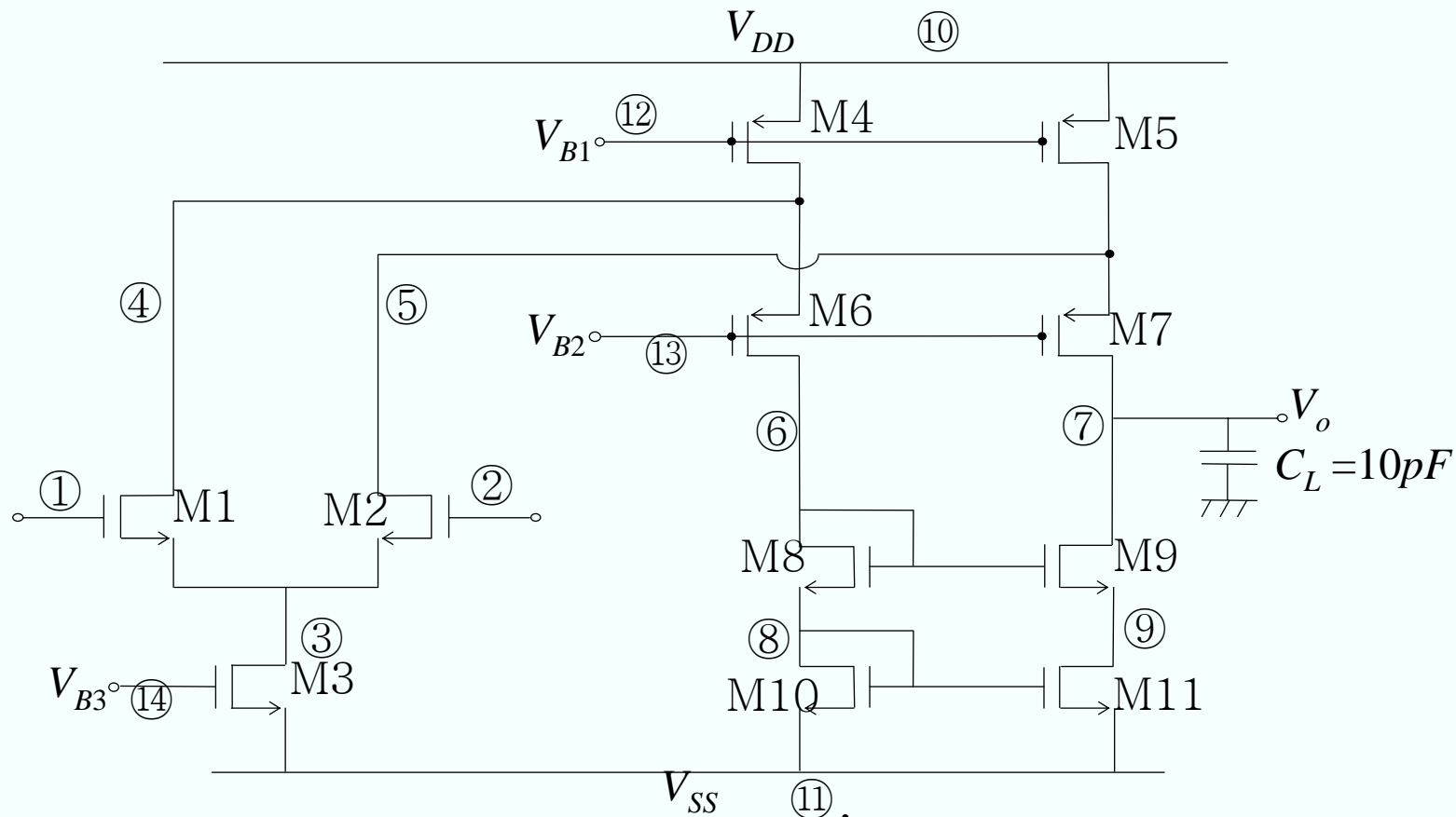
$$R_o = \frac{v_x}{i_x} = \{g_{m7}r_{o7} \cdot (r_{o2} \parallel r_{o5})\} \parallel \{g_{m9}r_{o9} \cdot r_{o11}\}$$



$$G_{mc} \triangleq \frac{i_{oc}}{v_{ic}} = - \frac{r_{s8} + r_{s10}}{(g_{m6} r_{o6}) \cdot (r_{o1} \parallel r_{o4}) \cdot 2r_{o3}}$$

No mismatch


$$CMRR \triangleq \left| \frac{A_{vd}}{A_{vc}} \right| = 2g_{m1} r_{o3} \cdot g_{m6} r_{o6} \cdot \frac{(r_{o1} \parallel r_{o4})}{(r_{s8} + r_{s10})}$$

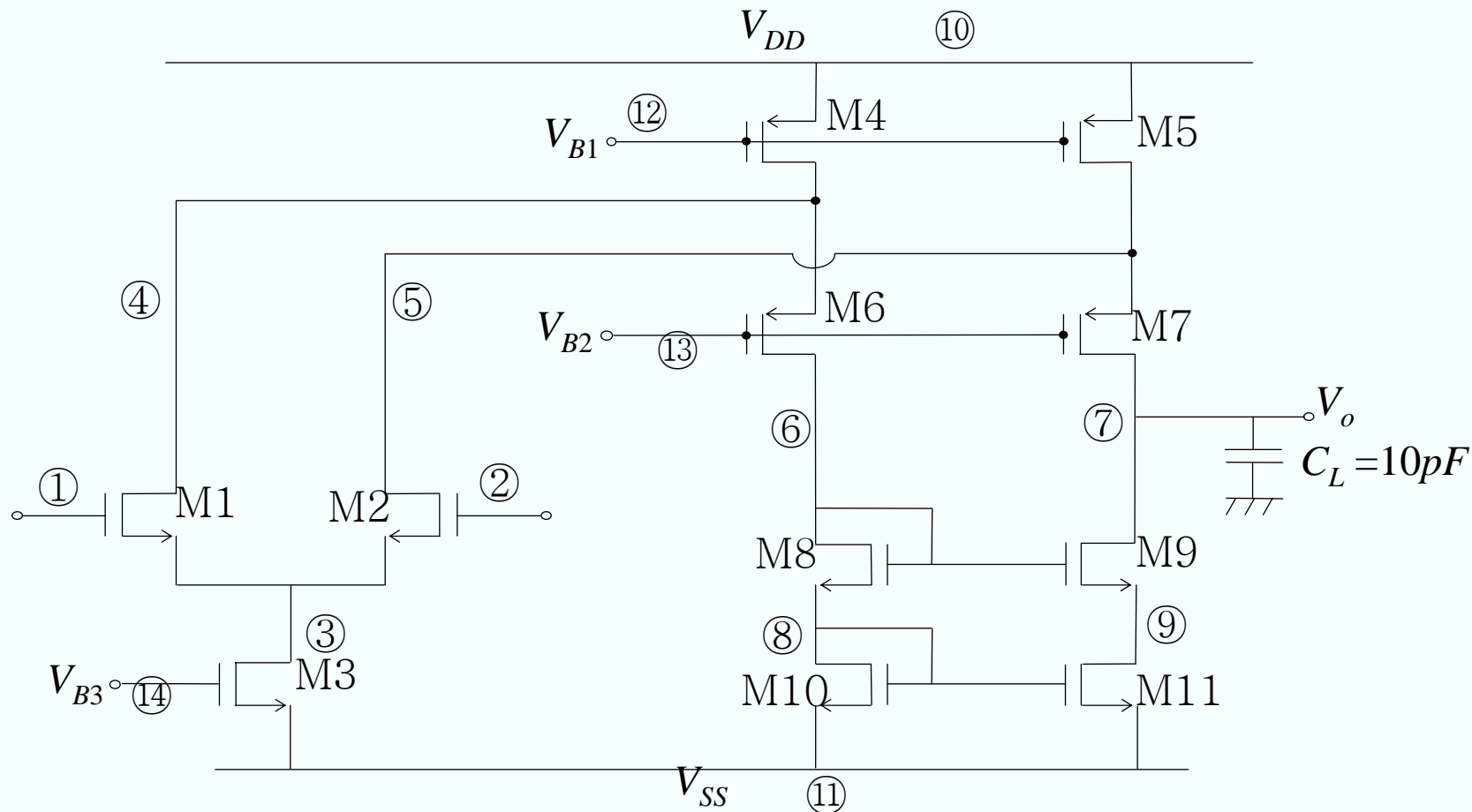

Active input common mode voltage range

$$V_{SS} + V_{DSAT3} + V_{GS1} = V_{SS} + V_{DSAT3} + V_{DSAT1} + V_{THn1}$$

$$V_{DD} - |V_{DSAT4}| + V_{THn1}$$

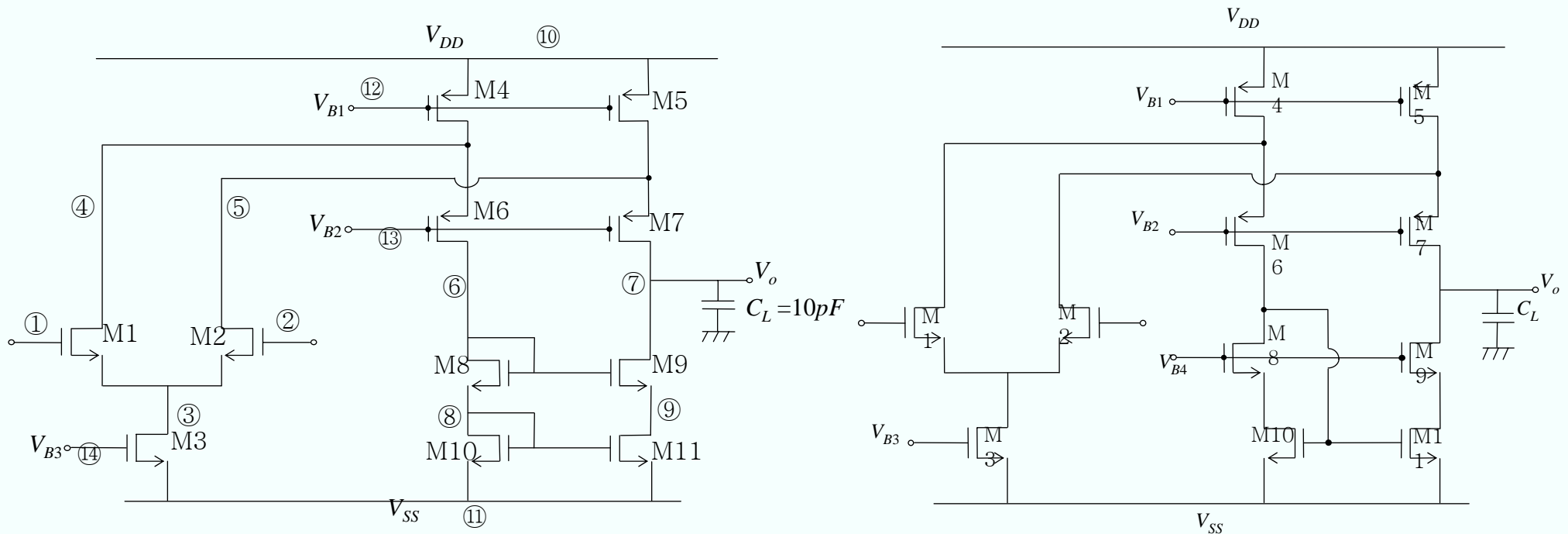

Output Voltage range (min, max)

$$= V_{SS} + V_{DSAT\ 11} + V_{DSAT\ 9} + V_{THn\ 11}$$

$$V_{B2} + |V_{THp\ 7}|$$

$$= V_{SS} + V_{DSAT\ 11} + V_{DSAT\ 9}$$

$$V_{B2} + |V_{THp\ 7}|$$

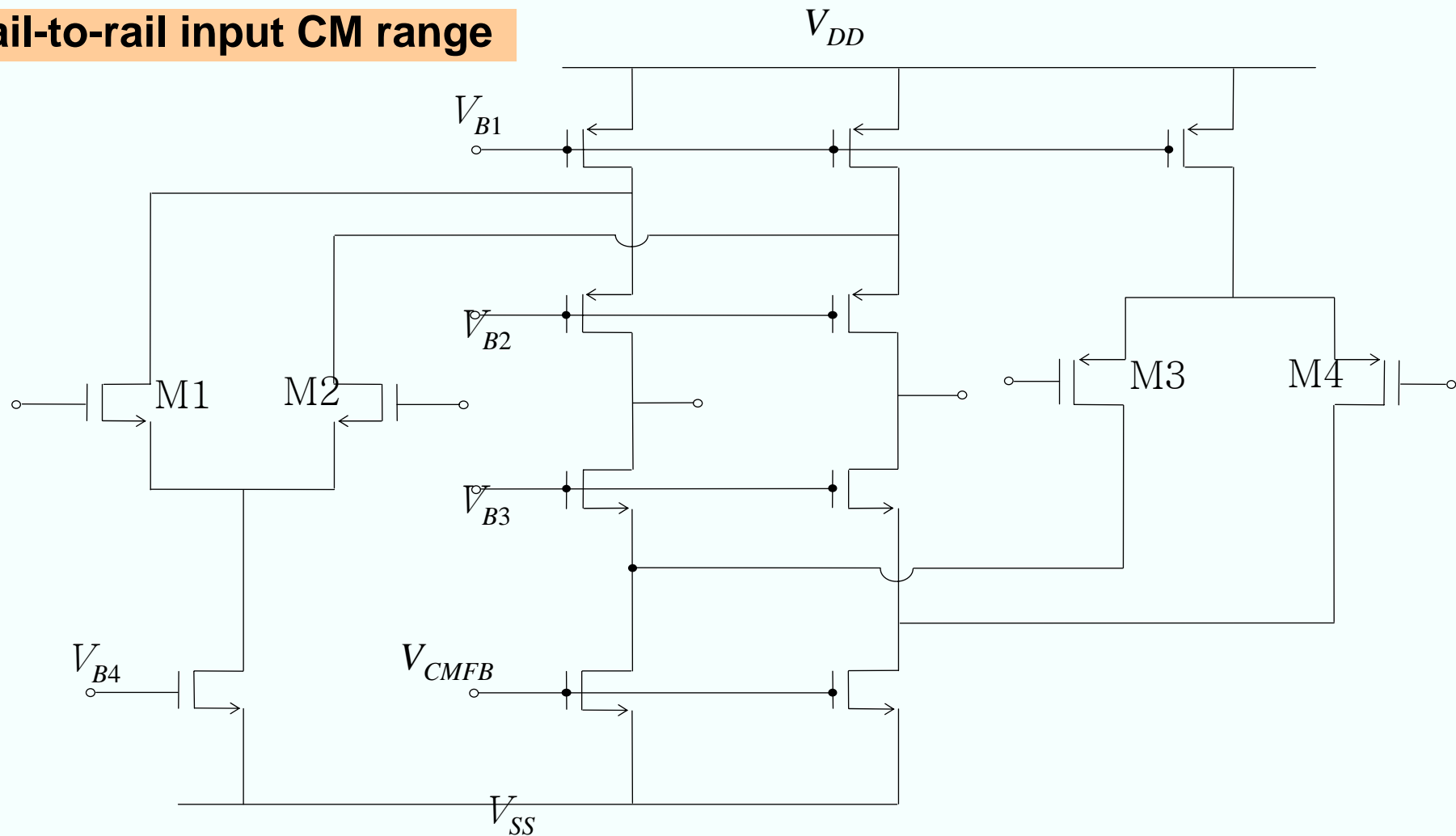
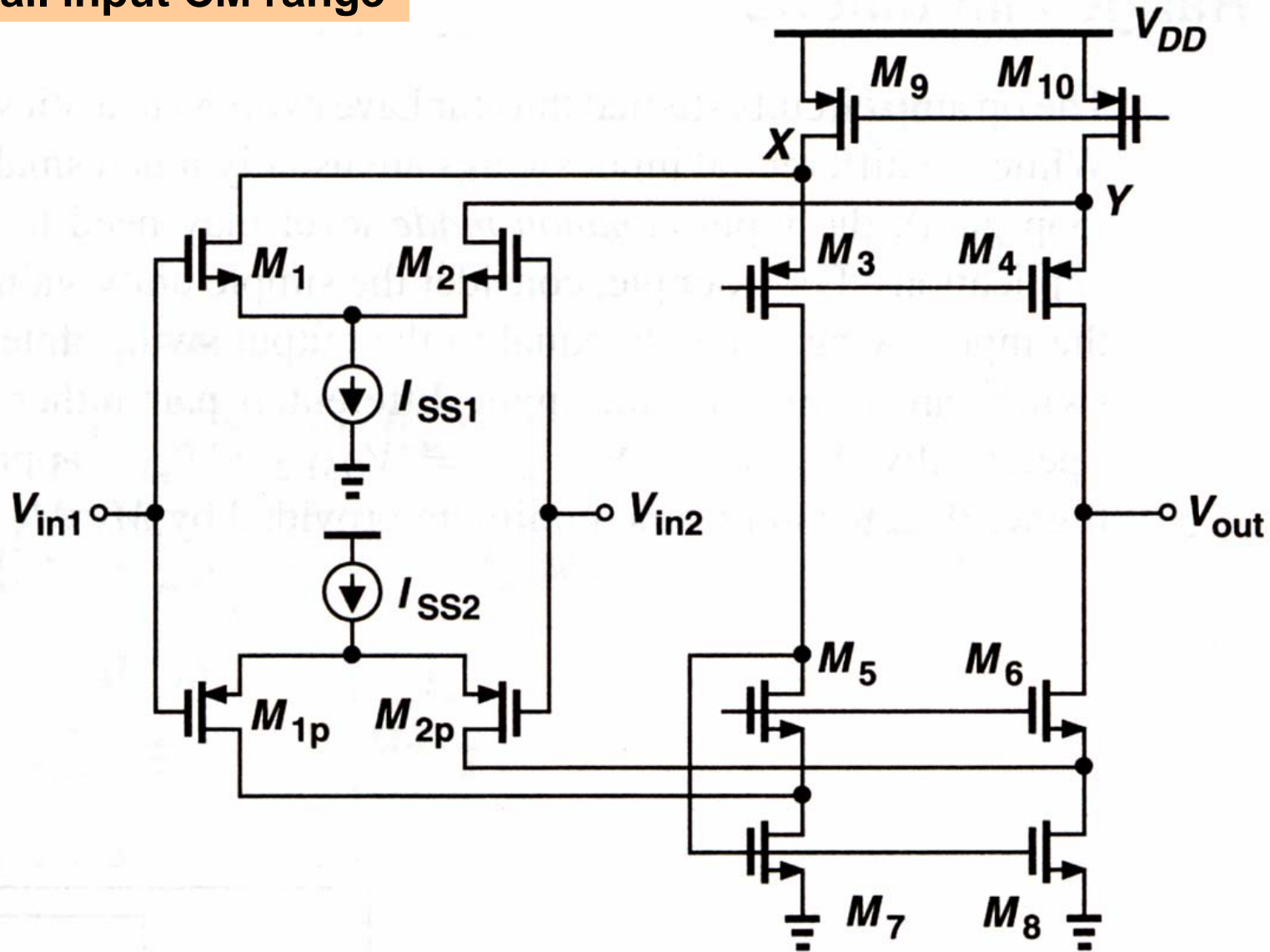
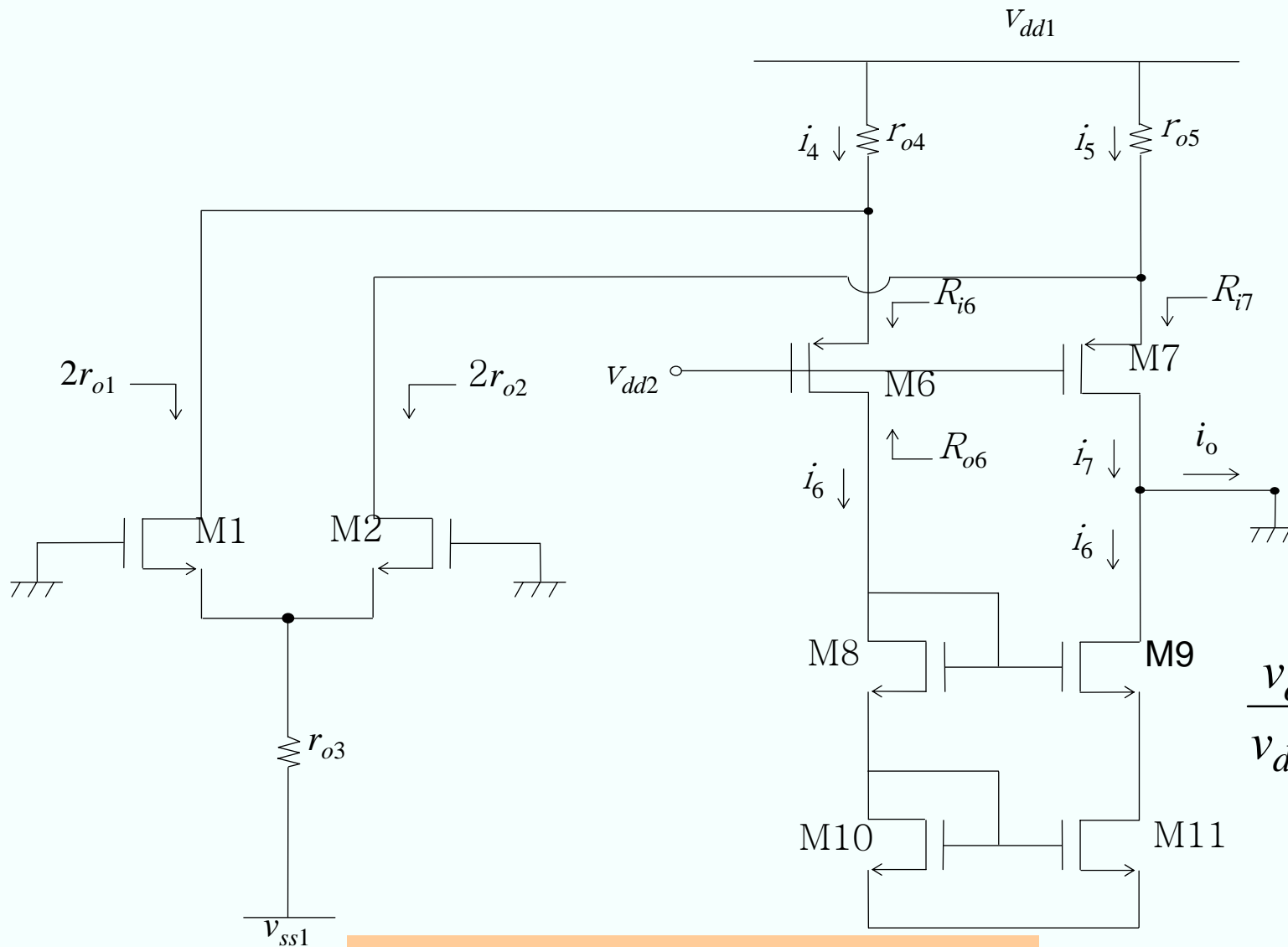
Rail-to-rail input CM range

Fig 9.2.11 fully differential folded cascode CMOS OP amp with the rail-to-rail input common mode voltage range

Rail-to-rail input CM range




PSRR+ \approx CMRR (very large)


PSRR- = A_{vd}

$$\left. \frac{v_o}{v_{dd}} \right|_{v_{ss}=0} = \frac{r_{o3}}{r_{o1}} \cdot A_{vc}$$

$$\left. \frac{v_o}{v_{ss}} \right|_{v_{dd}=0} = 1$$

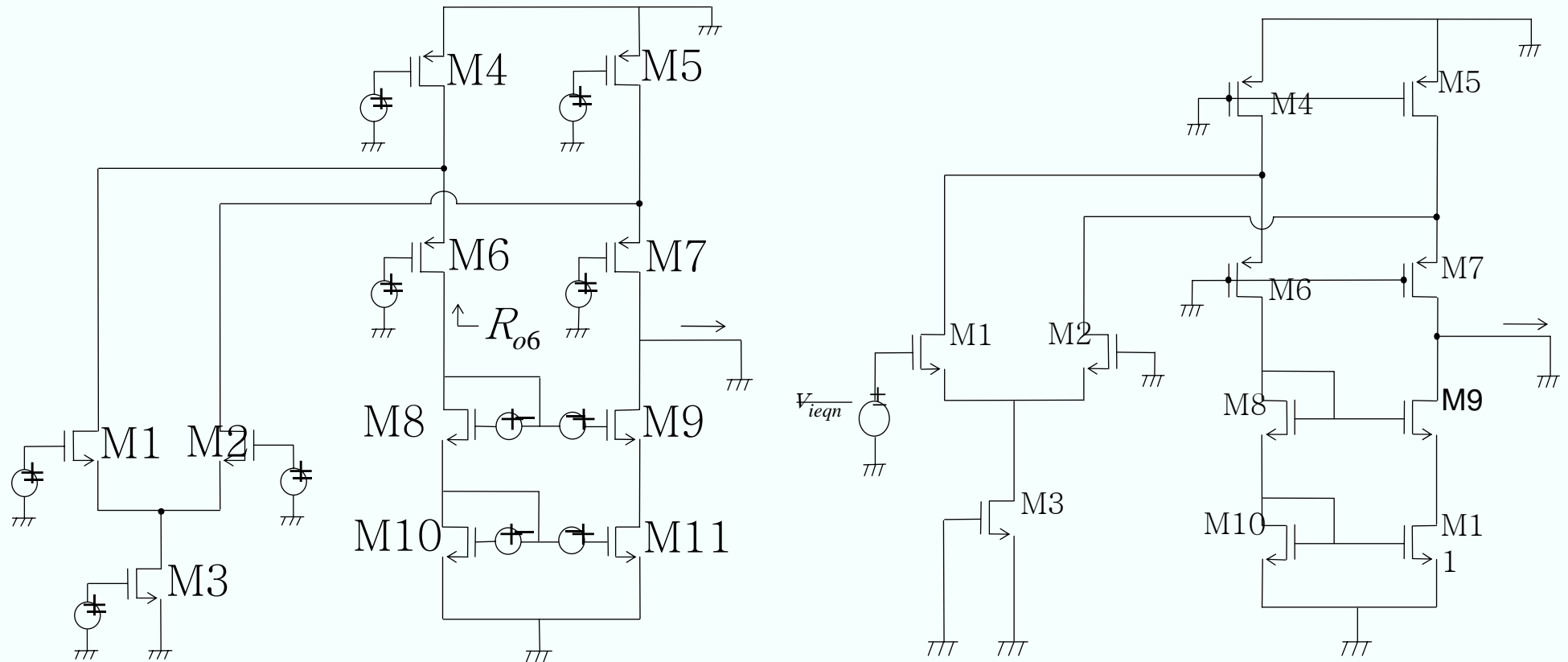
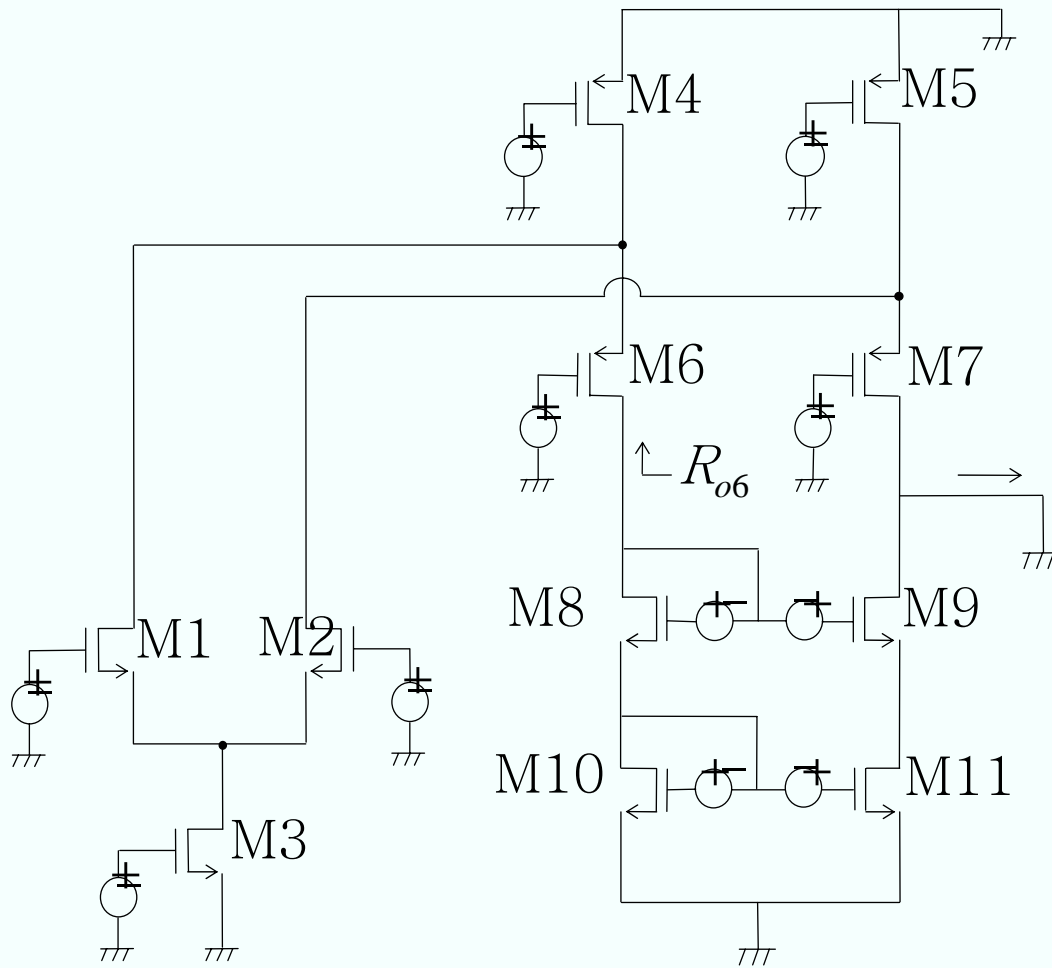
$$\overline{v_{ieqn}^2} = \overline{v_{gn1}^2} + \overline{v_{gn2}^2} + \left(\frac{g_{m4}}{g_{m1}} \right)^2 \cdot \left(\overline{v_{gn4}^2} + \overline{v_{gn5}^2} \right) + \left(\frac{g_{m11}}{g_{m1}} \right)^2 \cdot \left(\overline{v_{gn10}^2} + \overline{v_{gn11}^2} \right)$$



$$i_{on M1} = g_{m1} \cdot v_{gn1}$$

$$i_{on M2} = -g_{m2} \cdot v_{gn2} = -g_{m1} \cdot v_{gn1}$$


$$i_{on M4} = g_{m4} \cdot v_{gn4}$$


$$i_{on M5} = -g_{m5} \cdot v_{gn5} = -g_{m4} \cdot v_{gn5}$$


$$i_{on M6} = \frac{v_{gn6}}{r_{s6} + (r_{o4} \parallel 2r_{o1})} \cdot \left(1 + \frac{r_{o4}}{r_{o4} + 2r_{o1}}\right) \approx 0$$

$$i_{on M7} \approx 0$$

$$i_{on M8} \approx 0$$

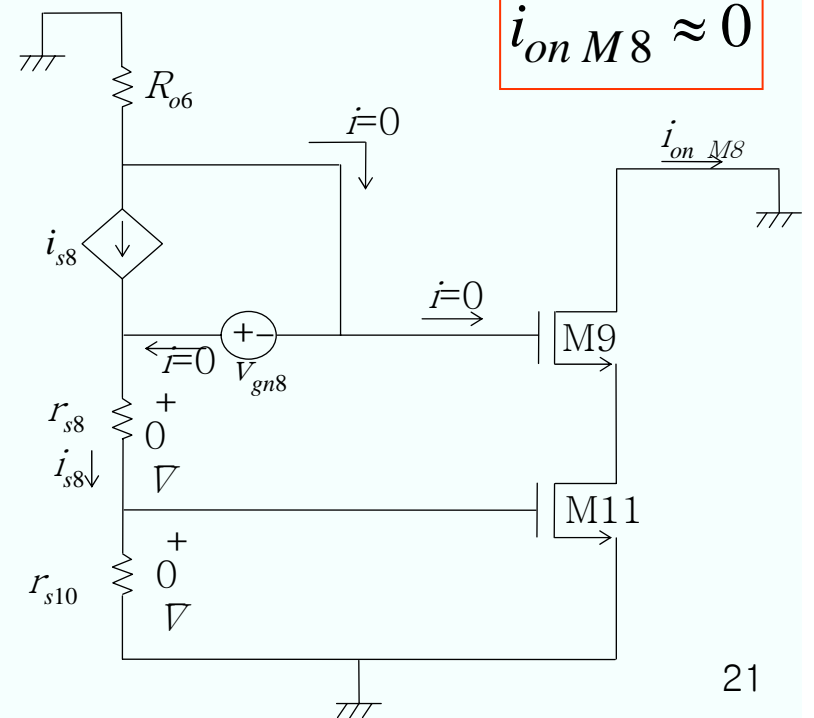

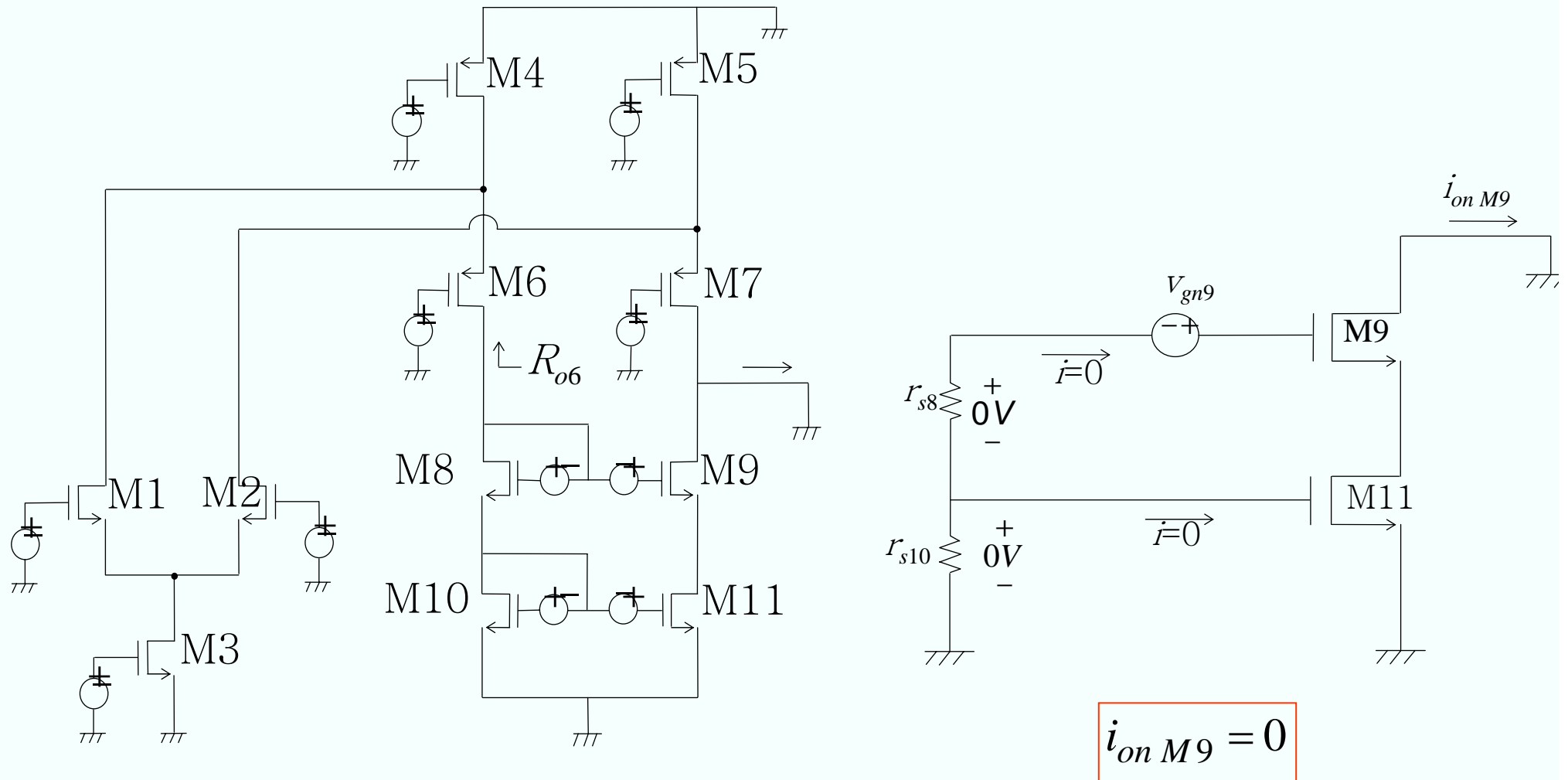


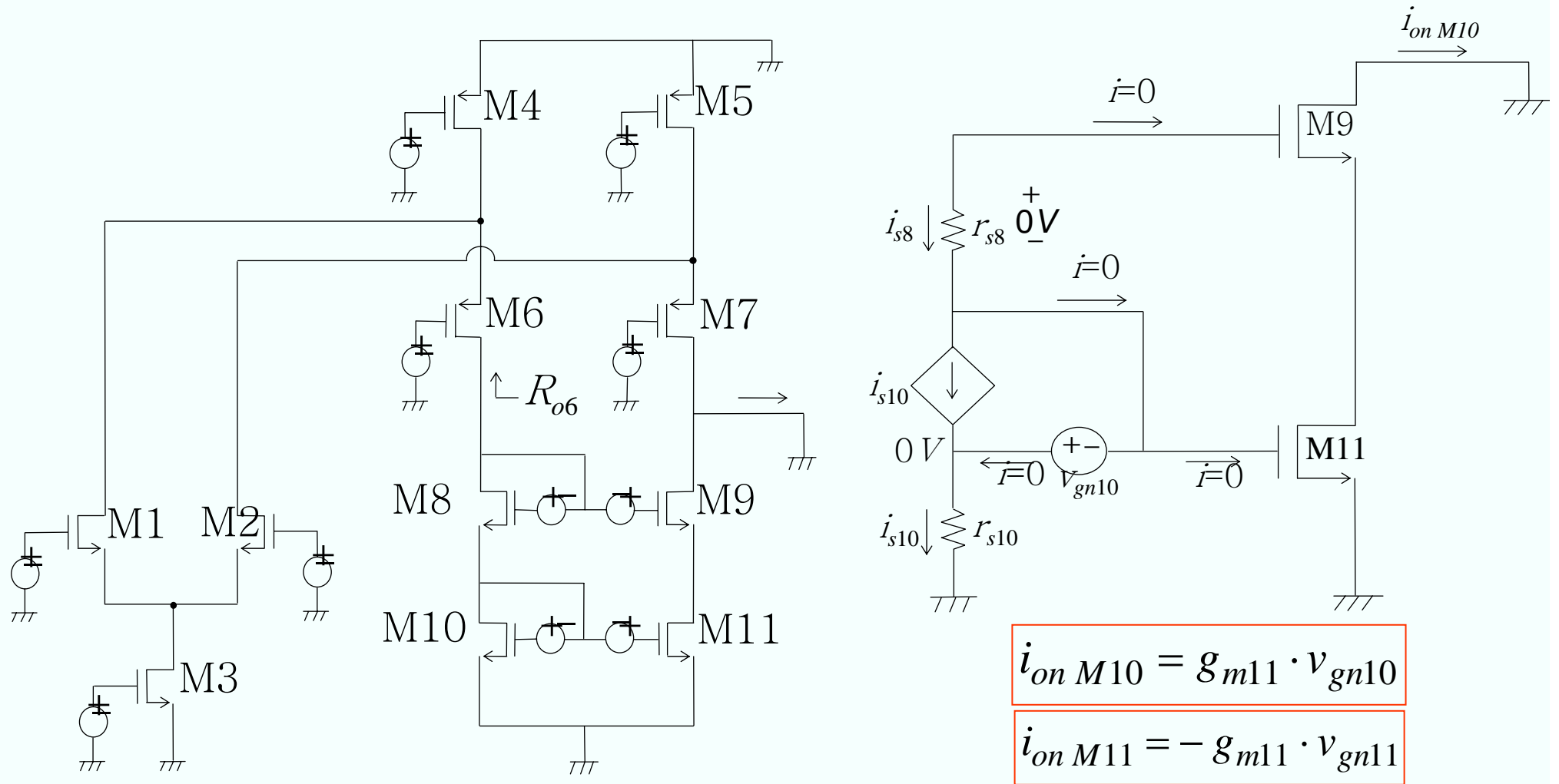

$$i_{on M10} = g_{m11} \cdot v_{gn10}$$

$$i_{on M11} = -g_{m11} \cdot v_{gn11}$$

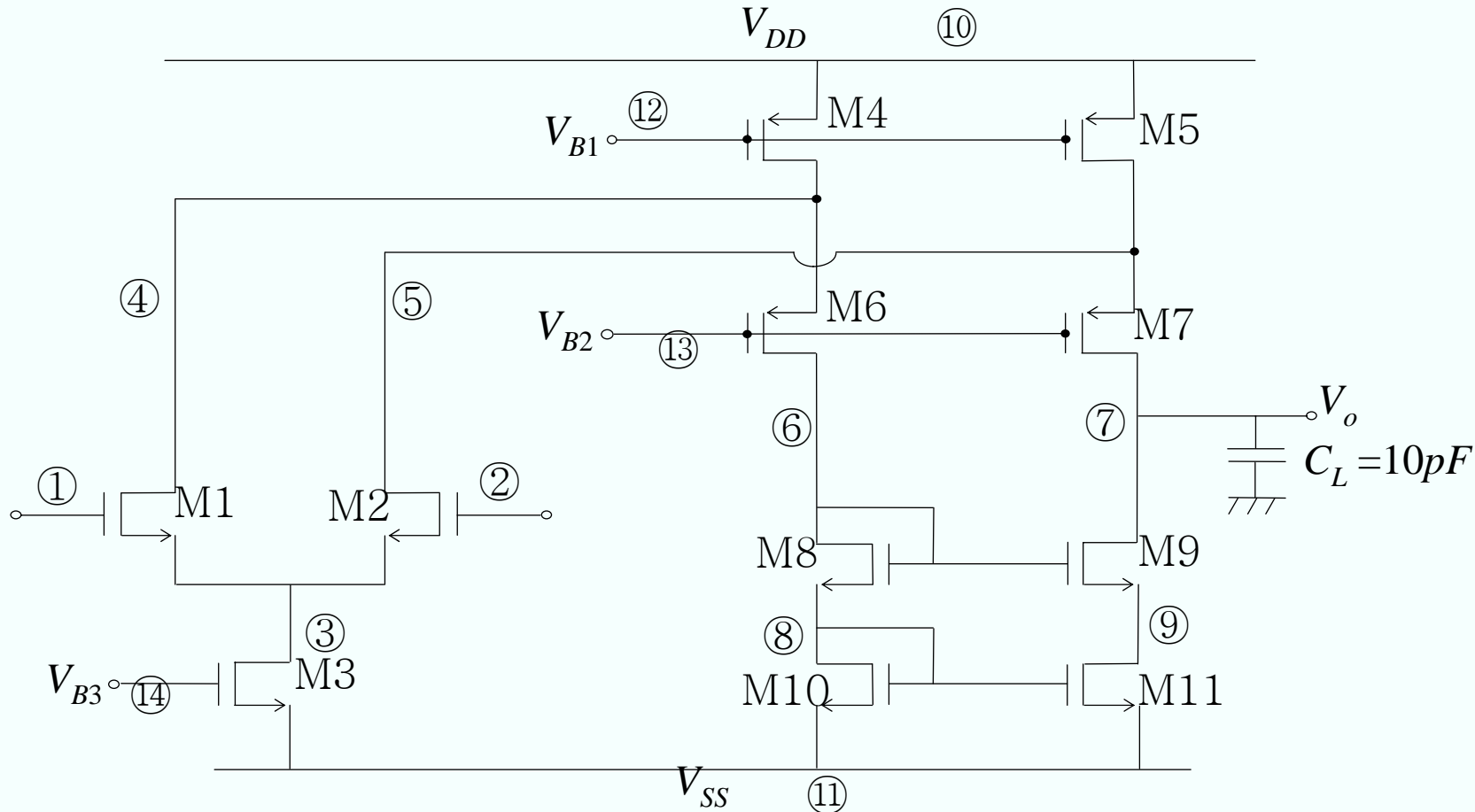
$$\overline{v_{ieqn}^2} = \overline{v_{gn1}^2} + \overline{v_{gn2}^2} + \left(\frac{g_{m4}}{g_{m1}} \right)^2 \cdot \left(\overline{v_{gn4}^2} + \overline{v_{gn5}^2} \right) + \left(\frac{g_{m11}}{g_{m1}} \right)^2 \cdot \left(\overline{v_{gn10}^2} + \overline{v_{gn11}^2} \right)$$



High Impedance Node : output node only


$$|p_1| = \frac{1}{R_o \cdot C_L}$$

$$|p_2| \approx \frac{1}{r_{s6} \cdot \left\{ C_{GS6} + C_{GSOV6} + C_{BS6} + C_{BD1} + C_{GDOV4} + C_{BD4} + C_{GDOV1} \cdot \left(1 + \frac{g_{m6}}{g_{m1}} \right) \right\}}$$

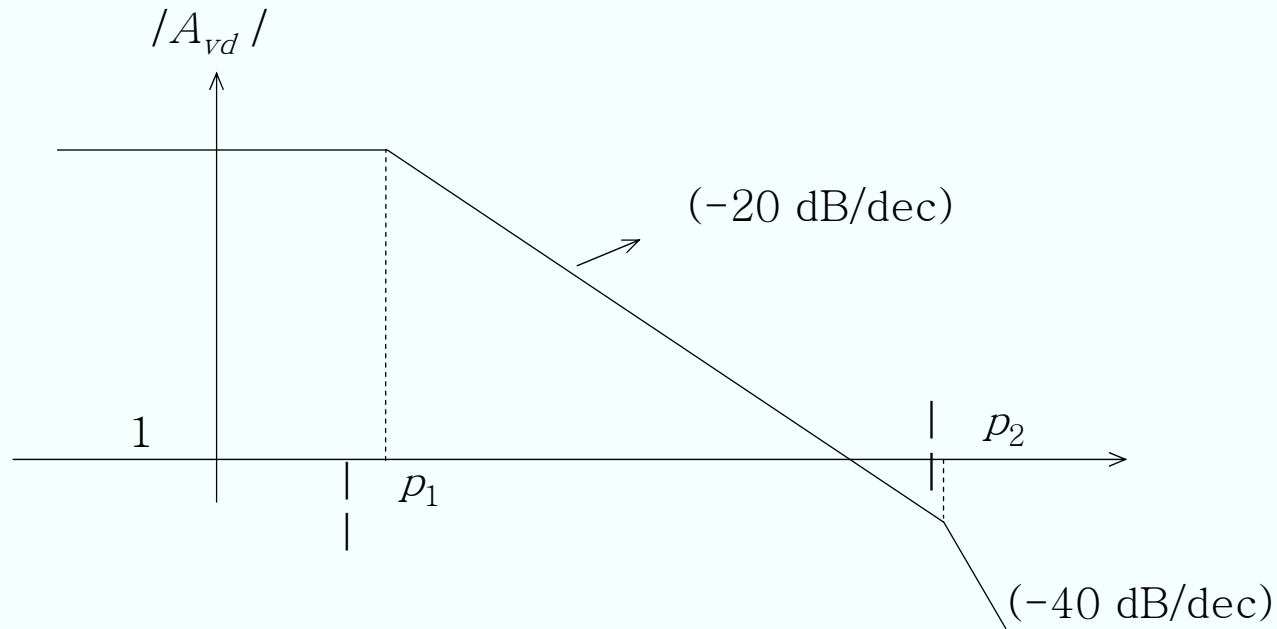


$$A_{vd} = g_{m1} R_o \quad |p_1| = \frac{1}{R_o C_L} \quad \omega_T = \frac{g_{m1}}{C_L} \quad |p_2| = \frac{1}{r_{s6} C_6}$$

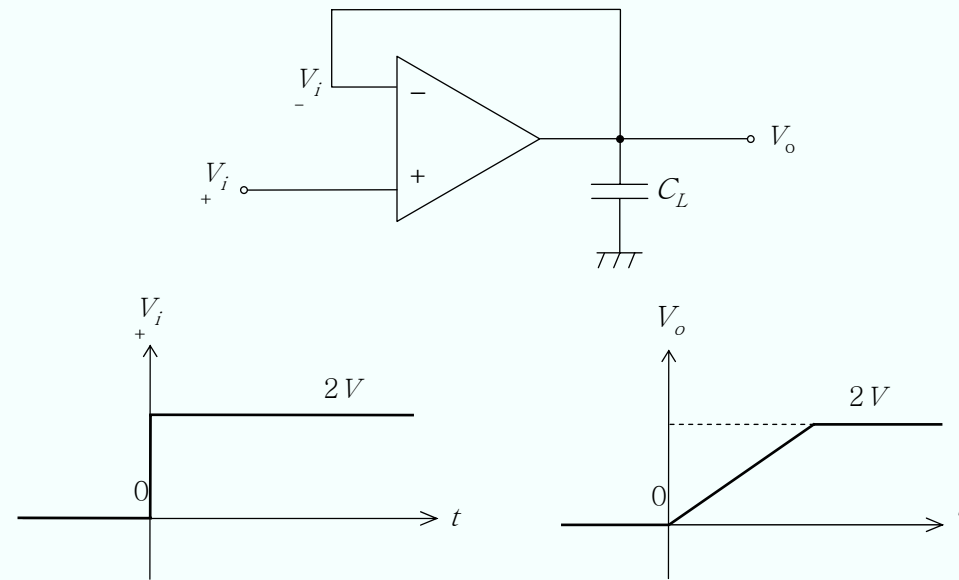increase $C_L \rightarrow$ decrease p_1 , no effect on p_2



Slew : non-linear behavior

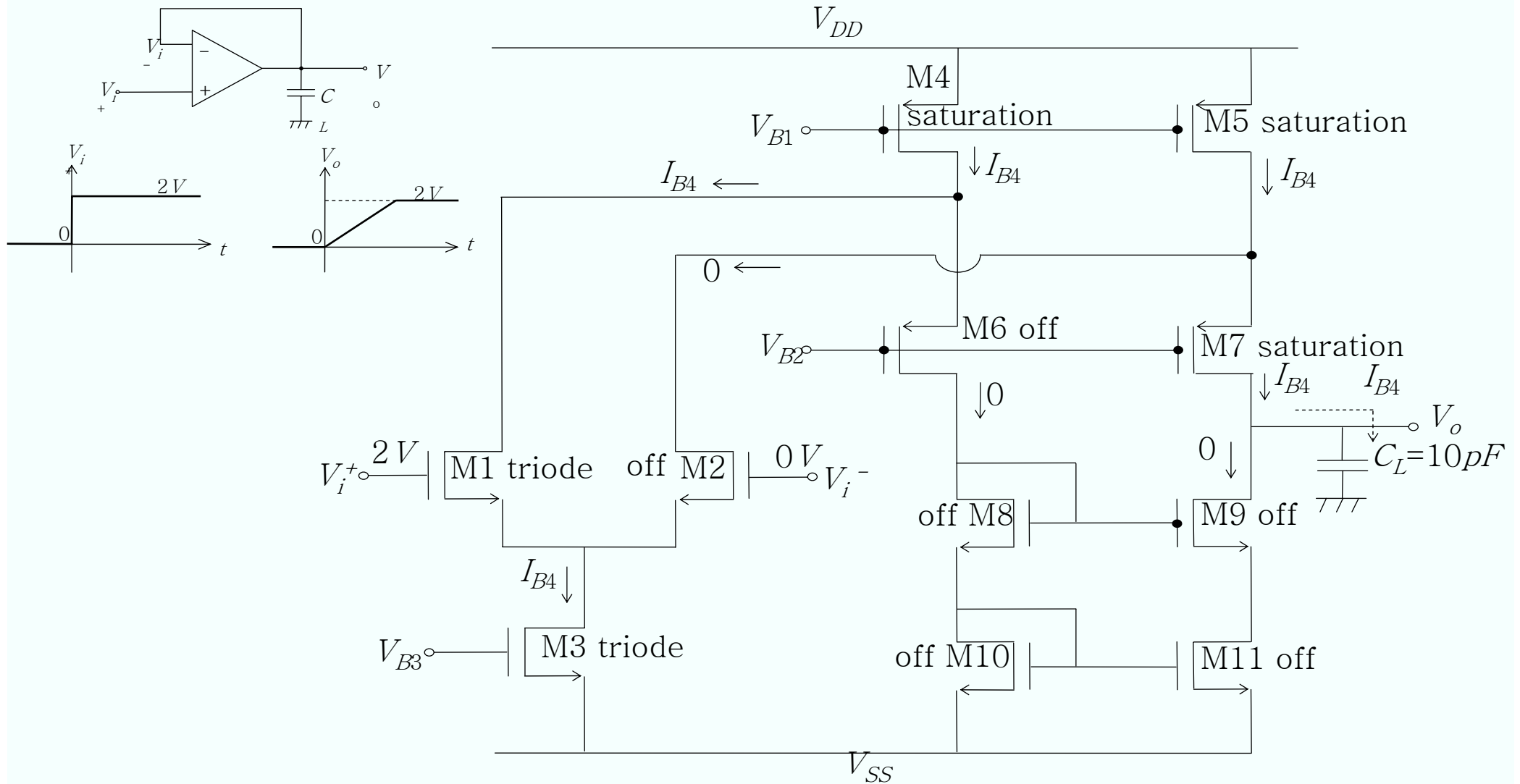


$$I_{B3} > I_{B4} > 0.5I_{B3}$$

$$V_o(t) = \frac{I_{B4}}{C_L} \cdot t$$


$$SR^+ \triangleq \left. \frac{dV_o}{dt} \right|_{\max} = \frac{I_{B4}}{C_L}$$

Slew rate

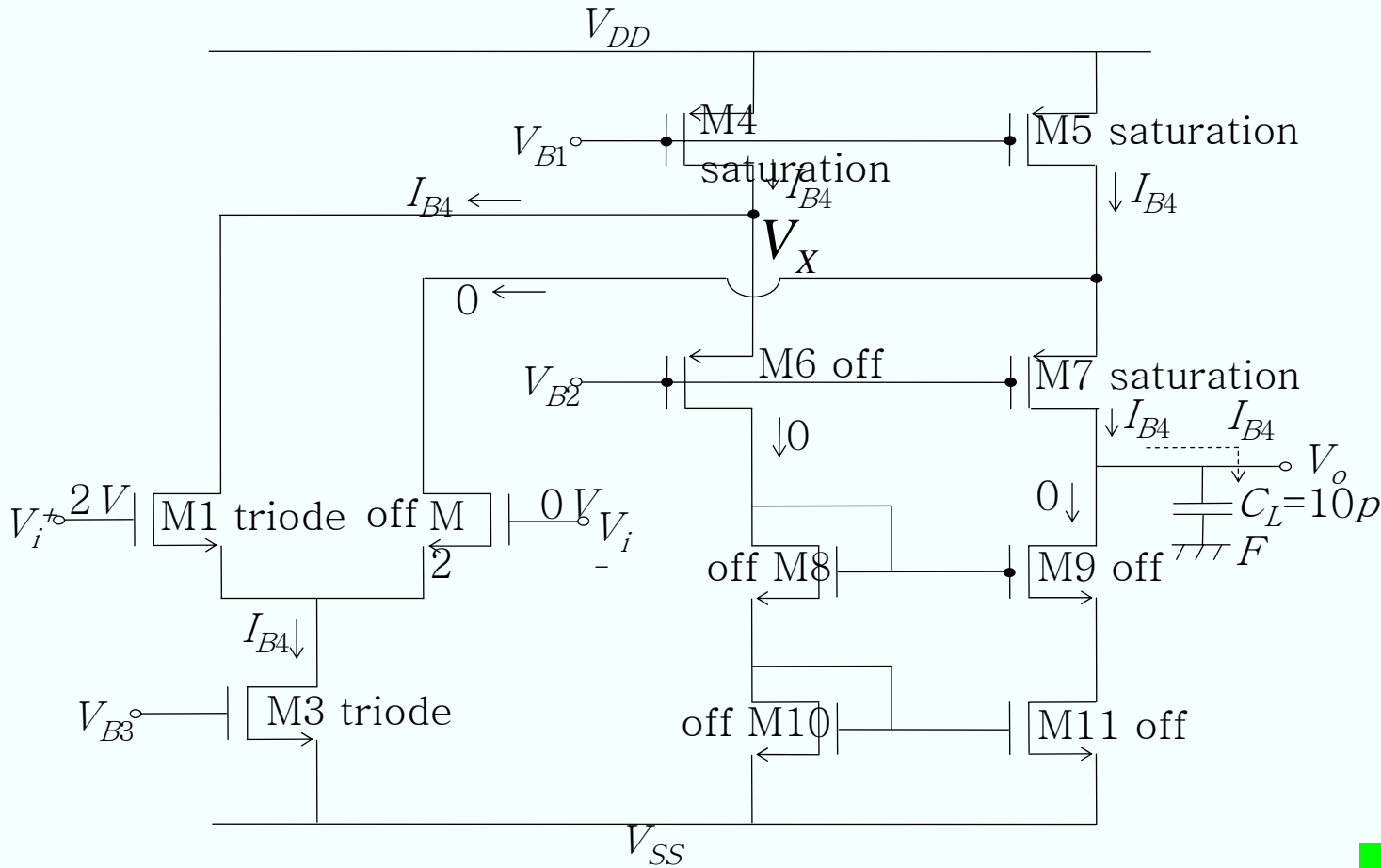

$$I_{B3} > I_{B4} > 0.5 I_{B3}$$


Droop in VX

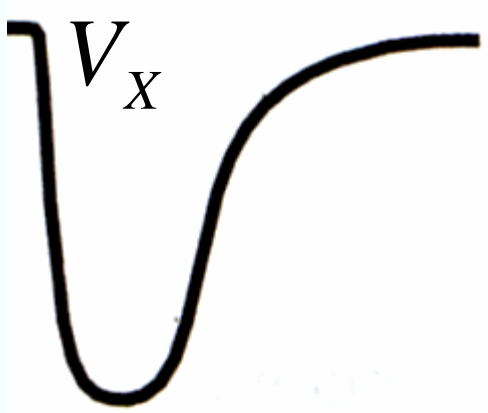

Slow in settling

$$V_o(t) = \frac{I_{B4}}{C_L} \cdot t$$

$$SR^+ \triangleq \left. \frac{dV_o}{dt} \right|_{\max} = \frac{I_{B4}}{C_L}$$

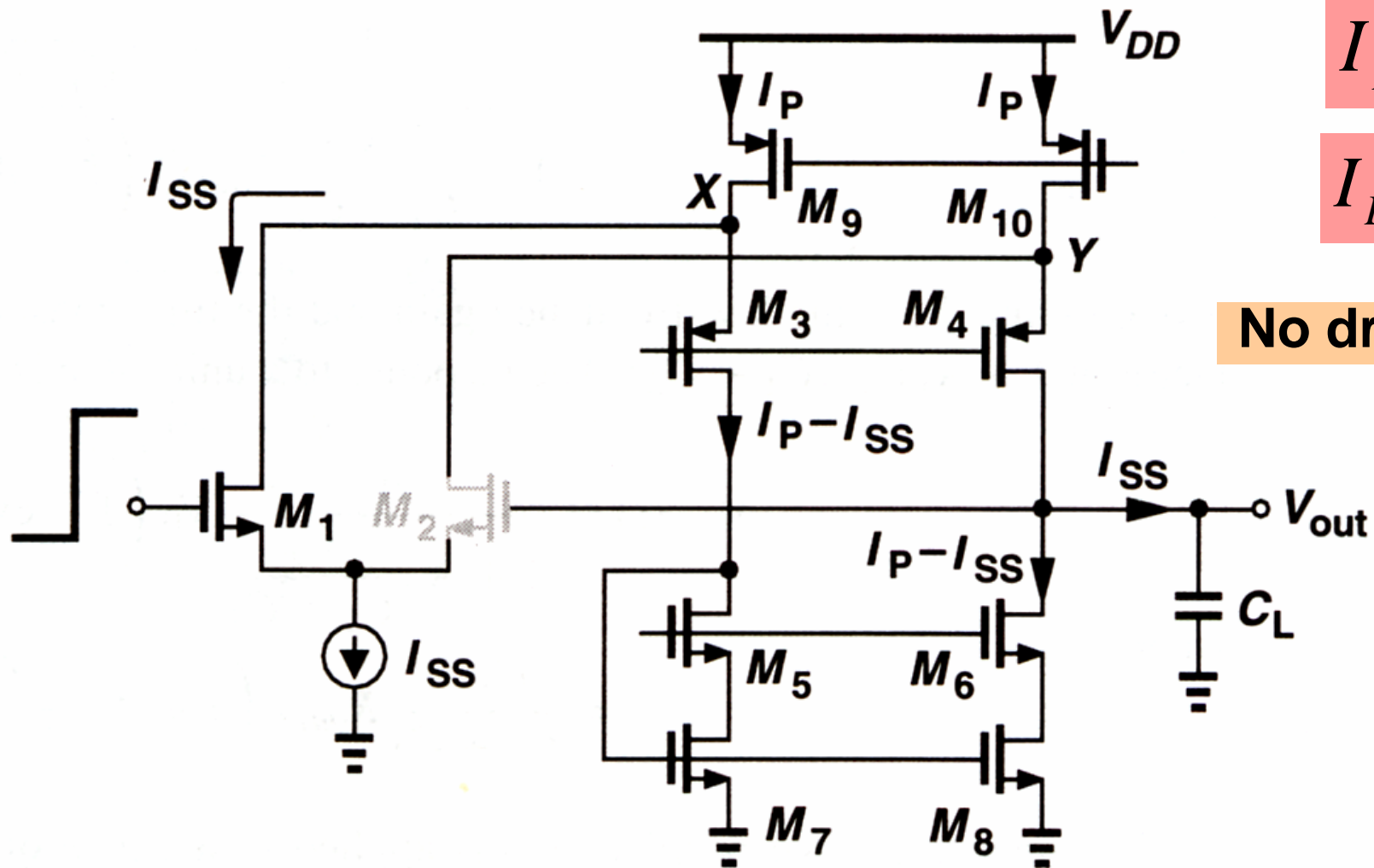

$$I_P > I_{SS}$$


$$I_{B4} > I_{B3}$$

No droop in V_X, V_Y



$$V_o(t) = \frac{I_{SS}}{C_L} \cdot t = \frac{I_{B3}}{C_L} \cdot t$$

$$SR^+ \triangleq \left. \frac{dV_o}{dt} \right|_{\max}$$
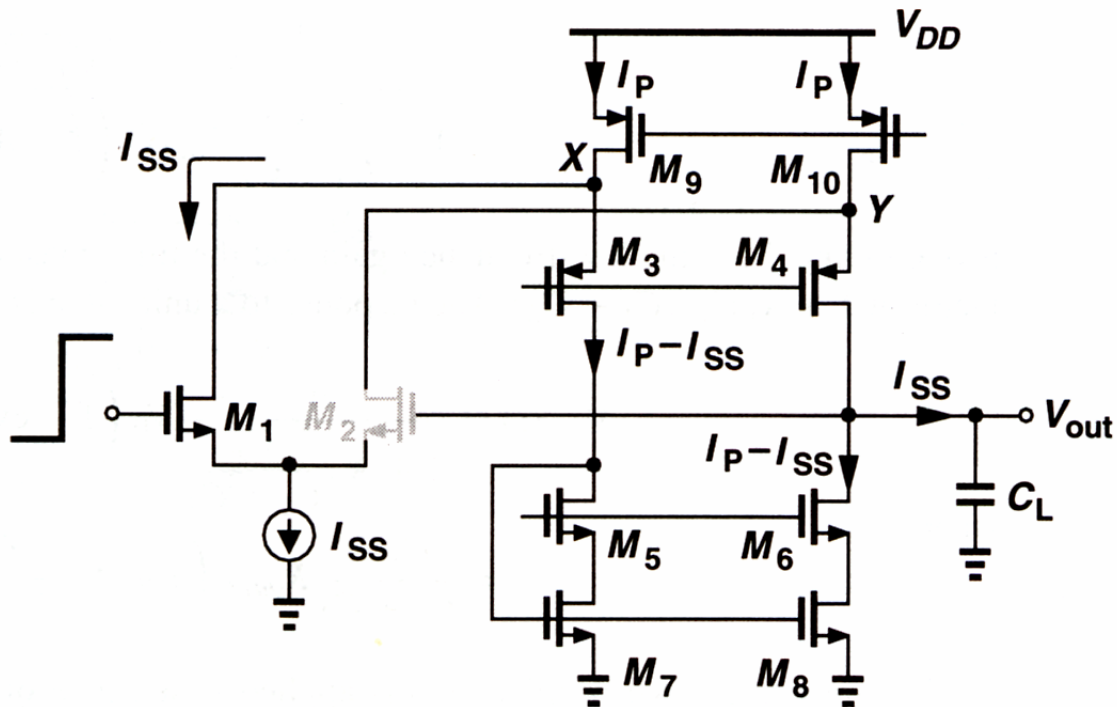
$$= \frac{I_{SS}}{C_L} = \frac{I_{B3}}{C_L}$$






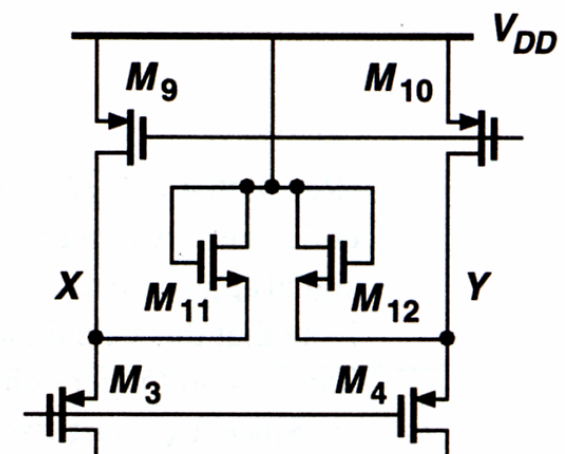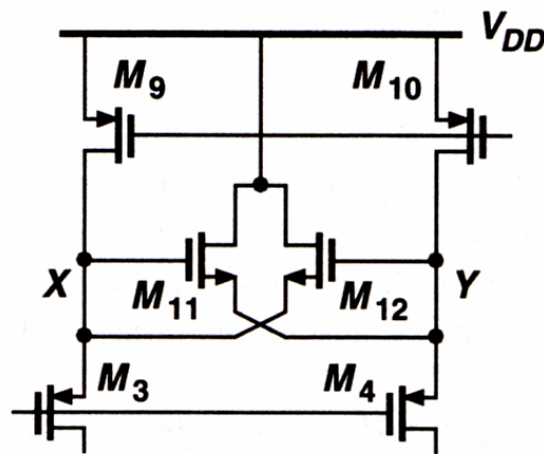Increase slew rate by
supplying extra
current during slewing



Increase gain of 1-stage cascode OP amp by gain-boosting




gain-boosting of cascode amp

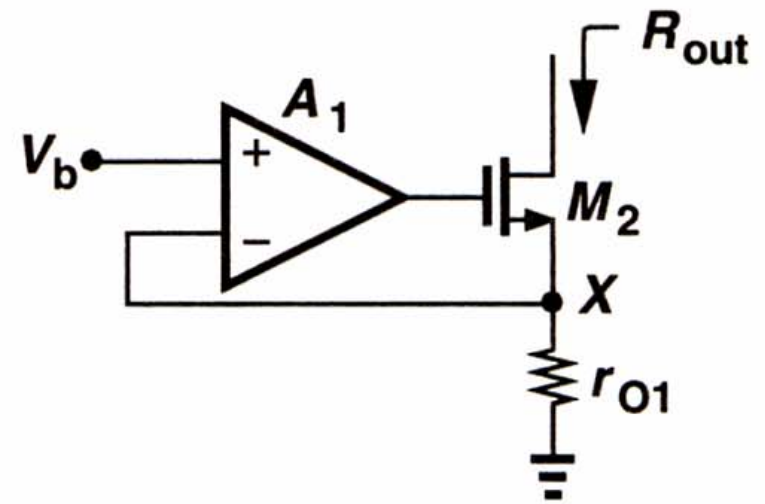
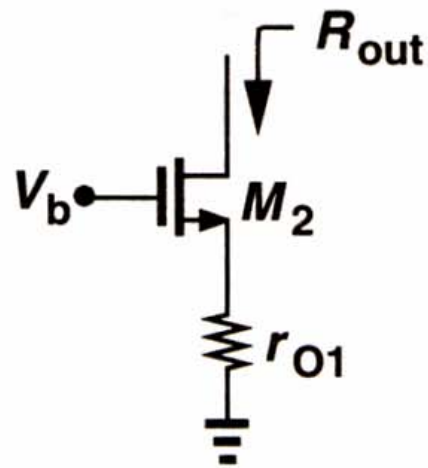
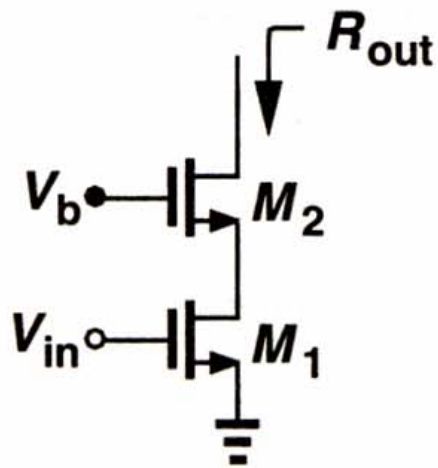



$$A_v = g_{m1} R_{out}$$

$$R_{out} \approx A_1 g_{m2} r_{o2} r_{o1}$$

gain-boosting of cascode amp

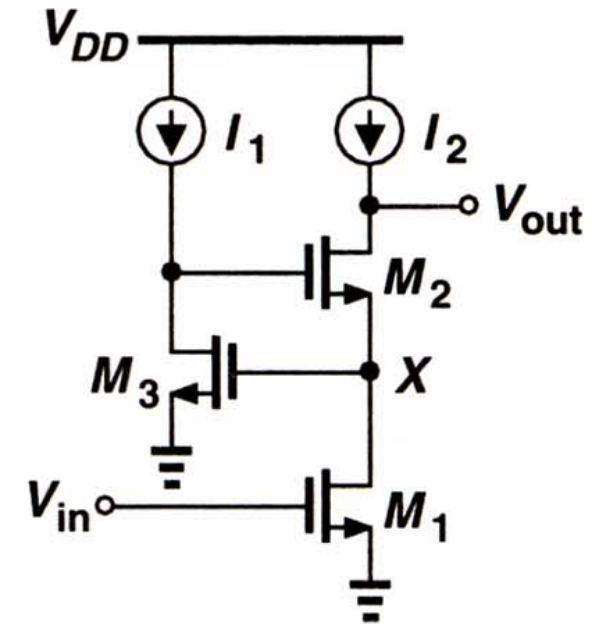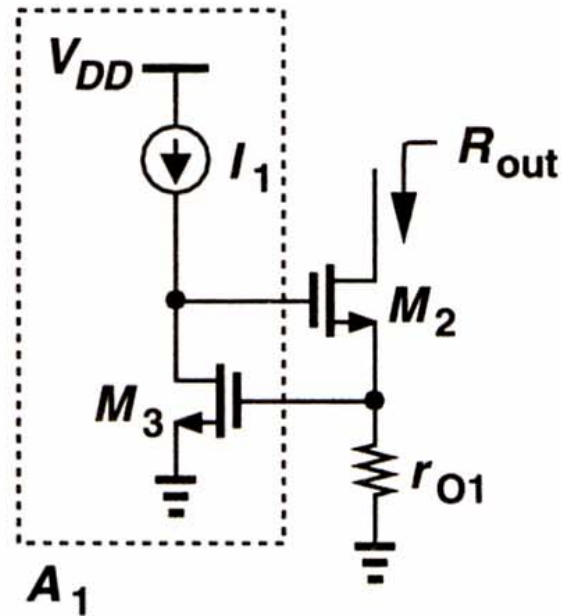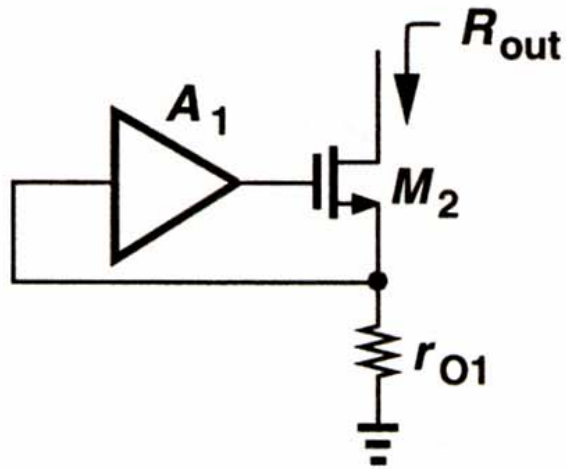


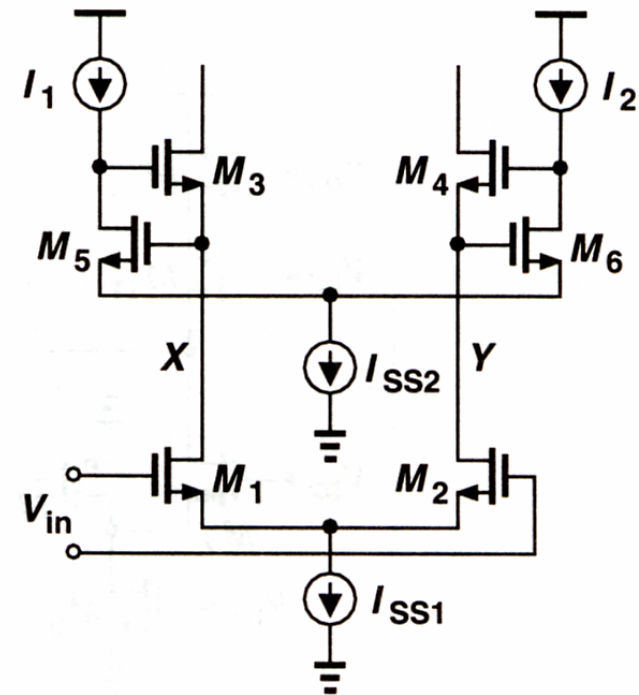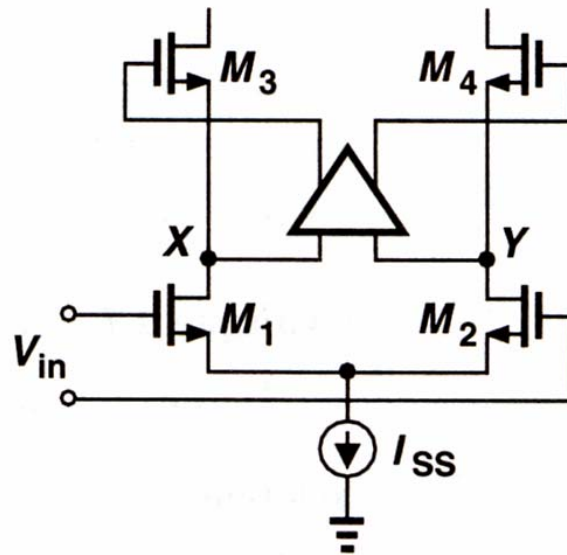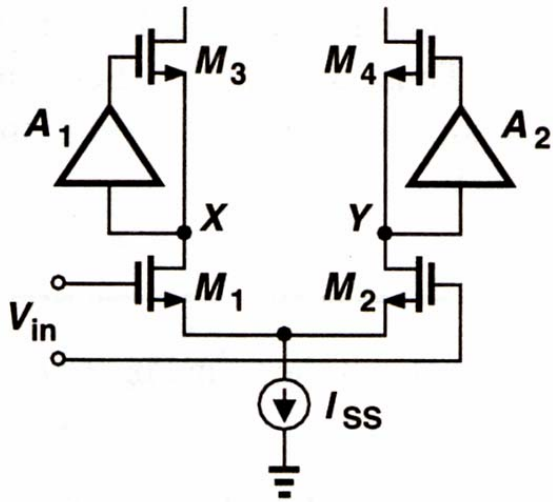

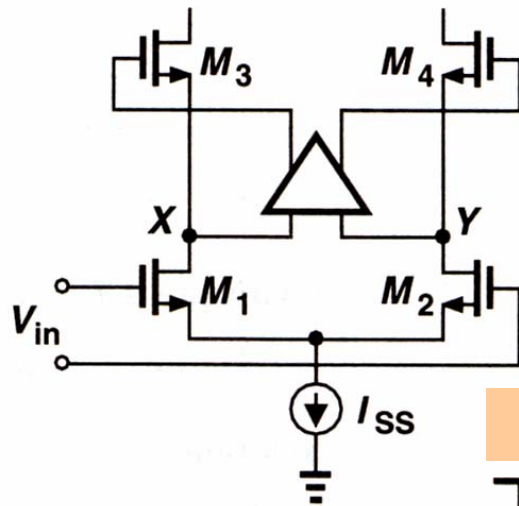


Limited output range



Improved output range

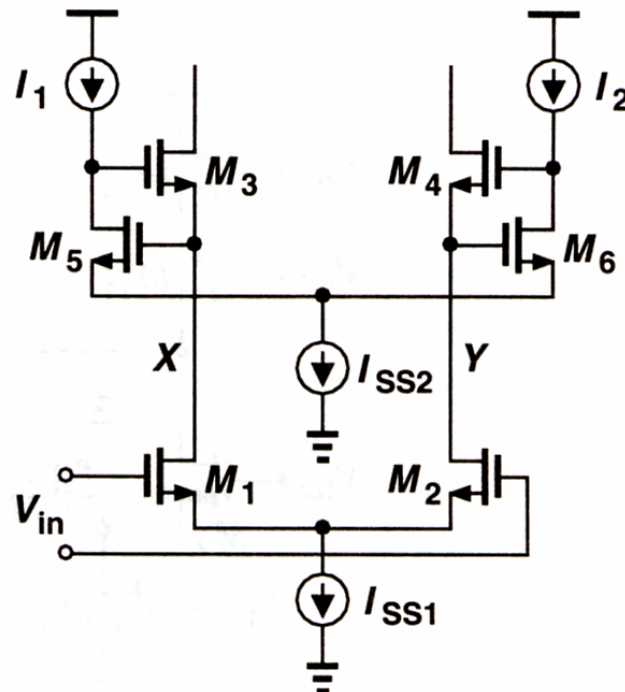

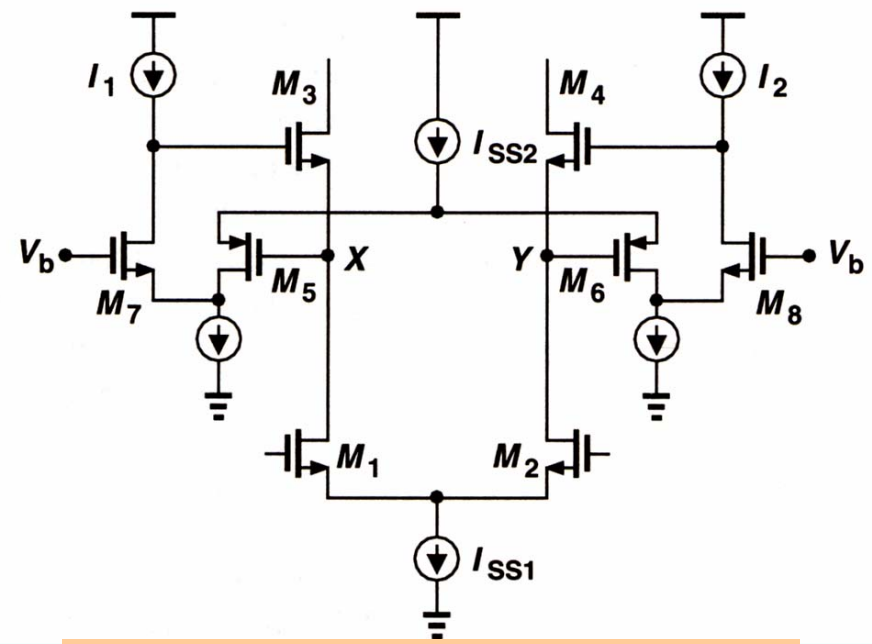Min V_{out} : $V_{DSAT}(I_{SS2})+V_{DSAT5}+V_{DSAT3}+V_{TH5}$




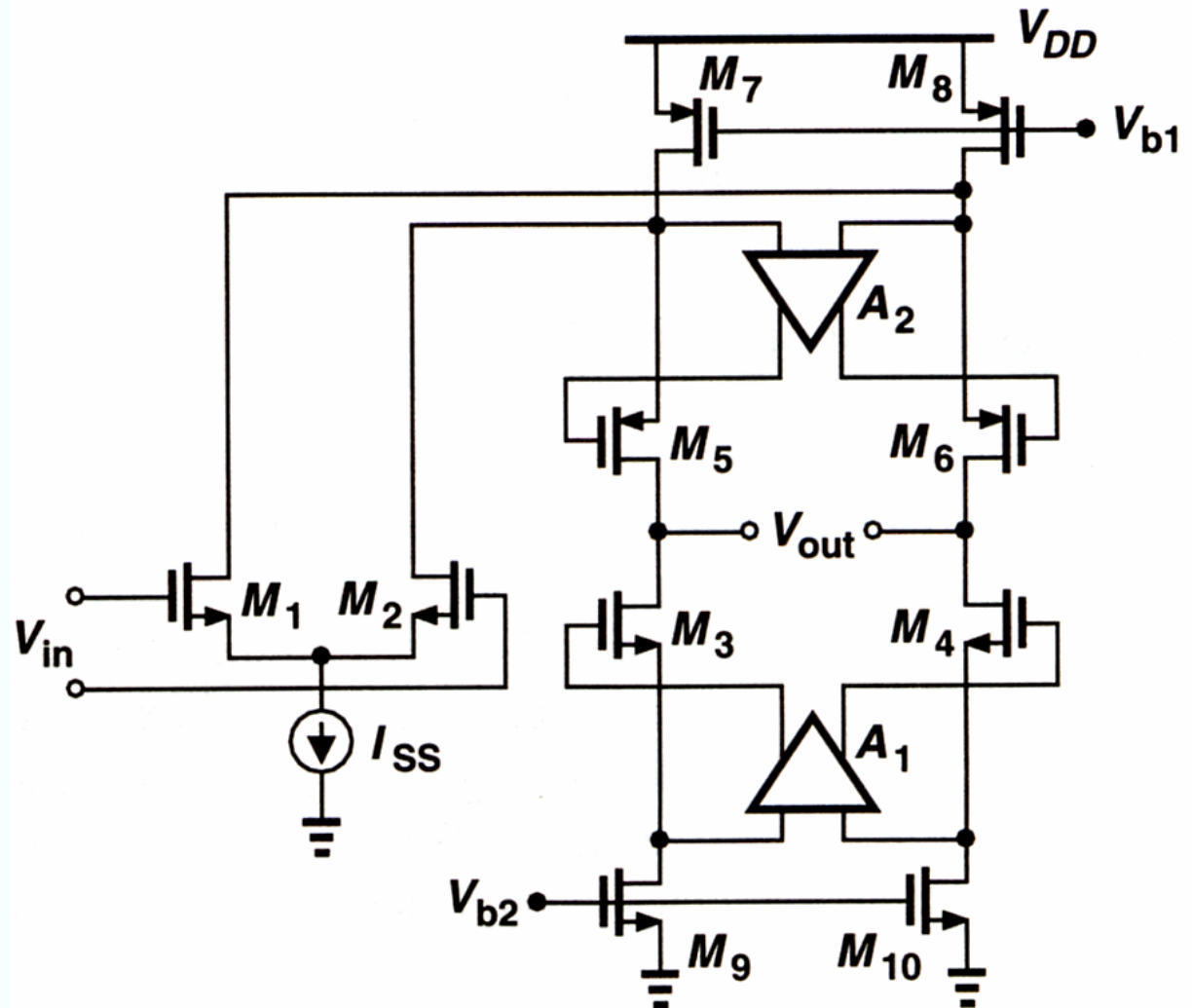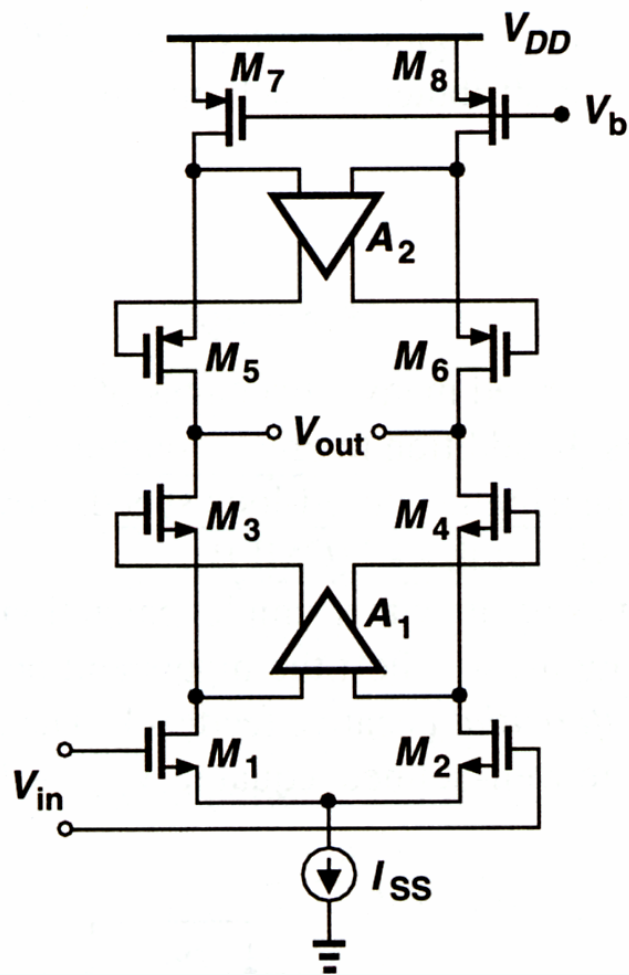Min V_{out} : $V_{DSAT}(I_{SS1})+V_{DSAT1}+V_{DSAT3}$



**Frequency response: not much degraded by gain-boosting amp
(due to only error signal passes gain-boosting amp)**

	Gain	Output Swing	Speed	Power Dissipation	Noise
Telescopic	Medium	Medium	Highest	Low	Low
Folded-Cascode	Medium	Medium	High	Medium	Medium
Two-Stage	High	Highest	Low	Medium	Low
Gain-Boosted	High	Medium	Medium	High	Medium

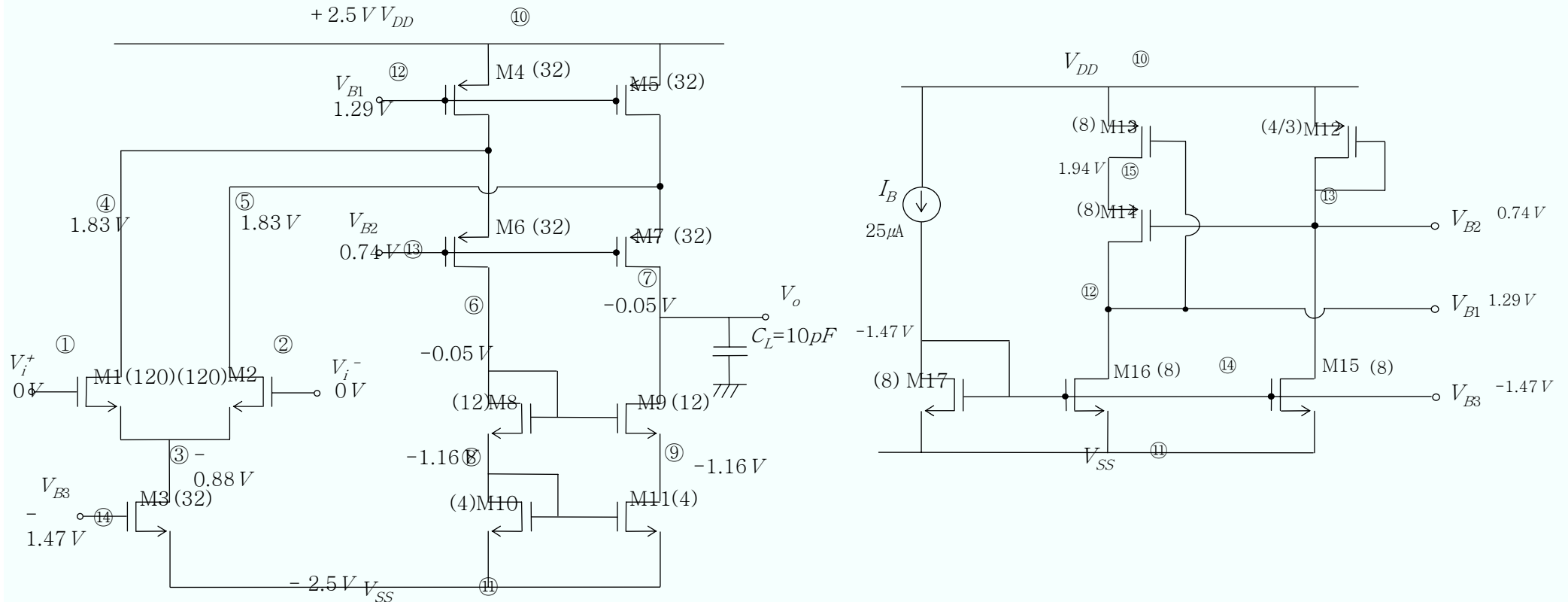

L=1.2um



↵	식↵	계산 값↵	SPICE↵
$G_{md} [Siemens]↵$	$g_{m1}↵$	$1.28 \times 10^{-3}↵$	$1.24 \times 10^{-3}↵$
$G_{mc} [Siemens]↵$	$-\frac{r_{s8} + r_{s10}}{g_{m6} r_{o6} \cdot (r_{o1} \parallel r_{o4}) \cdot 2r_{o3}}↵$	$-4.12 \times 10^{-9}↵$	$-5.00 \times 10^{-9}↵$
$R_o \cdot [\Omega]↵$	$\{g_{m7} r_{o7} \cdot (r_{o2} \parallel r_{o5})\} \parallel g_{m9} r_{o9} r_{o1}↵$	$4.17 \times 10^6↵$	$4.33 \times 10^6↵$

$A_{vd} \cdot [V/V]$ $([dB])$	$G_{md} \cdot R_o$	5.34×10^3 $(74.6dB)$	5.38×10^3 $(74.6dB)$
$A_{vc} \cdot [V/V]$ $([dB])$	$G_{mc} \cdot R_o$	-1.72×10^{-2} $(-35.3dB)$	-2.17×10^{-2} $(-33.3dB)$
$\frac{\partial \mathcal{N}_o}{\partial \mathcal{N}_{DD}} [V/V]$	$\frac{r_{o3}}{r_{o1}} \cdot A_{vc}$	-7.98×10^{-3}	4.50×10^{-2} $(*)7.57 \times 10^{-4}$
$\frac{\partial \mathcal{N}_o}{\partial \mathcal{N}_{SS}} [V/V]$	1	1	0.998 $(*)1.02$
$CMRR \cdot [\dots]$	$\left \frac{A_{vd}}{A_{vc}} \right $	3.11×10^5 $(110dB)$	2.48×10^5 $(108dB)$
$PSRR^+$	$\left \frac{A_{vd}}{\frac{\partial \mathcal{N}_o}{\partial \mathcal{N}_{DD}}} \right $	6.69×10^5 $(117dB)$	1.20×10^5 $(102dB)$
$PSRR^-$	$\left \frac{A_{vd}}{\frac{\partial \mathcal{N}_o}{\partial \mathcal{N}_{SS}}} \right = A_{vd}$	5.34×10^3 $(74.6dB)$	5.38×10^3 $(74.6dB)$

표 9.2.1 OP amp 의 주파수 특성 관련 파라미터들(부하 커패시터 $C_L = 10pF$)

식	계산 값	SPICE	
Dominant pole freq. [Hz] ($ p_1 /2\pi$)	$\frac{1}{2\pi} \cdot \frac{1}{R_o C_L}$	3.8KHz	3.7 KHz
non-dominant pole freq. ($ p_2 /2\pi$) [Hz]	$\frac{1}{2\pi \cdot r_{s6} \cdot \left[C_{GS6} + C_{GSOV6} + C_{BS6} + C_{GDOV1} \cdot \left(1 + \frac{g_{m6}}{g_{m1}} \right) + C_{BD1} + C_{GDOV4} + C_{BD4} \right]}$	478 MHz	336 MHz
Gain-bandwidth $\frac{\omega_T}{2\pi}$ ($\omega_T/2\pi$) [Hz]	$\frac{1}{2\pi} \cdot \frac{g_{m1}}{C_L}$	20.4 MHz	19.7 MHz
phase margin at unity-gain 피드백	$90^\circ - \tan^{-1} \left \frac{\omega_{0dB}}{P_2} \right $	88°	87°

Layout : Folded cascode OP amp

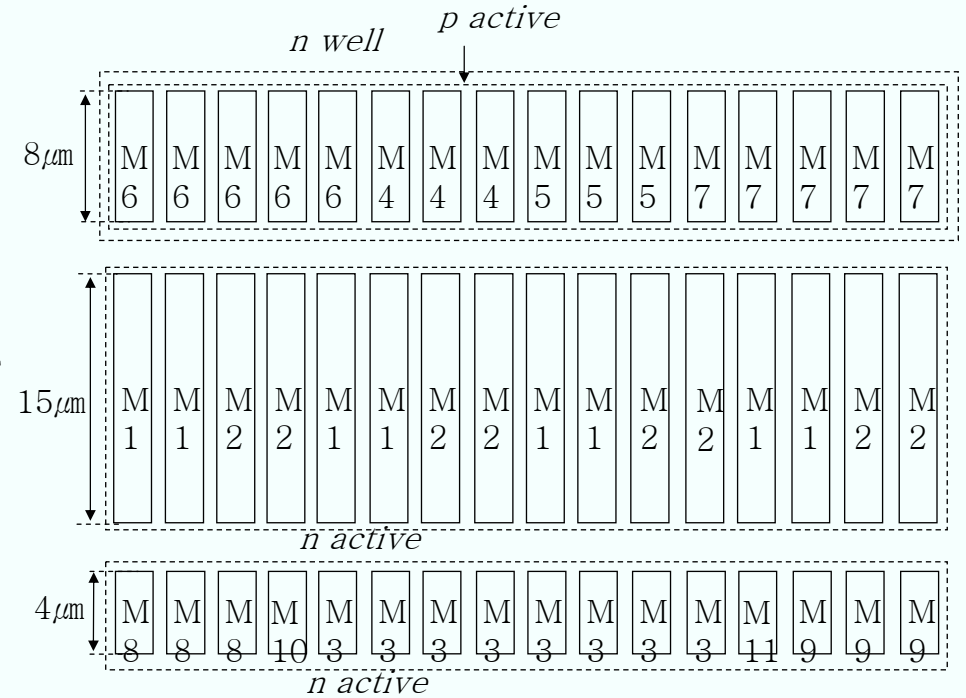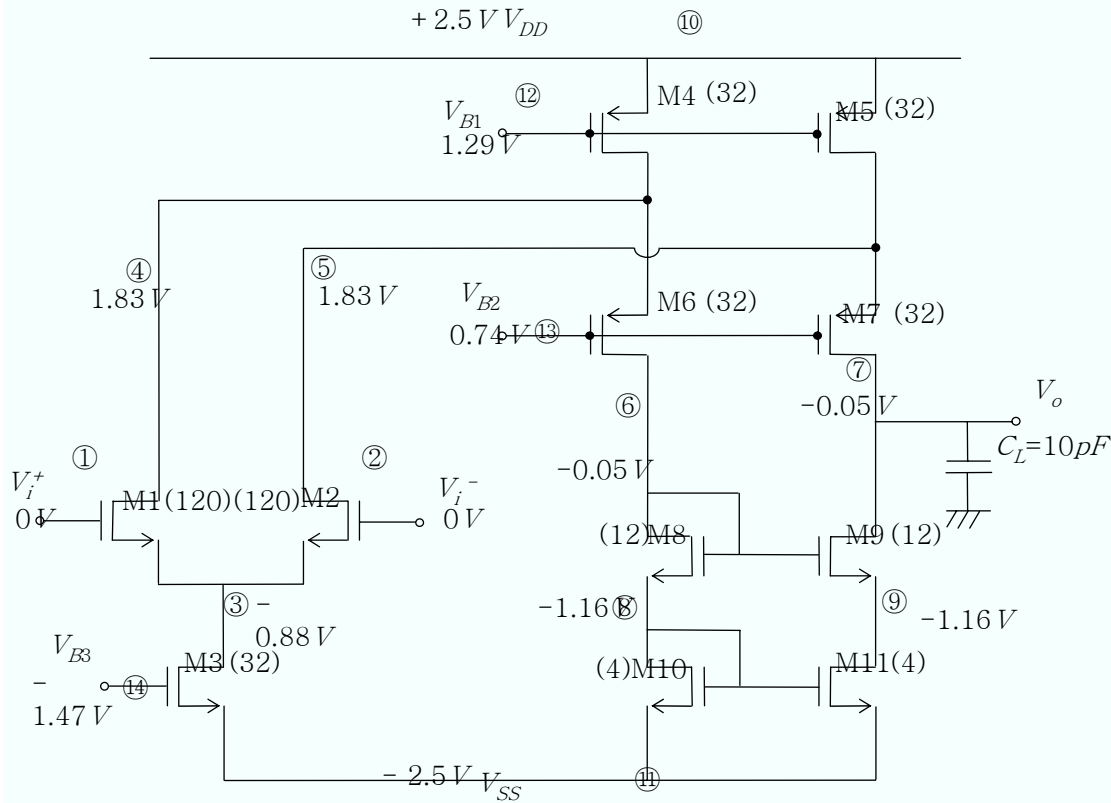

Layout : Folded cascode OP amp

