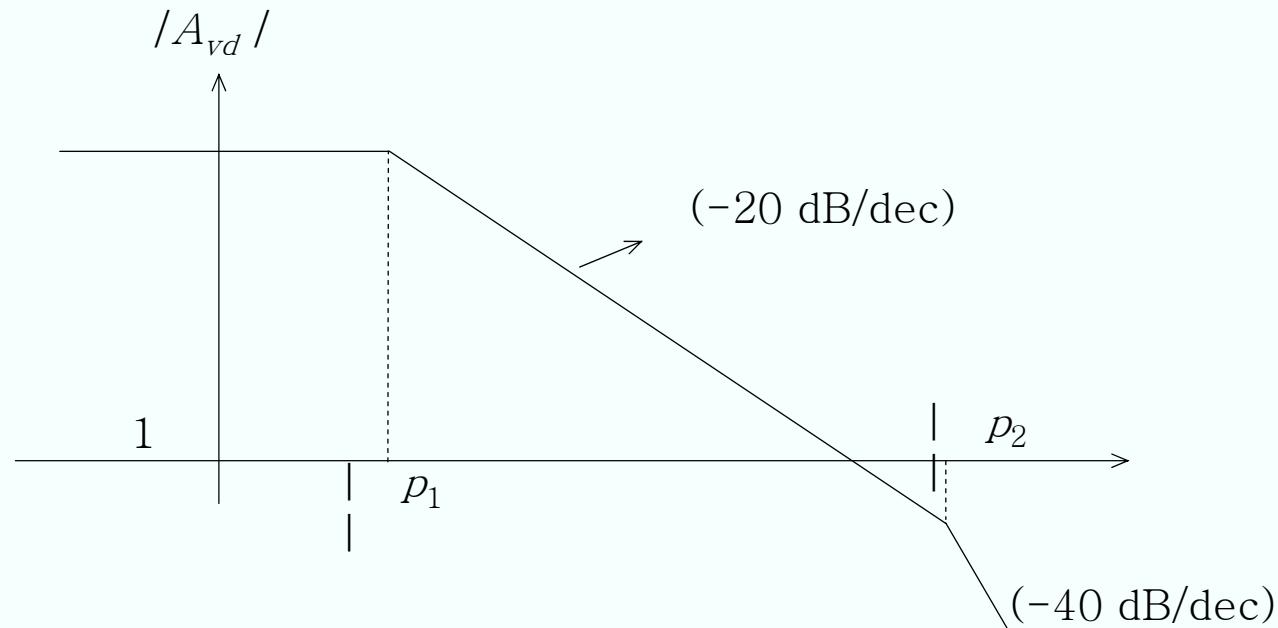


$$PM = 180 - 90 - \tan^{-1}\left(\frac{\omega_T}{p_2}\right)$$

$$\approx 180 - 90 - 45 - 45 \cdot \log_{10} \frac{\omega_T}{p_2}$$

$$= 45 \cdot \log_{10} \frac{10 \cdot p_2}{\omega_T}$$



$$A_{vd} = g_{m1} R_o \quad |p_1| = \frac{1}{R_o C_L} \quad \omega_T = \frac{g_{m1}}{C_L} \quad |p_2| = \frac{1}{r_{s6} C_6}$$


**increase $C_L \rightarrow$ decrease p_1 & ω_T , no effect on p_2
 \rightarrow Increase phase margin (PM)**

Parameters	$ A_{dv}(0) $	p_1	p_2	z_1	ω_T
Equations	$G_{m1}R_{o1} \cdot G_{m2}R_{o2}$	$\frac{-1}{R_{o1} \cdot G_{m2}R_{o2} \cdot C_C}$	$-\frac{G_{m2}}{C_L}$	$+\frac{G_{m2}}{C_C}$	$\frac{G_{m1}}{C_C}$


$$z_1 = \frac{G_{m2}}{C_C} \cdot \frac{1}{1 - G_{m2} \cdot R_Z}$$

increase $C_L \rightarrow$ decrease p_2 , no effect on ω_T
 \rightarrow Decrease phase margin (PM)

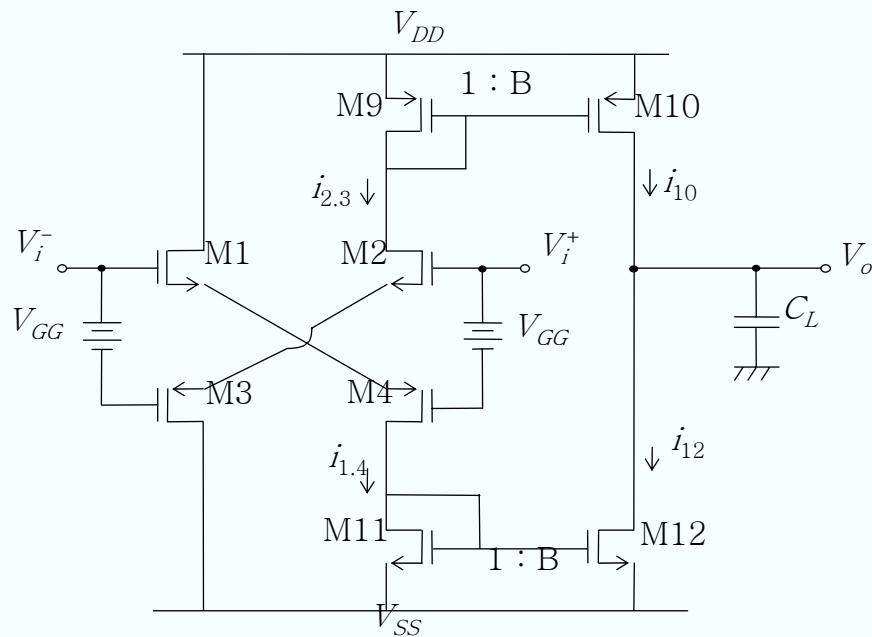
- (1) Class AB input OP amp
for large slew rate
- (2) Class AB output stage
for low power at small input
- (3) Current amplifier



For Large Slew Rate

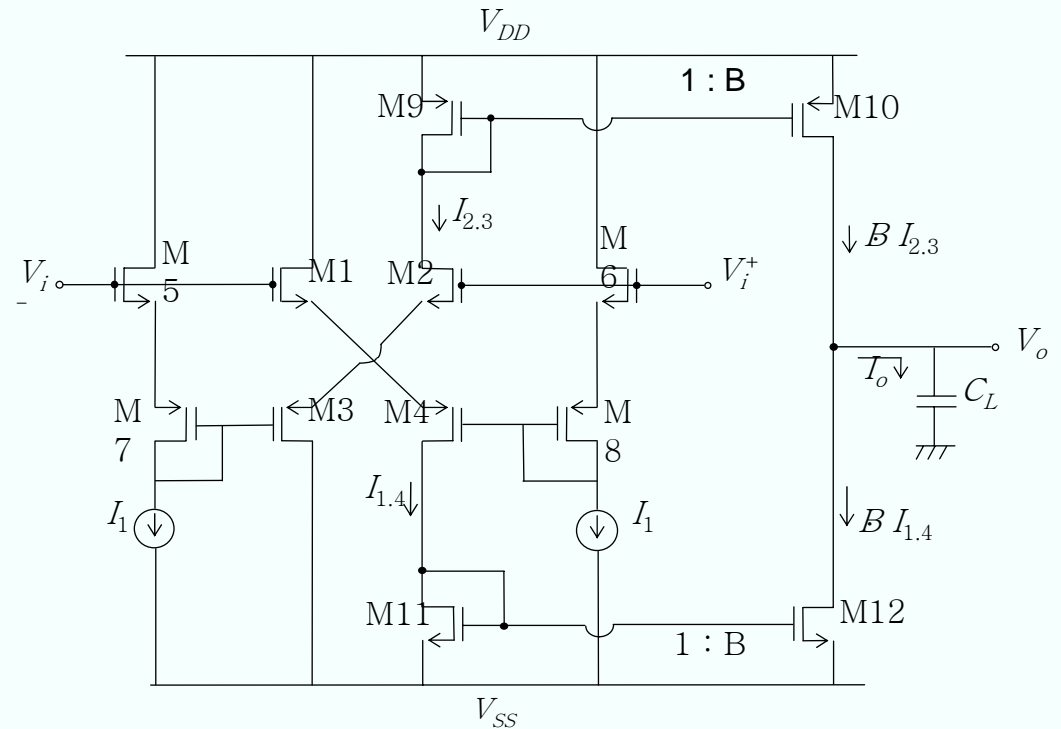

With bias circuit


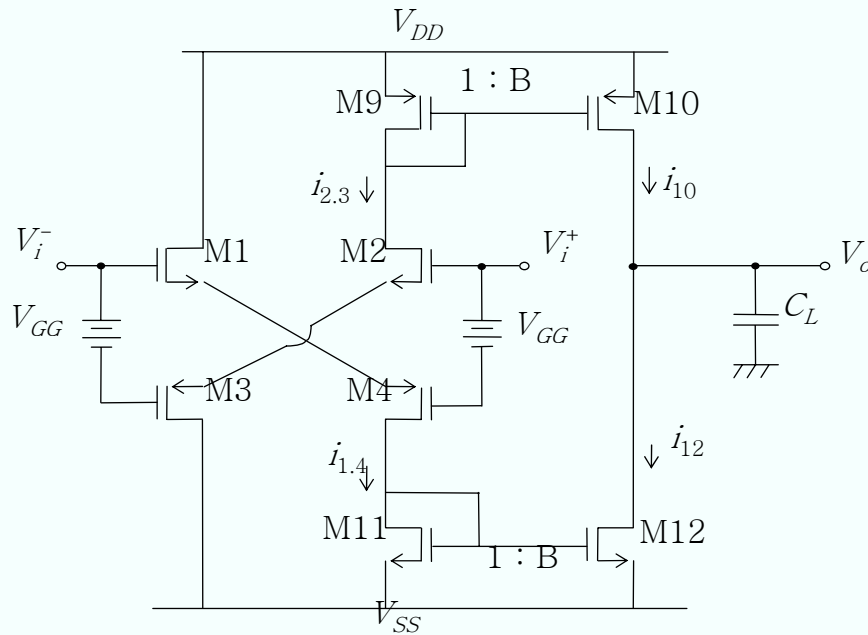


$$i_{2,3} = \frac{1}{r_{s2} + r_{s3}} \cdot (v_i^+ - v_i^-)$$

$$i_{10} = B \cdot i_{2,3} = \frac{B}{r_{s2} + r_{s3}} \cdot (v_i^+ - v_i^-)$$

$$i_{12} = B \cdot i_{1,4} = \frac{B}{r_{s1} + r_{s4}} \cdot (v_i^- - v_i^+)$$
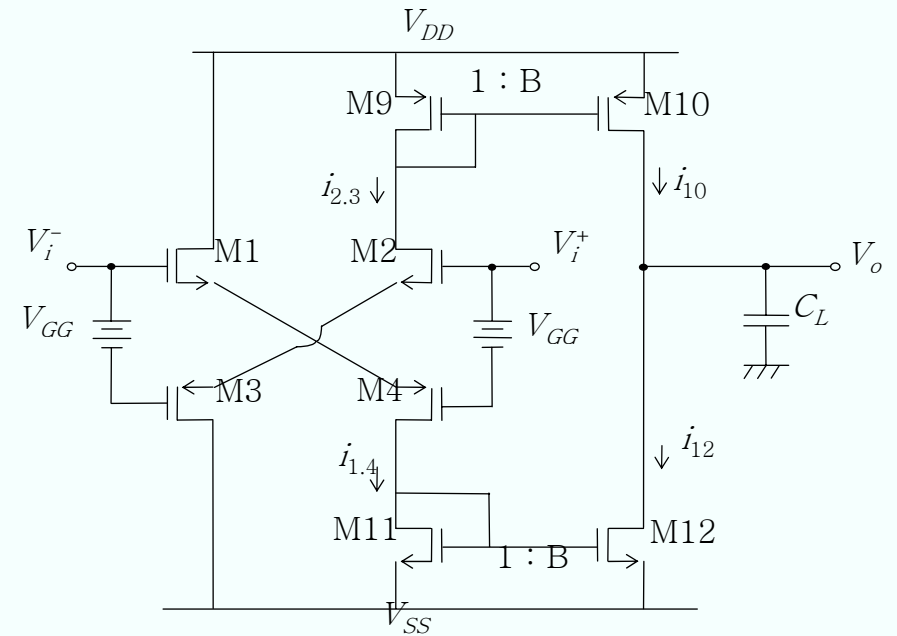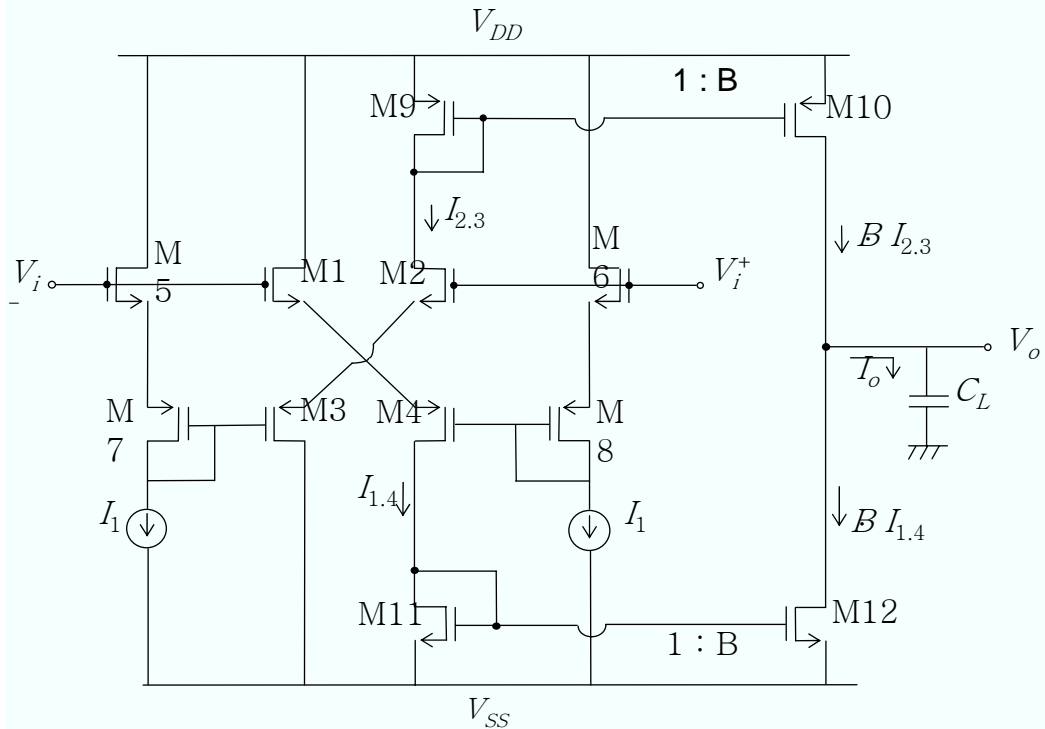
$$v_o = (i_{10} - i_{12}) \cdot (r_{o10} \parallel r_{o12}) = 2B \cdot \frac{r_{o10} \parallel r_{o12}}{r_{s1} + r_{s4}} \cdot (v_i^+ - v_i^-)$$



$$V_{GG} = V_{THn} + \sqrt{\frac{2I_B}{\mu_n C_{ox}} \cdot \left(\frac{L}{W}\right)_1} + |V_{THp}| + \sqrt{\frac{2I_B}{\mu_p C_{ox}} \cdot \left(\frac{L}{W}\right)_4}$$

$$\sqrt{\frac{2I_{1.4}}{\mu_n C_{ox}} \cdot \left(\frac{L}{W}\right)_1} + \sqrt{\frac{2I_{1.4}}{\mu_p C_{ox}} \cdot \left(\frac{L}{W}\right)_4} + V_{THn} + |V_{THp}| = V_{GG} - (V_i^+ - V_i^-)$$

$$(V_i^+ - V_i^-) < (V_{GG} - V_{THn} - |V_{THp}|) \quad I_{1.4} = I_B \cdot \left(1 - \frac{V_i^+ - V_i^-}{V_{GG} - V_{THn} - |V_{THp}|}\right)^2$$

$$(V_i^+ - V_i^-) \geq (V_{GG} - V_{THn} - |V_{THp}|) \quad I_{1.4} = 0$$

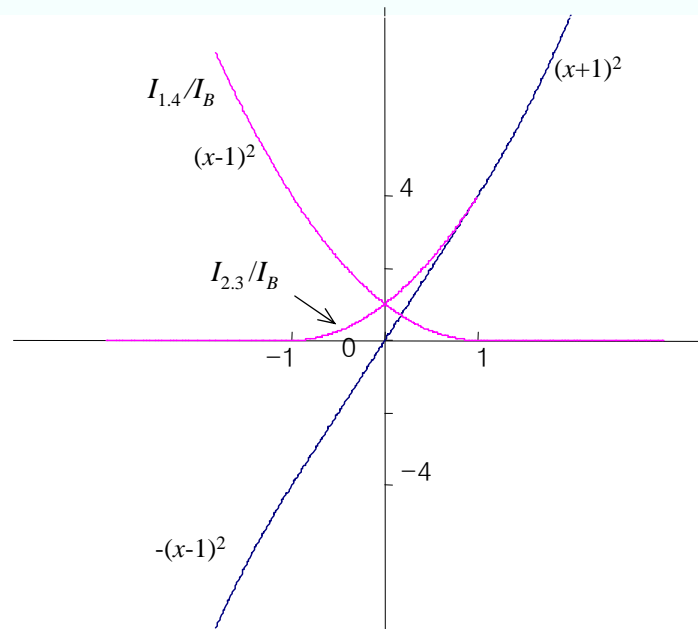


Fig 9.3.2 Output current versus differential input voltage of Class AB input OP amp

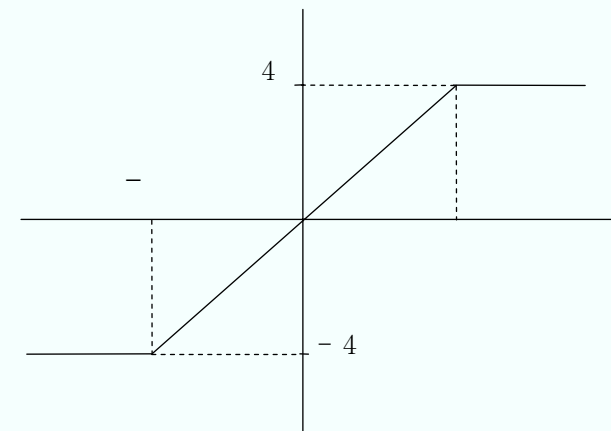


Fig 9.3.3 Output current versus differential input voltage of standard diff pair with a tail current source


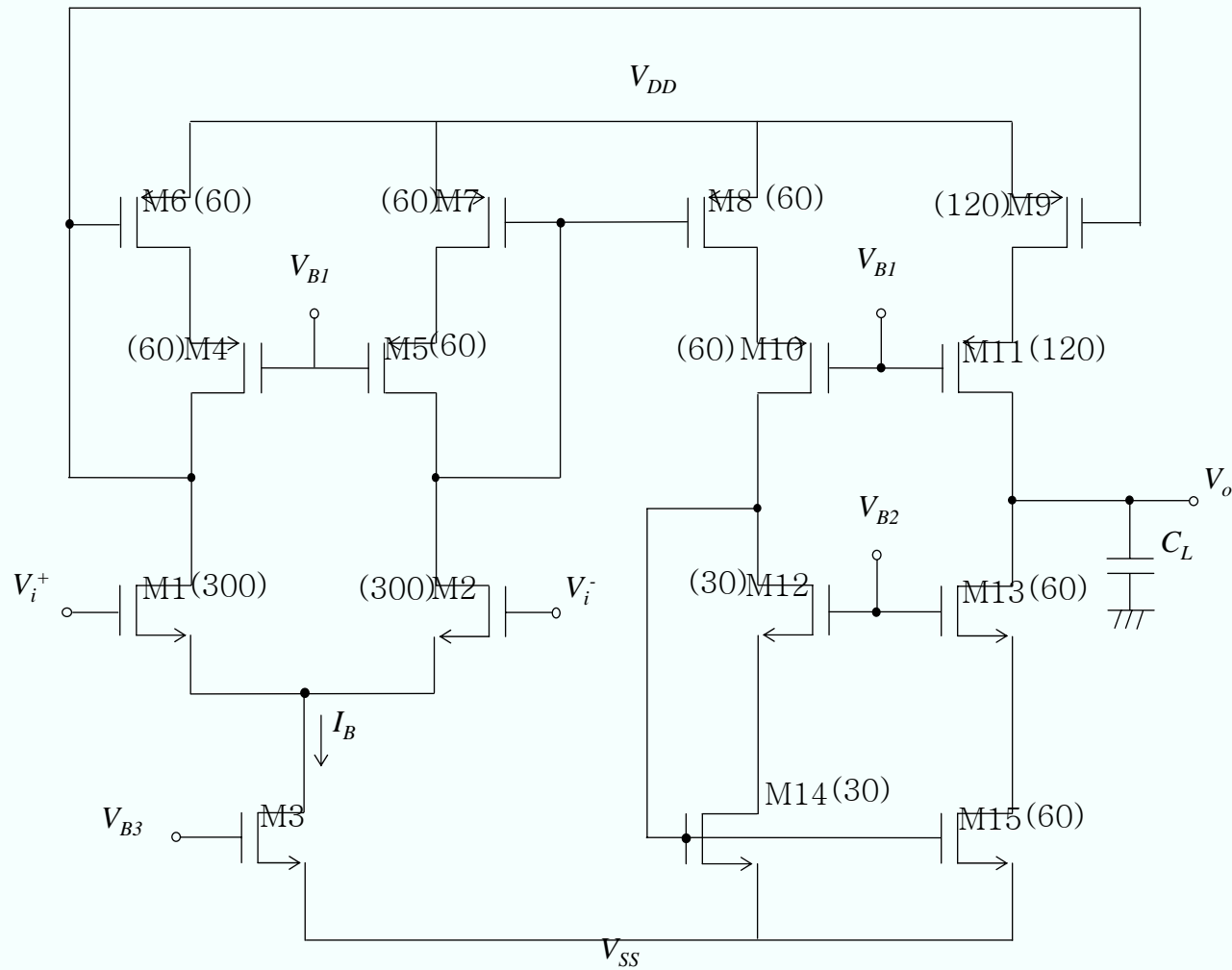


Fig 9.3.6 Current mirror OP amp

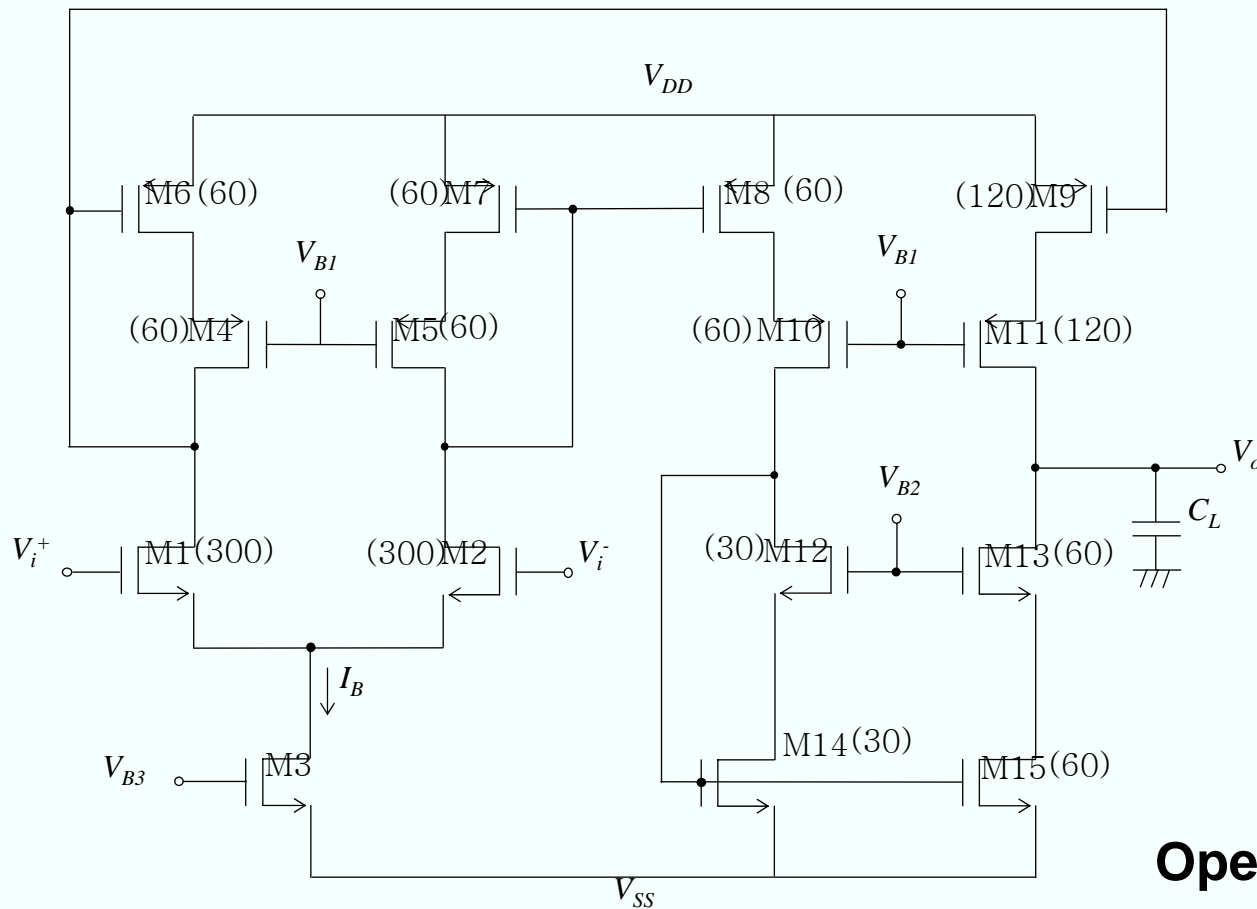

Large Slew rate
Large p2

$$R_o = (g_{m11}r_{o11} \cdot r_{o9}) \parallel (g_{m13}r_{o13} \cdot r_{o15})$$

$$A_{vd} = K \cdot g_{m1} \cdot R_o$$

$$A_{vd}(s) = \frac{K \cdot g_{m1} \cdot R_o}{1 + s \cdot R_o \cdot C_L}$$

$$\omega_T = \frac{K \cdot g_{m1}}{C_L}$$

$$\omega_{p2} = \frac{1}{RC} = \frac{1}{R_1C_1 + R_2C_2 + R_{10}C_{10}}$$

Open circuit time constant method

$$SR = \frac{K \cdot I_B}{C_L}$$

