

# CH10 Common mode feedback and fully differential OP amp


10.1 Common mode feedback (CMFB)

10.2 Fully differential OP amp
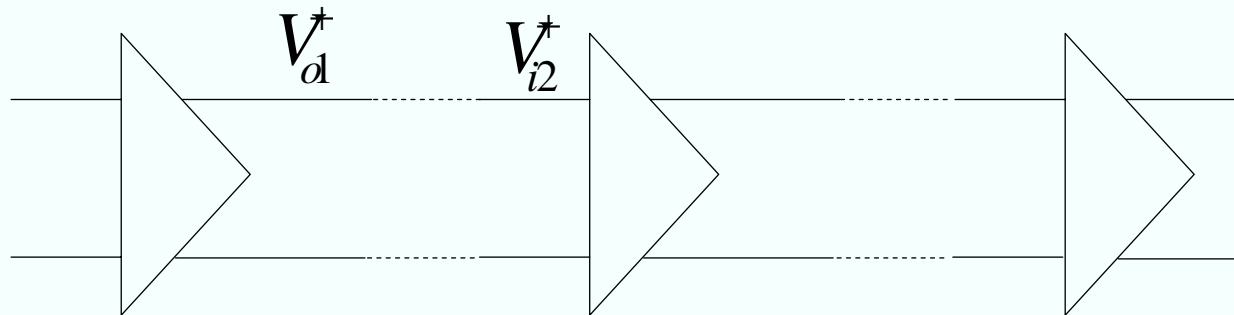
## Fully differential OP amp



Differential input, Differential output

- Easy to cascade OP amps
- insensitive to supply noise
- High gain Fully diff OP amp requires CMFB



Low-gain fully differential OP amp:

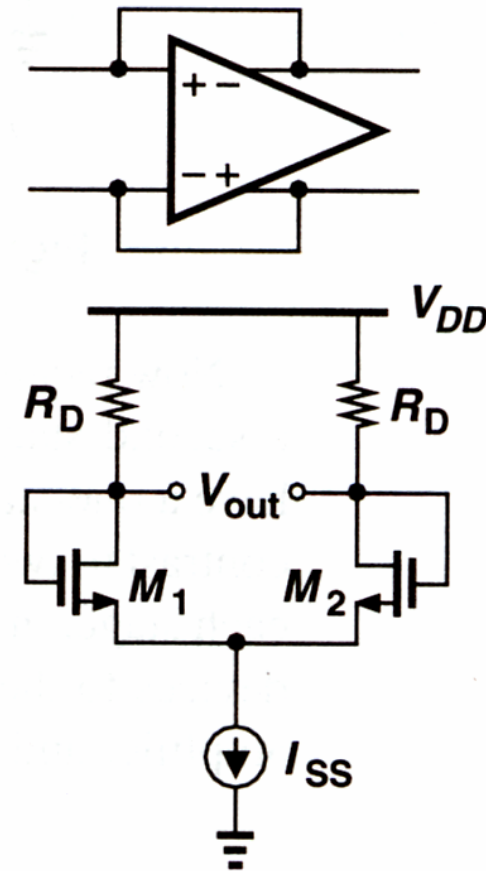
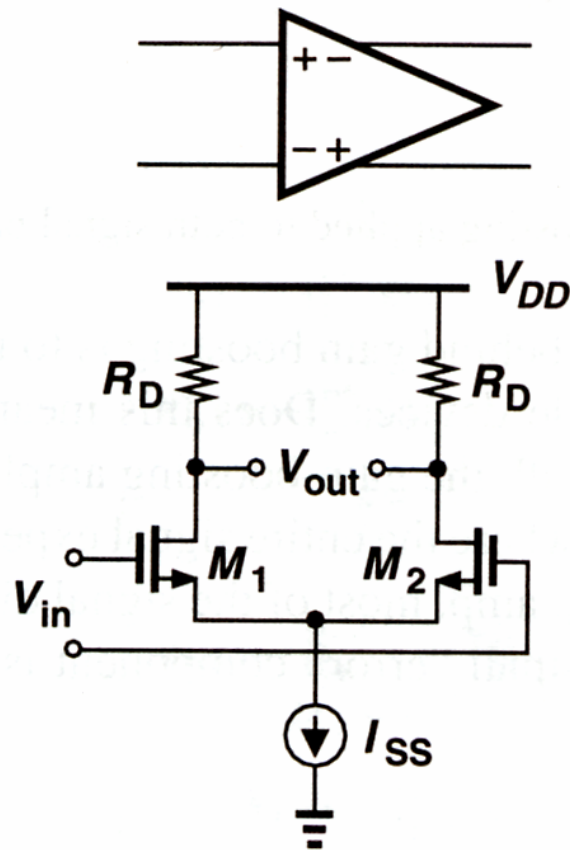
- $V_{outCM}$  common mode output voltage =  $V_{DD} - 0.5 R_D \times I_{SS}$  (well defined)
- CMFB ckt not required



$V_{outCM}$  : determined by unity-gain FB

High-gain fully differential OP amp:

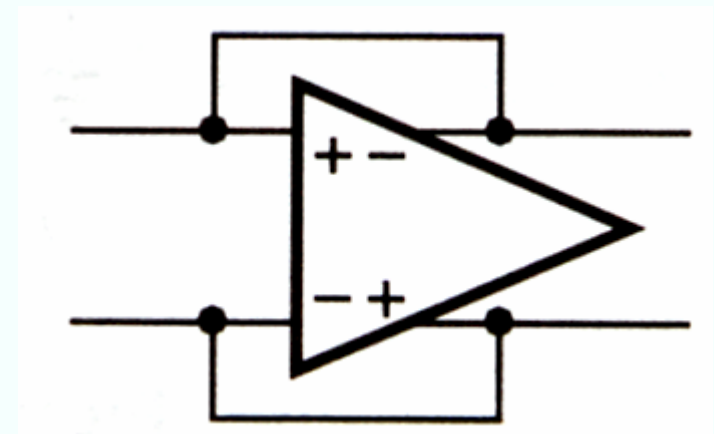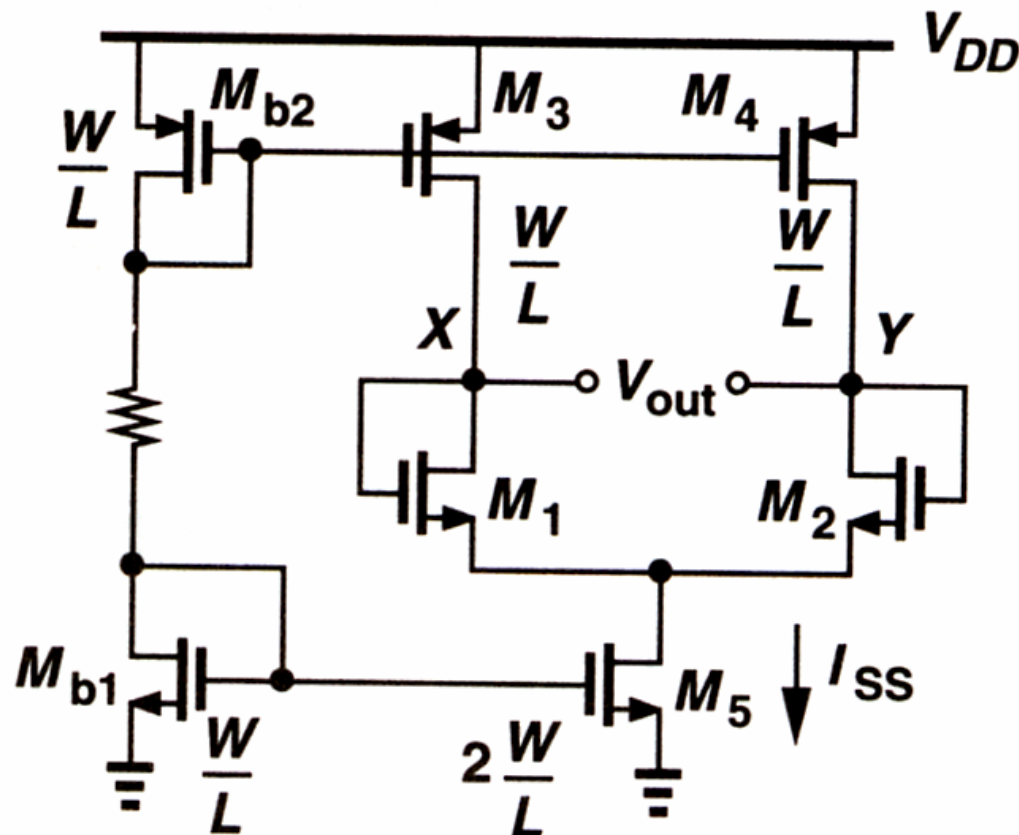
- $V_{outCM}$  : function of device parameters : Not well defined  
 (if  $I_{D3} > 0.5 I_{SS}$ ,  $M_3$   $M_4$  triode,  $V_{outCM}$ : close to  $V_{DD}$ ,  
 if  $I_{D3} < 0.5 I_{SS}$ ,  $M_5$  triode,  $V_{outCM}$ : close to  $V_{SS}$ ) → very low diff gain
- CMFB ckt required



Differential unity-gain FB

$V_{outCM}$  : well defined

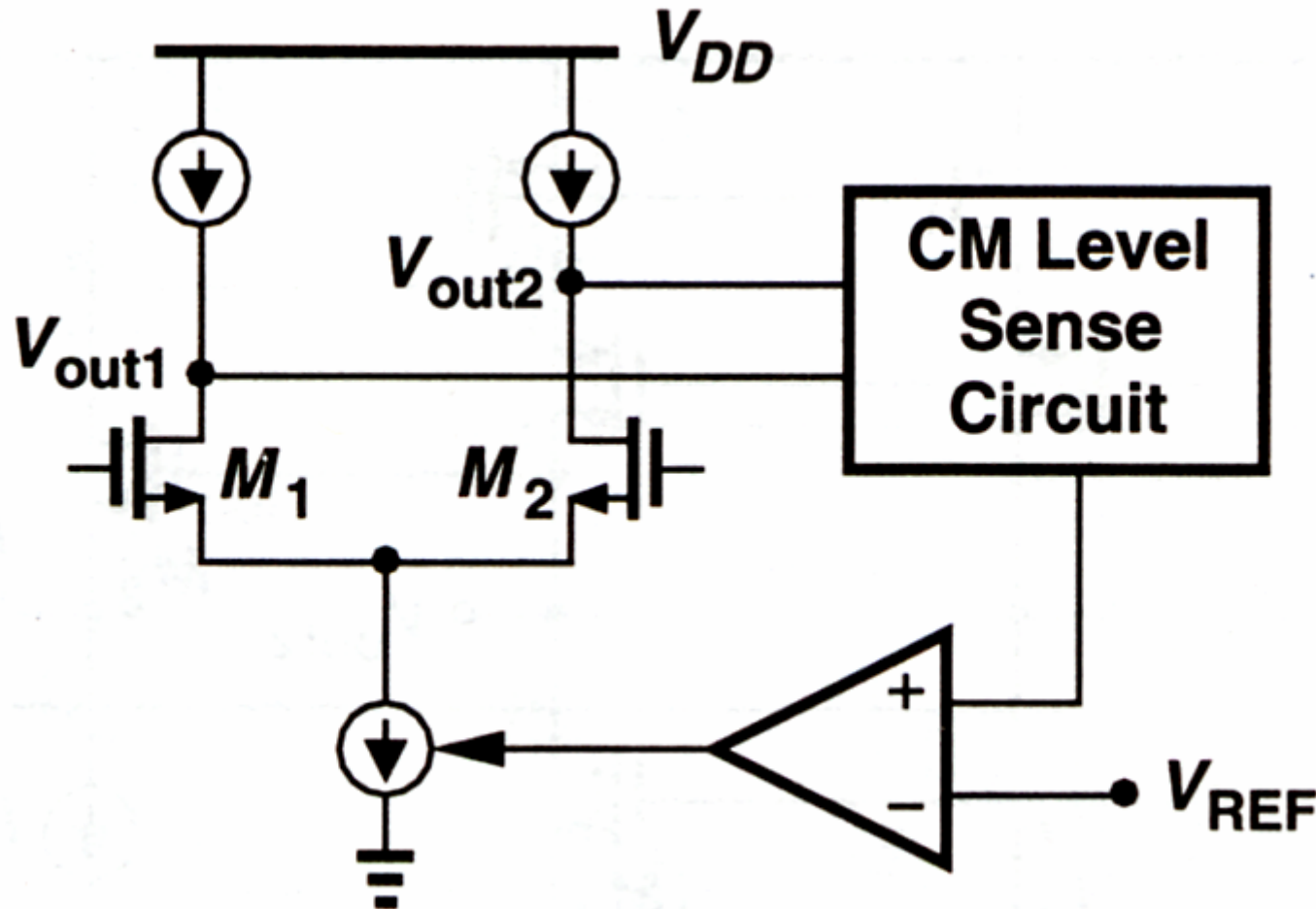→ all TR in saturation region → high diff gain




Only a part of current sources can be driven by CMFB circuit

# CMFB circuits

- (1) Source follower + resistor divider CMFB ckt
- (2) Triode TR CMFB ckt
- (3) Diff pair CMFB ckt
- (4) Switched-capacitor CMFB ckt
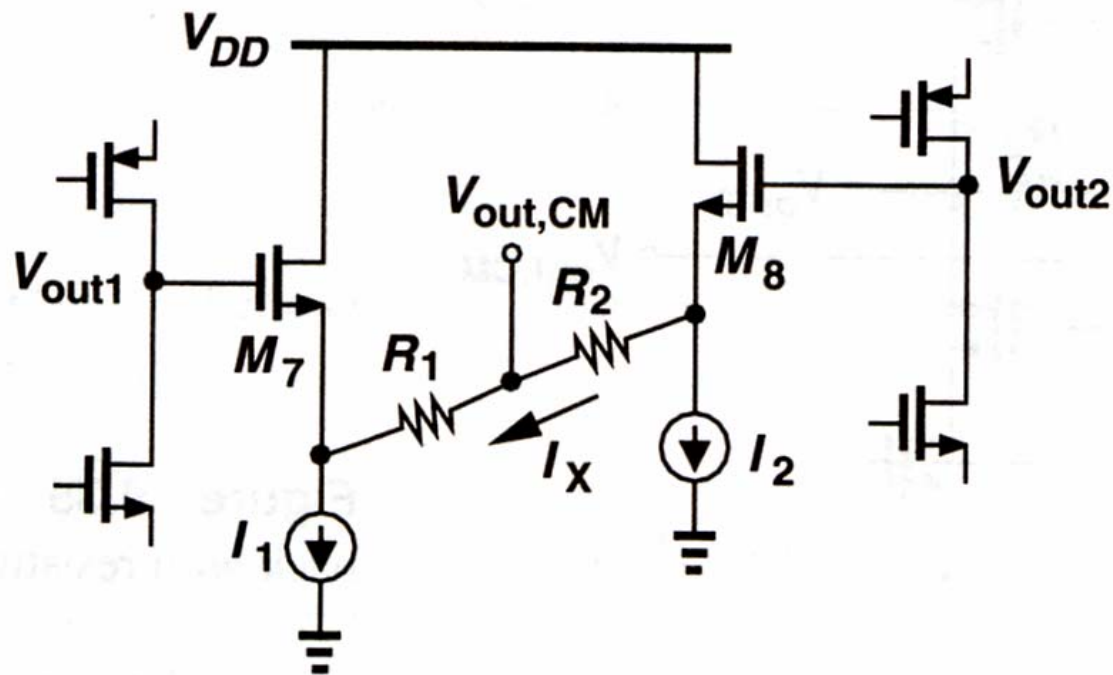
## (1) Source follower + resistor divider CMFB ckt




$V_{out}$  MIN limited to  $V_{GS7} + V(I1)$

$I1 \times (R1 + R2) > V_{out}$  swing  $\rightarrow$  large  $I1$  or large  $R1, R2$

Usually  $W/L$  ( $M7, M8$ ) very large


## (2) Triode TR CMFB ckt

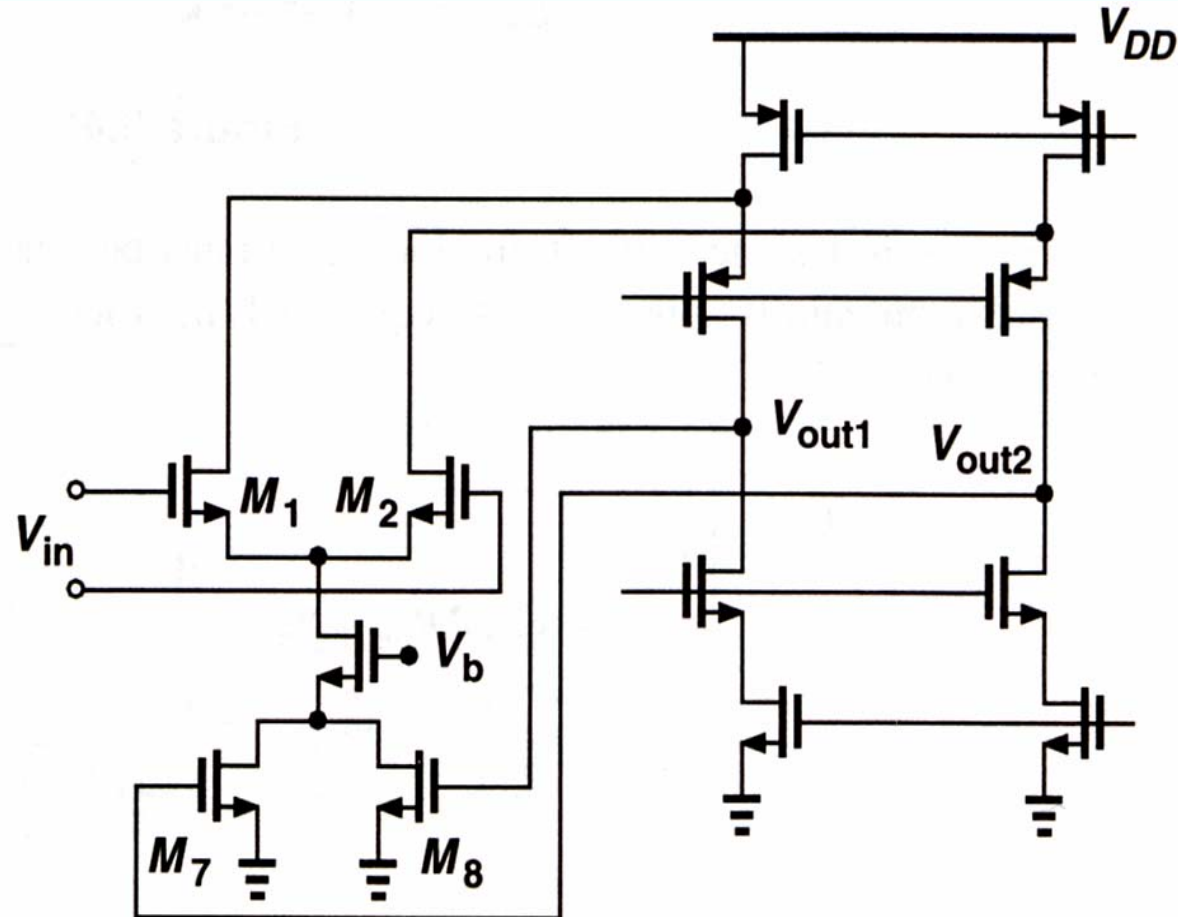

$V_{out}$  MIN limited to  $V_{THn}$   
 M7, M8: deep triode, large W/L  $\rightarrow$  large cap

M7, M8: not in the signal path  
 $\rightarrow$  large cap no effect in diff gain

### (3) Diff pair CMFB circuit 1

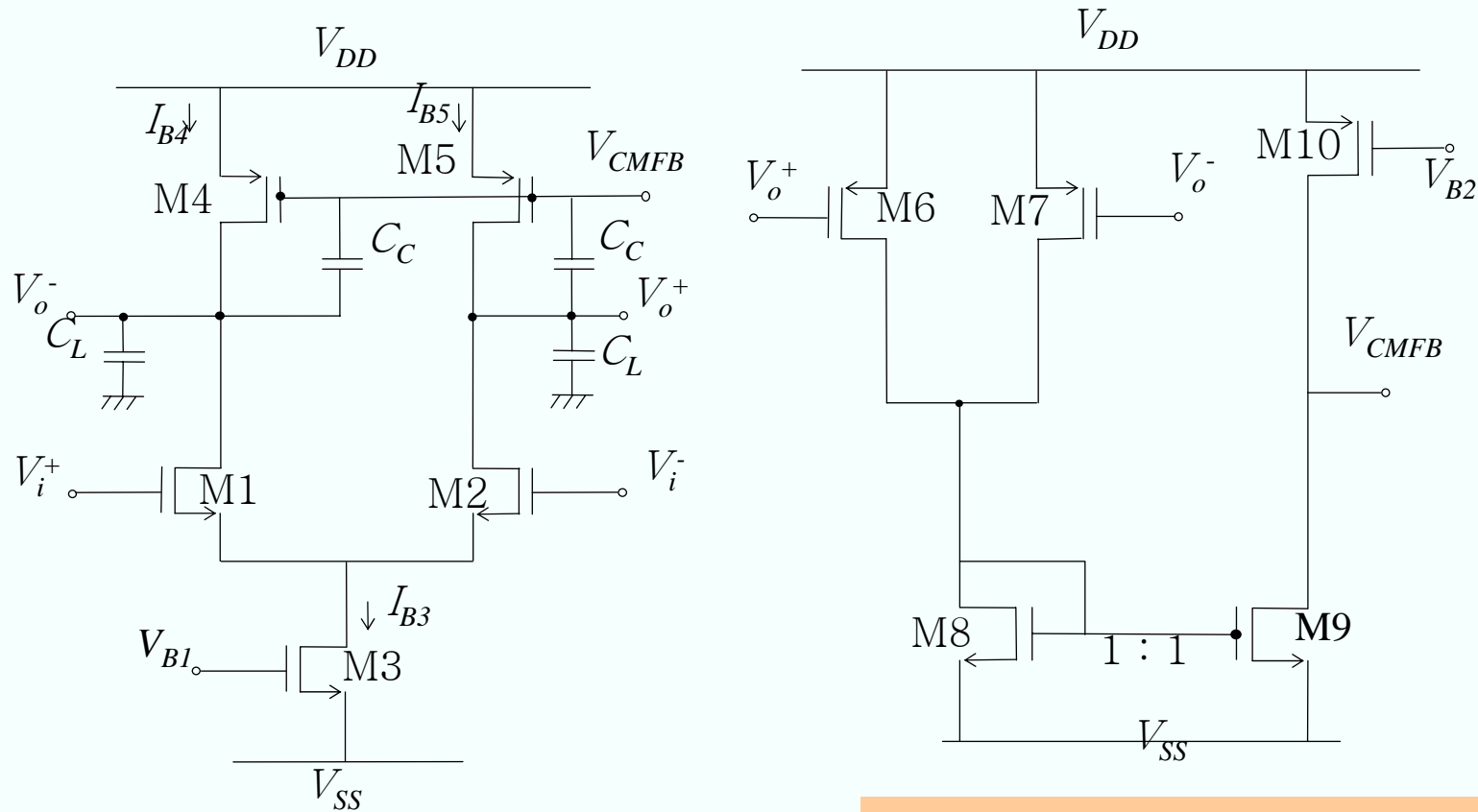


Fully Diff OP amp  
 Vout MAX limited to  $V_{DD} - |V_{THp}|$   
 2-stage CM amp  $\rightarrow$  needs freq compensation


CMFB circuit :  
 $V_{cmfb} = A \times 0.5(V_{o+} + V_{o-})$   
 W/L(M6,M7) very small to increase  
 linear operating range



# (4) Switched-capacitor CMFB ckt

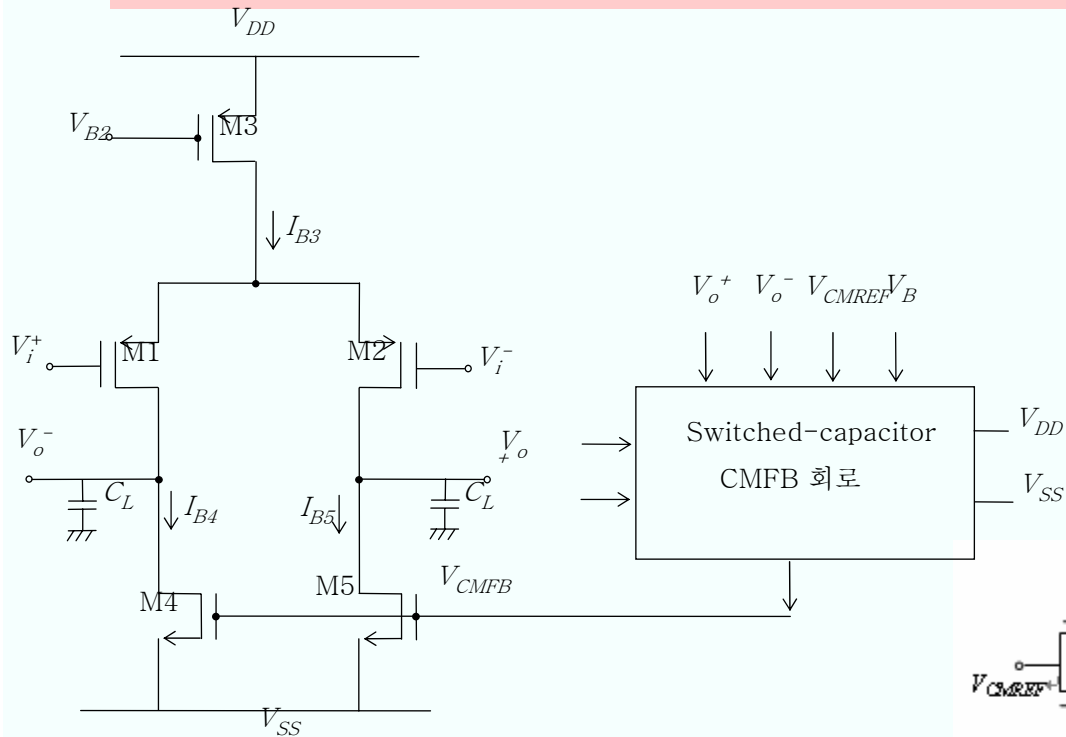

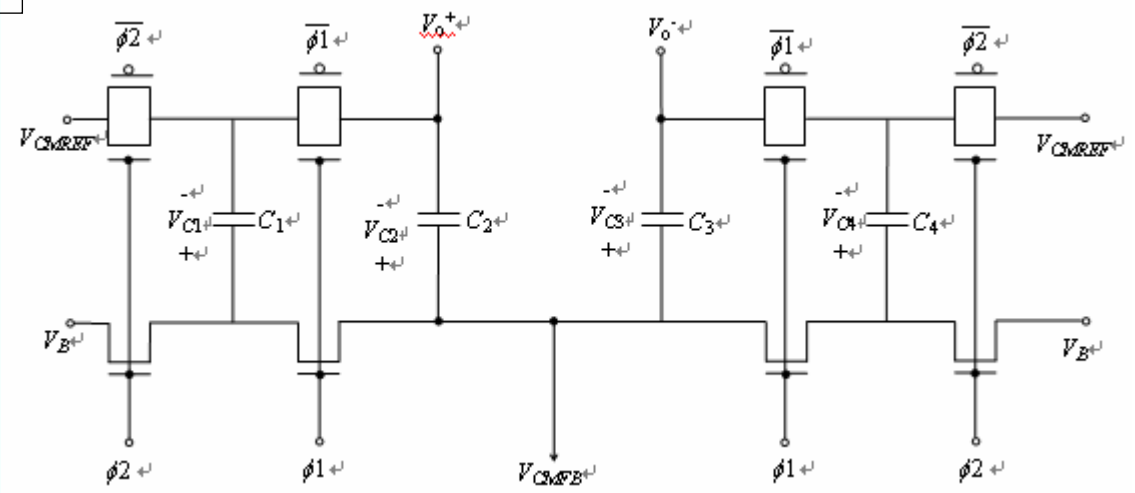
$$V_{CMFB} = V_B + \left( \frac{V_o^+ + V_o^-}{2} - V_{CMREF} \right)$$



Can be used in switching circuits  
No limit in Vout

10.1.1 Function of CMFB circuit

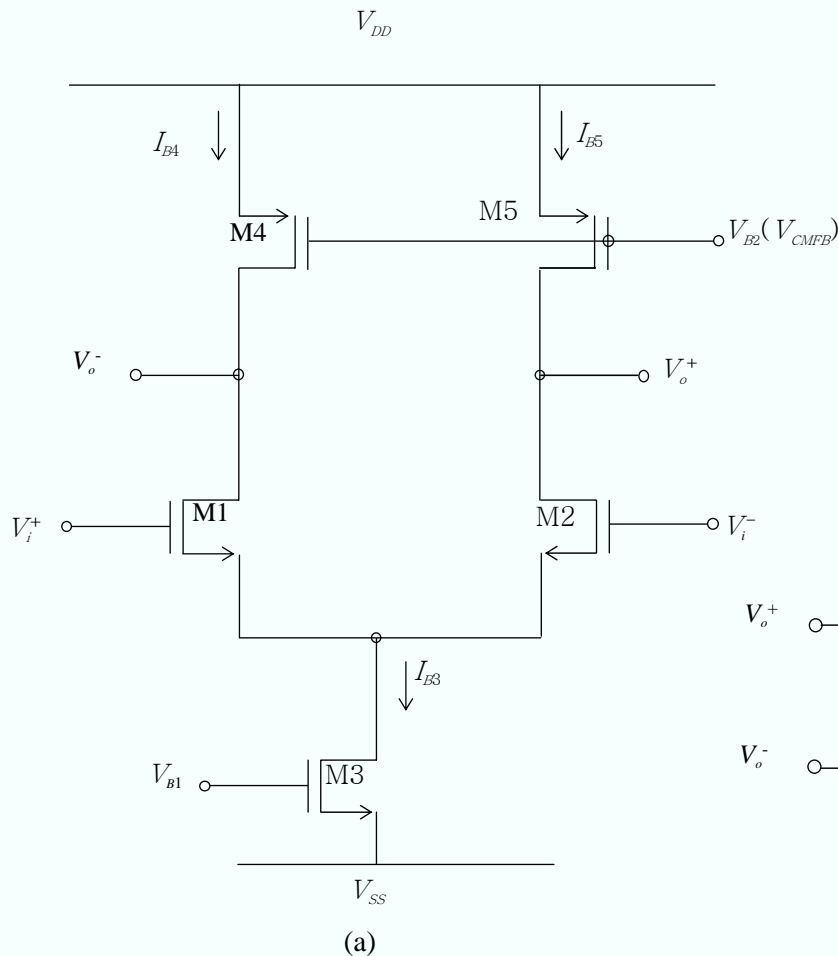

$$\frac{\partial V_o^+}{\partial V_{B1}} = \frac{\partial V_o^-}{\partial V_{B1}} = \frac{1}{2} \cdot g_{m3} \cdot \left\{ r_{o4} \parallel (g_{m1} r_{o1} \cdot 2r_{o3}) \right\}$$

$$\frac{\partial V_o^+}{\partial V_{B2}} = \frac{\partial V_o^-}{\partial V_{B2}} = g_{m4} \cdot r_{o4} \parallel (g_{m1} r_{o1} \cdot 2r_{o3})$$

Apply a negative FB on CM signal

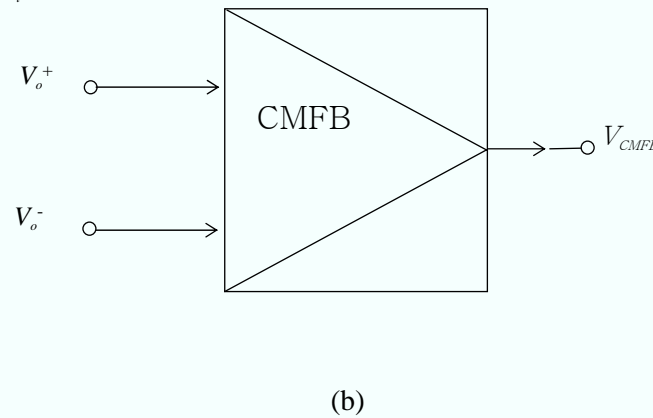


Fig. 10.1.2 (a) Simple fully differential CMOS OP amp circuit  
 (b) CMFB(common mode feedback) circuit

## 10.1.2 CMFB circuit 1 using MOS diff amp (\*)


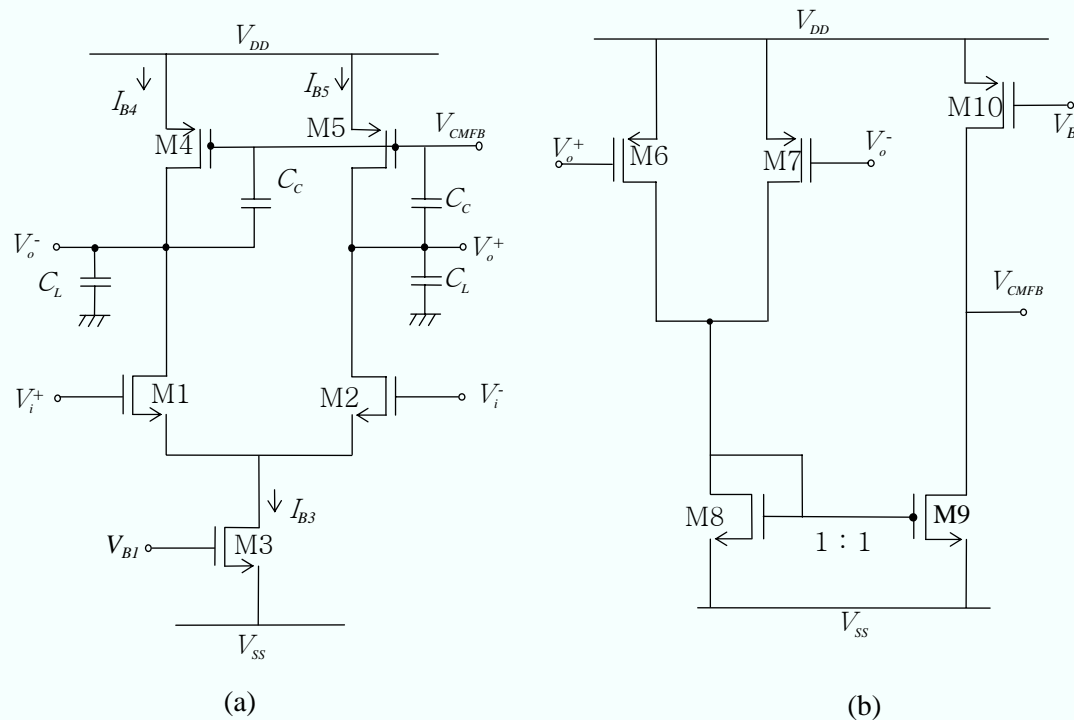


Fig10.1.3 CMFB circuit 1 using MOS diff amp (a) OP amp (b) CMFB circuit

$$v_{CMFB} = + g_{m6} \cdot (r_{o9} \parallel r_{o10}) \cdot (v_o^+ + v_o^-)$$

No reference for  $V_{outCM}$

## Small-signal common mode voltage gain

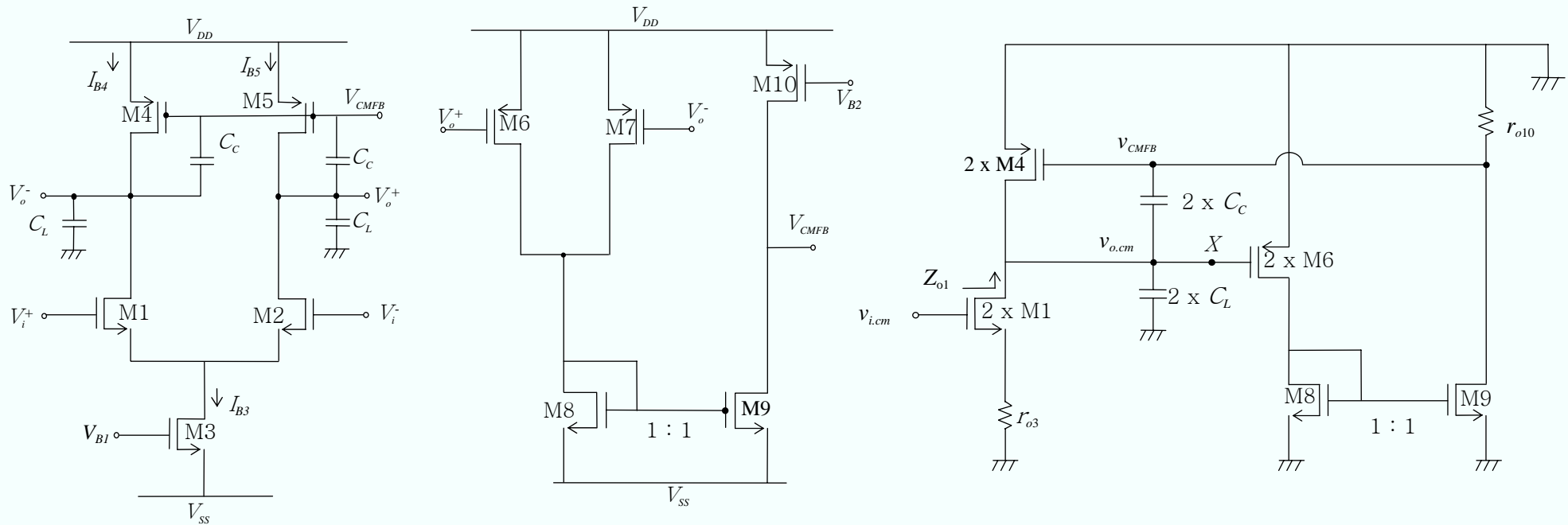

$$(CMFB \text{ loop gain}) = \frac{2g_{m6} \cdot (r_{o9} \parallel r_{o10}) \cdot (g_{m4} \cdot r_{o4})}{1 + s \cdot (r_{o9} \parallel r_{o10}) \cdot (g_{m4} \cdot r_{o4}) \cdot (2C_c)}$$

$$g_{m1}r_{o1} \cdot r_{o3} \gg 0.5 \cdot r_{o4}$$

$$\omega_{T.CMFB} = \frac{g_{m6}}{C_c}$$



## Small-signal differential mode voltage gain


$$i_x = \frac{v_x}{r_{o4} + r_{o5}} + \frac{v_x}{2r_{o1}} = \frac{v_x}{2r_{o4}} + \frac{v_x}{2r_{o1}} = \frac{v_x}{2 \cdot (r_{o1} \parallel r_{o4})}$$

$$R_o = 2 \cdot (r_{o1} \parallel r_{o4})$$

$$A_{vd} \triangleq \frac{v_o^+ - v_o^-}{v_i^+ - v_i^-} = \frac{g_{m1} \cdot (r_{o1} \parallel r_{o4})}{1 + s \cdot (r_{o1} \parallel r_{o4}) \cdot (C_L + C_C)}$$

$$\omega_{T.dm} = \frac{g_{m1}}{C_C + C_L}$$

$$\omega_{T.CMFB} = \frac{g_{m6}}{C_C}$$

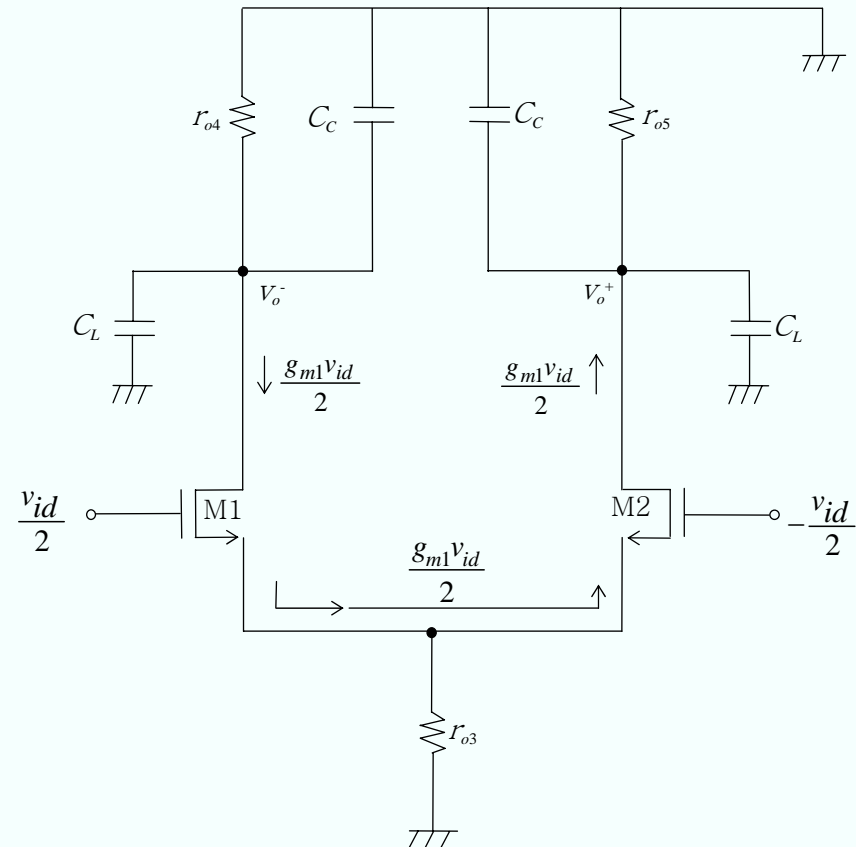

$$A_{vd} \triangleq \frac{v_o^+ - v_o^-}{v_i^+ - v_i^-} = \frac{g_{m1} \cdot (r_{o1} \parallel r_{o4})}{1 + s \cdot (r_{o1} \parallel r_{o4}) \cdot (C_L + C_C)}$$

$$\omega_{T.dm} = \frac{g_{m1}}{C_C + C_L}$$

$$(\text{CMFB loop gain}) = \frac{2g_{m6} \cdot (r_{o9} \parallel r_{o10}) \cdot (g_{m4} \cdot r_{o4})}{1 + s \cdot (r_{o9} \parallel r_{o10}) \cdot (g_{m4} \cdot r_{o4}) \cdot (2C_c)}$$

$$\omega_{T.CMFB} = \frac{g_{m6}}{C_c}$$

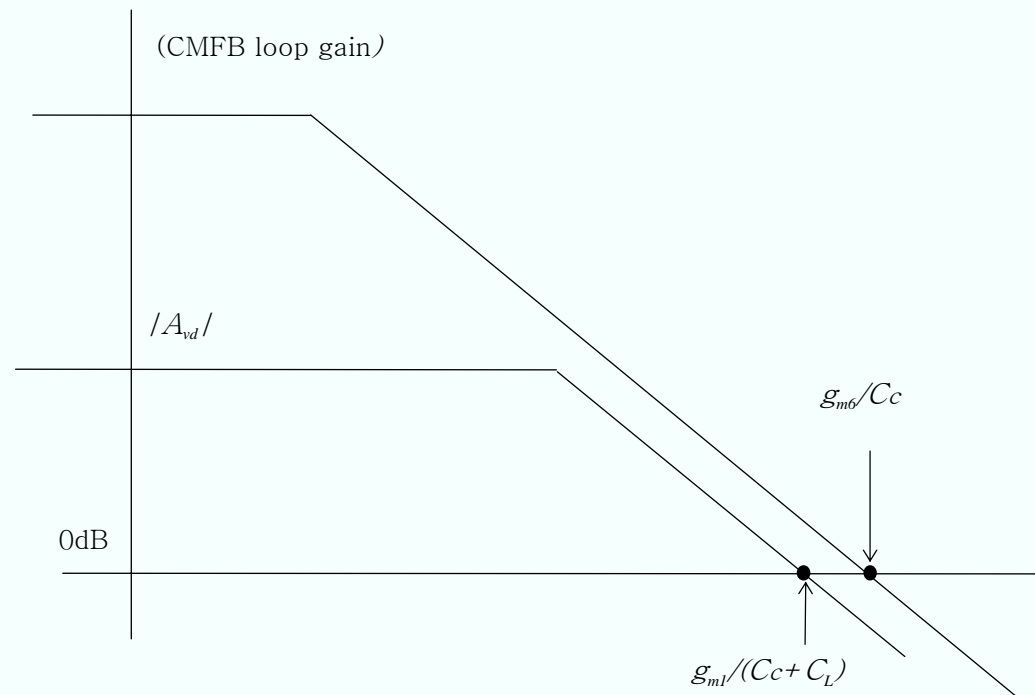


Fig 10.1.6 Bode plot of CMFB loop gain of Fig.10.1.3 circuit






## 10.1.3 CMFB circuit using a triode TR feedback

$$g_{m6} = \mu_p C_{ox} \cdot \left(\frac{W}{L}\right)_6 \cdot |V_{DS}|$$

M6, M7 deep triode  
 → No gain stage  
 → No freq comp.

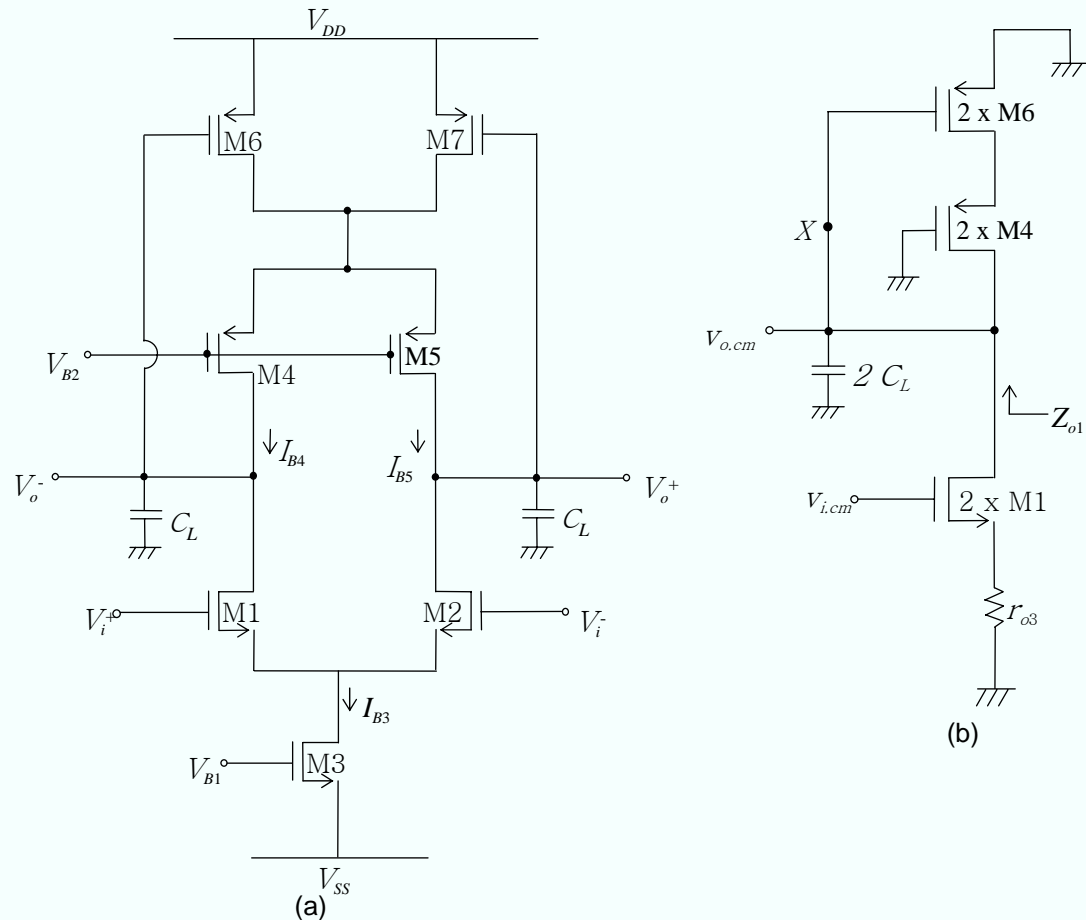

**Fig 10.1.7** (a) Fully differential CMOS OP amp using a triode TR feedback


(b) Small-signal equivalent circuit of (a) circuit

$$(CMFB \text{ loop gain}) = 2g_{m6} \cdot \frac{\frac{r_{o6}}{2}}{\frac{r_{s4}}{2} + \frac{r_{o6}}{2}} \cdot R_o \cdot \frac{1}{1 + s \cdot R_o \cdot 2C_L} = 2 \cdot g_{m6} R_o \cdot \frac{r_{o6}}{r_{s4} + r_{o6}} \cdot \frac{1}{1 + s \cdot R_o \cdot 2C_L}$$

$$R_o = \left( 2g_{m1} \cdot \frac{r_{o1}}{2} \cdot r_{o3} \right) \parallel \left( 2g_{m4} \cdot \frac{r_{o4}}{2} \cdot \frac{r_{o6}}{2} \right) = (g_{m1} r_{o1} \cdot r_{o3}) \parallel \left\{ \frac{g_{m4} r_{o4} \cdot r_{o6}}{2} \right\} \approx \frac{g_{m4} r_{o4} \cdot r_{o6}}{2}$$

$GBW(CMFB) =$
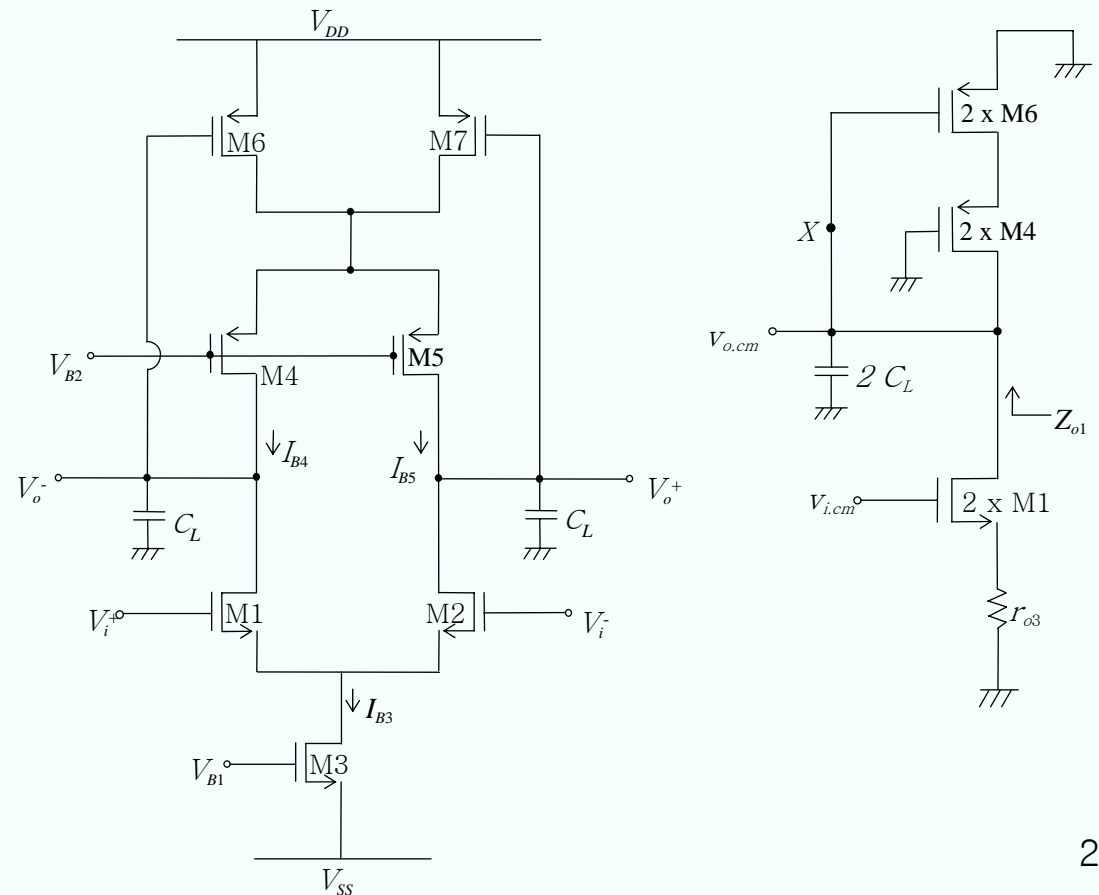
$$\frac{g_{m6}}{C_L} \cdot \frac{r_{o6}}{r_{s4} + r_{o6}}$$



## Small-signal common mode voltage gain



$$A_{vc}(s) \triangleq \frac{v_{o.cm}}{v_{i.cm}} = - \frac{Z_{o1}(s)}{\frac{r_{s1}}{2} + r_{o3}} \approx - \frac{Z_{o1}(s)}{r_{o3}}$$

$$(2g_{m4} \cdot \frac{r_{o4}}{2} \cdot \frac{r_{o6}}{2}) \parallel \frac{1}{s \cdot 2C_L} = (0.5 \cdot g_{m4} r_{o4} \cdot r_{o6}) \parallel \frac{1}{s \cdot 2C_L} = \frac{0.5 \cdot g_{m4} r_{o4} \cdot r_{o6}}{1 + s \cdot g_{m4} r_{o4} \cdot r_{o6} \cdot C_L}$$

$$Z_{o1}(s) = \frac{0.5 \cdot g_{m4} r_{o4} \cdot r_{o6}}{1 + s \cdot g_{m4} r_{o4} \cdot r_{o6} \cdot C_L} \cdot \frac{1}{1 + (\text{CMFB loop gain})}$$

$$\approx \frac{0.5 \cdot g_{m4} r_{o4} \cdot r_{o6}}{1 + s \cdot g_{m4} r_{o4} \cdot r_{o6} \cdot C_L} \cdot \frac{1}{(\text{CMFB loop gain})} = \frac{r_{s4} + r_{o6}}{2 \cdot g_{m6} r_{o6}}$$

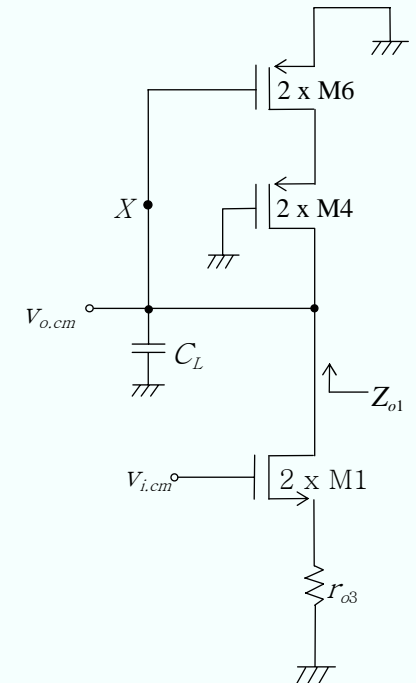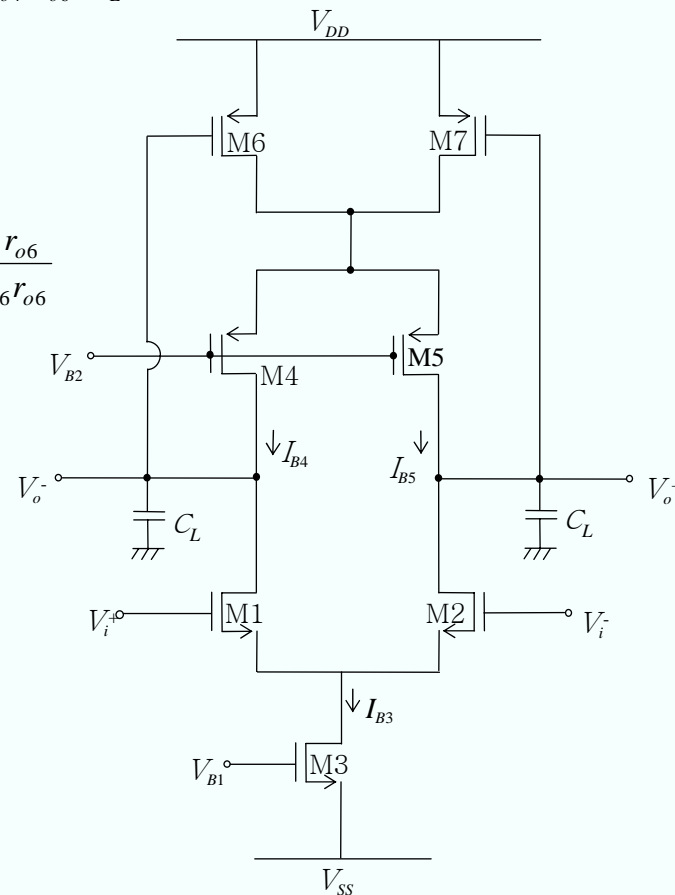
$$A_{vc}(s) = - \frac{1}{2 \cdot g_{m6} r_{o3}} \cdot \frac{r_{s4} + r_{o6}}{r_{o6}}$$



## Small-signal differential mode voltage gain

$$A_{vd}(s) \triangleq \frac{v_{od}}{v_{id}} = \frac{g_{m1} \cdot (r_{o1} \parallel r_{o4})}{1 + s \cdot (r_{o1} \parallel r_{o4}) \cdot C_L}$$


$$GBW(A_{vd}) = \frac{g_{m1}}{C_L}$$

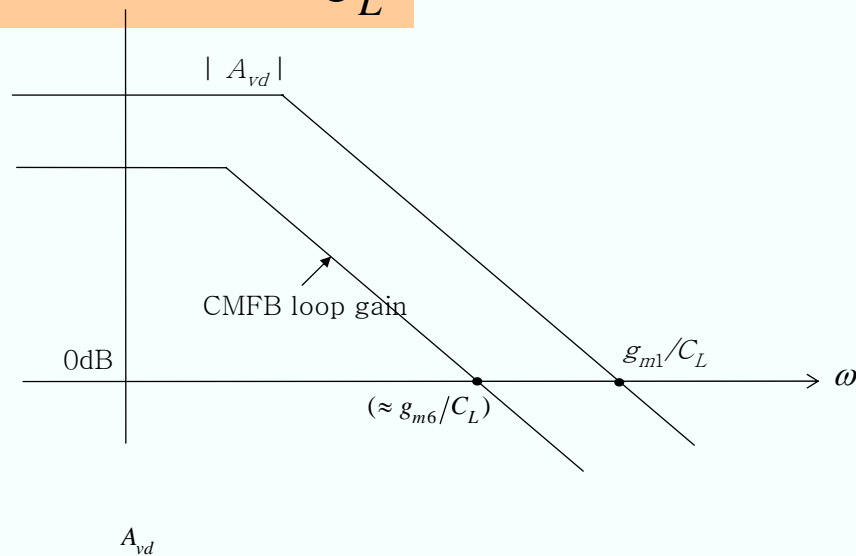


$$g_{m1} = \mu_n C_{ox} \cdot \left(\frac{W}{L}\right)_1 \cdot (V_{GS1} - V_{THn})$$


$$g_{m6} = \mu_p C_{ox} \cdot \left(\frac{W}{L}\right)_6 \cdot |V_{DS6}|$$

Triode region

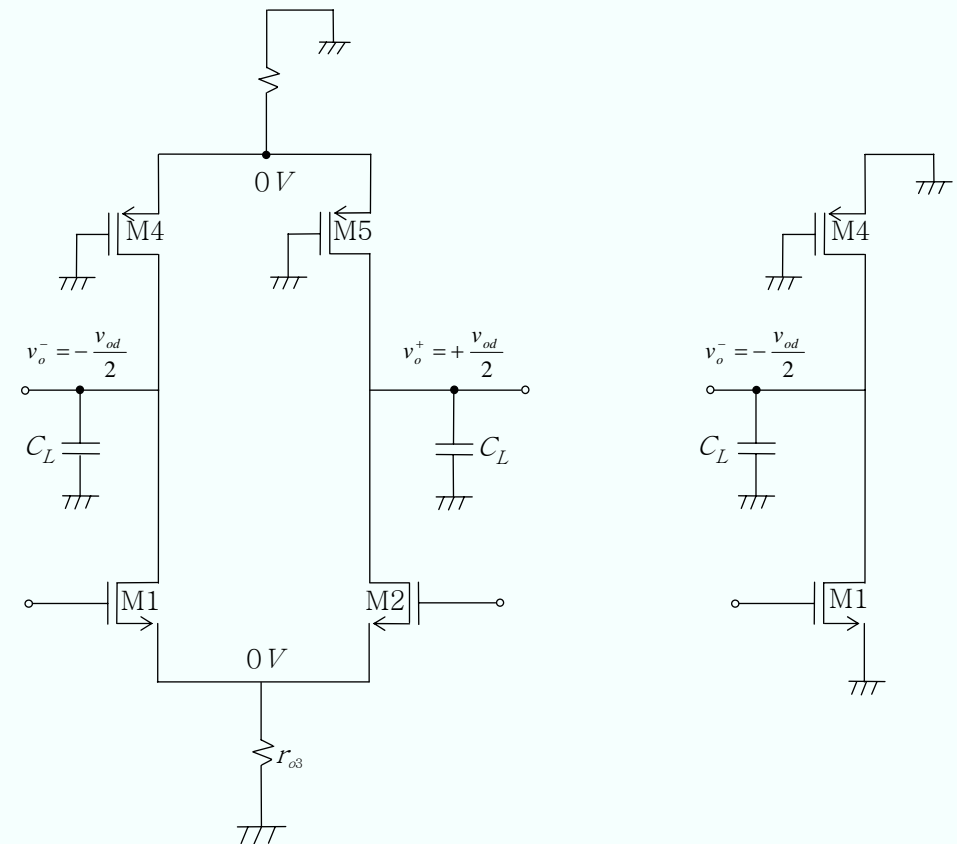

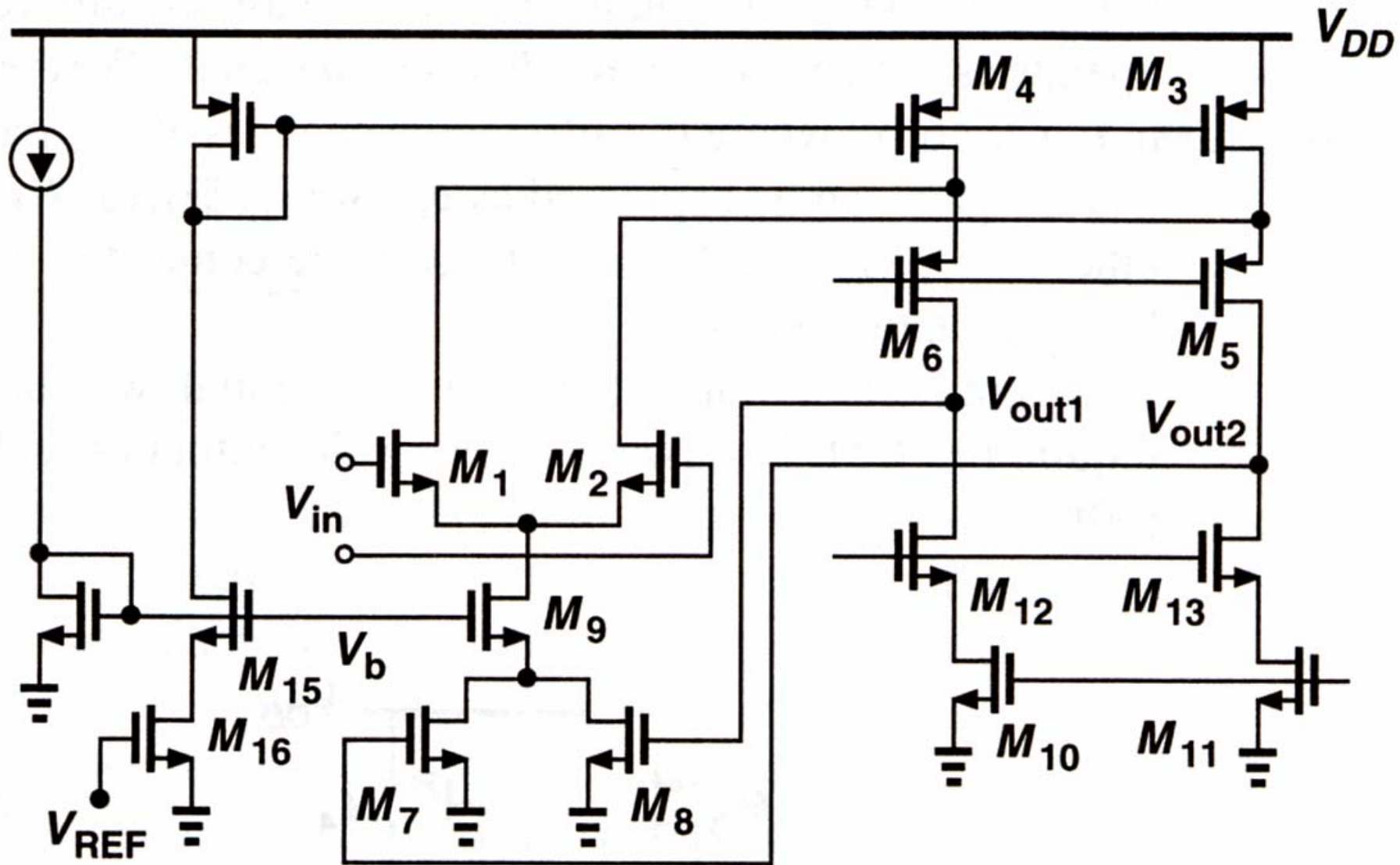


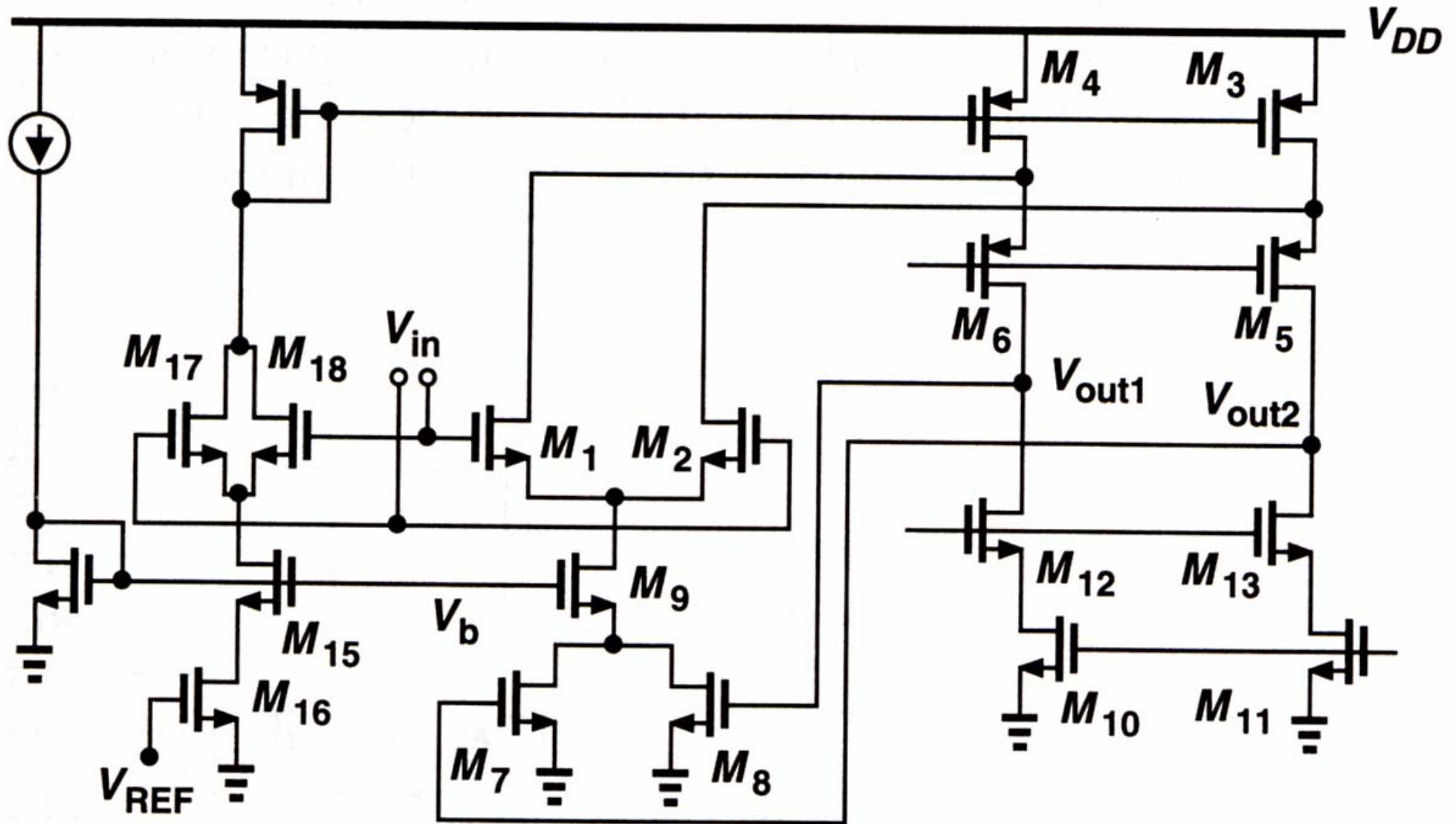$V_{outCM}$  slightly larger than  $V_{REF}$  because  $V_{DS}(M_{15}) \gg V_{DS}(M_9)$



$$V_{outCM} \approx V_{REF}$$

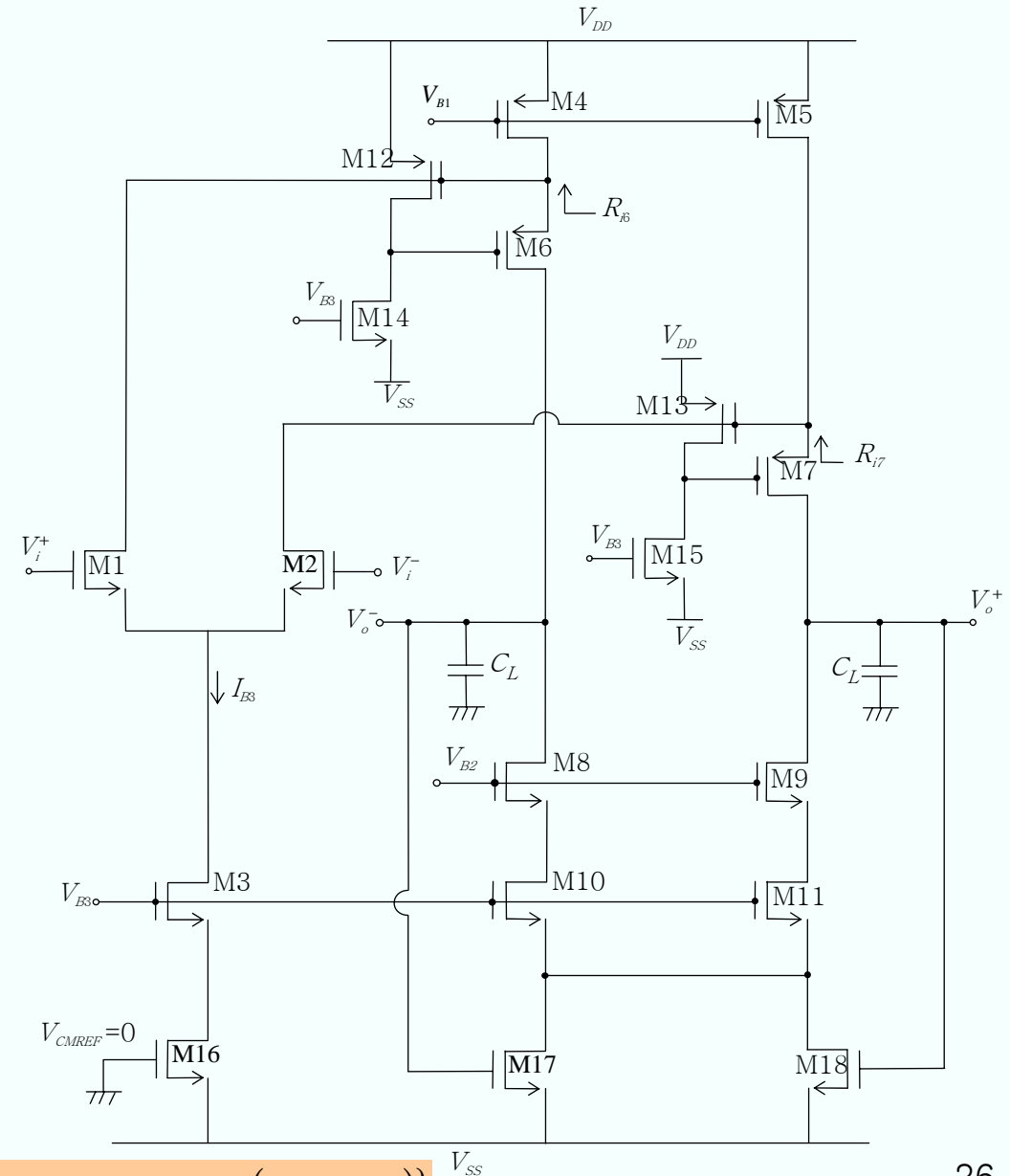Fully differential Folded cascode OP amp  
With gain boosting for PMOS and  
Triode TR feedback CMFB



$$R_o = \left\{ g_{m9} r_{o9} \cdot r_{o11} \cdot (0.5 \cdot g_{m11} r_{o18} + 1) \right\} \parallel \left\{ g_{m7} r_{o7} \cdot g_{m13} (r_{o13} \parallel r_{o15}) \cdot (r_{o2} \parallel r_{o5}) \right\}$$




CMFB loop gain =

$$2 \cdot g_{m6} \cdot (0.5r_{o6} \parallel r_{o12}) \cdot g_{m4}r_{o4}$$

Error voltage =

$$0.5 \cdot (V_o^+ + V_o^-) - V_{CMREF}$$
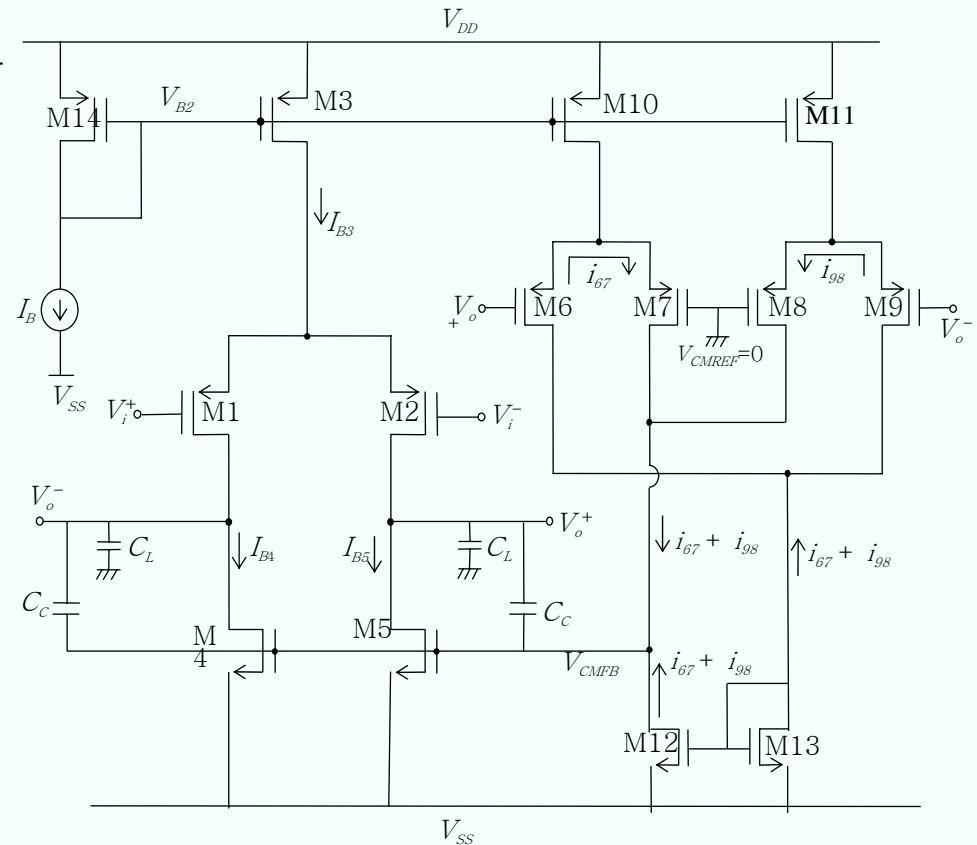
$$V_{OC} = \frac{\text{Required } V_{CMFB} - (V_{CMFB} @ 0.5(V_o^+ + V_o^-) = V_{CMREF})}{\text{Small-signal Voltage Gain of CMFB circuit}}$$



$$\frac{(W/L)_3}{(W/L)_{10}} = 2 \cdot \frac{(W/L)_4}{(W/L)_{12}}$$

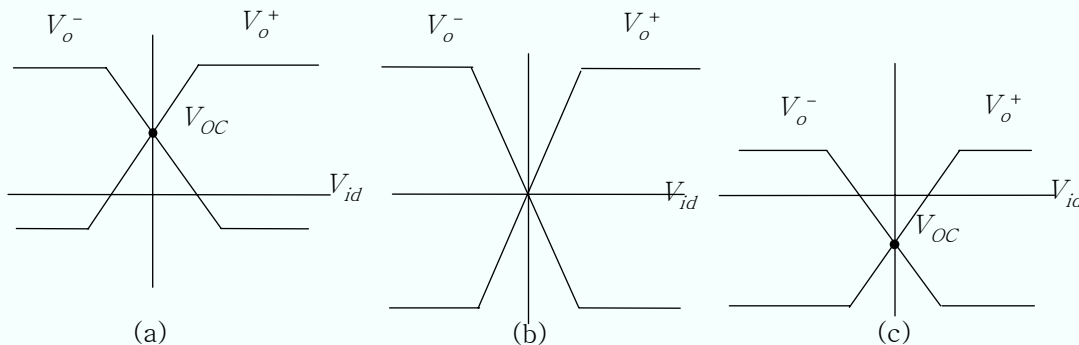


Fig 10.1.12 DC transfer curve of Fig 10.1.11 circuit for different voltage gains of CMFB circuits (a) & (c): Low CMFB gain (b) Large CMFB gain

Requires a large common mode gain for small offset

## Small-signal common mode voltage gain

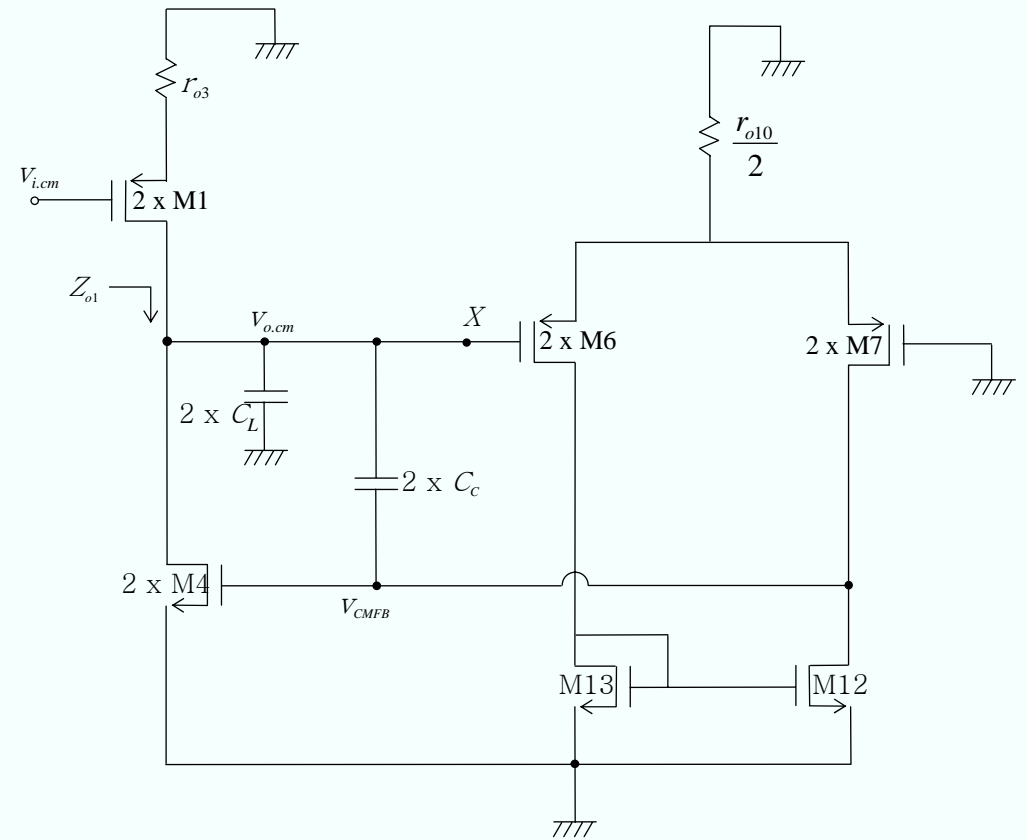
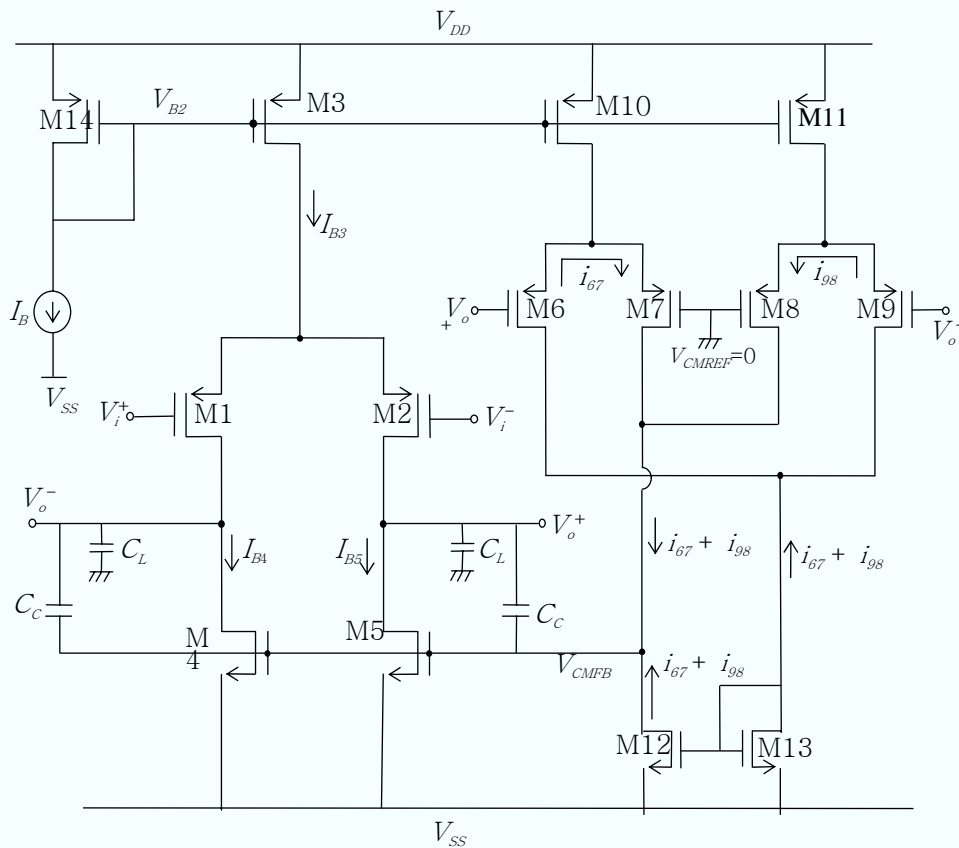


Fig 10.1.13 Common mode small-signal circuit of Fig 10.1.11 circuit

## Small-signal common mode voltage gain

$$(CMFB \text{ loop gain}) = \frac{2g_{m6} \cdot \left( \frac{r_{o6}}{2} \parallel r_{o13} \right) \cdot g_{m4}r_{o4}}{1 + s \cdot 2C_C \cdot \left( \frac{r_{o6}}{2} \parallel r_{o13} \right) \cdot g_{m4}r_{o4}}$$


$$Z_{o1}(\text{no feedback}) = \frac{0.5 \cdot r_{o4}}{1 + s \cdot r_{o4} \cdot (C_L + C_C)}$$

$$Z_{o1}(s) = \frac{Z_{o1}(\text{no feedback})}{1 + (CMFB \text{ loop gain})} \approx \frac{Z_{o1}(\text{no feedback})}{(CMFB \text{ loop gain})}$$

$$= \frac{1}{4 \cdot g_{m6} \cdot (0.5r_{o6} \parallel r_{o13}) \cdot g_{m4}} \cdot \frac{1 + s \cdot 2C_C \cdot (0.5r_{o6} \parallel r_{o13}) \cdot g_{m4}r_{o4}}{1 + s \cdot r_{o4} \cdot (C_L + C_C)}$$

$$A_{vc}(s) \triangleq \frac{v_{o,cm}}{v_{i,cm}} = - \frac{Z_{o1}(s) \parallel (g_{m1}r_{o1} \cdot r_{o3})}{0.5 \cdot r_{s1} + r_{o3}} \approx - \frac{Z_{o1}(s)}{r_{o3}}$$
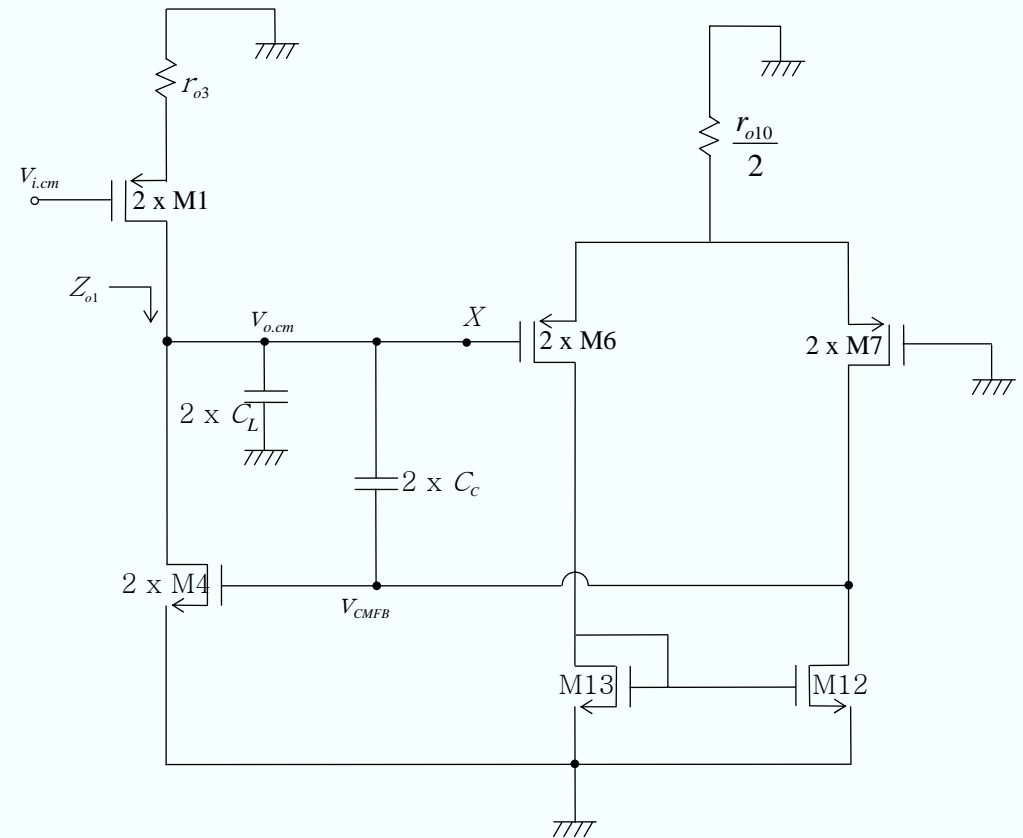
$$= - \frac{1}{4 \cdot g_{m6} \cdot (0.5r_{o6} \parallel r_{o13}) \cdot g_{m4}r_{o3}} \cdot \frac{1 + s \cdot 2C_C \cdot ((0.5r_{o6} \parallel r_{o13}) \cdot g_{m4}r_{o4})}{1 + s \cdot r_{o4} \cdot (C_L + C_C)}$$



$$GBW(CMFB \text{ loop gain}) = \frac{g_{m6}}{C_C}$$



## Linear output voltage range of fully differential OP amp

$$V_o \text{ max : } \min \left[ \left\{ (V_i^+ \text{ or } V_i^-) + |V_{THp}| \right\}, \left\{ V_{DD} - |V_{DSAT3}| - |V_{DSAT1}| \right\} \right]$$


$$V_o \text{ min : } V_{SS} + V_{DSAT4}$$


$$V_o - V_{CMREF} \text{ max : } +\sqrt{2} \cdot |V_{DSAT6}|$$

$$V_o - V_{CMREF} \text{ min : } -\sqrt{2} \cdot |V_{DSAT6}|$$

$$V_o \text{ max : } V_{CMREF} + \sqrt{2} \cdot |V_{DSAT6}|$$

$$V_o \text{ min : } V_{CMREF} - \sqrt{2} \cdot |V_{DSAT6}|$$

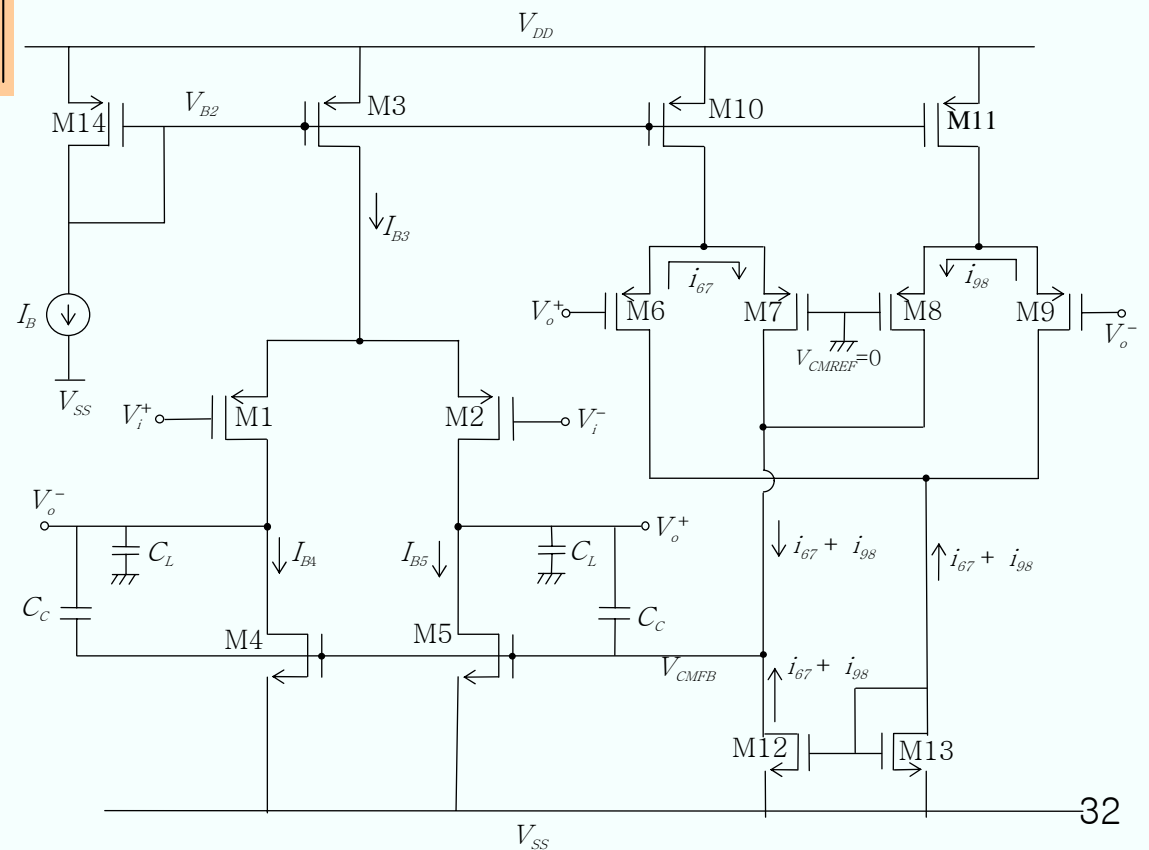

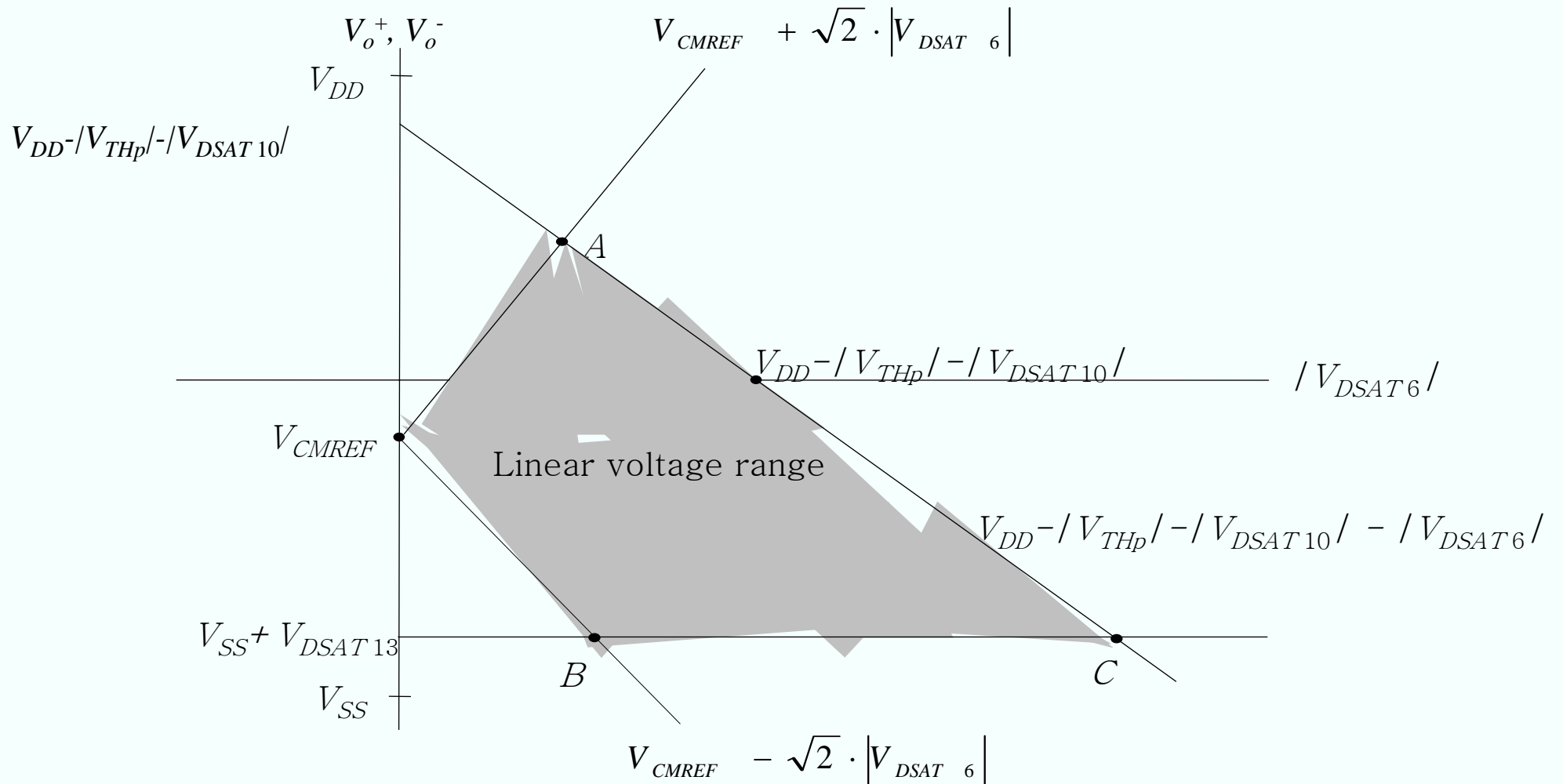

**Fig 10.1.15** Linear voltage range

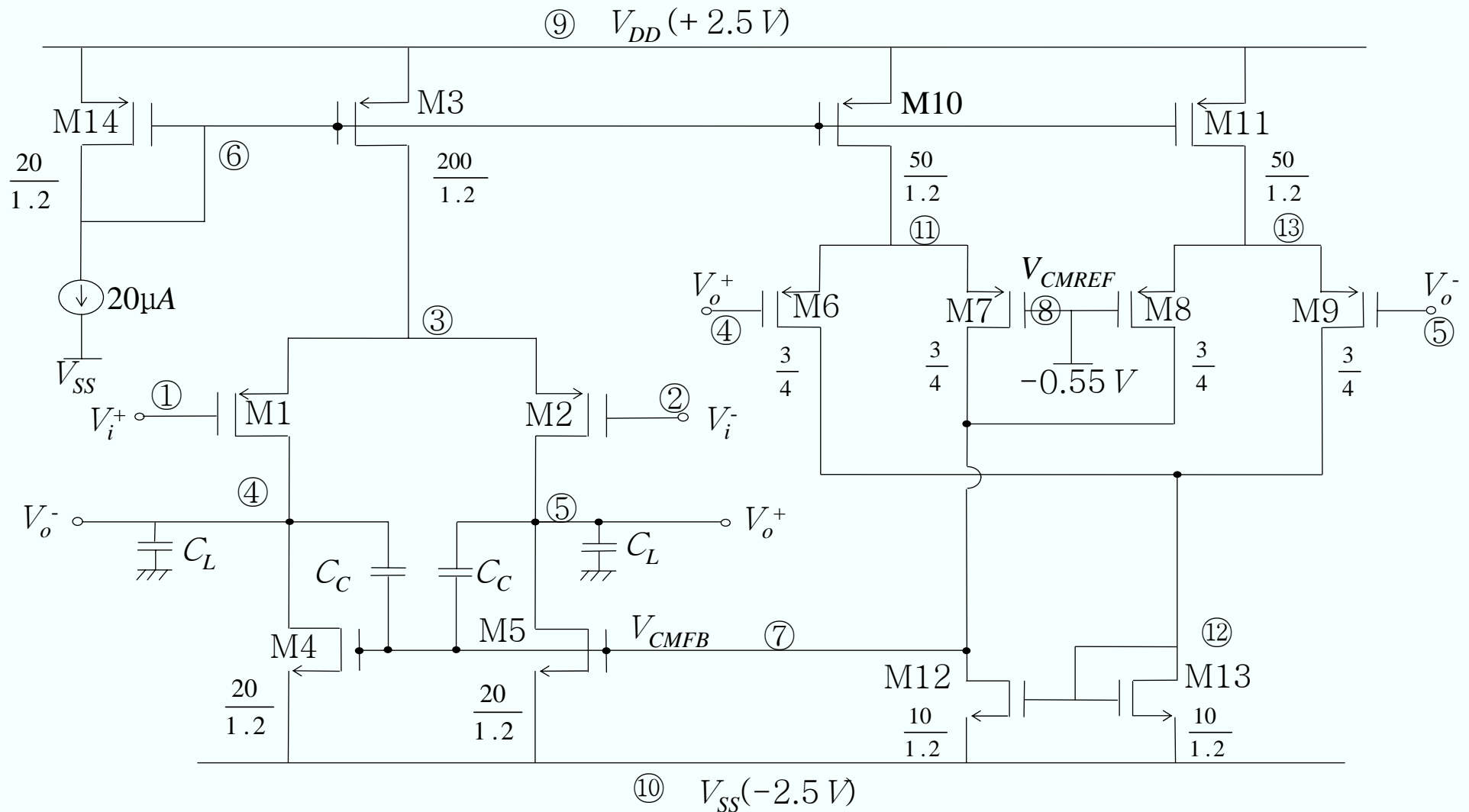


Fig 10.1.17 Example design of Fig. 10.1.11 circuit

Fully differential CMOS amplifier with diff.pair CMFB ckt.

main diff amp

\*

m1 4 1 3 9 pmos w=300u l=1.2u ad=1080p as=1080p pd=307u ps=307u

m2 5 2 3 9 pmos w=300u l=1.2u ad=1080p as=1080p pd=307u ps=307u

m3 3 6 9 9 pmos w=200u l=1.2u as=720p as=720p pd=207u ps=207u

m4 4 7 10 10 nmos w=20u l=1.2u ad=72p as=72p pd=27u ps=27u

m5 5 7 10 10 nmos w=20u l=1.2u ad=72p as=72p pd=27u ps=27u

\*

CMFB ckt.

\*

m6 12 4 11 9 pmos w=3u l=4.0u ad=11p pd=10u as=11p ps=10u

m7 7 8 11 9 pmos w=3u l=4.0u ad=11p pd=10u as=11p ps=10u

m8 7 8 13 9 pmos w=3u l=4.0u ad=11p pd=10u as=11p ps=10u

m9 12 5 13 9 pmos w=3u l=4.0u ad=11p pd=10u as=11p ps=10u

\*

current sources for CMFB

\*

m10 11 6 9 9 pmos w=50u l=1.2u ad=180p pd=57u as=180p pd=57u

m11 13 6 9 9 pmos w=50u l=1.2u ad=180p pd=57u as=180p pd=57u

high gain for CMFB ckt.

\*

m12 7 12 10 10 nmos w=10u l=1.2u ad=36p pd=17u as=36p ps=17u

\*

low gain for CMFB ckt.

\*

\*m12 7 7 10 10 nmos w=10u l=1.2u ad=36p pd=17u as=36p ps=17u

m13 12 12 10 10 nmos w=10u l=1.2u ad=36p pd=17u as=36p ps=17u


\*

bias ckt

```
*
m14 6 6 9 9 pmos w=20u l=1.2u ad=72p as=72p pd=27u ps=27u
idd 6 10 dc 20u
*
* bias voltages
*
vcmref 8 0 dc -0.55
vi1 1 0 dc 0 ac 0.5
vi2 2 0 dc 0 ac -0.5
*
* supply voltages
*
vdd 9 0 dc 2.5
vss 10 0 dc -2.5
*
* load capacitors
*
cl1 4 0 10p
cl2 5 0 10p
*
** compensation capacitor
*
cc1 7 4 1p
cc2 7 5 1p
.op
```


```
*.dc vi1 -2.5 2.5 .01
.dc vi1 -50m 50m 0.1m
.probe v(5) v(40) v(11) v(7) v(12) v(6) v(3) v(13)
.print dc v(4)
.print dc v(5)
.ac dec 10 1 gig
.print ac vdb(5)
.print ac vp(5)
*.tran 0.01 10
*.print tran v(4)
*.print tran v(5)
.model nmos nmos tox=200e-10 uo=500 vto=0.8 gamma=0.0
+ lambda=0.08 cgdo=300p cgso=300p cj=2.75e-4 cjsw=1.9e-10
+ ld=0.2u level=1 af=1 kf=5e-26
.model pmos pmos tox=200e-10 uo=200 vot=-0.8 gamma=0.0
+ lambda=0.1 cgdo=300p cgso=300p cj=2.75e-4 cjsw=1.9e-10
+ ld=0.2u level=1 af=1 kf=1e-26
.end
```

**Fig 10.1.18** SPICE netlist of Fig.10.1.17 circuit

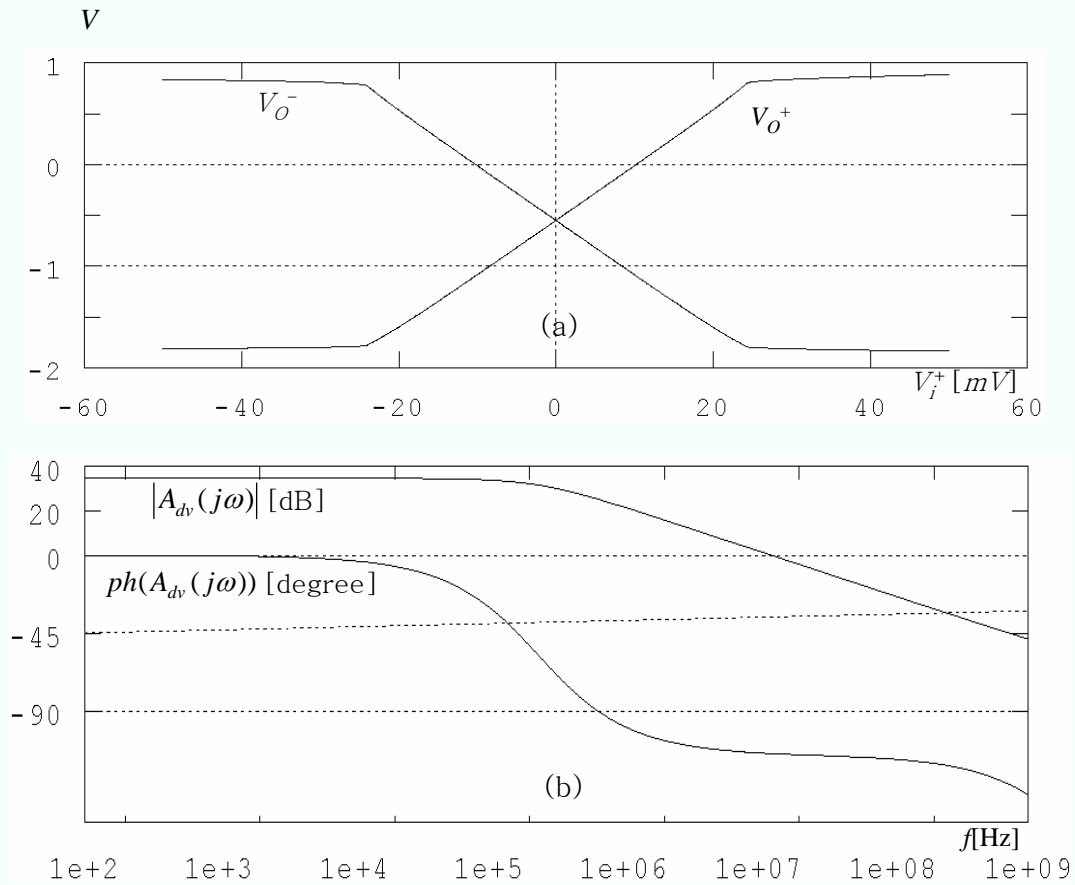

**Fig 10.1.19** SPICE simulation results of Fig. 10.1.17 circuit

(a) DC transfer curve (b) Differential mode voltage gain (c) Common mode voltage gain

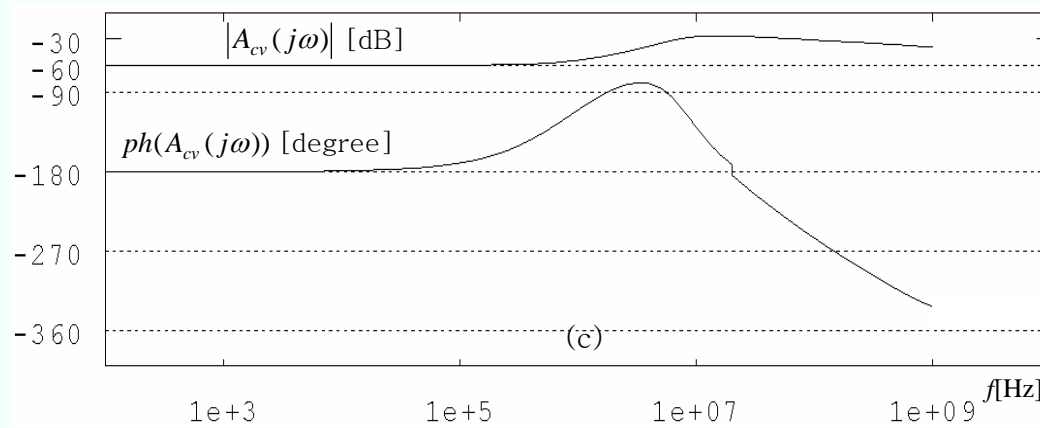

**Fig 10.1.19** SPICE simulation results of Fig. 10.1.17 circuit

(a) DC transfer curve (b) Differential mode voltage gain (c) Common mode voltage gain