

National Technological University

NEEI 6331 / IC 570-CA

Fall 2005

Midterm

Instructions


- You may use one sheet (8.5" x 11") of your own notes. No other materials can be used. Calculator is allowed.
- There are two problems. Answer all of them.
- The total marks for this midterm is 100.
- The time allocated for this midterm is one and a half hours.
- There are a total of 6 pages, including this page.

Name : Solutions

1	
2	
Total	

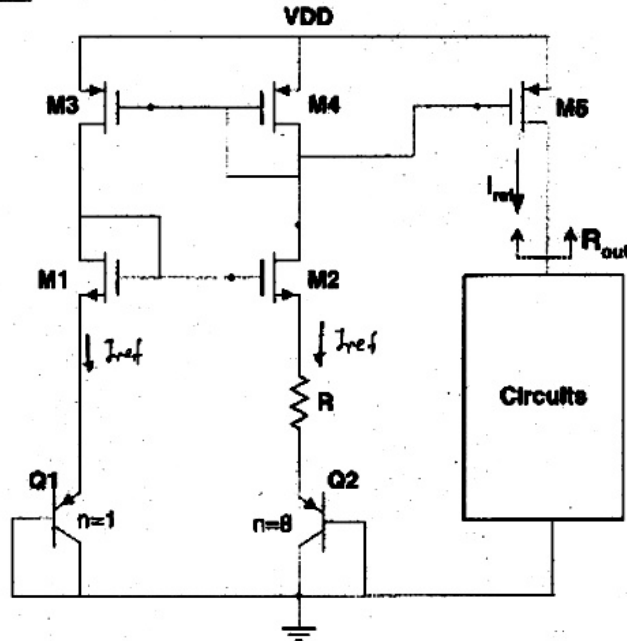Question 1: (35 marks)

The figure below shows a current reference. You may assume all MOS transistors have the same (W/L) and are perfectly matched. Neglect body effect. Take $I_s = 10^{-16}$ for Q1 and thermal voltage, $V_{thermal} = 26mV$.



- (a) Determine the value of R for $I_{ref} = 10\mu A$. You may ignore r_o of the transistors. (15 marks)

$$I_{ref} = I_{D3} = I_{D4} \quad (\text{Current mirror})$$

$$\left. \begin{array}{l} I_{D1} = I_{D3} \quad (\text{KCL}) \\ I_{D2} = I_{D4} \quad (\text{KCL}) \end{array} \right\} \Rightarrow I_{D1} = I_{D2} \Rightarrow V_{GS1} = V_{GS2}$$

We have by KVL,

$$V_{GS1} + V_{GS1} = V_{GS2} + I_{ref} R + V_{GS2}$$

$$\Rightarrow V_T \ln \left(\frac{I_{D1}}{I_{S1}} \right) = I_{ref} R + V_T \ln \left(\frac{I_{D2}}{I_{S2}} \right)$$

$$\Rightarrow R = \frac{V_T \ln \left(\frac{I_{S2}}{I_{S1}} \cdot \frac{I_{D1}}{I_{D2}} \right)}{I_{ref}} \quad \text{ANS: } \boxed{R = 5.4 k\Omega}$$

$$= \frac{26mV}{10\mu A} \ln 8 = 5.4 k\Omega$$

(b) Determine R_{out}
(10 marks)


$$R_{out} = r_{o5}$$

V_{GS} is an a.c ground

ANS: $R_{out} = r_{o5}$

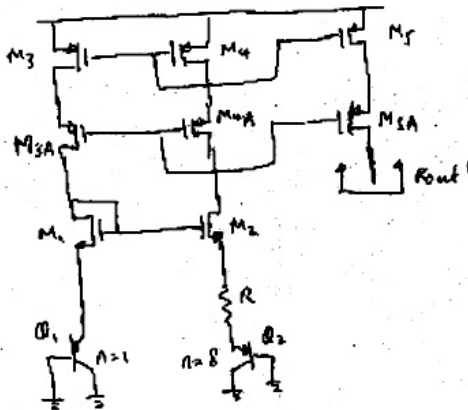(c) Suggest a way to improve R_{out} .
(10 marks)

Use cascode transistors. (M_{3A} , M_{4A} , M_{5A})



$$\text{Now } R_{out}' = r_{o5} + r_{o5A} + g_{m5A} r_{o5} r_{o5A}$$

$$\approx \underbrace{g_{m5A} r_{o5A} r_{o5}}_{\text{Improvement in } R_{out} \text{ by a factor of } g_{m5A} r_{o5A}}$$

Improvement in R_{out} by a factor of $g_{m5A} r_{o5A}$

ANS: Add cascode transistors.


Note: You can also add source degeneration resistor for M_3 , M_4 , M_5

End of Paper

though it is not commonly use for MOS (more common in BJT circuits)

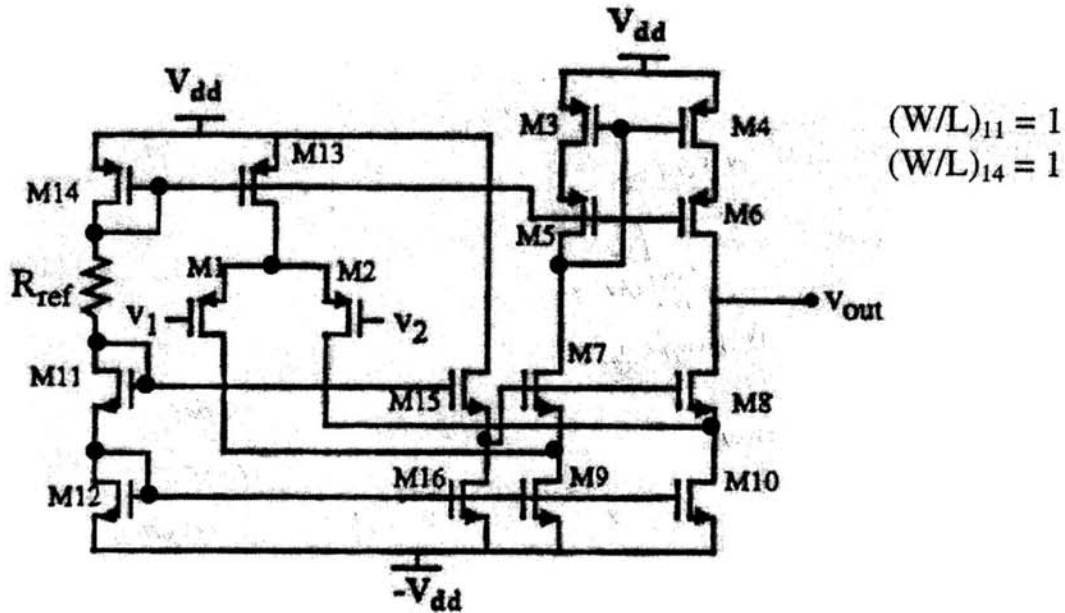Question 2: (65 marks)

The figure below shows a folded cascode amplifier. Assume the bulk of all transistors are connected to their sources.



Choose the values of W/L 's for all the transistors (except for M11 and M14 which are 1), so that the currents in all devices have the same value of I_0 , except for M9, M10 and M13 which are twice that value or $2I_0$. Also choose those sizes so that M3, M4, M9 and M10 are biased at the edge of saturation and all other devices are in saturation. (Assume $\lambda=0$ for all devices).

$(W/L)_1$	Don't care
$(W/L)_2$	Don't care
$(W/L)_3$	4
$(W/L)_4$	4

PMOS:
 ① $(W/L)_1 = (W/L)_2 = \text{any value}$

② $I_3 = 2I_4 \Rightarrow (W/L)_3 = 2 \quad \#$

③ $V_{GS} \quad V_{GS} - V_{GS} = V_1 + \Delta V_5$

$(V_{DD} - \Delta V_3) - (V_{DD} - V_1 - \Delta V_{14}) = V_1 + \Delta V_5$

$\Delta V_{14} = \Delta V_3 + \Delta V_5$

Choose $\Delta V_3 = \Delta V_5 = \Delta V$

$\Delta V_{14} = 2\Delta V$

$\sqrt{\frac{I_0}{(W/L)_4}} = \sqrt{\frac{4I_0}{(W/L)_{3,5}}} \Rightarrow (W/L)_{3,5} = 4 \quad \#$

$I_3 = I_4 \Rightarrow (W/L)_3 = (W/L)_4 \quad 4 \quad \#$

$I_5 = I_6 \Rightarrow (W/L)_5 = (W/L)_6 \quad 4 \quad \#$

(W/L) ₅	4
(W/L) ₆	4
(W/L) ₇	4
(W/L) ₈	4
(W/L) ₉	8
(W/L) ₁₀	8
(W/L) ₁₂	4
(W/L) ₁₃	2
(W/L) ₁₅	4
(W/L) ₁₆	4

NMOS

① $V_{GS12} = V_{GS16} = V_{GS9} = V_{GS10}$

$\Rightarrow \Delta V_{12} = \Delta V_{16} = \Delta V_9 = \Delta V_{10} \quad (*)$

② Also,

$V_{GS12} + V_{GS11} = V_{GS15} + V_{GS8} + \Delta V_{10}$

$\Delta V_{12} + \Delta V_{11} = \Delta V_{15} + \Delta V_8 + \Delta V_{10}$

Using (*), $\Delta V_{11} = \Delta V_{15} + \Delta V_8$

Choose $\Delta V_8 = \Delta V_{15} = \Delta V'$

$\Delta V_{11} = 2\Delta V'$

$\sqrt{\frac{I_0}{(\frac{W}{L})_{11}}} = \sqrt{\frac{4I_0}{(\frac{W}{L})_{8,15}}} \Rightarrow (\frac{W}{L})_{8,15} = 4$

$V_{GS7} = V_{GS8} \Rightarrow (\frac{W}{L})_7 = (\frac{W}{L})_8 = 4$

③ From (*), choose $\Delta V_{12} = \Delta V_{16} = \Delta V_9 = \Delta V_{10} = \Delta V'$

$\therefore (\frac{W}{L})_{12} = (\frac{W}{L})_{16} = 4$

$(\frac{W}{L})_9 = (\frac{W}{L})_{10} = 8 \quad (\because \text{of } 2I_0)$


- (b) Determine the voltage gain of the amplifier. Express your answer in terms parameters (g_{m_i} , r_{o_i} , etc). Ignore body effect. (13 marks)

$$Gain = g_{m1} R_{out}$$

$$R_{out} \approx g_{m6} r_{o6} r_{o4} \parallel g_{m8} r_{o8} (2r_{o2} \parallel r_{i0})$$

#

Note that impedance looking into M_2

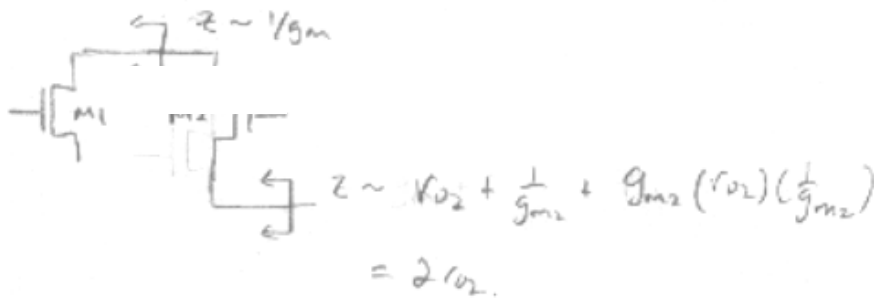

- (c) Determine the output swing of the amplifier. Express your answer in terms of V_{dd} , V_t and V_{dsat_i} of the transistors. (10 marks)

$$-V_{dd} + v_{dsat10} + v_{dsat8} \leq V_{out} \leq V_{dd} - v_{dsat4} - v_{dsat6}$$

End of Paper